



# Discussion 1

9/22/2016



# Outline

- Review
  - ✦the slides last week
- Extension
  - ✦Something new
- Q & A
  - ✦Homework
  - ✦Something that you are interested in



# What we have learned?

- Introduction
- Circuit Analysis: An Overview
  - ✦ Voltage and Current
  - ✦ The Ideal Basic Circuit Element
    - I-V characteristics of circuit elements
  - ✦ Power and Energy
- Circuit Elements
  - ✦ Voltage and Current Sources
  - ✦ Electrical Resistance (Ohm's Law)
- Kirchhoff's Laws (KCL and KVL)
- Simple Resistive Circuits
  - ✦ Resistors in Series and Parallel
  - ✦ Voltage Division and Current Division



# Extension Contents

- Dependent sources (Example: Transistor)
- Ohm's Law: Nonlinearity
- Voltmeter/Ammeter
- Wye-Delta Transformations



# Electric Current Voltage and Power



$$I = \frac{\text{Net Charge crossing surface in time } \Delta t}{\Delta t} = \frac{dq}{dt}$$

$$v = \frac{dw}{dq}$$

$$E = \Delta q \cdot V_{AB}, \quad V_{AB} \equiv V_A - V_B$$

$$p \triangleq \frac{dw}{dt} = \frac{dw}{dq} \cdot \frac{dq}{dt} = v \cdot i$$

# Passive Sign Convention (for Power)

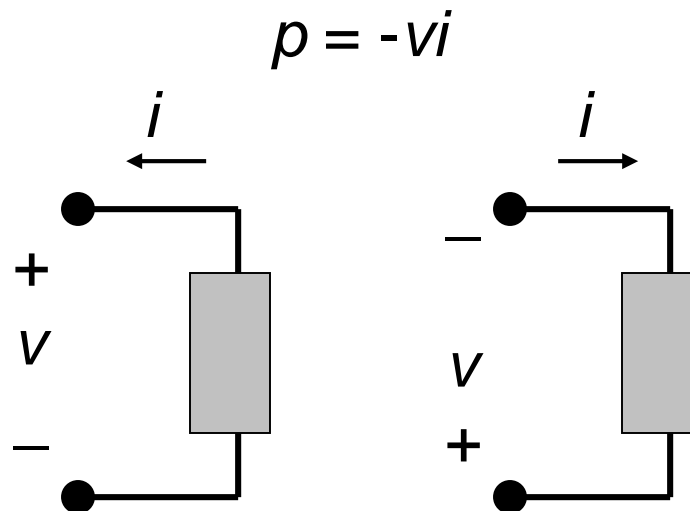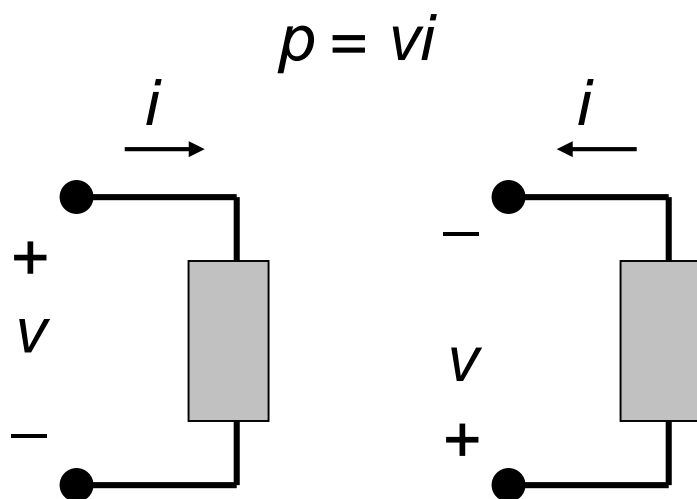


- If  $p > 0$ , power is absorbed by the element.
  - ✦ electrical energy into heat (resistors in toasters), light (light bulbs), or acoustic energy (speakers); by storing energy (charging a battery).
- If  $p < 0$ , power is extracted from the element.
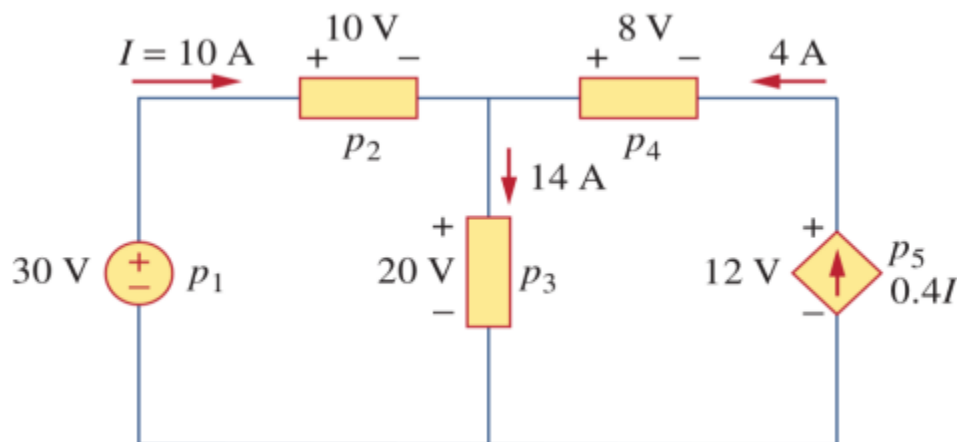
## Example

- Find the power absorbed by each of the elements


$$\begin{aligned}p_1 &= 30 \text{ V} * (-10 \text{ A}) = -300 \text{ W} \\p_2 &= 10 \text{ V} * 10 \text{ A} = 100 \text{ W} \\p_3 &= 20 \text{ V} * 14 \text{ A} = 280 \text{ W} \\p_4 &= 8 \text{ V} * (-4 \text{ A}) = -32 \text{ W} \\p_5 &= 12 \text{ V} * (-0.4 * 10 \text{ A}) = -48 \text{ W}\end{aligned}$$




# Kirchhoff's laws (KVL/KCL)

- KCL and KVL

$$\sum_{n=1}^N i_n = 0$$

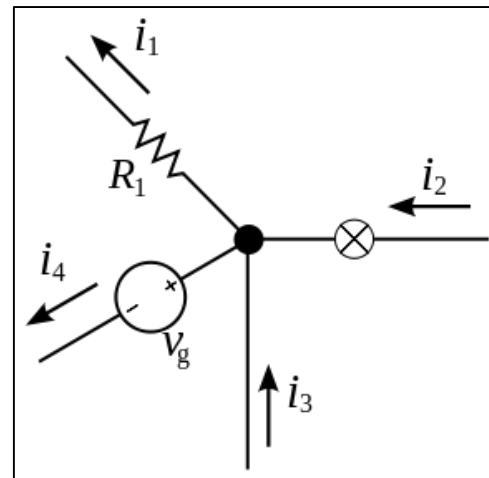

$$\sum_{m=1}^M v_m = 0$$

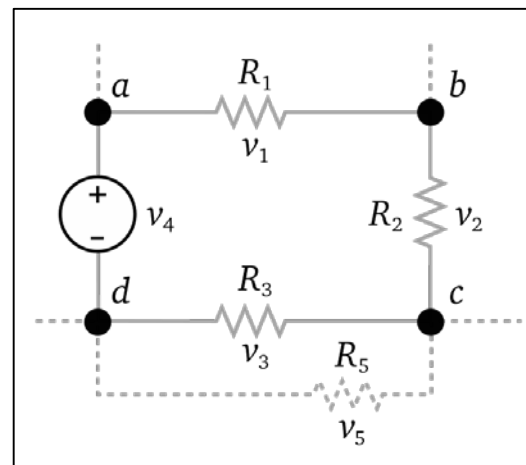





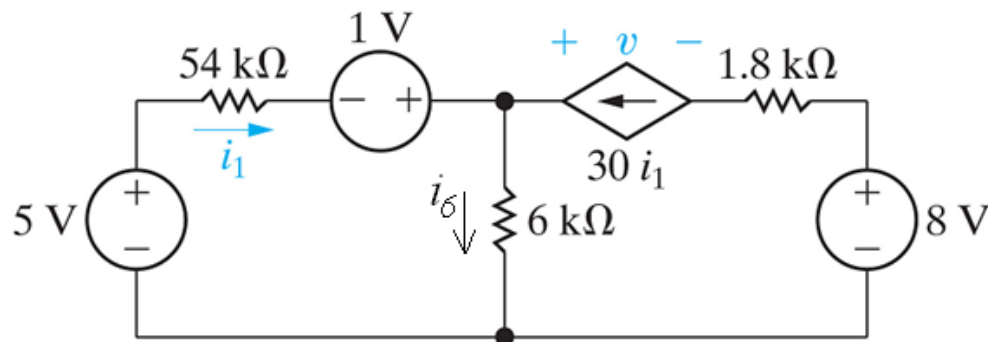
## Example

Find  $i_1$ ,  $v$ , and show that the power balances.



$$\text{KVL left : } -5 + 54,000i_1 - 1 + 6000i_6 = 0$$

$$\text{KCL top : } i_1 + 30i_1 = i_6 = 31i_1$$

$$\Rightarrow -5 + 54,000i_1 - 1 + 6000(31i_1) = 0$$

$$\Rightarrow [54,000 + (6000)(31)]i_1 = 6 \quad \therefore i_1 = 25\mu\text{A}$$


$$\text{KVL right : } -v + (6000)(31i_1) - 8 + 1800(30i_1) = 0$$

$$\Rightarrow v = (6000)(31)(25\mu) - 8 + (1800)(30)(25\mu) = -2 \text{ V}$$


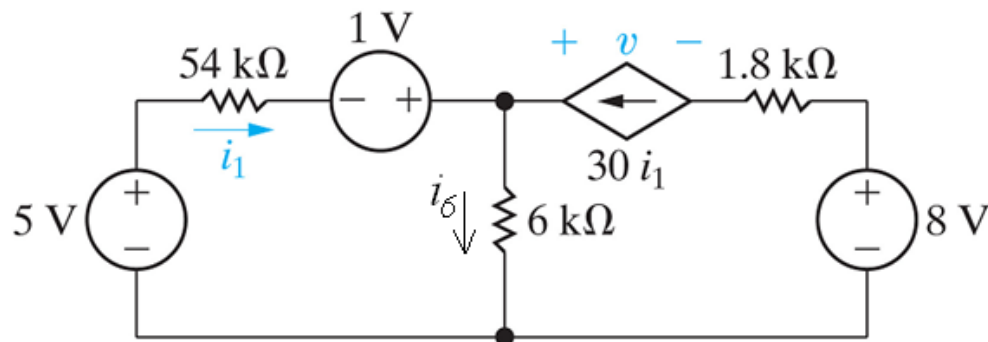
## Example

Find  $i_1$ ,  $v$ , and show that the power balances.



$$p_{5V} = -(5)(25\mu) = -120\mu\text{W}$$

$$p_{d.s.} = (2)(750\mu) = 1500\mu\text{W}$$

$$p_{54k} = (55,000)(25\mu)^2 = 33.75\mu\text{W}$$

$$p_{1.8k} = (1800)(750\mu)^2 = 1012.5\mu\text{W}$$

$$p_{1V} = -(1)(25\mu) = -25\mu\text{W}$$

$$p_{8V} = -(8)(750\mu) = -6000\mu\text{W}$$

$$p_{6k} = (6000)(775\mu)^2 = 3603.75\mu\text{W}$$

The sum of the power is

$$-120 + 1500 + 33.75 + 1012.5 - 25 - 6000 + 3603.75 = 0!$$



## Parallel/Series Resistors and Current/Voltage division

- Series Resistors and Voltage division

$$v = v_1 + v_2 = i(R_1 + R_2)$$

$$R_{eq} = R_1 + R_2$$

$$v_1 = \frac{R_1}{R_1 + R_2} v \quad v_2 = \frac{R_2}{R_1 + R_2} v$$

- Parallel Resistors and Current division

$$v = i_1 R_1 = i_2 R_2$$


$$R_{eq} = \frac{R_1 R_2}{R_1 + R_2}$$

$$i_1 = \frac{i R_2}{R_1 + R_2} \quad i_2 = \frac{i R_1}{R_1 + R_2}$$



## Example

Find  $R$

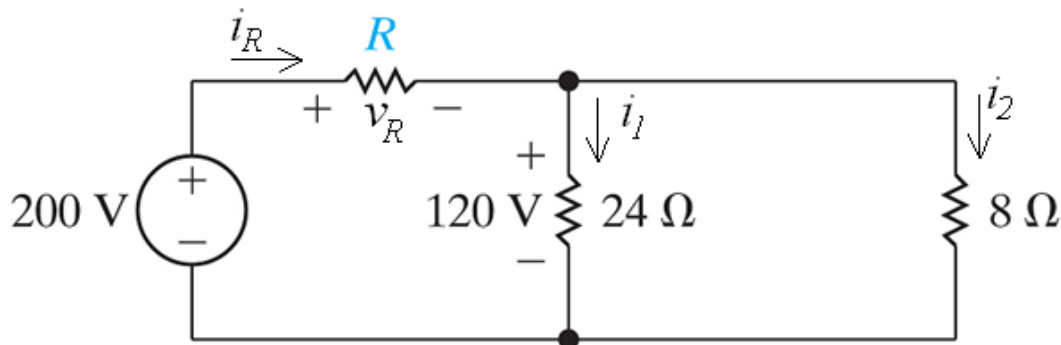

To find  $R$  we need to find the voltage drop across  $R$  and the current through  $R$ :

$$\text{KVL left : } -200 + v_R + 120 = 0 \quad \Rightarrow \quad v_R = 200 - 120 = 80 \text{ V}$$

$$\text{KCL top : } i_R = i_1 + i_2$$

$$\text{KVL right : } -120 + v_2 = 0 \quad \Rightarrow \quad v_2 = 120 \text{ V}$$

$$\therefore i_R = \frac{120 \text{ V}}{24\Omega} + \frac{120 \text{ V}}{8\Omega} = 5 + 15 = 20 \text{ A}$$


$$\Rightarrow R = \frac{v_R}{i_R} = \frac{80}{20} = 4\Omega$$

---

Or we can use equivalent resistance of series-connected and parallel-connected resistors

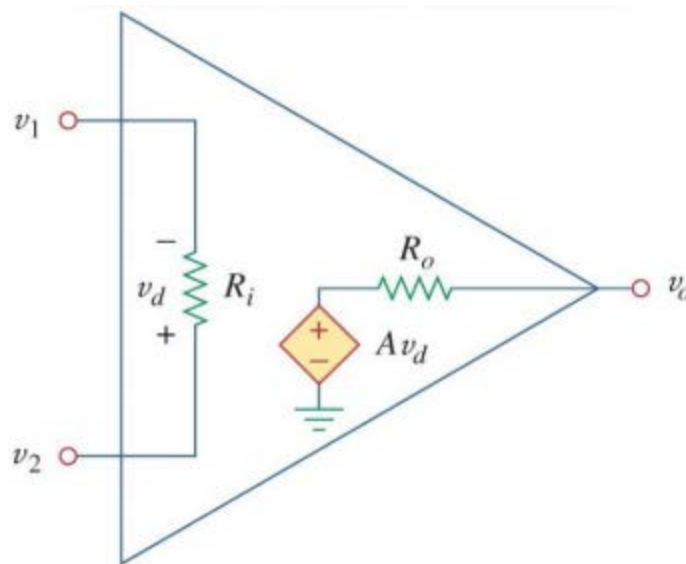
## Extension 1: Dependent Sources

- Dependent sources are good models for some common circuit elements:
  - ✦ Transistors: In certain modes of operation, transistors take either a voltage or current input to one terminal and cause a current that is somehow proportional to the input to appear at two other terminals.
  - ✦ Operational Amplifiers: Not covered yet, but the basic concept is they take an input voltage and generate an output voltage that is proportional to that.




# Transistors

- There are two basic types of transistors: *bipolar junction transistors* (BJTs) and *field-effect transistors* (FETs).
- There are two types of BJTs: *npn* and *pnp*, with their circuit symbols as shown in Fig. 3.38. Each type has three terminals, designated as emitter (E), base (B), and collector (C).

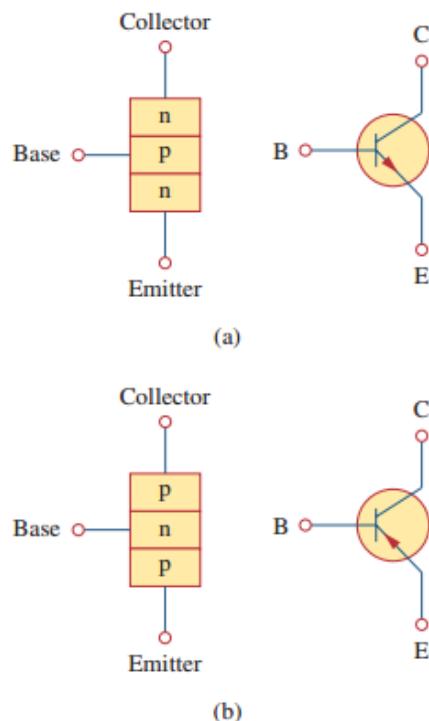

**Figure 3.38**

Two types of BJTs and their circuit symbols: (a) *npn*, (b) *pnp*.

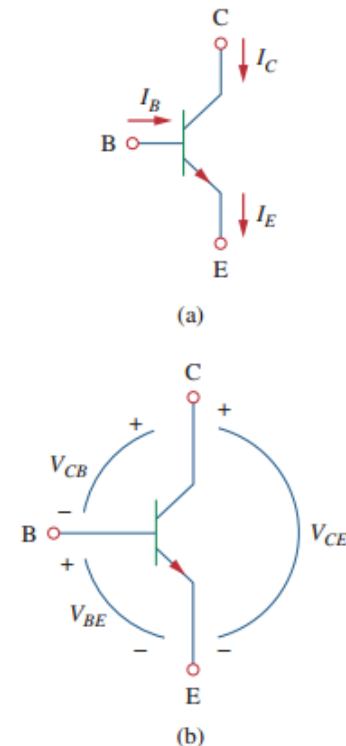


**Figure 3.39**

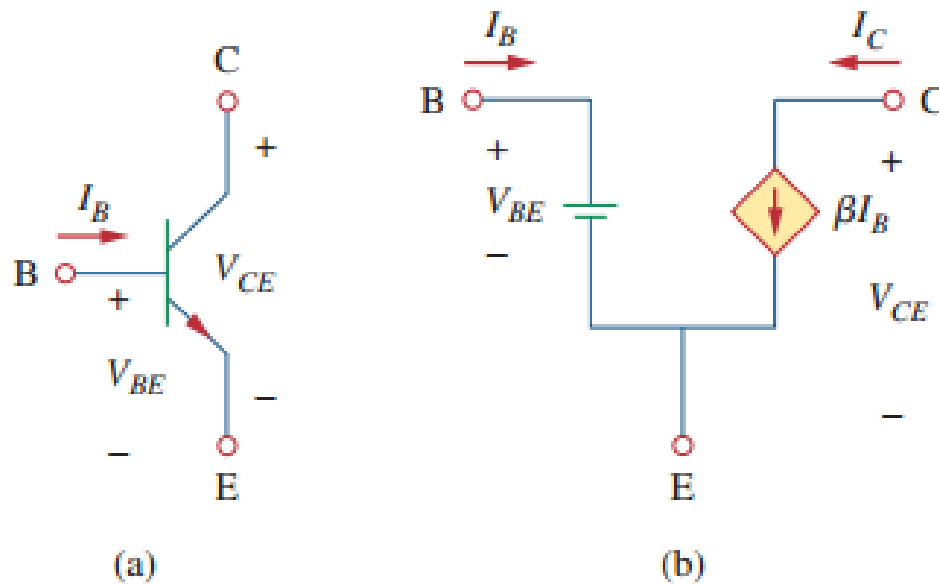The terminal variables of an *npn* transistor: (a) currents, (b) voltages.

## What we finally get

- The equivalent model of a npn transistor.






**Figure 3.40**

(a) An npn transistor, (b) its dc equivalent model.
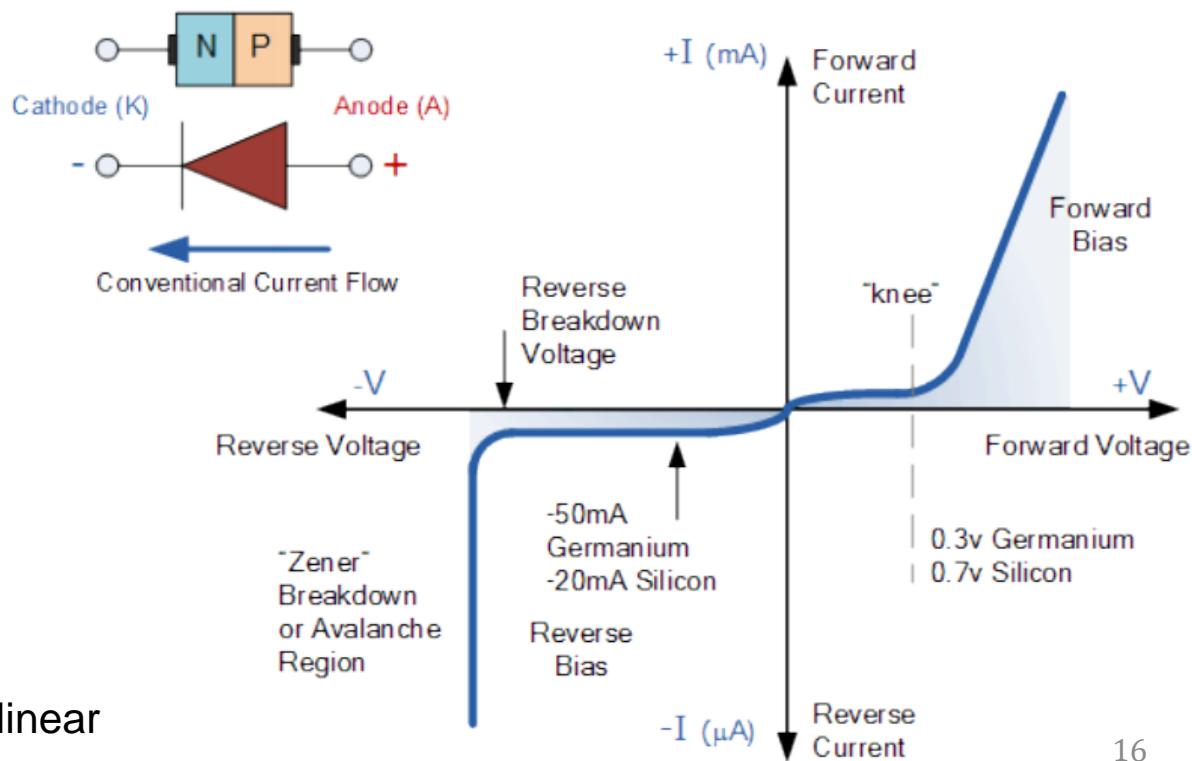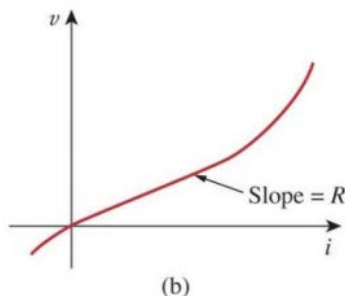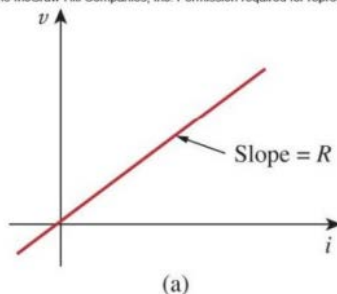
## Extension 2: Linearity vs Nonlinearity

- Not all resistors obey Ohm's Law
  - Resistors that do are called linear resistors because their current voltage relationship is always linearly proportional.
  - Diodes and light bulbs are examples of non-linear elements

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display



I-V characteristics linear and nonlinear



- In the circuit world, we have i-v graphs. Therefore, we classify a circuit as linear or non-linear by examining its i-v graph. If the i-v graph of the circuit is a straight line, then the circuit is classified as linear. Note that the definition can be extended even to circuit elements. For instance, a resistor's i-v graph is a straight line, hence it is a linear device.

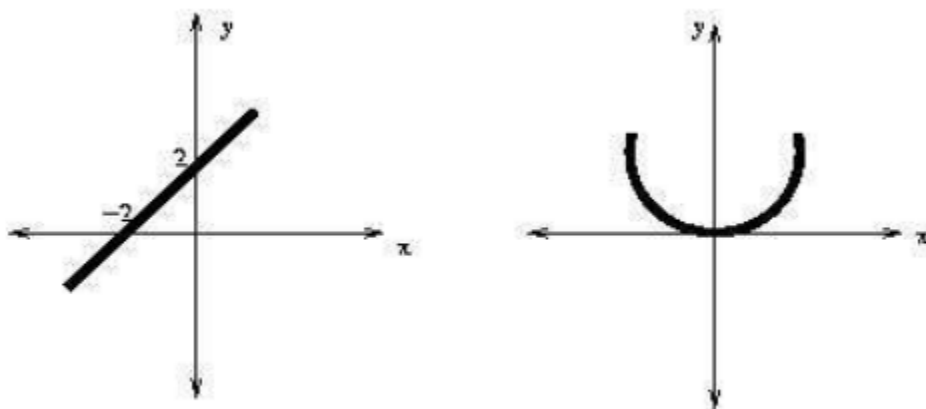


Figure 1. A linear versus nonlinear function

# Quick glance at negative resistance converter

- According to some analyze and calculation, we obtain following equations

$$i = \frac{-R_a}{(R_b R_f)} \times v$$


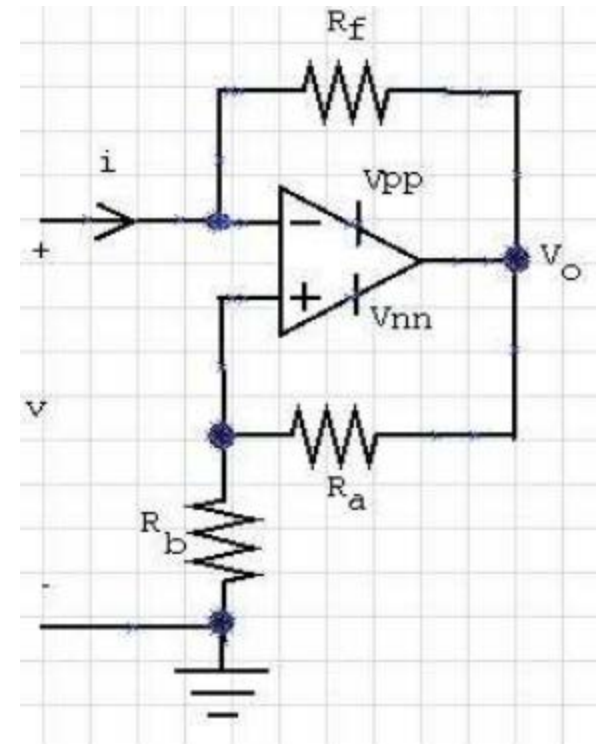
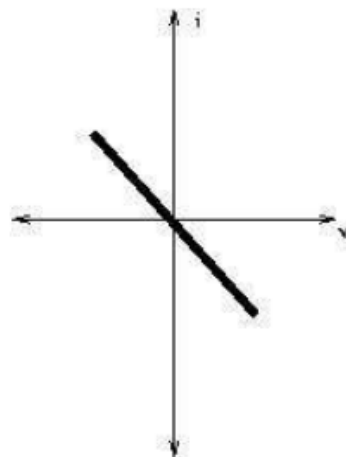


Figure 5. The i-v graph of the circuit when the op-amp is in the linear region.
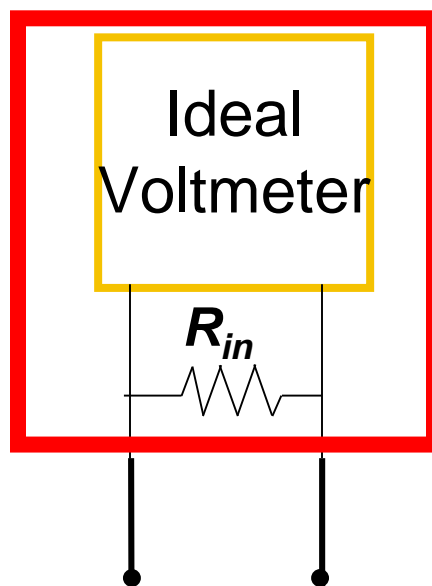
## Extension 3: Measuring Voltage (Voltmeter)

To measure the voltage drop across an element in a real circuit, insert a voltmeter (digital multimeter in voltage mode) **in parallel** with the element.


Voltmeters are characterized by their “voltmeter input resistance” ( $R_{in}$ ). Ideally, this should be very high (typical value 10 M $\Omega$ )






## Effect of Voltmeter

### undisturbed circuit

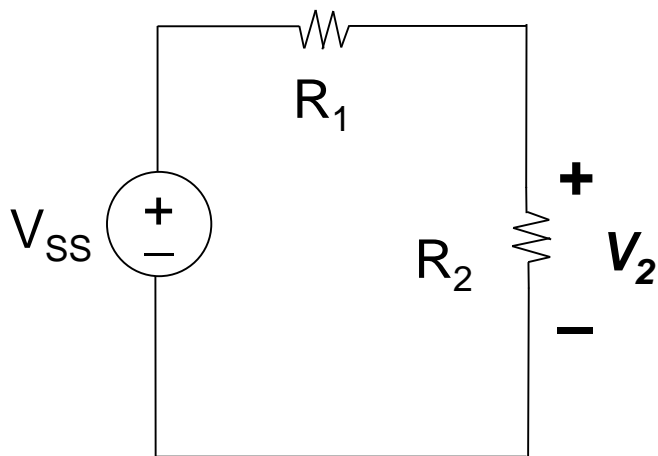

$$V_2 = V_{SS} \left[ \frac{R_2}{R_1 + R_2} \right]$$

### circuit with voltmeter inserted

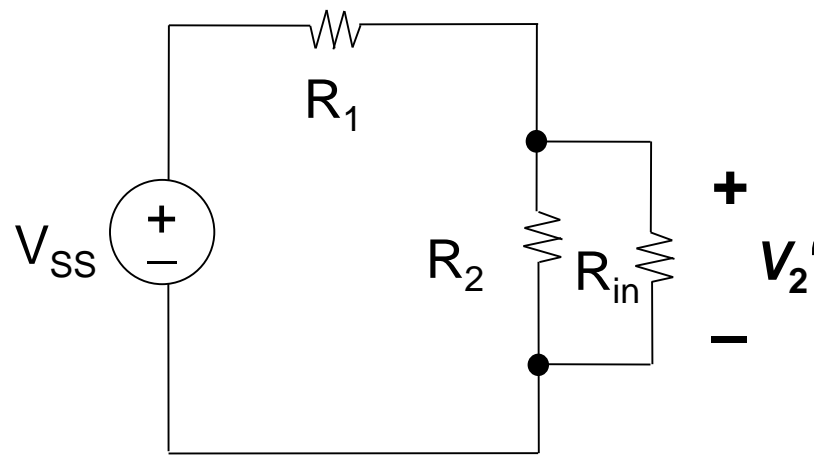

$$V_2' = V_{SS} \left[ \frac{R_2 \parallel R_{in}}{R_2 \parallel R_{in} + R_1} \right]$$


Example:  $V_{SS} = 10V, R_2 = 100K, R_1 = 900K \Rightarrow V_2 = 1V$

$R_{in} = 10M, V_2' = ?$
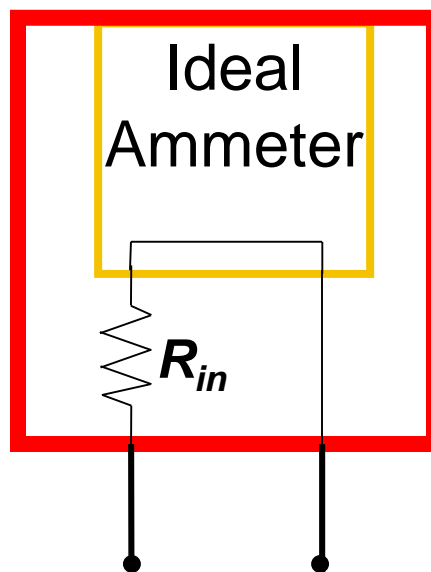
## Extention 3: Measuring Current (Ammeter)

To measure the current flowing through an element in a real circuit, insert an ammeter (digital multimeter in current mode) **in series** with the element.


Ammeters are characterized by their “ammeter input resistance” ( $R_{in}$ ). Ideally, this should be very low (typical value  $1\Omega$ ).



# Effect of Ammeter


Measurement error due to non-zero input resistance:

undisturbed circuit

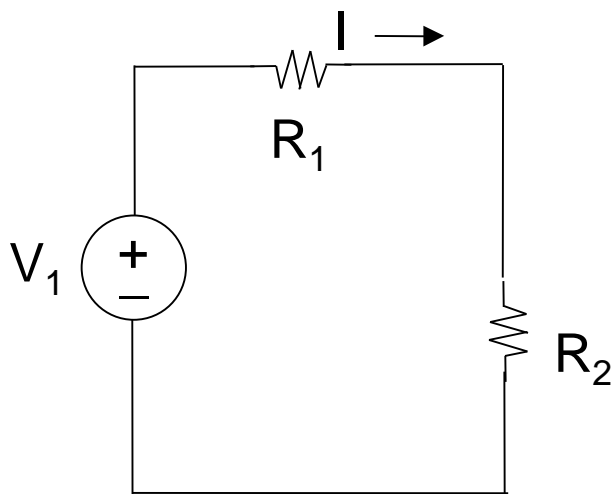

$$I = \frac{V_1}{R_1 + R_2}$$

circuit with ammeter inserted

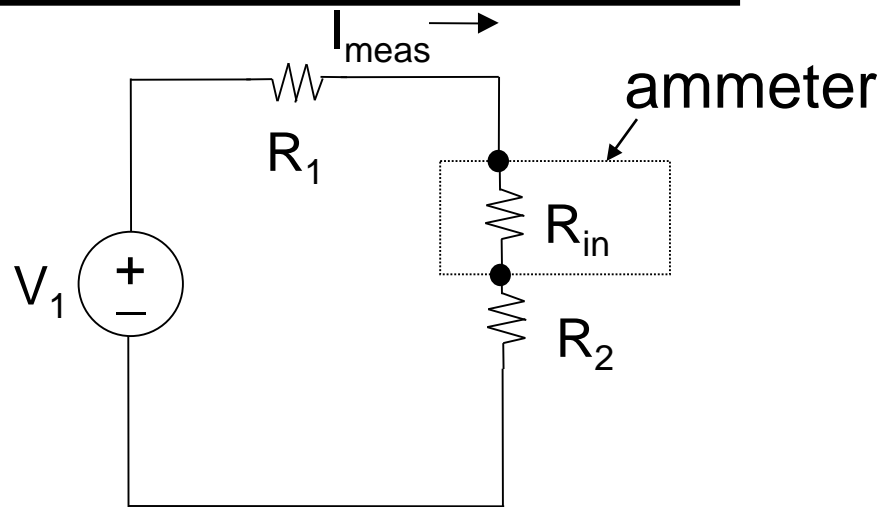

$$I_{\text{meas}} = \frac{V_1}{R_1 + R_2 + R_{\text{in}}}$$

Example:  $V_1 = 1 \text{ V}$ ,  $R_1 = R_2 = 500 \Omega$ ,  $R_{\text{in}} = 1 \Omega$


$$I = \frac{1\text{V}}{500\Omega + 500\Omega} = 1\text{mA}, \quad I_{\text{meas}} = ?$$


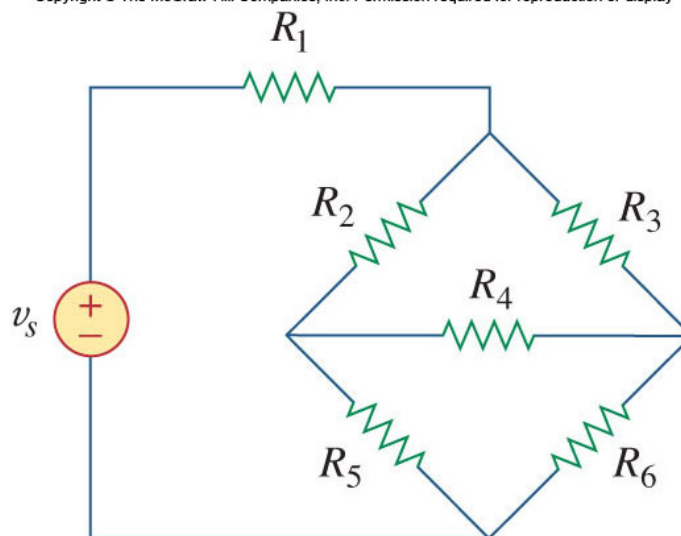
## Extention 4: Wye-Delta Transformations

- There are cases where resistors are neither parallel nor series.
- Consider the bridge circuit shown here. This circuit can be simplified to a three-terminal equivalent

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display





## Delta to Wye

- The conversion formula for a delta to wye transformation are:

$$R_1 = \frac{R_b R_c}{R_a + R_b + R_c}$$


$$R_2 = \frac{R_c R_a}{R_a + R_b + R_c}$$

$$R_3 = \frac{R_a R_b}{R_a + R_b + R_c}$$

$$R_{ab}(Y) = R_{ab}(\Delta) \Rightarrow R_1 + R_2 = \frac{R_c(R_a + R_b)}{R_a + R_b + R_c}$$

$$R_{ac}(Y) = R_{ac}(\Delta) \Rightarrow R_1 + R_3 = \frac{R_b(R_a + R_c)}{R_a + R_b + R_c}$$
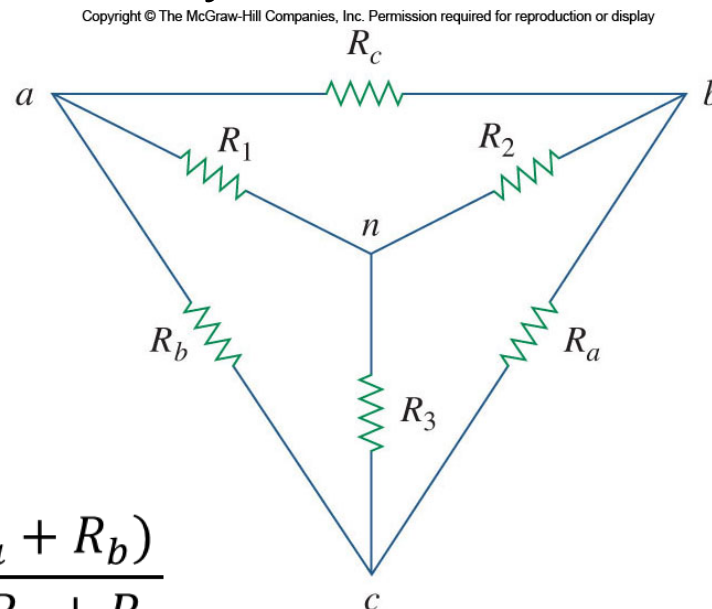
$$R_{bc}(Y) = R_{bc}(\Delta) \Rightarrow R_2 + R_3 = \frac{R_a(R_b + R_c)}{R_a + R_b + R_c}$$








## Wye to Delta

- The conversion formula for a wye to delta transformation are:

$$R_a = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_1}$$

$$R_b = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_2}$$
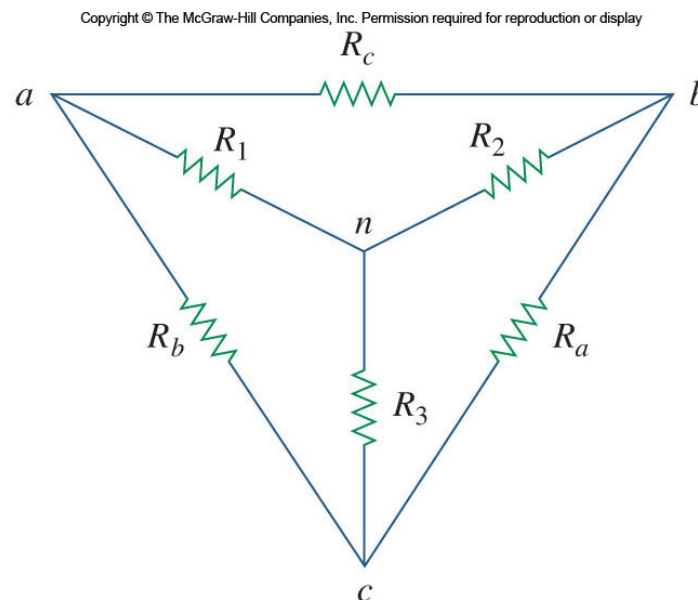
$$R_c = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_3}$$



$$R_1 R_2 + R_1 R_3 + R_2 R_3 = \frac{R_a R_b R_c}{R_a + R_b + R_c}$$




# Example


- Find the equivalent resistance

Wye  $\rightarrow$  Delta

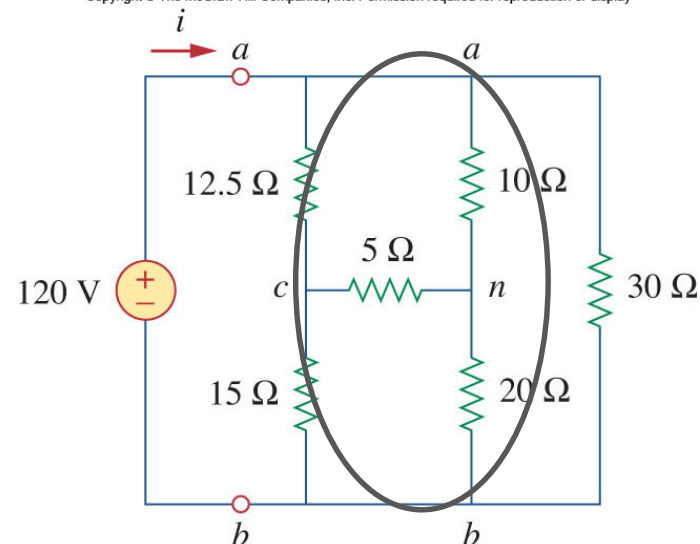
Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display



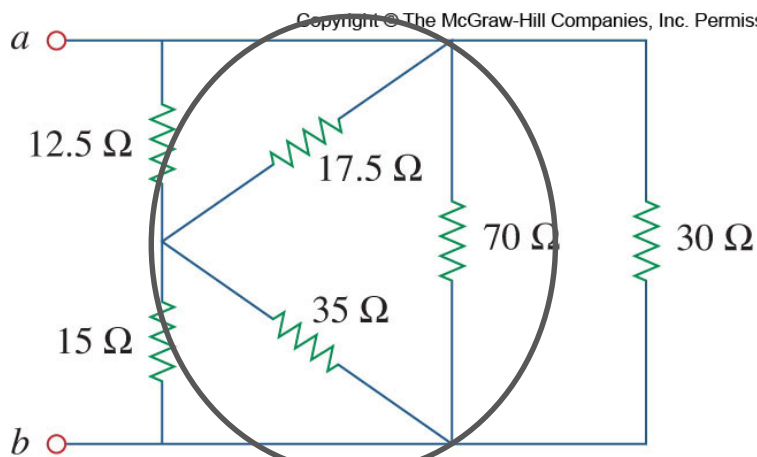Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display



(a)

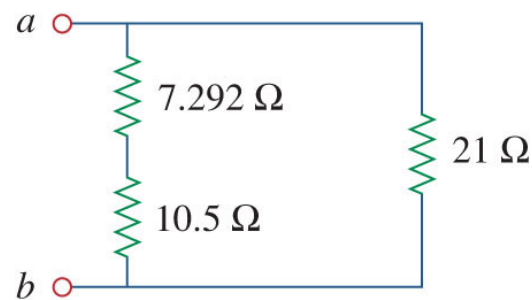

(b)



## Q & A

- Any question will be welcomed