



Lecture 11

- Magnetically Coupled Circuits





Outline

- Mutual inductance
- Transformers



Review: Self Inductance

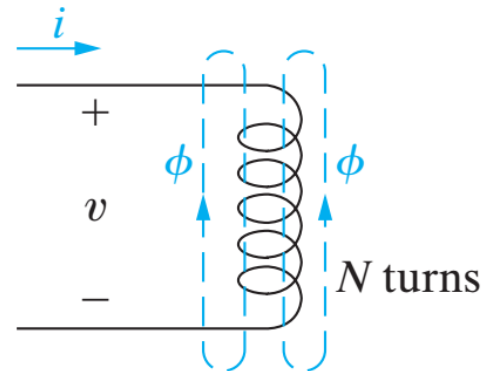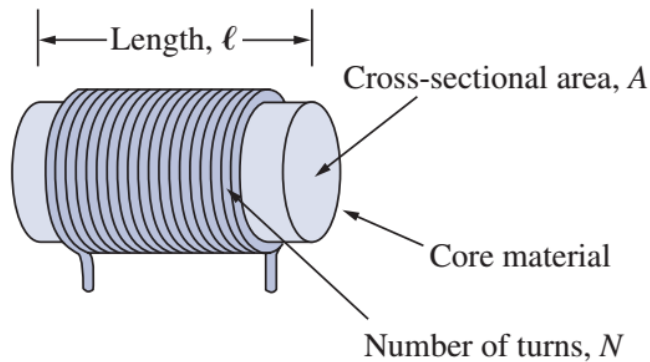- Self inductance:
reaction of the inductor to the change in current ***through itself***.




$$v = L \frac{di}{dt}$$



Mutual Inductance

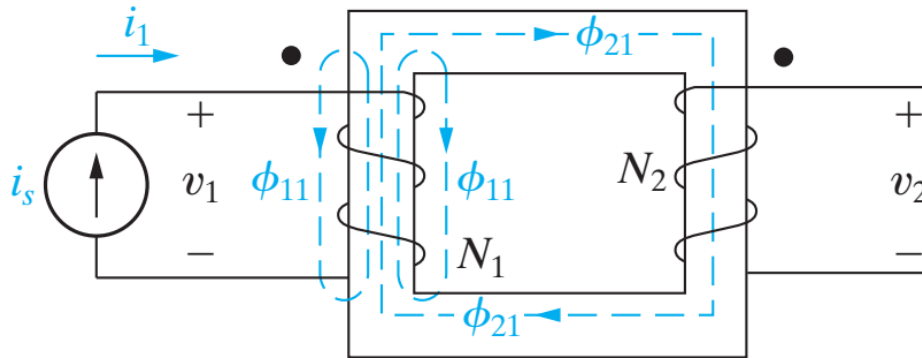
- Mutual inductance: reaction of one inductor to the change in current ***through another inductor.***



$$\begin{aligned} v_2 &= \frac{d(N_2\phi_{21})}{dt} = N_2 \frac{d}{dt}(\mathcal{P}_{21}N_1i_1) \\ &= N_2N_1\mathcal{P}_{21} \frac{di_1}{dt} \\ &= \boxed{M_{21} \frac{di_1}{dt}} \end{aligned}$$



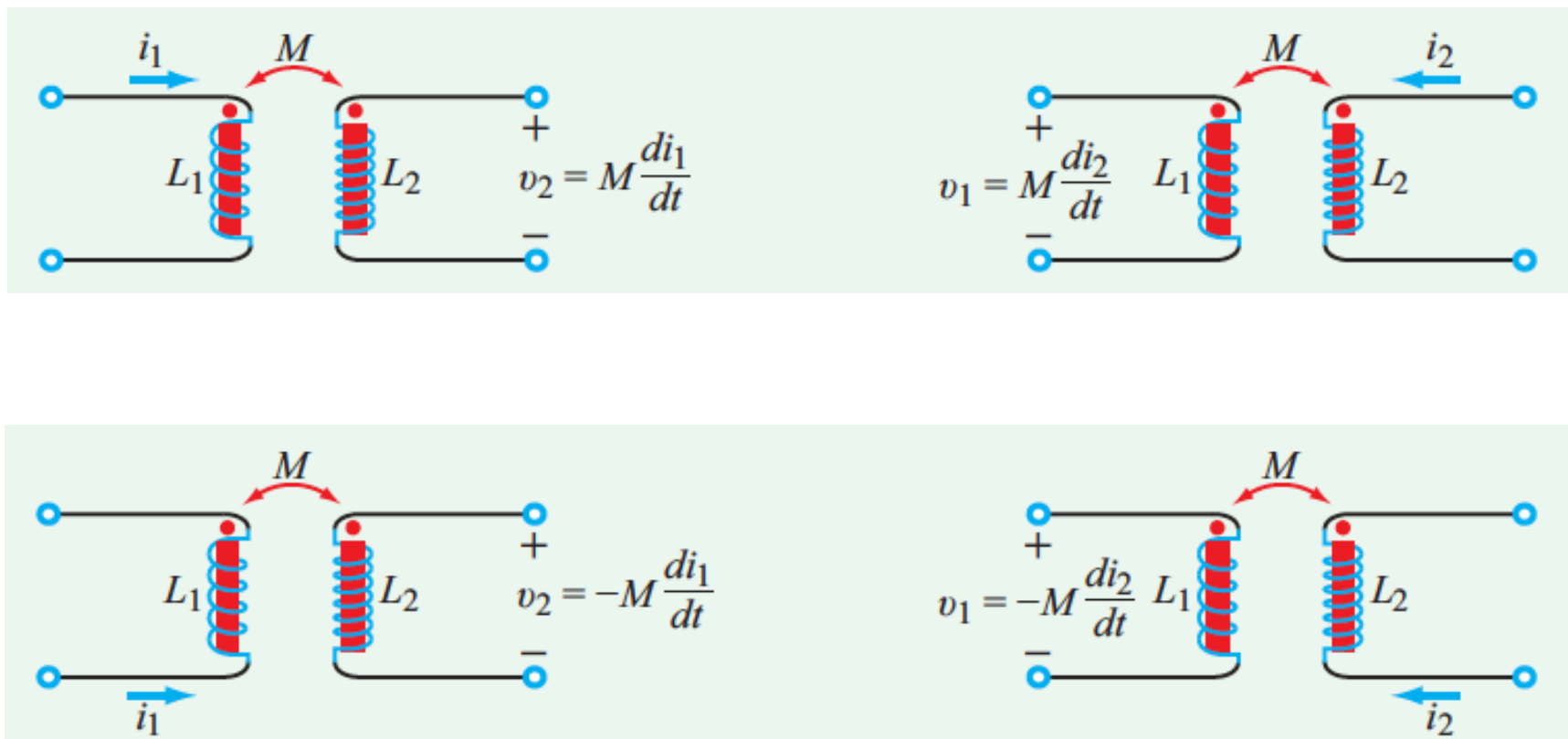Dot Convention: Defines Directions of Windings



If a current enters the dotted terminal of one coil, the reference polarity of mutual voltage in the 2nd coil is the positive at the dotted terminal of the 2nd coil.






Magnetically Coupled Circuits

- L_1, L_2 : self-inductances
- M : mutual inductance
- Dots: indicating polarity of mutually induced voltages.

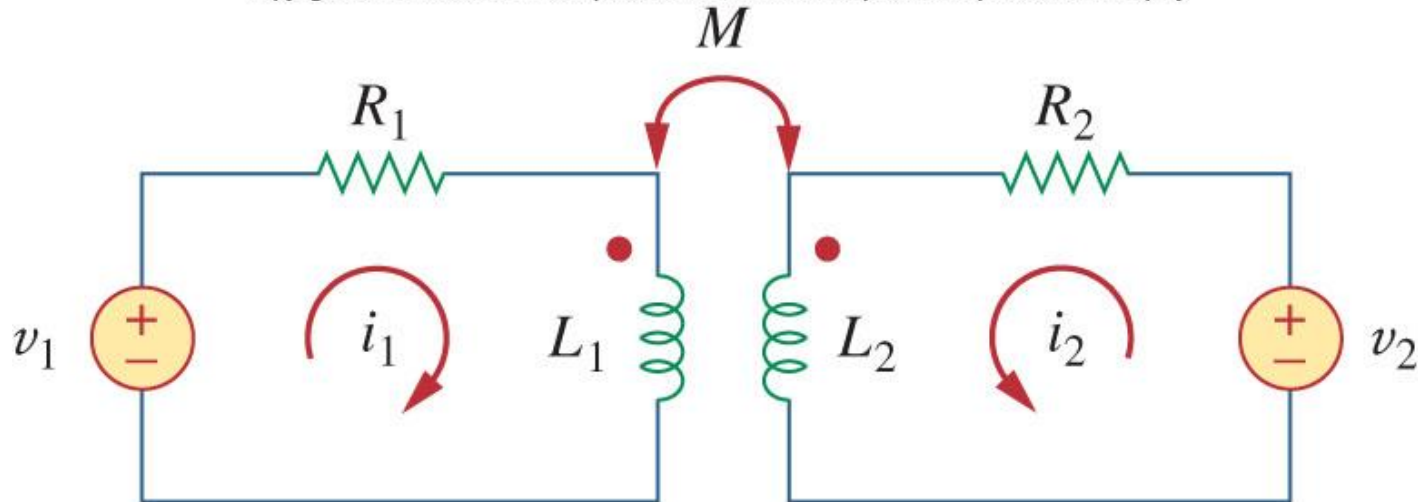
Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display





Analysis

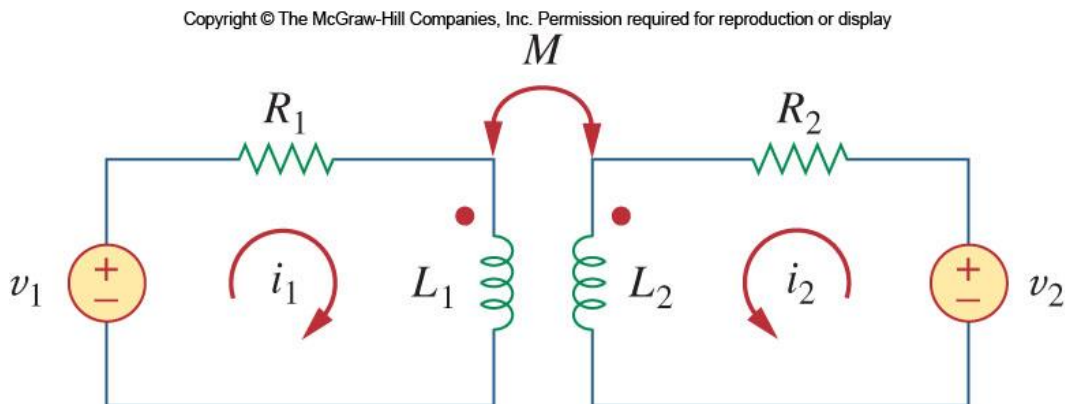
- Find i_1 and i_2 .
 - In time domain
 - In phasor domain







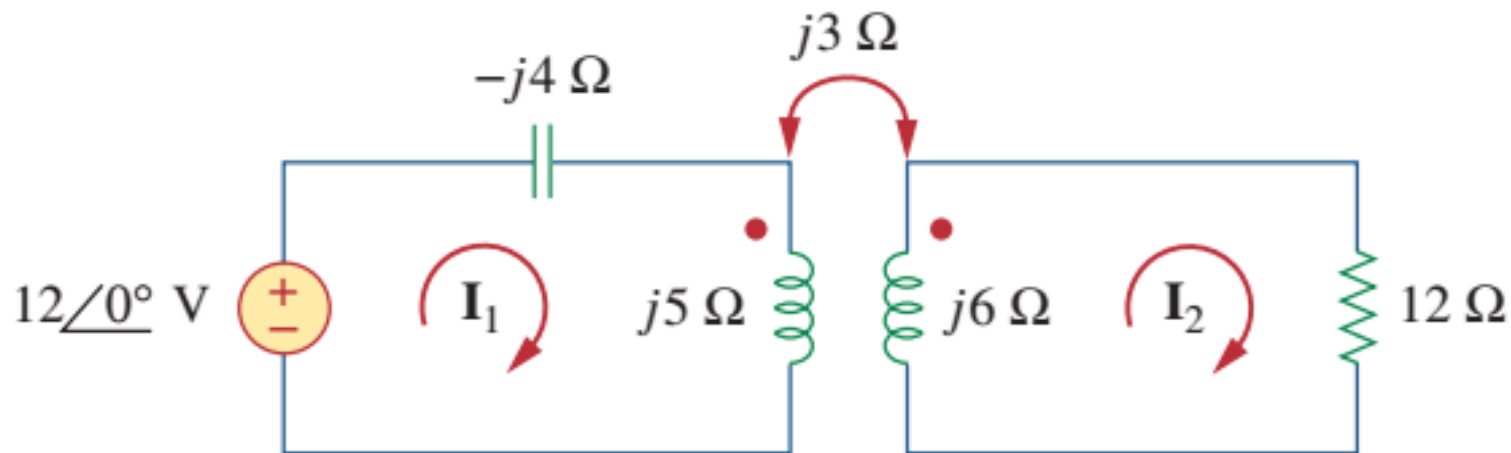- Calculate the phasor currents \mathbf{I}_1 , and \mathbf{I}_2
- Calculate the phasor voltages \mathbf{V}_1 , and \mathbf{V}_2 across the inductors








Transformers


- A transformer is a magnetic device that takes advantage of mutual inductance.

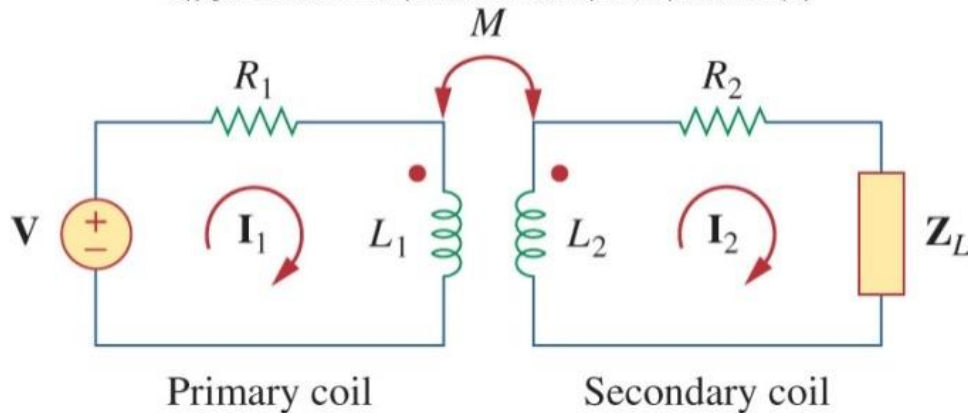Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display



Transformer Impedance

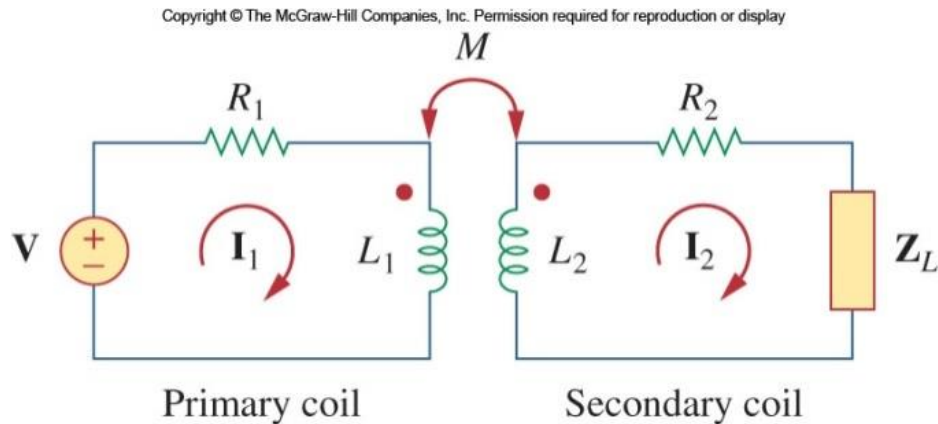- An important parameter to know for a transformer is how the input impedance Z_{in} is seen from the source.



$$Z_{in} = \frac{V}{I_1} = R_1 + j\omega L_1 + \frac{\omega^2 M^2}{R_2 + j\omega L_2 + Z_L}$$


Reflected impedance from
secondary to primary

Energy in a Coupled Circuit


- The energy stored in an inductor is
- For coupled inductors, the total energy stored is

$$w = \frac{1}{2} L_1 i_1^2 + \frac{1}{2} L_2 i_2^2 \pm M i_1 i_2$$

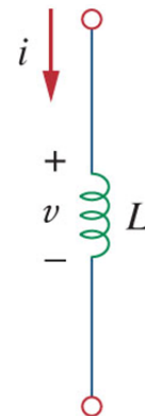- The positive sign is selected when the currents both enter or leave the dotted terminals.



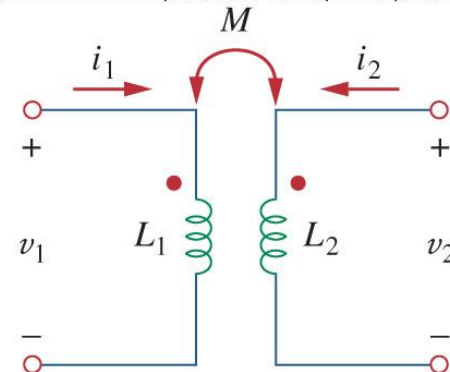Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display





Coupling Coefficient k

- The system cannot have negative energy

$$\frac{1}{2}L_1 i_1^2 + \frac{1}{2}L_2 i_2^2 - M i_1 i_2 \geq 0 \quad \Rightarrow \quad M \leq \sqrt{L_1 L_2}$$

- Define a parameter describes how closely M approaches upper limit.


$$k = \frac{M}{\sqrt{L_1 L_2}}$$

- Coupling coefficient, $0 \leq k \leq 1$.


Ideal Transformers

- The ideal transformer has:
 - Coils with very large reactance
($L_1, L_2, M \rightarrow \infty$)
 - Coupling coefficient $k=1$.
 - Primary and secondary coils are lossless, $R_1 = R_2 = 0$.

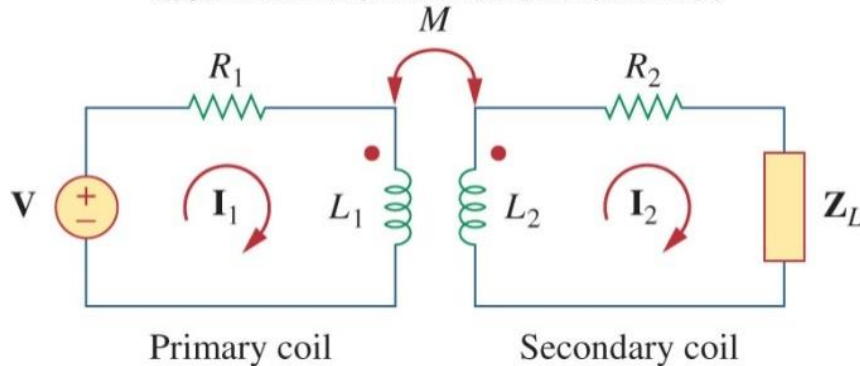Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display



Ideal Transformers

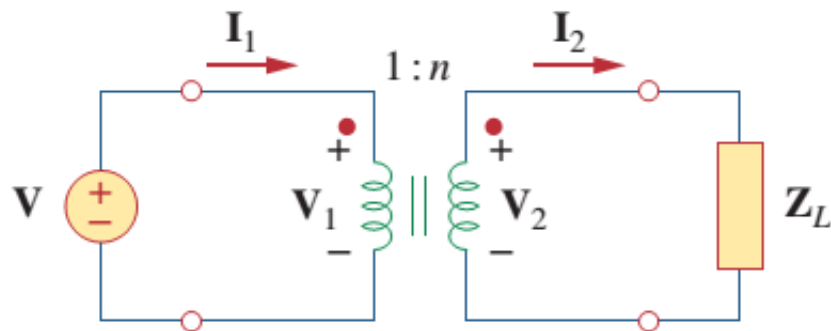


- The voltage is related as:

$$\frac{V_2}{V_1} = \frac{N_2}{N_1} = n$$


- The current is related as:



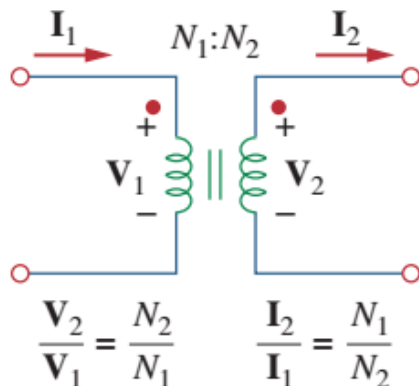
1. If V_1 and V_2 are *both* positive or both negative at the dotted terminals, use $+n$ in Eq. (13.52). Otherwise, use $-n$.
2. If I_1 and I_2 *both* enter into or both leave the dotted terminals, use $-n$ in Eq. (13.55). Otherwise, use $+n$.




(a)

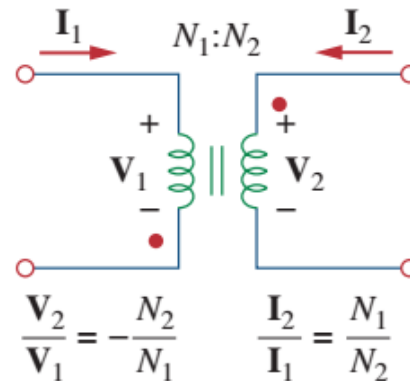

(c)

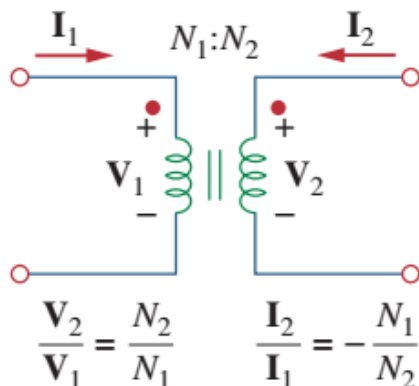

(b)

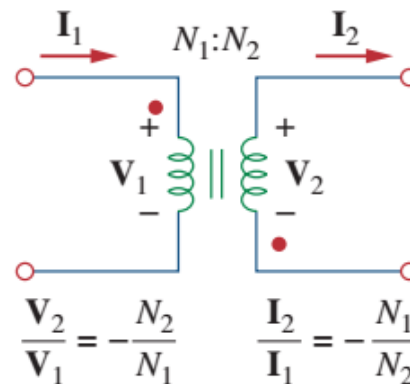


(d)




Practice

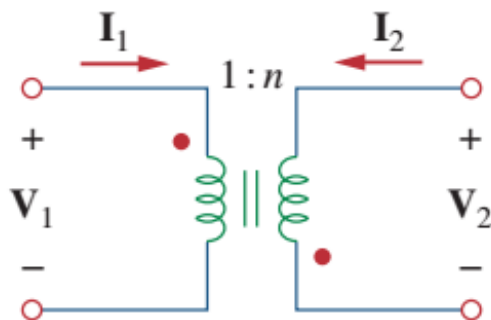
13.36 As done in Fig. 13.32, obtain the relationships between terminal voltages and currents for each of the ideal transformers in Fig. 13.105.




(a)

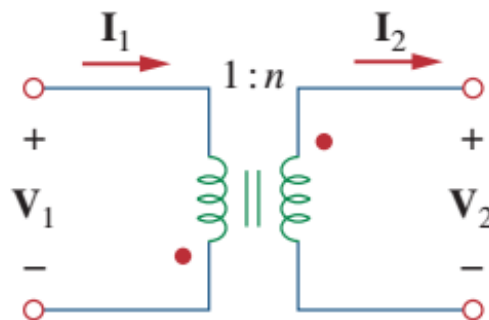

(b)

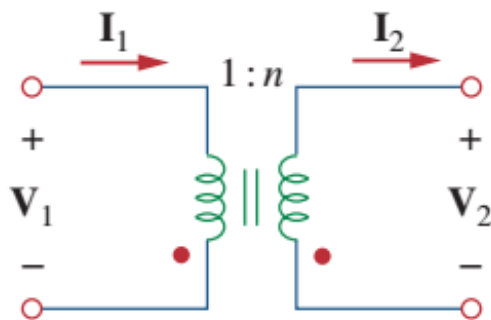


(c)

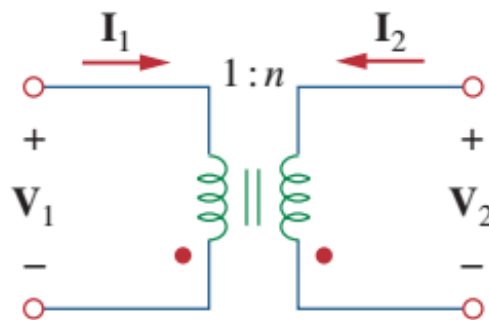

(d)



Ideal Transformers

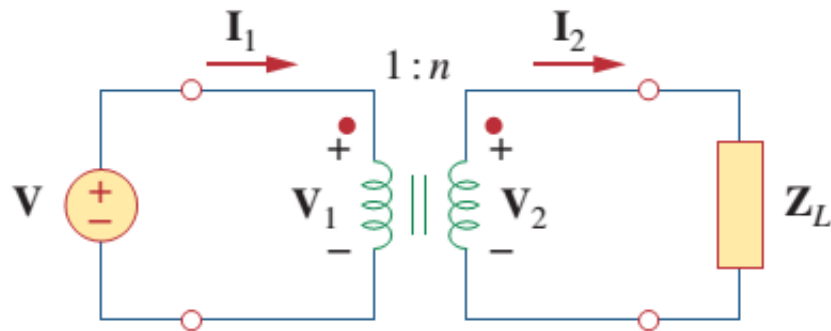


$$\frac{V_2}{V_1} = \frac{N_2}{N_1} = n$$

- Reflected impedance

$$Z_{\text{in}} = \frac{V_1}{I_1} =$$



Ideal Transformers


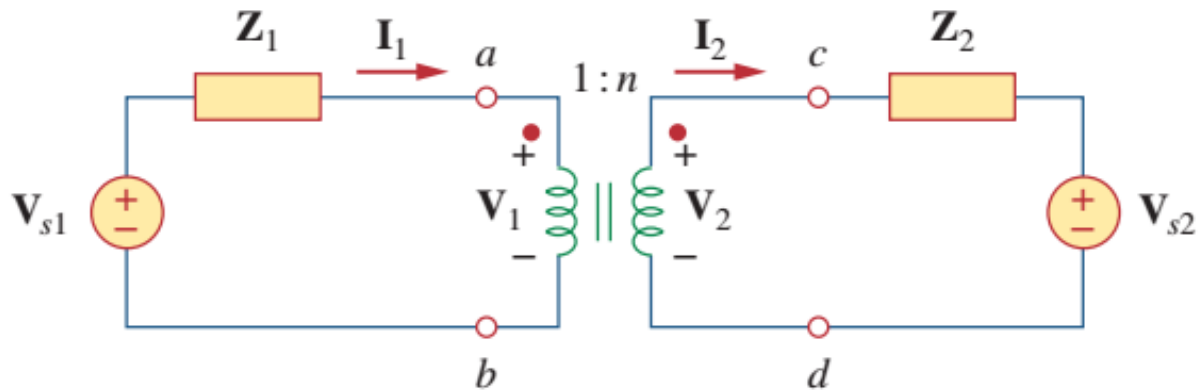


$$\frac{V_2}{V_1} = \frac{N_2}{N_1} = n$$






Ideal Transformers

- Reflected impedance and source

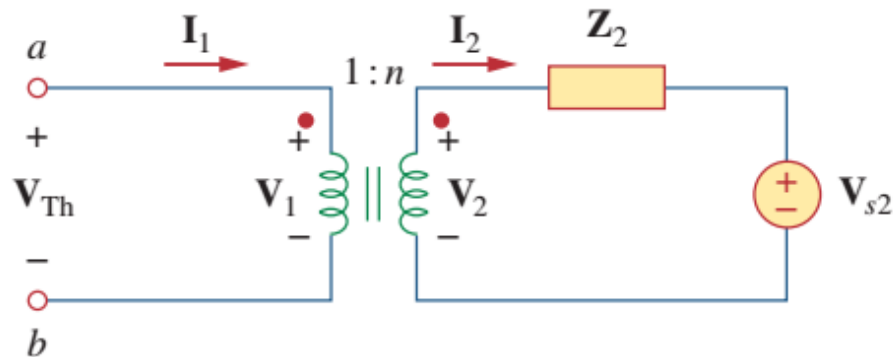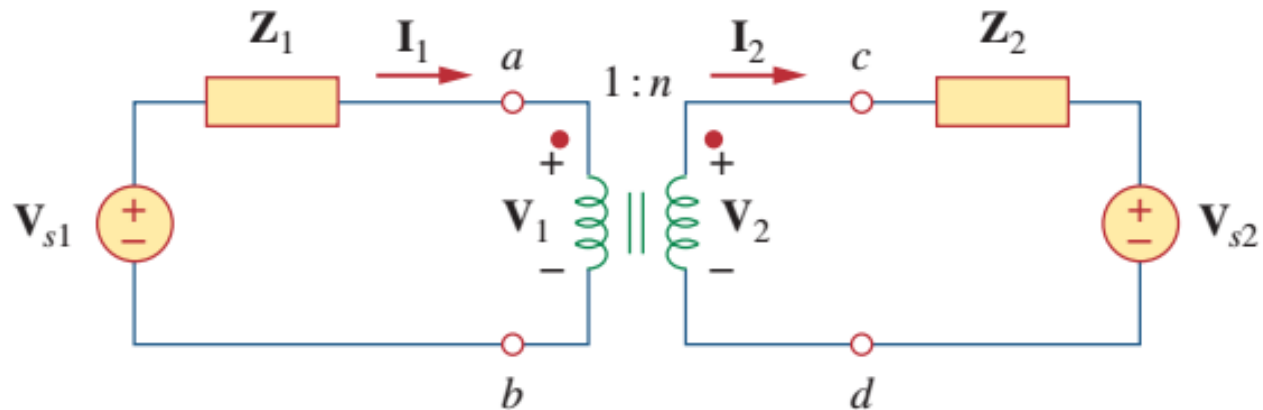

(a)

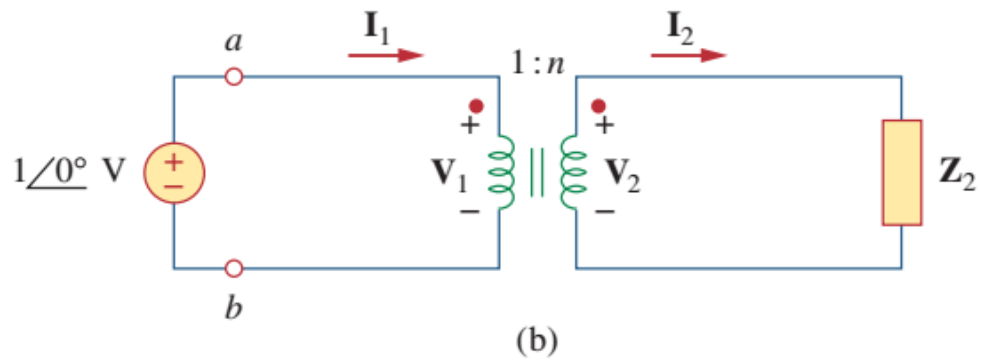


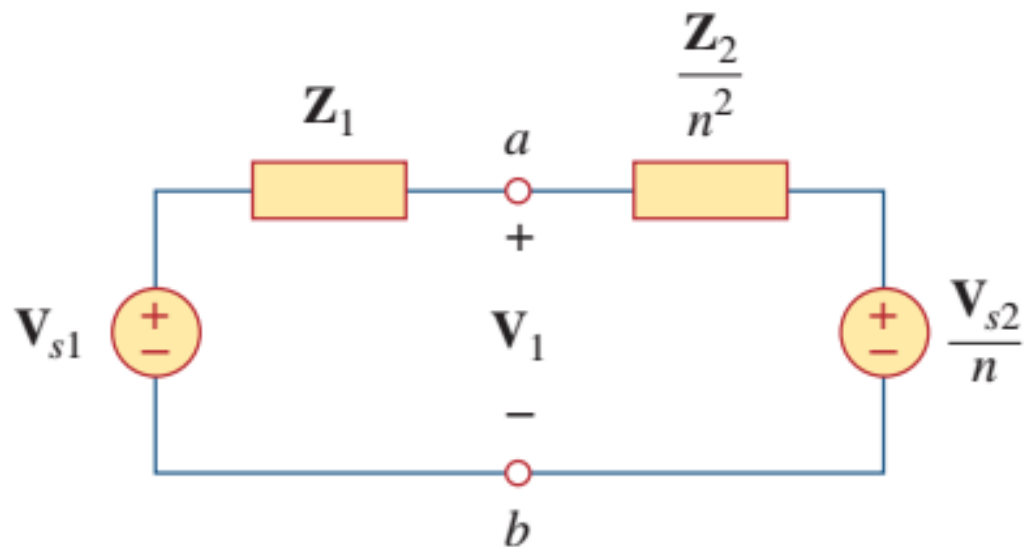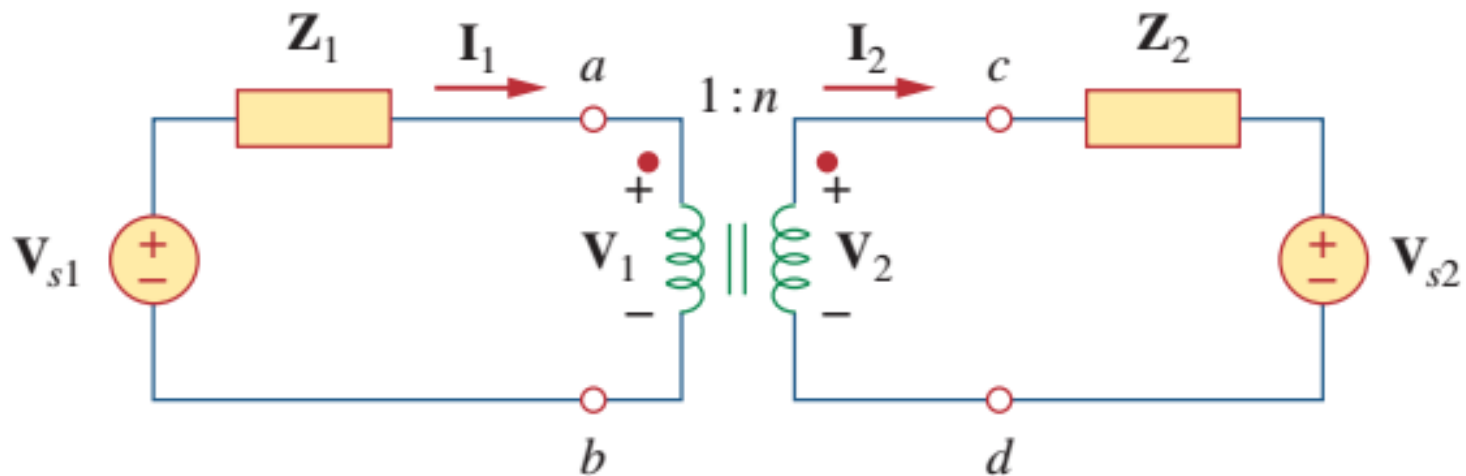




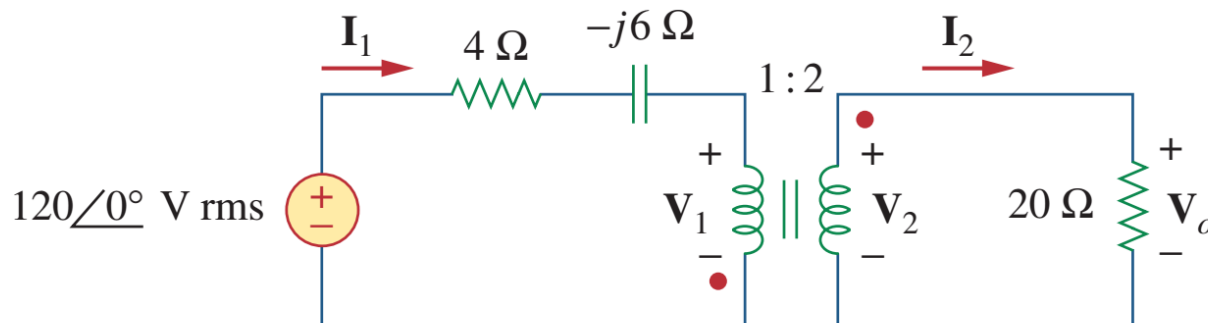Example

For the ideal transformer circuit of Fig. 13.37, find: (a) the source current \mathbf{I}_1 , (b) the output voltage \mathbf{V}_o , and (c) the complex power supplied by the source.



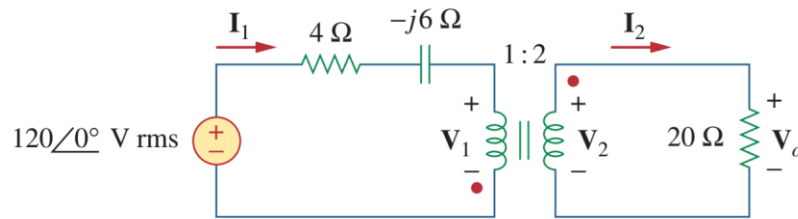

Solution:

(a) The 20-Ω impedance can be reflected to the primary side and we get

$$\mathbf{Z}_R = \frac{20}{n^2} = \frac{20}{4} = 5 \, \Omega$$

Thus,

$$\begin{aligned} \mathbf{Z}_{\text{in}} &= 4 - j6 + \mathbf{Z}_R = 9 - j6 = 10.82 \angle -33.69^\circ \, \Omega \\ \mathbf{I}_1 &= \frac{120 \angle 0^\circ}{\mathbf{Z}_{\text{in}}} = \frac{120 \angle 0^\circ}{10.82 \angle -33.69^\circ} = 11.09 \angle 33.69^\circ \, \text{A} \end{aligned}$$

(b) Since both \mathbf{I}_1 and \mathbf{I}_2 leave the dotted terminals,

$$\begin{aligned} \mathbf{I}_2 &= -\frac{1}{n} \mathbf{I}_1 = -5.545 \angle 33.69^\circ \, \text{A} \\ \mathbf{V}_o &= 20 \mathbf{I}_2 = 110.9 \angle 213.69^\circ \, \text{V} \end{aligned}$$


(c) The complex power supplied is

$$\mathbf{S} = \mathbf{V}_s \mathbf{I}_1^* = (120 \angle 0^\circ)(11.09 \angle -33.69^\circ) = 1,330.8 \angle -33.69^\circ \, \text{VA}$$



Practice

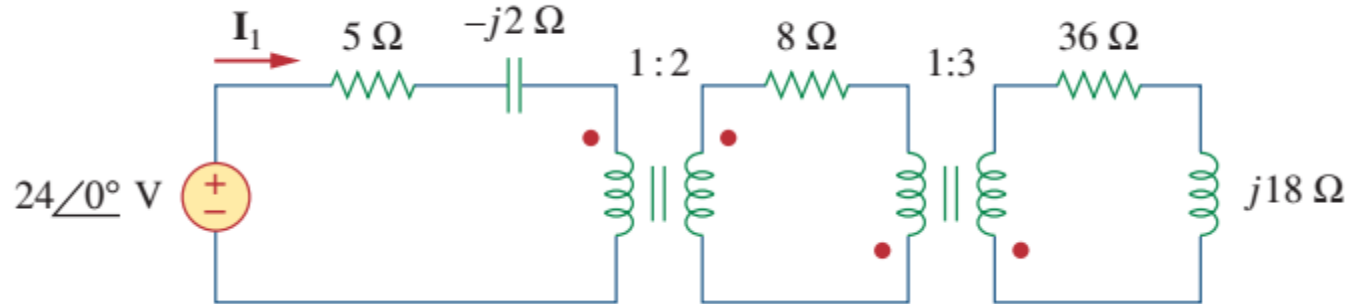
- Find reflected impedance and \mathbf{I}_1





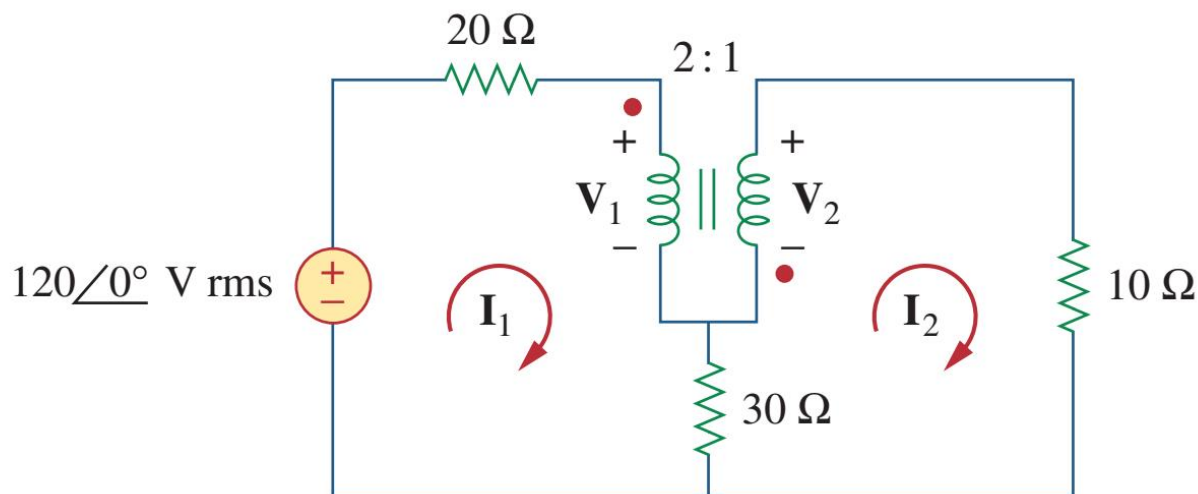Example

Calculate the power supplied to the $10\text{-}\Omega$ resistor in the ideal transformer circuit of Fig. 13.39.





$$-120 + (20 + 30)\mathbf{I}_1 - 30\mathbf{I}_2 + \mathbf{V}_1 = 0$$

or

$$50\mathbf{I}_1 - 30\mathbf{I}_2 + \mathbf{V}_1 = 120 \quad (13.9.1)$$

For mesh 2,

$$-\mathbf{V}_2 + (10 + 30)\mathbf{I}_2 - 30\mathbf{I}_1 = 0$$

or

$$-30\mathbf{I}_1 + 40\mathbf{I}_2 - \mathbf{V}_2 = 0 \quad (13.9.2)$$

At the transformer terminals,

$$\mathbf{V}_2 = -\frac{1}{2}\mathbf{V}_1 \quad (13.9.3)$$

$$\mathbf{I}_2 = -2\mathbf{I}_1 \quad (13.9.4)$$

(Note that $n = 1/2$.) We now have four equations and four unknowns, but our goal is to get \mathbf{I}_2 . So we substitute for \mathbf{V}_1 and \mathbf{I}_1 in terms of \mathbf{V}_2 and \mathbf{I}_2 in Eqs. (13.9.1) and (13.9.2). Equation (13.9.1) becomes

$$-55\mathbf{I}_2 - 2\mathbf{V}_2 = 120 \quad (13.9.5)$$

and Eq. (13.9.2) becomes

$$15\mathbf{I}_2 + 40\mathbf{I}_2 - \mathbf{V}_2 = 0 \quad \Rightarrow \quad \mathbf{V}_2 = 55\mathbf{I}_2 \quad (13.9.6)$$

Substituting Eq. (13.9.6) in Eq. (13.9.5),

$$-165\mathbf{I}_2 = 120 \quad \Rightarrow \quad \mathbf{I}_2 = -\frac{120}{165} = -0.7272 \text{ A}$$

The power absorbed by the $10\text{-}\Omega$ resistor is

$$P = (-0.7272)^2(10) = 5.3 \text{ W}$$