


# LABORATORY 10

## RLC Circuits

### Guide


#### Introduction

When an AC signal is input to an RLC circuit, voltage across each element varies as a function of time. The voltage will oscillate with a frequency of the AC signal. Likewise, the current will also oscillate with the same frequency. Nevertheless, the voltage and current may not rise and fall at the same time. The voltage and current is said to be out of phase as shown below.

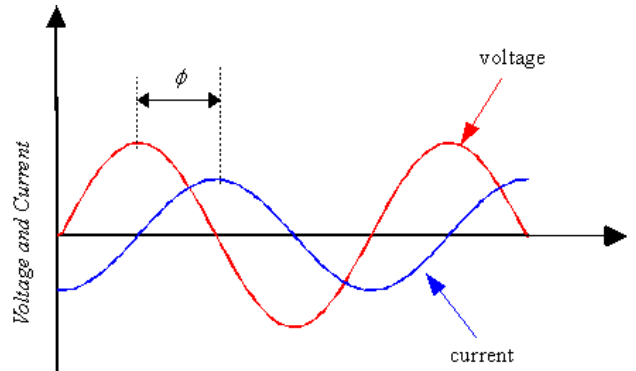

**Figure 1: Voltage and current in an AC circuit**

The phase angle  $\phi$  represents the difference between the maximum voltage and the maximum current. The phase angle will depend on the nature of the circuit. Consider a circuit consisting of a resistor, capacitor, and an inductor in series

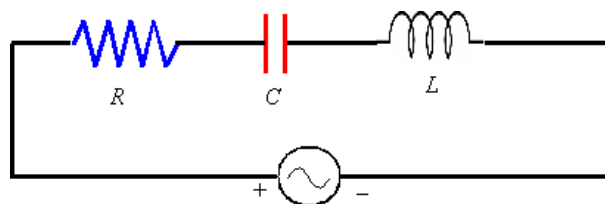

**Figure 2: RLC series circuit**

In an AC circuit, the Ohm's law cannot be directly applied. However, the law can be applied for maximum values of current and voltages. The maximum voltage across the resistor is given by

$$V_R = I_{\max} R \quad (1)$$

and the maximum voltage across the capacitor is given by

$$V_C = I_{\max} X_C \quad (2)$$

where  $X_C$  is known as the **capacitive reactance** and measures the effective resistance of the capacitor. The value of the capacitance reactance is defined as

$$X_C = \frac{1}{2\pi f C} \quad (3)$$

Likewise, the maximum voltage across the inductor is given by

$$V_L = I_{\max} X_L \quad (4)$$

where  $X_L$  is the **inductive reactance** and is defined as

$$X_L = 2\pi f L \quad (5)$$

The maximum voltage of the AC signal is given by

$$V_{\max} = I_{\max} Z \quad (6)$$

where  $Z$  is the known as the **impedance** of the circuit.

$$Z = \sqrt{R^2 + (X_L - X_C)^2} \quad (7)$$

The minus sign in front of the capacitive reactance reflects the  $180^\circ$  phase difference between the voltage across the inductor and the voltage across the capacitor. At a unique single frequency,  $X_L = X_C$ . This frequency is known as the **resonant frequency**. At resonant frequency, the current will be in phase with the source voltage. Setting the inductive and capacitive reactance equal to each other gives the resonant frequency to be

$$f_r = \frac{1}{2\pi \sqrt{LC}} \quad (9)$$

At resonant frequency, the impedance will be a minimum and the current in the circuit will be a maximum. The voltage across the inductor-capacitor combination will also be zero at resonant frequency.

The resonant frequency can be readily observed by using the XY mode on the oscilloscope. In the XY mode, the display will measure the voltage from one channel as a function of the voltage from the second channel. The resonance condition will be given by a single diagonal line on the oscilloscope display.

By measuring the half-life, either the inductance of an unknown inductor or the resistance of an unknown resistor can be found.

# Lab10 Prelab


---

Name \_\_\_\_\_ TA Checkoff \_\_\_\_\_

Teammate \_\_\_\_\_ Score \_\_\_\_\_

---

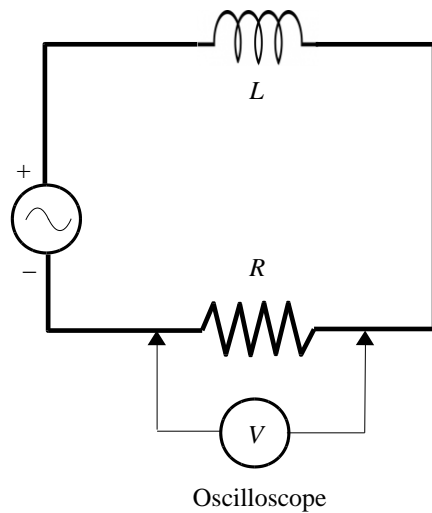1. Power supply output voltage is  $V_s = V_{\max} \sin(\omega t)$ ,  $V_{\max} = 10V$ ,  $R = 100\Omega$ ,  
 $L = 10mH$ ,  $f = 20Hz$ .




What is oscilloscope voltage expression?

\_\_\_/6pt

2. Power supply output voltage is  $V_s = V_{\max} \sin(\omega t)$ ,  $V_{\max} = 10V$ ,  $R = 100\Omega$ ,

$L = 10mH$ ,  $f = 15Hz$ ,  $C = 330\mu F$ .

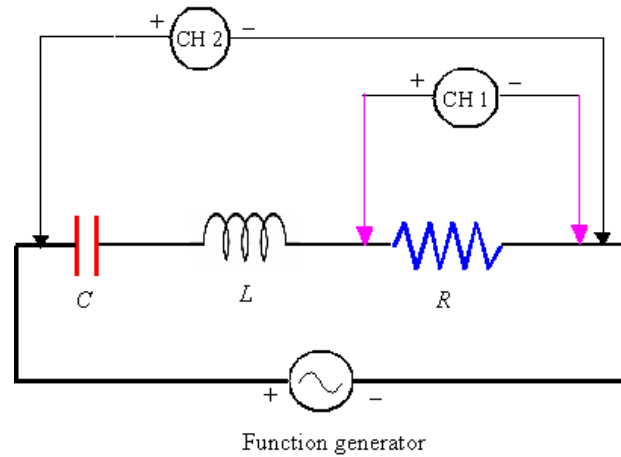

**Figure 3: Oscilloscope connections for the RLC circuit**

What are CH1 and CH2 expression?

\_\_\_/11pt

# Lab10 Report

---


Name \_\_\_\_\_ TA Checkoff \_\_\_\_\_

Teammate \_\_\_\_\_ Score \_\_\_\_\_

---

## Part I: Resistance of the Function Generator

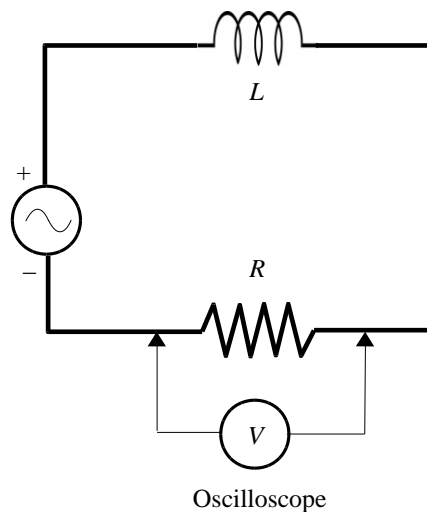
1. Use multimeter to measure and record the actual resistances of the  $100\ \Omega$  resistor and that of the 10 mH inductor.
2. Use  $100\ \Omega$  resistor and the 10 mH inductor on the BREAD board to create the RL circuit shown below.



3. Attach the oscilloscope probe between the inductor and resistor and the oscilloscope ground between the square wave generator ground and resistor
4. Set the function generator to sinusoidal wave.
5. Use the function generator output knob to set the peak-to-peak voltage to be about  $\pm 10$  V.
6. Adjust the oscilloscope voltage and horizontal time scale to obtain a single trace similar to either an exponential decay or growth diagram.
7. Measure the half-life from the oscilloscope display.

**Part II: Phase Measurement**

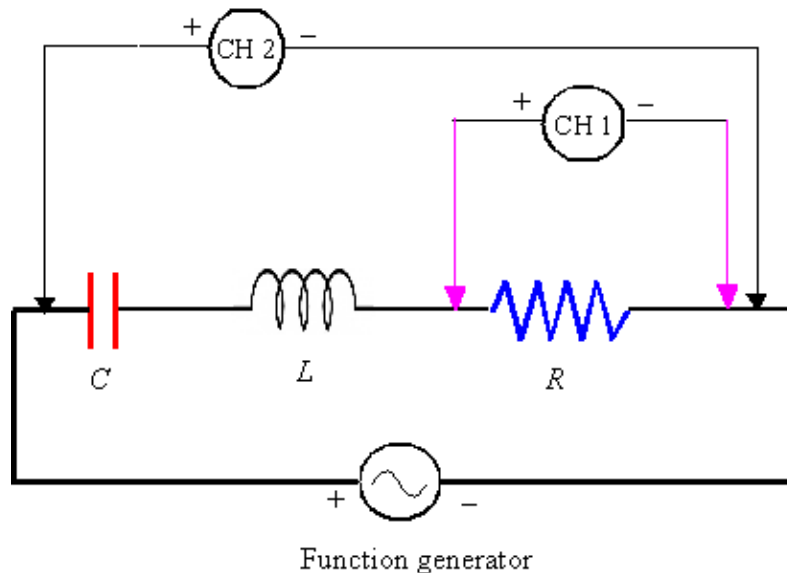1. Use multimeter to measure and record the actual resistances of the  $100\ \Omega$  resistor and that of the  $10\ \text{mH}$  inductor.
2. Use a  $330\ \mu\text{F}$  capacitor,  $100\ \Omega$  resistor, and  $10\ \text{mH}$  inductor in the BREAD circuit board to create an RLC circuit shown below.



3. Set the function generator to sinusoidal mode with a frequency of  $15\ \text{Hz}$  and the peak-to-peak voltage to be about  $\pm 10\ \text{V}$ .
4. Connect the alligator clip of the oscilloscope probe to the ground of the function generator.
5. Use vertical controls and set the coupling for CH 1 and CH 2 to AC.
6. Obtain simultaneous displays of the voltage across the resistor, i.e. current, and the voltage across the source.
7. Turn the sec/div knob to obtain about two complete cycles on the display.
8. Use the time cursors to measure the phase,  $\Delta t$ , between the current and the voltage across the source. Record the phase in the data table.
9. Measure and record the amplitude of the resistor and source voltage.
10. Repeat the phase and amplitude measurements for frequencies of  $1500\ \text{Hz}$  and  $2000\ \text{Hz}$ .

**Part III: Resonance**

1. Adjust the frequency until the current and the voltage across the source are in phase.
2. Record the resonant frequency of the RLC circuit.
3. Replace the  $330\ \mu\text{F}$  capacitor with  $100\ \mu\text{F}$  capacitor and determine the resonant frequency.

4. Use a breadboard and create a RLC circuit using a  $300\ \Omega$  resistor,  $470\ \mu\text{F}$  capacitor, and unknown inductor.
5. Measure and record the resonant frequency.
6. Replace the  $470\ \mu\text{F}$  capacitor with a  $1000\ \mu\text{F}$  capacitor and again measure the resonant frequency.

**Data Sheet:****Part I: Resistance of the Function Generator**Resistance of the inductor,  $R_L =$  \_\_\_\_\_

\_\_\_/1pt

Trial	Frequency (in Hz)	Resistance of the Resistor (in $\Omega$ )	Half-life (in s)
1	10		
2	15		
3	20		

\_\_\_/18pt

**Part II: Phase Angle Measurement**

Resistance of the resistor = \_\_\_\_\_

Resistance of the inductor = \_\_\_\_\_

Capacitance of the capacitor = \_\_\_\_\_

\_\_\_/4pt

Trial	Frequency (in Hz)	Phase, $\Delta t$ (in )	Maximum $V_R$ (in )	Maximum $V_{RLC}$ (in )
1	15			
2	1500			
3	2000			

\_\_\_/18pt



**Part III: Resonant Frequency**

	<b>Resistance (in <math>\Omega</math>)</b>	<b>Capacitance (in <math>\mu\text{F}</math>)</b>	<b>Resonant Frequency (in Hz)</b>
<b>Circuit I – Bread Board</b>		330	
<b>Circuit II – Bread Board</b>		100	
<b>Circuit III – Bread Board</b>		470	
<b>Circuit IV – Bread Board</b>		1000	

\_\_\_/12pt

**Calculations:**

1. Compare the value of half-life to the actual half-life.
2. From the phase measurement, calculate the phase angle.
3. Calculate the theoretical phase angle for each frequency.
4. Determine the % difference between the expected and the actual resonant frequency.

**Results:****Part I: Resistance of the Function Generator**

<b>Trial</b>	<b>Experimental Half-life</b>	<b>Theoretical Half-life</b>
<b>1</b>		
<b>2</b>		
<b>3</b>		

\_\_\_/10pt

**Part II: Phase Angle Measurement**

<b>Trial</b>	<b>Experimental Phase Angle</b>	<b>Theoretical Phase Angle</b>
<b>1</b>		
<b>2</b>		
<b>3</b>		

\_\_\_/10pt

**Part III: Resonant Frequency Measurement**

	<b>Theoretical Resonant Frequency (in Hz)</b>	<b>Experimental Resonant Frequency (in Hz)</b>	<b>% Error</b>
<b>Circuit I – Bread Board</b>			
<b>Circuit II – Bread Board</b>			
<b>Circuit III – Bread Board</b>			
<b>Circuit IV – Bread Board</b>			

\_\_\_/10pt

TA: \_\_\_\_\_

Part One: \_\_\_\_\_ of 19 Pt.

Part Two: \_\_\_\_\_ of 22 Pt.

Part Three: \_\_\_\_\_ of 42 Pt.

Prelab: \_\_\_\_\_ of 17Pt.

Total: \_\_\_\_\_ of 100Pt.