

EE 111 Homework 3

Due date: Apr. 1<sup>st</sup>, 2019  
Turn in your homework in class

Rule:

- Work on your own. Discussion is permissible, but similar submissions will be judged as plagiarism.
- Please show all intermediate steps: a correct solution without an explanation will get zero credit.
- Please submit on time. No late submission will be accepted.
- Please prepare your submission in English only. No Chinese submission will be accepted.

1. (8pt) In the circuit shown in Fig.1 below

$$v(t) = 72e^{-100t}V, t > 0$$

$$i(t) = 9e^{-100t}mA, t > 0$$

- (a) Find the values of  $R$  and  $C$ .  
 (b) Calculate the time constant  $\tau$ .  
 (c) Determine the time required for the voltage to decay half its initial value at  $t = 0$ .

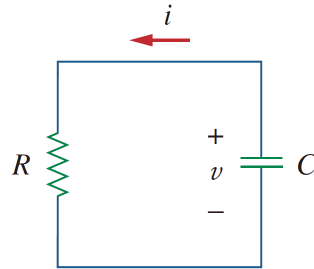


Fig. 1

**Solution:**

- (a)

$$R = \frac{v(t)}{i(t)} = \frac{72e^{-100t}}{9e^{-100t}} = 8k\Omega \quad (1')$$

$$\tau = RC = \frac{1}{100}s$$

$$C = \frac{1}{100R} = \frac{1}{100 \times 8 \times 10^3} = 1.25\mu F \quad (2')$$

- (b)

$$\tau = \frac{1}{100} = 10ms \quad (1')$$

- (c)

$$v(0) = 72V \quad (1')$$

$$v(t) = \frac{1}{2}v(0) \quad (1')$$

$$72e^{-100t} = 36$$

$$t = \frac{\ln 2}{100} = 6.93ms \quad (2')$$

2. (10pt) Assuming that the switch in Fig.2 has been in position  $A$  for a long time and is moved to position  $B$  at  $t = 0$ , Then at  $t = 1$  second, the switch moves from  $B$  to  $C$ . Find  $v_C(t)$  for  $t \geq 0$ .

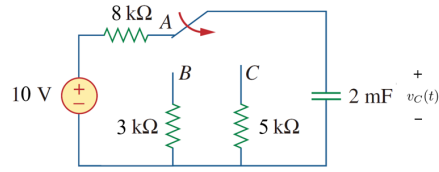


Fig. 2

**Solution:**

$$v_C(0) = 10V \quad (1')$$

For  $0 < t < 1$ ,

$$\tau_1 = R_B C = 3000 \times 2^{-3} = 6s \quad (1')$$

$$v_C(t) = v_C(0)e^{-\frac{t}{\tau_1}} = 10e^{-\frac{t}{6}}V \quad (2')$$

When  $t = 1s$ ,

$$v_C(1) = 10e^{-\frac{1}{6}}V \quad (1')$$

For  $t > 1$ ,

$$\tau_2 = R_C C = 5000 \times 2^{-3} = 10s \quad (1')$$

$$v_C(t) = v_C(1)e^{-\frac{t-1}{\tau_2}} = 10e^{-\frac{1}{6}}e^{-\frac{t-1}{10}} = 9.355e^{-\frac{t}{10}}V \quad (2')$$

$$\therefore v_C(t) = \begin{cases} 10e^{-\frac{t}{6}}V, & 0 \leq t < 1 \\ 9.355e^{-\frac{t}{10}}V, & t \geq 1 \end{cases} \quad (2')$$

3. (8pt) For the circuit in Fig.3, find  $i_o$  for  $t > 0$ .

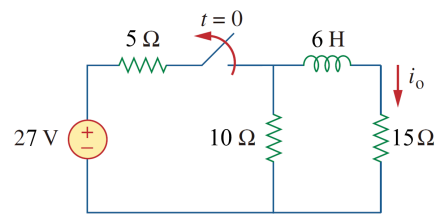


Fig. 3

**Solution:**

$$i_o(0) = \frac{27}{10 \parallel 15 + 5} \cdot \frac{10}{15 + 10} = \frac{54}{55} A \quad (2')$$

$$\tau = \frac{L}{R} = \frac{6}{10 + 15} = \frac{6}{25} s \quad (2')$$

$$i_o(t) = i_o(0)e^{-\frac{t}{\tau}} = \frac{54}{55}e^{-\frac{25t}{6}} A \quad (4')$$

4. (10pt) Consider the circuit of Fig.4.

(a) Find  $v_o(t)$  in Fig.4(a) if  $i(0) = 6A$  and  $v(t) = 0V$ .

(b) Find  $v_o(t)$  in Fig.4(b) if  $i(0) = 6A$  and  $v(t) = 24u(t)V$ .

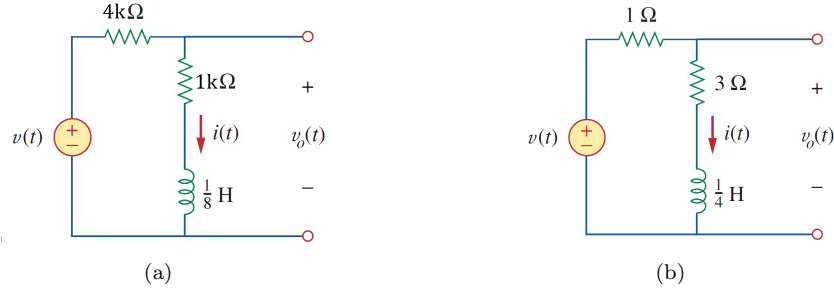


Fig. 4

**Solution:**

(a) For  $t > 0$ ,

$$i(t) = i(0)e^{-\frac{R}{L}t} = 6e^{-\frac{5000}{1/8}t} = 6e^{-40000t} A \quad (2')$$

$$v_o(t) = -4000i(t) = -24000e^{-40000t} V$$

$$\therefore v_o(t) = -24000e^{-40000t}u(t)V \quad (2')$$

(b) Apply KVL to the mesh,

$$-24 + 1 \cdot i(t) + 3 \cdot i(t) + \frac{1}{4} \frac{di(t)}{dt} = 0 \quad (2')$$

Simplify it,

$$\frac{di(t)}{dt} + 16i(t) = 96$$

$$i(t) = e^{-\int 16dt} \left( \int 96e^{\int 16dt} dt + C \right) = 6 + Ce^{-16t} A \quad (1')$$

$$i(0) = 6 + C = 6 \rightarrow C = 0 \rightarrow i(t) = 6A \quad (1')$$

$$v_o(t) = 24 - 1 \cdot i(t) = 24 - 6 = 18V \quad (2')$$

5. (10pt) For the circuit in Fig.5,

$$v = 40e^{-25t}V$$

and

$$i = 10e^{-25t}A, \quad t > 0$$

- (a) Find  $L$  and  $R$ .
- (b) Determine the time constant.
- (c) Calculate the initial energy in the inductor.
- (d) What fraction of the initial energy is dissipated in 20 ms?

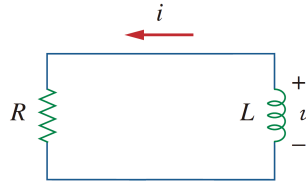


Fig. 5

**Solution:**

(a)

$$R = \frac{v}{i} = \frac{40e^{-25t}}{10e^{-25t}} = 4\Omega \quad (1')$$

$$\tau = \frac{L}{R} = \frac{1}{25}s$$

$$L = R\tau = 4/25 = 0.16H \quad (2')$$

(b)

$$\tau = \frac{1}{25} = 0.04s \quad (2')$$

(c)

$$w(0) = \frac{1}{2}Li^2(0) = \frac{1}{2} \frac{4}{25} \times 10^2 = 8J \quad (2')$$

(d) The value of the energy remaining at 20ms is given by:

$$w(20) = \frac{1}{2}Li^2(20) = \frac{1}{2} \frac{4}{25} \times (10e^{-25 \times 0.02})^2 = 8e^{-1} \quad (2')$$

So the fraction of the energy dissipated in the first 20ms is given by:

$$\frac{8 - 8e^{-1}}{8} \cdot 100\% = (1 - e^{-1}) \cdot 100\% = 63.21\% \quad (1')$$

- 10pt 6. The switch in Fig.6 has been in position  $a$  for a long time. At  $t = 0$ , it moves to position  $b$ . Calculate  $i(t)$  for  $t > 0$ .


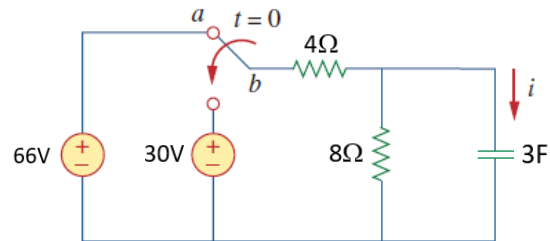


Fig. 6

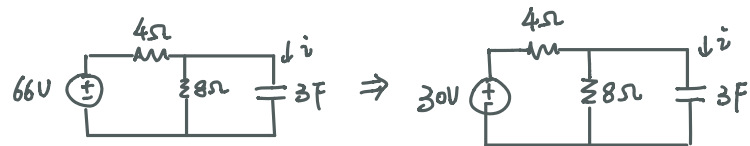

$$R_{eq} = 4 \parallel 8 = \frac{8}{3} \Omega$$

$$\tau = R \cdot C = 3 \times \frac{8}{3} = 8 \text{ s} \quad 2'$$

$$V(0) = \frac{8}{4+8} \times 66 = 44 \text{ V} \quad 1'$$

$$V(\infty) = \frac{8}{4+8} \times 30 = 20 \text{ V} \quad 1'$$

$$V(t) = V(\infty) + [V(0) - V(\infty)] \cdot e^{-t/\tau}$$

$$= 20 + (44 - 20) \cdot e^{-t/8}$$

$$= 20 + 24 \cdot e^{-t/8} \text{ V} \quad 3'$$

$$i(t) = C \frac{dV(t)}{dt}$$

$$= 3 \times 24 \times e^{-\frac{t}{8}} \cdot \left(-\frac{1}{8}\right)$$

$$= -9 e^{-0.125t} u(t) \text{ A} \quad 3'$$

10pt

7. The switch in Fig. 7 has been in position a for a long time, at  $t = 0$ , it moves to position b. Find  $v(t)$  for  $t < 0$  and  $t > 0$  in the circuit.


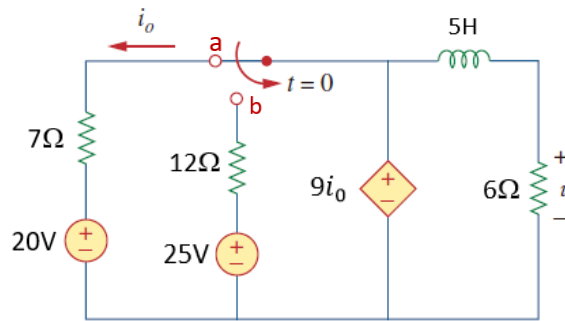


Fig. 7

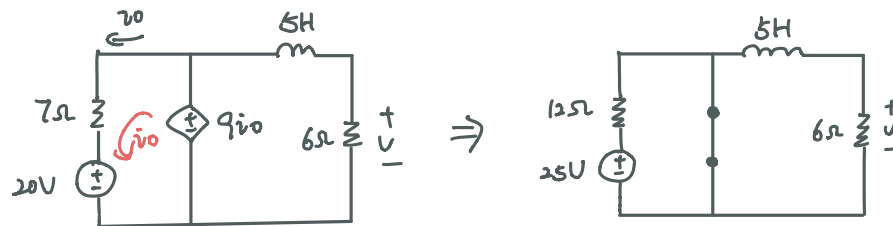

(4) ①  $7i_0 + 20 - 9i_0 = 0 \Rightarrow i_0 = 10 \text{ A}$  2'

5H inductance short cut

for  $t < 0$ ,  $v = 9i_0 = 90 \text{ V}$  2'

$$i = \frac{V}{6} = 15 \text{ A}$$

(6) ② for  $t > 0$

$$i(0) = 15, i(\infty) = 0$$

$$\tau = \frac{L}{R_{th}} = \frac{5}{6} \text{ s}$$

$$\therefore i(t) = i(\infty) + [i(0) - i(\infty)] \cdot e^{-t/\tau}$$

$$= 15 \cdot e^{-1.2t} \text{ A} \quad 2'$$

$$v(t) = 6 \cdot i(t) = 90 e^{-1.2t} u(t) \text{ V} \quad 2'$$

$$\therefore v(t) = \begin{cases} 90 \text{ V} & \text{for } t < 0 \\ 90 \cdot e^{-1.2t} \text{ V} & \text{for } t > 0 \end{cases}$$



lopt

8. If the input pulse in Fig.8 is applied to the circuit in Fig. 8 (b), determine the response  $i(t)$  while  $i(0) = 0.75A$ .

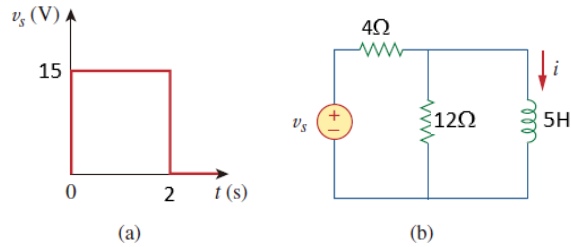


Fig. 8

① for  $0 < t < 2$ ,  $i(0) = 0$ ,  $i(\infty) = \frac{15}{4} = 3.75$

$$R_{th} = 4 \parallel 12 = 3 \Omega$$

$$\tau = \frac{L}{R_{th}} = \frac{5}{3} \text{ s}$$

$$i(t) = i(\infty) + [i(0) - i(\infty)] \cdot e^{-t/\tau}$$

$$= 3.75 - 3 \cdot e^{-0.6t} \text{ A}$$

② for  $t > 2$ ,  $i(\infty) = 0$

now  $v_s = 0$

$$i(t) = i(\infty) + [i(2) - i(\infty)] \cdot e^{-\frac{t-2}{\tau}}$$

$$= i(2) \cdot e^{-\frac{t-2}{\tau}}$$

$$= (3.75 - 3 \cdot e^{-1.2}) \cdot e^{-0.6t+1.2} \text{ A}$$

$$= 3.75 e^{-0.6t+1.2} - 3e^{-0.6t} \text{ A}$$

$$\therefore i(t) = \begin{cases} 3.75 - 3 \cdot e^{-0.6t} \text{ A} & 0 < t < 2 \\ 3.75 e^{-0.6t+1.2} - 3e^{-0.6t} \text{ A} & t > 2 \end{cases}$$

/opt

9. If  $v(0) = 6\text{ V}$ , find  $v_o(t)$  for  $t > 0$  in the op amp circuit in Fig.9. Let  $R = 3\text{ k}\Omega$  and  $C = \frac{1}{3}\text{ }\mu\text{F}$ .

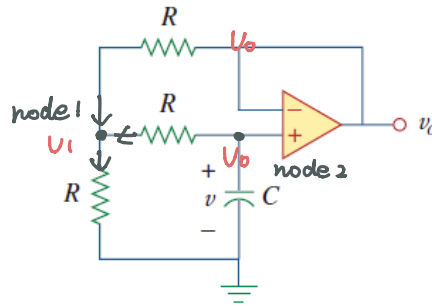


Fig. 9

for node 1:

$$\frac{V_o - V_1}{R} + \frac{V_o - V_1}{R} = \frac{V_1}{R}$$

$$\Rightarrow V_1 = \frac{2}{3} V_o \quad 2'$$

for node 2:

$$C \frac{dV_o}{dt} + \frac{V_o - V_1}{R} = 0 \quad 2'$$

$$-RC \frac{dV_o}{dt} = V_o - V_1 = \frac{1}{3} V_o$$

$$\frac{dV_o}{dt} = -\frac{V_o}{3RC}$$

$$\frac{dV_o}{V_o} = -\frac{1}{3RC} dt$$

$$\ln V_o = -\frac{1}{3RC} t + C \quad \leftarrow \text{常数 } C$$

$$V_o(t) = e^{-\frac{t}{3RC}} \cdot V_o(0) \quad \leftarrow \text{常数 } e^C$$

$$\therefore V_o(0) = 6\text{ V}$$

$$\tau = 3RC = 3 \times 3000 \times \frac{1}{3} \times 10^{-6} = 3 \times 10^{-3}\text{ s} \quad 2'$$

$$\therefore V_o(t) = 6 e^{-1000t/3} u(t) \text{ V} \quad 2'$$

$$\text{当 } t=0 \text{ 时, } V_o(0) = e^{-\frac{t}{3RC}} \cdot e^C = e^C$$

过程 2'

14 pt

10. At the time the double-pole switch in the circuit shown in Fig. 10 is closed, the initial voltages on the capacitors are 12V and 4V, as shown. Find the numerical expressions for  $v_o(t)$ ,  $v_2(t)$ , and  $v_f(t)$  that are applicable, as long as the ideal op amp operates in its linear range.


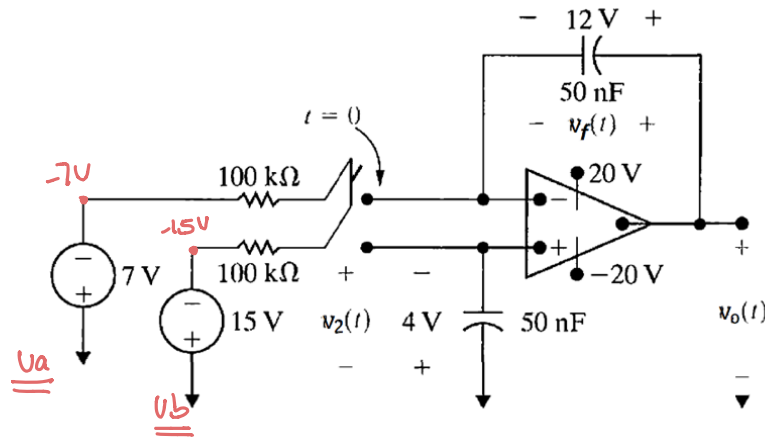


Fig. 10

equation for an integrating amplifier:

$$v_o = \frac{1}{RC} \int_0^t (v_b - v_a) dx + v_o(0)$$

extension

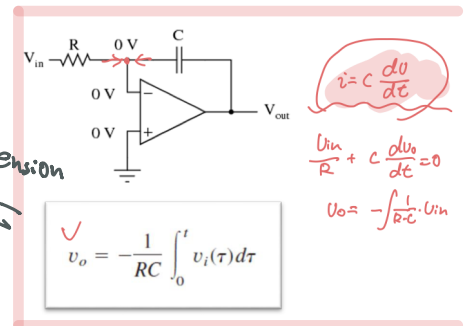

(4) for  $v_o(t)$   $RC = 10 \times 10^3 \times 0.05 \times 10^{-6} = 5 \text{ ms}$

$$\therefore \frac{1}{RC} = 200$$

$$\therefore v_b - v_a = -15 - (-7) = -8 \text{ V}$$

$$v_o(0) = -4 - (-12) = 8 \text{ V}$$

$$\Rightarrow v_o(t) = \frac{1}{RC} \int_0^t (v_b - v_a) dx + v_o(0)$$

$$= 200 \int_0^t -8 dx + 8$$

$$= (-1600t + 8) \text{ V} \quad 0 \leq t \leq t_{\text{sat}}$$

(4) for  $v_2(t)$   $v_2(0^+) = -4 \text{ V}$ ,  $v_2(\infty) = -15 \text{ V}$ ,  $\tau = 5 \text{ ms}$

$$\therefore v_2(t) = v_2(\infty) + [v_2(0^+) - v_2(\infty)] e^{-t/\tau}$$


$$= -15 + (-4 + 15) e^{-200t}$$

$$= -15 + 11e^{-200t} \text{ V} \quad 0 \leq t \leq t_{\text{sat}}$$

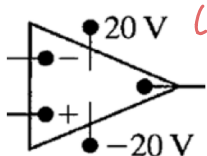(4) for  $v_f(t)$   $\therefore v_f + v_2 = v_o$

$$\Rightarrow v_f(t) = v_o(t) - v_2(t)$$

$$= 23 - 1600t - 11e^{-200t} \text{ V} \quad 0 \leq t \leq t_{\text{sat}}$$



(2) for  $-1600t_{\text{sat}} + 8 = -20 \Rightarrow t_{\text{sat}} = 17.5 \text{ ms}$

2' 运放线性工作区域时间