

Homework 4

Due date:

Apr. 14th, 2021

Turn in your homework in class

Rules:

- Please work on your own. Discussion is permissible, but extremely similar submissions will be judged as plagiarism!
- Please show all intermediate steps: a correct solution without an explanation will get zero credit.
- Please submit on time. No late submission will be accepted.
- Please prepare your submission in English only. No Chinese submission will be accepted.

1. [8%] Equivalent capacitance and inductance

- Obtain the equivalent capacitance of the circuit at terminals a and b in **Fig. 1(a)**.
- Obtain the equivalent inductance of the circuit at terminals a and b in **Fig. 1(b)**.

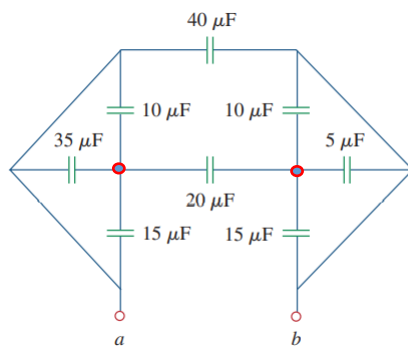


Fig. 1(a).

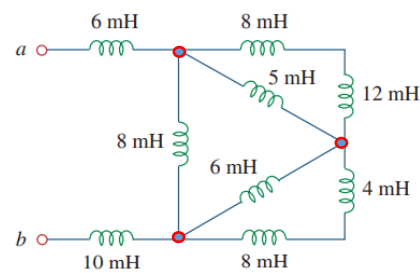
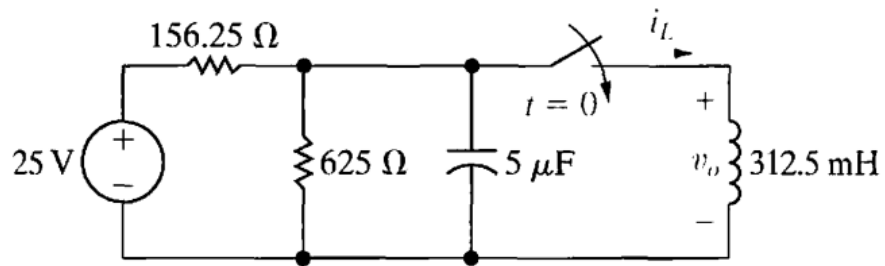


Fig. 1(b).

2. [10%] Assume the switch is open for a long time and the system is stable when $t < 0$. Then the switch is closed at time $t = 0$. Use the circuit as shown in **Fig 2**:
- Find the total energy delivered to the inductor in the time period $[0, \infty]$.
 - Find the total energy delivered to the capacitor in the time period $[0, \infty]$.

**Fig. 2.**

3. [13%] At $t = 0$, the voltage signal of **Fig. 3(b)** is applied to the cascaded integrating amplifiers shown in **Fig. 3(a)**. There is no energy stored in the capacitors when $t = 0^-$. Find $v_{o1}(t)$ and $v_o(t)$ for $t > 0$.

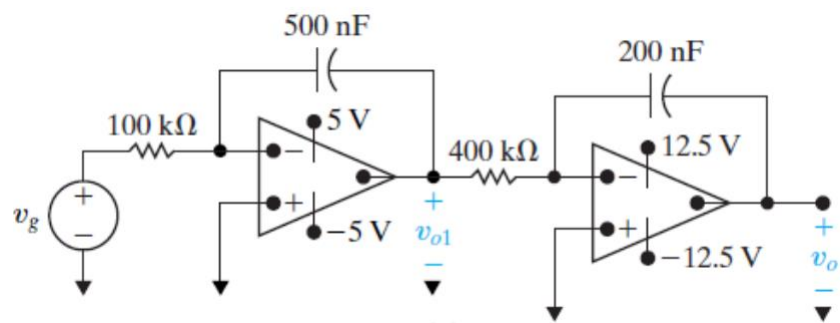


Fig. 3(a).

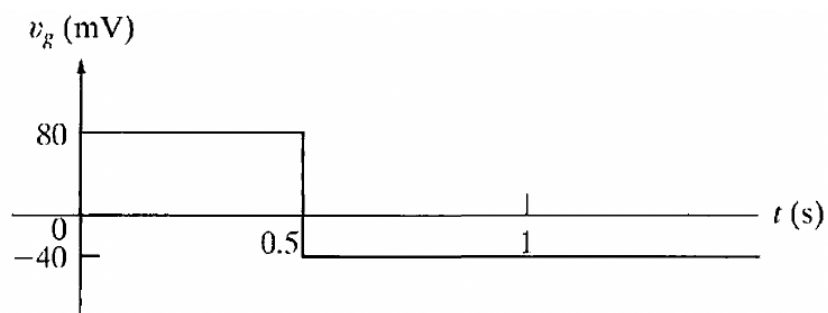


Fig. 3(b).

4. [15%] In the circuit shown in **Fig. 4**, the switch is closed at $t = 0$ s and re-opened at $t = 0.5$ s.
- Given $V_s = 18$ V, $R_s = 1\Omega$, $R_1 = 5\Omega$, $R_2 = 2\Omega$, $L = 2$ H and $C = \frac{1}{17}$ F. Determine the response for $i_L(t)$ of $t \geq 0$. There is no energy stored in the inductor and capacitor when $t < 0$.

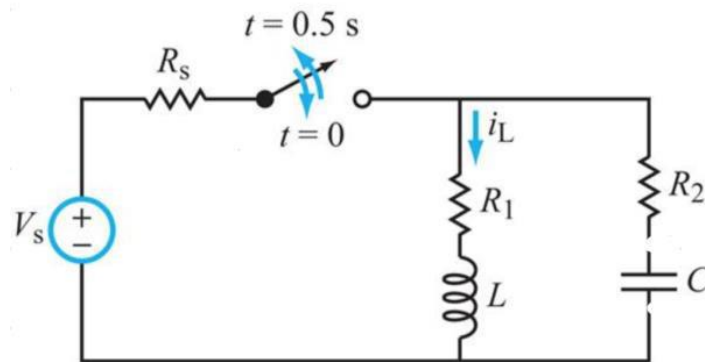


Fig. 4.

5. [10%] In the circuit below, $R_1 = 10\Omega$, $R_2 = 5\Omega$, $L = 4\text{mH}$, $C = 10\text{mF}$. When $t < 0$, the input voltage (U) is 5V. When $t = 0$, the input voltage changes to $U = 12\text{V}$. Assume that the circuit reaches steady state before $t = 0$. Determine the expression for $V_C(t)$ when $t \geq 0$.

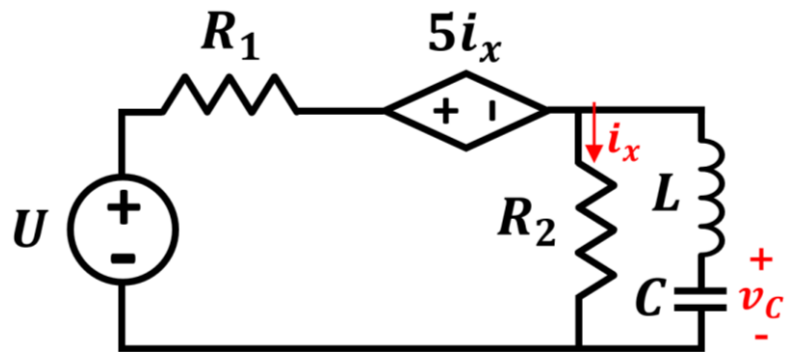


Fig. 5.

6. [12%] The circuit is shown in **Fig.6**. the gap in the circuit seen in figure will be shorted whenever the voltage across the gap reaches 30 kV . The initial current in the inductor is zero. The value of β is adjusted so the Thevenin resistance with respect to the terminals of the inductor when the switch is closed is $-4\text{ k}\Omega$ (Thevenin equivalent to the rest of the circuit excluding the inductor; assuming the gap remains open circuit during the Thevenin equivalencing).
- (1) What is the value of β ?
- (2) How many microseconds after the switch is closed will the gap be shorted?

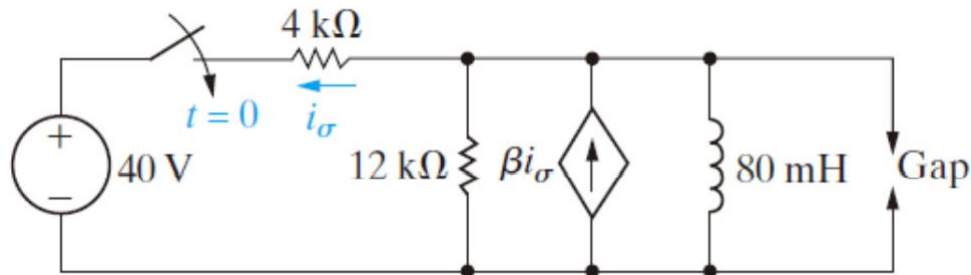


Fig.6.

7. [20%] The initial value of the voltage $v(0^+)$ in the circuit shown in **Fig. 7** is zero, and the initial value of the capacitor current, $i_c(0^+)$, is 45mA. The expression for the capacitor current is known to be $i_c(t) = A_1 e^{-200t} + A_2 e^{-800t}$, $t > 0$. $R = 250\Omega$ Find
- The values of L , C , A_1 and A_2 .
 - The express for $v(t)$, $t \geq 0$.

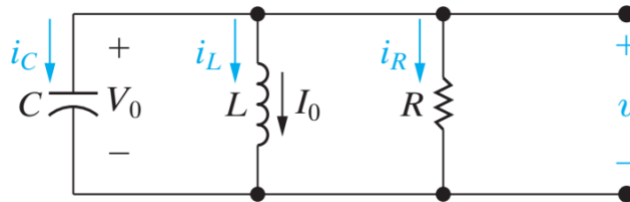


Fig. 7.

8. [12%] Consider a simple series RLC circuit. Before $t=0$ there is no energy stored in the capacitor and inductor. The switch is closed at $t = 0$. The voltage source is:

$$V(t) = 32e^{-40t}V, t > 0$$

Express i_L , knowing that $R = 75\Omega$, $C = 0.125F$ and $L = 4H$.

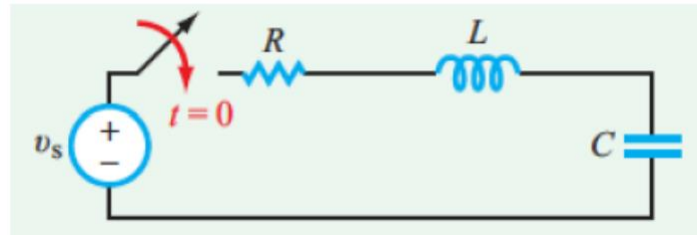


Fig. 8.