



Lecture 2

Basic Laws & Circuit Analysis




Outline

- Terminology: Branches, Nodes, and Loops
- Basic Laws
 - Ohm's Law
 - Kirchhoff's Laws -- KCL, KVL
- Circuit Analysis
 - Nodal Analysis
 - Mesh Analysis


Terminology: Branches, Nodes, and Loops

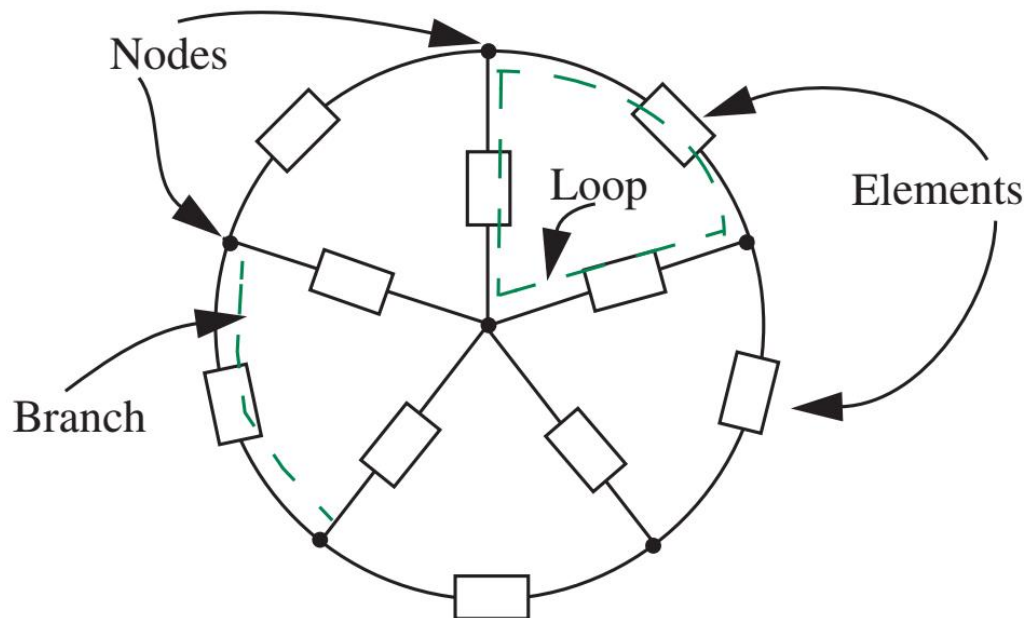- **Branch**: represents a single element;
- **Node**: a point of connection between two or more branches;
- **Loop**: **Any** closed path in a circuit.



Loop, Independent Loop, Mesh

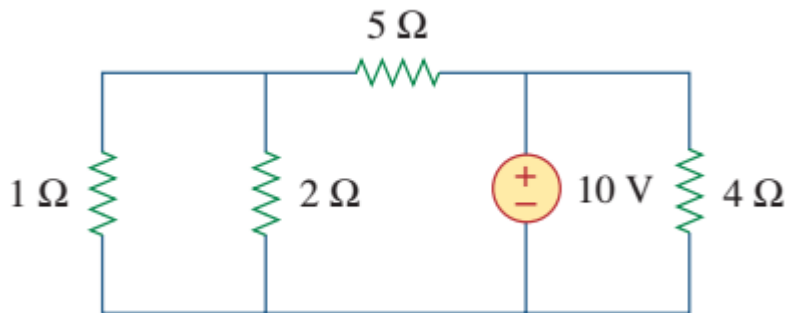- A loop is a closed path with no node passed more than once.
- A loop is independent if it contains at least one branch which is not a part of any other independent loop.
- A mesh is a loop that does not contain any other loop within it.



- b – number of branches
- n – number of nodes
- l_{ind} – number of ind. loops

$$l_{ind} = b - (n - 1)$$

Mesh = Independent loop?

Ohm's Law

- Resistance: the ratio of voltage drop and current. The circuit element used to model this behavior is the resistor.

Circuit symbol: 

- The current flowing in the resistor is proportional to the voltage across the resistor:

$$v = i R$$

(Ohm's Law)

- Conductance** is the reciprocal of resistance

$$G = \frac{1}{R} = \frac{i}{v}$$




Werner von Siemens
1816-1892



Kirchhoff's Laws

- Kirchhoff's Current Law (KCL):
 - The algebraic sum of all the **currents** entering any **node** in a circuit equals zero.
 - Why?

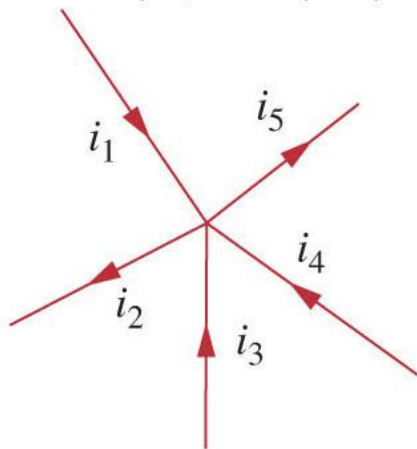Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display




Gustav Robert Kirchhoff
1824-1887



A Major Implication of KCL

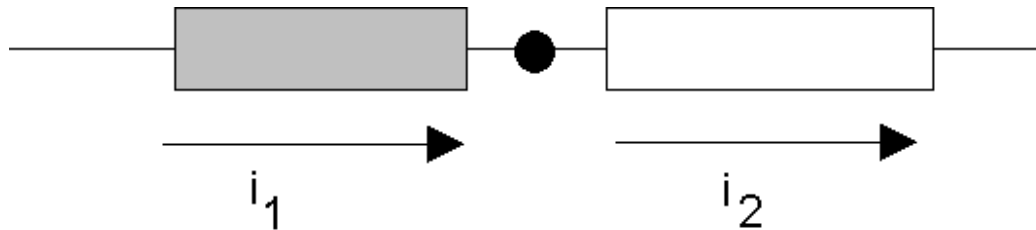- KCL tells us that **all of the elements that are connected *in series* carry the same current.**




Current entering node = Current leaving node

Generalization of KCL



- The sum of currents entering/leaving a **closed surface** is zero.
 - Circuit branches can be inside this surface, *i.e.* the surface can enclose more than one node!

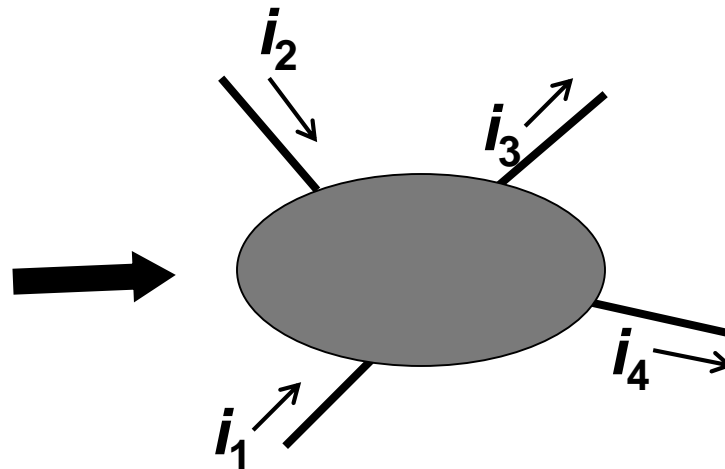This could be a big chunk of a circuit, *e.g.* a “black box”






Generalized KCL Examples

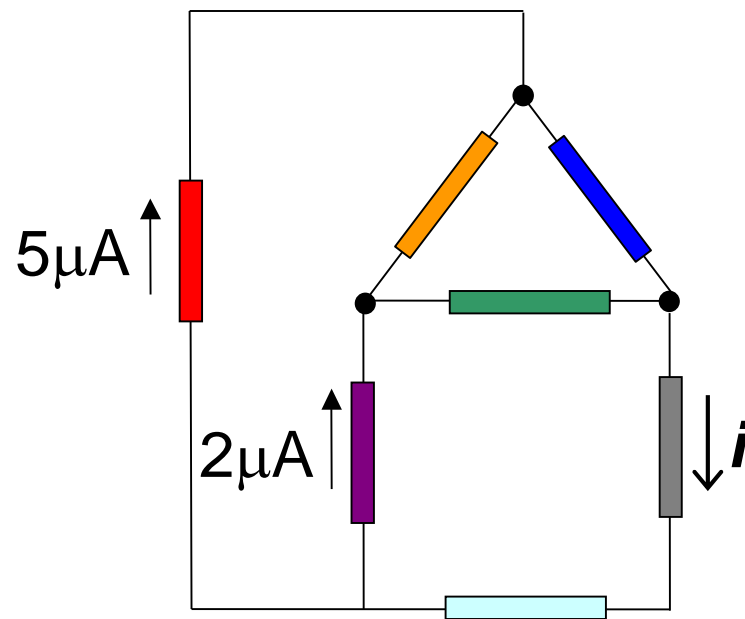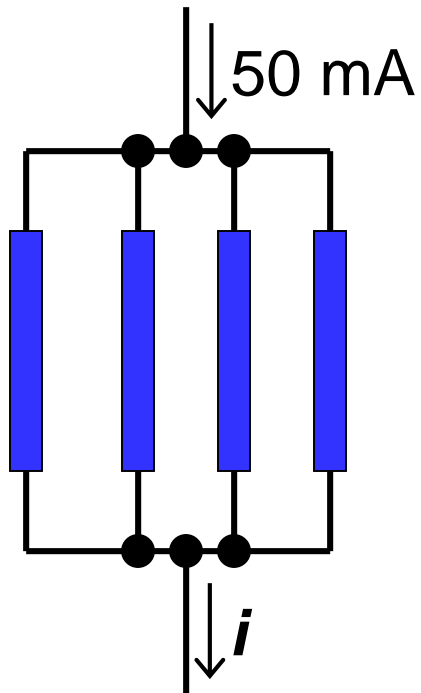



Notation: Node and Branch Voltages

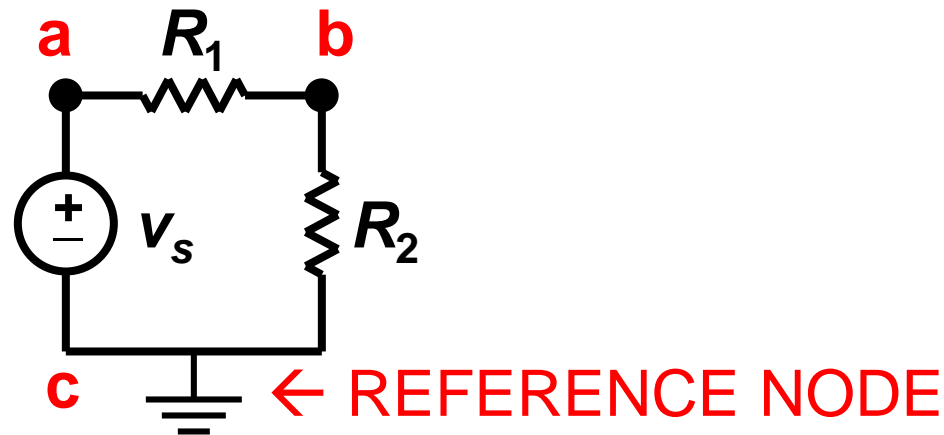


- Use one node as the reference (the “common” or “ground” node) – label it with a symbol.
- The voltage drop from node x to the reference node is called the **node voltage** V_x .
- The voltage across a circuit element is defined as the difference between the node voltages at its terminals.



Kirchhoff's Voltage Law (KVL)

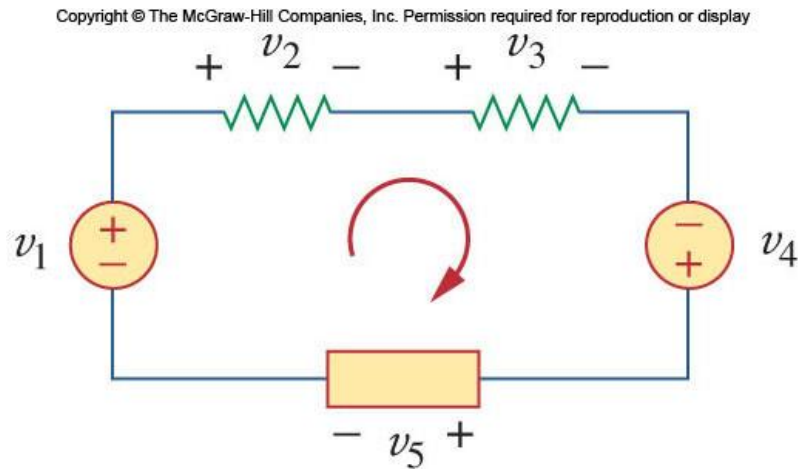
- The algebraic sum of all the **voltages** around any **loop** in a circuit equals zero.
- **Why?**





KVL Example

Three closed paths:

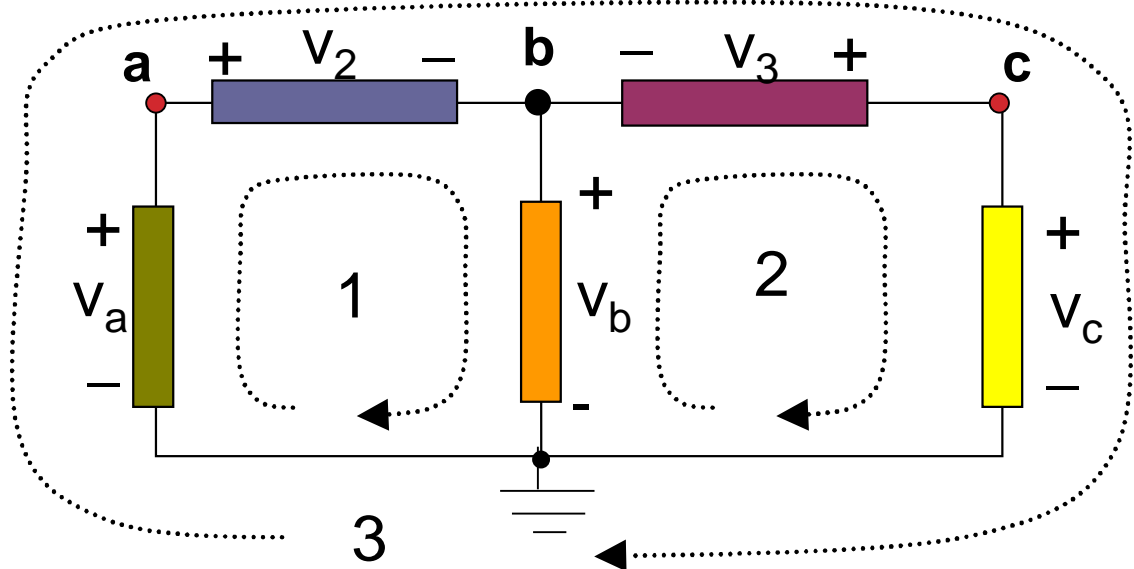

Path 1:


Path 2:

Path 3:




A Major Implication of KVL

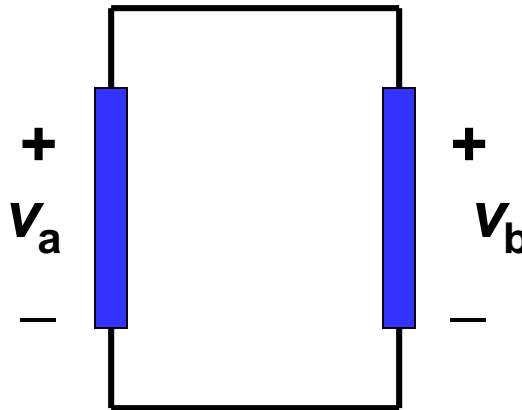- KVL tells us that **any set of elements which are connected at both ends carry the same voltage.**
- We say these elements are connected **in parallel**.






Series Resistors

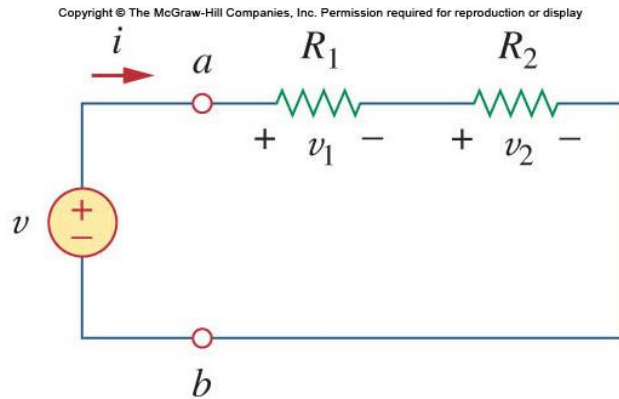


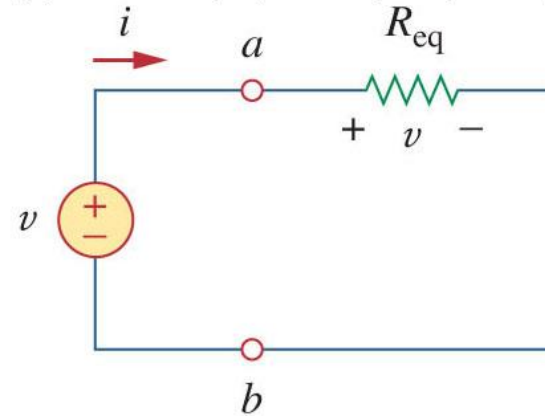Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display





Voltage Division


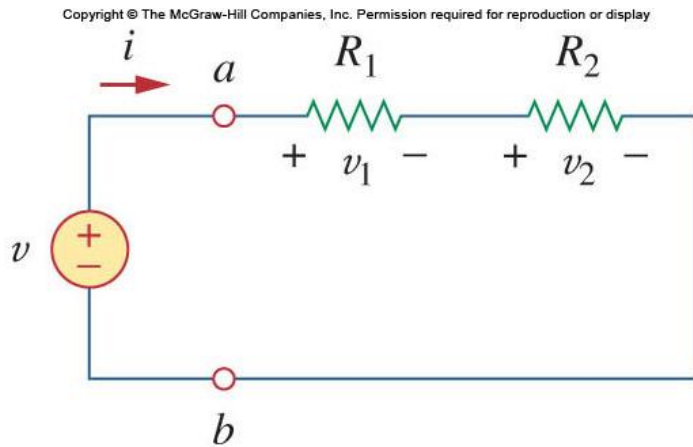


Three-terminal rheostat






Voltage Divider

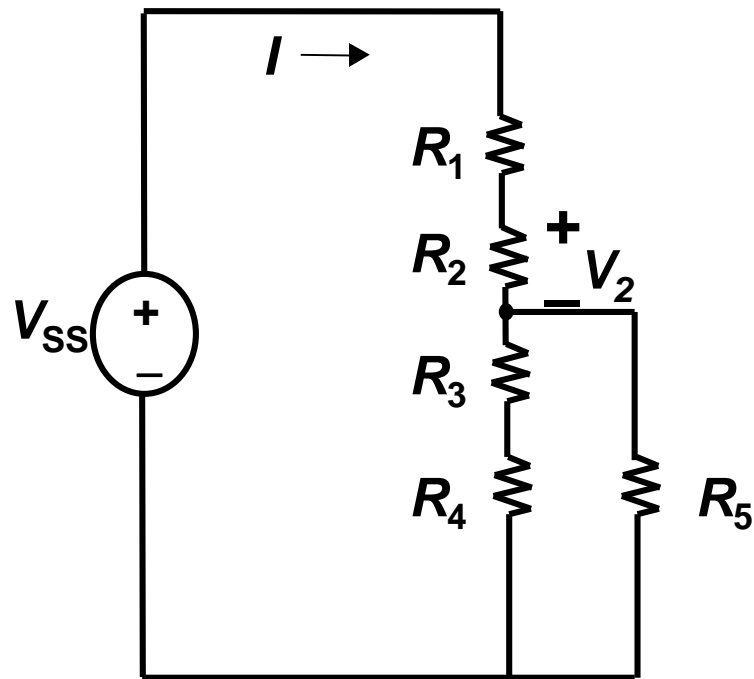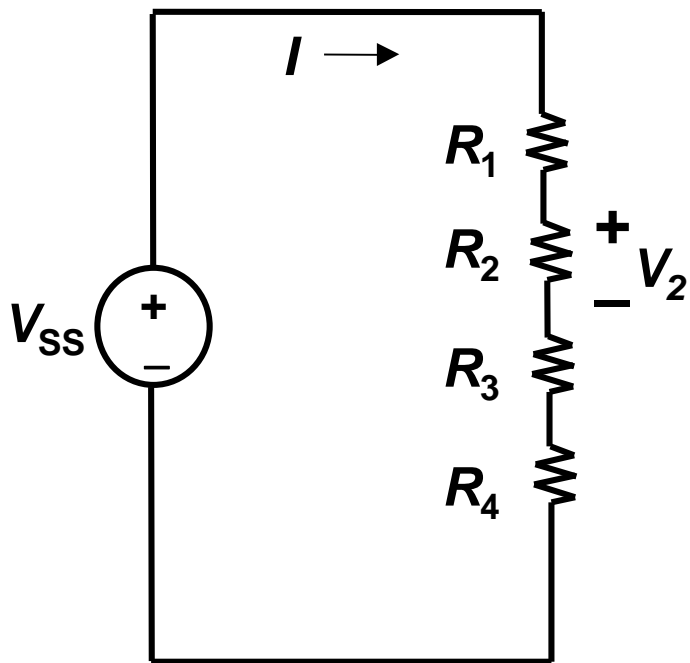




Parallel Resistors

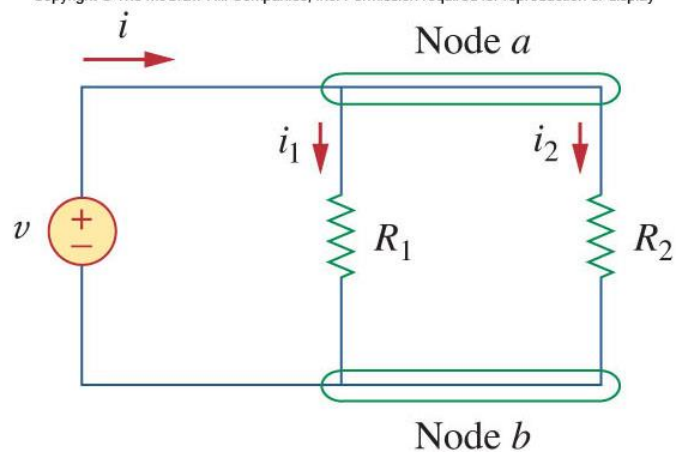Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display



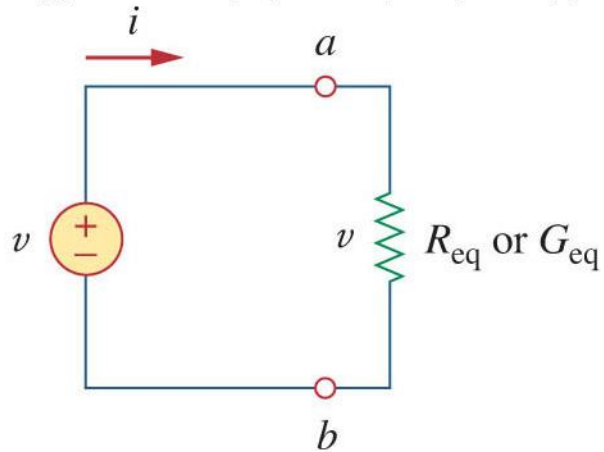
Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display





Current Division

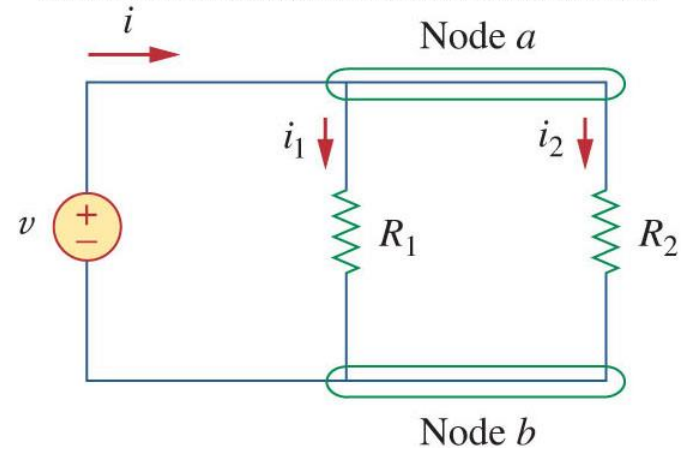Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display






Summary

- KCL and KVL


$$\sum_{n=1}^N i_n = 0$$

$$\sum_{m=1}^M v_m = 0$$

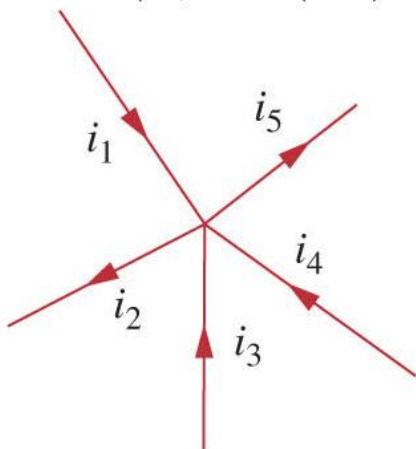Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display



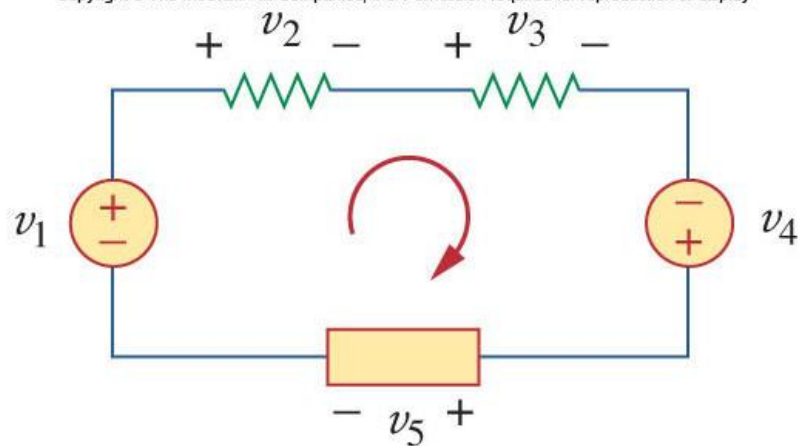
Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display








What you have learned

- KCL
- KVL
- Element relationships

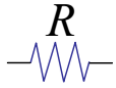For R, $V = IR$ 

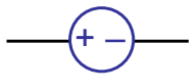For voltage source, $V = V_0$ 

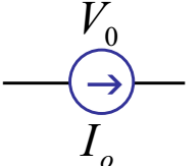For current source, $I = I_0$ 

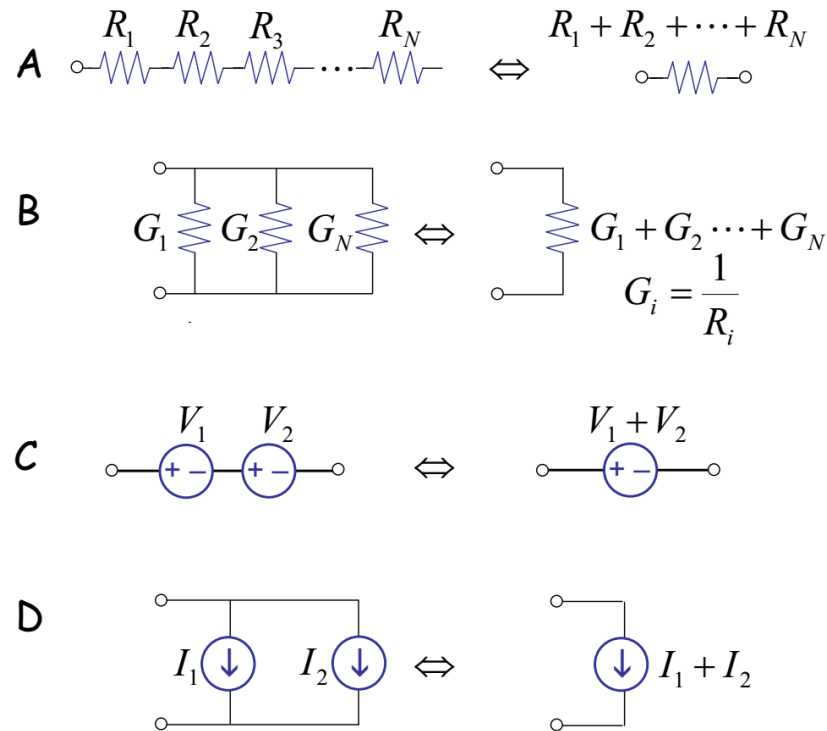



Outline

- Basic Laws
 - Ohm's Law
 - Kirchhoff's Laws -- KCL, KVL
- Circuit Analysis
 - Nodal Analysis
 - Mesh Analysis



Circuit Analysis

- Two techniques will be presented in this part:
 - Nodal analysis, which is based on **KCL**
 - Used in SPICE, the internal engine of circuit simulators.
 - Mesh analysis, which is based on **KVL**
- The analysis will result in a set of simultaneous equations which may be solved by Cramer's rule or computationally (using MATLAB for example)

<http://bwracs.eecs.berkeley.edu/Courses/IcBook/SPICE/>
<http://www.ni.com/white-paper/5413/zhs/>








Nodal Analysis – Three Steps

- Given a circuit with n nodes, the nodal analysis is accomplished via three steps:
 1. Select a node as the reference (i.e., ground) node. Assign the node voltages to the remaining **$(n-1)$** nodes. Voltages are relative to the reference node.
 2. Apply KCL to the **$(n-1)$** nodes, expressing branch current in terms of the node voltages (using the I - V relationships of branch elements).
 3. Solve the resulting simultaneous equations to obtain the unknown node voltages.




Nodal Analysis Example #1

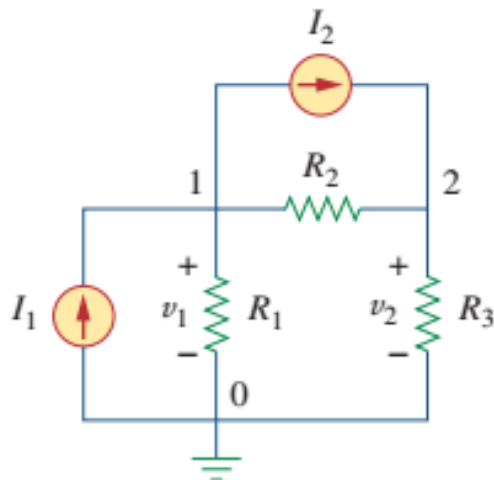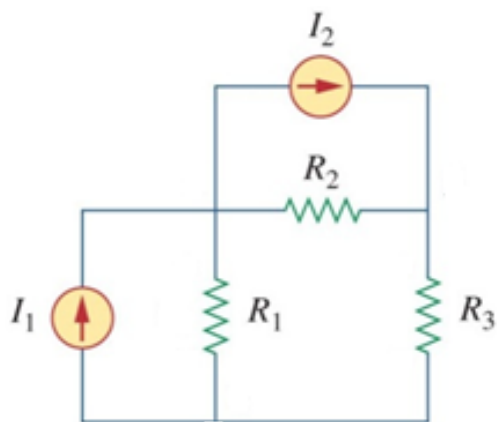

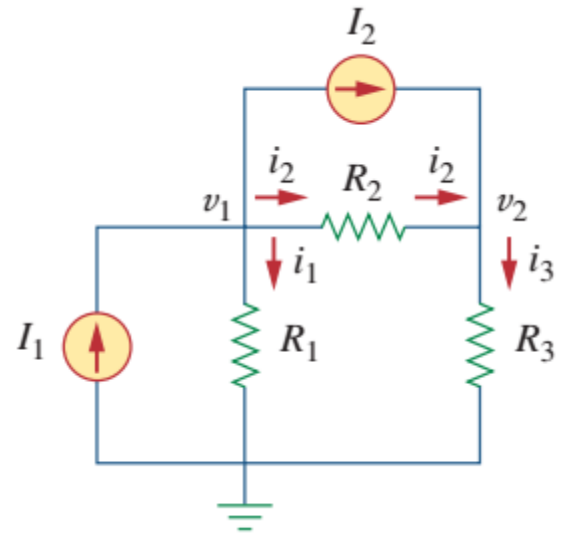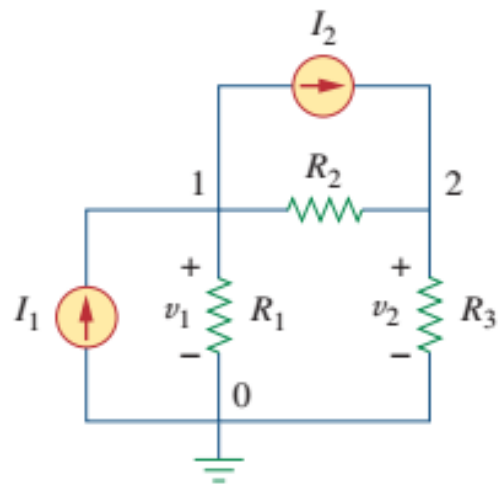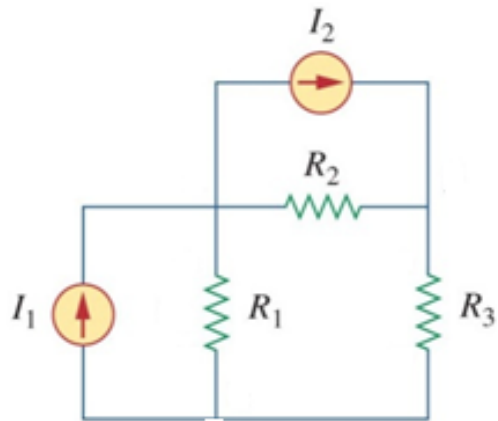





Nodal Analysis: Example #2

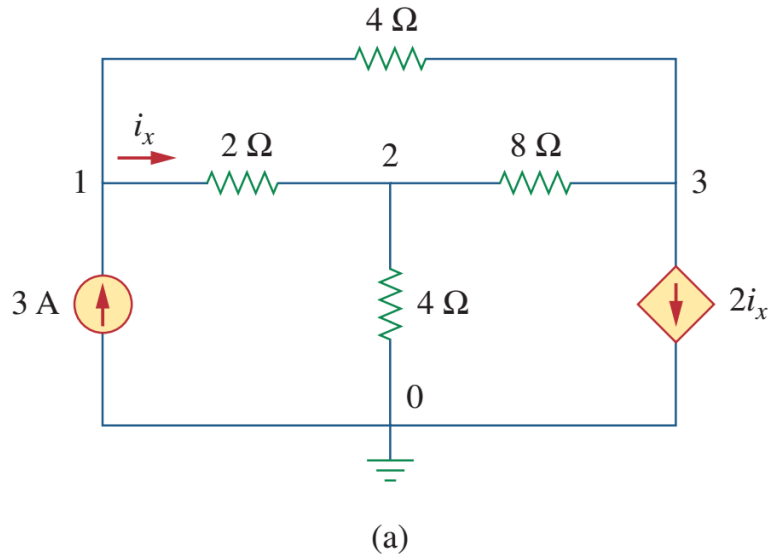




Nodal Analysis: Example #2

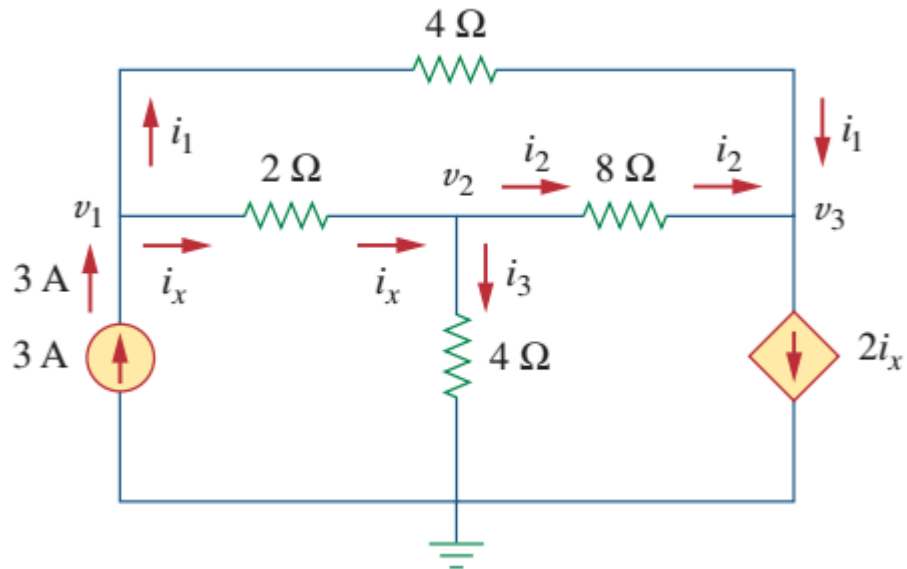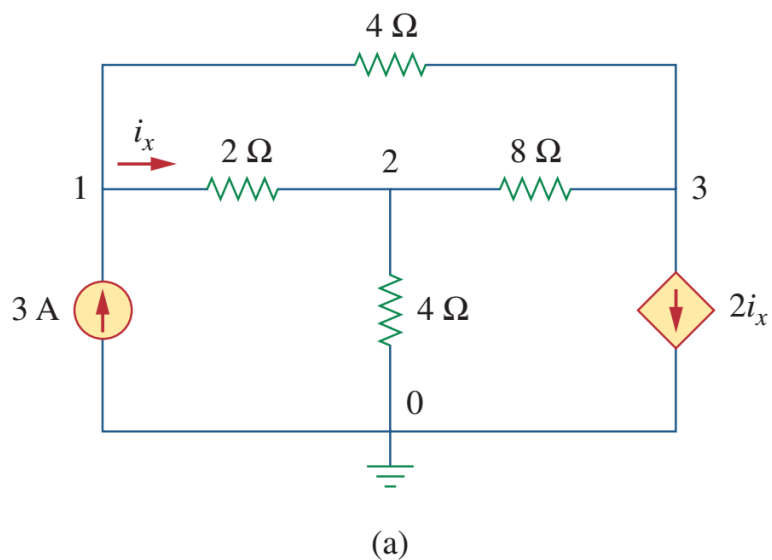



Nodal Analysis with Voltage Sources

Case I:

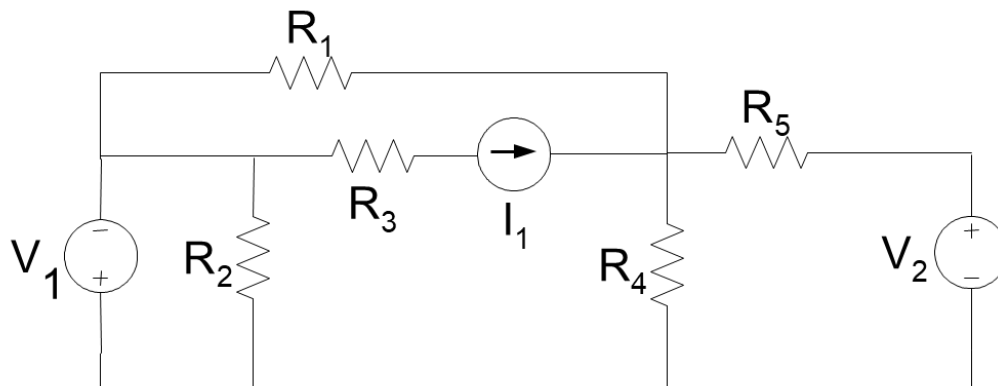




Nodal Analysis: Supernode

Case II

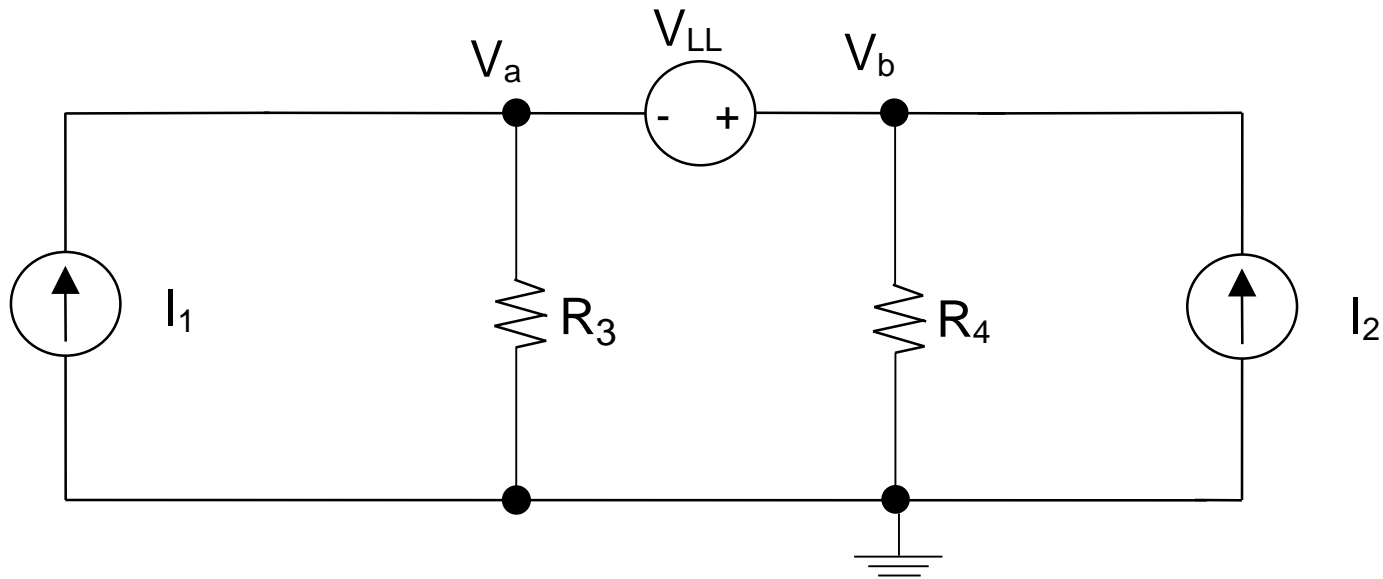A “floating” voltage source is one for which **neither** side is connected to the reference node, e.g. V_{LL} in the circuit below:




A supernode is formed by enclosing a (dependent or independent) voltage source connected between two nonreference nodes and any elements connected in parallel with it.



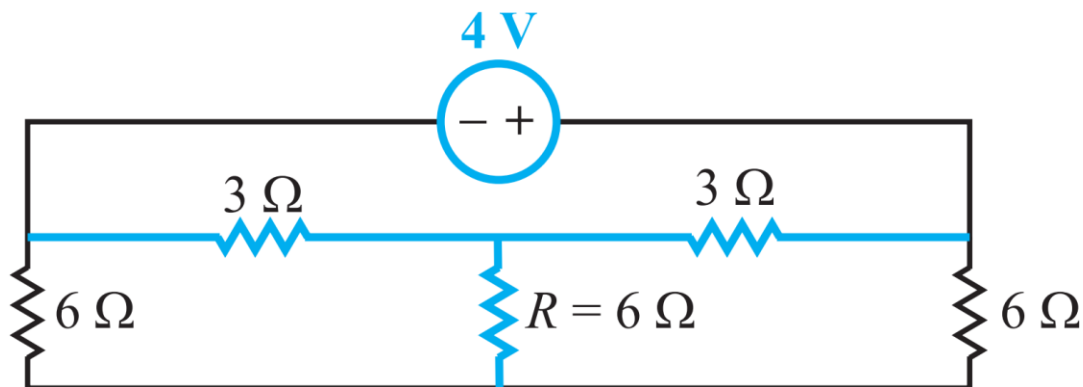Exercise


- Find the power supplied by the voltage source.





Mesh Analysis

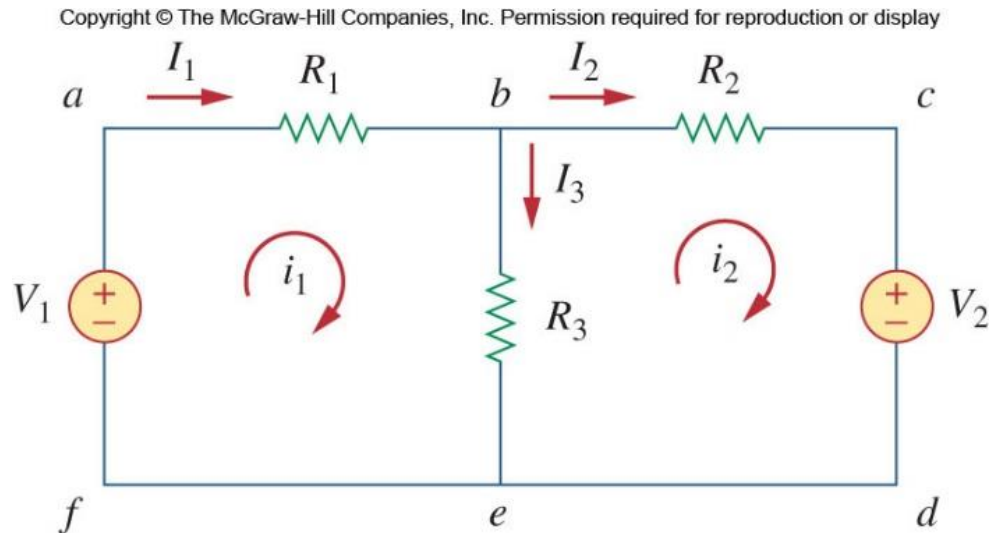- Another general procedure for analyzing circuits is to use the mesh currents as the circuit variables.




- Mesh analysis uses KVL to find unknown currents.

Loop, Independent Loop, Mesh

- A loop is a closed path with no node passed more than once.
- A loop is independent if it contains at least one branch which is not a part of any other independent loop.
- A mesh is a loop that does not contain any other loop within it.

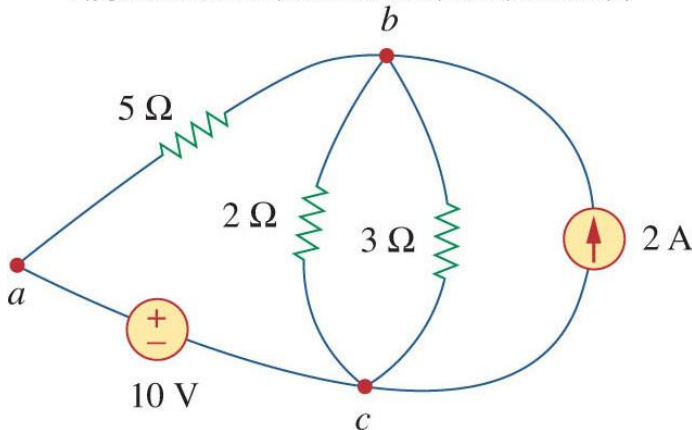Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display



- b – number of branches
- n – number of nodes
- l_{ind} – number of ind. loops


Mesh = Independent loop?

$$l_{ind} = b - (n - 1)$$




Mesh Analysis Steps

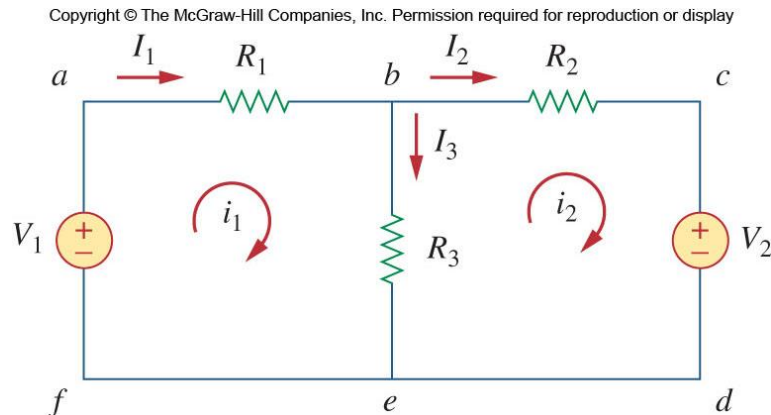- Mesh analysis follows these steps:
 1. Assign mesh currents i_1, i_2, \dots, i_x to the x meshes
 2. Apply KVL to each of the x mesh currents.
 3. Solve the resulting x simultaneous equations to get the mesh currents.






Example

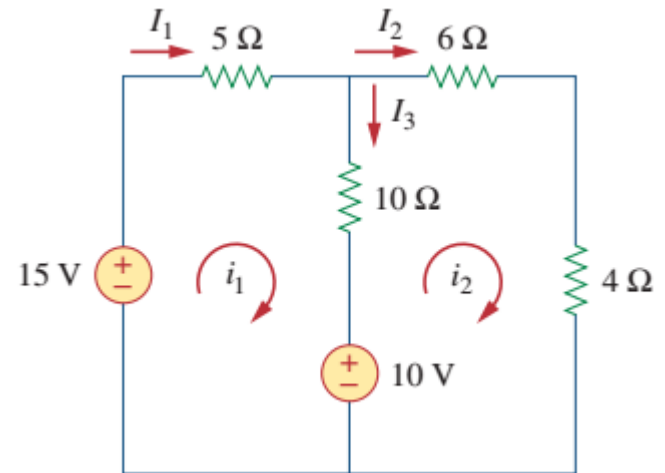


Mesh Analysis with Current Sources

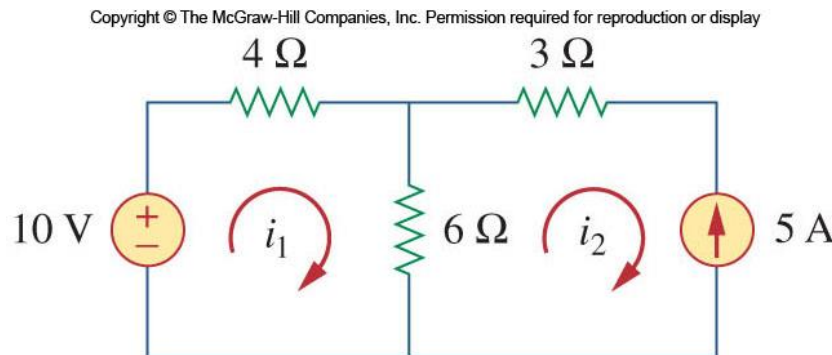- The presence of a current source makes the mesh analysis simpler in that it reduces the number of equations.
 - If the current source is located on only one mesh, the current for that mesh is defined by the source. For example:







If the current source is located...

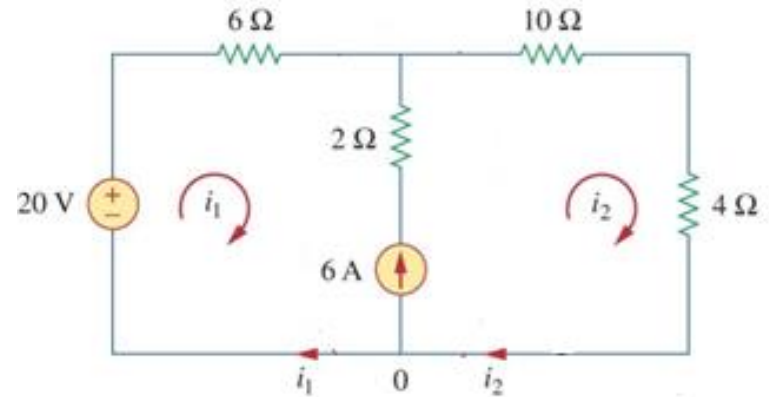




Supermesh

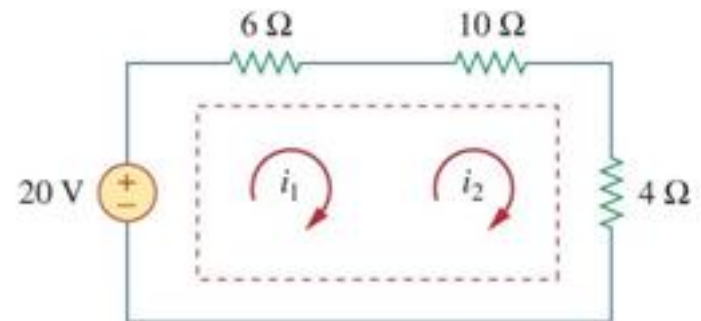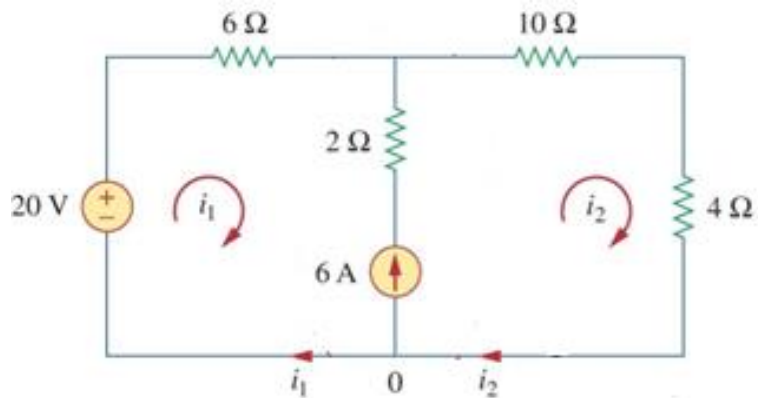

Summary


• Node Analysis

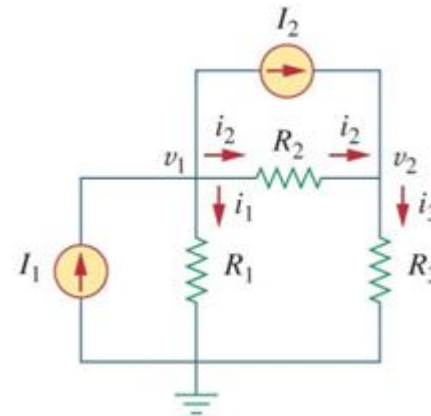- Node voltage is the unknown
- Solve by KCL
- Special case: Floating voltage source




• Mesh Analysis

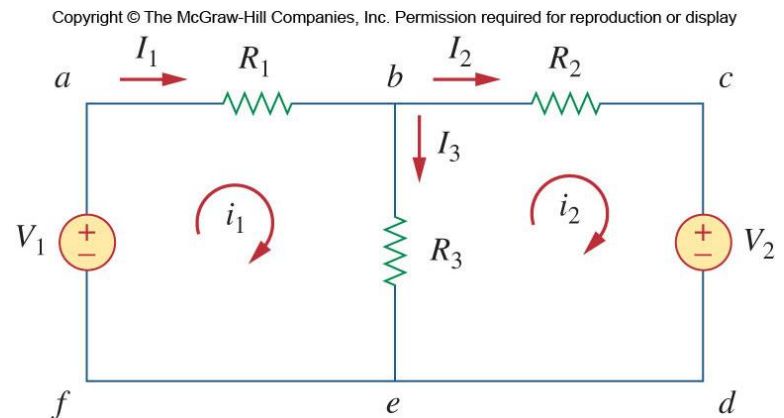- Loop current is the unknown
- Solve by KVL
- Special case: Current source





Application: DC Transistor Circuit

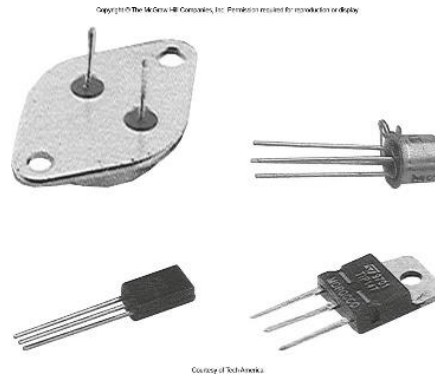- In general, there are two types of transistors commonly used: Field Effect (FET) and Bipolar Junction (BJT). Here we will use the approaches learned in this lecture to analyze a BJT circuit.



- A BJT is a three terminal device, where
 - The input current into one terminal (the base) affects the current flowing out of a second terminal (the collector).
 - The third terminal (the emitter) is the common terminal for both currents.

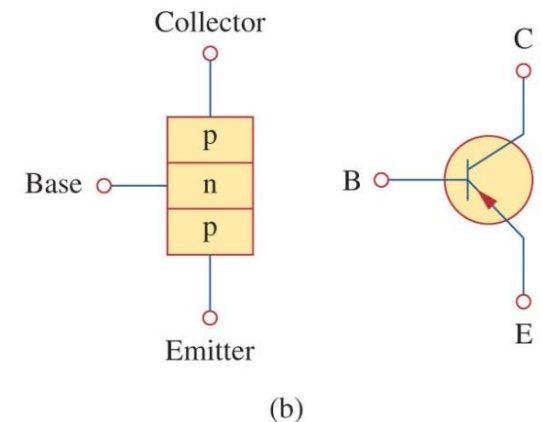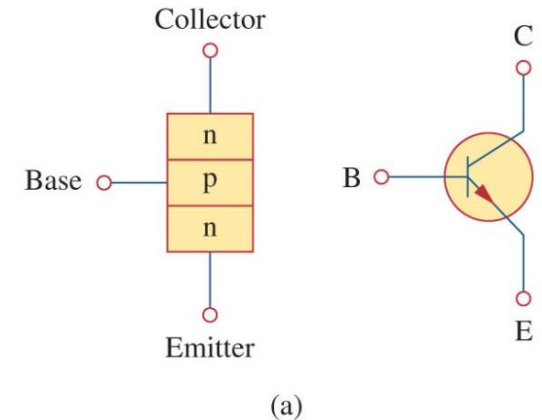Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display




KCL and KVL for a BJT

- The currents from each terminal can be related to each other as follows:
- The base and collector current can be related to each other by the parameter β , which can range from 50-1000

$$I_C = \beta I_B$$


- Applying KVL to the BJT gives:

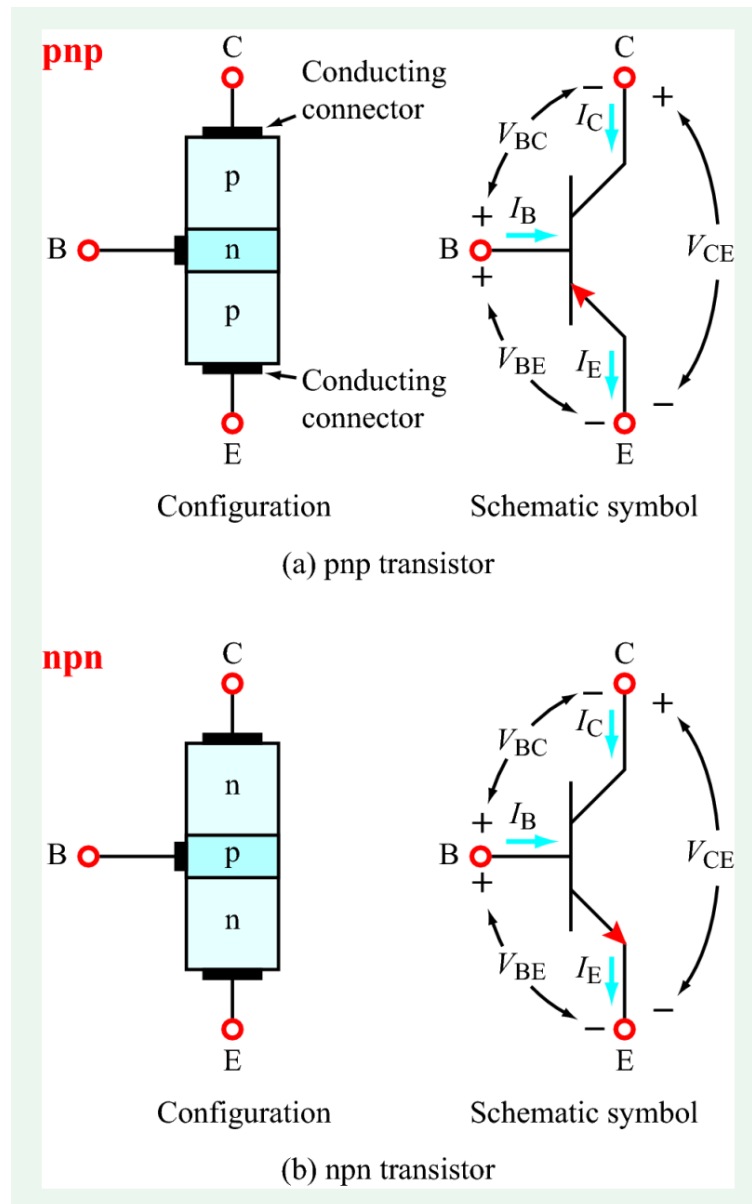



Analysis of a BJT Circuit

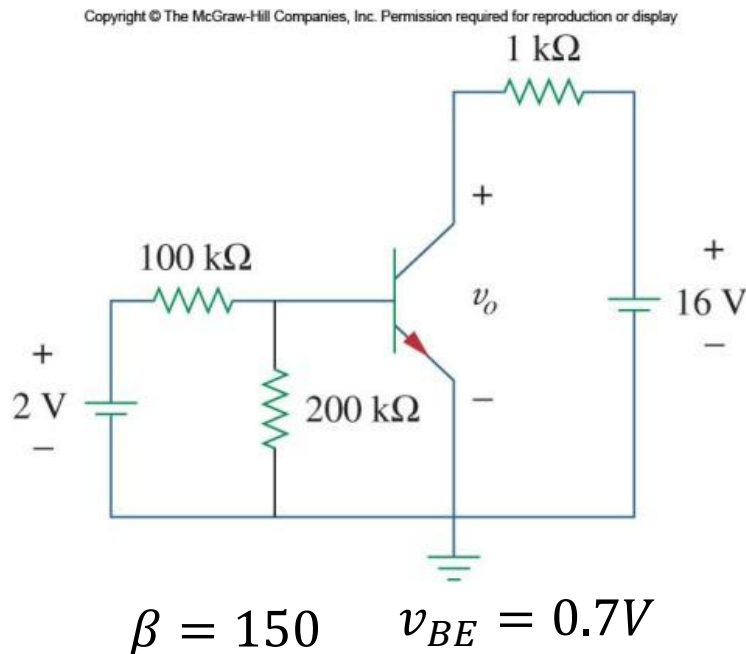- A transistor has a few operating modes depending on the applied voltages/currents. In this problem, we will be interested in the operation in “active mode”
 - the mode used for amplifying signals.






Mesh Analysis?


$$\beta = 150 \quad v_{BE} = 0.7V$$

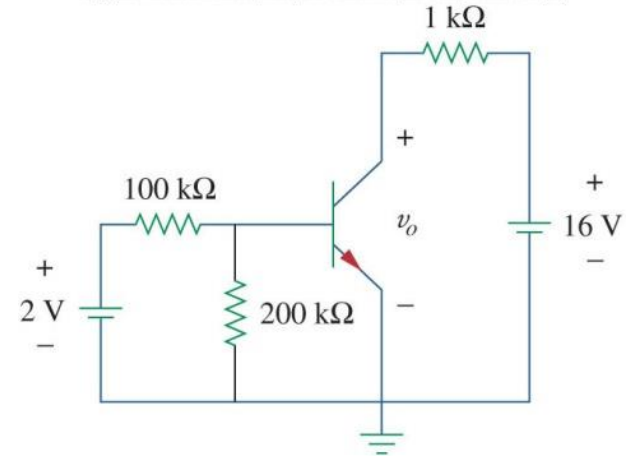Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display




DC model of a BJT

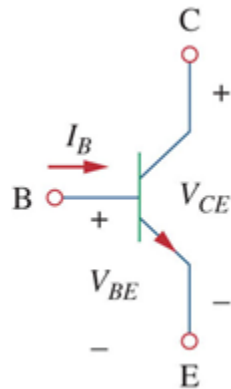- The figure below shows the equivalent DC model for a BJT in active mode.



$$I_C = \beta I_B$$

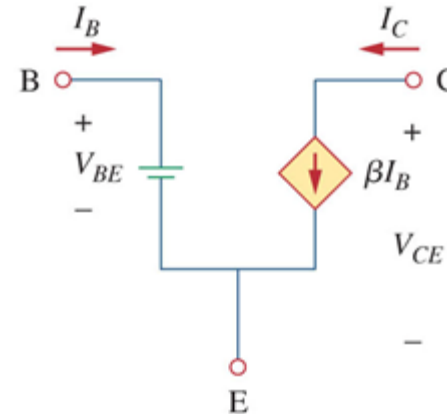


Note that nodal analysis can be applied after using this model.




Setting up a BJT circuit

$$\beta = 150$$

$$v_{BE} = 0.7V$$

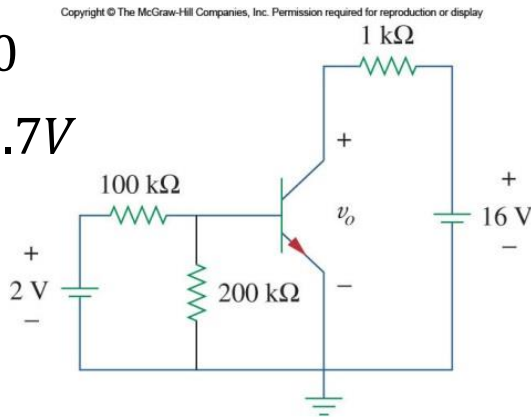

Original circuit

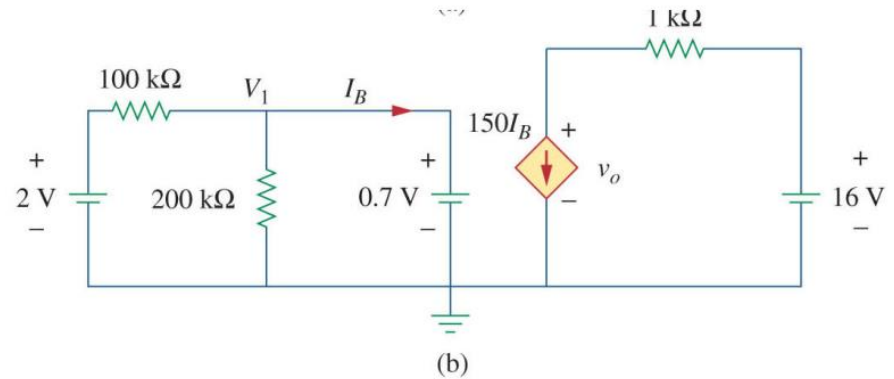

Circuit for nodal analysis