

EE 111 Homework 7

Due date: **May. 17th, 2019**

Turn in your homework in class


Rules:

- Work on your own. Discussion is permissible, but similar submissions will be judged as plagiarism.
- Please show all intermediate steps: a correct solution without an explanation will get zero credit.
- Please submit on time. No late submission will be accepted.
- Please prepare your submission in English only. No Chinese submission will be accepted.


1. (a) For the three coupled coils in Fig. (a), calculate the total inductance. 6'

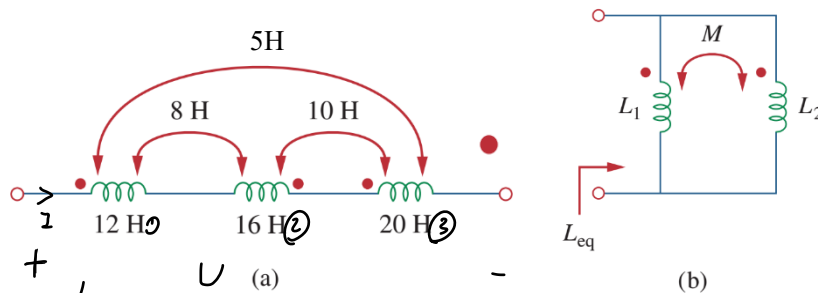(b) For the coupled coils in Fig. (b), show that 6'

$$L_{eq} = \frac{L_1 L_2 - M^2}{L_1 + L_2 - 2M}$$



(a) $U = I j\omega L_{eq}$

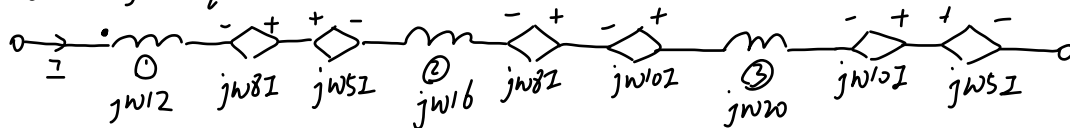


$$\therefore U = j\omega 12I - j\omega 8I + j\omega 5I + j\omega 16I - j\omega 8I - j\omega 10I + j\omega 20I - j\omega 10I + j\omega 5I$$

$$= j\omega 22I$$

$$\Rightarrow \underline{L_{eq} = 22H}$$

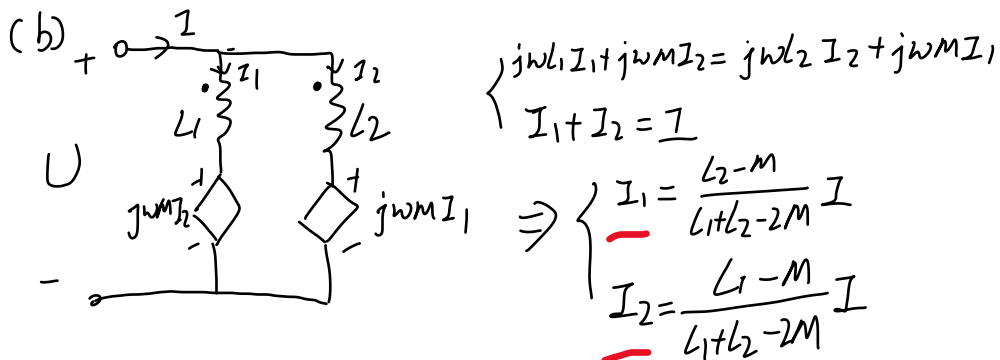Or (a) $L_{eq} = L_1 + L_2 + L_3 + 2M_{13} - 2M_{12} - 2M_{23} = 22H$ (6')



$$\therefore U = j\omega L_1 I_1 + j\omega M I_2$$

$$= j\omega \left(\frac{L_1(L_2 - M)}{L_1 + L_2 - 2M} + \frac{M(L_1 - M)}{L_1 + L_2 - 2M} \right) I = j\omega \frac{L_1 L_2 - M^2}{L_1 + L_2 - 2M} I$$


$$\therefore \underline{L_{eq} = \frac{L_1 L_2 - M^2}{L_1 + L_2 - 2M}}$$

2. With $i_s = 8\cos(600t)$ A and $V_s = 100\cos(600t + 60^\circ)$ V,

(a) find the coupling coefficient, **2'**

(b) use mesh analysis to find i_x , **6'**

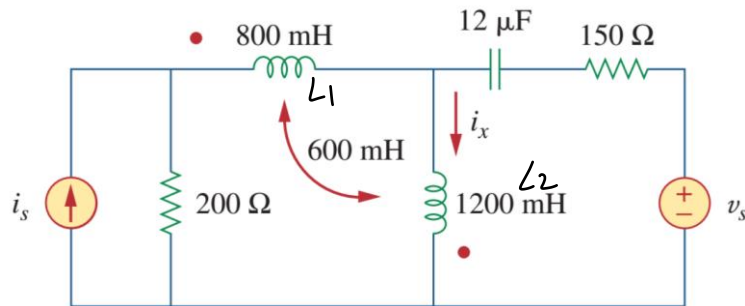(c) determine the energy stored in the coupled inductors at $t = 2$ s. **4'**



(a) $k = \frac{M}{\sqrt{L_1 L_2}} = \frac{\sqrt{6}}{4} = 0.6124 \approx 0.61$ **2'**


(b) $\omega = 600$ rad/s

$800\text{ mH} \leftrightarrow j480\Omega$

$600\text{ mH} \leftrightarrow j360\Omega$

$1200\text{ mH} \leftrightarrow j720\Omega$

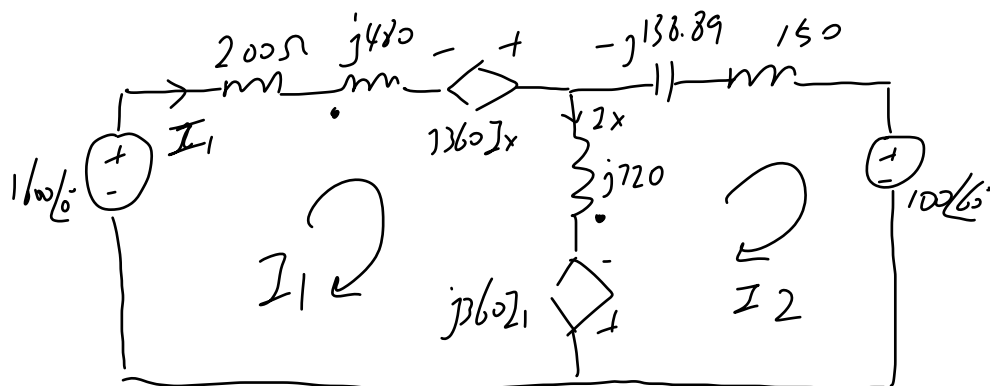$12\mu\text{F} \leftrightarrow -j138.89\Omega$



$I_x = I_1 - I_2$

Mesh ①: $-1600 + 200I_1 + j480I_1 - j360(I_1 - I_2) + j720(I_1 - I_2) - j360I_1 = 0$ **2'**

Mesh ②: $(-j138.89 + 150)I_2 + 100\angle 60^\circ + j360I_1 + j720(I_2 - I_1) = 0$ **2'**

$\Rightarrow \begin{cases} -1600 + (200 + j480)I_1 - j360I_2 = 0 \\ (j720 - j138.89 + 150)I_2 - j360I_1 + 100\angle 60^\circ = 0 \end{cases} \Rightarrow \begin{cases} I_1 = 2.30 - 3.22j = 4.27 \angle -48.99^\circ \\ I_2 = 1.95 - 1.40j = 2.40 \angle -35.68^\circ \end{cases}$

$\therefore I_x = I_1 - I_2 = 0.35 - 1.82j = 2.01 \angle -64.97^\circ$ A

$\therefore i_x = 2.01 \cos(600t - 64.97^\circ)$ A **2'**


(c) $t = 2$ s. $i_x = 2.01 \cos(600 \cdot 2 - 64.97^\circ) = 0.69$ A, $i_1 = 4.17 \cos(600 \cdot 2 - 48.99^\circ) = 2.51$ A **1'**

$\therefore W_{L_1 \leftrightarrow L_2} = \frac{1}{2} L_1 i_1^2 + \frac{1}{2} L_2 i_x^2 - M i_1 \cdot i_x = \frac{1}{2} 0.8 (2.51)^2 + \frac{1}{2} 12 (0.69)^2 - 0.6 (2.51)(0.69)$
2' $= 1.77$ J

3、 For the network in the figure, find

(a) the complex power supplied by the source,

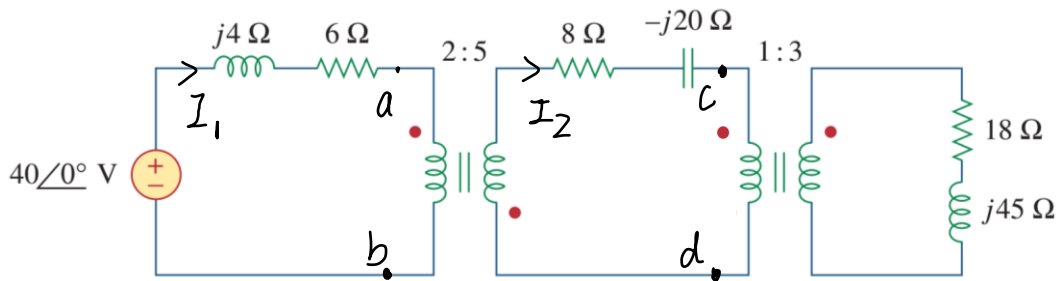(b) the average power delivered to the 8-Ω resistor.



$$(a) \quad Z_{cd} = \frac{18 + j45}{\left(\frac{3}{1}\right)^2} = 2 + j5 \quad 2'$$

$$Z_{ab} = \frac{8 - j20 + Z_{cd}}{\left(\frac{5}{2}\right)^2} = 1.6 - 2.4j \quad 2'$$

$$\therefore I_1 = \frac{40\angle 0^\circ}{j4 + 6 + Z_{ab}} = \frac{40\angle 0^\circ}{7.6 + 1.6j} = 5.04 - 1.06j = 5.15 \angle -11.89^\circ \text{ A} \quad 2'$$


$$\therefore S = \frac{1}{2} 40\angle 0^\circ \cdot I_1^* = \frac{1}{2} 40\angle 0^\circ 5.15 \angle 11.89^\circ = 103 \angle 11.89^\circ \text{ VA} \quad 2'$$

$$(b) \quad \therefore \frac{I_2}{I_1} = -\frac{2}{5}$$

$$\therefore I_2 = -0.4 I_1 = -0.4 \cdot 5.15 \angle -11.89^\circ = -2.06 \angle -11.89^\circ \text{ A} \quad 2'$$

$$\therefore P_{8-\Omega} = \frac{1}{2} |I_2|^2 \cdot 8 = 16.97 \text{ W} \quad 2'$$

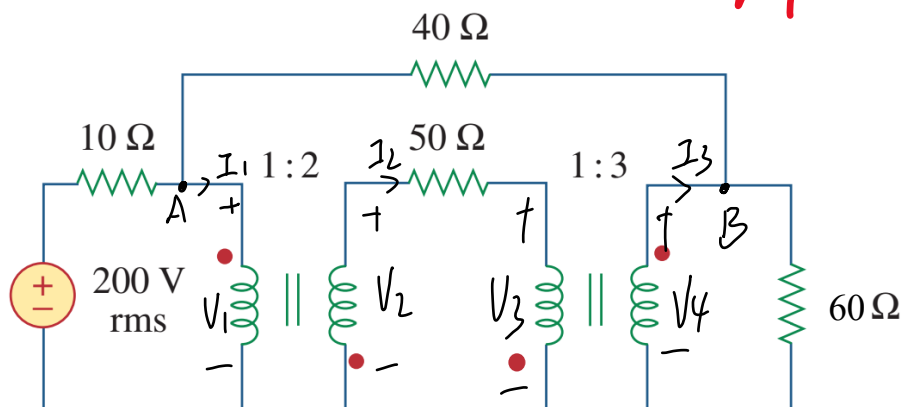4. Calculate the average power dissipated by the 40Ω resistor.



Nodal analysis.

$$\text{Node A: } \frac{V_1 - 200}{10} + \frac{V_1 - V_4}{40} + I_1 = 0$$

$$\text{Node B: } \frac{V_4 - V_1}{40} + \frac{V_4}{60} - I_3 = 0$$

$$V_2 \Leftrightarrow V_3: I_2 = \frac{V_2 - V_3}{50}$$


$$\text{transformers: } \frac{V_2}{V_1} = -\frac{2}{1} \quad \frac{I_2}{I_1} = -\frac{1}{2}$$

$$\frac{V_4}{V_3} = -\frac{3}{1} \quad \frac{I_3}{I_2} = -\frac{1}{3}$$

$$\begin{aligned} I_1 &= 7.97 \text{ A} \\ I_2 &= -3.99 \text{ A} \\ I_3 &= 1.33 \text{ A} \\ V_1 &= 116.61 \text{ V} \\ V_2 &= -233.21 \text{ V} \\ V_3 &= -33.95 \text{ V} \\ V_4 &= 101.85 \text{ V} \end{aligned}$$

$$\therefore P_{40\Omega} = \frac{(V_1 - V_4)^2}{40} = \frac{14.76^2}{40} = 5.45 \text{ W}$$

Mesh Analysis.

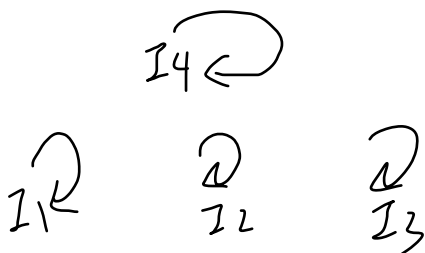

$$\text{Mesh 1: } -200 + 10I_1 + V_1 = 0$$

$$\text{Mesh 2: } -V_2 + 50(I_2 - I_4) + V_3 = 0$$

$$\text{Mesh 3: } -V_4 + 60I_3 = 0$$

$$\text{Mesh 4: } 40I_4 + V_4 - V_3 + 50(I_4 - I_2) + V_2 - V_1 = 0$$

$$\text{Transformers: } \frac{V_2}{V_1} = -\frac{2}{1} \quad \frac{I_2 - I_4}{I_1 - I_4} = -\frac{1}{2}$$

$$\frac{V_4}{V_3} = -\frac{3}{1} \quad \frac{I_3 - I_4}{I_2 - I_4} = -\frac{1}{3}$$

$$\begin{aligned} I_1 &= 8.34 \text{ A} \\ I_2 &= -3.62 \text{ A} \\ I_3 &= 1.70 \text{ A} \\ I_4 &= 0.37 \text{ A} \\ V_1 &= 116.61 \text{ V} \\ V_2 &= -233.21 \text{ V} \\ V_3 &= -33.95 \text{ V} \\ V_4 &= 101.85 \text{ V} \end{aligned}$$

$$P_{40\Omega} = I_4^2 40 = 0.37^2 40 = 5.48 \text{ W}$$

$$\text{or } P_{40\Omega} = I_4^2 40 = 0.369^2 40 = 5.45 \text{ W}$$

5. Sketch the Bode plots for

$$G(s) = \frac{s}{(s+2)^2(s+1)}, \quad s = j\omega$$


5. Solution:

$$G(\omega) = \frac{(1/4)j\omega}{(1+j\omega)(1+j\omega/2)^2}$$


$$G_{dB} = -20\log_{10} 4 + 20\log_{10} |j\omega| - 20\log_{10} |1+j\omega| - 40\log_{10} |1+j\omega/2|$$

$$\phi = 90^\circ - \tan^{-1}\omega - 2\tan^{-1}\omega/2$$

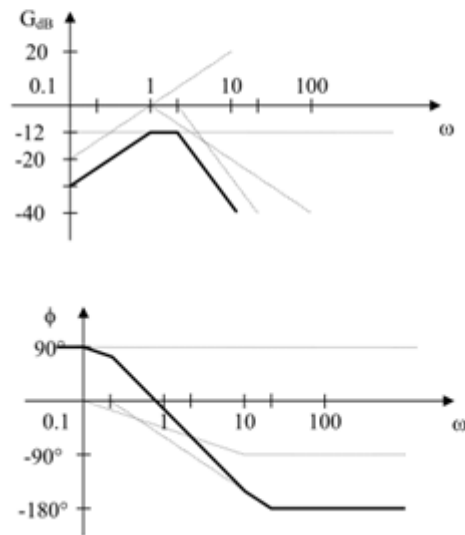
The magnitude and phase plots are shown below.



MATLAB:

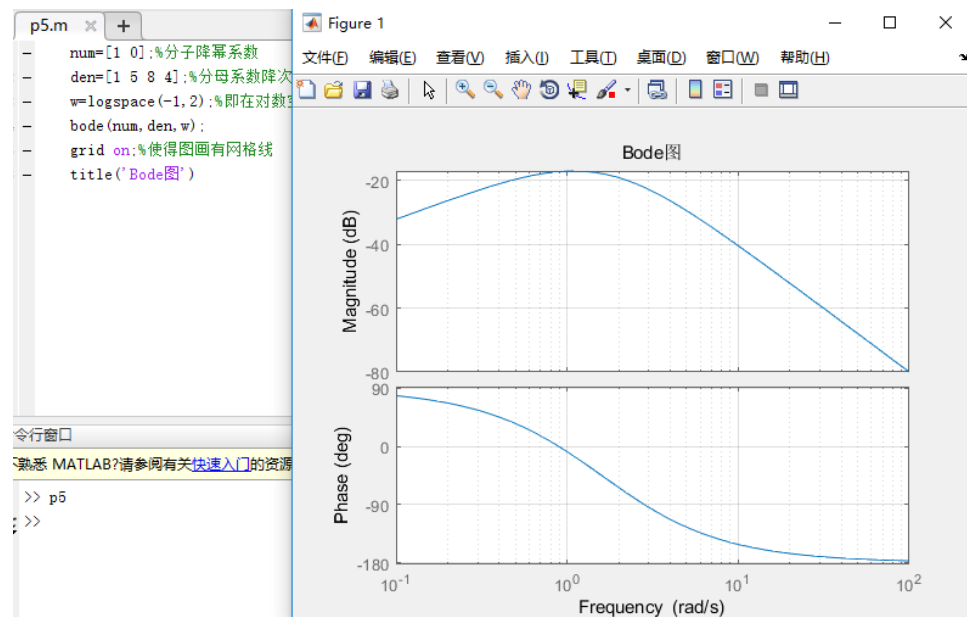

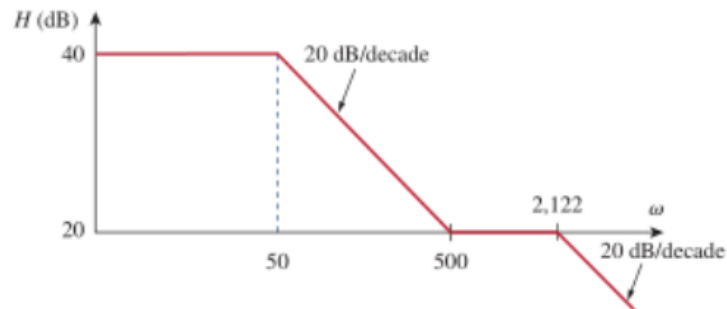6. The magnitude plot below represents the transfer function of a preamplifier. Find $H(s)$.



6.Solution

$$40 = 20 \log_{10} K \longrightarrow K = 100$$

There is a pole at $\omega=50$ giving $1/(1+j\omega/50)$

There is a zero at $\omega=500$ giving $(1 + j\omega/500)$.

There is another pole at $\omega=2122$ giving $1/(1 + j\omega/2122)$.

Thus,

$$H(\omega) = \frac{100(1 + j\omega/500)}{(1 + j\omega/50)(1 + j\omega/2122)} = \frac{100 \times \frac{1}{500} (s + 500)}{\frac{1}{50} \times \frac{1}{2122} (s + 50)(s + 2122)}$$


or

$$H(s) = \frac{21220(s + 500)}{(s + 50)(s + 2122)}$$

➤ Hint:


- $H(S) = \frac{-21220(S+500)}{(S+50)(S+2122)}$ is also correct.
- One solution gets full marks.

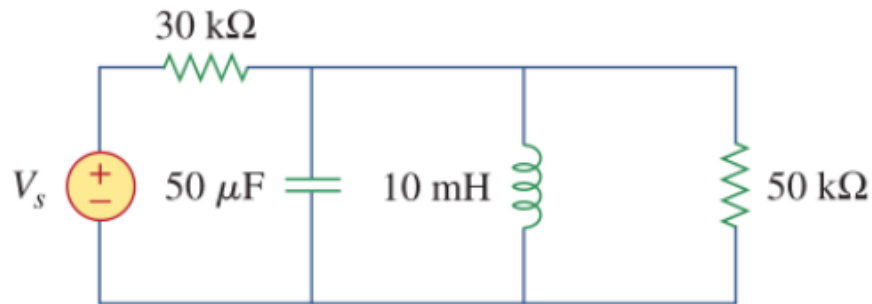7. For the circuit shown, find ω_0 , B, and Q, as seen by the voltage across the inductor.



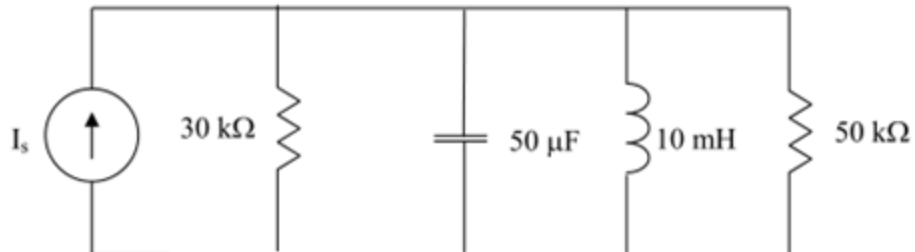7.Solution:

Convert the voltage source to a current source as shown below.



$$R = 30 // 50 = \frac{30 \times 50}{80} = 18.75\text{ k}\Omega$$

This is a parallel resonant circuit.

$$\omega_o = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{10 \times 10^{-3} \times 50 \times 10^{-6}}} = \underline{1414.21\text{ rad/s}}$$

$$B = \frac{1}{RC} = \frac{1}{18.75 \times 10^3 \times 50 \times 10^{-6}} = \underline{1.067\text{ rad/s}}$$


$$Q = \frac{\omega_o}{B} = \frac{1414.21}{1.067} = \underline{1325.41}$$

8. For the circuit below, $R=50\Omega$, $L_1=5\text{mH}$, $L_2=20\text{mH}$, $C_2=1\mu\text{F}$, when the frequency

of voltage source $f = \frac{10^4}{2\pi}$ Hz, R , L_1 , C_1 is in resonance as observed between Points

A and B.

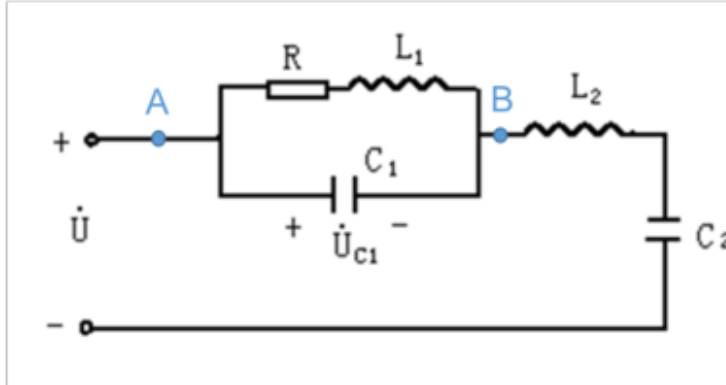At this moment, the voltage U_{C1} of capacitor C_1 is 10 V ($U_{C1}=10\text{ V}$). Please find C_1 and $U(\text{rms})$.



8.Solution: when R , L_1 , C_1 is resonance, the

resonance angular frequency is: $\omega_1 = 2\pi f = 2\pi \times \frac{10^4}{2\pi} = 10^4$ Hz

$$Y_1 = \frac{1}{R + j\omega_1 L_1} + j\omega_1 C_1 = \left[\frac{R}{R^2 + (\omega_1 L_1)^2} \right] + j \left[\omega_1 C_1 - \frac{\omega_1 L_1}{R^2 + (\omega_1 L_1)^2} \right]$$

$$I_m[Y_1] = 0, \quad \omega_1 C_1 - \frac{\omega_1 L_1}{R^2 + (\omega_1 L_1)^2} = 0$$

$$\therefore C_1 = \frac{L_1}{R^2 + (\omega_1 L_1)^2} = 10^{-6} \text{ F} = 1\mu\text{ F}$$

$$Z = \frac{1}{\text{Re}[Y_1]} + j\omega_1 L_2 + \frac{1}{j\omega_1 C_2} = \frac{R^2 + (\omega_1 L_1)^2}{R} + j(\omega_1 L_2 - \frac{1}{\omega_1 C_2}) = 100(1 + j)$$

$$R_1 = \frac{1}{\text{Re}[Y_1]} = 100\Omega \quad I = \frac{U_{C1}}{R_1} = \frac{10\text{ V}}{100\Omega} = 0.1\text{ A}$$

$$U = I \cdot Z = 0.1 \times 100(1 + j) = 10(1 + j) \text{ V} = 10\sqrt{2}\angle 45^\circ \text{ V}$$

$$\dot{U} = 20 \cos(\omega t + 45^\circ) \text{ V} \quad \therefore U = \frac{20}{\sqrt{2}} = \sqrt{2} \times 10 = 14.14 \text{ V}$$