



Lecture 15

-- Laplace Transform in Circuit Analysis



Introduction

- In this lecture, we introduce the concept of modeling circuits in the s domain **using the Laplace transform**.
- The elegance of using the Laplace transform in circuit analysis lies in (1) transforming the differential equation into an *algebraic* equation; and (2) automatic inclusion of initial conditions in the transformation process, thus providing a complete (transient and steady-state) solution.



Steps in Applying the Laplace transform

- Transform the circuit from the time domain to the Laplace (s) domain, including possible initial conditions.
- Solve the circuit using nodal analysis, mesh analysis, source transformation, superposition, or any other analysis technique with which we are familiar.
- Take the inverse transform of the solution and thus obtain the solution in the time domain.



V-I relations of R,L,C

• R $U_R(s) = RI_R(s)$

• C
$$V(s) = \frac{1}{sC} I(s) + \frac{V_0}{s}$$

$$I(s) = sCV(s) - CV_0$$


• L
$$I(s) = \frac{1}{sL} V(s) + \frac{I_0}{s}$$

$$V(s) = sLI(s) - LI_0$$



S-domain circuit models for a capacitor


s-Domain Circuit Models

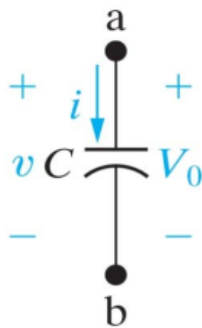


$$i(t) = C \frac{dv(t)}{dt}$$

For a capacitor
(with initial conditions)

$$I(s) = sCV(s) - CV_0$$

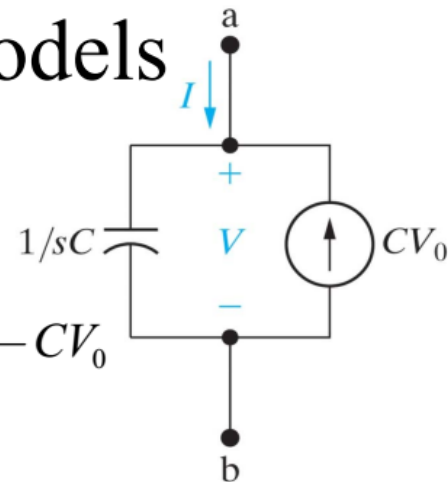

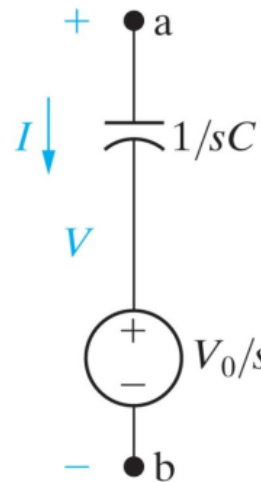
$$V(s) = \frac{1}{sC} I(s) + \frac{V_0}{s}$$



S-domain circuit models for an inductor

s-Domain Circuit Models

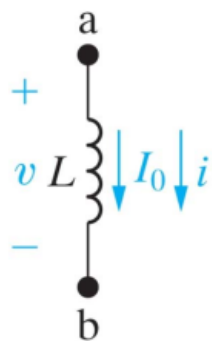


For an inductor
(with initial conditions)


$$v(t) = L \frac{di(t)}{dt}$$



$$V(s) = sLI(s) - LI_0$$

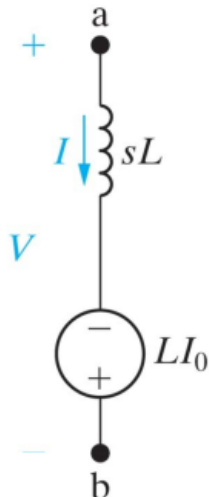



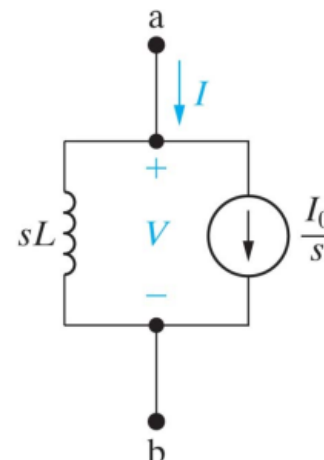
$$I(s) = \frac{1}{sL} V(s) + \frac{I_0}{s}$$










Summary

Time domain

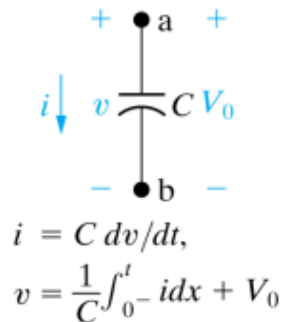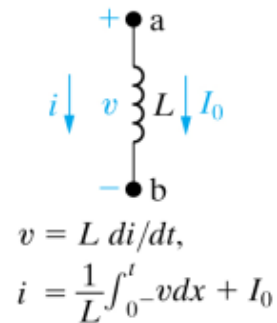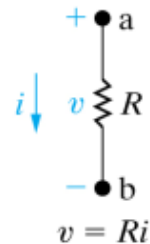

s-domain

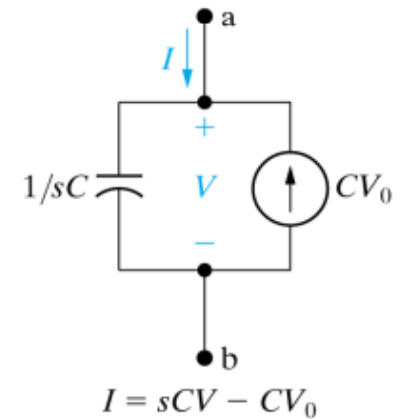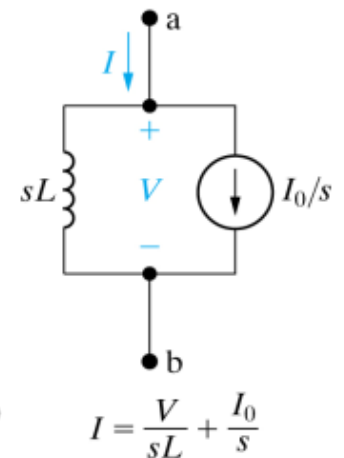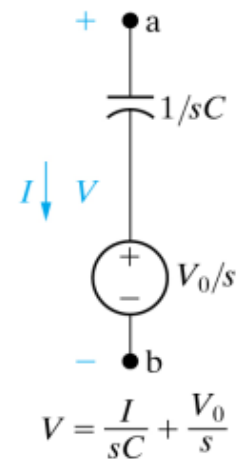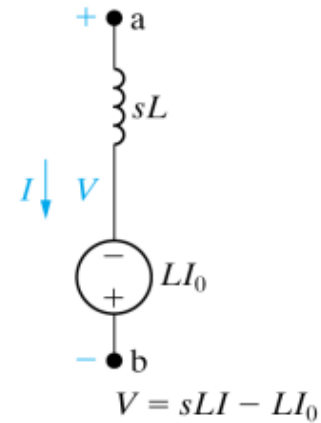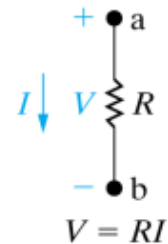



Dependent Sources

- The models for dependent sources are easy to develop, drawing from the simple fact that if the Laplace transform of $f(t)$ is $F(s)$, then the Laplace transform of $af(t)$ is $aF(s)$ — the linearity property.

$$\mathcal{L}[av(t)] = aV(s)$$

$$\mathcal{L}[ai(t)] = aI(s)$$




Steps in Applying the Laplace transform

- Transform the circuit from the time domain to the Laplace (s) domain, including possible initial conditions.
- Solve the circuit using nodal analysis, mesh analysis, source transformation, superposition, or any other analysis technique with which we are familiar.
- Take the inverse transform of the solution and thus obtain the solution in the time domain.



Example 1

Assuming no initial energy storage, find $i_1(t)$ and $i_2(t)$ for $t > 0$.

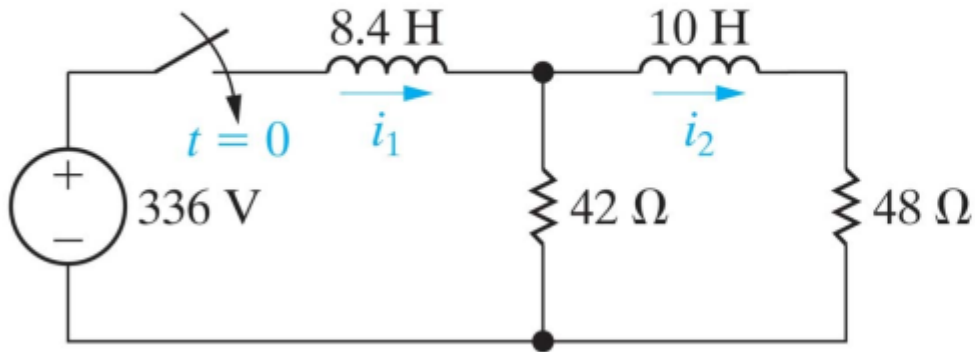






Example 2


Determine $v_o(t)$ for $t > 0$ assuming zero initial conditions:

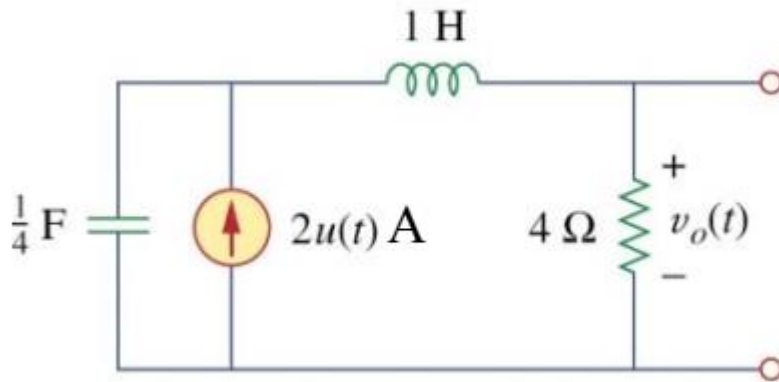



Example 3

- The switch has been in position b for a long time. It is moved to position a at $t = 0$. Determine $v(t)$ for $t > 0$.

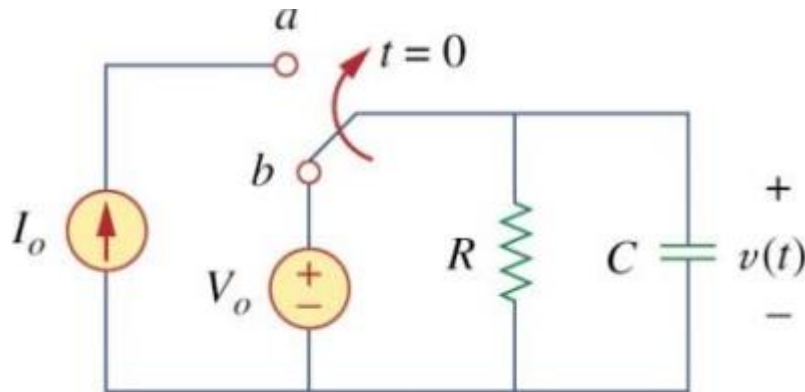




Example 4



- Find (1) the voltage across the capacitor
(2) current through the inductor

assuming that $v_s(t) = 10u(t)$ V, and assume that at $t = 0$, -1 A flows through the inductor and +5 V is across the capacitor.

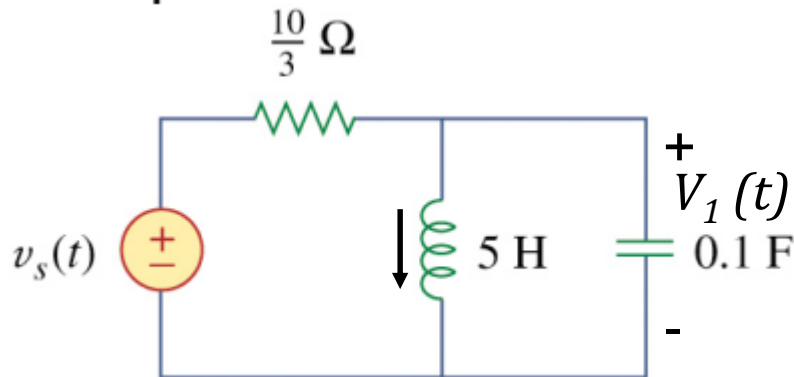

Example 4


- Find (1) the voltage across the capacitor
(2) current through the inductor
assuming that $v_s(t) = 10u(t)$ V, and assume that at $t = 0$, -1 A flows through the inductor and +5 V is across the capacitor.

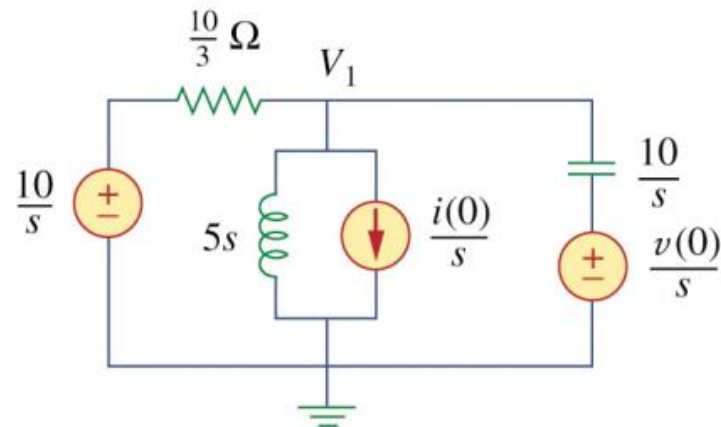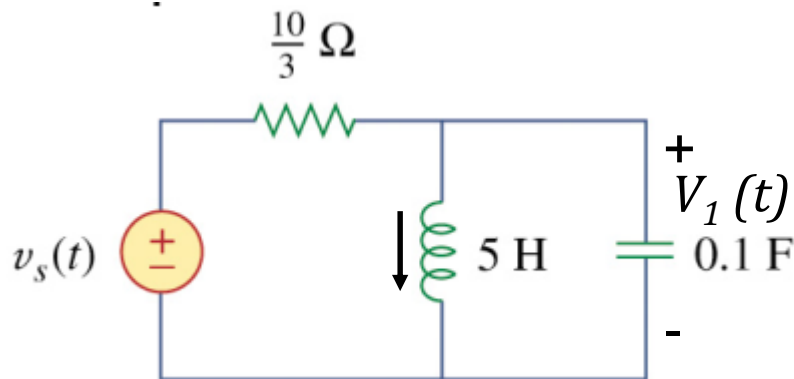



Example 5

- Use Thevenin's equivalent circuit w.r.t terminals a - b to find current $i_C(t)$.

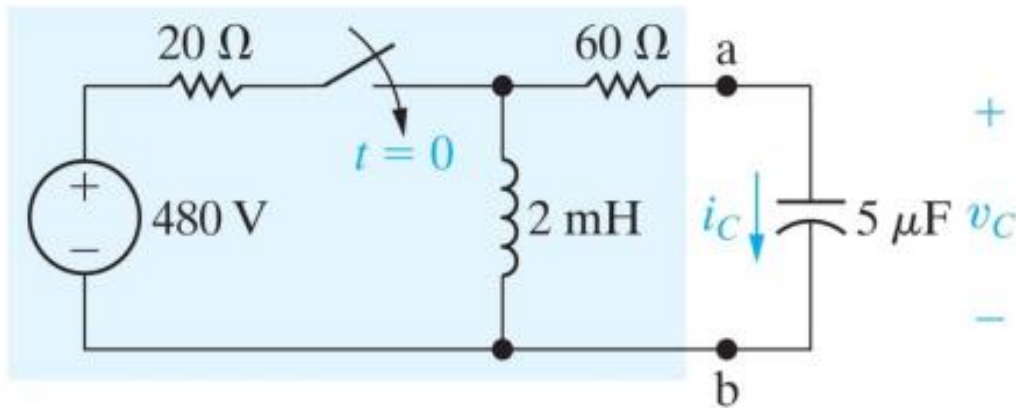






Example 6


- Find $v_o(t)$

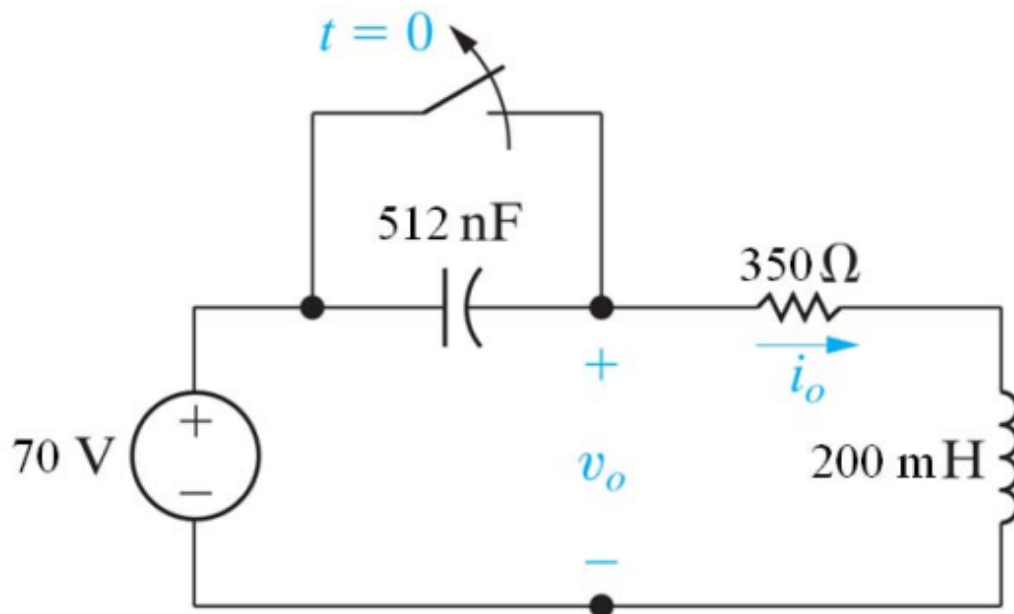





Example 7

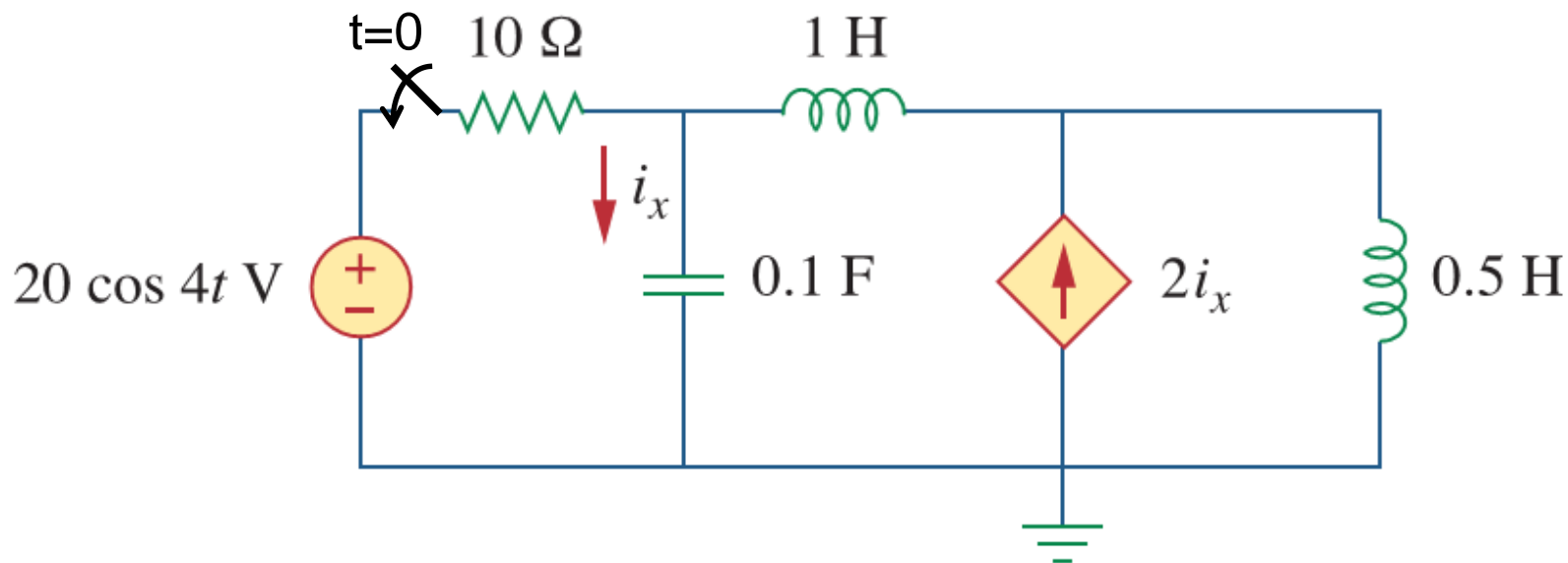- Example---Find i_x (s.s) assuming no initial energy stored
- **Using phasor method and Laplace transform method**



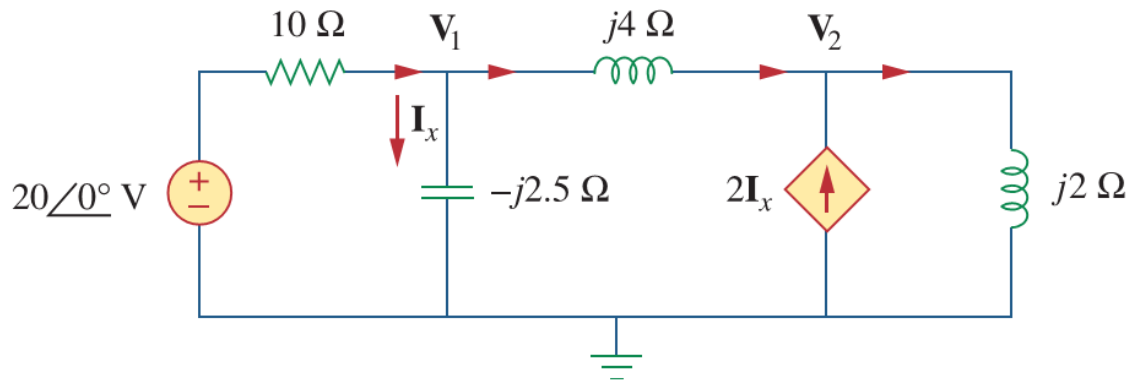
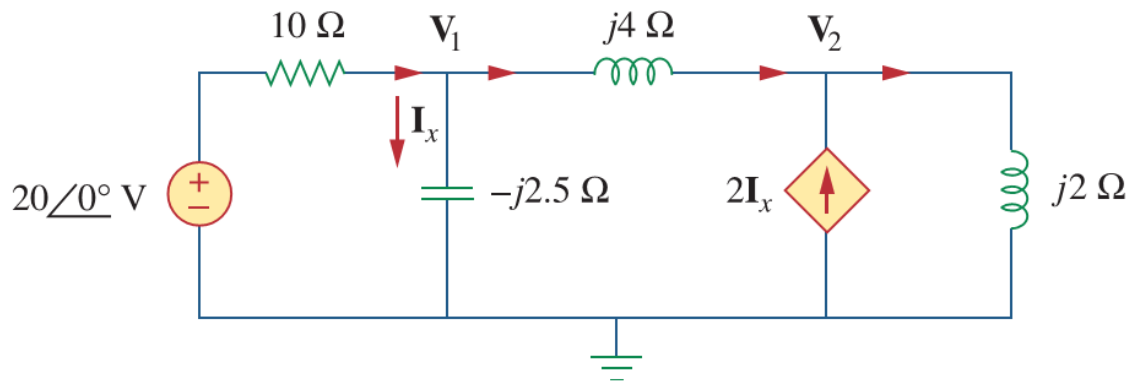
$$\frac{20 - \mathbf{V}_1}{10} = \frac{\mathbf{V}_1}{-j2.5} + \frac{\mathbf{V}_1 - \mathbf{V}_2}{j4}$$
$$2\mathbf{I}_x + \frac{\mathbf{V}_1 - \mathbf{V}_2}{j4} = \frac{\mathbf{V}_2}{j2}$$



$$\frac{20 - \mathbf{V}_1}{10} = \frac{\mathbf{V}_1}{-j2.5} + \frac{\mathbf{V}_1 - \mathbf{V}_2}{j4}$$
$$2\mathbf{I}_x + \frac{\mathbf{V}_1 - \mathbf{V}_2}{j4} = \frac{\mathbf{V}_2}{j2}$$

$$i_x = 7.59 \cos(4t + 108.4^\circ) \text{ A}$$





Example 8

- There is no initial energy stored in this circuit. Find $i(t)$ if
- $v(t) = e^{-0.6t} \sin 0.8t$ V.

