




Lecture 9

- AC Power Calculation

Power in AC Circuits

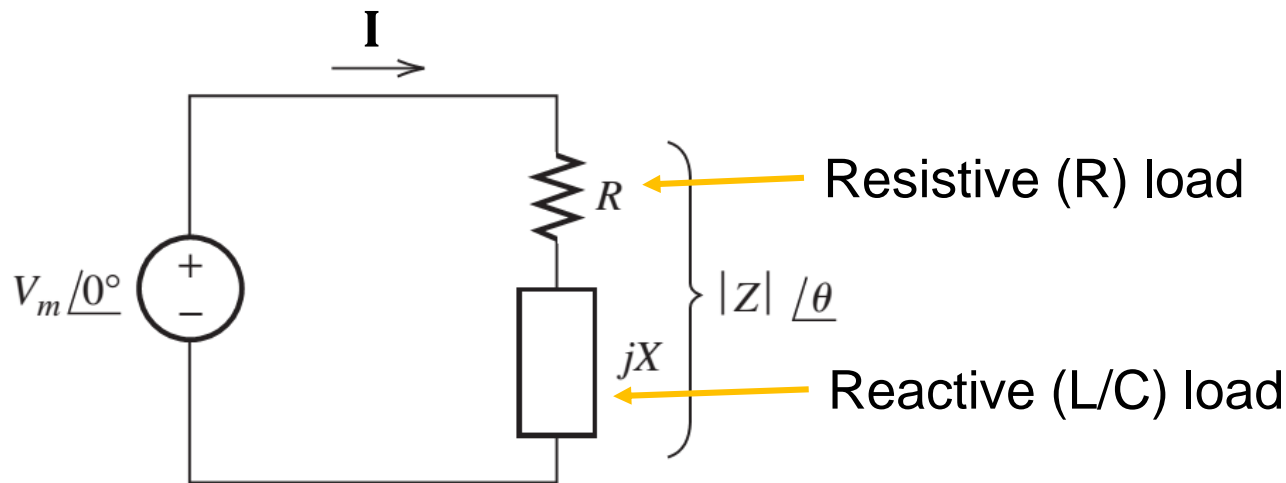- Consider the situation shown below: A voltage $v(t) = V_m \cos(\omega t)$ is applied to an **RLC network**.





Outline


- Instantaneous power
 - A function of time
- Average power
 - For R
- Reactive power
 - For L/C
- Complex power
 - Apparent power
 - Power factor

AC Power in Time Domain: Instantaneous

$$v(t) = V_m \cos(\omega t + \theta_v) \quad i(t) = I_m \cos(\omega t + \theta_i)$$


Instantaneous power:
power at any instant of time.

$$p(t) = v(t)i(t) =$$

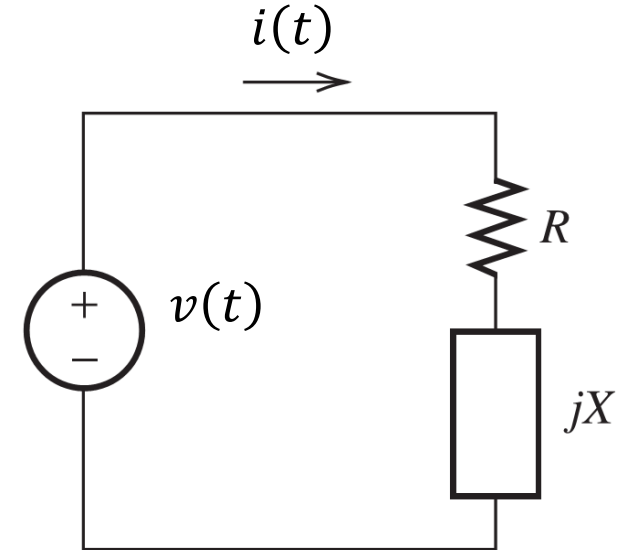




Instantaneous Power: Resistive Load

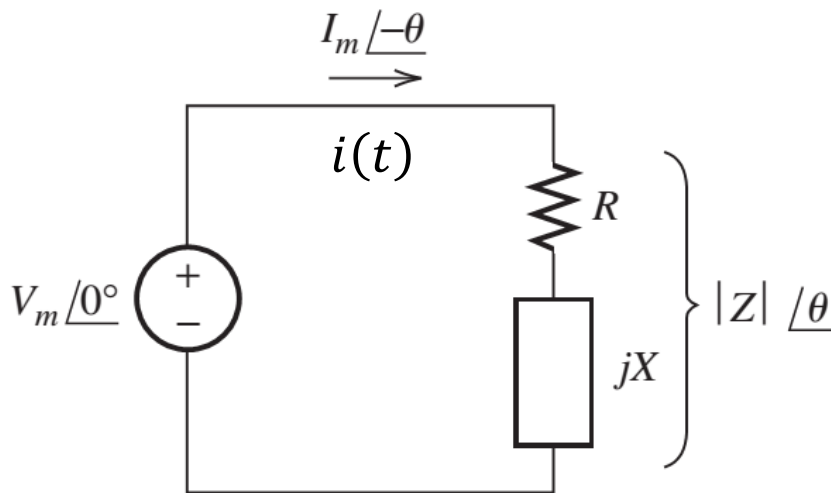

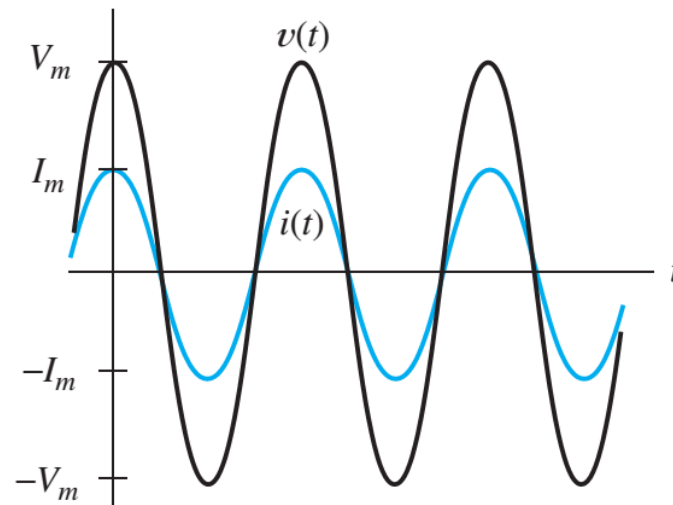
$$v(t) = V_m \cos(\omega t) \quad \theta_v = 0^\circ$$



$$p(t) = \frac{1}{2} V_m I_m \cos(\theta_v - \theta_i) + \frac{1}{2} V_m I_m \cos(2\omega t + \theta_v + \theta_i)$$


$$Z = R, \theta = \theta_v - \theta_i =$$

$$p(t) = v(t)i(t) =$$

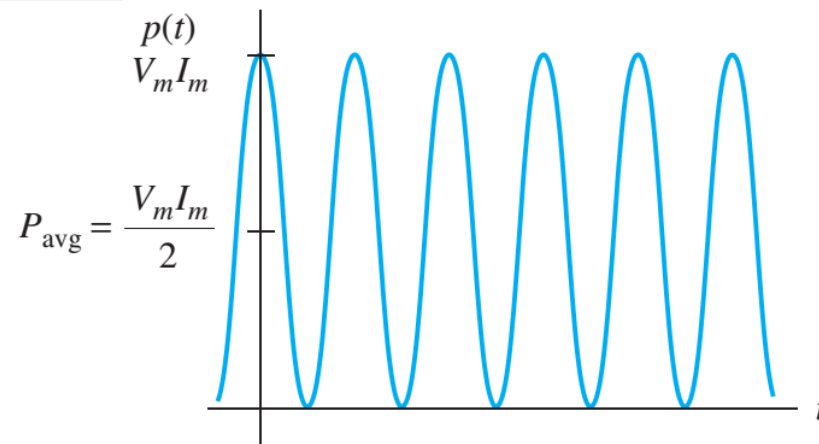



Instantaneous Power: Capacitive Load


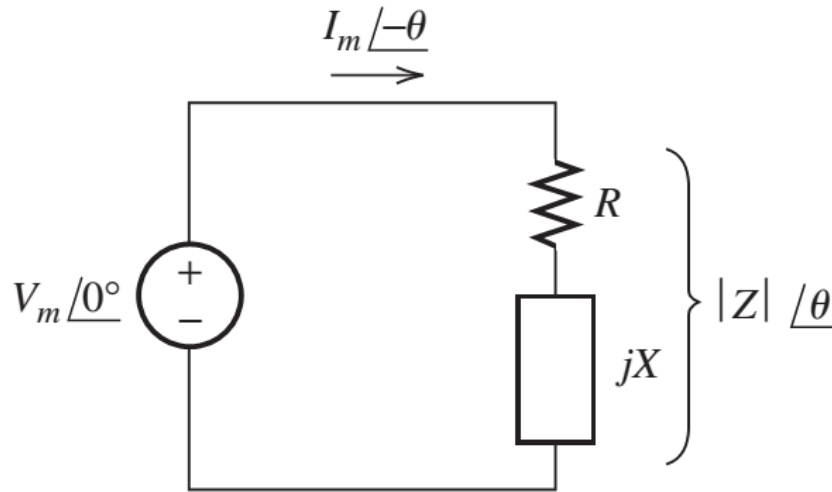


$$Z = \frac{1}{\omega C} \angle -90^\circ, \theta = \theta_v - \theta_i =$$

$$p(t) = \frac{1}{2} V_m I_m \cos(\theta_v - \theta_i) + \frac{1}{2} V_m I_m \cos(2\omega t + \theta_v + \theta_i)$$


$$p(t) = v(t)i(t) = -\frac{V_m I_m}{2} \sin(2\omega t)$$
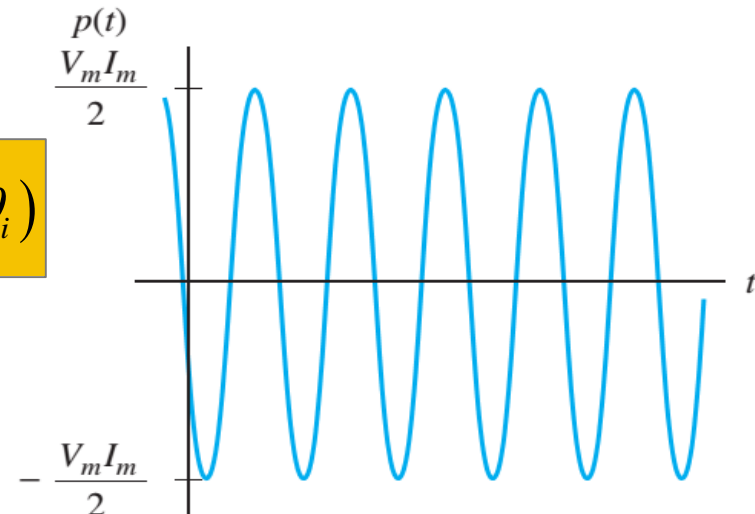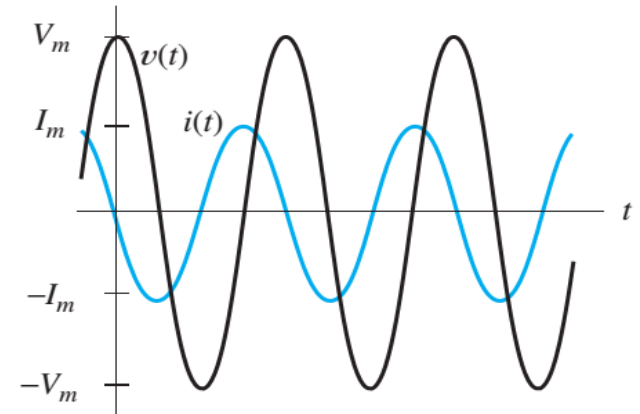
$$v(t) = V_m \cos(\omega t) \quad \theta_v = 0^\circ$$





Instantaneous Power: Inductive Load


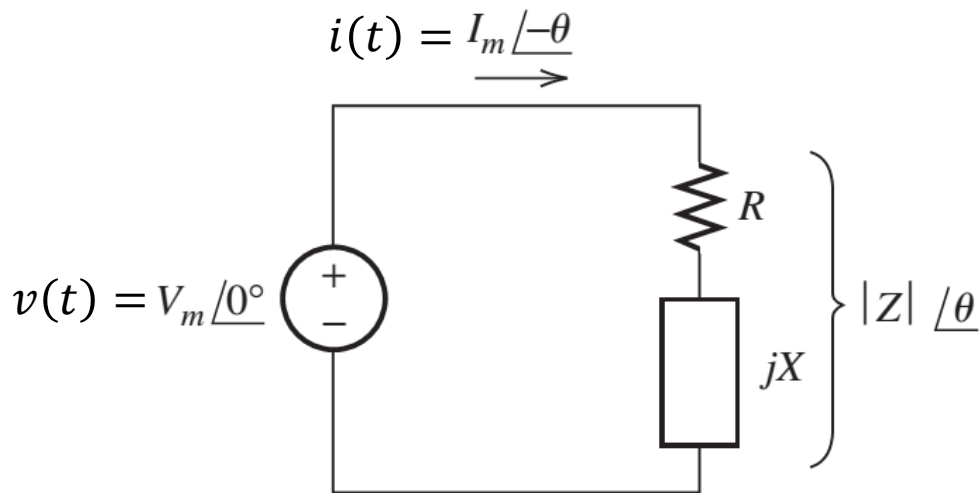


$$Z = \omega L \angle 90^\circ, \theta = \theta_v - \theta_i =$$

$$p(t) = \frac{1}{2} V_m I_m \cos(\theta_v - \theta_i) + \frac{1}{2} V_m I_m \cos(2\omega t + \theta_v + \theta_i)$$

$$p(t) = v(t)i(t) = \frac{V_m I_m}{2} \sin(2\omega t)$$
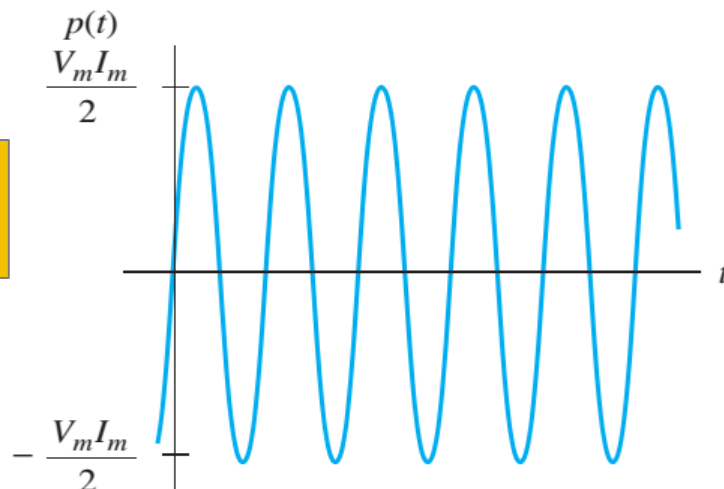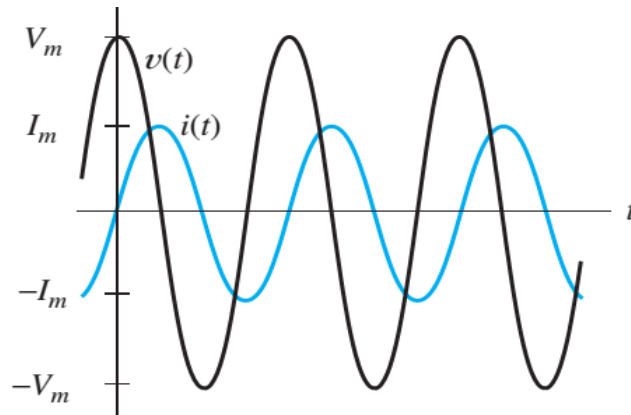
$$v(t) = V_m \cos(\omega t) \quad \theta_v = 0^\circ$$





Outline

- Instantaneous power
 - A function of time
- Average power
 - For R
- Reactive power
 - For L/C
- Complex power
 - Apparent power
 - Power factor



Average Power P : Real Dissipated Power

$$v(t) = V_m \cos(\omega t + \theta_v) \quad i(t) = I_m \cos(\omega t + \theta_i)$$


$$p(t) = \frac{1}{2} V_m I_m \cos(\theta_v - \theta_i) + \frac{1}{2} V_m I_m \cos(2\omega t + \theta_v + \theta_i)$$

Average (or real) power (unit: watts):

$$P = \frac{1}{T} \int_0^T p(t) dt$$

$p(t)$: First item + second item

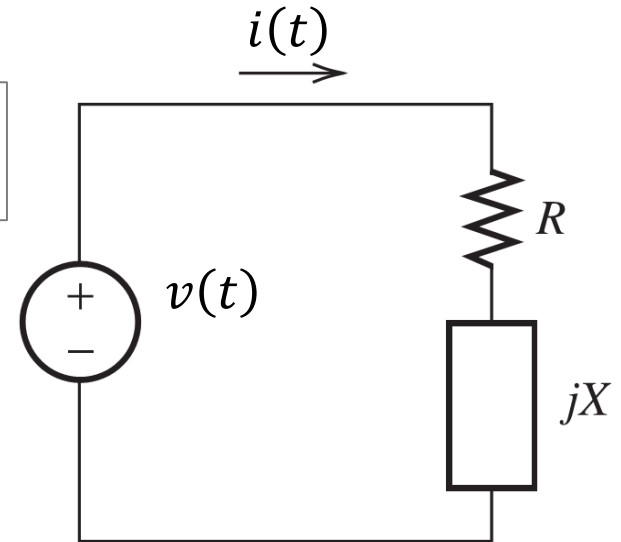$\theta_v - \theta_i =$ 0 for a resistor
90 degrees for inductor
-90 degrees for capacitor



$$P =$$


$$=$$



Resistive vs. Inductive


$$p(t) = \frac{1}{2} V_m I_m \cos(\theta_v - \theta_i) + \frac{1}{2} V_m I_m \cos(2\omega t + \theta_v + \theta_i)$$

$$\theta_v - \theta_i = 0$$

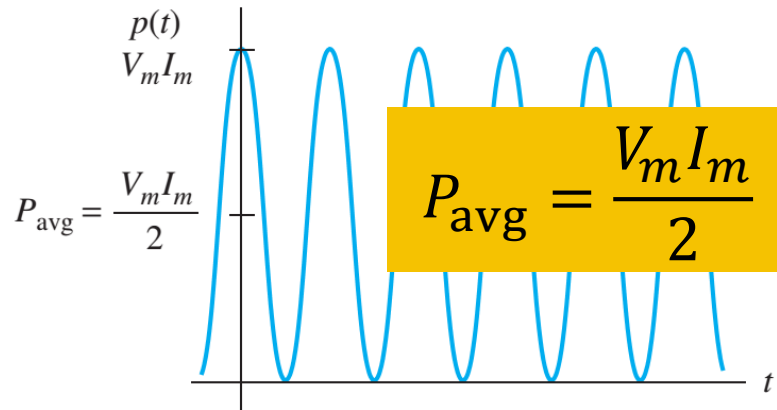


Pure resistive load
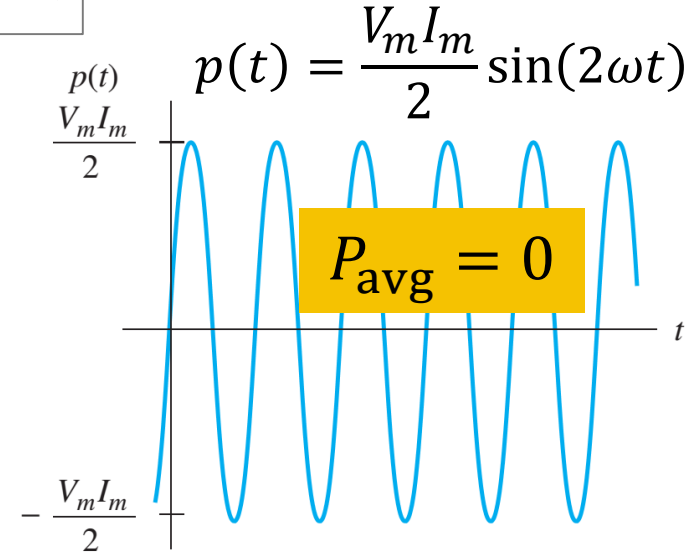
$$\theta_v = 0^\circ \quad \begin{aligned} \theta_v - \theta_i &= 90 \\ \theta_v + \theta_i &= -90 \end{aligned}$$



Pure inductive load

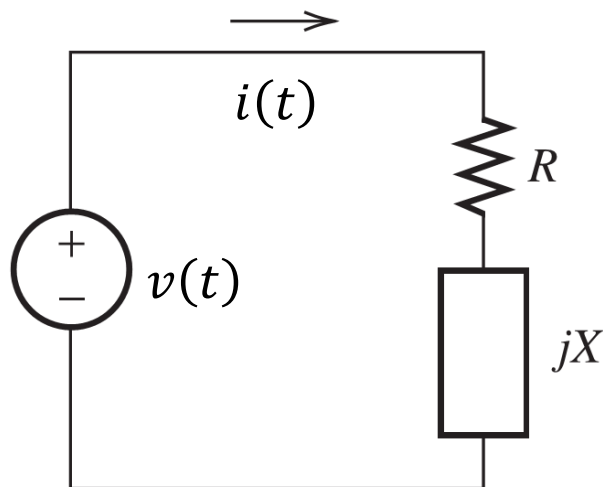


- Half the time, the energy is delivered to the inductance;
- The other half time, energy is returned to the source.



Reactive Power Q


Let us look at Instantaneous power again
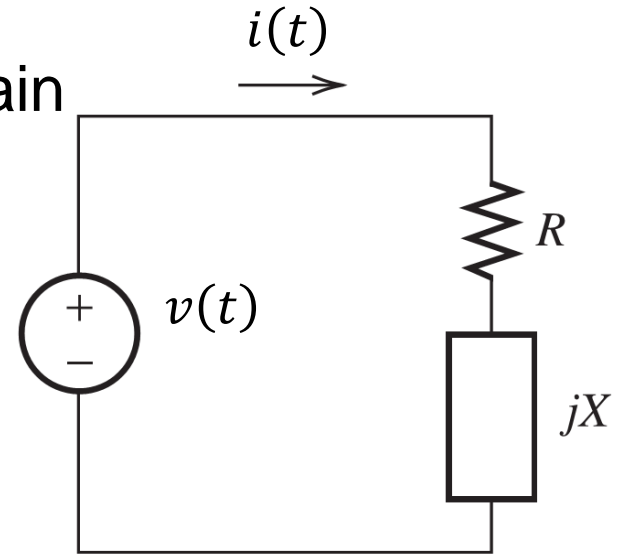
$$\begin{aligned} p(t) &= v(t)i(t) \\ p(t) &= p_R(t) + p_X(t) \\ p_R(t) &= \\ p_X(t) &= \end{aligned}$$



Reactive Power Q : Peak Exchanged Power

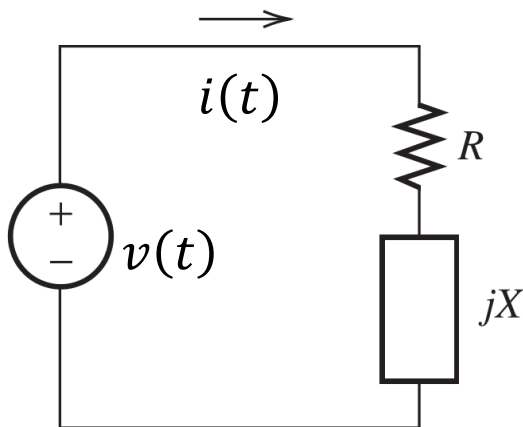- Definition: The peak instantaneous power associated with the energy storage elements contained in a general load.




$$Q = \frac{1}{2} V_m I_m \sin(\theta_v - \theta_i) = V_{rms} I_{rms} \sin(\theta_v - \theta_i)$$

$$Q = \begin{cases} 0 & \text{for a resistive } (\theta_v - \theta_i = 0^\circ) \\ \frac{1}{2} V_m I_m & \text{for inductive } (\theta_v - \theta_i = 90^\circ) \\ -\frac{1}{2} V_m I_m & \text{for capacitive } (\theta_v - \theta_i = -90^\circ) \end{cases}$$

- Reactive power is still of concern to power-system engineers
 - Transmission lines/transformers/fuses et al. must be capable of withstanding the current associated with reactive power.

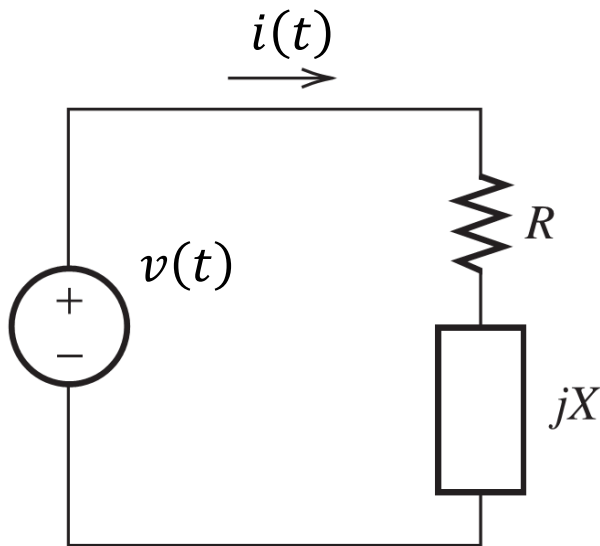Example

- Find the average power and reactive power absorbed by an impedance $Z = 30 - j70\Omega$, when a voltage $V = 120\angle 0^\circ$ is applied across it.



$$\mathbf{I} = \frac{\mathbf{V}}{\mathbf{Z}} = \frac{120\angle 0^\circ}{30 - j70} = \frac{120\angle 0^\circ}{76.16\angle -66.8^\circ} \\ = 1.576\angle 66.8^\circ \text{ A}$$

$$P = \frac{1}{2} V_m I_m \cos(\theta_v - \theta_i) = 37.24 \text{ W}$$


$$Q = \frac{1}{2} V_m I_m \sin(\theta_v - \theta_i) = -86.91 \text{ VAR}$$



Review: Effective (=RMS) Value

- For any periodic function $x(t)$ in general, its rms value is
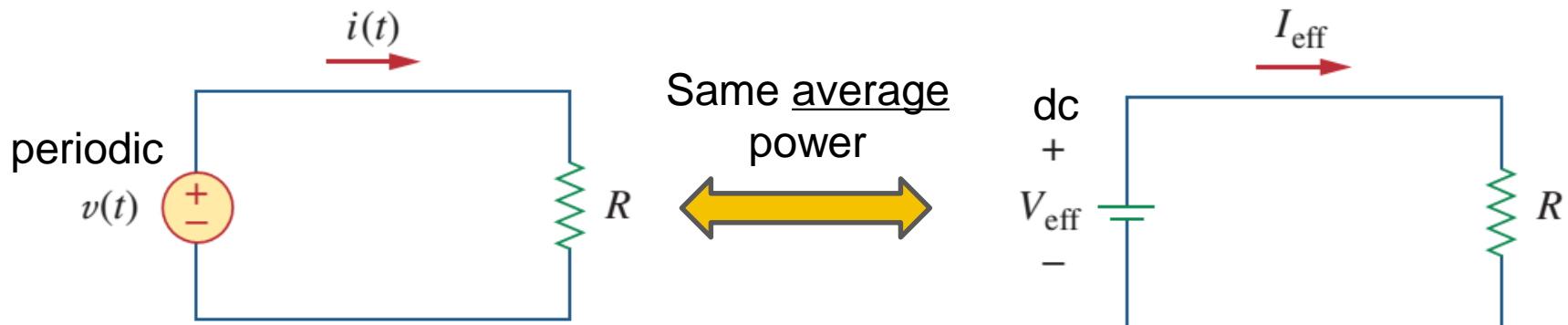
$$X_{\text{eff}} = X_{\text{rms}} = \sqrt{\frac{1}{T} \int_0^T x^2(t) dt}$$




$$I_{\text{eff}} = \sqrt{\frac{1}{T} \int_0^T i^2(t) dt}$$

$$V_{\text{eff}} = \sqrt{\frac{1}{T} \int_0^T v^2(t) dt}$$

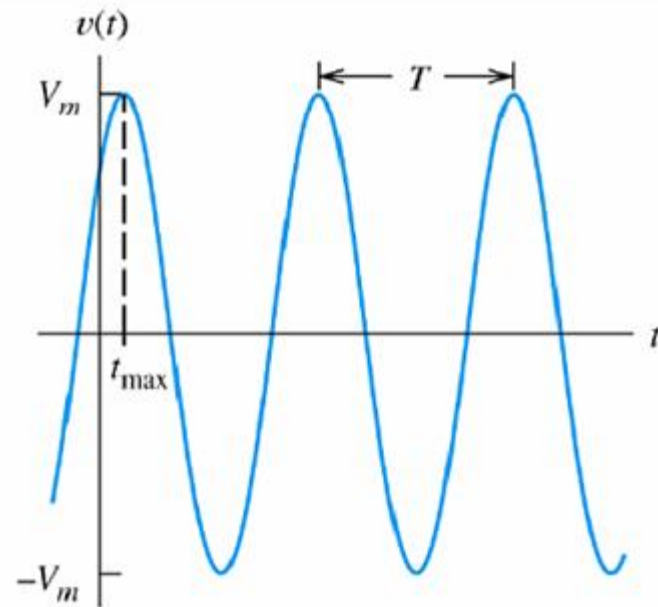Example: RMS of a Sinusoidal

- The RMS value of $v(t) = V_m \cos(\omega t + \phi)$ is

$$\begin{aligned} V_{\text{rms}} &= \sqrt{\frac{1}{T} \int_{t_0}^{t_0+T} v^2(t) dt} \\ &= \sqrt{\frac{1}{T} \int_{t_0}^{t_0+T} V_m^2 \cdot \cos^2(\omega t + \phi) dt} \\ &= \end{aligned}$$





Outline

- Instantaneous power
 - A function of time
- Average power
 - For R
- Reactive power
 - For L/C
- Complex power
 - Apparent power
 - Power factor

AC Power for General Load: Phasor Domain

$$v(t) = V_m \cos(\omega t + \theta_v) \Rightarrow \mathbf{V} = V_m \angle \theta_v$$

$$i(t) = I_m \cos(\omega t + \theta_i) \Rightarrow \mathbf{I} = I_m \angle \theta_i$$

$$P = \frac{1}{2} V_m I_m \cos(\theta_v - \theta_i) \quad Q = \frac{1}{2} V_m I_m \sin(\theta_v - \theta_i)$$

We observe that:

$$\frac{1}{2} \mathbf{V} \mathbf{I}^* = \frac{1}{2} V_m I_m \angle (\theta_v - \theta_i)$$

$$= \frac{1}{2} V_m I_m \cos(\theta_v - \theta_i) + j \frac{1}{2} V_m I_m \sin(\theta_v - \theta_i)$$



Average (or real) power

$$P = \operatorname{Re} \left[\frac{1}{2} \mathbf{V} \mathbf{I}^* \right]$$


Unit: Watts



Reactive power

$$Q = \operatorname{Im} \left[\frac{1}{2} \mathbf{V} \mathbf{I}^* \right]$$

Unit: Volt Amperes Reactive (VARs)

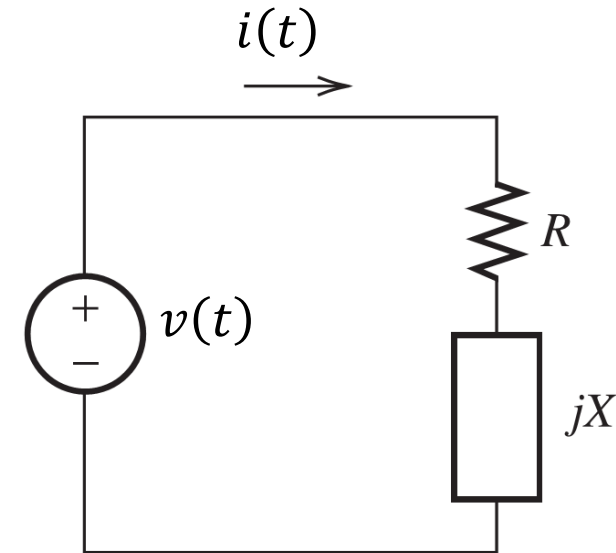



Complex Power S

- Define a *single* power metric to include both P and Q .

$$\mathbf{S} = \frac{1}{2} \mathbf{V} \mathbf{I}^* = V_{\text{rms}} \mathbf{I}_{\text{rms}}^* = V_{\text{rms}} I_{\text{rms}} \angle(\theta_v - \theta_i) = P + jQ$$

Unit: volt-amp (VA)

Complex power is important in power analysis because it contains *all* the information pertaining to the power absorbed by a given load.




- Apparent power

$$s = |\mathbf{S}| = \frac{1}{2} V_m I_m = V_{\text{rms}} I_{\text{rms}}$$

Unit: volt-amp (VA)

it seems apparent that the power should be the voltage-current product, by analogy with dc resistive circuits.

Power Triangle

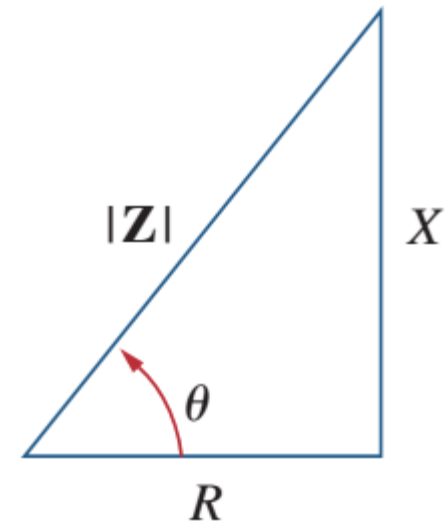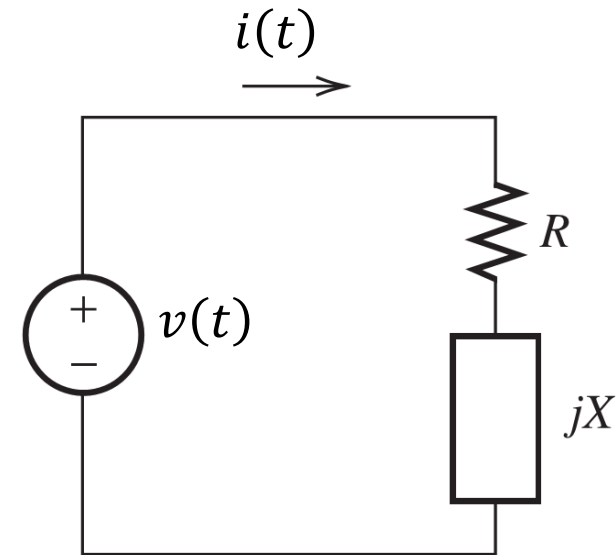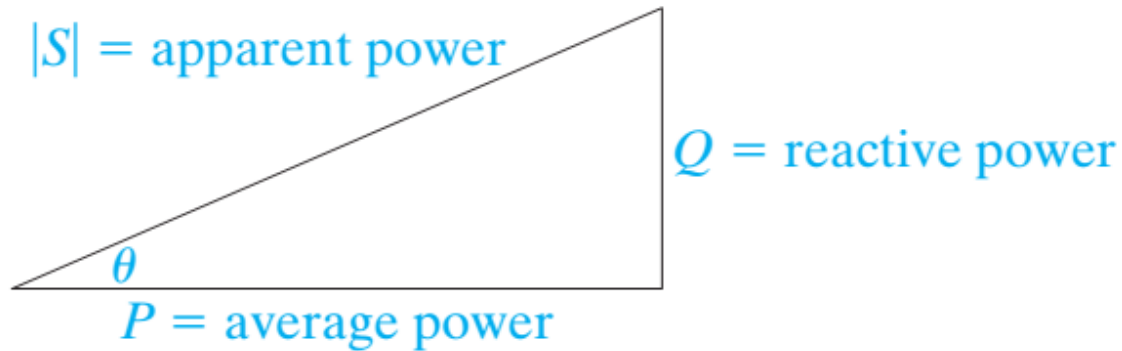

Quantity	Units
Complex power	volt-amps
Average power	watts
Reactive power	var


Power Factor

$$\begin{aligned} P &= \frac{1}{2} V_m I_m \cos(\theta_v - \theta_i) \\ &= V_{rms} I_{rms} \cos(\theta_v - \theta_i) \\ &= S \cos(\theta_v - \theta_i) \end{aligned}$$


- The power factor

$$\text{pf} = \frac{P}{S} = \cos(\theta_v - \theta_i)$$

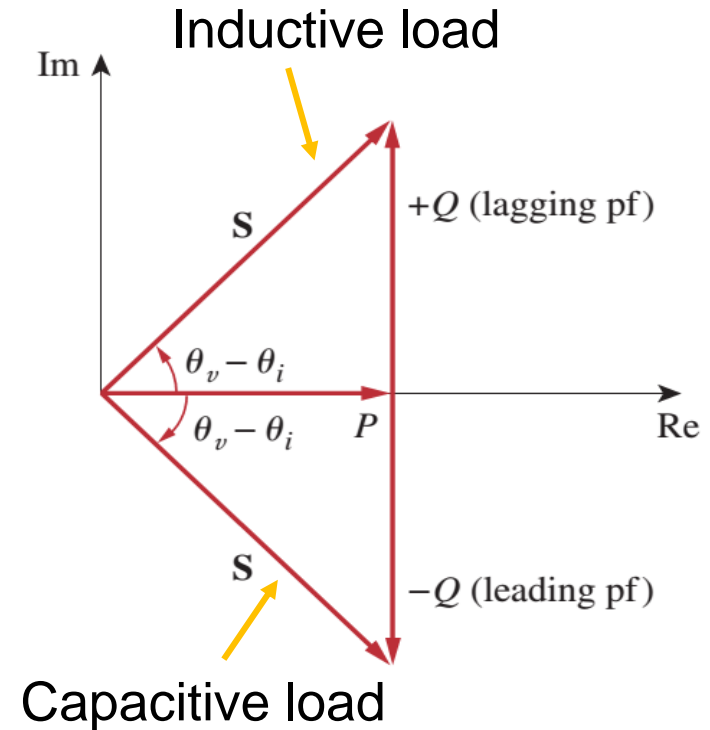- $(\theta_v - \theta_i)$ is called power factor angle.
 - >0 means a *lagging* pf (current lags voltage)
 - <0 means a *leading* pf (current leads voltage)
- pf ranges from 0 to 1.



Power Factor

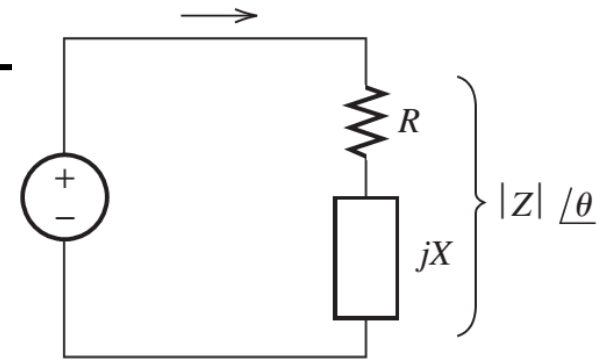

Power factor leading and lagging relationships for a load $\mathbf{Z} = R + jX$.

Load Type	$\phi_z = \phi_v - \phi_i$	I-V Relationship	pf
Purely Resistive ($X = 0$)	$\phi_z = 0$	\mathbf{I} in-phase with \mathbf{V}	1
Inductive ($X > 0$)	$0 < \phi_z \leq 90^\circ$	\mathbf{I} lags \mathbf{V}	lagging
Purely Inductive ($X > 0$ and $R = 0$)	$\phi_z = 90^\circ$	\mathbf{I} lags \mathbf{V} by 90°	lagging
Capacitive ($X < 0$)	$-90^\circ \leq \phi_z < 0$	\mathbf{I} leads \mathbf{V}	leading
Purely Capacitive ($X < 0$ and $R = 0$)	$\phi_z = -90^\circ$	\mathbf{I} leads \mathbf{V} by 90°	leading



Example

- A series-connected load draws a current

$$i(t) = 4\cos(100\pi t + 10^\circ)\text{A}$$

when the applied voltage is

$$v(t) = 120\cos(100\pi t - 20^\circ)\text{V}$$

- Find the apparent power and the power factor of the load.
- Determine the values that form the series-connected load.

$$V_{\text{rms}} I_{\text{rms}} = 240 \text{ VA}$$

$$\text{pf} = \cos(\theta_v - \theta_i) = 0.866 \quad (\text{leading})$$

$$\mathbf{Z} = \frac{\mathbf{V}}{\mathbf{I}} = 25.98 - j15 \, \Omega$$

$$C = \frac{1}{15\omega} = \frac{1}{15 \times 100\pi} = 212.2 \, \mu\text{F}$$



Exercise

- The voltage across a load is $v(t) = 60\cos(\omega t - 10^\circ)\text{V}$, and the current through the load is $i(t) = 1.5\cos(\omega t + 50^\circ)$. Find
 - The complex and apparent powers.
 - The real and reactive powers.
 - The power factor and the load impedance.

$$\mathbf{S} = \mathbf{V}_{\text{rms}} \mathbf{I}_{\text{rms}}^* = 45 \angle -60^\circ \text{ VA}$$

$$\text{pf} = 0.5 \text{ (leading)}$$

$$\mathbf{Z} = \frac{\mathbf{V}}{\mathbf{I}} = 40 \angle -60^\circ \Omega$$



Quick Summary – Power Calculation

$$v(t) = V_m \cos(\omega t + \theta_v) \Rightarrow \mathbf{V} = V_m \angle \theta_v$$


$$i(t) = I_m \cos(\omega t + \theta_i) \Rightarrow \mathbf{I} = I_m \angle \theta_i$$

$$P = \frac{1}{2} V_m I_m \cos(\theta_v - \theta_i) = V_{rms} I_{rms} \cos(\theta_v - \theta_i)$$

$$Q = \frac{1}{2} V_m I_m \sin(\theta_v - \theta_i) = V_{rms} I_{rms} \sin(\theta_v - \theta_i)$$

$$S = \frac{1}{2} V_m I_m = V_{rms} I_{rms}$$
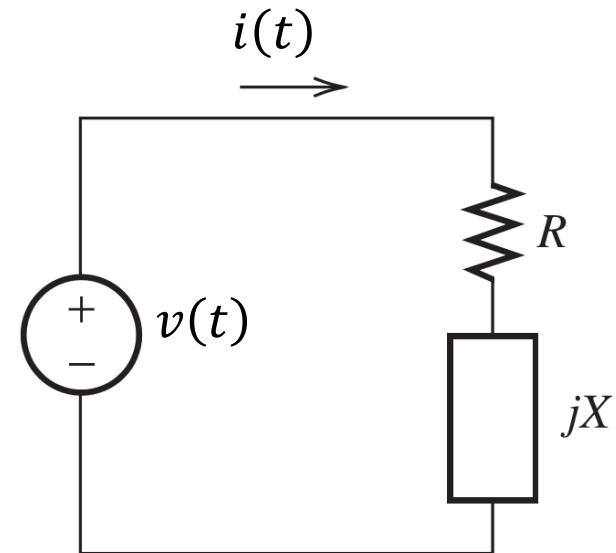
$$\mathbf{S} = S \angle (\theta_v - \theta_i) = P + jQ$$



Another Way to Calculate Complex Power

$$\mathbf{S} = \mathbf{V}_{\text{rms}} \mathbf{I}_{\text{rms}}^*$$

$$= \mathbf{V}_{\text{rms}} \left(\frac{\mathbf{V}_{\text{rms}}}{\mathbf{Z}} \right)^*$$

$$= \frac{|\mathbf{V}_{\text{rms}}|^2}{\mathbf{Z}^*}$$

$$\mathbf{S} = \mathbf{V}_{\text{rms}} \mathbf{I}_{\text{rms}}^*$$


$$= \mathbf{I}_{\text{rms}} \mathbf{Z} \mathbf{I}_{\text{rms}}^*$$

$$= |\mathbf{I}_{\text{rms}}|^2 \mathbf{Z}$$

$$= |\mathbf{I}_{\text{rms}}|^2 (R + jX)$$

$$= |\mathbf{I}_{\text{rms}}|^2 R + j |\mathbf{I}_{\text{rms}}|^2 X$$
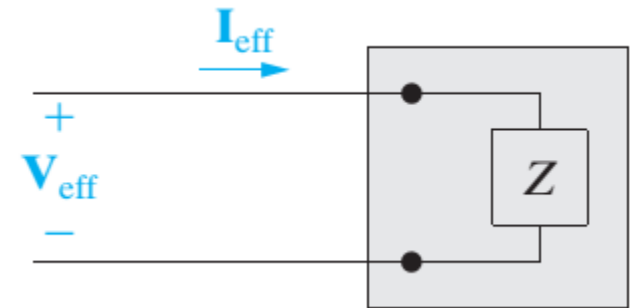
$$= I_{\text{rms}}^2 R + j I_{\text{rms}}^2 X$$



$$\mathbf{V}_{\text{rms}} = \mathbf{I}_{\text{rms}} \mathbf{Z}$$


$$P = \text{Re}(\mathbf{S}) = I_{\text{rms}}^2 R$$

$$Q = \text{Im}(\mathbf{S}) = I_{\text{rms}}^2 X$$

$$\mathbf{S} = I_{\text{rms}}^2 \mathbf{Z} = \frac{V_{\text{rms}}^2}{\mathbf{Z}^*} = \mathbf{V}_{\text{rms}} \mathbf{I}_{\text{rms}}^*$$



Example

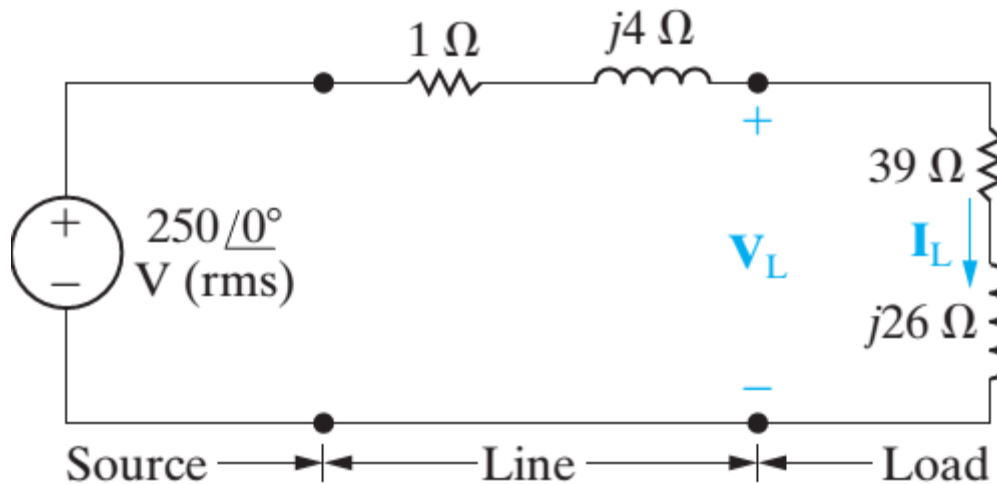

- Find V_L and I_L .
- Find the average and reactive power
 - Delivered to the load
 - Delivered to the line
 - Supplied by the source

$$\begin{aligned} I_L &= \frac{250\angle 0^\circ}{40 + j30} = 4 - j3 \\ &= 5\angle -36.87^\circ \text{ (rms)} \end{aligned}$$

$$\begin{aligned} V_L &= I_L(39 + j26) \\ &= 234 - j13 \\ &= 234.36\angle -3.18^\circ \end{aligned}$$

Load:

$$V_L I_L^* = 975 + j650 \text{ VA}$$

Line:

$$P = (5)^2(1) = 25 \text{ W}$$

$$Q = (5)^2(4) = 100 \text{ VAR}$$


Source:

$$250\angle 0^\circ I_L^* = 1000 + j750 \text{ VA}$$




Complex Power

Time Domain

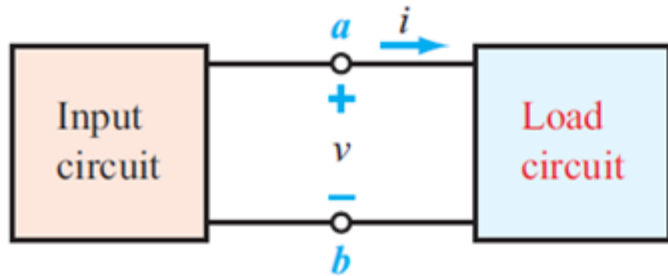

$$\begin{aligned} v(t) &= V_m \cos(\omega t + \phi_v) \\ i(t) &= I_m \cos(\omega t + \phi_i) \\ V_{\text{rms}} &= V_m / \sqrt{2} \\ I_{\text{rms}} &= I_m / \sqrt{2} \end{aligned}$$

Phasor Domain

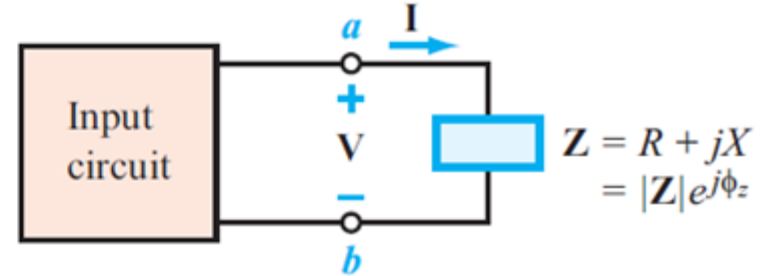

$$\begin{aligned} V &= V_m e^{j\phi_v} \\ I &= I_m e^{j\phi_i} \\ V_{\text{rms}} &= V_m / \sqrt{2} \\ I_{\text{rms}} &= I_m / \sqrt{2} \end{aligned}$$

Complex Power

$$S = \frac{1}{2} \mathbf{V} \mathbf{I}^* = V_{\text{rms}} I_{\text{rms}}^* = P + jQ$$

Real Average Power

$$\begin{aligned} P &= \Re[S] \text{ [W]} \\ &= V_{\text{rms}} I_{\text{rms}} \cos(\phi_v - \phi_i) \\ &= I_{\text{rms}}^2 R \end{aligned}$$

Apparent Power

$$\begin{aligned} S &= |S| = \sqrt{P^2 + Q^2} \\ &= V_{\text{rms}} I_{\text{rms}} \\ &= I_{\text{rms}}^2 |Z| \end{aligned}$$

Reactive Power

$$\begin{aligned} Q &= \Im[S] \text{ [VAr]} \\ &= V_{\text{rms}} I_{\text{rms}} \sin(\phi_v - \phi_i) \\ &= I_{\text{rms}}^2 X \end{aligned}$$

Power Factor

$$\begin{aligned} pf &= \frac{P}{S} \\ &= \cos(\phi_v - \phi_i) \\ &= \cos \phi_z \end{aligned}$$

$$\begin{aligned} S &= S e^{j\phi_s} \\ \phi_s &= \phi_v - \phi_i = \phi_z \end{aligned}$$