

Homework 7

Due date: 18:30 of Dec.16th, 2021

Turn in your homework in Class or to Tutorial Course Classroom 1B-110



Rules:

- Work on your own. Discussion is permissible, but extremely similar submissions will be judged as plagiarism.
- Please show all intermediate steps: a correct solution without an explanation will get zero credit.
- Please submit on time. No late submission will be accepted.
- Please prepare your submission in English only. No Chinese submission will be accepted.
- If needed, round the number to the nearest hundredths, i.e., rounding it to 2 decimal places.


Notes : $\frac{1}{Aj^2\omega^2 + Bj\omega + C}$

OR $\left(\frac{j\omega}{\omega_1} + 1\right) \left(\frac{j\omega}{\omega_2} + 1\right)$

These plots are all correct.

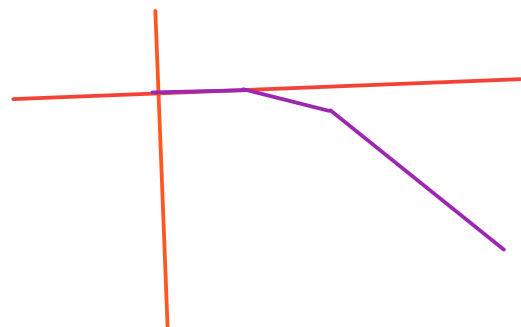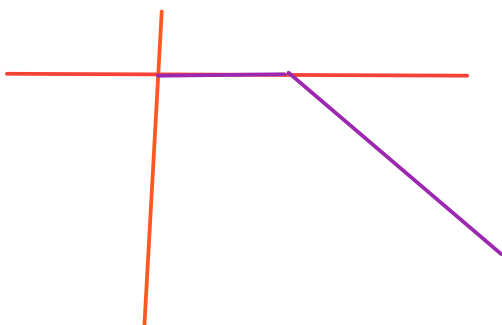

25

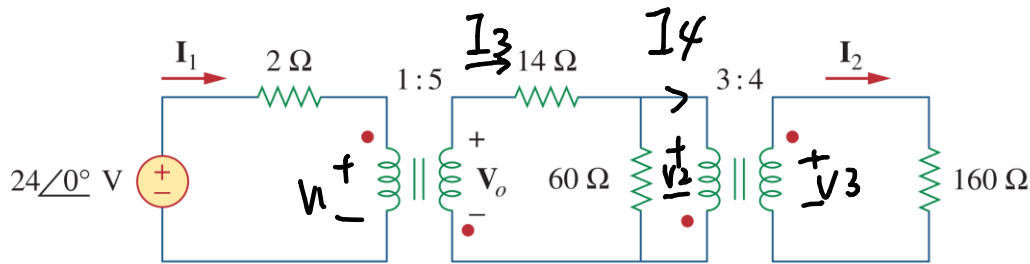1. For the following ideal transformer circuit, calculate I_1 , I_2 , and V_o .

$$\begin{cases} \frac{V_o}{V_1} = -5, & \frac{I_3}{I_1} = -\frac{1}{5} \\ \frac{V_3}{V_2} = -\frac{4}{3}, & \frac{I_2}{I_4} = -\frac{3}{4} \end{cases} \quad \text{Suppose } \begin{cases} V_1 = X \\ I_1 = Y \\ I_4 = Z \end{cases} \Rightarrow \begin{cases} V_o = -5X \\ I_3 = -\frac{1}{5}Y \\ I_2 = -\frac{3}{4}Z \end{cases}$$

$$\text{KVL: } \begin{cases} V_s = I_1 \cdot 2\Omega + V_1 \Rightarrow 24\angle 0^\circ = 2Y + X & (1) \\ V_o = I_3 \cdot 14\Omega + V_2 \Rightarrow -5X = -\frac{14}{5}Y + V_2 \end{cases}$$

$$\text{KCL: } I_3 = I_4 + \frac{V_2}{60\Omega} \Rightarrow -\frac{1}{5}Y = Z + \frac{V_2}{60}$$

$$V_2 = -5X + \frac{14}{5}Y \quad Z = -\frac{37}{150}Y + \frac{1}{12}X$$

$$V_3 = -\frac{4}{3}V_2 = \frac{20}{3}X - \frac{56}{15}Y \quad I_2 = \frac{37}{200}Y - \frac{1}{16}X$$


$$\text{KVL: } V_3 = I_2 \cdot 160\Omega \Rightarrow X = 2Y$$

$$\text{Back to (1): } Y = 6\angle 0^\circ \quad X = 12\angle 0^\circ$$

$$\begin{cases} I_1 = Y = 6\angle 0^\circ \text{ A} \\ V_o = -5X = 60\angle -180^\circ \text{ V} \end{cases} \quad I_2 = \frac{37}{200}Y - \frac{1}{16}X = 0.36\angle 0^\circ \text{ A}$$

21

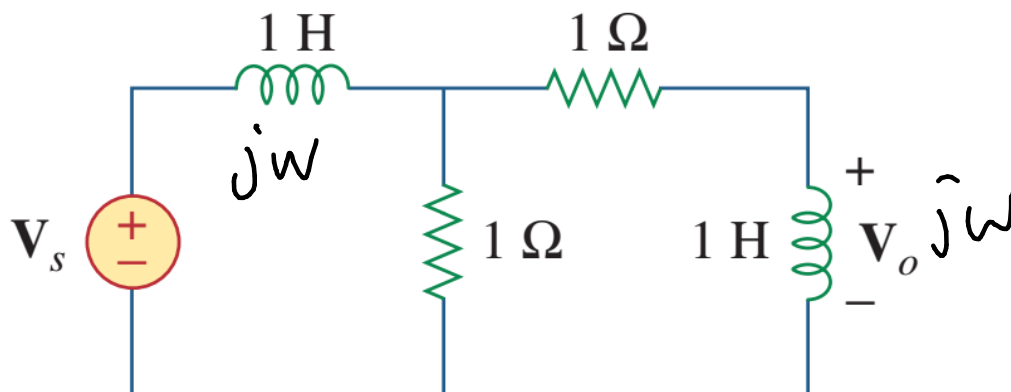2. Derive the transfer function $Y(\omega)$, the voltage gain between V_o and the voltage source V_s . Draw the corresponding bode plot.







$$V_o = V_s \cdot \frac{\frac{1+j\omega}{2+j\omega}}{\frac{1+j\omega}{2+j\omega} + j\omega} \cdot \left(\frac{j\omega}{1+j\omega} \right) \quad 3$$

$$= V_s \frac{1+j\omega}{1+j\omega + 2j\omega - \omega^2} \cdot \frac{j\omega}{1+j\omega}$$


$$= V_s \cdot \frac{j\omega}{(j^2\omega^2 + 3j\omega + 1)} \quad 2$$
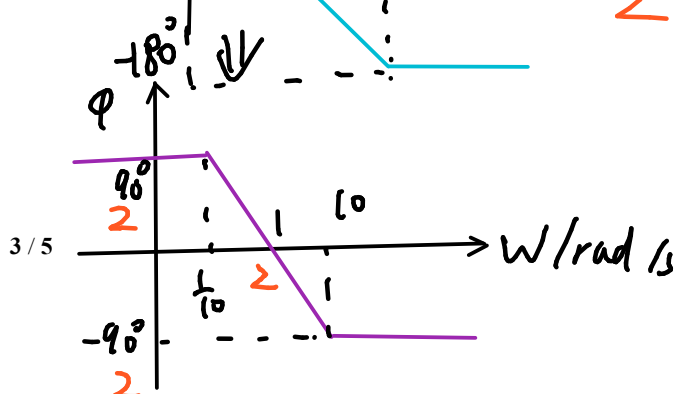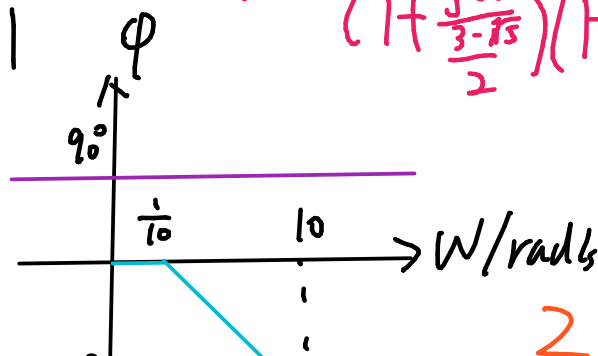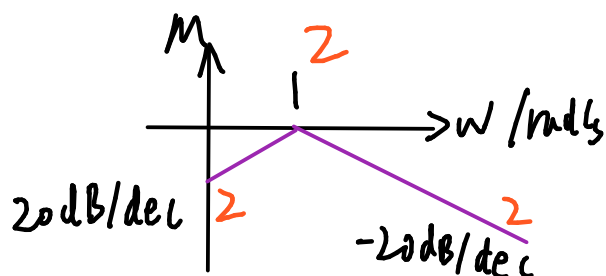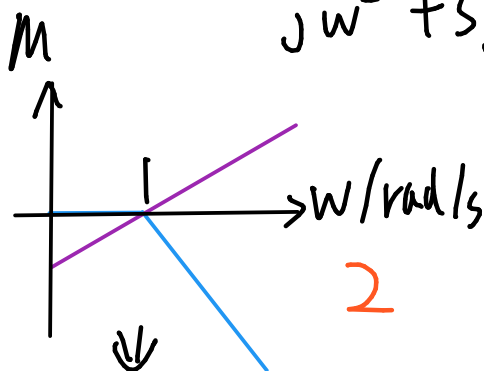
$$Y(\omega) = \frac{j\omega}{j^2\omega^2 + 3j\omega + 1} = \frac{j\omega}{\left(1 + \frac{j\omega}{3 - j5}\right) \left(1 + \frac{j\omega}{2}\right)}$$



3. Consider the following circuit with an operational amplifier working in the linear region. The input/output voltage are V_i , V_o , respectively. The circuit is operating at the angular frequency ω rad/s.

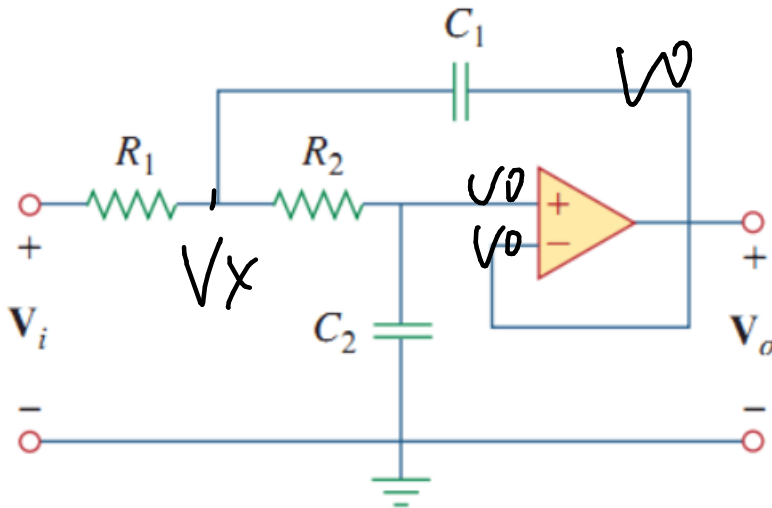- 1) Find the transfer function of the circuit $Y(\omega) = V_o / V_i$.
- 2) Sketch the magnitude-frequency relation of bode plot wof $Y(\omega)$.
- 3) Determine what kind of filter it is from the bode plot.



$$1) \frac{V_i - V_x}{R_1} + \frac{V_o - V_x}{R_2} + j\omega C_1 \cdot (V_o - V_x) = 0 \quad 4$$

$$\frac{V_x - V_o}{R_2} = j\omega C_2 \cdot V_o \quad 4$$

$$V_x = V_o \cdot (R_2 j\omega C_2 + 1) \quad 2$$

$$R_2 V_i - R_2 V_x + R_1 V_o - R_1 V_x = j\omega C_1 R_1 R_2 (V_x - V_o)$$


$$R_2 V_i + R_1 V_o - (R_1 + R_2)(R_2 j\omega C_2 + 1) V_o = j\omega^2 C_1 R_1 R_2^2 C_2 V_o \quad 2$$

$$\frac{V_o}{V_i} = \frac{R_2}{R_2 + (R_1 + R_2)(R_2 j\omega C_2) + j^2 \omega^2 R_1 R_2^2 C_1 C_2} \quad 2$$

$$= \frac{1}{R_1 R_2 C_1 C_2 j^2 \omega^2 + (R_1 + R_2) C_2 j\omega + 1}$$

3. Consider the following circuit with an operational amplifier working in the linear region. The input/output voltage are V_i , V_o , respectively. The circuit is operating at the angular frequency ω rad/s.

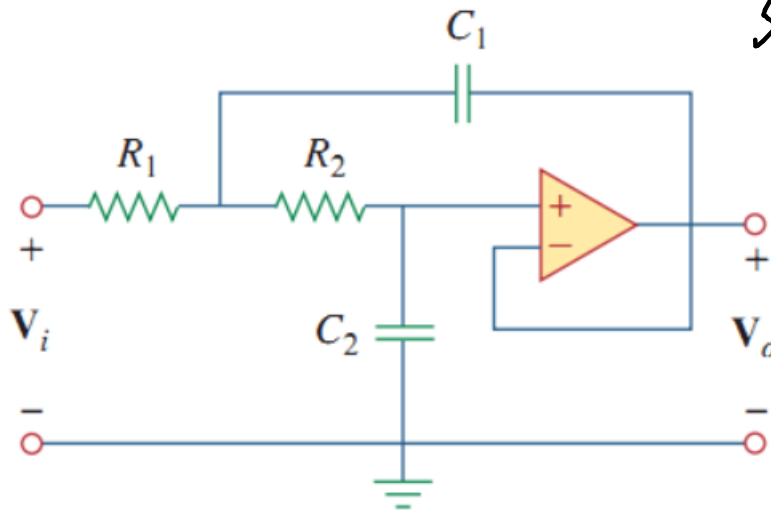- 1) Find the transfer function of the circuit $Y(\omega) = V_o / V_i$.
- 2) Sketch the magnitude-frequency relation of bode plot wof $Y(\omega)$.
- 3) Determine what kind of filter it is from the bode plot.



3) Low Pass Filter

3

$$Y(\omega) = \frac{1}{R_1 R_2 C_1 C_2 j^2 \omega^2 + (R_1 + R_2) C_2 j\omega + 1}$$

3

$$\approx \frac{1}{\frac{j^2 \omega^2}{R_1 R_2 C_1 C_2} + (R_1 + R_2) C_2 j\omega + 1}$$

$$\omega_k = \sqrt{\frac{1}{R_1 R_2 C_1 C_2}}$$


2

$$M = |Y(\omega)| = \frac{1}{\sqrt{R_1 R_2 C_1 C_2}} \rightarrow \omega \text{ rad/s}$$

-40 dB/dec

2

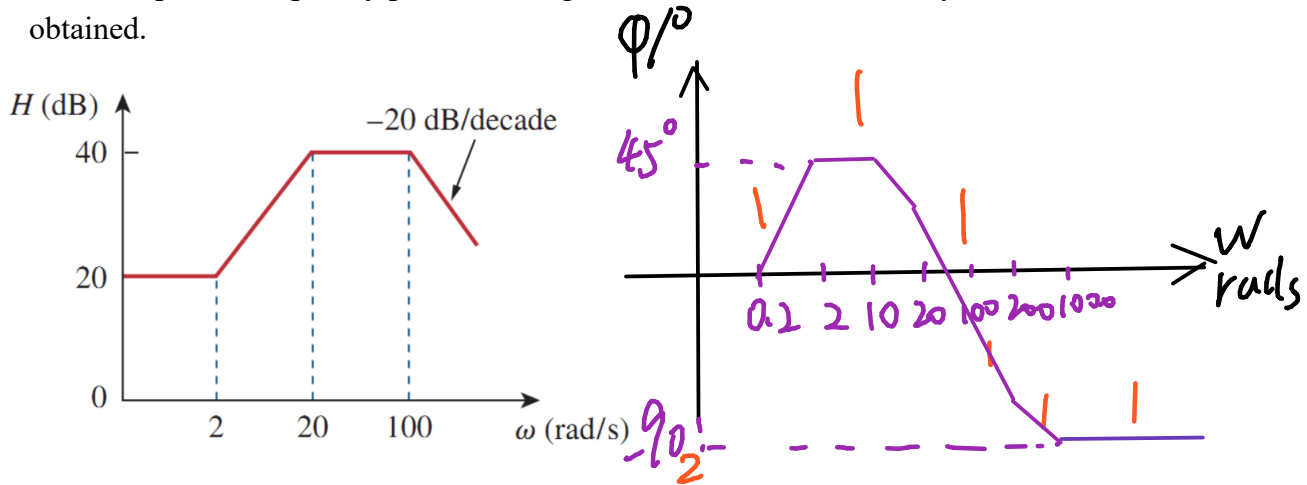4. Determine a possible **transfer function** for the following magnitude graph;
Draw the **phase-frequency plot** according to the transfer function that you obtained.



Constant: $20 \log_{10} K = 20 \cdot 2 \quad K = 10^2$

Slope 1 = 20 dB/decade 2

$H_1(\omega) = \left(1 + \frac{j\omega}{2}\right)$ 2

Slope 2 = 0 $\Rightarrow H_2(\omega) = \frac{1}{\left(1 + \frac{j\omega}{20}\right)}$ 2

Slope 3 = -20 dB $\Rightarrow H_3(\omega) = \frac{1}{1 + \frac{j\omega}{100}}$ 2

$H(\omega) = \frac{10^2 \left(1 + \frac{j\omega}{2}\right)}{\left(1 + \frac{j\omega}{20}\right) \cdot \left(1 + \frac{j\omega}{100}\right)}$ 4