



Lecture 11

- Magnetically Coupled Circuits





Outline

- Mutual inductance
- Transformers



Review: Self Inductance

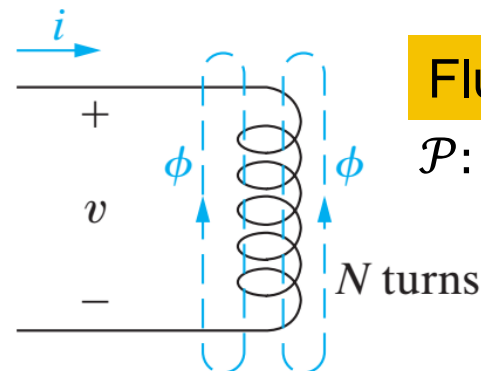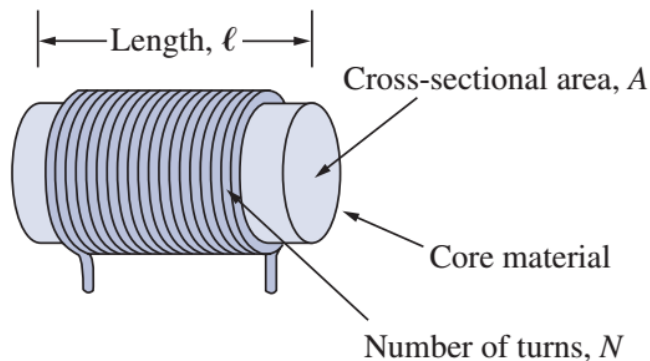- Self inductance: reaction of the inductor to the change in current through itself.



$$\text{Flux } \phi = \mathcal{P}Ni$$

\mathcal{P} : permeance


$$v = N \frac{d\phi}{dt} = L \frac{di}{dt}$$

$$\text{where } L = N \frac{d\phi}{di}$$



Mutual Inductance

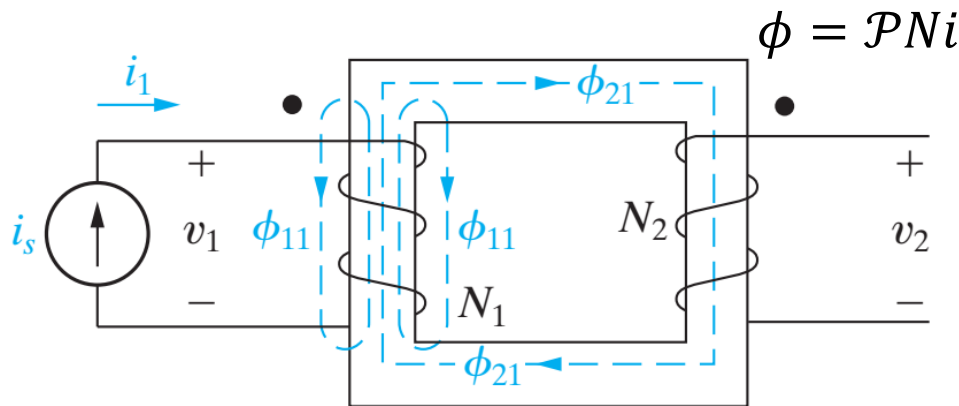- Mutual inductance: reaction of the inductor to change in current through another inductor.



$$\phi_1 = \phi_{11} + \phi_{21}$$

$$\phi_{11} = \mathcal{P}_{11}N_1i_1, \quad \phi_{21} = \mathcal{P}_{21}N_1i_1,$$


$$\phi_1 = \mathcal{P}_1N_1i_1$$

$$\begin{aligned} v_1 &= \frac{d(N_1\phi_1)}{dt} = N_1 \frac{d}{dt}(\phi_{11} + \phi_{21}) \\ &= N_1^2(\mathcal{P}_{11} + \mathcal{P}_{21}) \frac{di_1}{dt} = N_1^2\mathcal{P}_1 \frac{di_1}{dt} \end{aligned}$$

$$\begin{aligned} v_2 &= \frac{d(N_2\phi_{21})}{dt} = N_2 \frac{d}{dt}(\mathcal{P}_{21}N_1i_1) \\ &= N_2N_1\mathcal{P}_{21} \frac{di_1}{dt} \\ &= M_{21} \frac{di_1}{dt} \end{aligned}$$



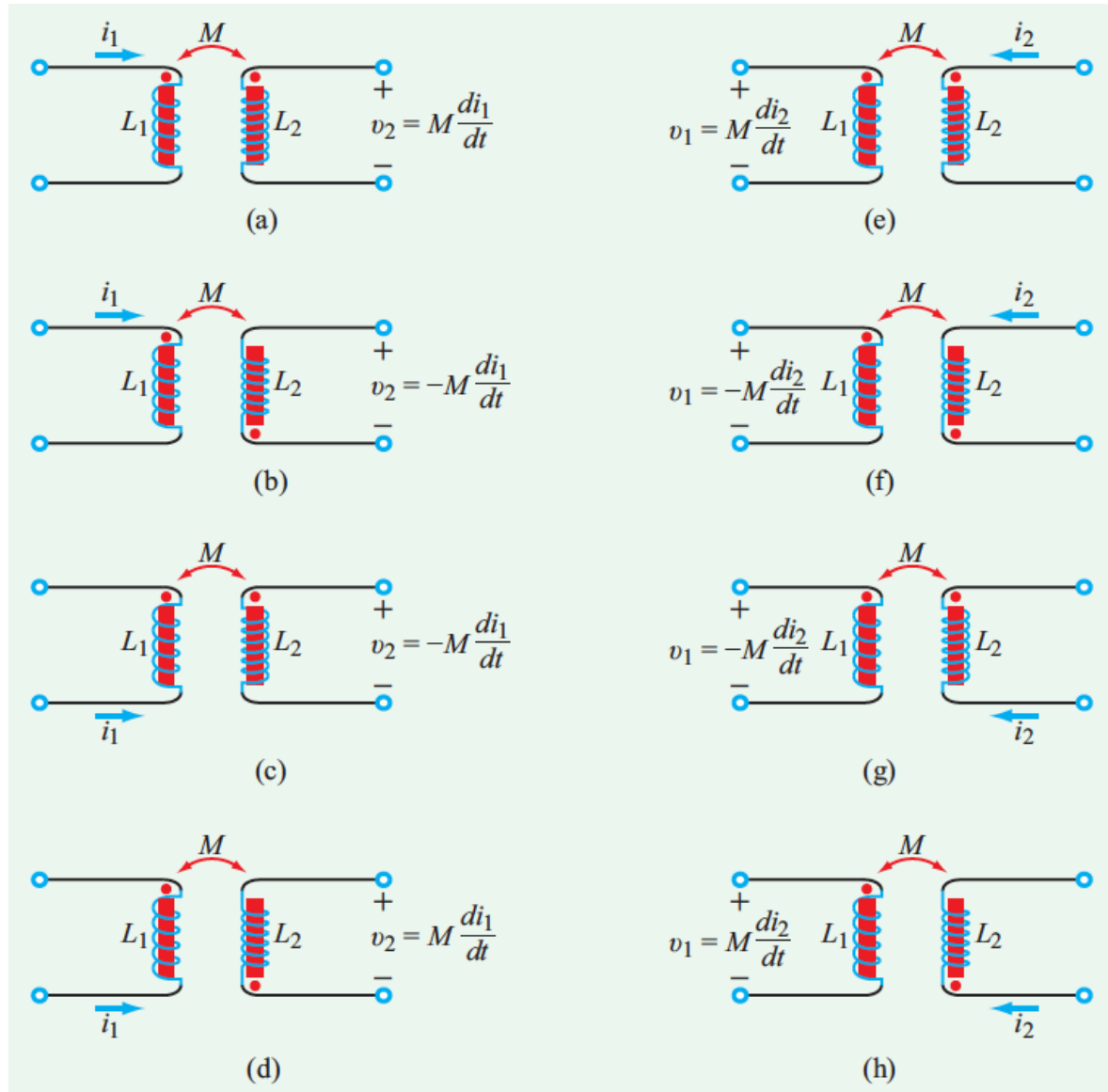Dot Convention: Defines Directions of Windings






Magnetically Coupled Circuits

- L_1, L_2 : self-inductances
- M : mutual inductance
- Dots: indicating polarity of mutually induced voltages.

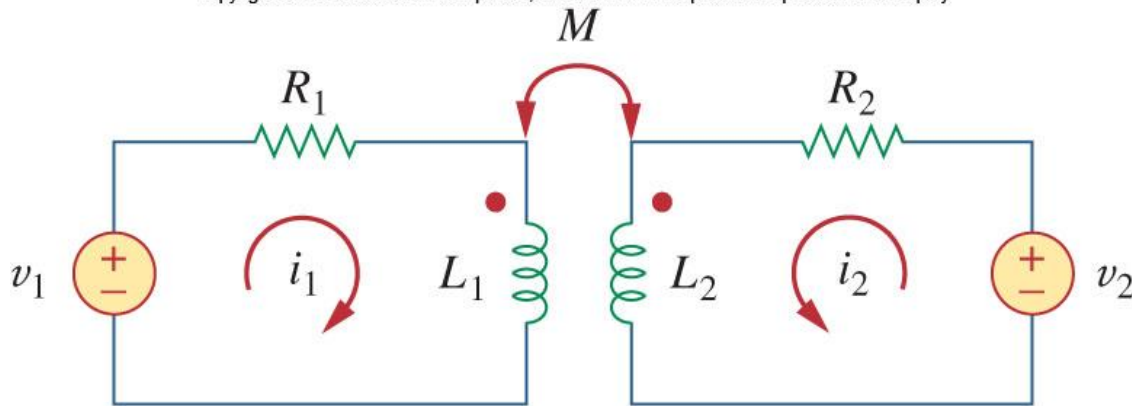
Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display





Analysis

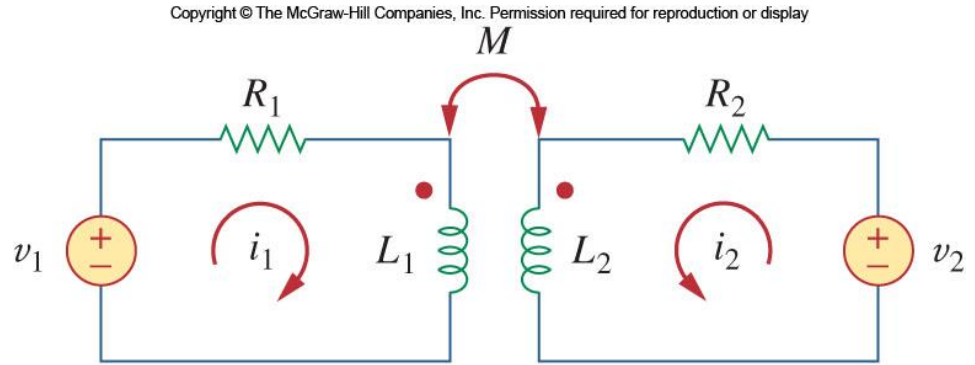
- Relate v_1, v_2 with i_1 and i_2 .
 - In time domain
 - In phasor domain





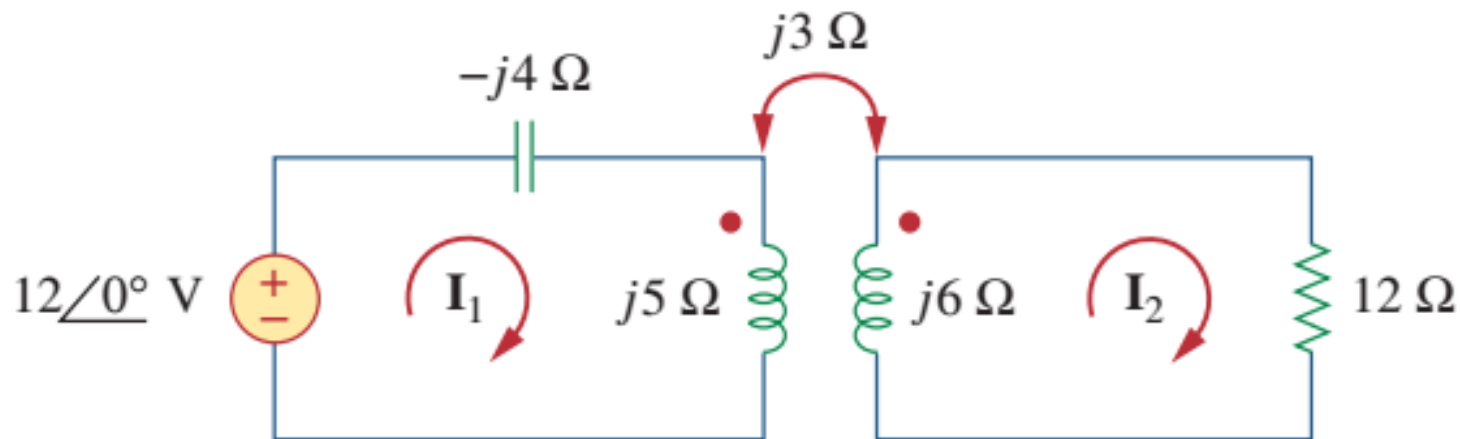Exercise


- Calculate the phasor currents \mathbf{I}_1 , and \mathbf{I}_2





Linear Transformers

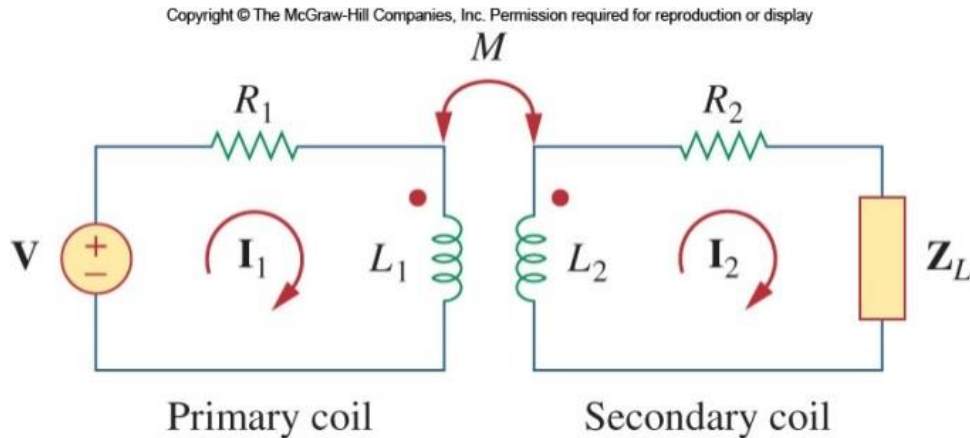
- A transformer is a magnetic device that takes advantage of mutual inductance.
 - Called linear if the coils are wound on a magnetically linear material, i.e. permeability μ is constant.





Revisit exercise

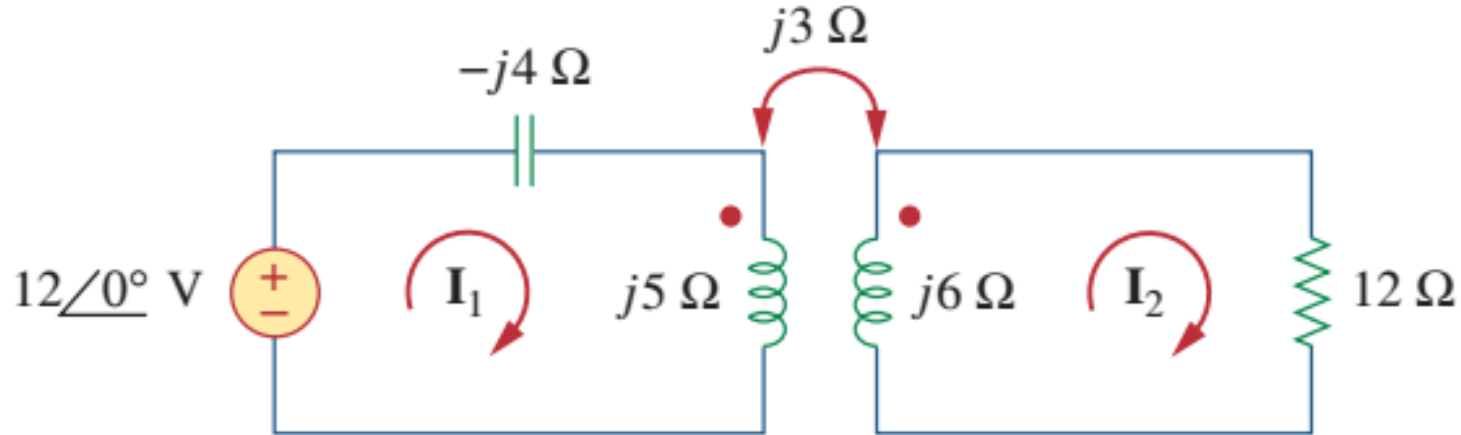- Calculate the phasor voltages V_1 , and V_2 across the inductors






Transformer Impedance

- An important parameter to know for a transformer is how the input impedance Z_{in} is seen from the source.
 - Z_{in} is important because it governs the behavior of the primary circuit.

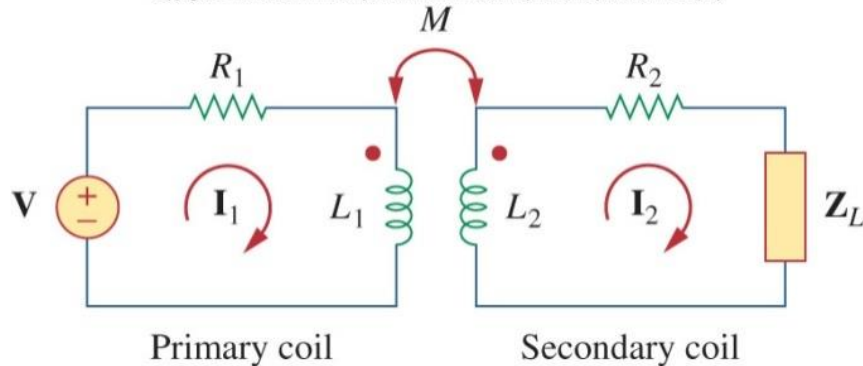Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display



$$Z_{in} = \frac{V}{I_1} = R_1 + j\omega L_1 + \frac{\omega^2 M^2}{R_2 + j\omega L_2 + Z_L}$$


Reflected impedance from secondary to primary

Energy in a Coupled Circuit


- The energy stored in an inductor is
- For coupled inductors, the total energy stored is

$$w = \frac{1}{2} L_1 i_1^2 + \frac{1}{2} L_2 i_2^2 \pm M i_1 i_2$$

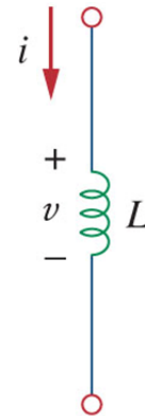- The positive sign is selected when the currents both enter or leave the dotted terminals.



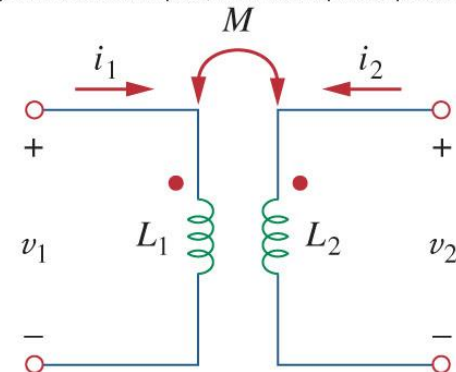Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display





Coupling Coefficient k


- The system cannot have negative energy

$$\frac{1}{2}L_1 i_1^2 + \frac{1}{2}L_2 i_2^2 - M i_1 i_2 \geq 0 \quad \Rightarrow \quad M \leq \sqrt{L_1 L_2}$$

- Define a parameter describes how closely M approaches upper limit.

$$k = \frac{M}{\sqrt{L_1 L_2}}$$


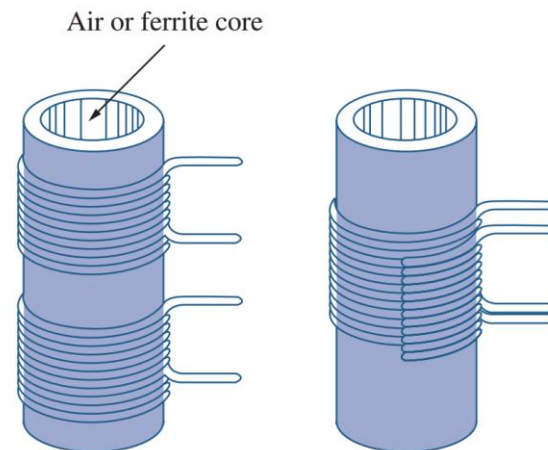
- Coupling coefficient, $0 \leq k \leq 1$.
- determined by the physical configuration of the coils.



Ideal Transformers

- The ideal transformer has:
 - Coils with very large reactance
($L_1, L_2, M \rightarrow \infty$)
 - Coupling coefficient $k=1$.
 - Primary and secondary coils are lossless, $R_1 = R_2 = 0$.

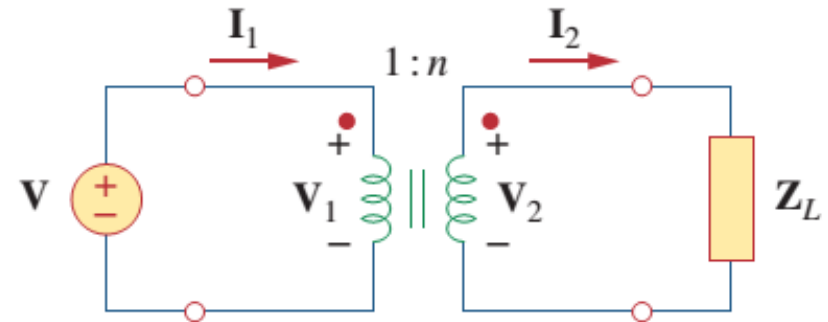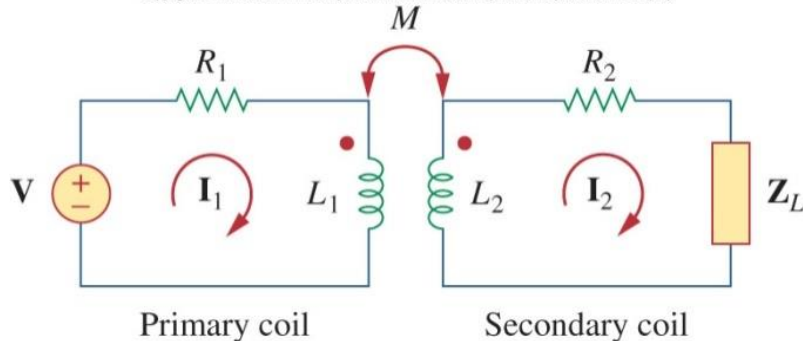
Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display



$$\frac{V_2}{V_1} = \frac{N_2}{N_1} = n$$

Ideal Transformers
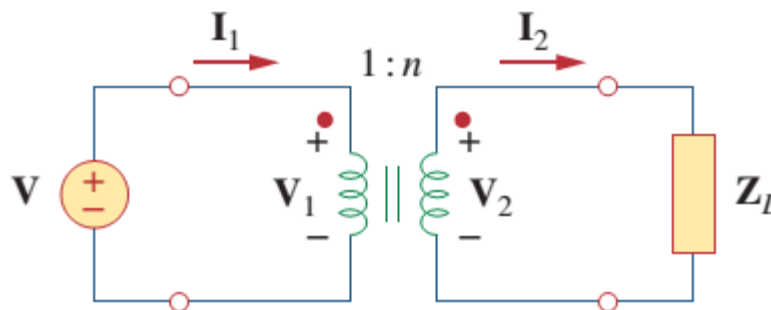
$$\frac{V_2}{V_1} = \frac{N_2}{N_1} = n$$




- The current is related as:
- Reflected impedance


$$Z_{in} = \frac{V_1}{I_1} =$$



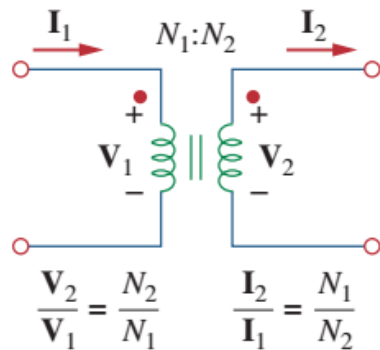
1. If V_1 and V_2 are *both* positive or both negative at the dotted terminals, use $+n$ in Eq. (13.52). Otherwise, use $-n$.
2. If I_1 and I_2 *both* enter into or both leave the dotted terminals, use $-n$ in Eq. (13.55). Otherwise, use $+n$.




(a)

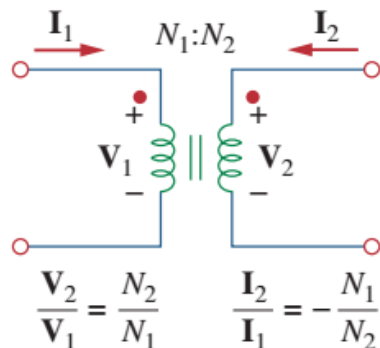

(b)

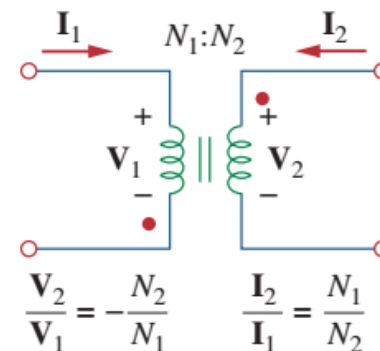

(c)

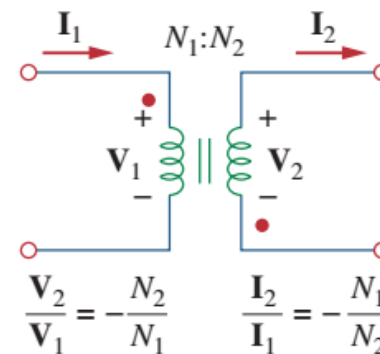


(d)




Practice

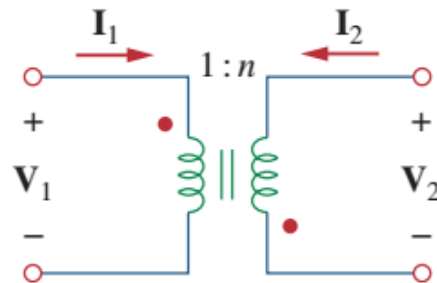
13.36 As done in Fig. 13.32, obtain the relationships between terminal voltages and currents for each of the ideal transformers in Fig. 13.105.




(a)

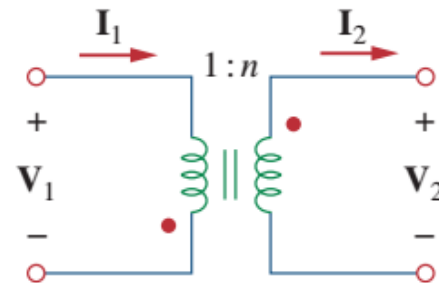

(b)

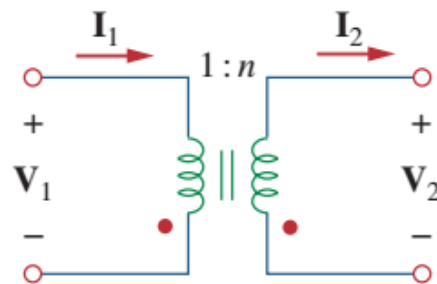

(c)

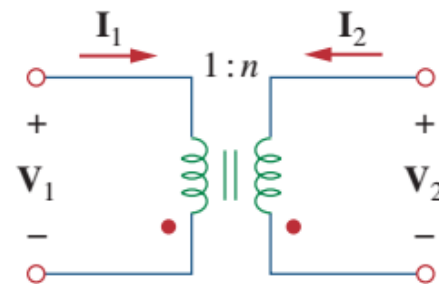


(d)



Ideal Transformers
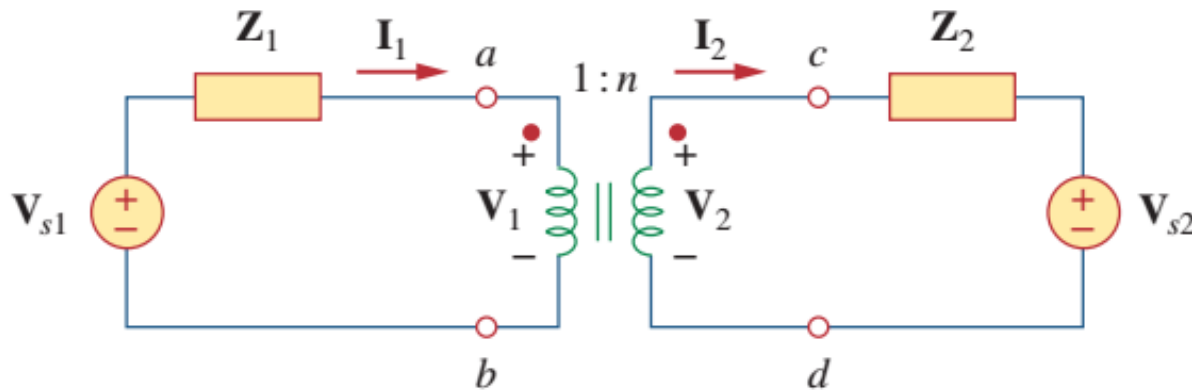
$$\frac{V_2}{V_1} = \frac{N_2}{N_1} = n$$





- The current is related as:




Ideal Transformers

$$\frac{V_2}{V_1} = \frac{N_2}{N_1} = n$$



- Reflected impedance and source

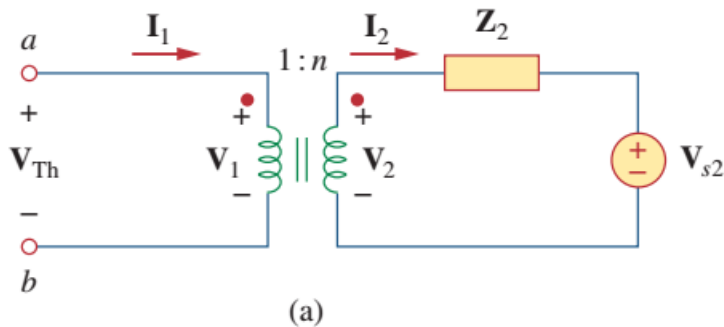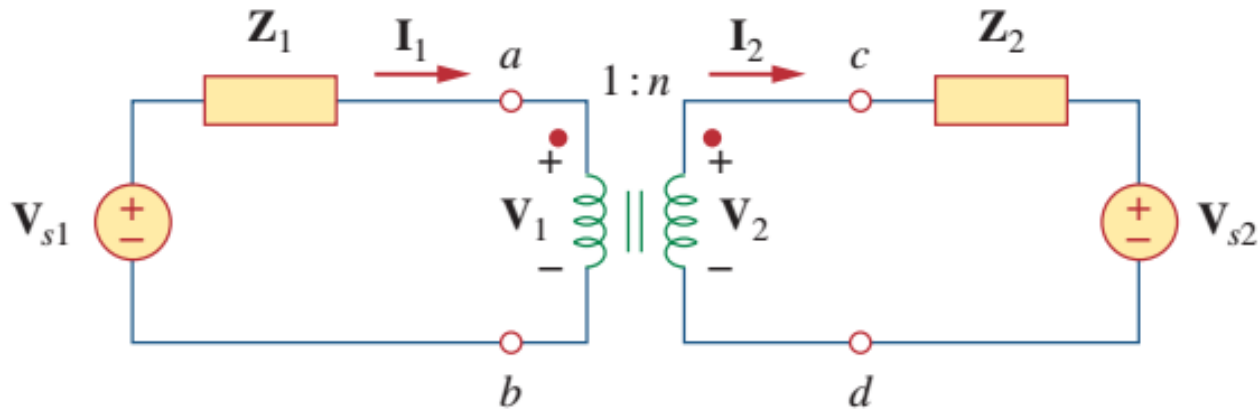

(a)

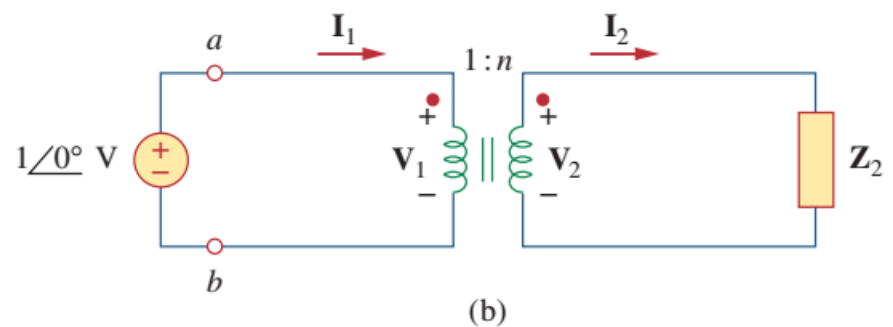


(b)

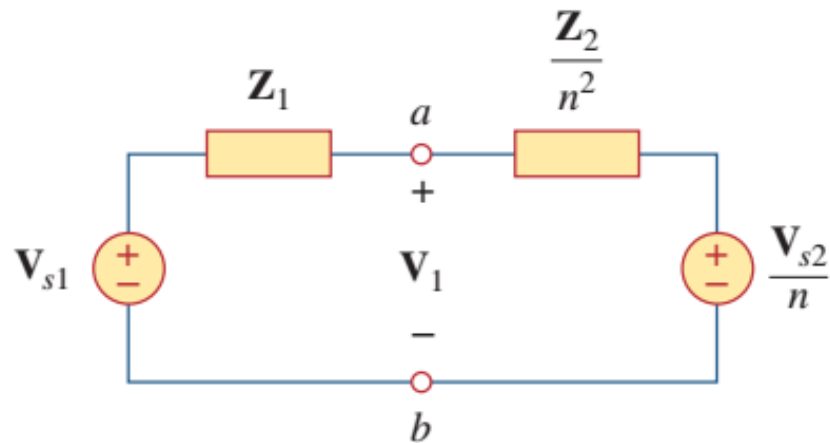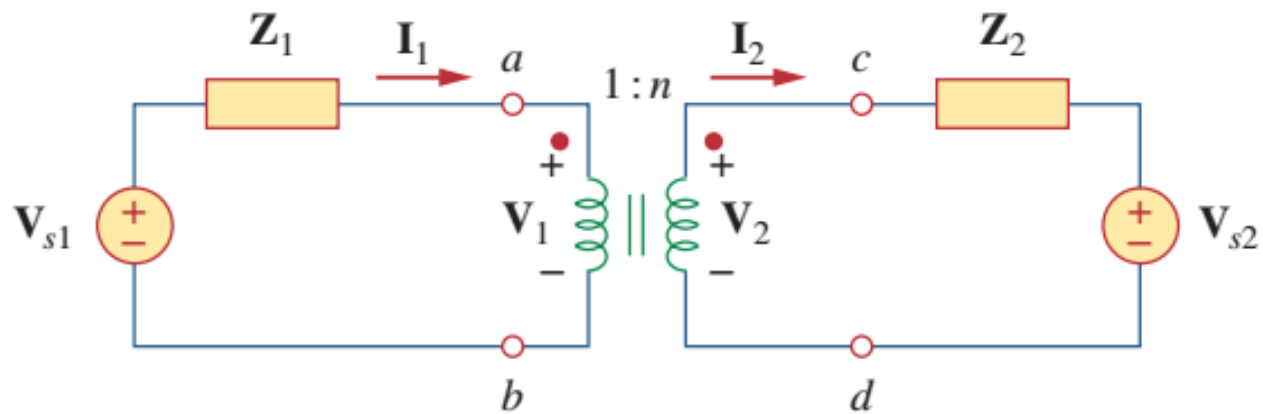




Ideal Autotransformer

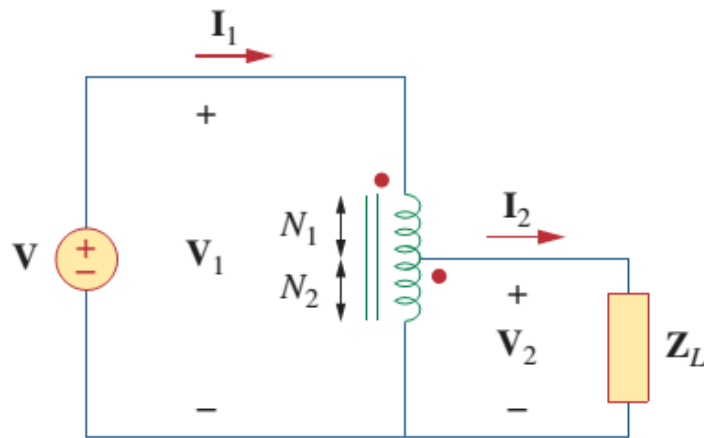- Autotransformer uses one winding for primary & secondary
 - It does not offer isolation!



$$\frac{V_1}{V_2} = \frac{N_1 + N_2}{N_2} = 1 + \frac{N_1}{N_2}$$
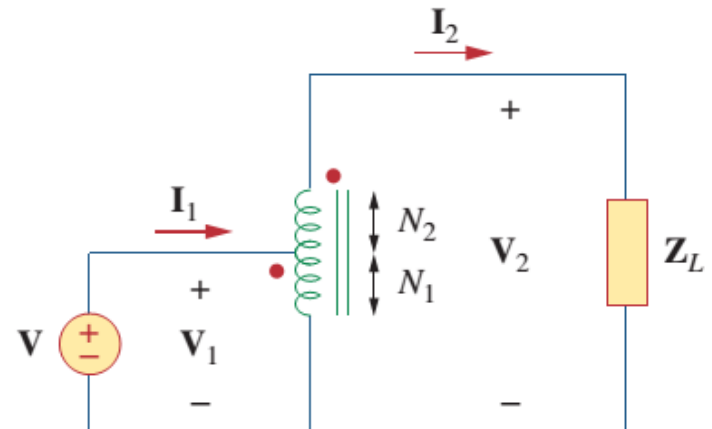
$$\frac{I_1}{I_2} = \frac{N_2}{N_1 + N_2}$$



$$\frac{V_1}{V_2} = \frac{N_1}{N_1 + N_2}$$

$$\frac{I_1}{I_2} = \frac{N_1 + N_2}{N_1} = 1 + \frac{N_2}{N_1}$$

$$S_1 = V_1 I_1^* = S_2 = V_2 I_2^*$$



Practice

- Find reflected impedance and \mathbf{I}_1

