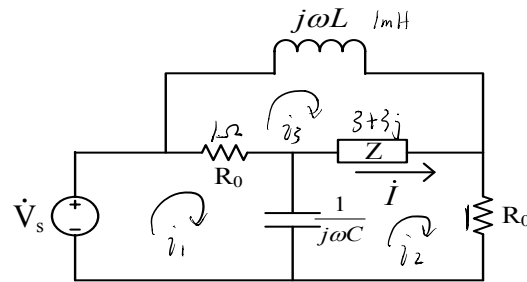


1. (10 points) Determine the value of C so that $\dot{I} = 0$ A. Assume $v_s(t) = \cos(1000t)$ V, $R_0 = 1 \Omega$, $Z = (3+j3) \Omega$ and $L = 1$ mH.



①


$$\begin{cases} -1 + 1 \cdot (i_1 - i_3) + \frac{1}{j\omega C} (i_1 - i_2) = 0 & -2 \\ \frac{1}{j\omega C} (i_2 - i_1) + (3+j3)(i_2 - i_3) + 1 \cdot i_2 = 0 & -2 \\ 1(i_3 - i_1) + j\omega L \cdot i_3 + (3+j3) \cdot (i_3 - i_2) = 0 & -2 \end{cases}$$

$$\Rightarrow \begin{cases} (1 + \frac{1}{j\omega C}) i_1 - \frac{1}{j\omega C} i_2 - i_3 = 1 \\ -\frac{1}{j\omega C} i_1 + (\frac{1}{j\omega C} + 4 + 3j) i_2 - (3+j3) i_3 = 0 \\ -i_1 - (3+j3) i_2 + (4 + j\omega L + 3j) i_3 = 0 \end{cases}$$

$$\therefore i = i_2 - i_3 = 0$$

$$\therefore i_2 = i_3 \quad -2$$
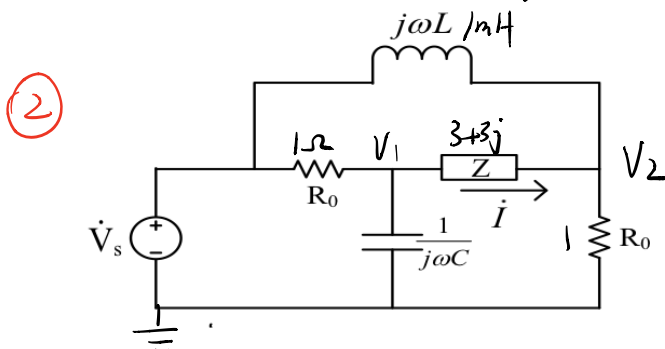
$$\Rightarrow C = \frac{1}{\omega} = 1 \text{ mF} \quad -2$$



$$\begin{cases} \frac{V_1 - 1}{1} + V_1 \cdot j\omega C + \frac{V_1 - V_2}{3+j3} = 0 & -3 \\ \frac{V_2 - 1}{1} + \frac{V_2 - V_1}{3+j3} + \frac{V_2}{1} = 0 & -3 \end{cases}$$


$$\therefore i = 0 \quad -2$$

$$\therefore V_1 = V_2$$


$$\Rightarrow C = \frac{1}{\omega} = 1 \text{ mF} \quad -2$$

2. (10 points) (1) Determine the value of R so that the maximum power can be delivered to the resistor R .

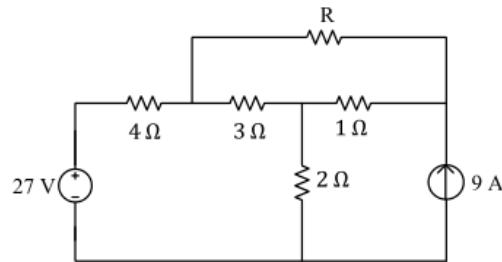
(2) Find the maximum power delivered to the resistor R .




2. Solution:

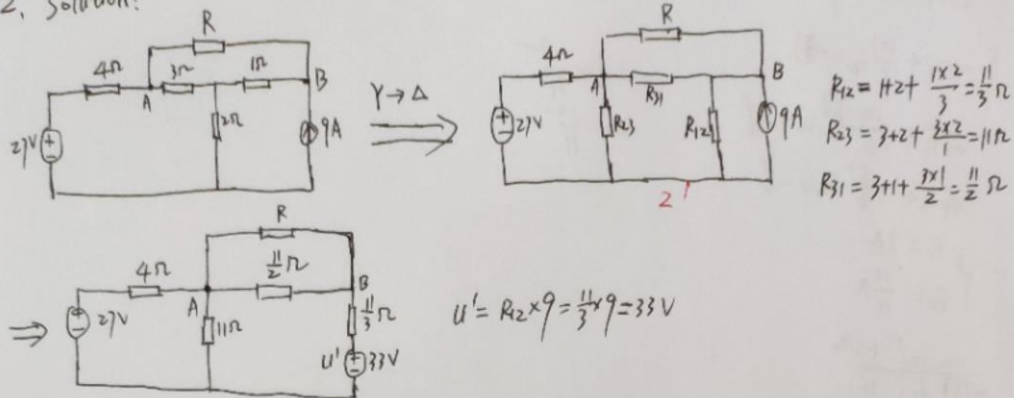

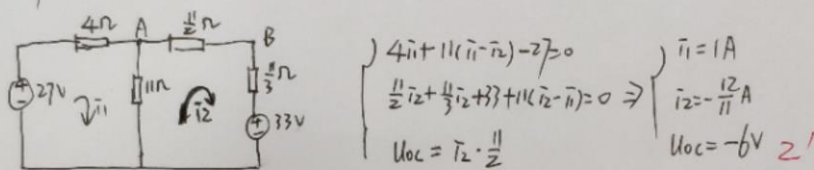
Firstly calculate open-circuit voltage of AB, U_{oc}



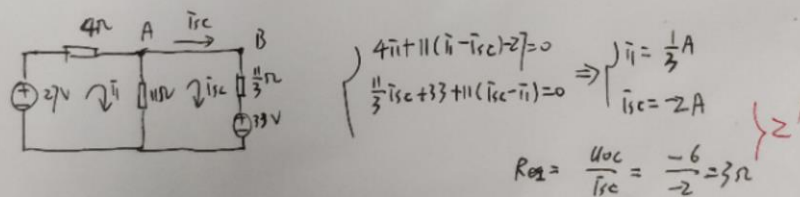Secondly, Calculate short-circuit current of AB, I_{sc}




So the Thevenin equivalent circuit is:

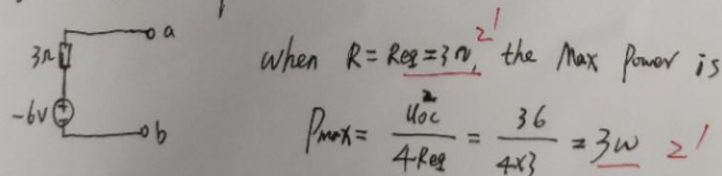

So, (1) the value of R is 3Ω

(2) Maximum power $P_{max} = 3W$

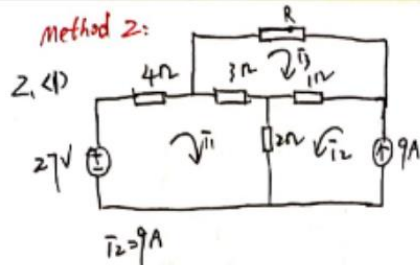

$$\begin{cases} 4i_1 + 3(i_1 - i_2) + 2(i_1 + 9) - 2 = 0 \\ i_2 R + 1 \times (i_2 + 9) + 3(i_2 - i_1) = 0 \end{cases} \quad (1)$$

$$\Rightarrow i_2 = \frac{-18}{3R+9} = \frac{-6}{R+3}$$

$$P_R = i_2^2 R = \left(\frac{-6}{R+3} \right)^2 \cdot R = \frac{36R}{(R+3)^2}$$

$$P_R' = 36 \frac{(R+3)^2 - 2R(R+3)}{(R+3)^4} = 36 \frac{-R+9}{(R+3)^3}$$

let $P_R' = 0$ we can get $R_1 = -3$ $R_2 = 9$

We know $R \in [0, +\infty]$

when $R \in [0, 3]$, P_R is monotone ~~decreased~~ ^{increased}

when $R \in [3, +\infty]$, P_R is monotone ~~increased~~ ^{decreased}


So when $R = 3\Omega$, the maximum power is

$$P_{R_{max}} = \frac{36 \times 3}{(3+3)^2} = 3W \quad (2)$$

(1) the value of R is 3Ω

(2) maximum power $P_{max} = 3W$


3. (10 points) In the following circuit, $V_s = 10\text{ V}$, $R_1 = 10\text{ k}\Omega$, $R_2 = 5\text{ k}\Omega$, $C = 50\text{ }\mu\text{F}$. The energy stored in the capacitor is $100\text{ }\mu\text{J}$ at $t = 0_-$. The switch is closed at $t = 0$. Find $v_{out}(t)$ for $t \geq 0$.

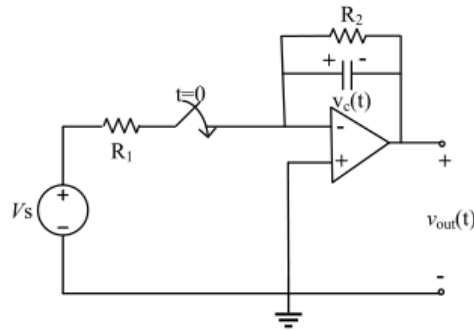

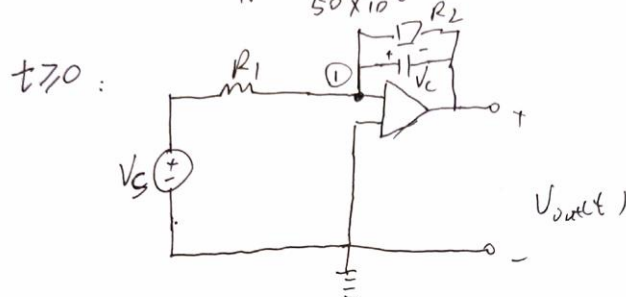Problem 3. (方法一)

$$\therefore W_C(0_-) = 100\text{ }\mu\text{J} = \frac{1}{2} \cdot C \cdot V_C(0_-)^2$$

$$\therefore V_C(0_-) = \pm \sqrt{\frac{2 \cdot 100 \cdot 10^{-6}}{50 \times 10^{-6}}} = \pm 2\text{ V}$$



For Node ①: $\frac{V_s}{R_1} = \frac{V_C}{R_2} + C \frac{dV_C}{dt}$

$$\therefore \frac{dV_C}{dt} + \frac{V_C}{R_2 C} = \frac{V_s}{R_1 C}$$

$$\Rightarrow \frac{dV_C}{dt} + 4V_C = 20$$

$$\therefore V_C = e^{-54t} \left[\int 20 e^{54t} dt + C_0 \right]$$

$$= e^{-4t} \left[\int 20 e^{4t} dt + C_0 \right]$$

$$= 5 + C_0 e^{-4t} \text{ V, } t \geq 0$$

Case A: $V_C(0_-) = 2\text{ V}$, $C_0 = -3$, $V_C(t) = 5 - 3e^{-4t} \text{ V, } t \geq 0$

$$\therefore v_{out}(t) = -V_C(t) = 3e^{-4t} - 5 \text{ V, } t \geq 0$$

Case B: $V_C(0_-) = -2\text{ V}$, $C_0 = -7$, $V_C(t) = 5 - 7e^{-4t} \text{ V, } t \geq 0$

$$\therefore v_{out}(t) = -V_C(t) = 7e^{-4t} - 5 \text{ V, } t \geq 0$$

Problem 3. (方法=)

$$t=0-, W_C(0-) = \frac{1}{2} C V_C^2(0-) = 100 \mu J$$

$$\therefore V_C(0-) = \pm \sqrt{\frac{2 \times 100 \times 10^{-6}}{50 \times 10^{-6}}} = \pm 2 V = V_C(0+)$$

$$\therefore V_{out}(0+) = -V_C(0+) = \pm 2 V. \quad 2'$$

$$t=\infty, \cancel{V_{out}(\infty)} = \frac{V_S}{R_1} + \frac{V_{out}(\infty)}{R_2} = 0.$$

$$\therefore V_{out}(\infty) = -\frac{R_2}{R_1} V_S = -5 V. \quad 2'$$

$$\tau = R_2 C = 5 \times 10^3 \times 50 \times 10^{-6} = 0.25 S. \quad 2'$$

$$\therefore V_{out}(t) = V_{out}(\infty) + (V_{out}(0) - V_{out}(\infty)) \cdot e^{-\frac{t}{\tau}}$$

$$= -5 + (2 - (-5)) e^{-4t}$$


$$= -5 + 7e^{-4t} V, \quad t \geq 0 \quad 2'$$

$$\text{OR } V_{out}(t) = -5 + (-2 - (-5)) e^{-4t}$$


$$= -5 + 3e^{-4t} V, \quad t \geq 0. \quad 2'$$

4. (10 points) The switch is closed at $t = 0$ s. $V_s = 6$ V, $R = 5$ Ω , $L = 1$ H, $C = 0.25$ F. $i(0_-) = 0$, $v_c(0_-) = 3$ V. Please

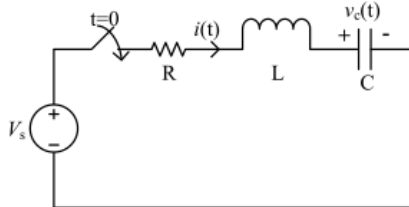- (1) write the differential equation that $v_c(t)$ should obey and solve $v_c(t)$ in time domain for $t \geq 0$,
- (2) construct the S-domain circuit. Then solve $V_c(S)$ in S-domain, and use inverse Laplace transform to find $v_c(t)$ in time domain for $t \geq 0$,



4. (10 points)

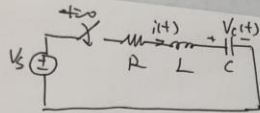

$V_s = 6$ V, $R = 5$ Ω , $L = 1$ H, $C = 0.25$ F. $i(0_-) = 0$, $v_c(0_-) = 3$ V.

- (1) write the differential equation that $v_c(t)$ should obey and solve $v_c(t)$.
- (2) construct the S-domain circuit, solve $V_c(S)$ in S-domain, use inverse Laplace transform to find $v_c(t)$.

Solution:

$$\begin{cases} LC \frac{d^2 v_c(t)}{dt^2} + R \frac{dv_c(t)}{dt} + v_c(t) = V_s & \dots 1' \\ v_c(0_+) = 3V & \dots 1' \\ \frac{dv_c(0_+)}{dt} = 0 & \dots 1' \end{cases}$$

$$\Rightarrow v_c(t) = A_1 e^{-t} + A_2 e^{-4t} + 6, \quad \dots 1'$$

$$A_1 = -4, A_2 = 1$$

$$\Rightarrow v_c(t) = -4e^{-t} + e^{-4t} + 6 \text{ V } (t \geq 0) \quad \dots 1'$$

$$V_c(s) = \frac{6 - \frac{3}{s}}{s + \frac{4}{s}} \times \frac{\frac{4}{s} + \frac{3}{s}}{s + \frac{4}{s}}$$


$$= \frac{12}{(s+4)(s+1)s} + \frac{3}{s}$$

$$= \frac{K_1}{s} + \frac{K_2}{s+1} + \frac{K_3}{s+4} + \frac{3}{s} \quad \dots 2'$$

$$\Rightarrow K_1 = 3, K_2 = -4, K_3 = 1$$



$$\Rightarrow V_c(s) = \frac{6}{s} - \frac{4}{s+1} + \frac{1}{s+4}$$
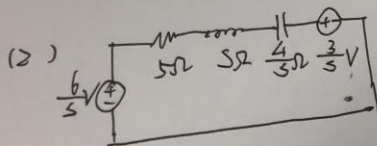
$$\Rightarrow v_c(t) = 6 - 4e^{-t} + e^{-4t} \text{ V } (t \geq 0) \quad \dots 1'$$




5. (12 points) Assume $v(t)=4\cos(4t)$ V, determine:

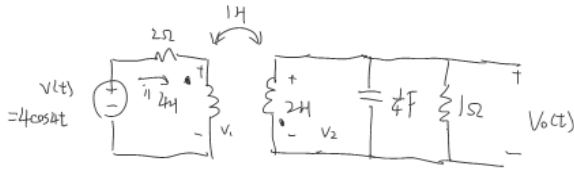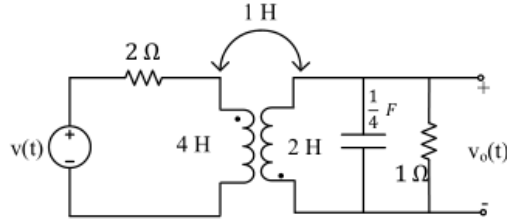- (1) the coupling coefficient,
- (2) voltage $v_o(t)$ across the $1\ \Omega$ resistor,
- (3) the input impedance Z_{in} as seen from the voltage source.



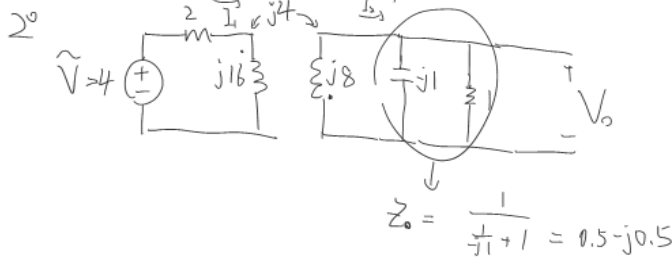2' 1° $k = \frac{M}{\sqrt{L_1 L_2}} = \frac{1}{\sqrt{8}} = \frac{\sqrt{2}}{4}$



4' 方程

$$\textcircled{1} I_1 R + L_1 \cdot j\omega I_1 + M \cdot j\omega I_2 = 4$$

$$\textcircled{2} M \cdot j\omega I_1 + L_2 \cdot j\omega I_2 + I_2 \cdot (0.5 - j0.5) = 0$$

$$\Rightarrow 2I_1 + j16I_1 + j4I_2 = 4$$

$$j4I_1 + j8I_2 + I_2(0.5 - j0.5) = 0$$

3' 结果 \Rightarrow

$$I_1(2 + j16) + j4I_2 = 4$$

$$j4I_1 = I_2(-0.5 - j7.5)$$


(中间步骤)

$$\therefore v_o(t) = 0.107 \cos(4t + 57.58^\circ) \text{ V}$$

3' $\textcircled{3} Z_{in} = 2 + j16 + \frac{\omega^2 M^2}{j8 + \frac{1-j}{2}} = 2.14 + j13.88 \Omega$

6. (12 points) In the following three-phase circuit, $\dot{U}_{A_{rms}} = 220 \angle 0^\circ \text{ V}$, $\dot{U}_{B_{rms}} = 220 \angle 120^\circ \text{ V}$, $\dot{U}_{C_{rms}} = 220 \angle 240^\circ \text{ V}$, $Z_1 = 50 + 50j \ \Omega$, $Z_2 = 20 \ \Omega$, $Z_3 = 40 + 80j \ \Omega$. Find:

- (1) the average power generated by \dot{U}_A ,
- (2) the power factor of \dot{U}_A ,
- (3) the total complex power generated by the three-phase voltage sources.

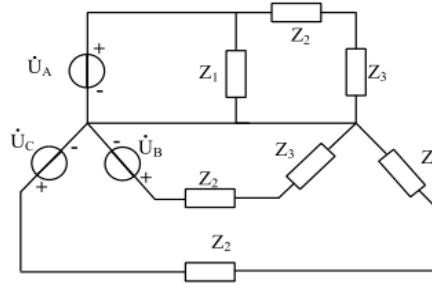

Pro6

Solution:

(1)

$$\dot{I}_{A_{rms}} = \frac{\dot{U}_{A_{rms}}}{Z_1} + \frac{\dot{U}_{A_{rms}}}{Z_2 + Z_3} \quad (1')$$

$$\begin{aligned} P_A &= U_{A_{rms}} \times I_{A_{rms}} \times \cos(\theta_{\dot{U}_{A_{rms}}} - \theta_{\dot{I}_{A_{rms}}}) \\ &= 220 \times \frac{220}{50\sqrt{2}} \times \cos(45^\circ) + 220 \times \frac{220}{100} \times \cos(53.1^\circ) \quad (2') \\ &= 774.4 \text{ W} \end{aligned}$$

(2)

$$\begin{aligned} Q_A &= U_{A_{rms}} \times I_{A_{rms}} \times \sin(\theta_{\dot{U}_{A_{rms}}} - \theta_{\dot{I}_{A_{rms}}}) \\ &= 220 \times \frac{220}{50\sqrt{2}} \times \sin(45^\circ) + 220 \times \frac{220}{100} \times \sin(53.1^\circ) \\ &= 871.2 \text{ var} \quad (2') \end{aligned}$$

$$pf_A = \frac{P_A}{\sqrt{P_A^2 + Q_A^2}} = \frac{774.4}{\sqrt{774.4^2 + 871.2^2}} = 0.664 \quad (2') \quad (\text{lagging}) \quad (1')$$

(2)

$$S_A = 774.4 + j871.2 \text{ VA}$$


$$\begin{aligned} S_B &= \dot{U}_{B_{rms}} \times \dot{I}_{B_{rms}}^* \\ &= \dot{U}_{B_{rms}} \times \left(\frac{\dot{U}_{B_{rms}}}{Z_2 + Z_3} \right)^* \\ &= 220 \angle 120^\circ \times \left(\frac{220 \angle 120^\circ}{20 + 40 + j80} \right)^* \\ &= 290.4 + j387.2 \text{ VA} \quad (1') \end{aligned}$$

$$\begin{aligned} S_C &= \dot{U}_{C_{rms}} \times \dot{I}_{C_{rms}}^* \\ &= \dot{U}_{C_{rms}} \times \left(\frac{\dot{U}_{C_{rms}}}{Z_2 + Z_3} \right)^* \\ &= 220 \angle 240^\circ \times \left(\frac{220 \angle 240^\circ}{20 + 40 + j80} \right)^* \\ &= 290.4 + j387.2 \text{ VA} \quad (1') \end{aligned}$$

$$\begin{aligned} S &= S_A + S_B + S_C \\ &= (774.4 + 290.4 + 290.4) + j(871.2 + 387.2 + 387.2) \text{ VA} \\ &= 1355.2 + j1645.6 \text{ VA} \quad (2') \end{aligned}$$

7. (12 points) The AC circuit is as shown below. Find:

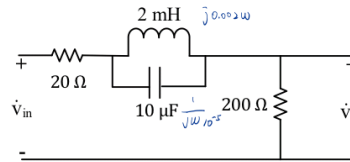- (1) the transfer function $H(j\omega) = \frac{\dot{V}_o}{\dot{V}_{in}}$,
- (2) the type of the filter,
- (3) the center frequency ω_0 ,
- (4) the bandwidth of the filter.



$$1) \frac{V_{in} - V_o}{R_1 + R_L \parallel R_C} = \frac{V_o}{R_2}$$

$$H(j\omega) = \frac{200}{20 + R_L \parallel R_C + 200} = \frac{200}{220 + \frac{200}{0.002j\omega + \frac{10^5}{j\omega}}} = \frac{200}{220 + j\omega \frac{2 \times 10^{-3}}{1 - \omega^2 \times 2 \times 10^{-8}}} = \frac{10}{1 + \frac{j\omega}{10^7 - 2 \times 10^{-5} \omega^2}}$$

$$= \frac{200 - 4 \times 10^{-6} \omega^2}{220 - 4.4 \times 10^{-6} \omega^2 + 2 \times 10^{-3} j\omega} = \frac{10^7 - 0.2 \omega^2}{1.1 \times 10^7 - 0.22 \omega^2 + 100 j\omega} = \frac{2 \times 10^{-5} j\omega + \frac{10^7}{2.2 \times 10^{-5} j\omega + 1}}{2.2 \times 10^{-5} j\omega + \frac{1.1 \times 10^7}{j\omega} + 1}$$

$$= \frac{5 \times 10^7 - \omega^2}{5.5 \times 10^7 - 1.1 \omega^2 + 500 j\omega} = \frac{200}{220 + \frac{j\omega 10^7}{5 \times 10^7 - \omega^2}} \quad 2'$$

以上形式及方便化简成以上形式的得4分，相差较远难以化简成以上形式的酌情扣1-2分。

未代入数据前都是正确的得2分，代入数据只有最后答案化错的得3分。

本小问共4分。

$$\begin{aligned} (2) \quad \omega \rightarrow 0 \quad H(j\omega) &\rightarrow \frac{10}{11} \\ \omega \rightarrow \infty \quad H(j\omega) &\rightarrow \frac{10}{11} \\ \omega \rightarrow \omega_0 \quad H(j\omega) &\rightarrow 0 \end{aligned} \quad \left. \begin{array}{l} \\ \\ \end{array} \right\} 1'$$

Bandreject Filter

答案正确过程错误不扣分，中文不得答案分。

$$(3) \quad j\omega L + \frac{1}{j\omega C} = 0 \quad 1'$$

$$\omega_0 = \sqrt{\frac{1}{LC}} \quad 1'$$

$$= 7071.07 \text{ rad/s} \quad 1'$$

单位及未化成小数扣1分。

$$(4) \quad |H(j\omega)| = \frac{-200 \omega^2 + 10^{10}}{\sqrt{(-220 \omega^2 + 1.1 \times 10^8)^2 + (10^5 \omega)^2}} = \frac{1}{\sqrt{2}} \frac{10}{11} \quad 1'$$

$$\textcircled{1} \quad \omega > 7071.07 \text{ rad/s}$$

$$\textcircled{2} \quad \omega < 7071.07 \text{ rad/s}$$

$$\omega_1 = -6847.446 \text{ rad/s} < 0$$

$$\omega_1 = 6847.446 \text{ rad/s}$$

$$\omega_2 = 7301.992 \text{ rad/s}$$


$$\omega_2 = -7301.992 \text{ rad/s} < 0 \quad 1'$$

$$B = \omega_2 - \omega_1 = 454.546 \text{ rad/s} \quad 1'$$


8. (12 points) In the following AC circuit, $R_1 = 10 \text{ k}\Omega$, $R_2 = 1 \text{ k}\Omega$, $R_3 = 10 \text{ k}\Omega$, $R_4 = 100 \text{ k}\Omega$, $R_5 = 5 \text{ k}\Omega$, $C_1 = 10 \text{ }\mu\text{F}$, $C_2 = 0.1 \text{ }\mu\text{F}$, $C_3 = 0.2 \text{ }\mu\text{F}$.

(1) find $H(j\omega) = \frac{\dot{V}_o}{\dot{V}_{in}}$,

(2) sketch the Bode plot of H, please label the corner frequencies, the gains, phases and slopes of the plot.

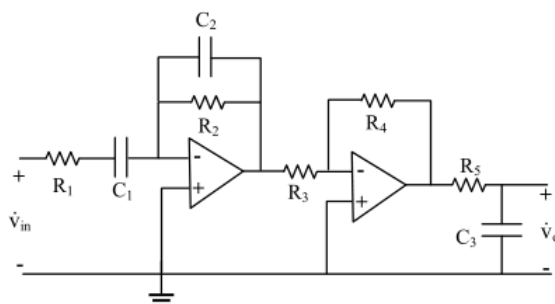

Question 8

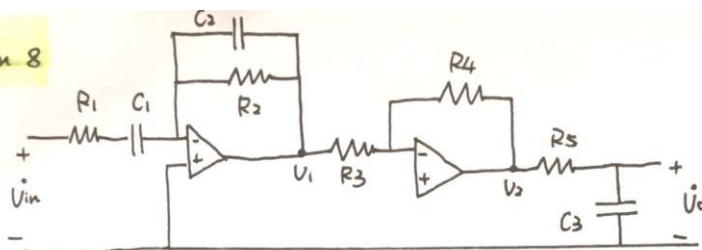

第1问共4分, 1) 公式2分, 答案2分


$$\frac{\dot{V}_{in}}{R_1 + 1/j\omega C_1} + \frac{V_1}{R_2} + \frac{V_1}{1/j\omega C_2} = 0$$

$$\frac{V_1}{R_3} + \frac{V_2}{R_4} = 0$$

$$\frac{V_2 - V_o}{R_5} = \frac{V_o}{1/j\omega C_3}$$


$$\Rightarrow H(j\omega) = \frac{\dot{V}_o}{\dot{V}_{in}} = \frac{0.1 j\omega}{(1 + \frac{j\omega}{10})(1 + \frac{j\omega}{10^3})(1 + \frac{j\omega}{10^4})}$$

第2问共8分, 2) 每图4分

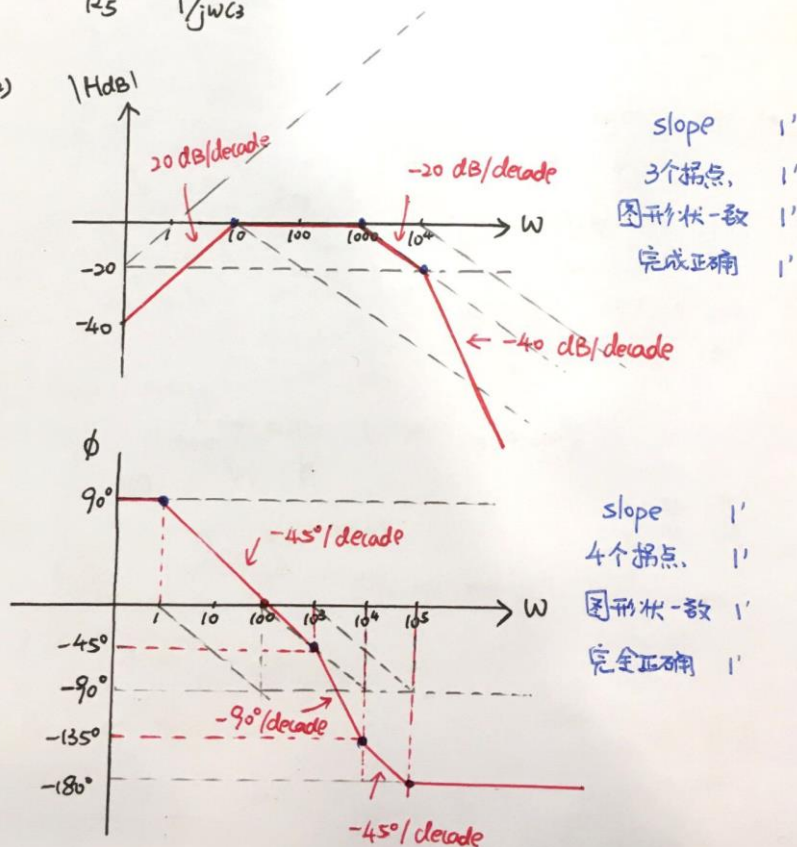


9. (12 points) Initially, $i(0_-) = 0$ A, $v_c(0_-) = 0$ V. The switch is closed at $t=0$ s.

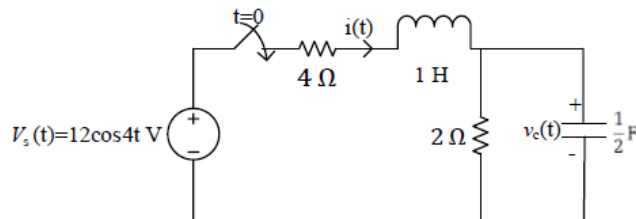- (1) build the phasor domain circuit, solve \tilde{V}_c in phasor domain, and convert it back to time domain to find $v_c(t)$ for $t \geq 0$,
 (2) construct the S-domain circuit, solve $V_c(s)$ in S-domain, and use inverse Laplace transform to find $v_c(t)$ for $t \geq 0$ in time domain,
 (3) compare the solutions of $v_c(t)$ for $t \geq 0$ in (1) and (2) and explain the relationship.



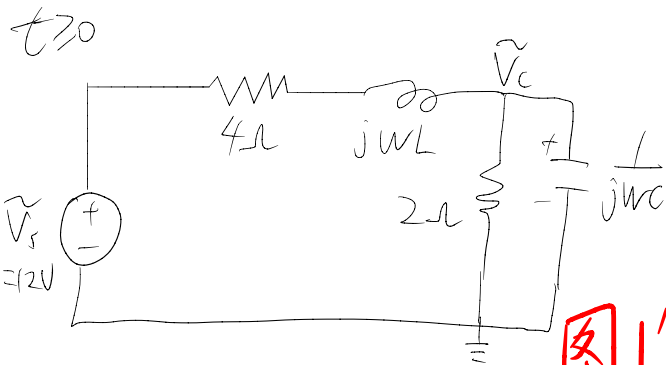(1) $\omega = 4 \text{ rad/s}$ $i(0^+) = i(0^-) = 0 \text{ A}$ $v_c(0^+) = v_c(0^-) = 0 \text{ V}$



$$\frac{\tilde{V}_c - 12}{4 + j4} + \frac{\tilde{V}_c}{2} + \frac{\tilde{V}_c}{-j0.5} = 0$$

$$\tilde{V}_c = 1.073 \angle -116.57^\circ = -0.48 - j0.96 \text{ V}$$


$$j\omega L = j4 \Omega \quad \frac{1}{j\omega C} = -j0.5 \Omega$$

$$v_c(t) = 1.073 \cos(4t - 116.57^\circ) \text{ V} \quad (t \geq 0)$$

$$= [1.073 \cos(4t - 116.57^\circ)] u(t) \text{ V}$$

$$= -1.073 \cos(4t + 63.43^\circ) \text{ V}$$

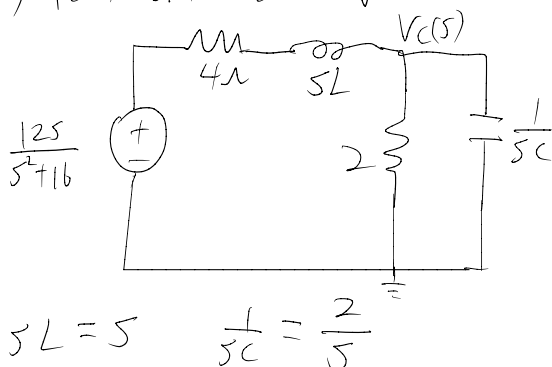(2) $i(0^+) = 0 \text{ A}$ $v_c(0^+) = 0 \text{ V}$



$$sL = s \quad \frac{1}{sC} = \frac{2}{s}$$

$$\frac{V_c(s) - \frac{12s}{s^2+16}}{4+s} + \frac{V_c(s)}{2} + \frac{V_c(s)}{\frac{2}{s}} = 0$$

$$V_c(s) = \frac{24s}{(s^2+16)(s+2)(s+3)}$$

图 1'

$$V_c(s) = \frac{As+B}{s^2+16} + \frac{C}{s+2} + \frac{D}{s+3}$$

$$C = -2.4 \quad D = 2.88$$

(ABCD 共 2')

$$(As+13)(s+2)(s+3) - 2.4(s^2+16)(s+3) + 2.88(s^2+16)(s+2) = 24s$$

$$A = -0.48$$

$$B = 3.84$$

$$V_c(s) = \frac{-0.48s + 3.84}{s^2 + 16} + \frac{-2.4}{s+2} + \frac{2.88}{s+3} = \frac{-0.48s + 0.96 \cdot 4}{s^2 + 16} + \frac{-2.4}{s+2} + \frac{2.88}{s+3}$$

$$V_c(t) = [-0.48 \cos 4t + 0.96 \sin 4t - 2.4e^{-2t} + 2.88e^{-3t}]u(t) \quad V \quad 1'$$

$$= [1.073 \cos(4t - 116.57^\circ) - 2.4e^{-2t} + 2.88e^{-3t}]u(t) \quad V \quad (1.11/0') \quad 1'$$

$$(3) \quad -0.48 \cos 4t + 0.96 \sin 4t = 1.073 \cos(4t - 116.57^\circ)$$

The solutions of $V_c(t)$ for $t \geq 0$ in (1) and (2) are the same at steady-state 2'

phasor \rightarrow steady-state Laplace \rightarrow Transient-state and steady-state

(2) is the absolutely correct way to solve this problem

1 第三问强调了steady-state相同即给2分，如果直接说 (1) 与 (2) 问

答案相等不得分

2 第二问ABCD处，求对一个给0.5分，满分2分

3 强调第一问和第二问 $V(t)$ 最终答案单位，少一个扣一分，单位扣分上限1分

4 答案写分数不额外扣分

5 允许答案有小量误差