


RULES:

- Please try to work on your own. Discussion is permissible, but identical submissions are unacceptable! See “上海科技大学学生学术诚信规范与管理办法”, <http://sist.shanghaitech.edu.cn/cn/NewsDetail.asp?id=782>.
- Please show all intermediate steps: a correct solution without an explanation will get zero credit.
- Please submit on time. **NO late submission will be accepted.**
- Please **prepare your submission in English only.** No Chinese submission will be accepted.


1. [10%] A 80KHz sinusoidal voltage has zero phase angle and a maximum amplitude of 25mV. When this voltage is applied across the terminals of a capacitor, the resulting steady-state current has a maximum amplitude of 628.32 μ A.
 - a) What is the frequency of the current in radians per second?
 - b) What is the phase angle of the current?
 - c) What is the capacitive reactance of the capacitor?
 - d) What is the capacitance of the capacitor in microfarads?
 - e) What is the impedance of the capacitor?

2. [8%] Use the concept of the phasor to combine the following sinusoidal functions into a single trigonometric expression:
 - a) $y = 50 \cos(500t + 60^\circ) + 100 \cos(500t - 30^\circ)$,
 - b) $y = 200 \cos(377t + 50^\circ) - 100 \sin(377t + 150^\circ)$,
 - c) $y = 80 \cos(100t + 30^\circ) - 100 \sin(100t - 135^\circ) + 50 \cos(100t - 90^\circ)$
 - d) $y = 250 \cos(\omega t) + 250 \cos(\omega t + 120^\circ) + 250 \cos(\omega t - 120^\circ)$.

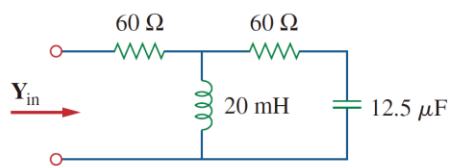3. [8%] At $\omega = 1000 \text{ rad/s}$, find the input admittance of each of the circuits in Fig.1.



(a)

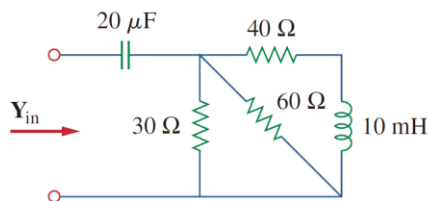

(b)

Fig. 1

4. [10%] Find Z_{ab} for the circuit shown in Fig.2.

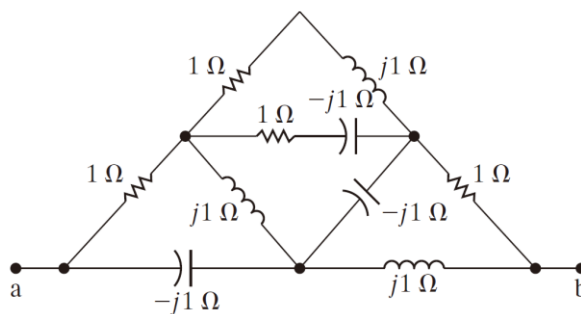


Fig. 2

5. [8%] Using node analysis to determine V_o and I_o in the circuit shown in Fig. 3.

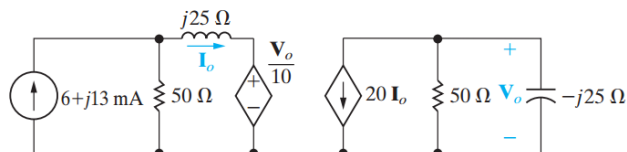


Fig. 3

6. [8%] Using mesh analysis to determine V_o and I_o in the circuit below.

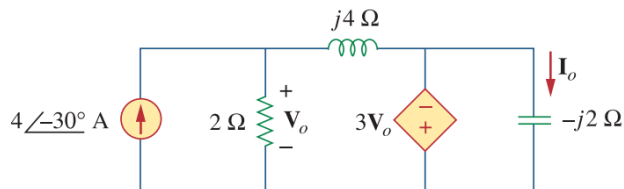


Fig. 4

7. [8%] Use the method of source transformation to find I_x in the circuit of Fig. 5.

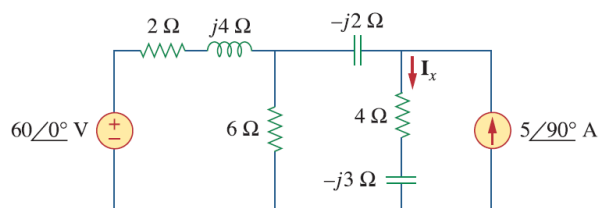


Fig. 5

8. [10%] Find the Norton equivalent circuit with respect to the terminals a,b for the circuit shown in Fig. 6 when $V_s = 5\angle 0^\circ V$.

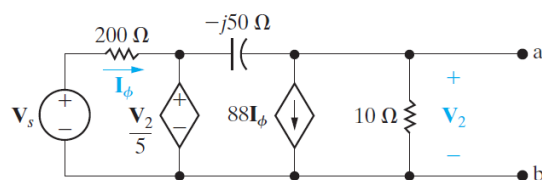


Fig. 6

9. [12%] The circuit shown in Fig. 7 is operating at a frequency of 10 rad/s. Assume α is real and lies between -10 and +10, that is, $-10 \leq \alpha \leq 10$.
- Find the value of α so that the Thevenin impedance looking into the terminals a,b is purely resistive.
 - What is the value of the Thevenin impedance for the α found in (a).
 - Can α be adjusted so that the Thevenin impedance equals $500 - j500 \Omega$? If so, what is the value of α ?
 - For what values of α will the Thevenin impedance be inductive?

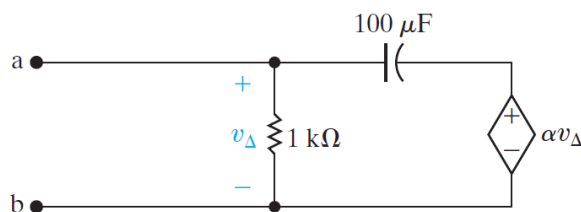


Fig. 7

10. [8%] For the op amp circuit in the figure below, obtain $V_o(t)$. Assume the op amp is ideal.

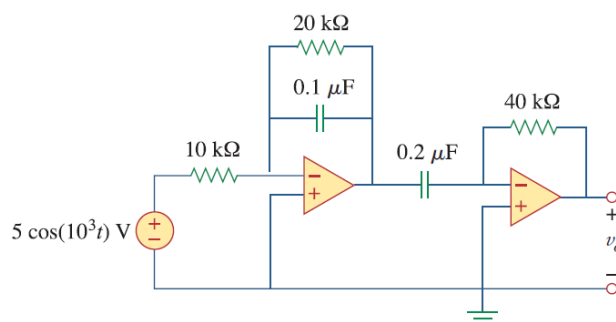


Fig. 8

11. [10%] The oscillator circuit in the figure below uses an ideal op amp.
- (a) Calculate the minimum value of R_o that will cause oscillation to occur.
- (b) Find the frequency of oscillation.

Hint: refer to Section 10.9.2 of reference

[1] Charles K. Alexander and Matthew N. O. Sadiku, *Fundamentals of Electric Circuits*, 5th edition, McGraw Hill, 2012.

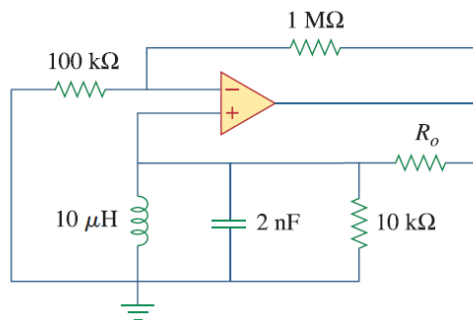


Fig. 9