

Homework 7

Due date:


May.26th, 2021

Turn in your homework in class

Rules:

- Please work on your own. Discussion is permissible, but extremely similar submissions will be judged as plagiarism!
- Please show all intermediate steps: a correct solution without an explanation will get zero credit.
- Please submit on time. No late submission will be accepted.
- Please prepare your submission in English only. No Chinese submission will be accepted.

1. [10%] In the phasor-domain circuit, $V = 30 \angle 60^\circ$ V (rms), $R_1 = 5 \Omega$, $R_2 = 20 \Omega$, $R_3 = 10 \Omega$, $Z_C = -j4 \Omega$, and $Z_L = j6 \Omega$. Choose the load impedance Z_{load} so that the average power dissipated in it is a maximum value. Find the values of load impedance Z_{load} and the maximum average power on Z_{load} .

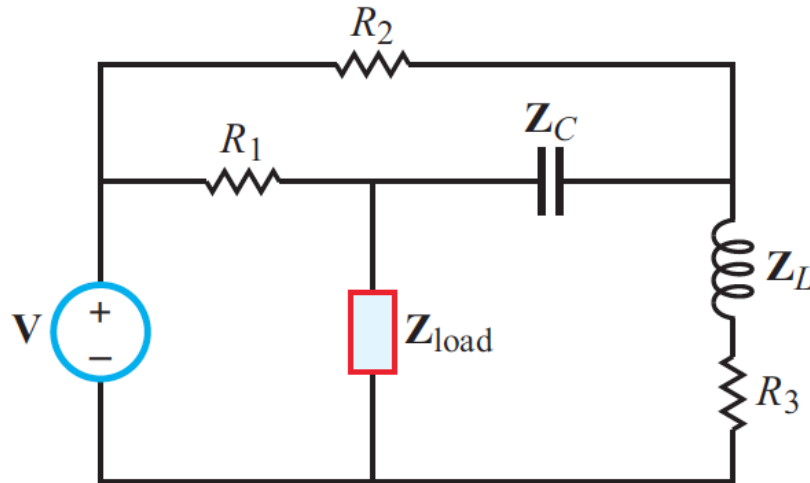**Fig. 1**

2. [12%] Given the circuit below, find
- The line current.
 - The total complex power absorbed by the load.
 - The total complex power dissipated on the line.

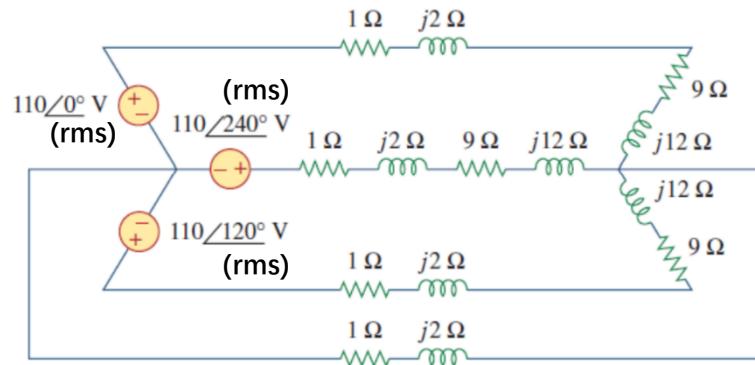


Fig. 2

3. [16%] The circuit is shown below, find
- The average power absorbed by the 20Ω resistor.
 - The current I_0 .

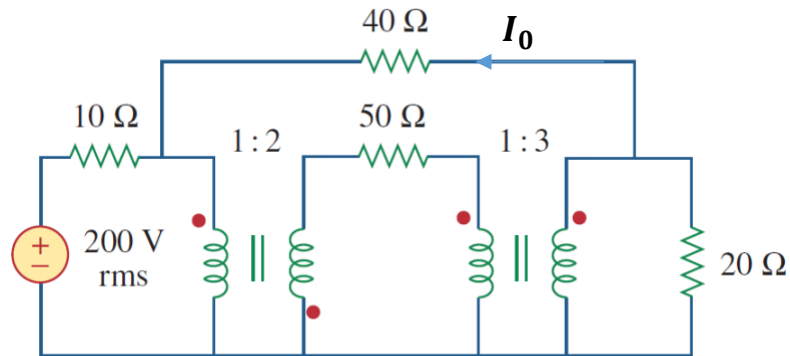


Fig. 3.

4. [10%] For the network circuit in Fig. 4, assume that 4Ω is the AC source resistor. Find out the input impedance Z_{ab} and the input current I_o .

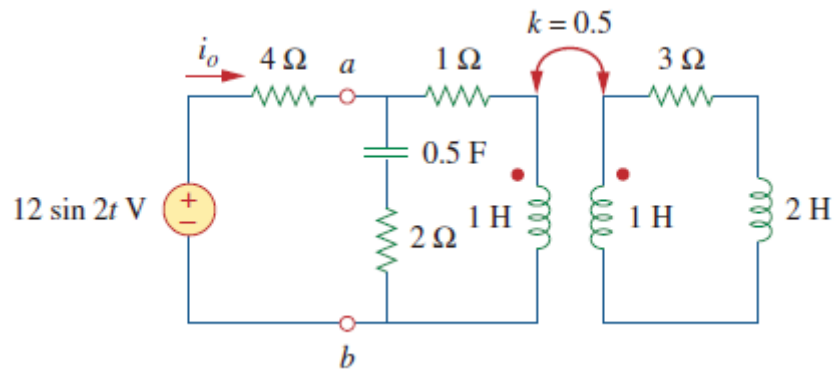


Fig. 4

5. [10%] For the circuit shown below, determine the transform function $\mathbf{H}(\omega) = \mathbf{V}_o/\mathbf{V}_i$, and determine the frequency ω at which $\mathbf{H}(\omega)$ is purely real.

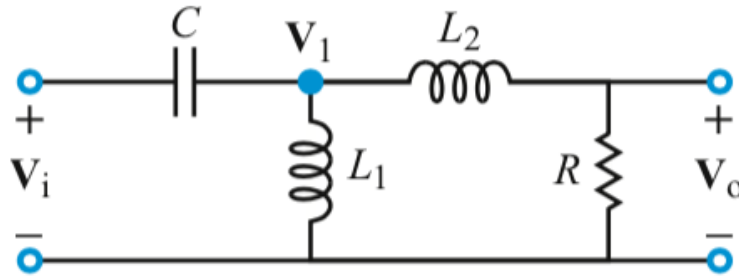


Fig. 5

6. [18%] Determine the voltage transfer function $\mathbf{H}(\omega)$ corresponding to the Bode magnitude plot shown in the Fig. 6

- The phase of $\mathbf{H}(\omega)$ is 90° at $\omega = 0$.
- The phase of $\mathbf{H}(\omega)$ is -90° at $\omega = 0$.
- The phase of $\mathbf{H}(\omega)$ is 0° at $\omega = 0$.

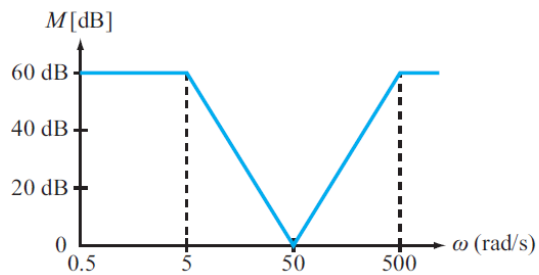


Fig. 6a

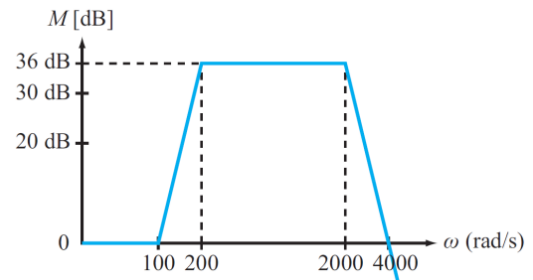


Fig. 6b

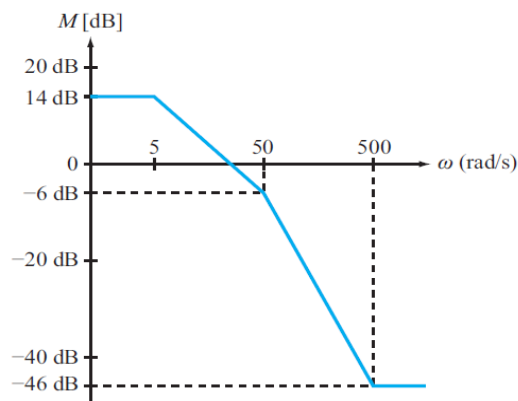


Fig. 6c

7. [12%] Determine the center frequency and bandwidth of the band-pass filters in Fig.7.

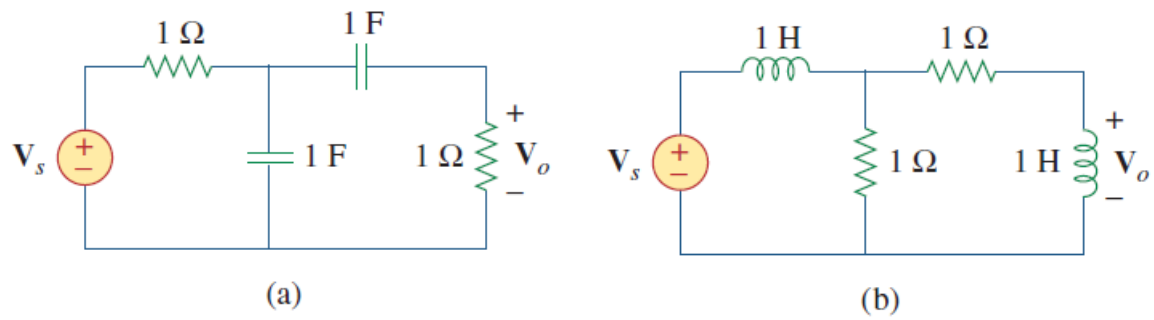


Fig. 7

8. For the op-amp circuit of Fig. 8:

- Obtain an expression for $\mathbf{H}(\omega) = \mathbf{V}_o/\mathbf{V}_s$ in standard form.
- Generate Bode Plots for the magnitude and phase of $\mathbf{H}(\omega)$, given that $R_1 = R_2 = 100\Omega$, and $C_1 = 10\mu F$, $C_2 = 0.4\mu F$.
- What type of filter is it? What is its maximum gain?

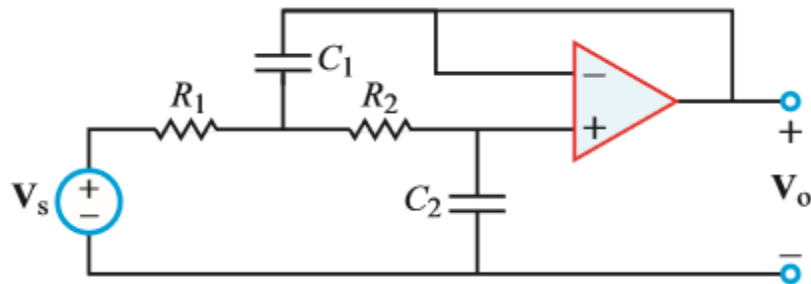


Fig. 8