

## ↓Homework 1

Due date: Mar. 11th, 2020, Wednesday  
Turn in your homework before class

Rules:

- Work on your own. Discussion is permissible, but extremely similar submissions will judged as plagiarism.
- Please show all intermediate steps: a correct solution without an explanation will get zero credit.
- Please submit on time.
- Please prepare your submission in English only. No Chinese submission will be accepted.

1. The voltage  $v$  across a device and the current  $i$  through it are

$$v(t) = 10 \cos 2.5t \text{ V}, \quad i(t) = 20(1 - e^{-0.25t}) \text{ mA}$$

Calculate:

- (a) the total charge through the device from  $t=0$  s to  $t=1$  s.  
 (b) the power consumed by the device at  $t = 1$  s. (10 points)

a)

$$v(t) = 10 \cos 2.5t \text{ V}$$

$$i(t) = 20(1 - e^{-0.25t}) \text{ mA} = 0.02(1 - e^{-0.25t}) \text{ A}$$

$$dq = i dt$$

$$q = \int i dt$$

2 points

$$q = \int_0^1 0.02(1 - e^{-0.25t}) = 2.30 \text{ mC}$$

2 points

b)

$$p = (10 \cos 2.5t)(0.02(1 - e^{-0.25t}))$$

2 points

At  $t=1$  s

$$p = (10 \cos 2.5)(0.02(1 - e^{-0.25}))$$

1 point

$$p = -35.44 \text{ mW}$$

3 points

2. Find  $I$  and the power absorbed by each element in the network of Fig. 1. (10 points)

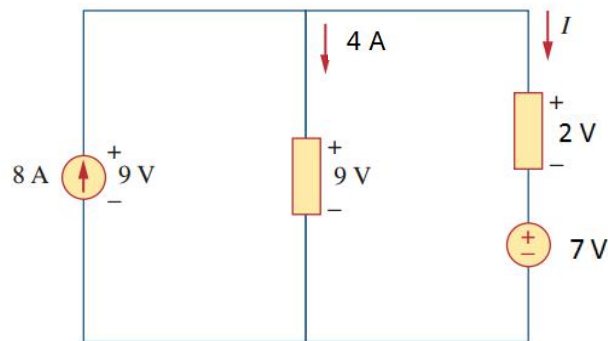


Figure 1.

$$8 = 4 + I \Rightarrow I = 4 A$$

2 points

$$P_{Source 8A} = -8 \times 9 = -72 W$$

2 points

$$P_{R1} = 4 \times 9 = 36 W$$

2 points

$$P_{R2} = 2 \times 4 = 8 W$$

2 points

$$P_{Source 7V} = 7 \times 4 = 28 W$$

2 ponits

*Check : power absorbed power produced = 0*

$$(36 + 8 + 28) - (-72) = 0$$

3. Find  $V_o$  in the circuit in Fig. 2 and the power absorbed by the dependent source.  
(10 points)

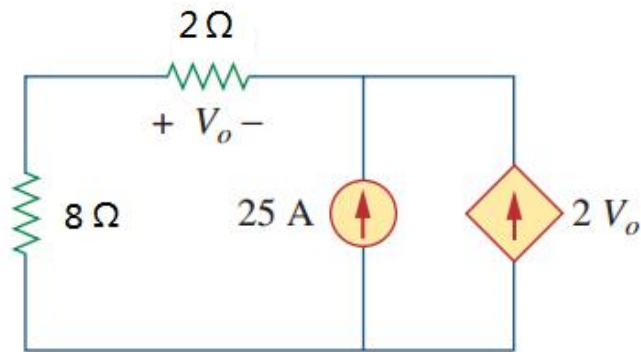


Figure 2.

$$2V_o + 25 + \frac{V_o}{2} = 0$$

2 points

$$\Rightarrow V_o = -10V$$

2 points

$$V_X = (2 + 8) \times \left(\frac{V_o}{2}\right)$$

2 points

$$\Rightarrow V_X = -50V$$

2 points

$$P = V_X \times (2V_o) = 1000W$$

2 points

4. Find the currents  $I_1$  through  $I_4$  and the voltage  $v_o$  in the circuit of Fig. 3. (10 points)

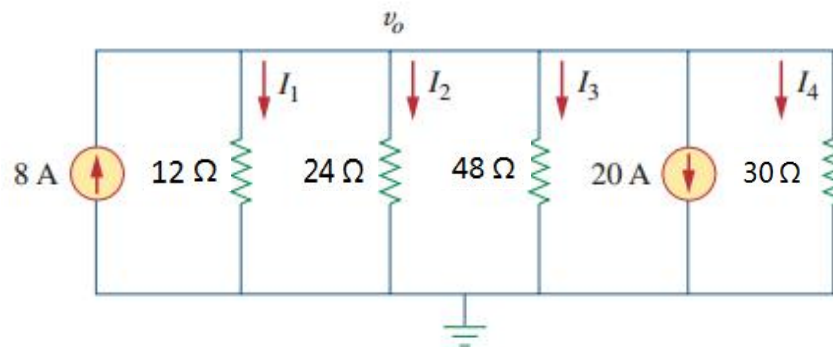


Figure 3.

$$8 = I_1 + I_2 + I_3 + 20 + I_4 \Rightarrow 8 = \frac{V_o}{12} + \frac{V_o}{24} + \frac{V_o}{48} + \frac{V_o}{30} + 20$$

$$\Rightarrow V_o \approx -66.98V$$

$$I_1 \approx -5.58A$$

$$I_2 \approx -2.79A$$

$$I_3 \approx -1.40A$$

$$I_4 \approx -2.23A$$

2 points

2 points

2 points

2 points

2 points

5. Find  $v_o$  and  $i_o$  in the circuit of Fig. 4.(20 points)

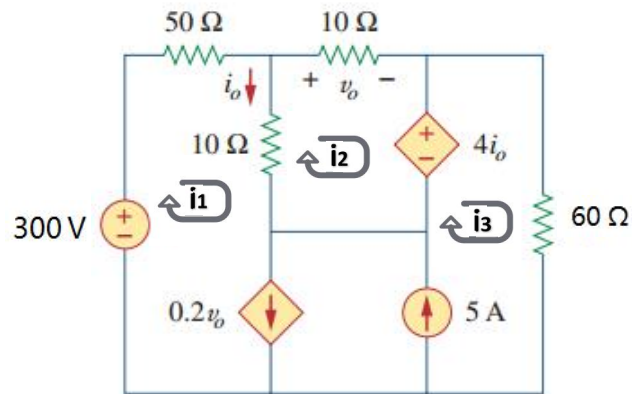


Figure 4.

$$i_0 + i_2 = i_1 \Rightarrow i_0 = i_1 - i_2$$

2 points

$$V_0 = 10i_2$$

2 points

Apply KVL to the super mesh between loop 1 and loop 3

$$-300 + 50i_1 + 10(i_1 - i_2) - 4i_0 + 60i_3 = 0$$

4 points

Apply KVL to mesh 2

$$10(i_2 - i_1) + 10i_2 + 40i_0 = 0$$

4 points

Apply KCL to node A

$$i_1 + 5 = 0.2V_0 + i_3$$

4 points

$$\Rightarrow i_1 = 0A$$

$$i_2 = 0A$$

$$i_3 = 5A$$

$$i_0 = 0A$$

$$V_0 = 10i_2 = 0V$$

4 points

6. Find  $v_1$  and  $v_2$  in the circuit in Fig. 5 using voltage and/or current division.  
(10 points)

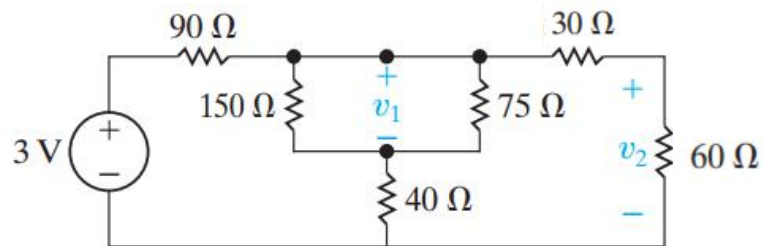


Figure 5.

$$R_{EQ} = ((150 \parallel 75) + 40) \parallel (30 + 60) = 45\Omega$$

4 points

$$V_{EQ} = 3 \times \frac{45}{45 + 90} = 1V$$

2 points

$$V_1 = 1 \times \frac{50}{50 + 40} = 0.56V$$

2 points

$$V_2 = 1 \times \frac{60}{60 + 30} = 0.67V$$

2 points

7. a) Use the node-voltage method to find  $v_o$  in the circuit in Fig.6.  
 b) Find the power absorbed by the dependent source.  
 c) Find the total power delivered by the independent sources.(10 points)

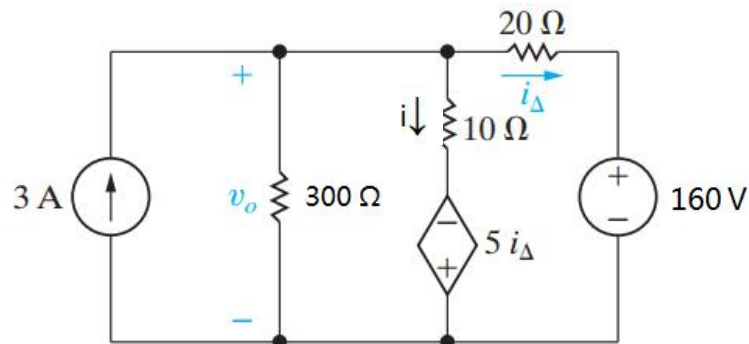


Figure 6.

a)

$$\frac{V_o}{300} + \frac{V_o - (-5i_\Delta)}{10} + \frac{V_o - 160}{20} - 3 = 0$$

$$i_\Delta = \frac{V_o - 160}{20}$$

$$\Rightarrow i_\Delta = -\frac{406}{107} A \approx -3.79 A$$

1 point

$$V_o = \frac{9000}{107} V \approx 84.11 V$$

1 point

b)

$$i = \frac{V_o - (-5i_\Delta)}{10} = \frac{697}{107} A \approx 6.514 A$$

2 points

$$P_{5i_\Delta} = -5i_\Delta \cdot i \approx 123.58 W$$

2 points

c)

$$P_{160V} = 160i_\Delta \approx -607.1 W$$

$$P_{3A} = -3V_o \approx -252.33 W$$

2 points

$$\sum P_{developed} = P_{160V} + P_{3A} \approx -859.43 W$$

1 point

So the power delivered by the independent sources is 859.43 W

1 point



8. a) Use the mesh-current method to find  $v_o$  in the circuit in Fig.7.  
 b) Find the power delivered by the dependent source.(20 points)

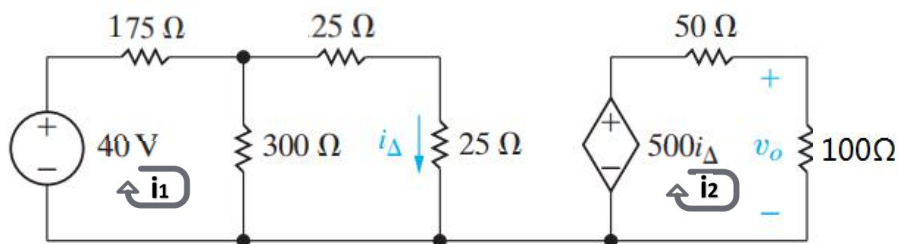


Figure 7.

a)

$$-40 + 175i_1 + 300(i_1 - i_\Delta) = 0 \quad 2.5 \text{ points}$$

$$25i_\Delta + 300(i_\Delta - i_1) + 25i_\Delta = 0 \quad 2.5 \text{ points}$$

$$-500i_\Delta + 50i_2 + 100i_2 = 0 \quad 2.5 \text{ points}$$

$$\Rightarrow i_1 \approx 0.1836A \quad 2.5 \text{ points}$$

$$i_\Delta \approx 0.1574A \quad 2.5 \text{ points}$$

$$i_2 \approx 0.5247A \quad 2.5 \text{ points}$$

$$V_o = 100i_2 \approx 52.47V \quad 2.5 \text{ points}$$

b)

$$P = (-i_2) \times 500i_\Delta \approx -41.28W \quad 1.5 \text{ points}$$

So the power delivered by the dependent source is 41.28 W. 1 point