

## Homework 3

Due date:

Mar.19th, 2018

Turn in your homework in class

Rules:

- Work on your own. Discussion is permissible, but extremely similar submissions will be judged as plagiarism.
- Please show all intermediate steps: a correct solution without an explanation will get zero credit.
- Please submit on time. No late submission will be accepted.
- Please prepare your submission in English only. No Chinese submission will be accepted.

1. Find the equivalent resistance in the circuit  $R_{ab}$  in Fig. 1 by using Y- $\Delta$  transformation.

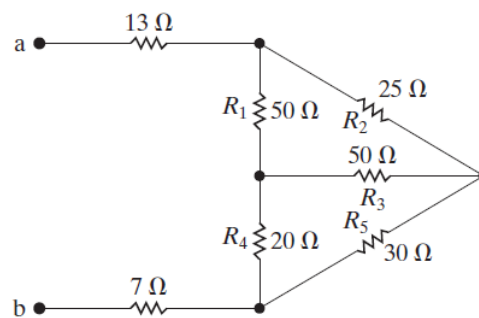


Figure 1

2. For the circuit in Fig. 2, determine the value of  $R$  such that the maximum power delivered to the load is 3 mW.



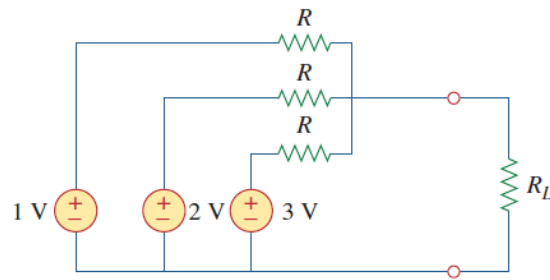


Figure 2


3. Calculate  $v_o$  in this circuit.

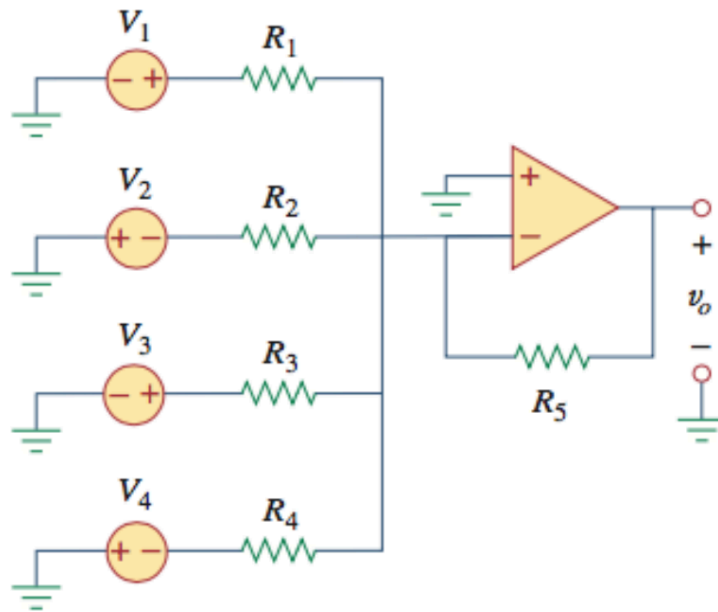

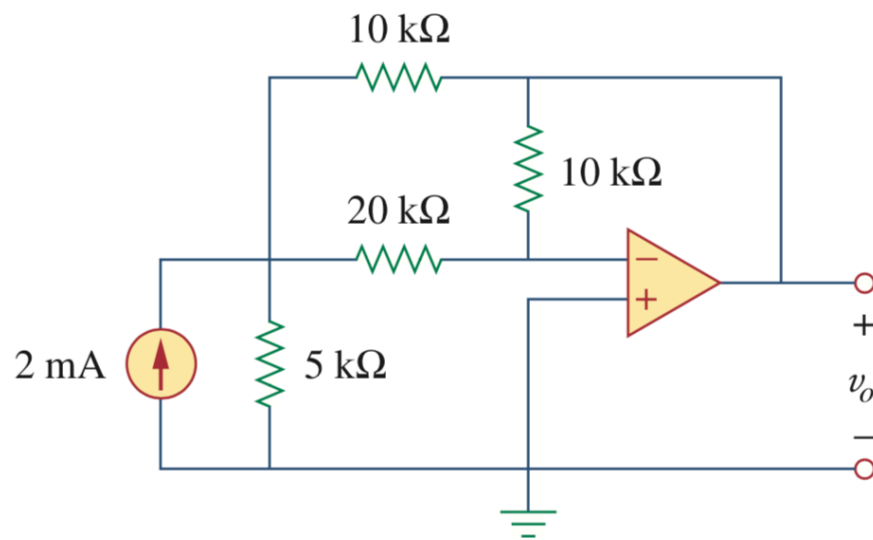4. Determine the output voltage  $v_o$  in the circuit below.




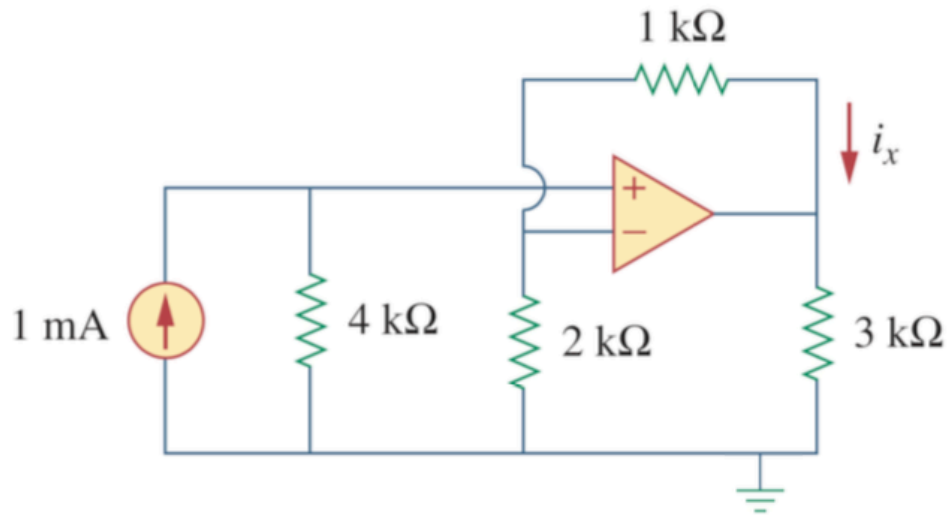5. Refer to the op amp circuit in Fig below. Calculate  $i_x$  and the power absorbed by the 3-k $\Omega$  resistor.




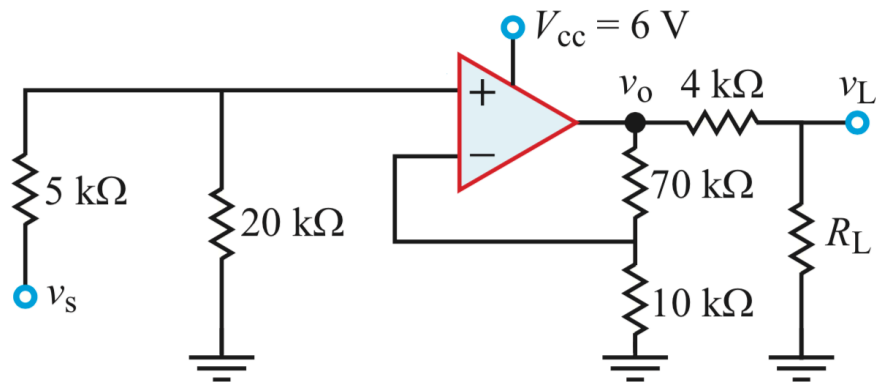6. For the circuit of the Fig below, what should the resistance of  $R_L$  be so as to have the maximum transfer of power into it?

We can assume that the operational amplifier operates in its linear region.



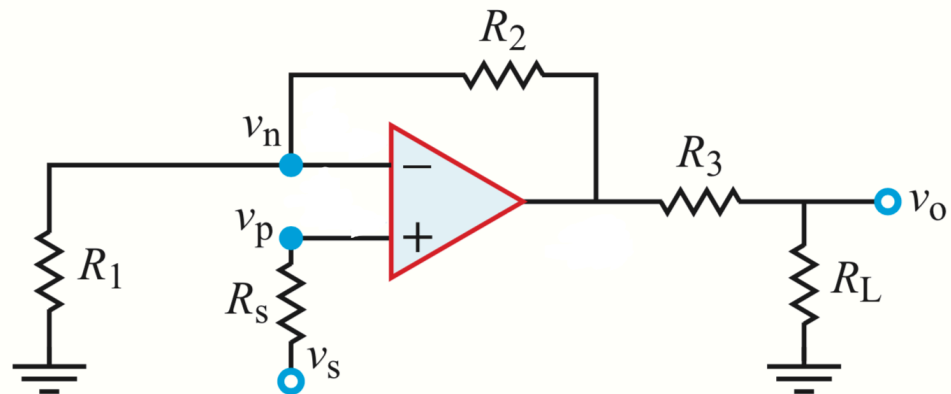7. Obtain an expression for the voltage gain  $G=v_o/v_s$  for the circuit in Fig below.



8. In the circuit of Fig below, a bridge circuit is connected at the input side of an inverting op-amp circuit.
- (a) Obtain the Thevenin equivalent at terminals (a , b) for the bridge circuit.
- (b) Use the result in (a) to obtain an expression for  $G = v_o/v_s$ .
- (c) Evaluate  $G$  for  $R_1 = R_4 = 100\Omega$ ,  $R_2 = R_3 = 101\Omega$ , and  $R_f = 100k\Omega$ .

