



Lecture 10

- Three-Phase Circuits




Outline--Three-Phase Circuits

- Balanced Three-Phase System
 - Balanced sources
 - Balanced loads
- Circuit analysis
 - Phase voltage/current
 - Line voltage/current




Three-Phase System (in USA)

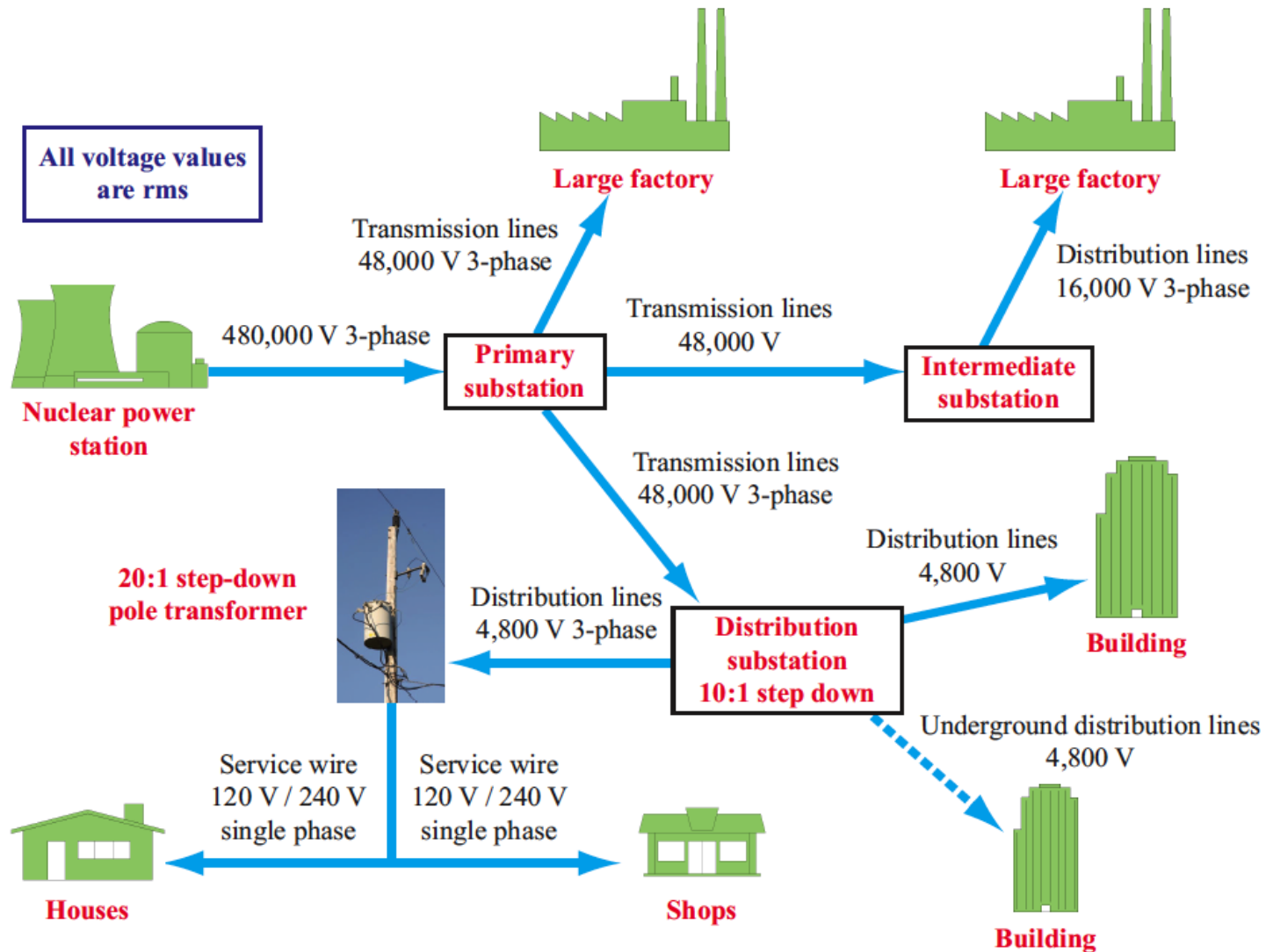





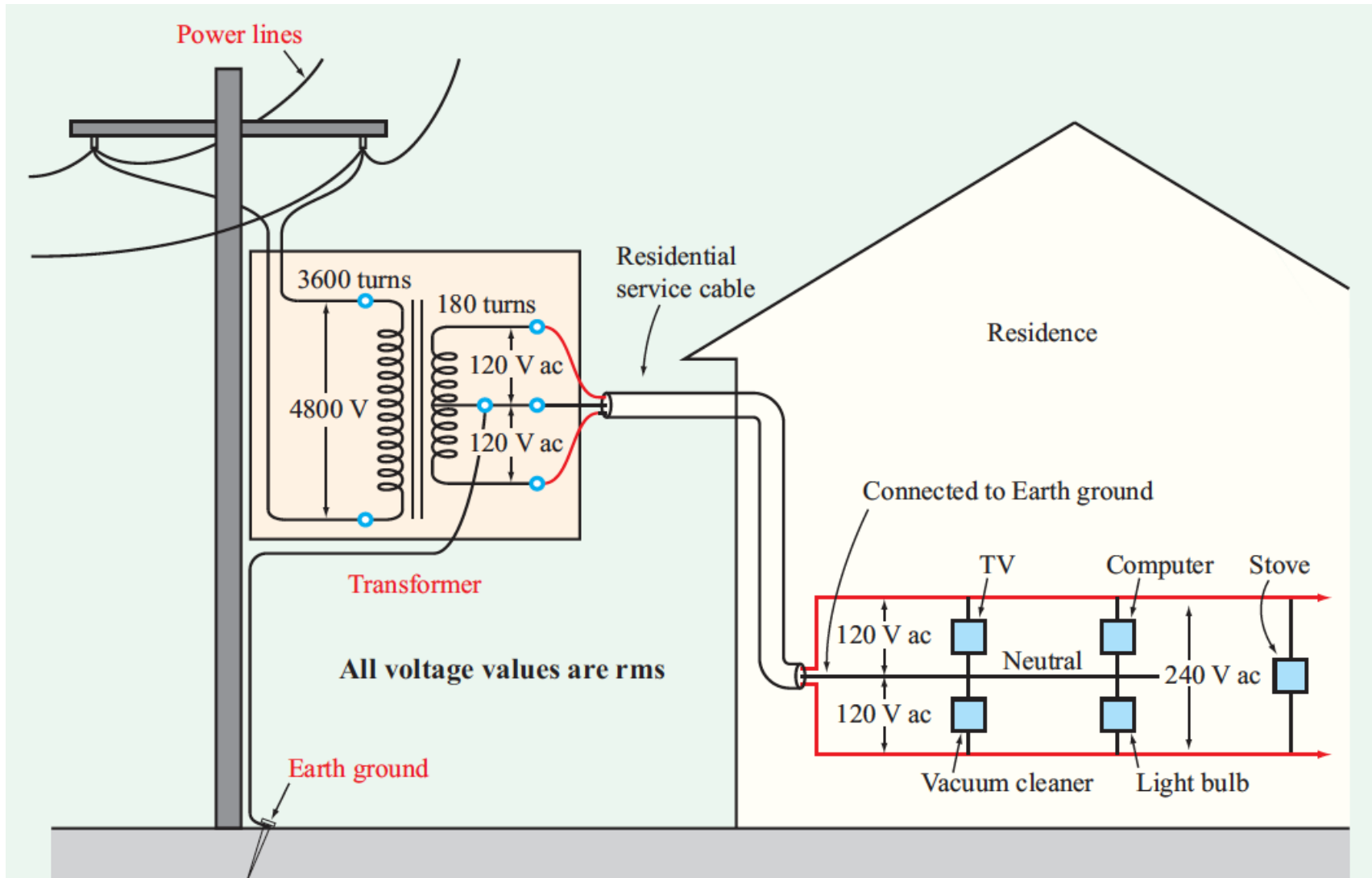A 4800-V rms single-phase connected to residential user through a 20 : 1 step-down transformer




Single Phase vs. Polyphase

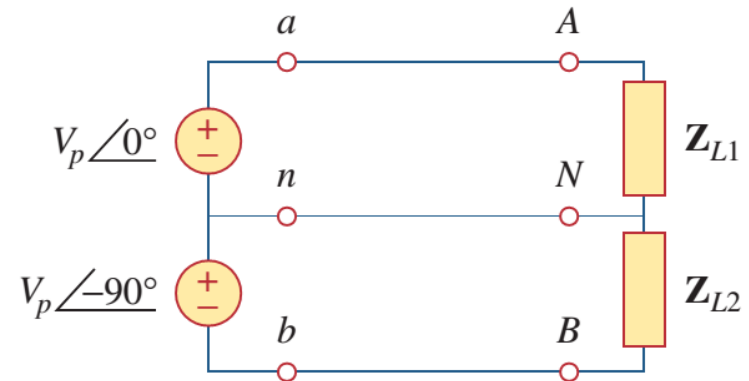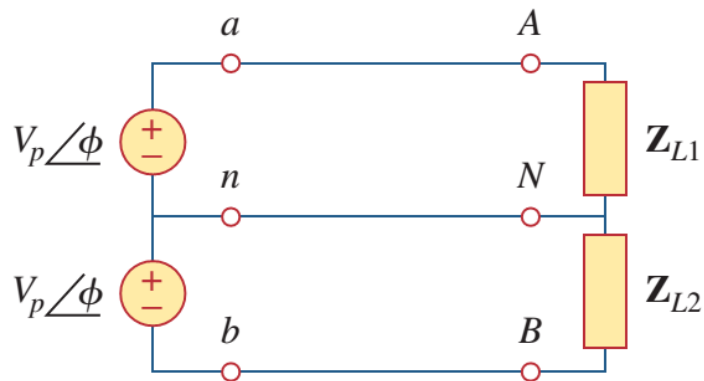- Households have single-phase power supply
 - This typically in a three wire form, where two 120V sources with the same phase are connected in series.
 - This allows for appliances to use either 120 or 240V
- Circuits that operate at the same frequency but with multiple sources at different phases are called polyphase.








Three-phase four-wire system in China

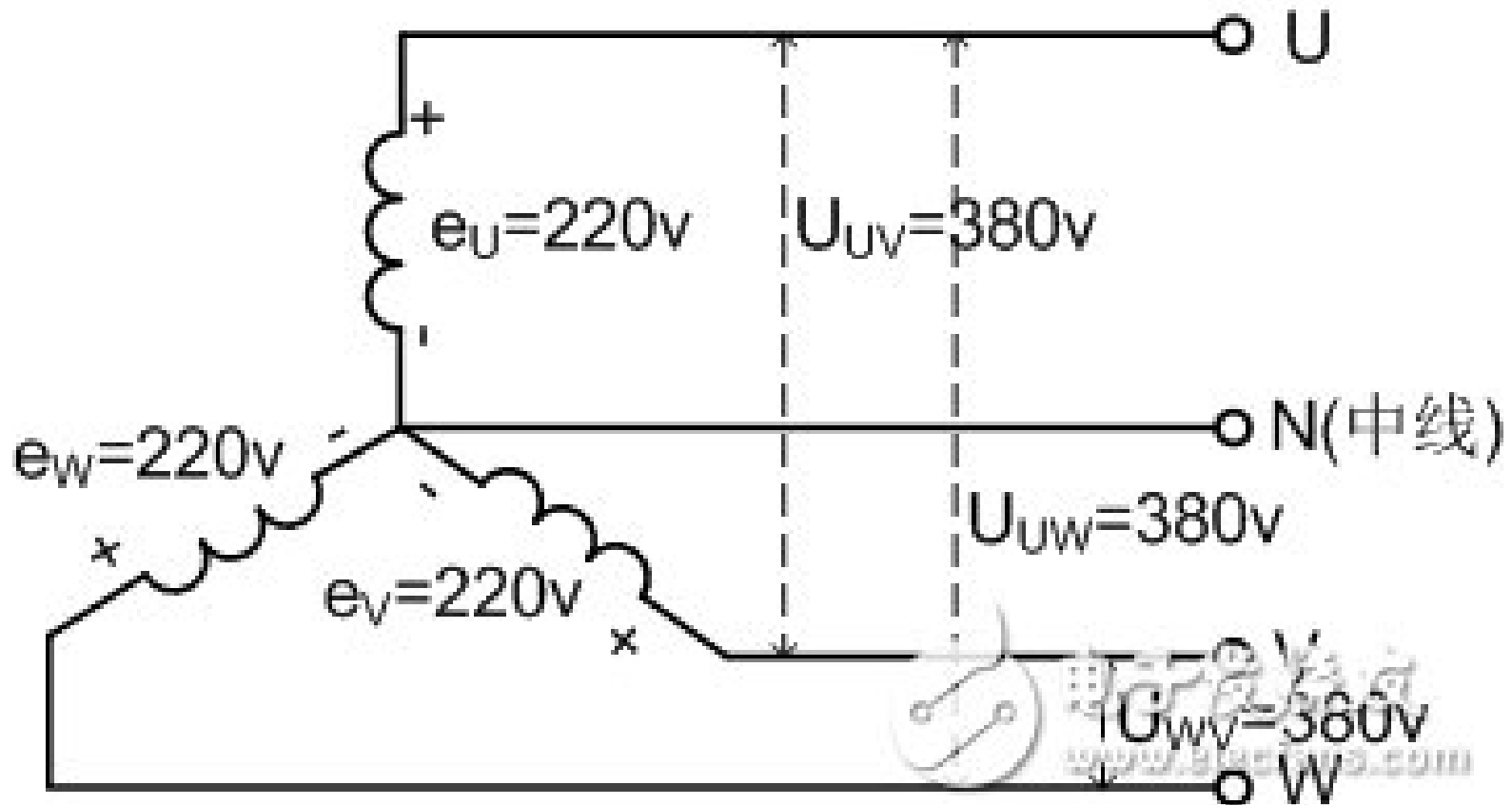


Three-Phase Sources

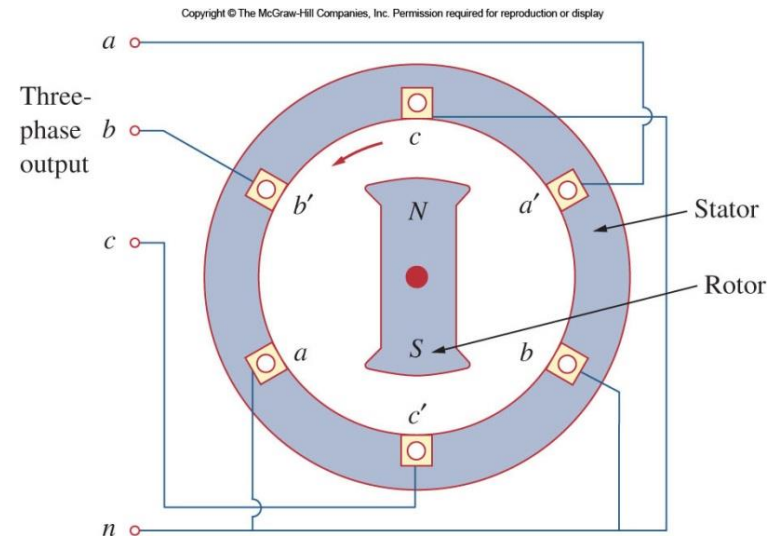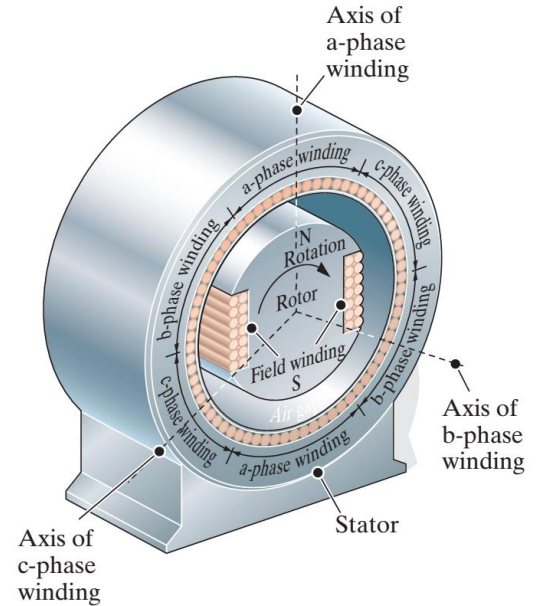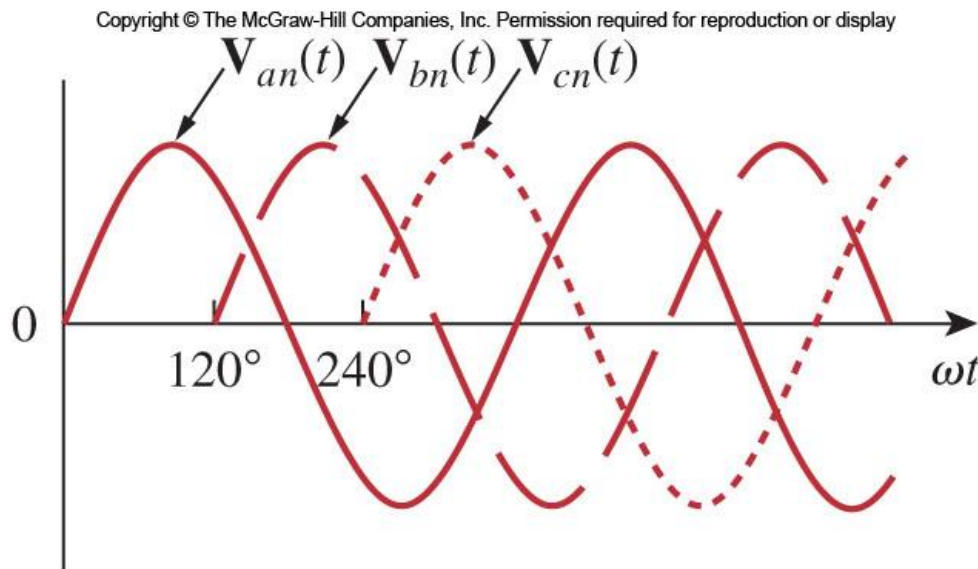- Three phase voltages are typically produced by a three-phase AC generator.
- The output voltages look like below.



Balanced Three-Phase Sources

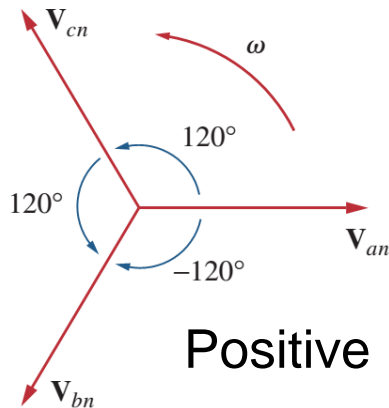
- Balanced phase voltage are equal in magnitude and are out of phase with each other by 120deg
- It's easy to know $V_{an} + V_{bn} + V_{cn} = 0$
- Two sequences for the phases:



$$V_{an} = V_p \angle 0^\circ$$

$$V_{bn} = V_p \angle -120^\circ$$
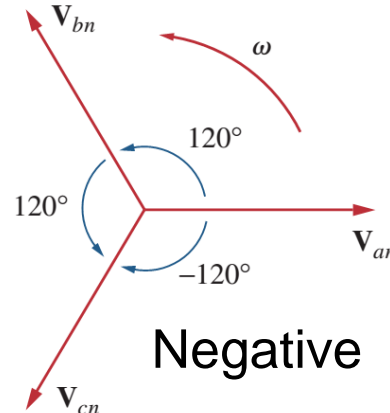
$$V_{cn} = V_p \angle -240^\circ = V_p \angle +120^\circ$$




$$V_{an} = V_p \angle 0^\circ$$

$$V_{cn} = V_p \angle -120^\circ$$

$$V_{bn} = V_p \angle -240^\circ = V_p \angle +120^\circ$$


Lecture 10

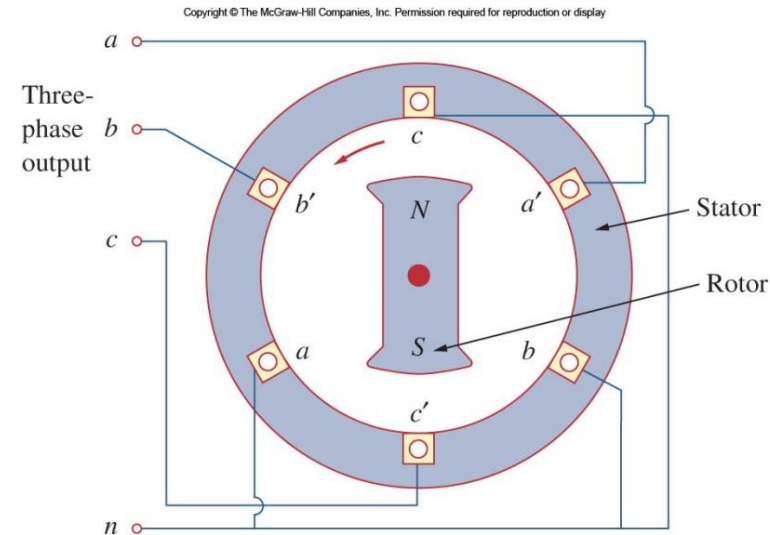


$$|V_{an}| = |V_{bn}| = |V_{cn}|$$

Connecting the Sources

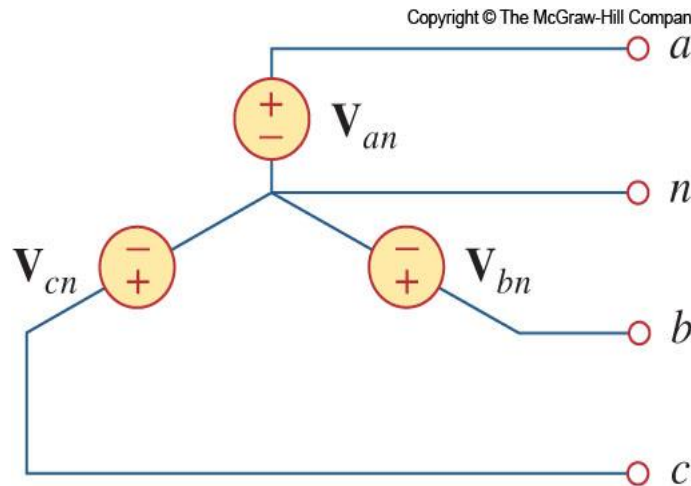- Three phase voltage sources can be connected by either three or four wire configurations.
 - Four-wire system accomplished using a Y(Wye) connected source.
 - Three-wire configuration accomplished by Delta connected source.



(a)

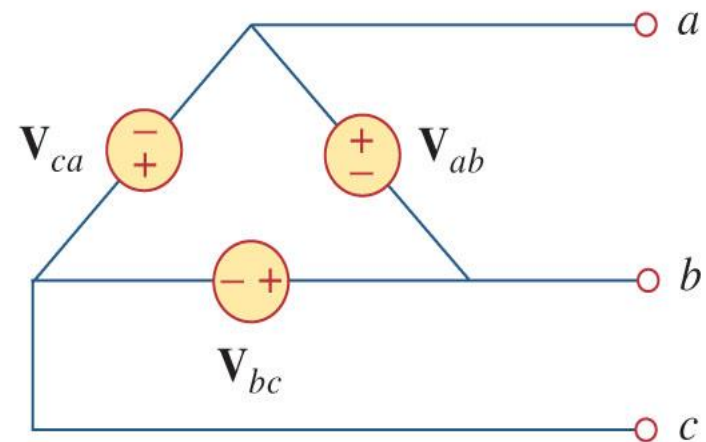

(b)



Balanced Loads

- A balanced load is one that has the same impedance presented to all three voltage sources.

-- *Impedance are equal in magnitude and in phase*

- They may also be connected in either Delta or wye

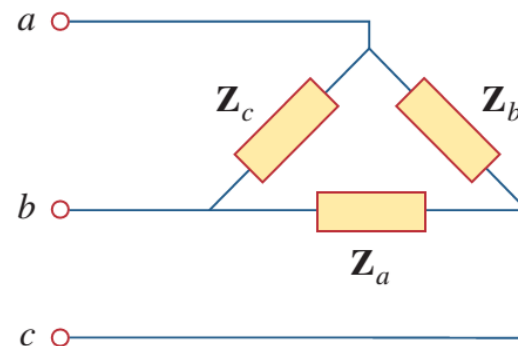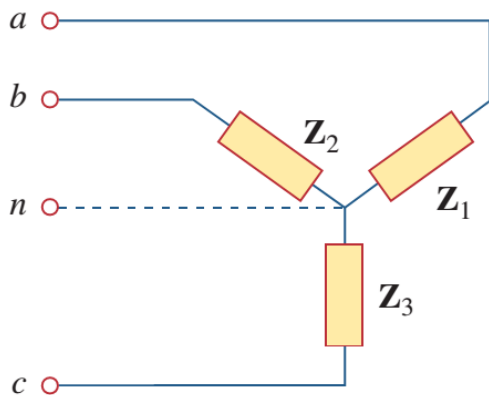
- For a balanced wye connected load: $Z_1 = Z_2 = Z_3 = Z_Y$
- For a balanced delta connected load: $Z_a = Z_b = Z_c = Z_\Delta$



- The load impedance per phase for the two load configurations can be interchanged.



Source-Load configurations

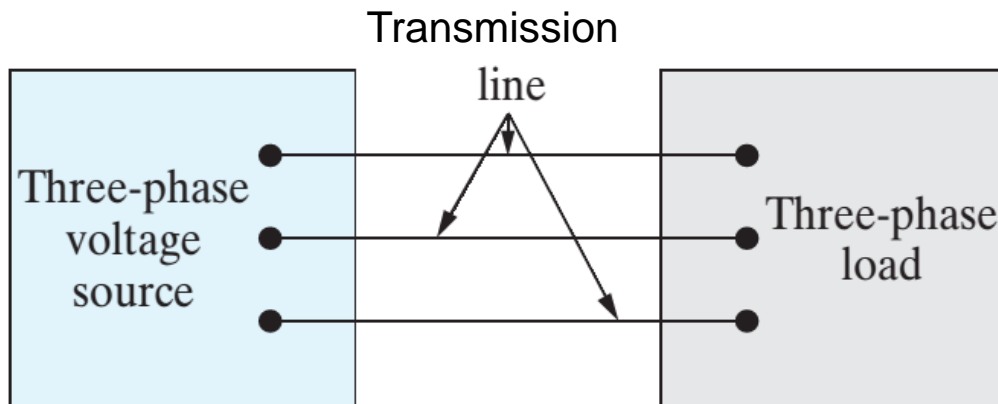


Source	Load
Y	Y
Y	Δ
Δ	Y
Δ	Δ



Source-Load Configurations

Y-Y

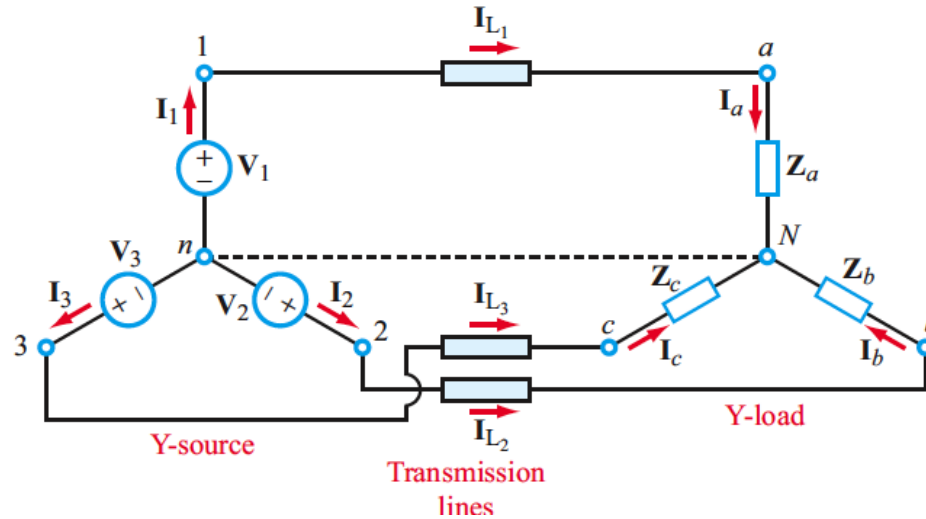


Load Phase Currents

I_a, I_b, I_c
(same as line currents
 $I_{L1}, I_{L2}, \text{ and } I_{L3}$)

Load Phase Voltages

V_{aN}, V_{bN}, V_{cN}

Y-Delta

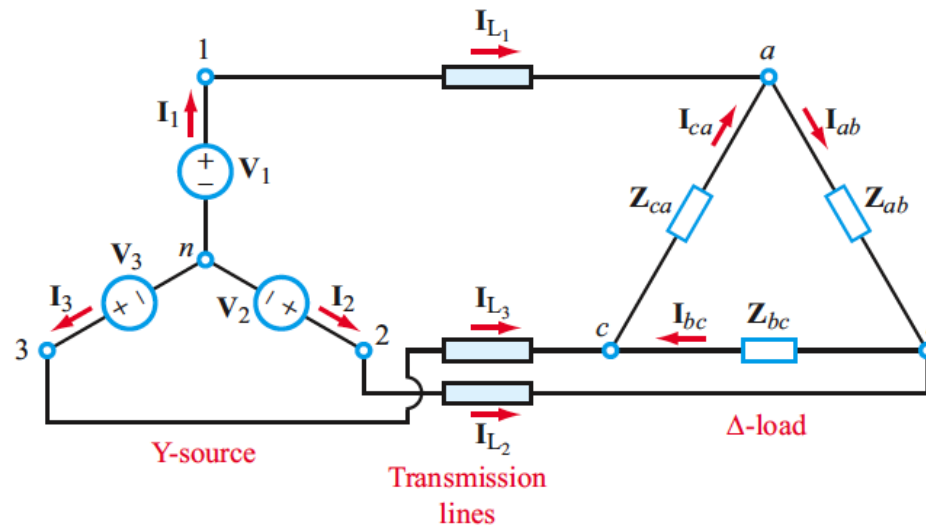

Load Phase Currents

I_{ab}, I_{bc}, I_{ca}


Load Phase Voltages

V_{ab}, V_{bc}, V_{ca}



Source-Load Configurations

Delta-Y

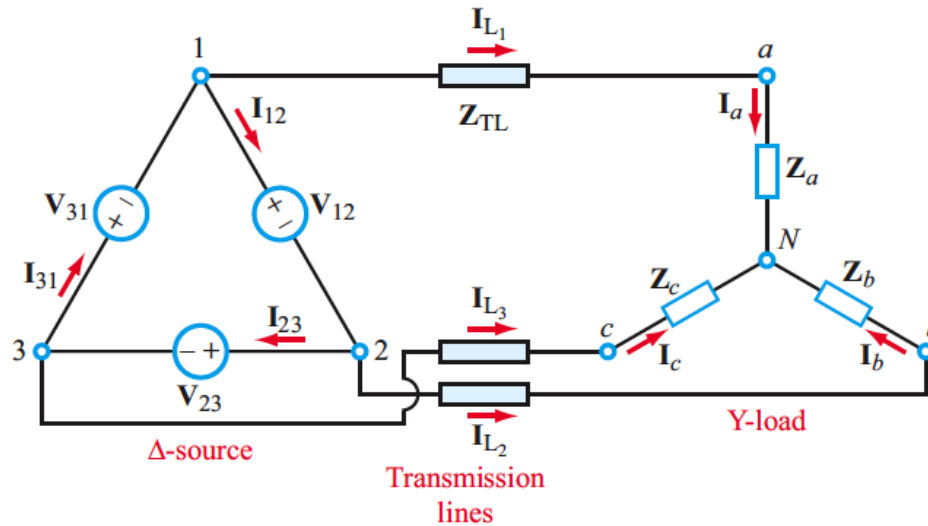


Load Phase Currents

I_a, I_b, I_c
(same as line currents
 $I_{L1}, I_{L2}, \text{ and } I_{L3}$)

Load Phase Voltages

V_{aN}, V_{bN}, V_{cN}

Delta-Delta

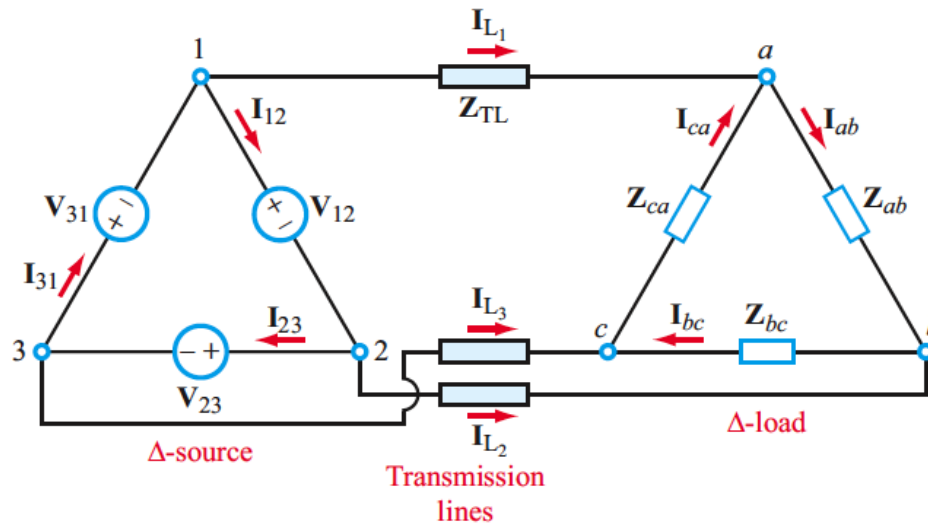

Load Phase Currents

I_{ab}, I_{bc}, I_{ca}



Load Phase Voltages

V_{ab}, V_{bc}, V_{ca}
(same as source voltages
if Z_{TL} is negligible)

Balanced Y-Y connection

- Any three-phase system **can be reduced to an equivalent Y-Y system.**
- The load impedances Z_Y will be assumed to be balanced.
 - This can be the source Z_s , line Z_l and load Z_L together.

$$Z_Y = Z_s + Z_\ell + Z_L$$

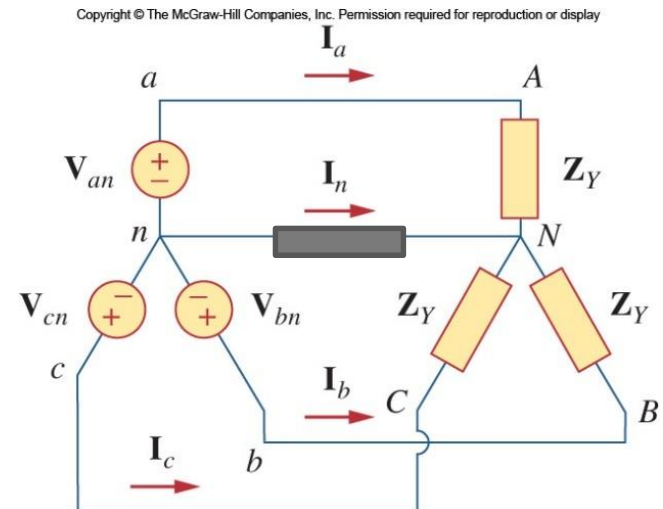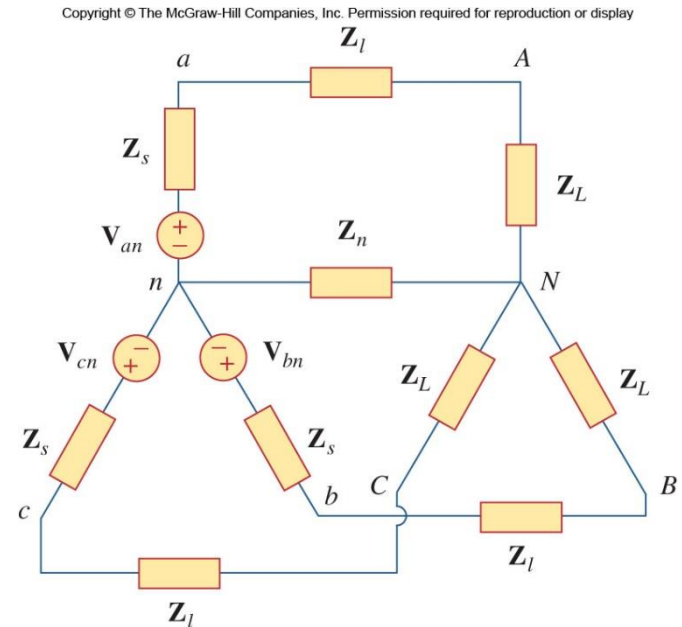



Phase Voltage & Line-to-Line Voltage



- Use the positive sequence:

Phase Voltage

$$V_{an} = V_p \angle 0^\circ$$


$$V_{bn} = V_p \angle -120^\circ \quad V_{cn} = V_p \angle +120^\circ$$

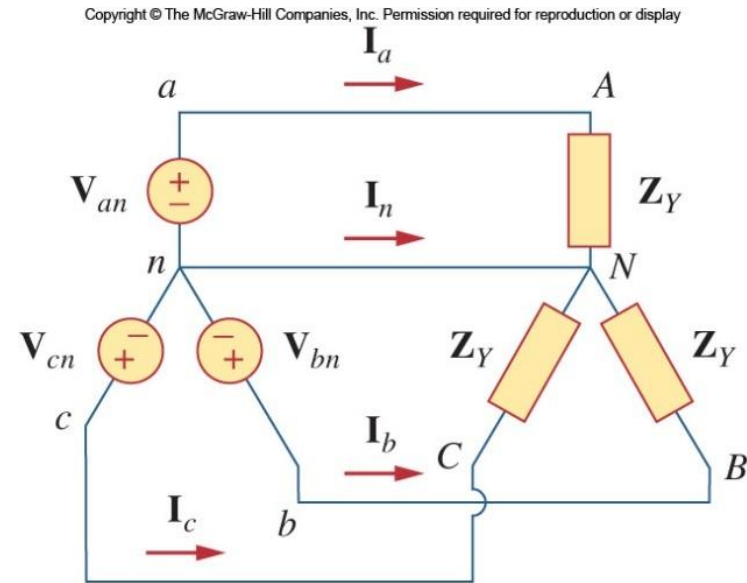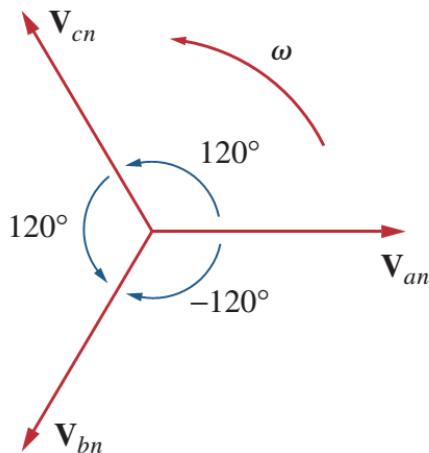- The line to line (or line in short) voltages:






Line Currents

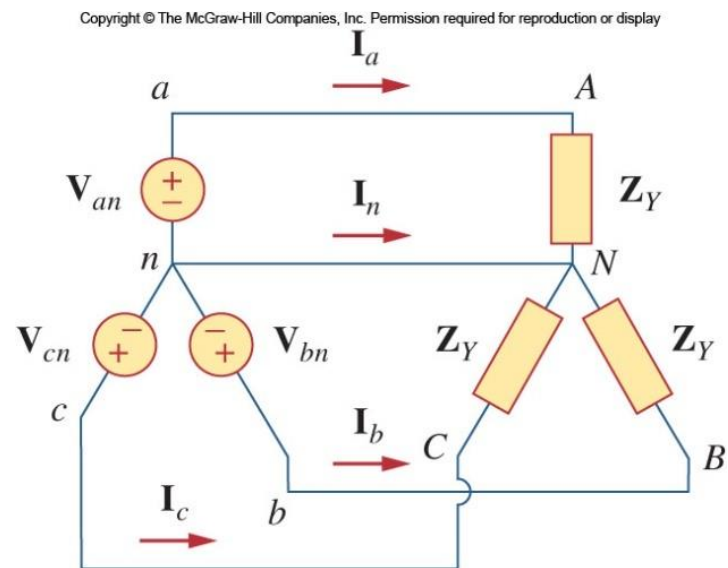




Example

- Calculate the line currents.

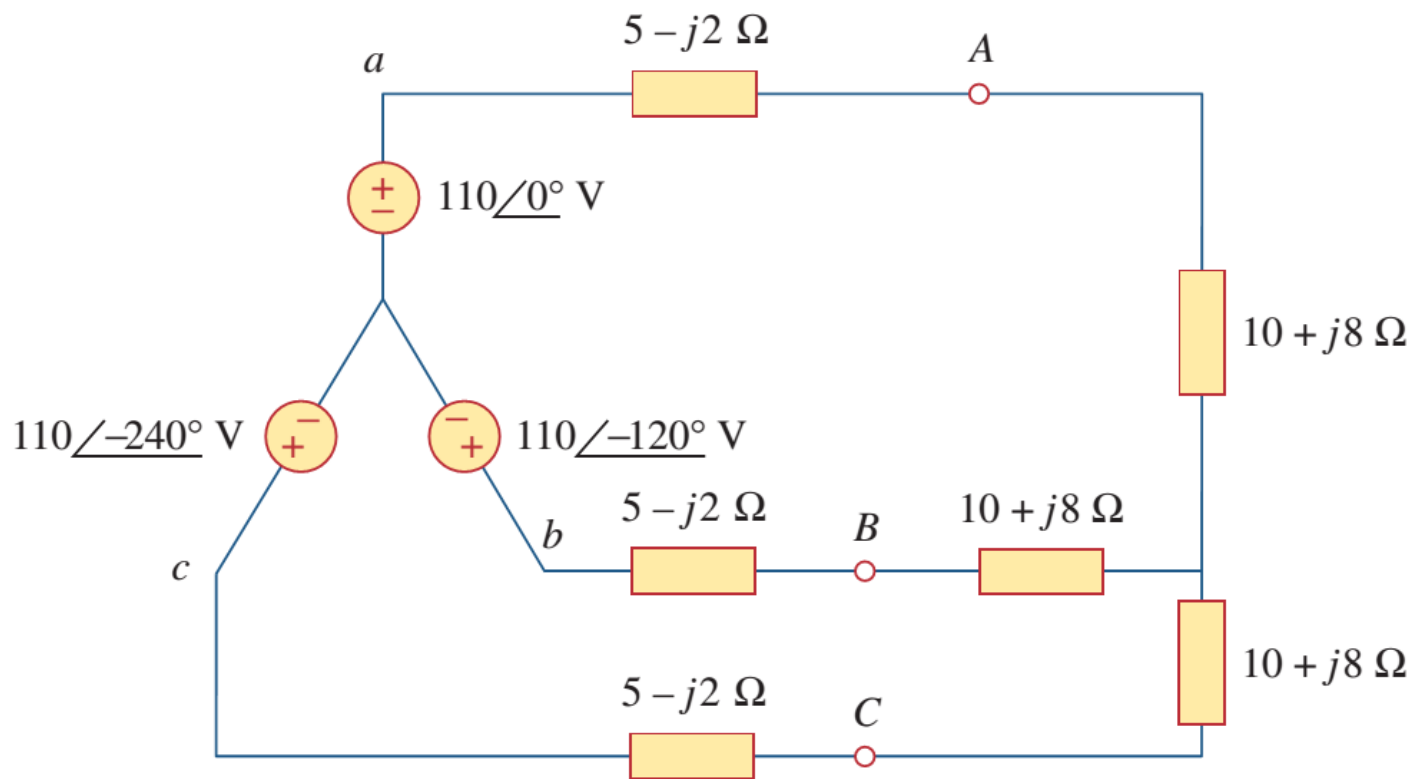



Wye- Δ

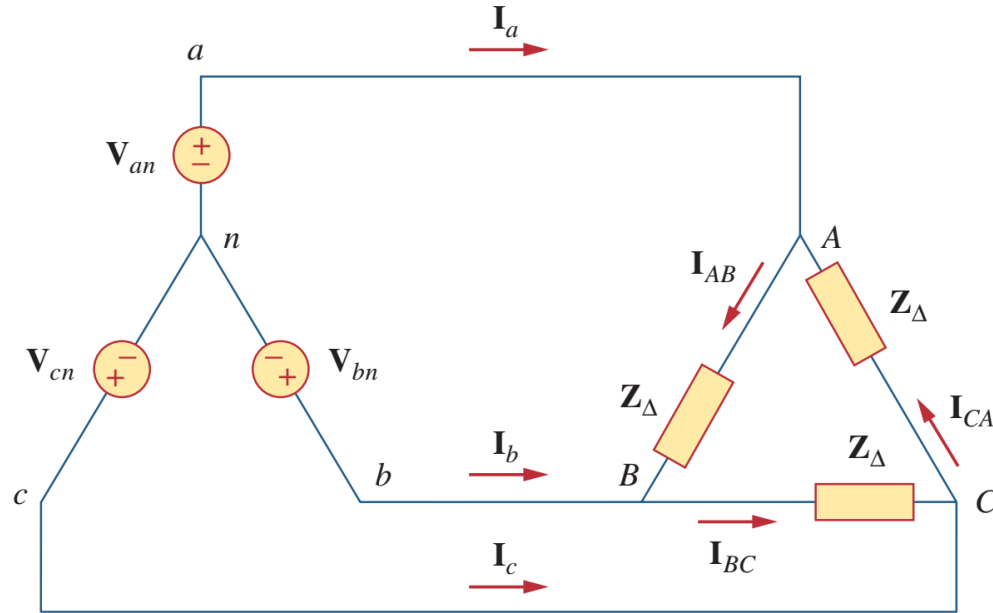


$$\begin{aligned} \mathbf{V}_{an} &= V_p \angle 0^\circ \\ \mathbf{V}_{bn} &= V_p \angle -120^\circ, \quad \mathbf{V}_{cn} = V_p \angle +120^\circ \end{aligned}$$

$$\begin{aligned} \mathbf{V}_{ab} &= \sqrt{3}V_p \angle 30^\circ = \mathbf{V}_{AB}, \quad \mathbf{V}_{bc} = \sqrt{3}V_p \angle -90^\circ = \mathbf{V}_{BC} \\ \mathbf{V}_{ca} &= \sqrt{3}V_p \angle -150^\circ = \mathbf{V}_{CA} \end{aligned}$$

$$\mathbf{I}_{AB} = \frac{\mathbf{V}_{AB}}{\mathbf{Z}_{\Delta}}, \quad \mathbf{I}_{BC} = \frac{\mathbf{V}_{BC}}{\mathbf{Z}_{\Delta}}, \quad \mathbf{I}_{CA} = \frac{\mathbf{V}_{CA}}{\mathbf{Z}_{\Delta}}$$




Wye- Δ

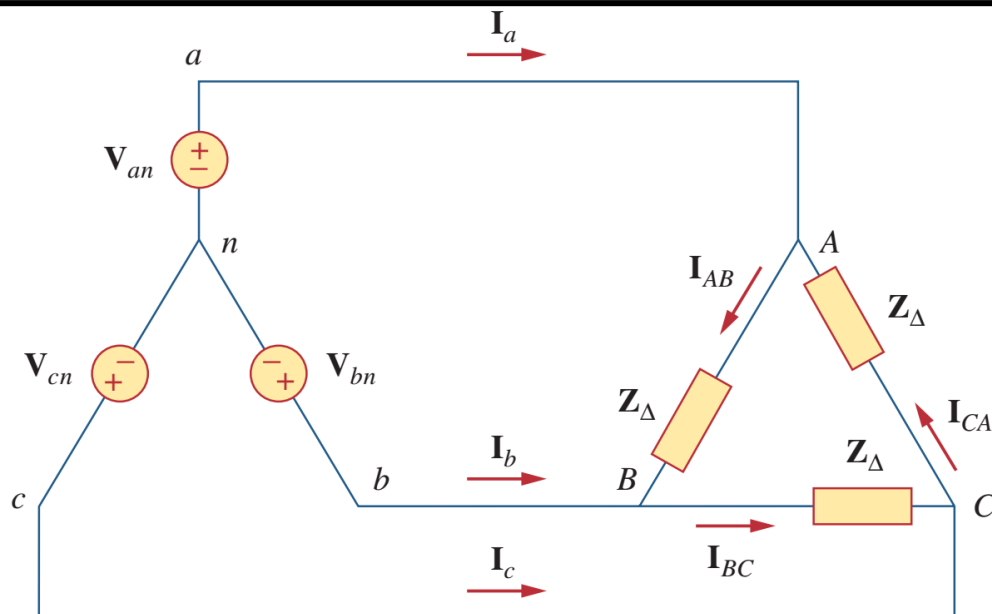

$$\mathbf{I}_a = \mathbf{I}_{AB} - \mathbf{I}_{CA}, \quad \mathbf{I}_b = \mathbf{I}_{BC} - \mathbf{I}_{AB}, \quad \mathbf{I}_c = \mathbf{I}_{CA} - \mathbf{I}_{BC}$$


Since $\mathbf{I}_{CA} = \mathbf{I}_{AB} \angle -240^\circ$,
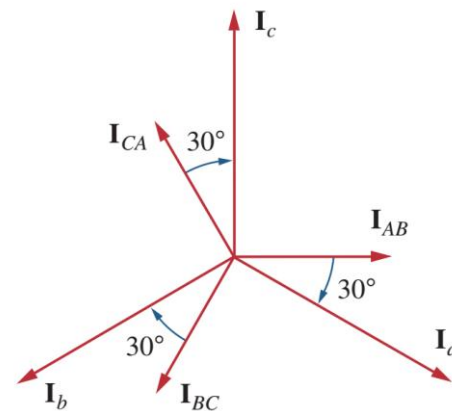
$$\begin{aligned} \mathbf{I}_a &= \mathbf{I}_{AB} - \mathbf{I}_{CA} = \mathbf{I}_{AB}(1 - 1 \angle -240^\circ) \\ &= \mathbf{I}_{AB}(1 + 0.5 - j0.866) = \mathbf{I}_{AB}\sqrt{3} \angle -30^\circ \end{aligned}$$






• Δ - Δ

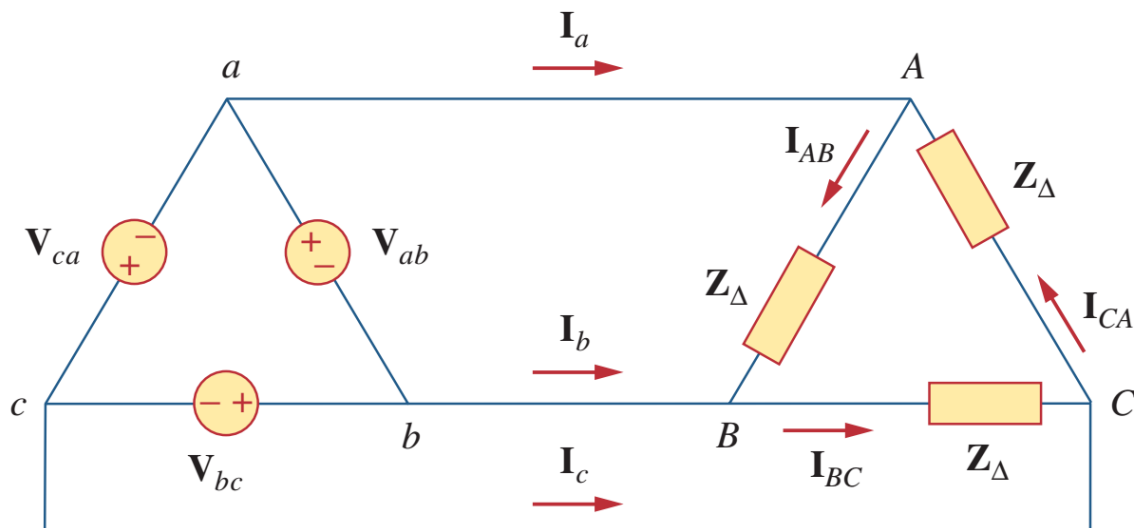

Δ -Wye

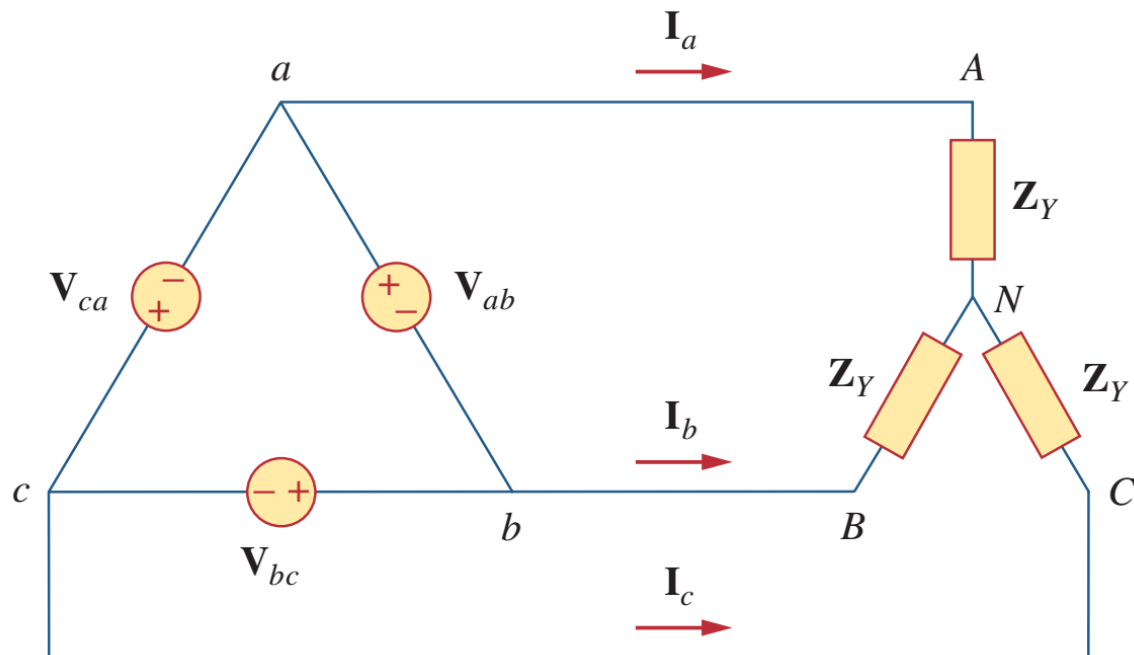



Y-Y	$\mathbf{V}_{an} = V_p \angle 0^\circ$ $\mathbf{V}_{bn} = V_p \angle -120^\circ$ $\mathbf{V}_{cn} = V_p \angle +120^\circ$ <p>Same as line currents</p>	$\mathbf{V}_{ab} = \sqrt{3}V_p \angle 30^\circ$ $\mathbf{V}_{bc} = \mathbf{V}_{ab} \angle -120^\circ$ $\mathbf{V}_{ca} = \mathbf{V}_{ab} \angle +120^\circ$ $\mathbf{I}_a = \mathbf{V}_{an} / \mathbf{Z}_Y$ $\mathbf{I}_b = \mathbf{I}_a \angle -120^\circ$ $\mathbf{I}_c = \mathbf{I}_a \angle +120^\circ$
Y-Δ	$\mathbf{V}_{an} = V_p \angle 0^\circ$ $\mathbf{V}_{bn} = V_p \angle -120^\circ$ $\mathbf{V}_{cn} = V_p \angle +120^\circ$ $\mathbf{I}_{AB} = \mathbf{V}_{AB} / \mathbf{Z}_\Delta$ $\mathbf{I}_{BC} = \mathbf{V}_{BC} / \mathbf{Z}_\Delta$ $\mathbf{I}_{CA} = \mathbf{V}_{CA} / \mathbf{Z}_\Delta$	$\mathbf{V}_{ab} = \mathbf{V}_{AB} = \sqrt{3}V_p \angle 30^\circ$ $\mathbf{V}_{bc} = \mathbf{V}_{BC} = \mathbf{V}_{ab} \angle -120^\circ$ $\mathbf{V}_{ca} = \mathbf{V}_{CA} = \mathbf{V}_{ab} \angle +120^\circ$ $\mathbf{I}_a = \mathbf{I}_{AB} \sqrt{3} \angle -30^\circ$ $\mathbf{I}_b = \mathbf{I}_a \angle -120^\circ$ $\mathbf{I}_c = \mathbf{I}_a \angle +120^\circ$
Δ-Δ	$\mathbf{V}_{ab} = V_p \angle 0^\circ$ $\mathbf{V}_{bc} = V_p \angle -120^\circ$ $\mathbf{V}_{ca} = V_p \angle +120^\circ$ $\mathbf{I}_{AB} = \mathbf{V}_{ab} / \mathbf{Z}_\Delta$ $\mathbf{I}_{BC} = \mathbf{V}_{bc} / \mathbf{Z}_\Delta$ $\mathbf{I}_{CA} = \mathbf{V}_{ca} / \mathbf{Z}_\Delta$	<p>Same as phase voltages</p> $\mathbf{I}_a = \mathbf{I}_{AB} \sqrt{3} \angle -30^\circ$ $\mathbf{I}_b = \mathbf{I}_a \angle -120^\circ$ $\mathbf{I}_c = \mathbf{I}_a \angle +120^\circ$
Δ-Y	$\mathbf{V}_{ab} = V_p \angle 0^\circ$ $\mathbf{V}_{bc} = V_p \angle -120^\circ$ $\mathbf{V}_{ca} = V_p \angle +120^\circ$ <p>Same as line currents</p>	<p>Same as phase voltages</p> $\mathbf{I}_a = \frac{V_p \angle -30^\circ}{\sqrt{3}\mathbf{Z}_Y}$ $\mathbf{I}_b = \mathbf{I}_a \angle -120^\circ$ $\mathbf{I}_c = \mathbf{I}_a \angle +120^\circ$



Unbalanced 3-phase circuits



Power calculations