

Problem 1 (8 points)


The energy delivering to the circuit element and the charge flowing through the element are given below:

$$E(t) = e^{t^2} \sin(2t^2) \text{ J}$$

$$q(t) = t^2 \text{ C}$$

(a) Determine the voltage at the terminals of the element.

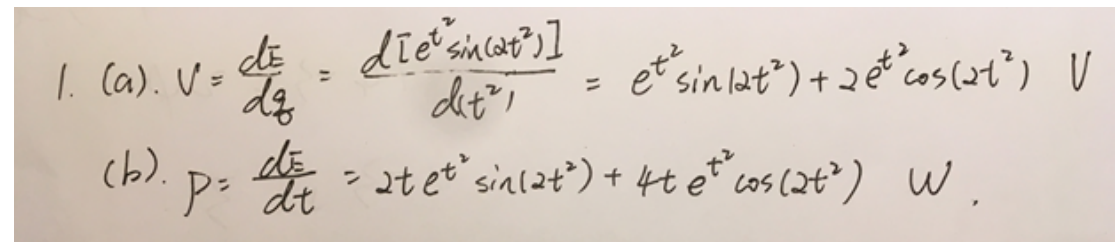(b) Determine the power supplied to the element.



Handwritten solution for Problem 1:

1. (a). $V = \frac{dE}{dq} = \frac{d[e^{t^2} \sin(2t^2)]}{d(t^2)} = e^{t^2} \sin(2t^2) + 2e^{t^2} \cos(2t^2) \text{ V}$

(b). $P = \frac{dE}{dt} = 2te^{t^2} \sin(2t^2) + 4te^{t^2} \cos(2t^2) \text{ W}$

Problem 2 (12 points)

Use the principle of superposition to find the current i_0 in the circuit shown in Fig. 2.



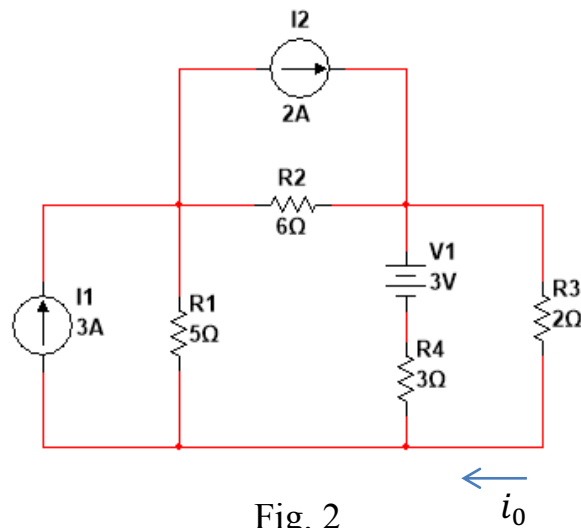


Fig. 2


2. Open I_1, I_2 :

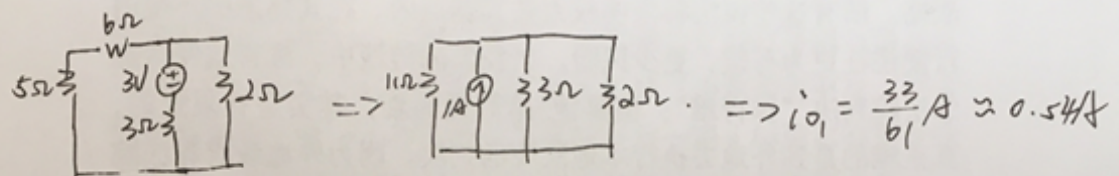

Short V_1 , Open I_2 :

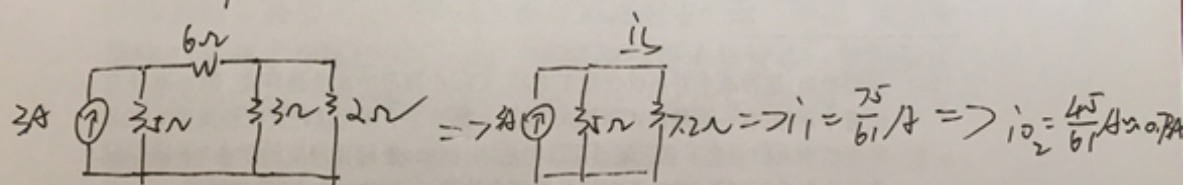

Short V_1 , Open I_1 :

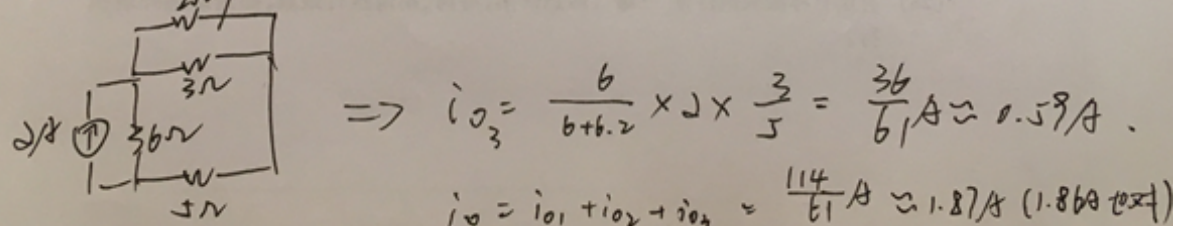

Problem 3 (12 points)

Find voltage difference value V_{ab} between node a and b from Fig. 3.


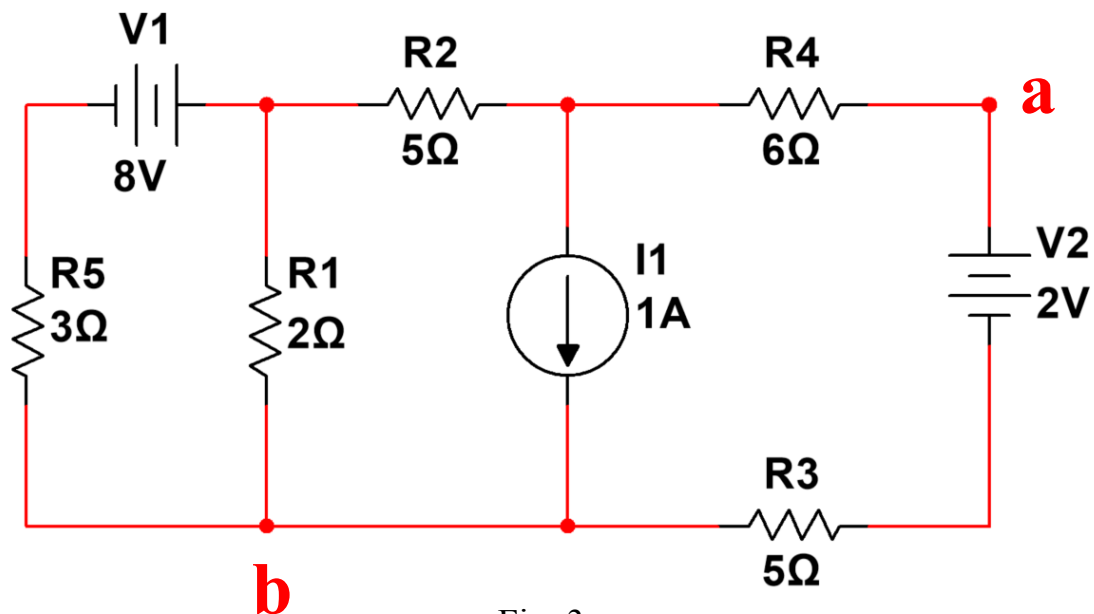


Fig. 3

Use supermesh to deal with the problem.

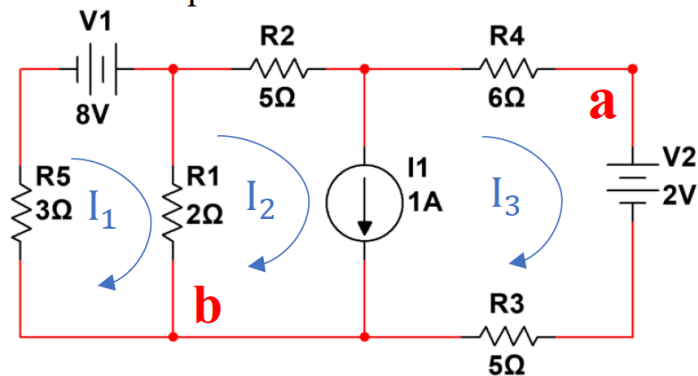

$$(2 + 3)I_1 - 2I_2 - 8 = 0$$

$$(5 + 2)I_2 + (6 + 5)I_3 - 2I_1 + 2 = 0 \text{ Supermesh}$$

$$I_2 - I_3 = 1A$$

$$\rightarrow I_1 = \frac{81}{43}A, I_2 = \frac{61}{86}A, I_3 = -\frac{25}{86}A$$

$$V_{ab} = 2V + 5\Omega * \left(-\frac{25}{86}A\right) = \frac{47}{86}A \approx 0.547A$$

Problem 4 (12 points)

In the circuit of Fig. 4, the maximum power delivered to R_L is 10W.

When R_L equals Thevenin equivalent resistance, the power of R_L reaches maximum. Find the current I_1 in Fig. 4 so that the power delivered to R_L is maximum.

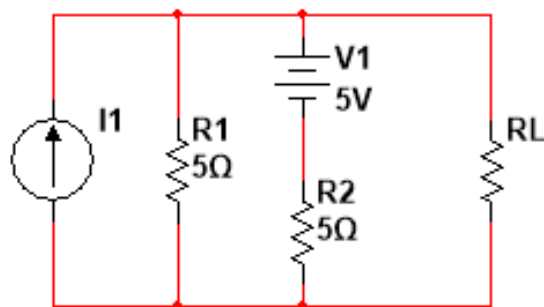


Fig. 4

4. $\Rightarrow \frac{V_{th}^2}{4R_L} = 10 \Rightarrow V_{th} = \pm 10V \Rightarrow I_{Th} = \pm 4A$
 $I_1 + 1A = I_{Th} \Rightarrow I_1 = 3A \text{ or } -5A.$

Problem 5 (12 points)

In the circuit shown in Fig. 5, find the Thevenin equivalent circuit for the network to the left of ab.

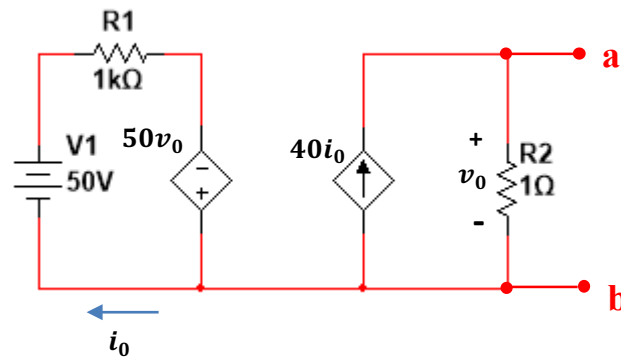


Fig. 5

5.

和 ab 左侧戴维南等效:

1. V_{oc} : 开路电压:

$$V_0 = 40i_0$$

$$\Rightarrow 50V_0 = 2000i_0$$

$$\Rightarrow i_0 = \frac{50 - (50V_0)}{1000} = \frac{50 + 2000i_0}{1000} \Rightarrow i_0 = -0.05A$$

$$\Rightarrow V_{oc} = V_0 = 40i_0 = -2V$$

I_{sc} : 短路电流:

$$V_0 = 0V \Rightarrow 50V_0 = 0V$$

$$\Rightarrow i_0 = \frac{50 - (50V_0)}{1000} = \frac{50}{1000} = 0.05A$$

$$\Rightarrow I_{sc} = +2A$$

$$\Rightarrow R_{Th} = \frac{V_{oc}}{I_{sc}} = \frac{-2V}{2A} = -1\Omega$$

Thevenin equivalent circuit: A 2V DC voltage source in series with a -1Ω resistor, connected to terminals a and b.

Problem 6 (12 points)

In the circuit shown in Fig. 6, find the voltage V_0 .

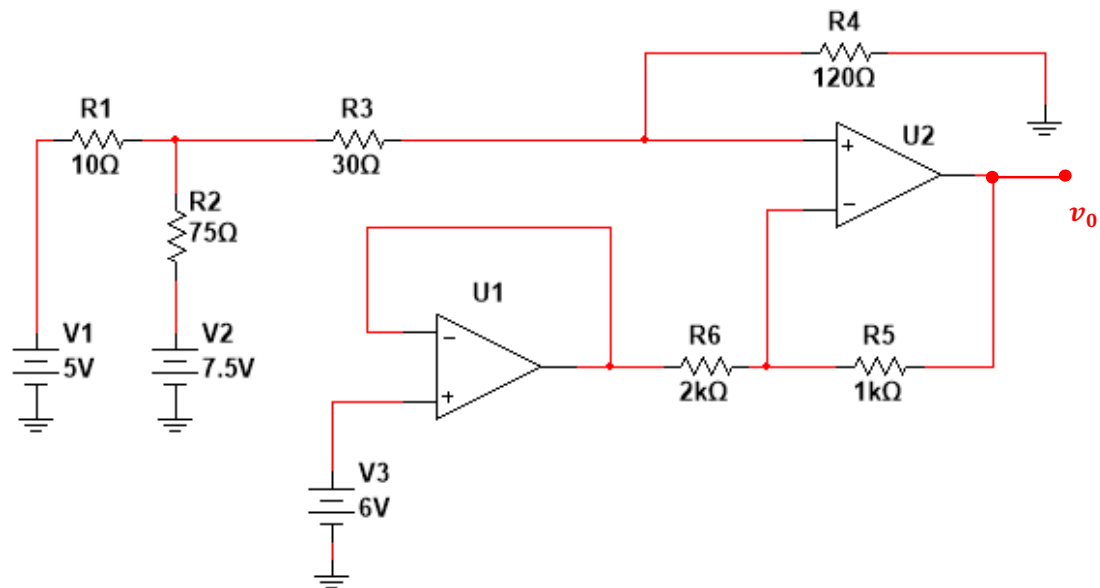


Fig. 6

6

$$\frac{5-V_a}{10} + \frac{2.5-V_a}{75} + \frac{0-V_a}{150} = 0.$$

$$\Rightarrow V_a = 5V.$$

$$V_b = 5 \times \frac{4}{5} = 4V.$$

$$\frac{6-4}{2k} + \frac{V_0-4}{1k} = 0$$

$$\Rightarrow V_0 = 3V$$

Problem 7 (12 points)

In the circuit shown in Fig. 7, find the output voltage V_{OUT} .

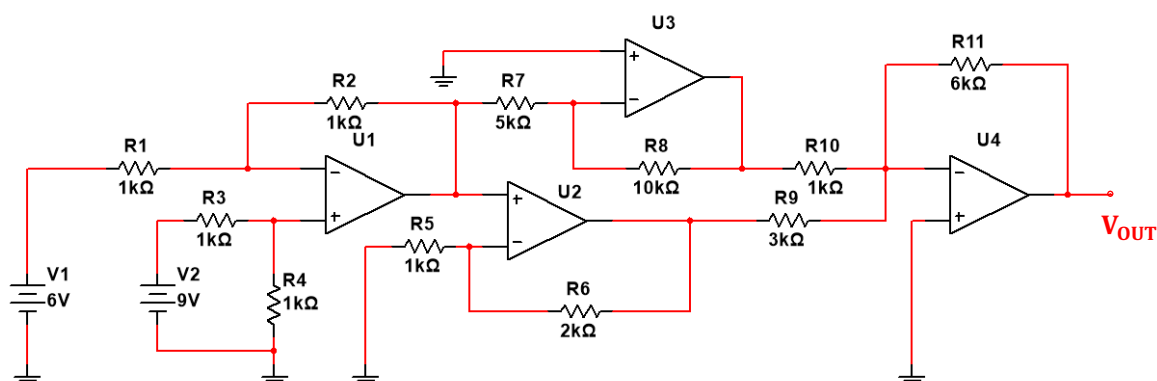


Fig. 7

7. U_1 is a difference amplifier.

$$\Rightarrow U_{1(out)} = \frac{R_2}{R_1} (V_2 - V_1) = 3V.$$

U_2 is a noninverting amplifier.

$$\Rightarrow U_{2(out)} = \left(1 + \frac{R_6}{R_5}\right) \cdot U_{1(out)} = 9V.$$

U_3 is an inverting amplifier.

$$\Rightarrow U_{3(out)} = -\frac{R_8}{R_7} \cdot U_{2(out)} = -6V.$$

U_4 is a summer amplifier.

$$\begin{aligned} \Rightarrow U_{4(out)} &= -\left(\frac{R_{11}}{R_{10}} U_{3(out)} + \frac{R_{11}}{R_9} U_{2(out)}\right) \\ &= - (6 \times (-6) + 2 \times 9) = 18V. \end{aligned}$$

Problem 8 (16 points)

The circuit inside the shaded area in Fig. 8 is a constant current source for a limited range of R_L . (You can assume that $i_n = i_p \approx 0$ under all operation conditions.)

- Find the value of i_L for $R_L = 4k\Omega$.
- Find the maximum value for R_L for which i_L will have the value in (a).
- Assume that $R_L = 16k\Omega$. Explain the operation of the circuit.
- Find the relation between i_L and R_L for $0 \leq R_L \leq 16k\Omega$, and sketch it out in a plot.

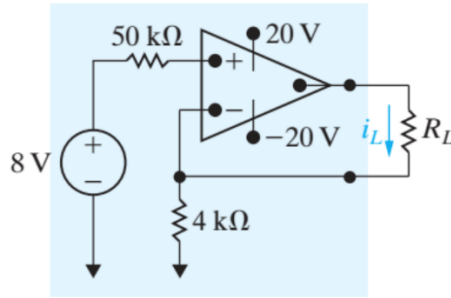


Fig.8

- [a] Assume the op-amp is operating within its linear range, then

$$i_L = \frac{8}{4000} = 2\text{mA}$$

$$\text{For } R_L = 4k\Omega \quad v_o = (4 + 4)(2) = 16\text{ V}$$

Now since $v_o < 20\text{ V}$ our assumption of linear operation is correct, therefore

$$i_L = 2\text{mA}$$

- [b] $20 = 2(4 + R_L); \quad R_L = 6k\Omega$

- [c] As long as the op-amp is operating in its linear region i_L is independent of R_L . From (b) we found the op-amp is operating in its linear region as long as $R_L \leq 6k\Omega$. Therefore when $R_L = 6k\Omega$ the op-amp is saturated. We can estimate the value of i_L by assuming $i_p = i_n \ll i_L$. Then $i_L = 20/(4000 + 16,000) = 1\text{mA}$. To justify neglecting the current into the op-amp assume the drop across the $50k\Omega$ resistor is negligible, since the input resistance to the op-amp is at least $500k\Omega$. Then $i_p = i_n = (8 - 4)/(500 \times 10^3) = 8\mu\text{A}$. But $8\mu\text{A} \ll 1\text{mA}$, hence our assumption is reasonable.

