



# **Lecture 14**

## **-- Laplace Transform in Circuit Analysis**




# Introduction

- In this lecture, we introduce the concept of modeling circuits in the  $s$  domain **using the Laplace transform**.
- The elegance of using the Laplace transform in circuit analysis lies in the automatic inclusion of initial conditions in the transformation process, thus providing a complete (transient and steady-state) solution.



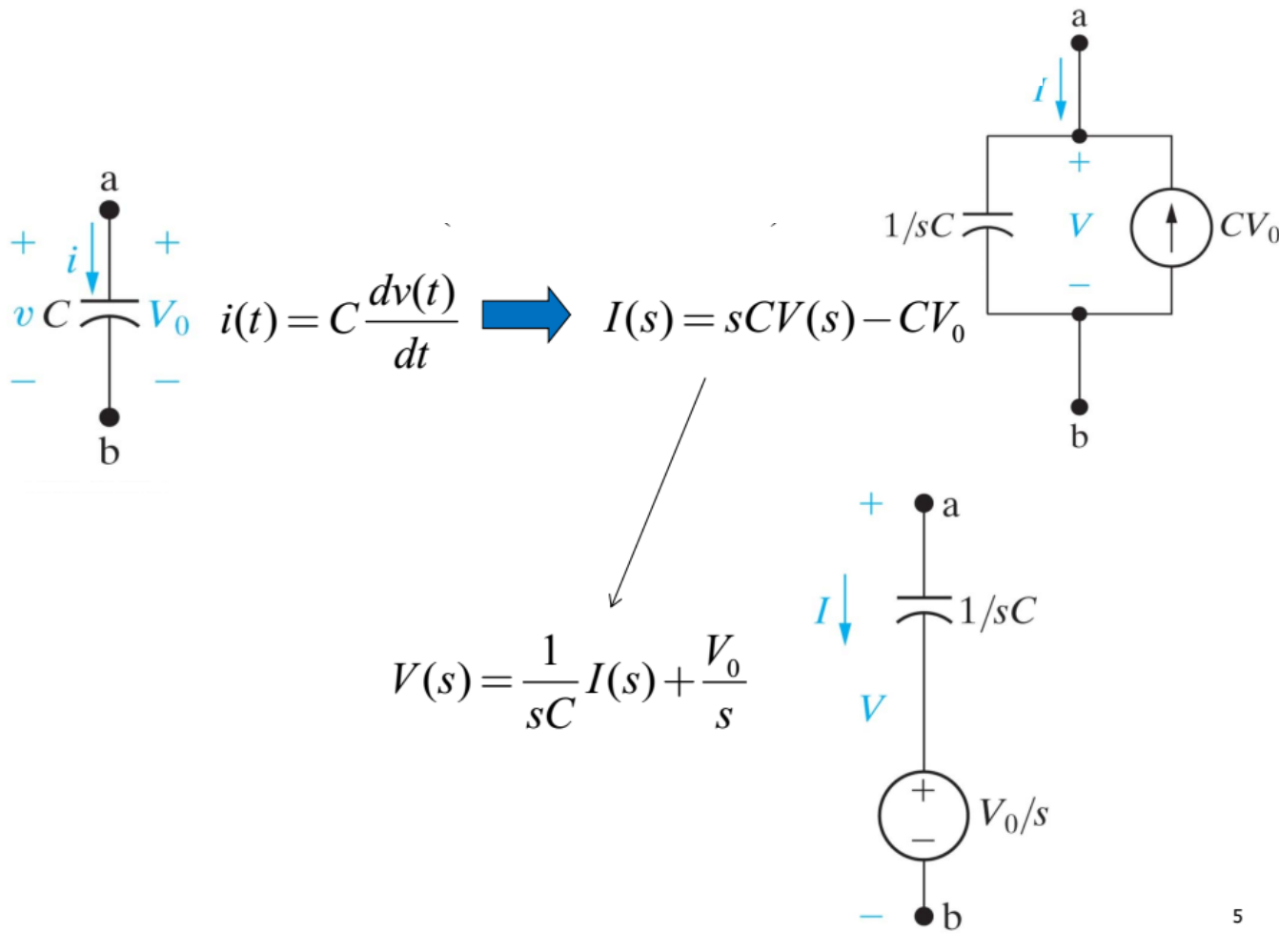
# S-domain circuit models for a capacitor







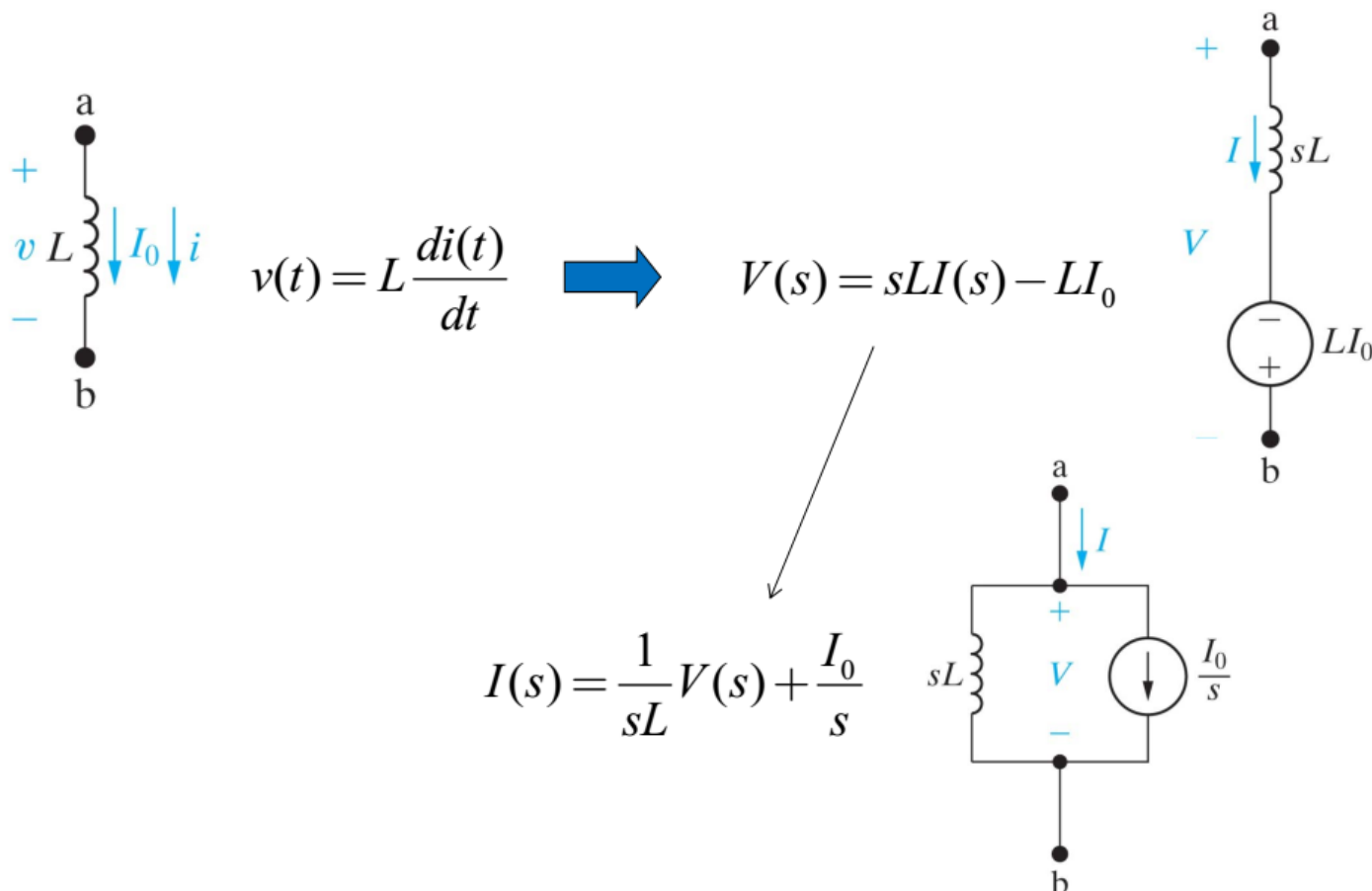
# S-domain circuit models for an inductor










# Summary

## Time domain

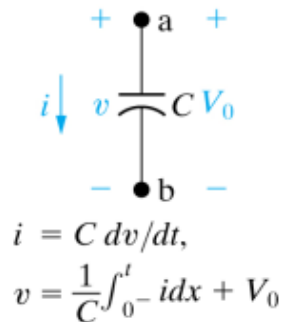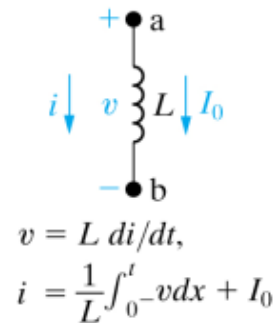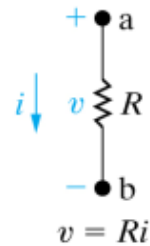

## s-domain

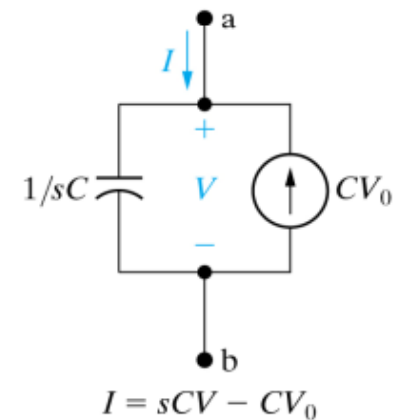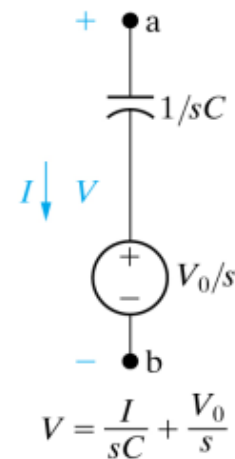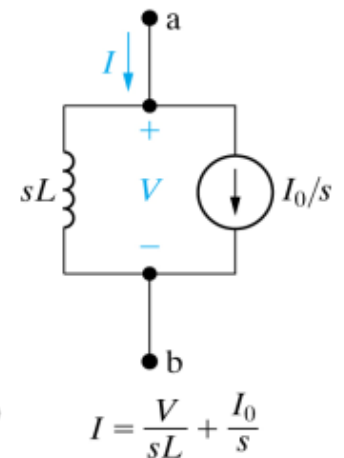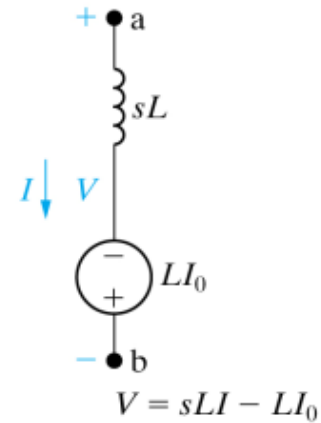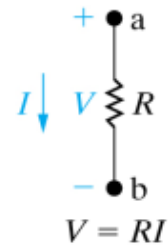



## Dependent Sources

- The models for dependent sources are easy to develop, drawing from the simple fact that if the Laplace transform of  $f(t)$  is  $F(s)$ , then the Laplace transform of  $af(t)$  is  $aF(s)$  — the linearity property.

$$\mathcal{L}[av(t)] = aV(s)$$

$$\mathcal{L}[ai(t)] = aI(s)$$




## Steps in Applying the Laplace transform

- Transform the circuit from the time domain to the Laplace ( $s$ ) domain, including possible initial conditions.
- Solve the circuit using nodal analysis, mesh analysis, source transformation, superposition, or any other analysis technique with which we are familiar.
- Take the inverse transform of the solution and thus obtain the solution in the time domain.


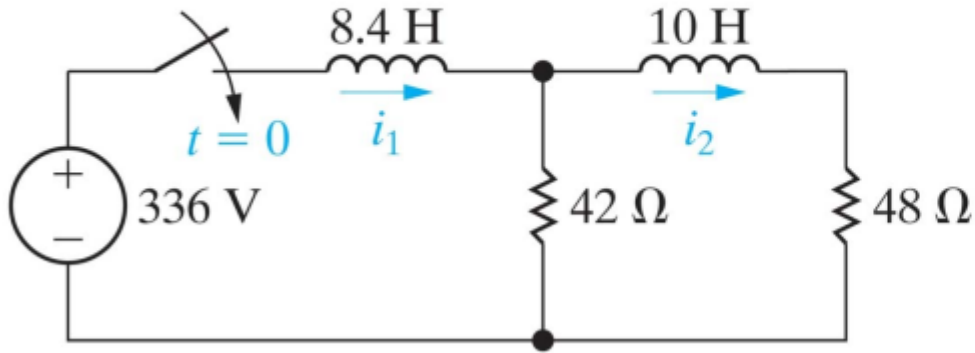
## Example 1

Assuming no initial energy storage, find  $i_1(t)$  and  $i_2(t)$  for  $t > 0$ .








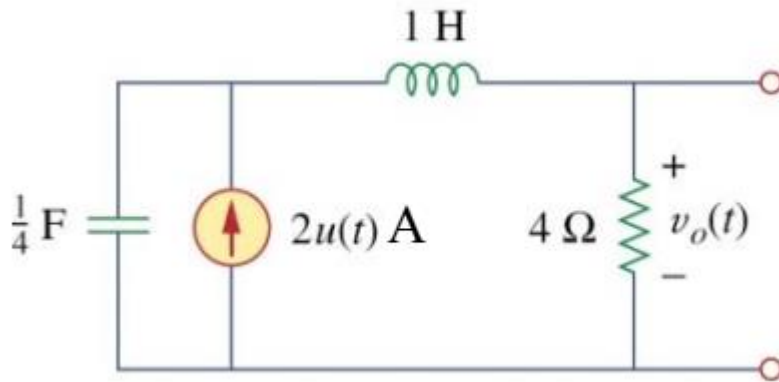
## Example 2

Determine  $v_o(t)$  for  $t > 0$  assuming zero initial conditions:




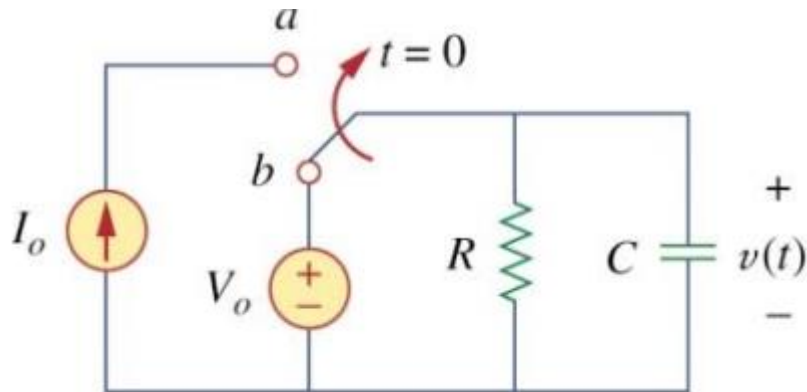
## Example 3

- The switch has been in position  $b$  for a long time. It is moved to position  $a$  at  $t = 0$ . Determine  $v(t)$  for  $t > 0$ .



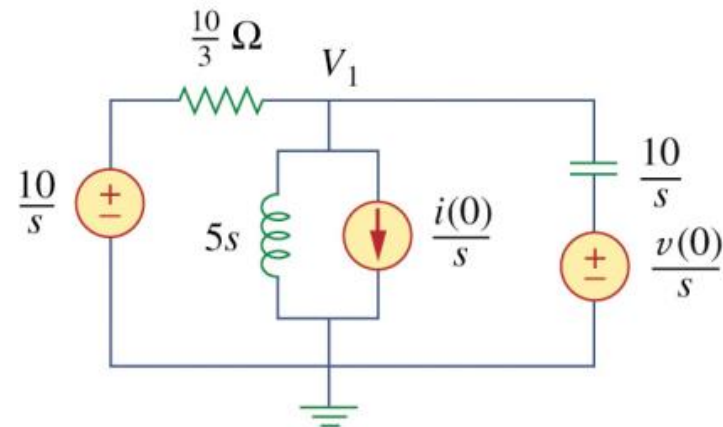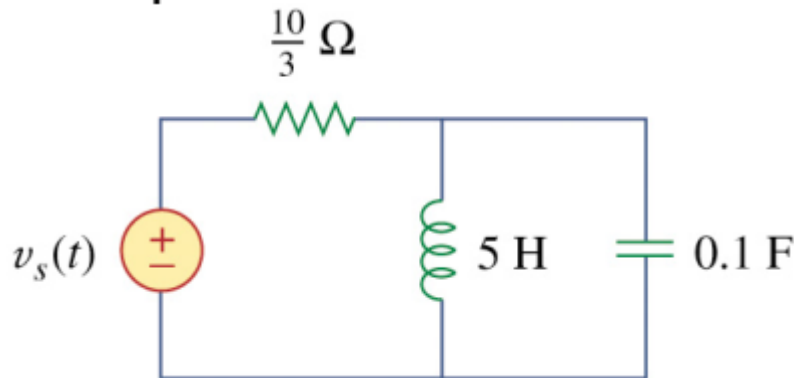
## Example 4

- Find the voltage across the capacitor assuming that  $v_s(t) = 10u(t)$  V, and assume that at  $t = 0$ ,  $-1$  A flows through the inductor and  $+5$  V is across the capacitor.


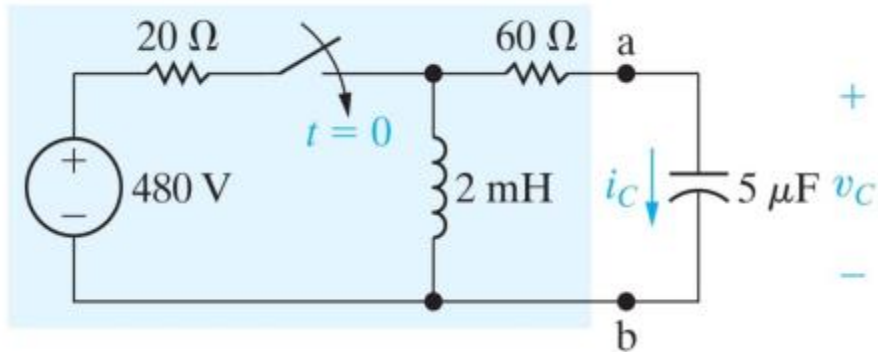
## Example 5



- Use Thevenin's equivalent circuit wrt terminals  $a$ - $b$  to find current  $i_C(t)$ .




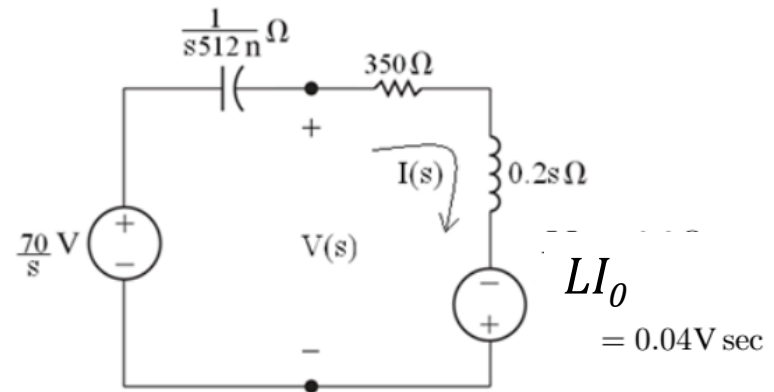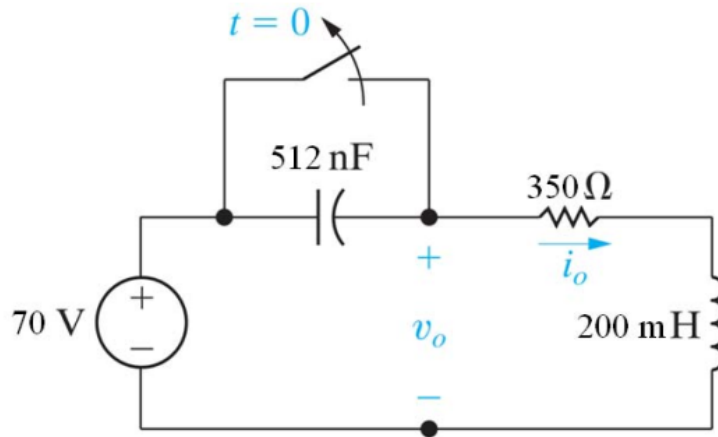
## Example 6

Laplace transform the circuit and solve for  $V_0(s)$ .



## Example 7

- There is no initial energy stored in this circuit. Find  $i(t)$  if
- $v(t) = e^{-0.6t} \sin 0.8t$  V.

