

EE 111 Homework 5

Due date: May. 06<sup>th</sup>, 2019

Turn in your homework in class

Rules:

- Work on your own. Discussion is permissible, but similar submissions will be judged as plagiarism.
- Please show all intermediate steps: a correct solution without an explanation will get zero credit.
- Please submit on time. No late submission will be accepted.
- Please prepare your submission in English only. No Chinese submission will be accepted.

**1. Calculation of Complex Numbers**

(1) 
$$\frac{(50 - j60)(220\angle 70^\circ + 150\angle -30^\circ)}{(70 - j80)90\angle 210^\circ}$$

(2) Solve  $x$  for

$$x^3 = (40\angle 50^\circ + 20 - j70) \frac{45 - j100}{30 - j80}$$



**2. Find the following results (using phasors if necessary)**

(1)  $3 \cos(30t + 40^\circ) - 20 \sin(30t - 70^\circ)$

(2)  $30 \cos^2(10t + 30^\circ) - 40 \sin(20t - 120^\circ)$


(3) Solve the integrodifferential equation:

$$\frac{dv(t)}{dt} + 4v(t) + 3 \int v(t) dt = 20 \sin(10t + 20^\circ)$$

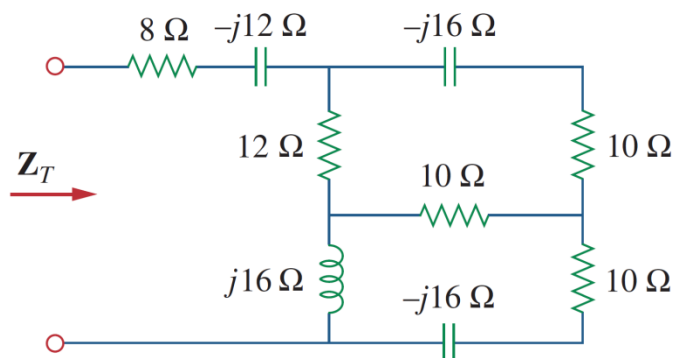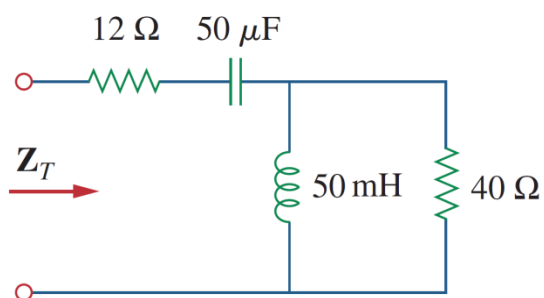**3. Find the equivalent impedance**(1) Find  $Z_T$ (2) Find  $Z_T$  where the system is operating at the frequency  $f = 50\text{ Hz}$ .

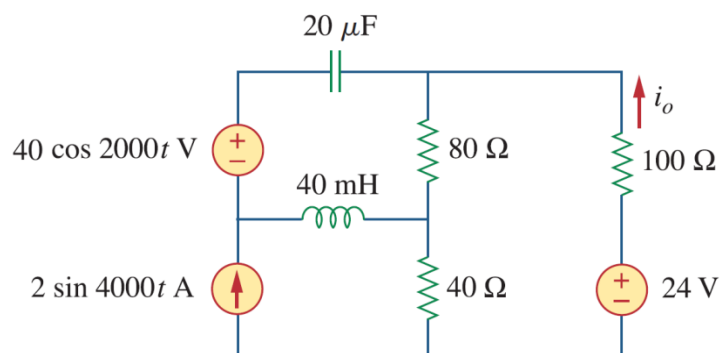
**4. Superposition Theorem**

Find steady state current  $i_o(t)$  using Superposition Theorem



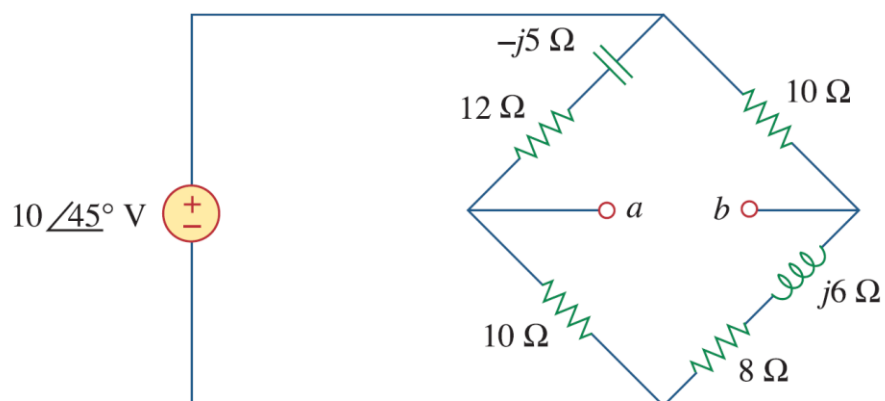
**5. Thevenin equivalent**

Find Thevenin equivalent circuit at terminals a-b



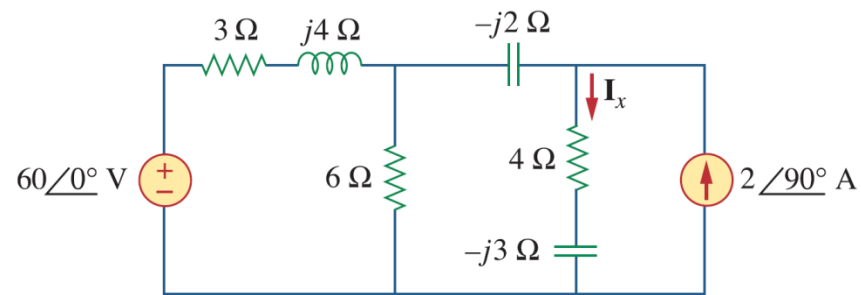**6. Source Transformation**

The two sources are with the same angular frequency. Use source transformation to find  $\tilde{I}_x$



7.  $\tilde{V}_{in}$  and  $\tilde{I}_{in}$  are phasors. Express  $\frac{\tilde{V}_{in}}{\tilde{I}_{in}}$  as functions of  $R_1, R_2, R_3, R_4$  and  $C$ .

