

Homework 6

Due date:

Apr. 23rd, 2018

Turn in your homework in class

Rules:

- Work on your own. Discussion is permissible, but extremely similar submissions will be judged as plagiarism.
- Please show all intermediate steps: a correct solution without an explanation will get zero credit.
- Please submit on time. No late submission will be accepted.
- Please prepare your submission in English only. No Chinese submission will be accepted.

1. A series RLC circuit exhibits the following voltage and current responses:

$$v_c(t) = (6\cos 4t - 3\sin 4t)e^{-2t}u(t) \text{ V}$$

$$i_c(t) = -(0.2\cos 4t + 0.18\sin 4t)e^{-2t}u(t) \text{ A}$$

Determine α , ω_0 , R, L and C

2. Determine $v_c(t)$ in the Fig.1 for $t \geq 0$.

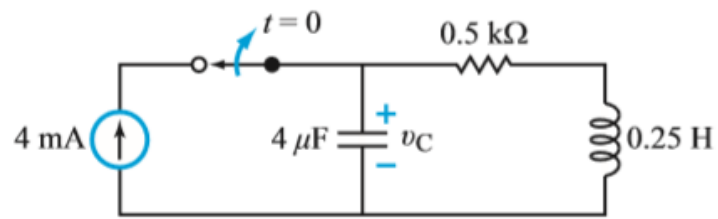


Figure 1

3. When $t < 0$, no energy is stored in the capacitor in Fig.2. The switch moves from position A to position B at $t = 0$. Determine $i(t)$ for $t \geq 0$.

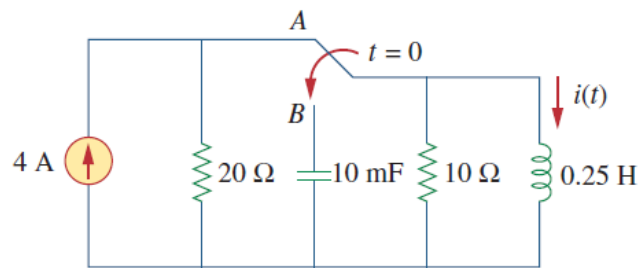


Figure 2

4. When $t < 0$, no energy is stored in the capacitor nor the inductor in the circuit of Fig. 3. Find $i(t)$ for $t \geq 0$.

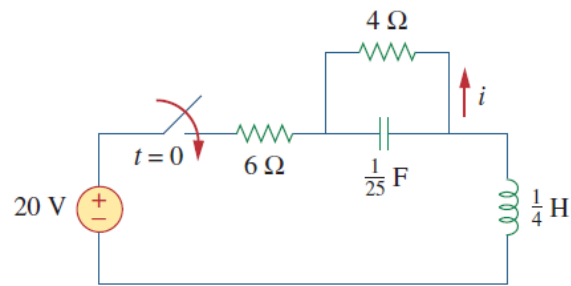


Figure 3

5. Choose the value of C in the circuit of Fig. 4 so that $v_c(t)$ has a critically damped response for $t \geq 0$.

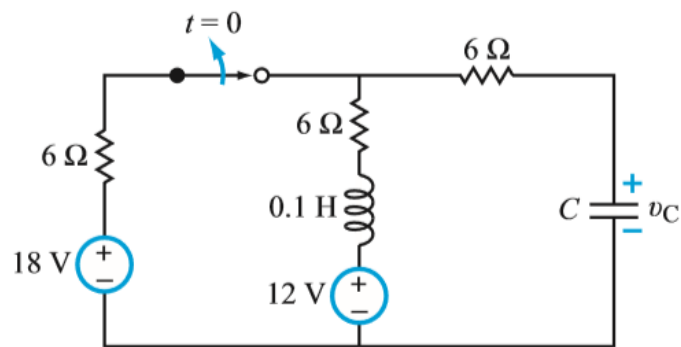


Figure 4

6. Determine $v_C(t)$ in the circuit for $t \geq 0$, given that $V_0 = 12V$, $R_1 = 0.4 \Omega$, $R_2 = 1.2 \Omega$, $L = 0.1 \text{ H}$ and $C = 0.4 \text{ F}$.

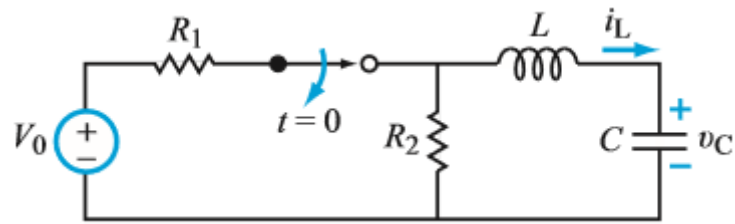


Figure 5

7. The initial value of the voltage v in the circuit shown in Fig. 6 is zero, and the initial value of the capacitor current, $i_C(0^+)$ is 45 mA. The expression for the capacitor current is known to be $i_C(t) = A_1 e^{-200t} + A_2 e^{-800t}$, $t \geq 0^+$,

$R=250\Omega$. Find:

- (a) The value of L , C , A_1 and A_2 .
(b) The express for $v(t)$ for $t \geq 0$.

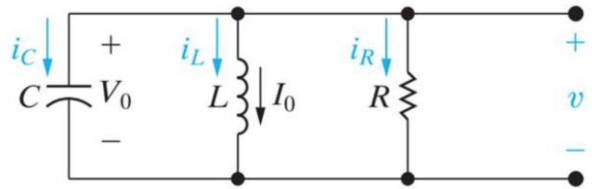


Figure 6

8. The op-amp circuit shown in Fig.7 is called a two-pole low-pass filter. If $v_{in} = Au(t)$, determine $v_{out}(t)$ for $t \geq 0$ when $A = 2V$, $R_1 = 5k\Omega$, $R_2 = 10k\Omega$, $R_3 = 12k\Omega$, $R_4 = 20k\Omega$, $C_1 = 100\mu F$, and $C_2 = 200\mu F$. (No energy is stored in the capacitors when $t < 0$).

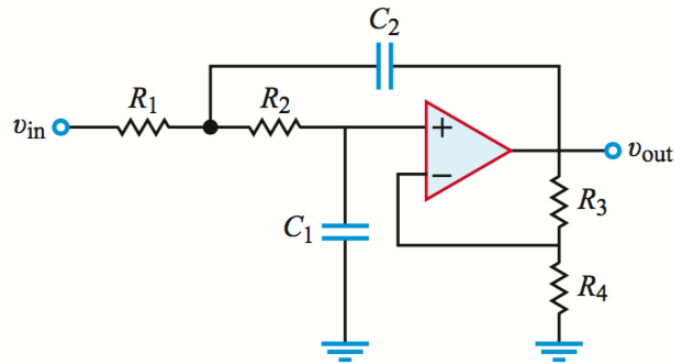


Figure 7

9. The voltage signal of Fig. 8 (b) is applied to the cascaded integrating amplifiers shown in Fig. 8 (a). There is no energy stored in the capacitors at the instant the signal is applied. Derive the numerical expressions for $v_{o1}(t)$ and $v_{o2}(t)$ for the time intervals $0 < t < 1$ s. Assume the Ops are working in their linear range.

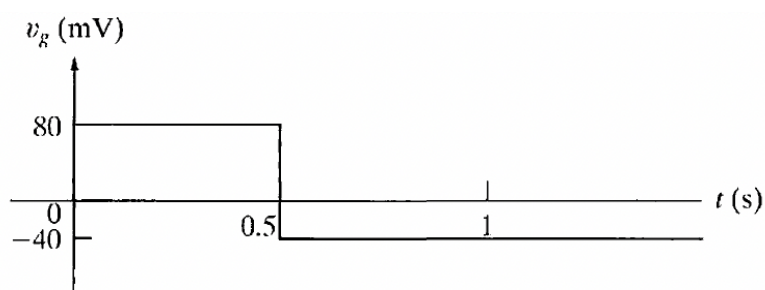
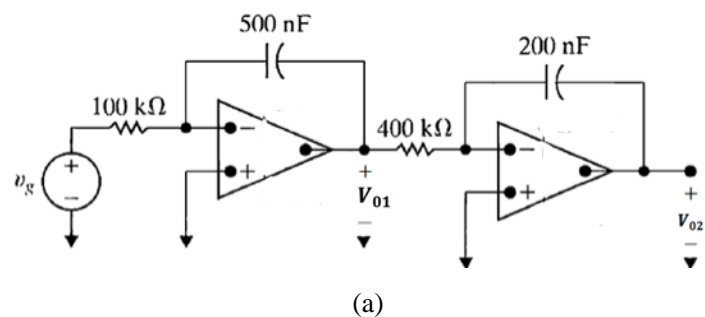


Figure 8

10. In the circuit shown in Fig.9, the switch is closed at $t = 0$ and re-opened at $t = 0.5$ s. Determine the response $i_L(t)$ for $t \geq 0$. There's no energy stored in the inductor and capacitor when $t < 0$.

Assume that $V_s = 18\text{V}$, $R_s = 1\Omega$, $R_1 = 5\Omega$, $R_2 = 2\Omega$, $L = 2\text{H}$ and $C = \frac{1}{17}\text{F}$.

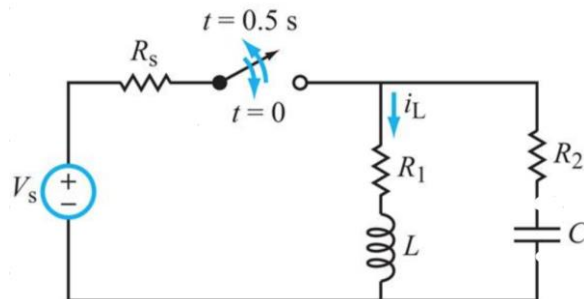


Figure 9