




Outline

- Capacitors and inductors
- Natural response of RC/RL circuits
- Step response of RC/RL circuits
- Others

Step Response of RC Circuit

- When a **DC source** is suddenly applied to a RC circuit, the circuit response is known as the step response.

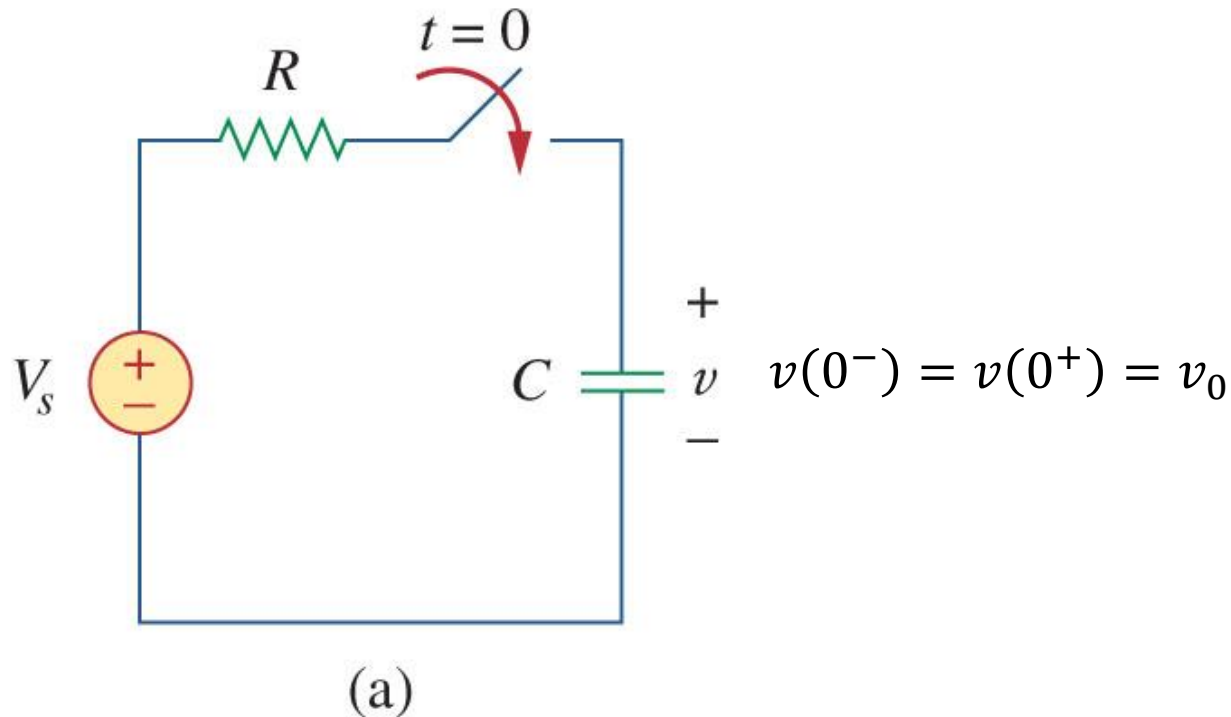
Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display



The Unit Step $u(t)$

- A step function is one that maintains a constant value before a certain time and then changes to another constant afterwards.

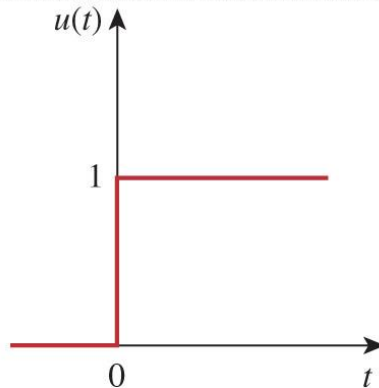Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display




$$u(t) = \begin{cases} 0, & t < 0 \\ 1, & t > 0 \end{cases}$$

switching time may be shifted to $t = t_0$ by


$$u(t - t_0) = \begin{cases} 0, & t < t_0 \\ 1, & t > t_0 \end{cases}$$

Equivalent Circuit of Unit Step

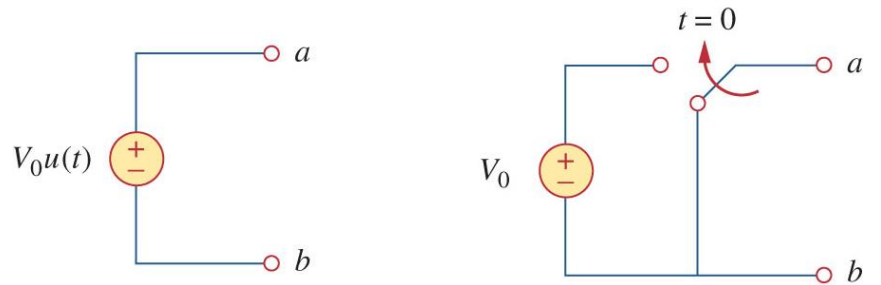- The unit step function has an equivalent circuit to represent when it is used to switch on a source.



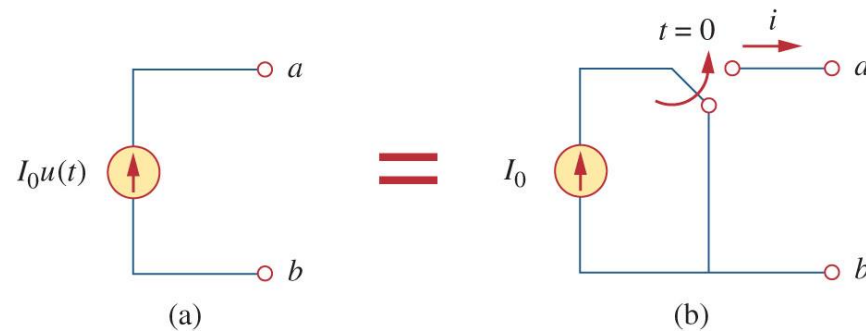
Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display





Step Response of the RC Circuit

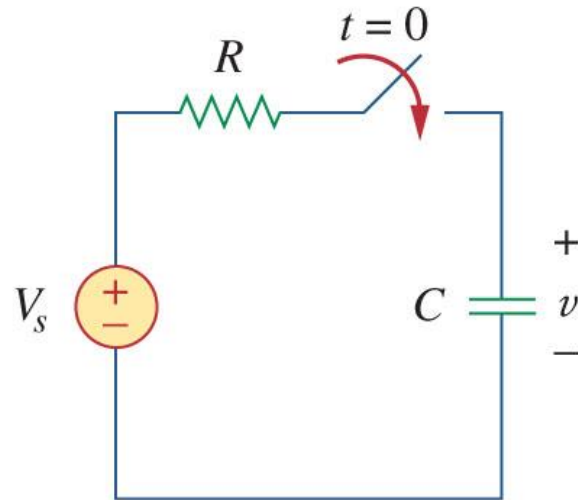Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display




$$v(0^-) = v(0^+) = V_0$$





Step Response of the RC Circuit

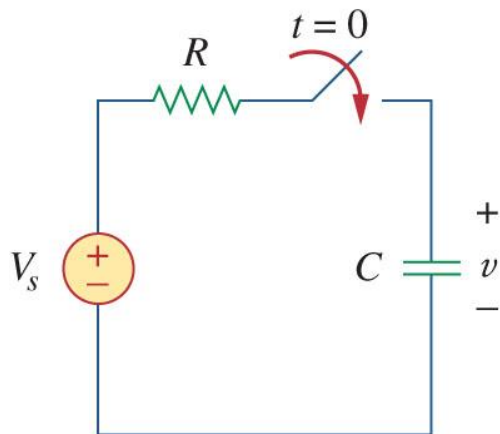
Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display



$$v(0^-) = v(0^+) = V_0$$

$$v(t) = \begin{cases} V_0, & t < 0 \\ V_s + (V_0 - V_s)e^{-t/\tau} & t > 0 \end{cases}$$

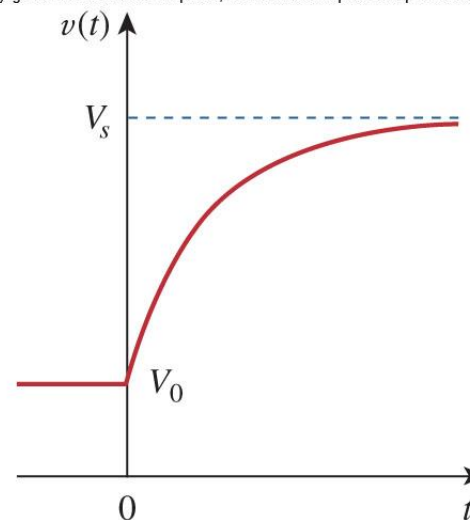Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display




- This is known as the complete response, or total response.



Complete response

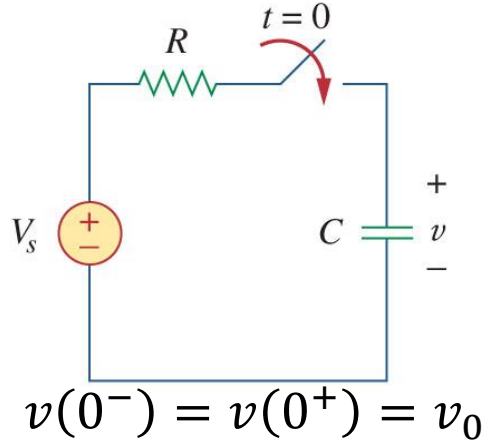Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display




- The complete response

$$v(t) = \begin{cases} V_0, & t < 0 \\ V_s + (V_0 - V_s)e^{-t/\tau} & t > 0 \end{cases}$$

can be written as:

$$v = v_n + v_f$$

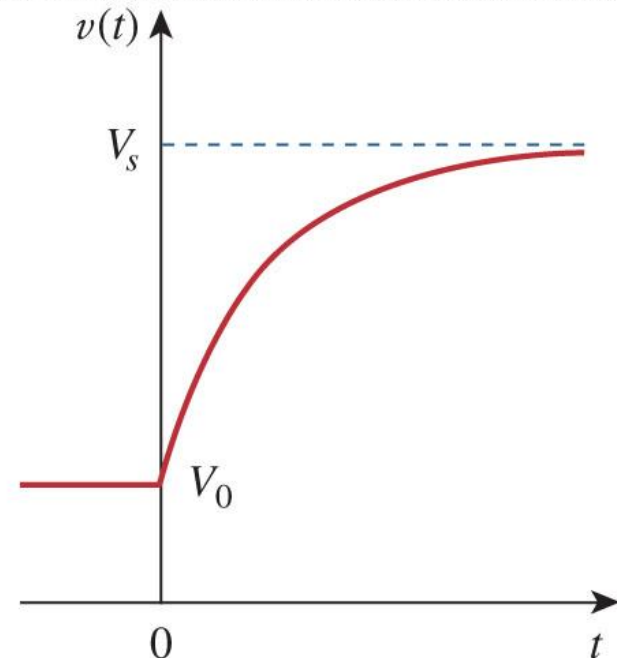Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display





$$\text{Complete response} = \underset{\text{stored energy}}{\text{natural response}} + \underset{\text{independent source}}{\text{forced response}}$$

or

$$v = v_n + v_f$$

where


$$v_n = V_o e^{-t/\tau}$$

and

$$v_f = V_s(1 - e^{-t/\tau})$$

Another Perspective
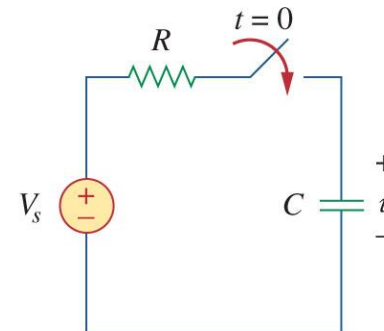
$$v(t) = \begin{cases} V_0, & t < 0 \\ V_s + (V_0 - V_s)e^{-t/\tau} & t > 0 \end{cases}$$




- Another way to look at the response is to break it up into the transient response and the steady state response:

$$v(t) = \underbrace{v(\infty)}_{\text{steady } v_{ss}} + \underbrace{[v(0) - v(\infty)]e^{-t/\tau}}_{\text{transient } v_t}$$



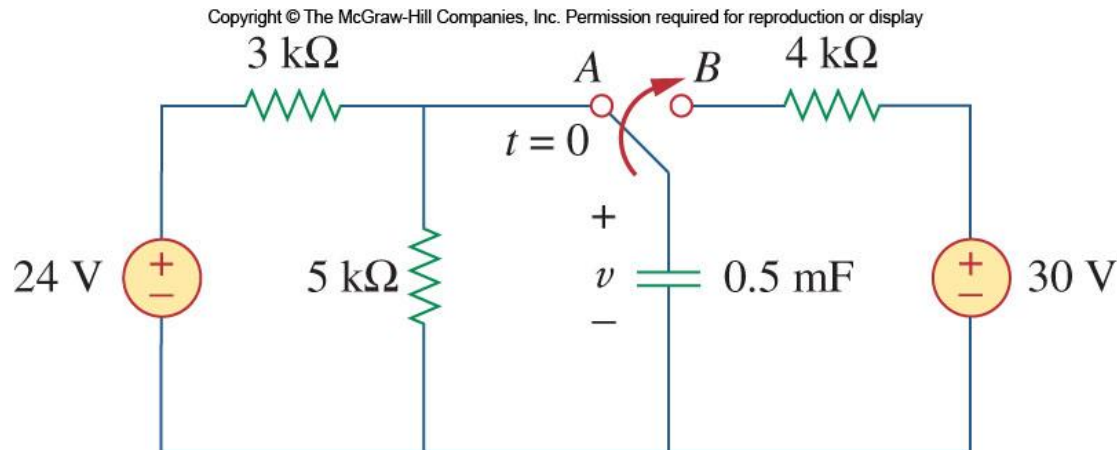Example


- The switch has been in position A for a long time. At $t = 0$, the switch moves to B. Find $v(t)$.





Step Response of the RL Circuit

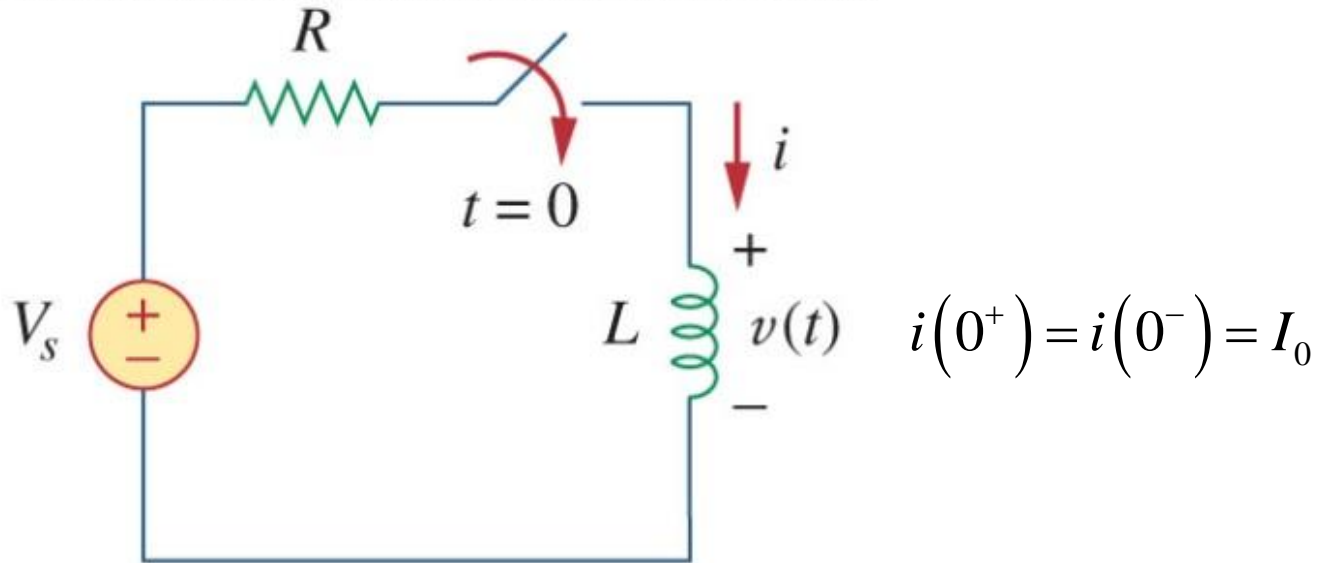Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display





Step Response of the RL Circuit



- We will use the transient and steady state response approach.
- We know that the transient response will be an exponential:

$$i_t = Ae^{-t/\tau}$$

- After a sufficiently long time, the current will reach the steady state:

$$i_{ss} = \frac{V_s}{R}$$

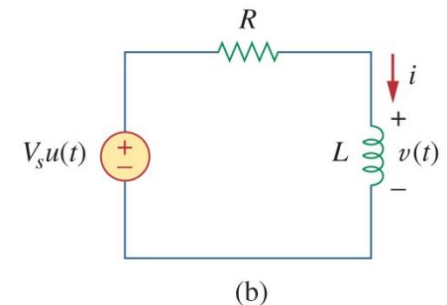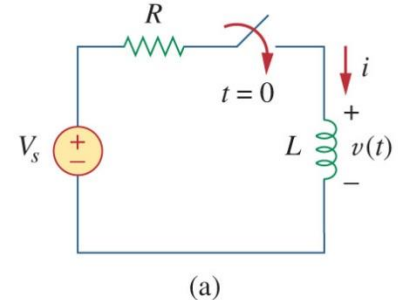
Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display



Step Response of RL Circuit

- This yields an overall response of:

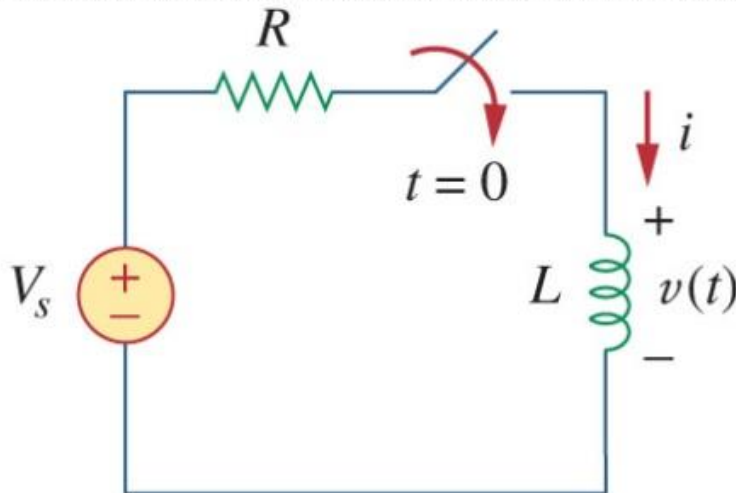Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display



$$i = Ae^{-t/\tau} + \frac{V_s}{R}$$

$$i(0^+) = i(0^-) = I_0 \quad A = I_0 - \frac{V_s}{R}$$

$$i(t) = \frac{V_s}{R} + \left(I_0 - \frac{V_s}{R} \right) e^{-t/\tau}$$



General Procedure of Finding RC/RL Response with D.C. sources

1. Identify the variable of interest

- For RL circuits, it is usually the inductor current $i_L(t)$.
- For RC circuits, it is usually the capacitor voltage $v_c(t)$.

2. Determine the initial value of the variable at t_0

- Recall that $i_L(t)$ and $v_c(t)$ are continuous variables:

$$i_L(t_0^+) = i_L(t_0^-) \quad \text{and} \quad v_c(t_0^+) = v_c(t_0^-)$$

3. Determine the final value of the variable (as $t \rightarrow \infty$)



If needed, recall an inductor behaves like a short circuit in steady state ($t \rightarrow \infty$) & that a capacitor behaves like an open circuit in steady state ($t \rightarrow \infty$).

4. Calculate the time constant for the circuit

- $\tau = CR$ for an RC circuit where R is the Thévenin equivalent resistance “seen” by the capacitor.
- $\tau = L/R$ for an RL circuit, where R is the Thévenin equivalent resistance “seen” by the inductor.




Response Form of Basic First-Order Circuits

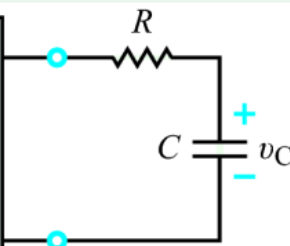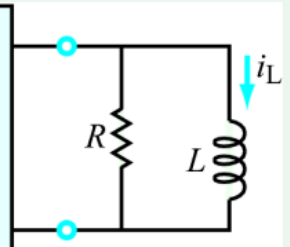Circuit	Diagram	Response
RC	<p>Input: dc circuit with switch action @ $t = T_0$</p> 	$v_C(t) = \left\{ v_C(\infty) + [v_C(T_0) - v_C(\infty)]e^{-(t-T_0)/\tau} \right\}$ <p style="text-align: center;">$(\tau = RC)$</p>
RL	<p>Input: dc circuit with switch action @ $t = T_0$</p> 	$i_L(t) = \left\{ i_L(\infty) + [i_L(T_0) - i_L(\infty)]e^{-(t-T_0)/\tau} \right\}$ <p style="text-align: center;">$(\tau = L/R)$</p>

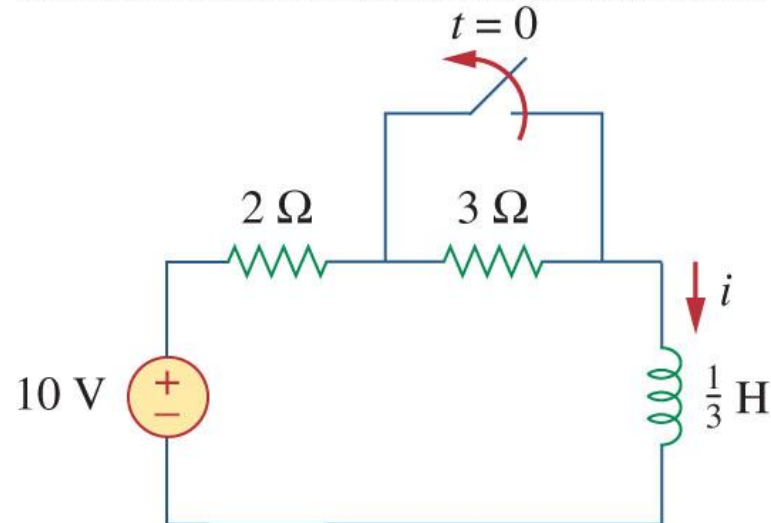Example

- Find $i(t)$ in the circuit for $t > 0$. Assume that the switch has been closed for a long time.


Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display





Sequential switch

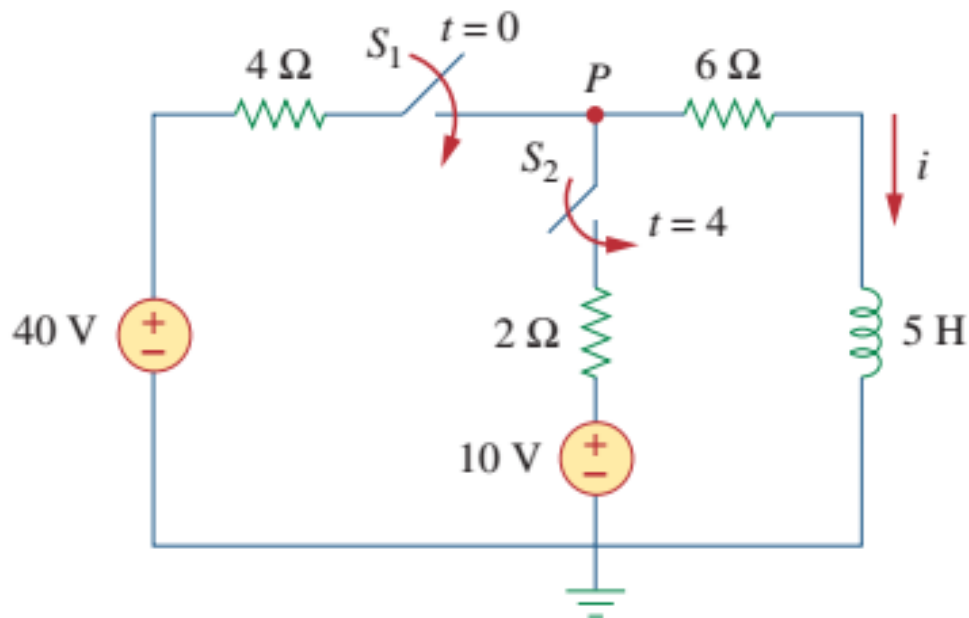At $t = 0$, switch 1 in Fig. 7.53 is closed, and switch 2 is closed 4 s later. Find $i(t)$ for $t > 0$. Calculate i for $t = 2$ s and $t = 5$ s.



We need to consider the three time intervals $t \leq 0$, $0 \leq t \leq 4$, and $t \geq 4$ separately. For $t < 0$, switches S_1 and S_2 are open so that $i = 0$. Since the inductor current cannot change instantly,

$$i(0^-) = i(0) = i(0^+) = 0$$



Practice

