

**Problem 1 (6 points) – Boost converter**

In Lab9, we learned a boost converter circuit as shown in Fig.1. For this circuit,

- 1) Find the ratio of  $T_{on}/T_{off}$ .
- 2) Find the value of inductance  $L$  when  $\Delta I_L = 2\text{mA}$  and  $T = 3\mu\text{s}$ .

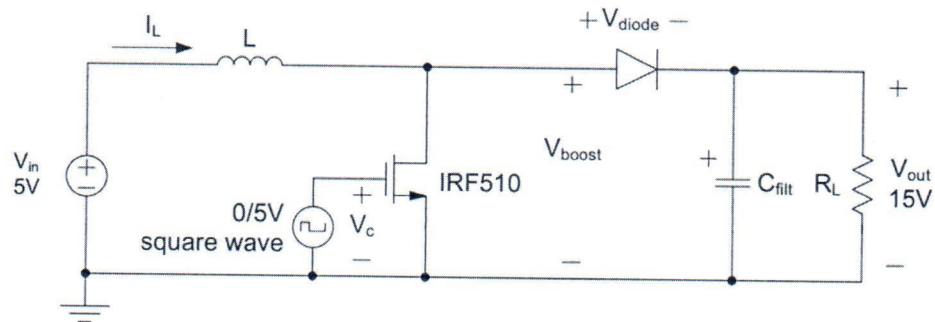


Fig. 1 (a) Boost Converter used in Lab 9.

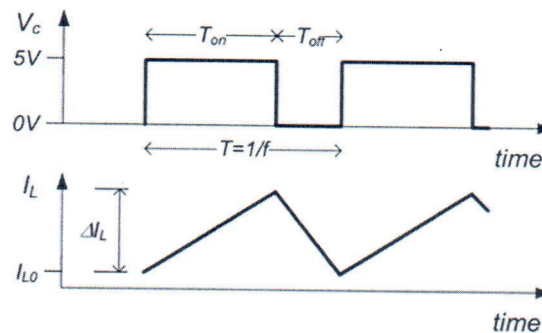


Fig. 1 (b) Timing diagram of the boost converter shown in Fig. 1(a).

Your answer:

①  $V = L \frac{di}{dt} \Rightarrow \Delta i = \frac{V}{L} \cdot \Delta t$

$\Delta I_{on} = \Delta I_{off}$

$\frac{5V}{L} \cdot T_{on} = \frac{15-5}{L} \cdot T_{off} \Rightarrow \frac{T_{on}}{T_{off}} = 2:1$

②  $\frac{5V}{L} \cdot T_{on} = 2\text{mA}$ ,  $T_{on} = \frac{2}{3}T = 2\mu\text{s}$

$L = \frac{5V \cdot 2\mu\text{s}}{2\text{mA}} = 5\text{mH}$

3+3=6

**Problem 2 (20 points) – First-order circuit analysis**

You must show your work to get full credit.

Determine the current  $i_o(t)$  in the circuit shown in Fig. 2.

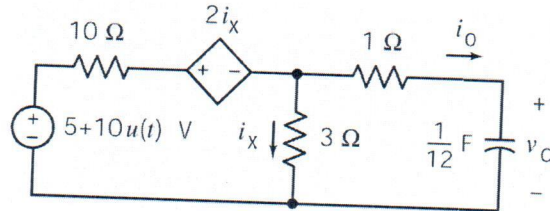


Fig. 2

Your answer:

Consider the circuit for time  $t < 0$ .

**Step 1:** Determine the initial capacitor voltage.

The circuit will be at steady state before the source voltage changes abruptly at time  $t = 0$ .

The source voltage will be 5 V, a constant.

The capacitor will act like an open circuit.


Apply KVL to the mesh to get:

$$(10 + 2 + 3)i_x - 5 = 0 \Rightarrow i_x = \frac{1}{3} \text{ A}$$

Then

$$v_C(0) = 3i_x = 1 \text{ V}$$


$t < 0$ , at steady state:

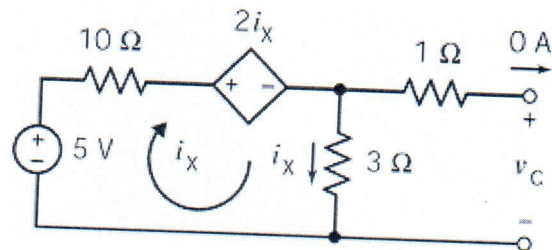

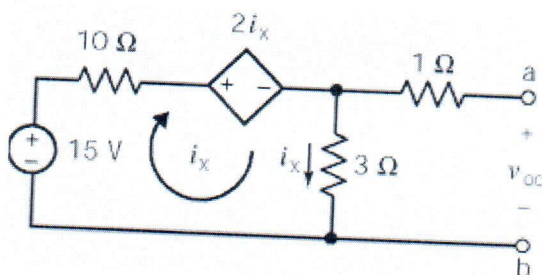(3)

Consider the circuit for time  $t > 0$ .

**Step 2.** The circuit will not be at steady state immediately after the source voltage changes abruptly at time  $t = 0$ . Determine the Thevenin equivalent circuit for the part of the circuit connected to the capacitor. First, determine the open circuit voltage,  $v_{oc}$ :



Apply KVL to the mesh to get:

$$(10 + 2 + 3)i_x - 15 = 0 \Rightarrow i_x = 1 \text{ A}$$


Then

$$v_{oc} = 3i_x = 3 \text{ V}$$

(3)

Next, determine the short circuit current,  $i_{sc}$ :

Blank Page

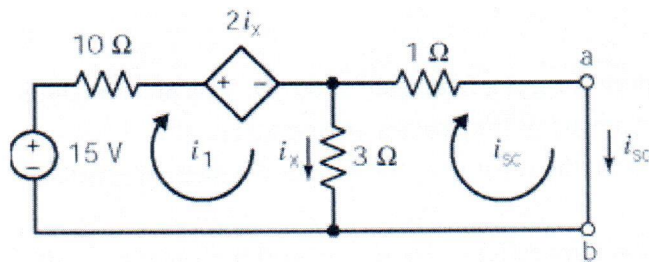

Express the controlling current of the CCVS in terms of the mesh currents:

$$i_x = i_1 - i_{sc}$$

The mesh equations are

$$10i_1 + 2(i_1 - i_{sc}) + 3(i_1 - i_{sc}) - 15 = 0 \Rightarrow 15i_1 - 5i_{sc} = 15$$

And

$$i_{sc} - 3(i_1 - i_{sc}) = 0 \Rightarrow i_1 = \frac{4}{3}i_{sc}$$

so

$$15\left(\frac{4}{3}i_{sc}\right) - 5i_{sc} = 15 \Rightarrow i_{sc} = 1 \text{ A}$$

The Thevenin resistance is


$$R_t = \frac{3}{1} = 3 \Omega$$

**Step 3.** The time constant of a first order circuit containing an capacitor is given by

$$\tau = R_t C$$

Consequently
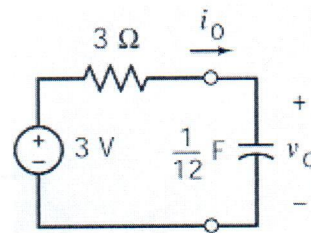
$$\tau = R_t C = 3\left(\frac{1}{12}\right) = 0.25 \text{ s and } a = \frac{1}{\tau} = 4 \frac{1}{\text{s}}$$



**Step 4.** The capacitor voltage is given by:

$$v_C(t) = v_{oc} + (v_C(0) - v_{oc})e^{-at} = 3 + (1 - 3)e^{-4t} = 3 - 2e^{-4t} \text{ for } t \geq 0$$

**Step 5.** Express the output current as a function of the source voltage and the capacitor voltage.

$$i_o(t) = C \frac{d}{dt} v_C(t) = \frac{1}{12} \frac{d}{dt} v_C(t)$$

**Step 6.** The output current is given by

$$i_o(t) = \frac{1}{12} \frac{d}{dt} (3 - 2e^{-4t}) = \frac{1}{12} (-2)(-4)e^{-4t} = \frac{2}{3} e^{-4t} \text{ for } t \geq 0$$

$$20 = 3 + 3 + 5 + 5 + 4$$



**Problem 3 (15 points) – Bandstop filter**

You must show your work to get full credit.

It is very common to see interference caused by the power lines, at a frequency of 60 Hz. This problem outlines the design of a notch filter, shown in Fig. 3(a), to reject a band of frequencies around 60 Hz.

- Write the impedance function for the filter of Fig. 3(a) (the resistor  $r_L$  represents the internal resistance of a practical inductor).
- For what value of  $C$  will the center frequency of the filter equal 60 Hz if  $L = 100 \text{ mH}$  and  $r_L = 5 \Omega$ ?
- Assume that the filter is used to eliminate the 60-Hz noise from a signal generator with output frequency of 1 kHz in Fig. 3(b). Evaluate the frequency response  $V_L(j\omega)/V_{in}(j\omega)$  at both frequencies (60 Hz and 1 kHz) if:

$$V_g(t) = \sin(2\pi 1000t) \text{ V}, \quad r_g = 50 \Omega$$

$$V_n(t) = 3\sin(2\pi 60t) \text{ V}, \quad R_L = 300 \Omega$$

and if  $L$  and  $C$  are as in part (b).

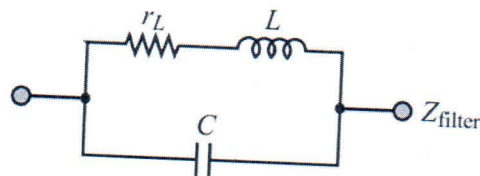


Fig. 3(a)

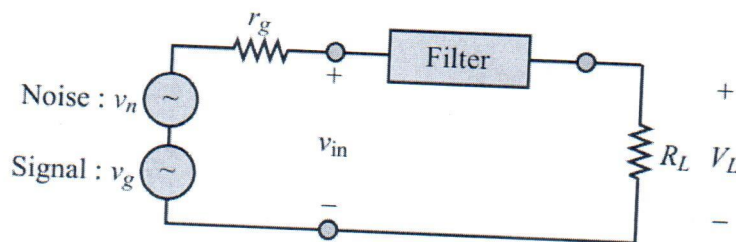


Fig. 3(b)

Your answer:

$$a) \quad Z_{\text{filter}} = (r_L + sL) \parallel \frac{1}{sC} = \frac{1}{\frac{1}{r_L + sL} + sC} = \frac{r_L + sL}{(r_L + sL)sC + 1}, \quad s = j\omega$$

b)

$$\frac{I}{V} = Y = \frac{1}{Z_{\text{filter}}} = \frac{1}{r_L + j\omega L} + j\omega C = \frac{r_L}{r_L^2 + \omega^2 L^2} + j\left(\omega C - \frac{\omega L}{r_L^2 + \omega^2 L^2}\right)$$

$$\text{At resonance, } \omega_0 C - \frac{\omega_0 L}{r_L^2 + \omega_0^2 L^2} = 0$$

$$\text{Which leads } C = \frac{L}{r_L^2 + \omega_0^2 L^2} = \frac{0.1}{25 + (2\pi \cdot 60)^2 \cdot 0.1^2} = 7 \times 10^{-5} \text{ F}$$

$$\frac{L}{r_L^2 + \omega_0^2 L^2} = C$$

$$L = Cr_L^2 + \omega_0^2 L^2 C$$

----- Blank Page -----

c)

$$\frac{V_L(j\omega)}{V_{in}(j\omega)} = \frac{R_L}{Z_{filter} + R_L} = \frac{Y R_L}{1 + Y R_L}$$

~~2~~ 3
When  $\omega = 2\pi 1000$ ,

$$Y = \frac{5}{25 + (2\pi 1000)^2 0.1^2} + j \left( 0.14\pi - \frac{2\pi 1000 \times 0.1}{25 + (2\pi 1000)^2 0.1^2} \right) \approx 0.14\pi j \text{ or } 0.44j$$

Then

$$\frac{V_L(2\pi 1000)}{V_{in}(2\pi 1000)} = \frac{j132}{1 + j132}$$

2

When  $\omega = 2\pi 60$ ,

$$Y = \frac{5}{25 + (2\pi 60)^2 0.1^2} = 3.45 \times 10^{-3}$$

Then

$$\frac{V_L(2\pi 1000)}{V_{in}(2\pi 1000)} = \frac{3.45 \times 10^{-3} \times 300}{1 + 3.45 \times 10^{-3} \times 30} = 0.51.$$

2

$$15 = 3 + 5 + 3 + 2 + 2$$

**Problem 4 (33 points) – Second-order circuit analysis**

You must show your work to get full credit.

For the circuit in Fig. 4,

- Find the  $t$ -domain differential equations for  $t > 0$  and solve for  $v(t)$  in time domain.
- Construct the  $s$ -domain equivalent circuit for  $t > 0$ , then find  $v(t)$  in  $s$ -domain.


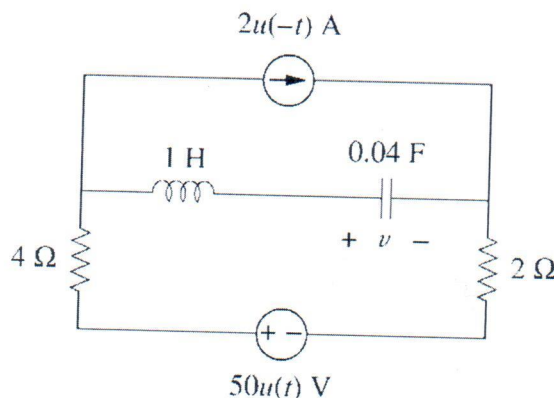


Fig. 4

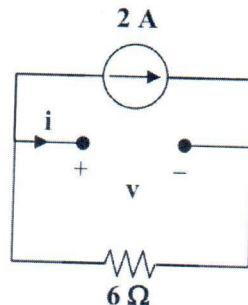**Your answer:**

- For  $t = 0^-$ , the equivalent circuit is shown below.



$$i(0^-) = 0, v(0^-) = -2 \times 6 = -12V \quad \leftarrow (2)$$

For  $t > 0$ , we have a series RLC circuit with a step input.

$$\alpha = \frac{R}{2L} = \frac{6}{2} = 3, \quad \omega_0 = \frac{1}{\sqrt{RC}} = \frac{1}{\sqrt{0.04}}, \quad s = -3 \pm \sqrt{9 - 25} = -3 \pm j4 \quad \leftarrow (3)$$

$$\text{Thus, } v(t) = V_\infty + [(A \cos 4t + B \sin 4t)e^{-3t}] \quad \leftarrow (2)$$

$$\text{where } V_\infty = 50V \quad \leftarrow (1)$$

$$v(t) = 50 + [(A \cos 4t + B \sin 4t)e^{-3t}]$$

$$v(0) = -12 = 50 + A \quad \text{which gives } A = -62. \quad \leftarrow (2)$$

$$i(0) = 0 = C \frac{dv}{dt} \Big|_{t=0}$$

$$\frac{dv}{dt} \Big|_{t=0} = [-3(A \cos 4t + B \sin 4t)e^{-3t}] + [4(-A \sin 4t + B \cos 4t)e^{-3t}] \Big|_{t=0} = -3A + 4B = 0 \quad \leftarrow (4)$$


$$\text{Thus } B = -46.5$$

$$v(t) = \{50 + [(-62 \cos 4t - 46.5 \sin 4t)e^{-3t}]\}V \quad \leftarrow (2)$$

$$2 + 3 + 2 + 1 + 2 + 4 + 2 = 16^{8/12}$$

## Blank Page

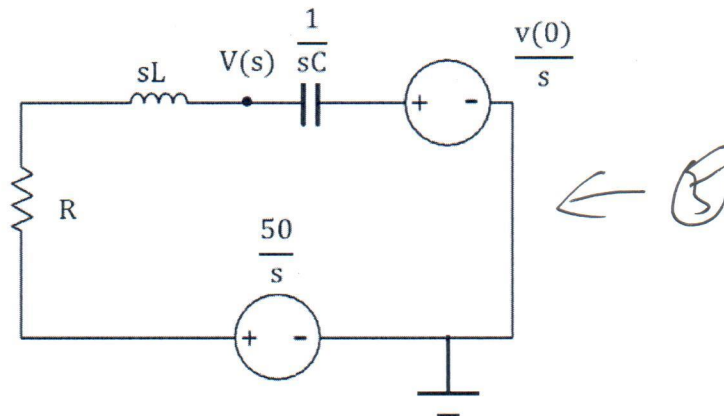b) In s-domain the equivalent circuit is shown below.



where  $R = 6\Omega$ ,  $L = 1H$ ,  $C = 0.04F$

$$V(s) = \frac{v(0)}{s} + \frac{\frac{1}{sC}}{R + sL + \frac{1}{sC}} \left[ \frac{50}{s} - \frac{v(0)}{s} \right] = -\frac{12}{s} + \frac{1550}{(s^2 + 6s + 25)s}$$

(3)

Let  $\frac{1}{(s^2 + 6s + 25)s} = F(s)$ , so let

$$F(s) = \frac{A}{s} + \frac{B(s+3) + C}{(s+3)^2 + 4^2} = \frac{(A+C)s^2 + (3A+B+6C)s + 25C}{(s^2 + 6s + 25)s} = \frac{1}{(s^2 + 6s + 25)s}$$

So

$$\begin{cases} A + C = 0 \\ 3A + B + 6C = 0 \\ 25C = 1 \end{cases} \rightarrow \begin{cases} A = -\frac{1}{25} \\ B = -\frac{3}{25} \\ C = \frac{1}{25} \end{cases} \quad 2 \times 3 = 6$$

So

$$V(s) = -62 \frac{(s+3) + 3}{(s+3)^2 + 4^2} + \frac{50}{s}$$

(3)

$$v(t) = \left[ -62 \left( e^{-3t} \cos 4t + \frac{3}{4} e^{-3t} \sin 4t \right) + 50u(t) \right] V$$

$$5 + 3 + 6 + 3 = 17$$

$$16 + 17 = 33$$

**Problem 5 (26 points) – Fourier series**

You must show your work to get full credit.

The transfer function for the narrowband band-pass filter circuit in Fig. 5(a) is

$$H(s) = \frac{-K_0 \beta s}{s^2 + \beta s + \omega_0^2}$$

- a) Find  $K_0$ ,  $\beta$  and  $\omega_0^2$  as functions of the circuit parameters  $R_1, R_2, R_3, C_1$  and  $C_2$ .
- b) Write the first three terms in the Fourier series that represents  $v_o$  if  $v_g$  is the periodic voltage in Fig. 5(b).

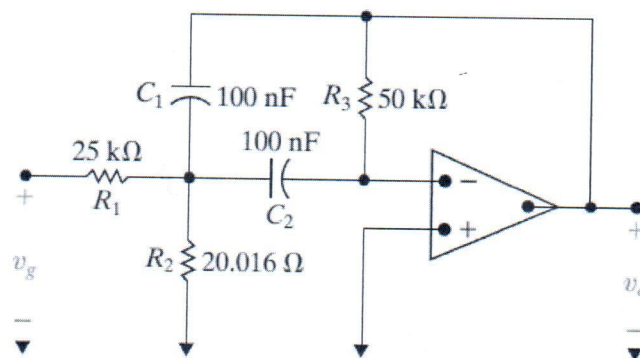


Fig. 5(a)

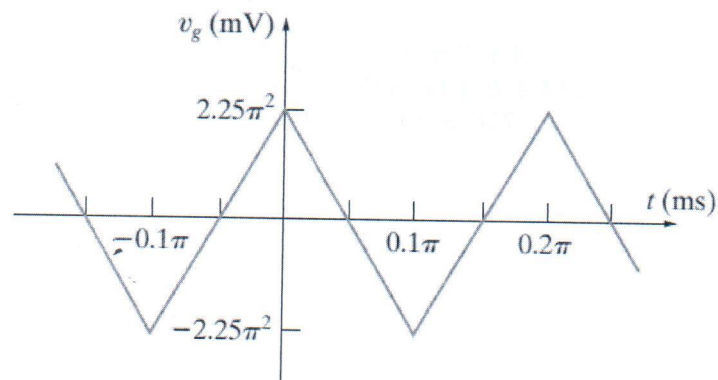


Fig. 5(b)

**Your answer:**

Let  $V_a$  represent the node voltage across  $R_2$ , then the node-voltage equations are

$$\frac{V_a - V_g}{R_1} + \frac{V_a}{R_2} + V_a s C_2 + (V_a - V_o) s C_1 = 0 \leftarrow \text{②}$$



## Blank Page

$$(0 - V_o)sC_2 + \frac{0 - V_o}{R_3} = 0 \quad \leftarrow \text{①}$$

Solving for  $V_o$  in terms of  $V_g$  yields

$$\frac{V_o}{V_g} = H(s) = \frac{\frac{-1}{R_1 C_1} s}{s^2 + \frac{1}{R_3} \left( \frac{1}{C_1} + \frac{1}{C_2} \right) s + \frac{R_1 + R_2}{R_1 R_2 R_3 C_1 C_2}}$$

It follows that

$$\omega_o^2 = \frac{R_1 + R_2}{R_1 R_2 R_3 C_1 C_2} \quad \leftarrow \text{②}$$

$$\beta = \frac{1}{R_3} \left( \frac{1}{C_1} + \frac{1}{C_2} \right) \quad \leftarrow \text{③}$$

$$K_o = \frac{R_3}{R_1} \left( \frac{C_2}{C_1 + C_2} \right) \quad \leftarrow \text{④}$$

Note that

$$H(s) = \frac{-\frac{R_3}{R_1} \left( \frac{C_2}{C_1 + C_2} \right) \frac{1}{R_3} \left( \frac{1}{C_1} + \frac{1}{C_2} \right) s}{s^2 + \frac{1}{R_3} \left( \frac{1}{C_1} + \frac{1}{C_2} \right) s + \left( \frac{R_1 + R_2}{R_1 R_2 R_3 C_1 C_2} \right)}$$

$$H_5 = \frac{-j5}{-600 + j5} = 0.0083/90.48^\circ$$

$$v_o = -18 \cos \omega_o t + 0.03 \cos(3\omega_o t + 90.86^\circ) \quad \leftarrow \text{⑤}$$

$$+ 0.006 \cos(5\omega_o t + 90.48^\circ) + \dots \text{ mV}$$

[c] The fundamental frequency component dominates the output, so we expect the quality factor  $Q$  to be quite high.

[d]  $\omega_o = 10^4$  rad/s and  $\beta = 400$  rad/s. Therefore,  $Q = 10,000/400 = 25$ . We expect the output voltage to be dominated by the fundamental frequency component since the bandpass filter is tuned to this frequency!

[b] For the given values of  $R_1, R_2, R_3, C_1$ , and  $C_2$  we have

$$H(s) = \frac{-400s}{s^2 + 400s + 10^8}$$

$$v_g = \frac{(8)(2.25\pi^2)}{\pi^2} \sum_{n=1,3,5,\dots}^{\infty} \frac{1}{n^2} \cos n\omega_o t$$

$$= 18 \left[ \cos \omega_o t + \frac{1}{9} \cos 3\omega_o t + \frac{1}{25} \cos 5\omega_o t + \dots \right] \text{ mV}$$

$$= [18 \cos \omega_o t + 2 \cos 3\omega_o t + 0.72 \cos 5\omega_o t + \dots] \text{ mV}$$

$$\omega_o = \frac{2\pi}{0.2\pi} \times 10^3 = 10^4 \text{ rad/s}$$

$$H(jk10^4) = \frac{-400jk10^4}{10^8 - k^2 10^8 + j400k10^4} = \frac{-jk}{25(1 - k^2) + jk}$$

$$H_1 = -1 = 1/180^\circ \quad \leftarrow \text{①}$$

$$H_3 = \frac{-j3}{-200 + j3} = 0.015/90.86^\circ \quad \leftarrow \text{②}$$

$$H_5 = \frac{-j5}{-600 + j5} = 0.0083/90.48^\circ \quad \leftarrow \text{③}$$

$$v_o = -18 \cos \omega_o t + 0.03 \cos(3\omega_o t + 90.86^\circ)$$

$$\underbrace{2+2+2+2+2}_{10} + \underbrace{8+1+2+2+3}_{16} = 26$$