

**Problem 1 (20 points)**

You must show your detailed work to get full credit.

For the Wheatstone bridge circuit shown in Fig.1, solve the following problems:

- Express  $I_a$ , the reading on the ammeter, as a function of all the circuit elements  $R_1$ ,  $R_2$ ,  $R_3$ ,  $R_x$ ,  $R_a$  and  $V_0$ .
- If  $R_1 = 1\Omega$ ,  $R_2 = 2\Omega$ , and  $R_x = 3\Omega$ , to what value should  $R_3$  be adjusted so as to achieve a balanced condition, that is,  $I_a = 0$ ?
- Further, if  $V_0 = 6V$ ,  $R_a = 0.1\Omega$ , and  $R_x$  were then to deviate by a small amount to  $R_x = 3.01\Omega$ , what would be the reading on the ammeter?


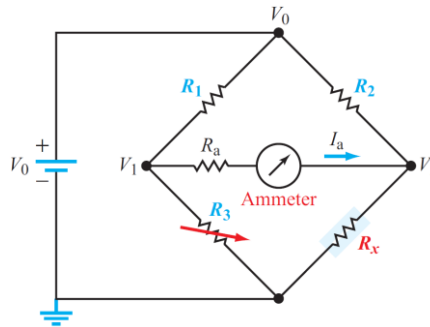


Fig. 1 for Problem 1.

**Solution**

(a)

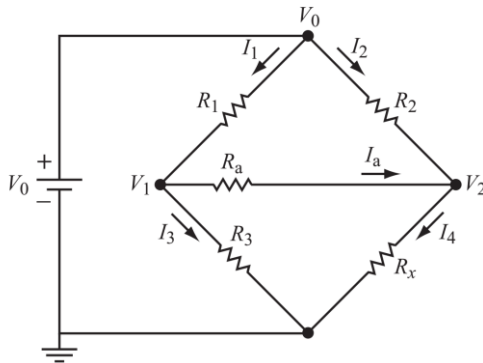

KCL equations at nodes  $V_1$  and  $V_2$  are

$$I_1 = I_3 + I_a$$

$$I_4 = I_2 + I_a$$

KVL for the left loop and outside perimeter loop are

$$-V_0 + I_1 R_1 + I_3 R_3 = 0,$$

$$-V_0 + I_2 R_2 + I_4 R_x = 0.$$

Also, for the upper triangle of the bridge,

$$I_1 R_1 + I_a R_a - I_2 R_2 = 0.$$

Simultaneous solution of the five equations leads to

$$I_a = \frac{(R_3 R_2 - R_x R_1) V_0}{R_2 R_x (R_1 + R_3) + (R_2 + R_x) [R_1 R_3 + R_a (R_1 + R_3)]}.$$

(b)

$$\frac{R_3}{R_1} = \frac{R_x}{R_2}, \quad R_3 = \frac{R_1 R_x}{R_2} = \frac{1 \times 3}{2} = 1.5 \Omega.$$

(c)

For  $R_1 = 1 \Omega$ ,  $R_2 = 2 \Omega$ ,  $R_3 = 1.5 \Omega$ ,  $R_x = 3.01 \Omega$ , and  $V_0 = 6 V$ ,

$$I_a = -2.5 \text{ mA}.$$

**Problem 2 (15 points)**

You must show your detailed work to get full credit.

The circuit shown in Fig. 2 contains a variable load  $R_L$ .

- (a) Choose  $R_s$  so that  $I_L$  never exceeds 4mA, regardless of the value of  $R_L$ .  
 (b) Given that choice, what is the maximum power that  $R_L$  can extract from the circuit?


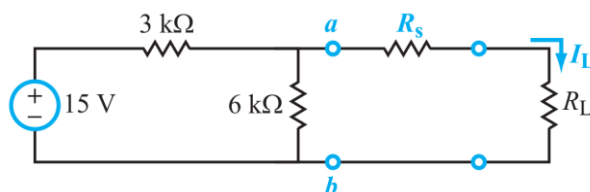


Fig. 2 for Problem 2.

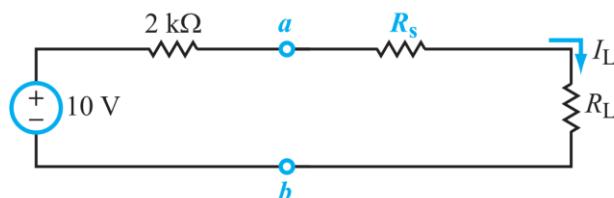**Solution:** We should start by finding the Thévenin equivalent of the circuit to the left of  $(a, b)$ . Simple source-transformation steps lead to:



To satisfy the stated condition, we need to choose  $R_s$  such that  $I_L = 4$  mA when  $R_L = 0$ . That is

$$I_L = 4 \text{ mA} = \frac{10}{2\text{k} + R_s},$$

which leads to  $R_s = 0.5 \text{ k}\Omega$ .

For maximum power transfer by  $R_L$ , it should be equal to:

$$R_L = 2 \text{ k}\Omega + R_s = 2.5 \text{ k}\Omega$$

$$I_L = \frac{10}{5\text{k}} = 2 \text{ mA}$$

$$P_{\max} = I_L^2 R_L = (2 \times 10^{-3})^2 \times 2.5 \times 10^3 = 10 \quad (\text{mW}).$$

**Problem 3 (20 points)**

You must show your detailed work to get full credit.

For the circuit shown in Fig. 3, assume the op amp is ideal. Given  $v_{in} = A u(t)$ ,  $A = 6V$ ,  $R_1 = 10\text{ k}\Omega$ ,  $R_2 = 5\text{ k}\Omega$ ,  $R_f = 50\text{ k}\Omega$ , and  $C_1 = C_2 = 1\text{ }\mu F$ , determine  $v_{out}(t)$  for  $t \geq 0$ .

Hint: There is no energy stored in the two capacitors at time  $t = 0$ .

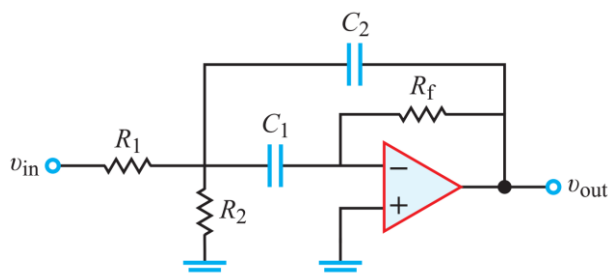


Fig. 3 for Problem 3.

**Solution:** Prior to  $t = 0$ ,  $v_{in}$  was equal to zero. Hence,

$$v_{C_1} = v_{C_1}(0^-) = 0, \quad [\text{short-circuit equivalent}]$$

$$v_{C_2} = v_{C_2}(0^-) = 0. \quad [\text{short-circuit equivalent}]$$

At  $t = 0$  (Fig. (a)):

The capacitors have been replaced with short circuits. Also, the input circuit has been modified by applying source transformation. The new input-circuit parameters are

$$V_s = \frac{AR_2}{R_1 + R_2} = \frac{6 \times 5 \times 10^3}{10 \times 10^3 + 5 \times 10^3} = 2\text{ V},$$


$$R_s = \frac{R_1 R_2}{R_1 + R_2} = \frac{5 \times 10}{5 + 10} = 3.33\text{ k}\Omega.$$

In view of  $i_n = 0$ , if a current is generated by  $V_s$ , it will flow to  $v_{out}$  entirely through the short-circuit branch containing  $C_2$ . Hence,


$$i_{C_1}(0) = 0,$$

which implies that
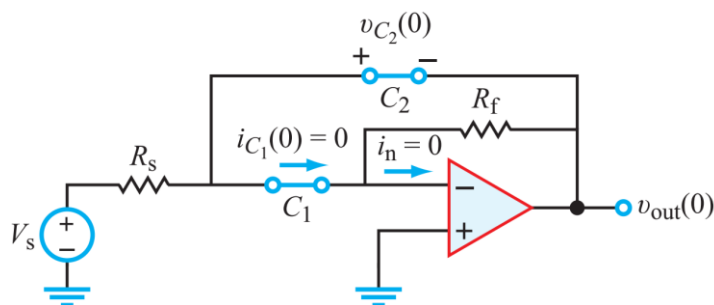
$$v'_{C_1}(0) = \frac{i_{C_1}(0)}{C} = 0.$$



(a) At  $t = 0$

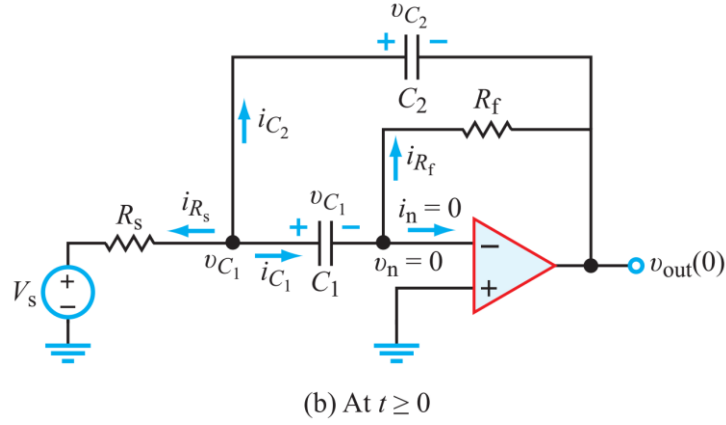

At  $t \geq 0$  (Fig. (b)):

At node  $v_{C_1}$ , KCL gives:

$$i_{R_s} + i_{C_2} + i_{C_1} = 0,$$

or

$$\frac{v_{C_1} - V_s}{R_s} + C_2(v'_{C_1} - v'_{out}) + C_1 v'_{C_1} = 0. \quad (1)$$

At node  $v_n$ :

$$i_{C_1} = i_{R_f},$$

or

$$C_1 v'_{C_1} = -\frac{v_{out}}{R_f}. \quad (2)$$

From (2)

$$v'_{out} = -R_f C_1 v''_{C_1}. \quad (3)$$

Upon using this expression for  $v'_{out}$  in Eq. (1) and rearranging terms, we have

$$v''_{C_1} + a v'_{C_1} + b v_C = c,$$

where

$$a = \frac{C_1 + C_2}{C_1 C_2 R_f} = \frac{2 \times 10^{-6}}{10^{-12} \times 5 \times 10^4} = 40,$$

$$b = \frac{1}{C_1 C_2 R_s R_f} = \frac{1}{10^{-12} \times 3.33 \times 10^3 \times 5 \times 10^4} = 6000,$$

$$c = \frac{V_s}{C_1 C_2 R_s R_f} = 12000.$$

$$\alpha = \frac{a}{2} = 20 \text{ Np/s},$$


$$\omega_0 = \sqrt{b} = \sqrt{6000} = 77.46 \text{ rad/s}.$$

Since  $\alpha < \omega_0$ , the response will be underdamped:

$$v_{C_1}(t) = v_{C_1}(\infty) + [D_1 \cos \omega_d t + D_2 \sin \omega_d t] e^{-\alpha t},$$

with

$$\omega_d = \sqrt{\omega_0^2 - \alpha^2} = \sqrt{6000 - 400} = 74.83 \text{ rad/s}.$$

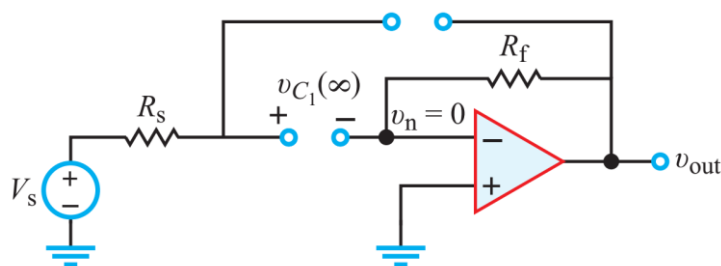(c) At  $t = \infty$ 

At  $t = \infty$  (Fig. (c)), both capacitors behave like open circuits. Consequently, no current flows through the circuit and

$$v_{C_1}(\infty) = V_s = 2 \text{ V}.$$

Given that  $v_{C_1}(0) = 0$ ,  $v'_{C_1}(0) = 0$ , and  $v_{C_1}(\infty) = 2 \text{ V}$ ,

$$D_1 = v_{C_1}(0) - v_{C_1}(\infty) = -2 \text{ V},$$

$$D_2 = \frac{v'_C(0) + \alpha[v_C(0) - v_C(\infty)]}{\omega_d} = \frac{0 + 20[0 - 2]}{74.83} = -0.53 \text{ V}.$$

Hence,

$$v_{C_1}(t) = 2 - [2 \cos 74.83t + 0.53 \sin 74.83t]e^{-20t} \quad (\text{V}).$$

Returning to Eq. (2),

$$\begin{aligned} v_{\text{out}} &= -R_f C_1 v'_{C_1} \\ &= -5 \times 10^4 \times 10^{-6} v'_{C_1} \\ &= -5 \times 10^{-2} \{ [2 \times 74.83 \sin 74.83t - 0.53 \times 74.83 \cos 74.83t] e^{-20t} \\ &\quad + 20[2 \cos 74.83t + 0.53 \sin 74.83t] e^{-20t} \} \\ &= -8e^{-20t} \sin 74.83t \quad (\text{V}). \end{aligned}$$

**Problem 4 (15 points)**

You must show your detailed work to get full credit.

Determine the amount of average power delivered to  $R_L$  in the circuit shown in Fig. 4. Assume that the op amp is ideal and  $v_{in}(t) = 0.5 \cos 2000t$  V,  $R_1 = 1 \text{ k}\Omega$ ,  $R_2 = 10 \text{ k}\Omega$ ,  $C = 0.1 \text{ }\mu\text{F}$ ,  $R_L = 1 \text{ k}\Omega$  and  $L = 0.2 \text{ H}$ .


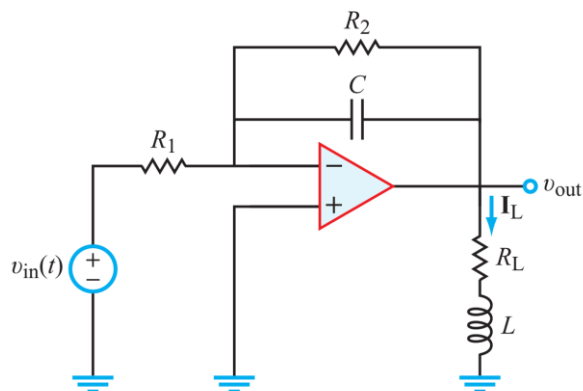


Fig. 4 for Problem 4.

**Solution:**

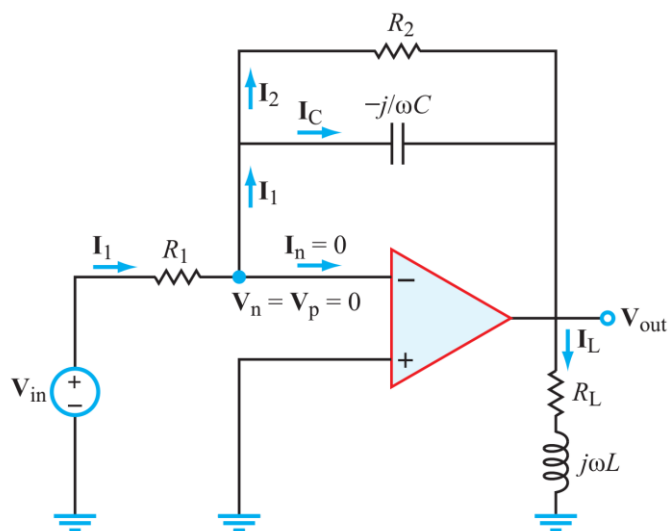

$$\mathbf{V}_{in} = 0.5 \angle 0^\circ \text{ V.}$$

Since  $\mathbf{V}_n = 0$ ,

$$\mathbf{I}_1 = \frac{\mathbf{V}_{in}}{R_1}.$$

Also,

$$\begin{aligned} \mathbf{I}_1 &= \mathbf{I}_2 + \mathbf{I}_C \\ &= \frac{\mathbf{V}_n - \mathbf{V}_{out}}{R_2} + \frac{\mathbf{V}_n - \mathbf{V}_{out}}{-j/\omega C} \\ &= -\mathbf{V}_{out} \left( \frac{1}{R_2} + j\omega C \right). \end{aligned}$$

Hence,

$$\begin{aligned}\mathbf{V}_{\text{out}} &= -\left(\frac{R_2}{R_1}\right) \left(\frac{1}{1+j\omega R_2 C}\right) \mathbf{V}_{\text{in}} \\ &= -\left(\frac{R_2}{R_1}\right) \frac{1-j\omega R_2 C}{1+\omega^2 R_2^2 C^2} \mathbf{V}_{\text{in}}.\end{aligned}$$

For  $\mathbf{V}_{\text{in}} = 0.5 \text{ V}$ ,  $R_1 = 1 \text{ k}\Omega$ ,  $R_2 = 10 \text{ k}\Omega$ ,  $\omega = 2000 \text{ rad/s}$ , and  $C = 0.1 \text{ }\mu\text{F}$ ,

$$\begin{aligned}\mathbf{V}_{\text{out}} &= -(1-j2) \\ &= 2.24e^{j116.6^\circ} \text{ V}.\end{aligned}$$

$$\begin{aligned}\mathbf{I}_L &= \frac{1}{R_L + j\omega L} \mathbf{V}_{\text{out}} \\ &= \frac{1}{10^3 + j400} \times 2.24e^{j116.6^\circ} = 2.08e^{j94.8^\circ} \quad (\text{mA}).\end{aligned}$$

Power delivered to  $R_L$  alone is:

$$P_{\text{av}} = \frac{1}{2} |\mathbf{I}_L|^2 R_L = \frac{1}{2} \times (2.08)^2 \times 10^{-6} \times 10^3 = 2.16 \text{ mW}.$$

**Problem 5 (15 points)**

You must show your detailed work to get full credit.

For the circuit shown in Fig. 5,

- Find the steady-state expressions for the currents  $i_g$  and  $i_L$  when  $v_g = 168 \cos 800t$  V.
- Find the coefficient of coupling  $k = \frac{M}{\sqrt{L_1 L_2}}$ .
- Find the total energy stored in the magnetically coupled coils at time  $t = 1250\pi \mu\text{s}$ .

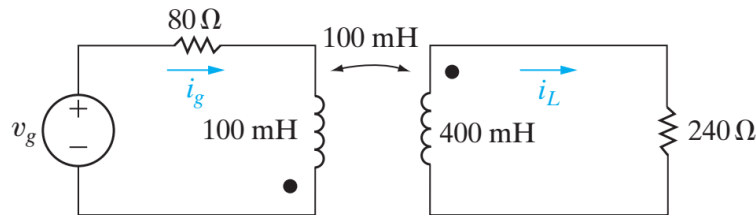



Fig. 5 for Problem 5.

**Solution**

$$[a] \quad j\omega L_1 = j(800)(100 \times 10^{-3}) = j80 \Omega$$

$$j\omega L_2 = j(800)(400 \times 10^{-3}) = j320 \Omega$$

$$j\omega M = j80 \Omega$$

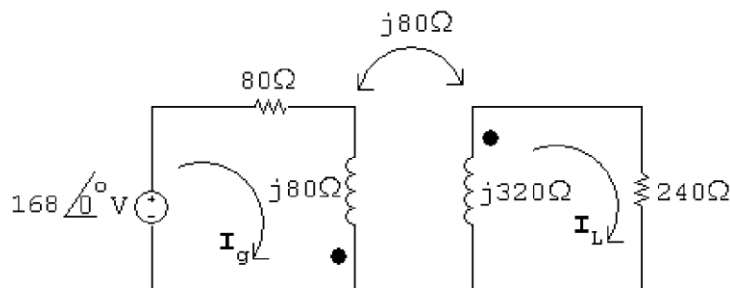

$$168 = (80 + j80)\mathbf{I}_g + j80\mathbf{I}_L$$

$$0 = j80\mathbf{I}_g + (240 + j320)\mathbf{I}_L$$

Solving,

$$\mathbf{I}_g = 1.2 - j0.9 \text{ A}; \quad \mathbf{I}_L = -0.3 \text{ A}$$

$$i_g = 1.5 \cos(800t - 36.87^\circ) \text{ A}$$

$$i_L = 0.3 \cos(800t - 180^\circ) \text{ A}$$



$$[\mathbf{b}] \quad k = \frac{M}{\sqrt{L_1 L_2}} = \frac{0.1}{\sqrt{(0.1)(0.4)}} = 0.5$$

**[c]**

When  $t = 1250\pi \mu\text{s}$ ,

$$800t = \pi \text{ rad} = 180^\circ$$

$$i_g(1250\pi \mu\text{s}) = 1.5 \cos(180 - 36.87) = -1.2 \text{ A}$$

$$i_L(1250\pi \mu\text{s}) = 0.3 \cos(180 - 180) = 0.3 \text{ A}$$

$$w = \frac{1}{2}(100 \times 10^{-3})(1.44) + \frac{1}{2}(400 \times 10^{-3})(0.09)$$

$$+ 100 \times 10^{-3}(-1.2)(0.3) = 54 \text{ mJ}$$

**Problem 6 (15 points)**

You must show your detailed work to get full credit.

For the series RLC circuit of Fig. 6,  $R = 5 \Omega$ ,  $L = 20 \text{ mH}$ ,  $C = 0.5 \mu\text{F}$ .

- Obtain an expression for the transfer function  $H(\omega) = V_R/V_s$ .
- What are the values of the resonant frequency  $\omega_0$  and quality factor  $Q$ ?
- What are the values of half-power frequencies  $\omega_{c1}$  and  $\omega_{c2}$ ?
- Is it possible to double the magnitude of  $Q$  by changing the values of  $L$  and/or  $C$ , while keeping  $\omega_0$  and  $R$  unchanged? If yes, propose such values, and if no, explain why.

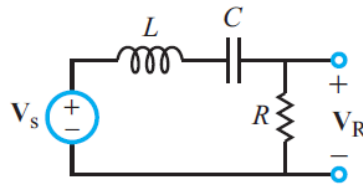


Fig. 6 for Problem 6.

**Solution:**

(a)

$$\frac{V_R}{V_s} = \frac{RI}{V_s} = \frac{j\omega RC}{(1 - \omega^2 LC) + j\omega RC}$$

(b)

$$\omega_0 = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{20 \times 10^{-3} \times 0.5 \times 10^{-6}}} = 10^4 \text{ rad/s},$$

$$Q = \frac{\omega_0 L}{R} = \frac{10^4 \times 20 \times 10^{-3}}{5} = 40,$$

(c) Approximately

$$\omega_{c1} = \omega_0 - \frac{B}{2} = 10^4 - \frac{250}{2} = 9875 \text{ rad/s},$$

$$\omega_{c2} = \omega_0 + \frac{B}{2} = 10^4 + \frac{250}{2} = 10125 \text{ rad/s}.$$

(d)

$$Q = \frac{\omega_0 L}{R} \implies \frac{\omega_0}{R} = \frac{Q}{L}.$$

Since  $\omega_0$  and  $R$  are constants, doubling  $Q$  requires that  $L$  be doubled, but to keep  $\omega_0$  constant would require  $C$  to be reduced to one half. Thus, the new set of element values are:

$$R = 5 \Omega, \quad L = 40 \text{ mH}, \quad \text{and } C = 0.25 \mu\text{F}.$$

The corresponding values of  $\omega_0$  and  $Q$  are:

$$\omega_0 = 10^4 \text{ rad/s (unchanged)}$$

$$Q = \frac{\omega_0 L}{R} = 80.$$