

## **Homework 5**

Due date: Apr. 28<sup>th</sup>, 2021, Wednesday

Turn in your homework in class

Rules:

- Work on your own. Discussion is permissible, but extremely similar submissions will be judged as plagiarism.
- Please show all intermediate steps: a correct solution without an explanation will get zero credit.
- Please submit on time. No late submission will be accepted.
- Please prepare your submission in English only. No Chinese submission will be accepted.


1. Find the following results (using phasors if necessary)

(1)  $\frac{(50-j60)(20\angle 70^\circ + 150\angle -30^\circ)}{(70-j120)90\angle 210^\circ}$ ;

(2) Solve the equation:  $\frac{dv(t)}{dt} + 4v(t) + 3 \int v(t) dt = 20\sin(10t + 20^\circ)$
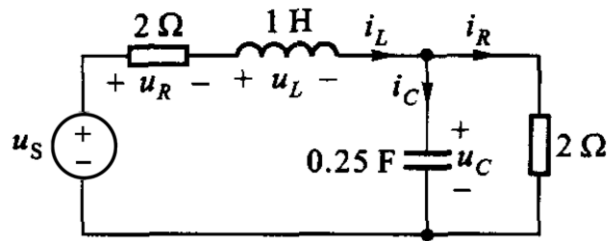
## 2. Phasor Diagrams

Find  $u_s(t)$  in the circuit below, assuming that  $u_c(t) = \sqrt{2}\cos 2t$  V. Sketch Phasors of  $u_s$ ,  $u_R$ ,  $u_L$ ,  $i_L$ ,  $i_C$ ,  $u_C$ ,  $i_R$  in one single phasor diagram.



3. Given that the voltage and current of a two-terminal element adopt the passive sign convention, its instantaneous value is expressed as:

(1)  $u(t) = 15\cos(400t + 30^\circ) \text{ V}$ ,  $i(t) = 3\sin(400t + 30^\circ) \text{ A}$ ;

(2)  $u(t) = 8\sin(500t + 50^\circ) \text{ V}$ ,  $i(t) = 2\sin(500t + 140^\circ) \text{ A}$ ;

(3)  $u(t) = 8\cos(250t + 60^\circ) \text{ V}$ ,  $i(t) = 5\sin(250t + 150^\circ) \text{ A}$ ;


Try to determine whether the element is a resistor, inductor or capacitor, and determine its value ( $R=?$ ,  $C=?$ ,  $L=?$ ).

**4. nodal analysis & mesh analysis**

Find  $\dot{U}_2$  and  $\dot{I}_2$  for the circuit below, assuming that  $\dot{U}_s = 10 \angle 0^\circ \text{ V}$ ,  $\mu = 0.5$ .


(1) Use nodal analysis;

(2) Use mesh analysis.

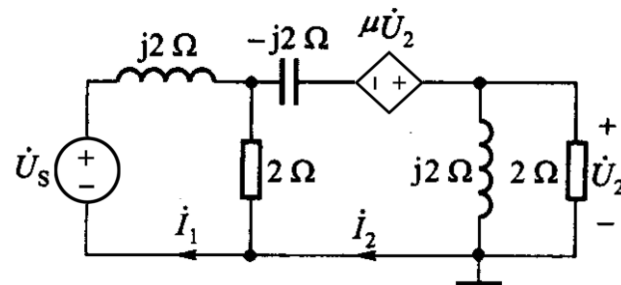


**5. Find the equivalent impedance.**

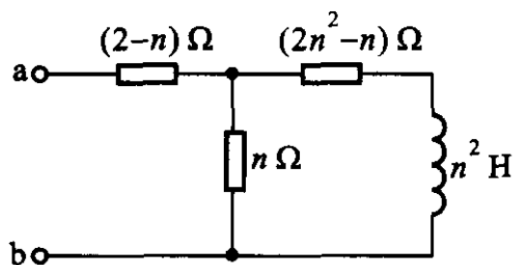(1) Find  $\mathbf{Z}_{ab}$  when the system is operating at the angular frequency  $\omega$ , assuming that  $n \neq 0$ .




(2) Find  $\mathbf{Z}_{ab}$ .

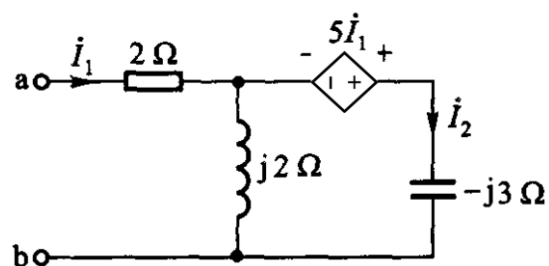

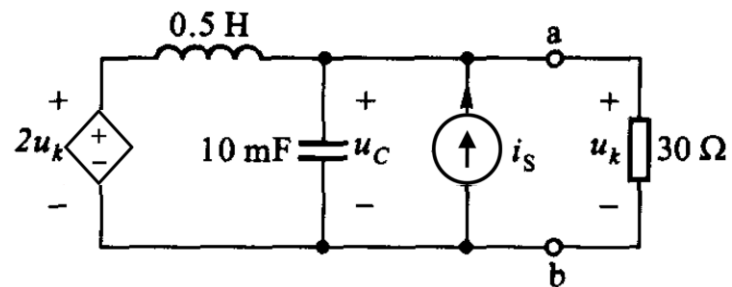
**6. Thevenin equivalent.**

Given that the circuit below is in steady state, use phasor method to find  $\mathbf{u_k(t)}$  in the circuit below by using Thevenin's theorem, assuming that  $i_s(t) = 30\sqrt{2}\cos 20t$  A. (Hint: find the Thevenin equivalent circuit of the left hand side part seen from the terminals a-b)


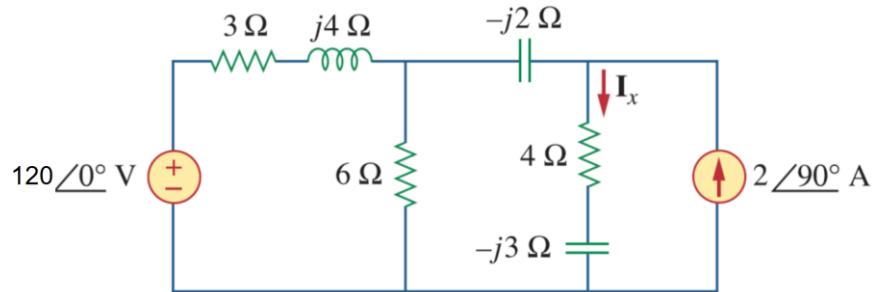
## 7. Source Transformation

The two sources are with the same angular frequency. Use source transformation to find  $\mathbf{I}_x$ .





### 8. Superposition Theorem

Using superposition to find  $i_L(t)$ , assuming that  $i_s(t) = 10\sqrt{2}\cos 100t$  A,  
 $u_s(t) = 100\sqrt{2}\cos 1000t$  V.

