

Homework 5

Due date: Nov. 25th, 2021

Turn in your homework in class

Rules:

- Work on your own. Discussion is permissible, but extremely similar submissions will be judged as plagiarism.
- Please show all intermediate steps: a correct solution without an explanation will get zero credit.
- Please submit on time. No late submission will be accepted.
- Please prepare your submission in English only. No Chinese submission will be accepted.
- If needed, round the number to the nearest hundredths, i.e., rounding it to 2 decimal places.

1. (a) For the following pairs of sinusoids, determine which one leads and by how much.

(a) $v(t) = 10 \cos(4t - 60^\circ)$ and
 $i(t) = 4 \sin(4t + 50^\circ)$

(b) $v_1(t) = 4 \cos(377t + 10^\circ)$ and
 $v_2(t) = -20 \cos 377t$

(c) $x(t) = 13 \cos 2t + 5 \sin 2t$ and
 $y(t) = 15 \cos(2t - 11.8^\circ)$

- (b) Transform the following sinusoids into phasors:

(a) $-20 \cos(4t + 135^\circ)$ (b) $8 \sin(20t + 30^\circ)$

(c) $20 \cos(2t) + 15 \sin(2t)$

a)

(a) $i(t) = 40 \cos(4t - 40^\circ)$ $i(t)$ leads $v(t)$ 20°

(b) $v_2(t) = 20 \cos(377t + 180^\circ)$

v_2 leads v_1 170°

(c) $x(t) = 13.928 \cos(2t - 21.04^\circ)$ $y(t)$ leads $x(t)$ 9.4°
 $= 13.928 \cos(2t - 21.04^\circ)$

b)

(a) $20 \angle -45^\circ$ $\omega = 4 \text{ rad/s}$ (b) $8 \angle -60^\circ$ $\omega = 20 \text{ rad/s}$

(c) $25 \cos(2t - 36.87^\circ) = 25 \angle -36.87^\circ$ $\omega = 2 \text{ rad/s}$


2. For the circuit below:

1) Calculate the equivalent impedance Z_{ab} ;

2) If $\bar{V}_{ab} = 20 \sin(5t + 105^\circ)$,

i. Calculate current through the 10Ω resistor, and indicate the reference direction in the circuit diagram;

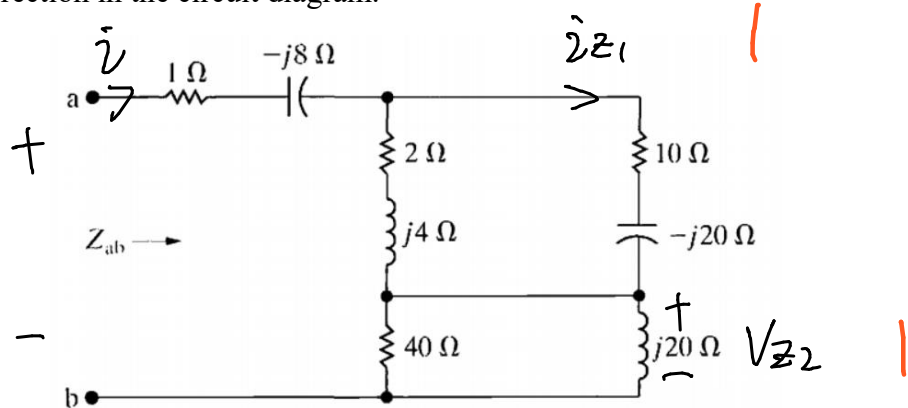ii. Calculate voltage over the $j20 \Omega$ inductor and indicate the reference direction in the circuit diagram.



$$1) Z_{ab} = 1 - j8 + (2 + j4) \parallel (10 - j20) + (40) \parallel (j20)$$

$$= 1 - j8 + 3 + j4 + 8 + j16 = 12 + j12 \Omega$$

$$2) V_{ab} = 20 \angle 15^\circ V$$

The current through the source is

$$\bar{i} = \frac{V_{ab}}{Z_{ab}} = 1.17 \angle -30^\circ A$$

$$= 1.02 - j0.59 A$$

$$i(t) = 1.17 \cos(5t - 30^\circ) A$$

Voltage over $(10 - j20) \Omega$ is $V_{z1} = \bar{i} \cdot (3 + j4) = 5.89 \angle 23.13^\circ V = (5.41 + j2.31) V$

$$\bar{i}_{z1} = \frac{V_{z1}}{10 - j20} = (0.02 + j0.26) A = 0.26 \angle 86.57^\circ A$$

$$3) V_{z2} = \bar{i} \cdot (8 + j16) = 17.59 + j11.62 V$$


$$= 21.08 \angle 33.43^\circ V$$

$$V(t) = 21.08 \cos(5t + 33.43^\circ) V$$

3. For the circuit below, given $\omega = 2 \text{ rad/s}$

1) Use nodal analysis to find $I_x(t)$, $V(t)$

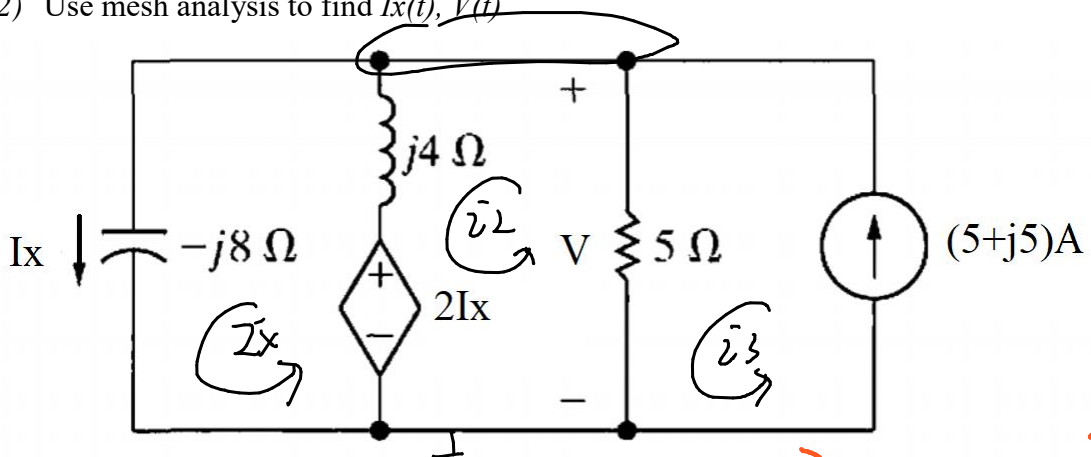2) Use mesh analysis to find $I_x(t)$, $V(t)$



$$1) \text{ KCL: } \begin{cases} 5+j5 = I_x + \frac{V-2I_x}{4j} + \frac{V}{5} \\ I_x = \frac{V}{-8j} \end{cases} \Rightarrow \begin{cases} I_x = -4.75 + 0.23j \text{ A} \\ = 4.76 \angle 177.27^\circ \text{ A} \\ V = 1.81 + 38.01j \text{ V} \\ = 38.05 \angle 87.27^\circ \text{ V} \end{cases}$$

2) KVL:



$$\begin{cases} I_x \cdot (-8j) - 2I_x + 4j \cdot (I_x - \hat{i}_2) = 0 \\ 4j \cdot (\hat{i}_2 - I_x) + 2I_x + 5 \cdot (\hat{i}_2 - \hat{i}_3) = 0 \\ \hat{i}_3 = 5 + 5j \text{ A} \end{cases} \Rightarrow \begin{cases} I_x = -4.75 + 0.23j \text{ A} \\ = 4.76 \angle 177.27^\circ \text{ A} \\ V = 1.81 + 38.01j \text{ V} \\ = 38.05 \angle 87.27^\circ \text{ V} \end{cases}$$

$$I(t) = 4.76 \cos(2t + 177.27^\circ) \text{ A}$$

$$V(t) = 38.05 \cos(2t + 87.27^\circ) \text{ V}$$

14

4. For the circuit below:

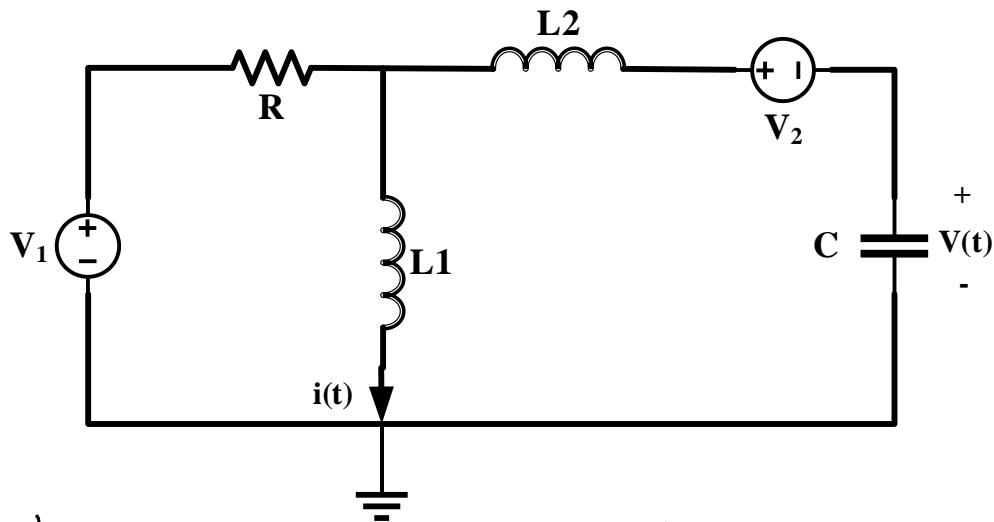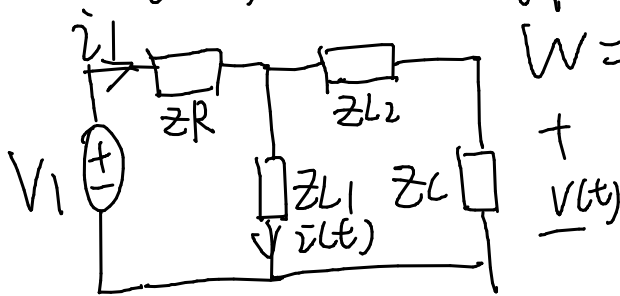 $R=10\Omega$, $L1=10\text{mH}$, $L2=20\text{mH}$, $C=200\text{nF}$, $V_1(t) = 10\sin(5t + 30^\circ)$, $V_2(t) = 4\cos(5t)$ Use superposition theorem to solve the $i(t)$ and $V(t)$ Only V_1 : $V_1 = 10\angle -60^\circ \text{ V}$ $\omega = 5$ 

$$Z_{eq} = 10 + (j \cdot 5 \cdot 0.01) \parallel \left(\frac{1}{j \cdot 200 \cdot 10^{-9} \cdot 5} + j \cdot 5 \cdot 0.02 \right)$$

$$= 10 + 0.05j \quad 2$$

$$\hat{i}_1 = \frac{V_1}{Z_{eq}} = 0.50 - 0.87j \text{ A} = 1.00\angle -60.29^\circ \text{ A}$$

$$V_{ZL1} = 0.05j \cdot \hat{i}_1(t) = 0.04 + 0.02j \text{ V} = 0.05\angle 29.72^\circ \text{ V}$$

$$\hat{v} = \frac{V_{ZL1}}{Z_{L1}} = 0.05 - 0.87j \text{ A} = 1.00\angle -60.29^\circ \text{ A} \quad 2$$


$$V = \frac{V_{ZL1} \cdot Z_C}{Z_C + Z_{L2}} = 0.04 + 0.02j \text{ V} = 0.05\angle 29.72^\circ \text{ V} \quad 2$$

4. For the circuit below:


$$R=10\Omega, L1=10\text{mH}, L2=20\text{mH}, C=200\text{nF},$$

$$V_1(t) = 10\sin(5t + 30^\circ), \quad V_2(t) = 4\cos(5t)$$

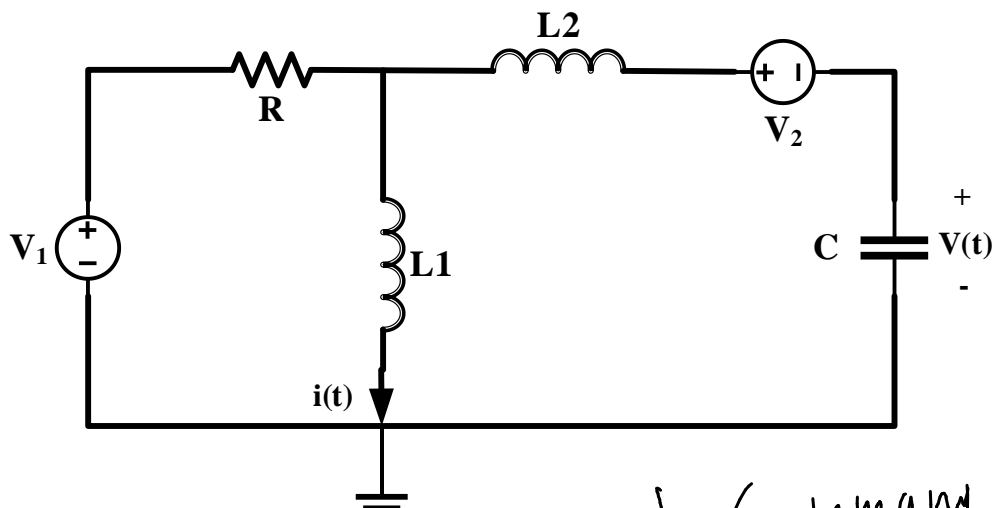Use superposition theorem to solve the $i(t)$ and $V(t)$



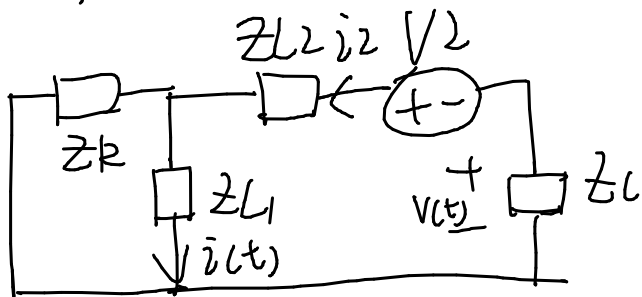Only V_2 $V_2(t) = 4\angle 0^\circ \text{ V}$



$$Z_{eq} = 10 \parallel 0.05j + 0.1j - 10^6j$$

$$= 2.5 \times 10^{-9} - 10^6j \Omega$$

$$\bar{i}_2 = \frac{V_2}{Z_{eq}} = 10^{-15} + 4 \times 10^{-6}j \text{ A}$$

$$V(t) = -\bar{i}_2 \cdot Z_C = -4 + 10^{-9}j \text{ V}$$

$$V_{ZL1} = \bar{i}_2 \cdot (10 \parallel 0.05j)$$

$$= -2 \times 10^{-7} + 10^9j \text{ V}$$

$$\bar{i}(t) = \frac{V_{ZL1}}{Z_{L1}} = 2 \times 10^{-8} + 4 \times 10^{-6}j \text{ A}$$

In Summary

$$\bar{i} = \bar{i}_1 + \bar{i}_2$$

$$= 0.496 - 0.869j \text{ A}$$

$$V = V_1 + V_2$$


$$= -3.96 + 0.02j \text{ V}$$

$$\bar{i}(t) = \cos(5t - 60.286^\circ) \text{ A}$$


$$V(t) = 3.96 \cos(5t + 179.71^\circ) \text{ V}$$

5. Find $i_o(t)$ by using superposition method.

18

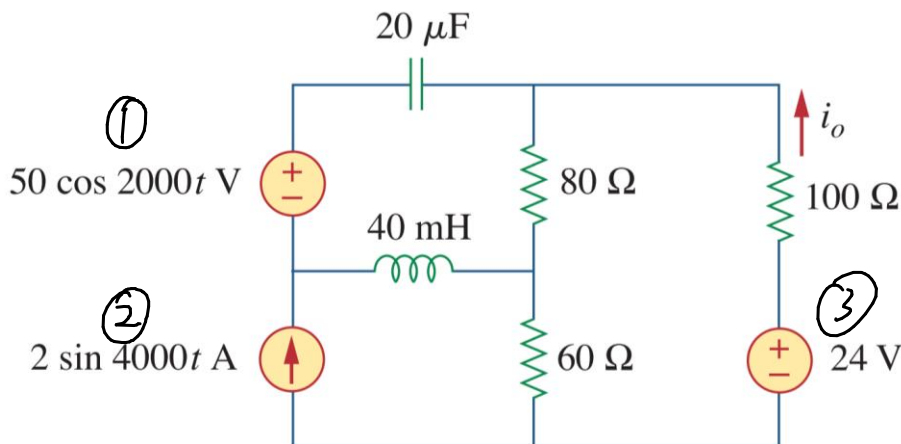

Only ①:

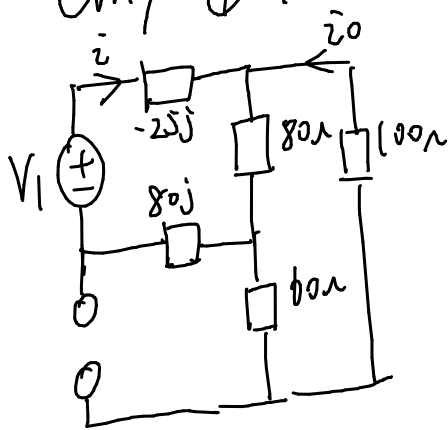

$$Z_C = \frac{1}{j \cdot 2000 \cdot 20 \times 10^{-6}} = -25j \, \Omega$$


$$Z_L = j \cdot 0.04 \cdot 2000 = 80j \, \Omega$$

$$Z_{eq} = -25j + 80j + 80 \parallel 160 = 55j + \frac{160}{3} \, \Omega$$

$$\bar{i} = \frac{V_1}{Z_{eq}} = 0.45 - 0.47j \, A = 0.65 \angle -45.88^\circ \, A$$

$$\bar{i}_o = -\frac{1}{3} \cdot \bar{i} = -0.15 + 0.16j \, A = 0.22 \angle 134.12^\circ \, A$$

Only ②:

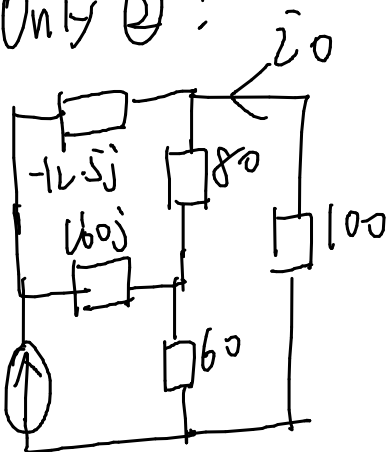

$$Z_C = \frac{1}{j \cdot 20 \times 10^{-6} \cdot 4000} = -12.5j \, \Omega$$


$$Z_L = j \cdot 0.04 \cdot 4000 = 160j \, \Omega$$

$Y \rightarrow D$ Transform: **ORKCL KVL**


$$Z_1 = \frac{160j \cdot 80 + 80 \cdot 60 + 60 \cdot 160j}{60} = 80 + \frac{1120}{3}j \, \Omega$$

$$Z_2 = \frac{4800 + 22400j}{160j} = 140 - 30j \, \Omega$$
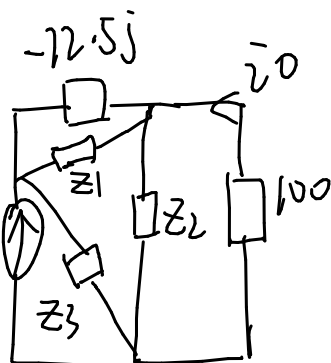
$$Z_3 = \frac{6/8 \cdot 4800 + 22400j}{80} = 60 + 280j \, \Omega$$



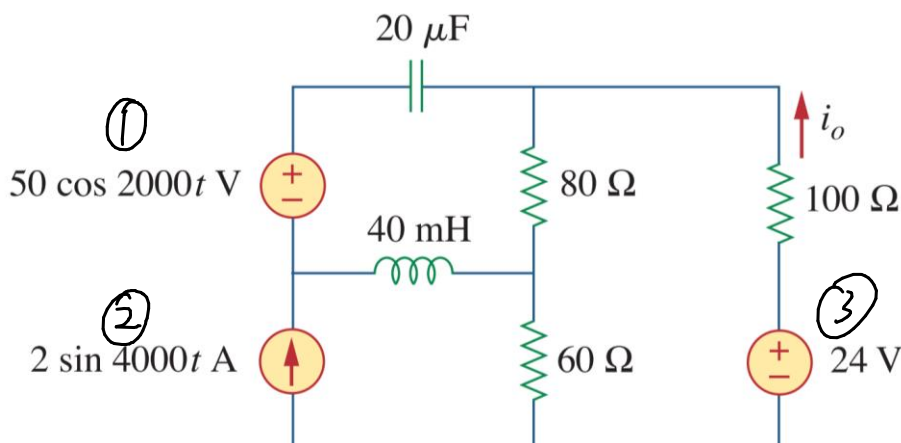5. Find $i_o(t)$ by using superposition method.



$\Upsilon \rightarrow \mathcal{D}$ Transform:

$$Z_1 = 80 + \frac{11\omega}{3} j \Omega \quad Z_2 = 140 - 30j \Omega \quad Z_3 = 60 + 280j \Omega$$

Source Transformation: $V_2 = Z_3 \cdot \hat{i}_2 = 560 - 120j \text{ V}$

$$Z_{eq} = Z_3 + Z_1 // (-12.5j) + Z_2 // 100 = 106.06 + 274.78j \Omega$$

$$\hat{i} = \frac{V_2}{Z_{eq}} = 0.30 - 1.92j \text{ A}$$


$$V_{Z_2} = (Z_2 // 100) \cdot \hat{i} = 8.11 - 114.82j \text{ V}$$

$$\hat{i}_o = -\frac{V_{Z_2}}{100} = -0.08 + 1.15j \text{ A} = 1.15 \angle 94.04^\circ \text{ A}$$

Only ③

In Steady state:

$$\hat{i}_o = 0.1 \text{ A}$$

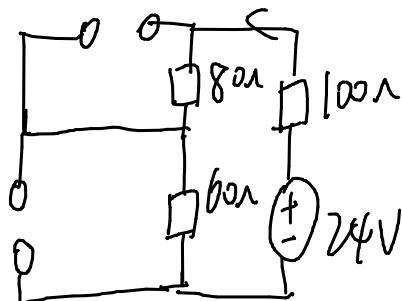


Superposition:

$$i_o(t) = 0.1 + 1.15 \cos(4000t + 94.04^\circ) + 0.22 \cos(2000t + 134.12^\circ) \text{ A}$$

18 6. For the circuit below. The circuit is working in sinusoidal, single frequency ($\omega = 2$ rad/s), and steady state.

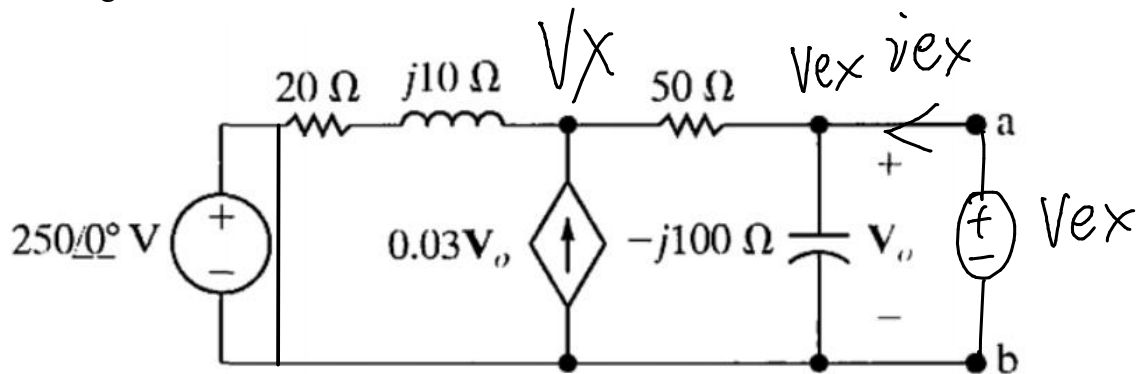- 1) Find the Thevenin AND Norton equivalent circuit at the terminals a and b.
- 2) Consider an inductor $L=5H$ is connected to the terminal a and b. Find the current through L $i_L(t)$ and indicate the reference direction in the circuit diagram.



$$1) \text{ KCL: } \frac{250 - V_x}{20 + j10} + 0.03 \cdot V_o = \frac{V_x - V_o}{50} = \frac{V_o}{-100j}$$



$$V_x = (1 + 0.5j) V_o$$

$$10 - 5j - 0.05 V_o + 0.03 V_o = 0.01j V_o$$

$$V_{Th} = V_o = \frac{10 - 5j}{0.01j + 0.02} V = 300 - 400j V = 500 \angle -53.13^\circ V$$



Z_{Th} : Apply External Voltage V_{ex} and KCL
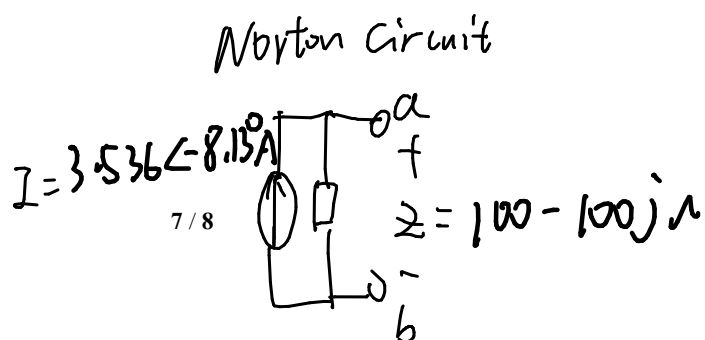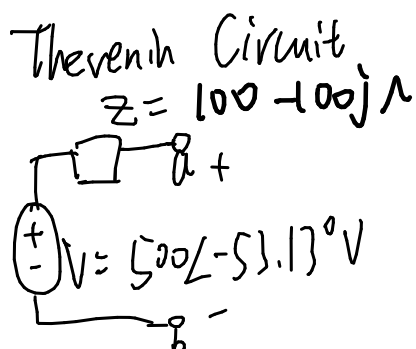
$$\left\{ \begin{array}{l} \frac{V_{ex} - V_x}{50} + 0.03 V_o = \frac{V_x}{20 + j10} \\ i_{ex} = \frac{V_{ex}}{-100j} + \frac{V_{ex} - V_x}{50} \\ V_{ex} = V_o \end{array} \right. \Rightarrow \left\{ \begin{array}{l} V_{Th} = 500 \angle -53.13^\circ V \\ i_{Th} = 3.536 \angle -8.13^\circ A \\ Z_{Th} = 100 - 100j \Omega \end{array} \right.$$



6. For the circuit below. The circuit is working in sinusoidal, single frequency ($\omega = 2$ rad/s), and steady state.

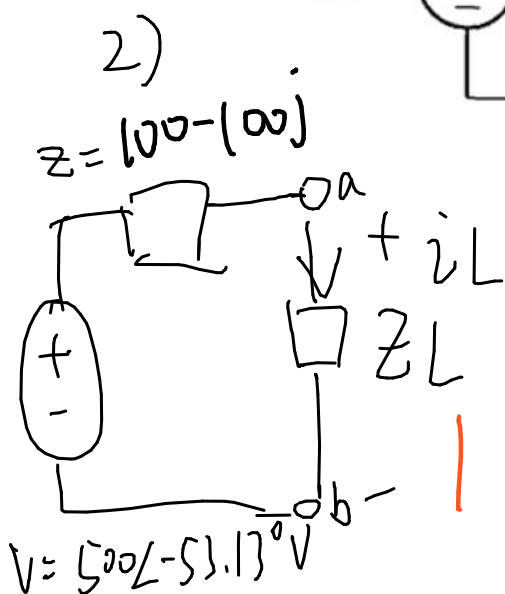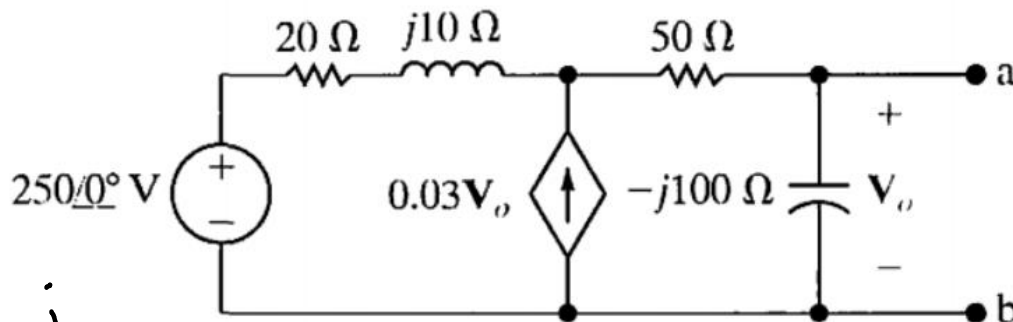- 1) Find the Thevenin AND Norton equivalent circuit at the terminals a and b.
- 2) Consider an inductor $L=5H$ is connected to the terminal a and b. Find the current through L $i_L(t)$ and indicate the reference direction in the circuit diagram.



$$i_L = \frac{V_{Th}}{Z_{Th} + Z_L}$$


$$= \frac{500 \angle -53.13^\circ}{j \cdot 2 \cdot 5 + 100 - j100}$$

$$= 3.646 - 0.178j \text{ A} = 3.716 \angle -11.14^\circ \text{ A}$$

$$i_L(t) = 3.716 \cos(2t - 11.14^\circ) \text{ A}$$

2

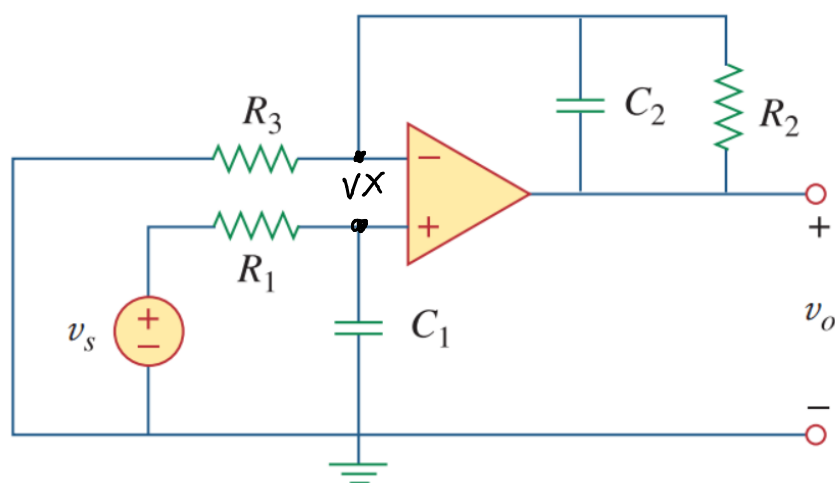- 6 7. For the circuit below. Suppose v_s is a sinusoidal voltage source with the angular frequency ω . Suppose the Op-amp is working in the linear mode. Find the expression for v_o/v_s .



$$\frac{V_s - V_x}{R_1} = V_x \cdot j\omega C_1 \quad 2$$


$$\frac{V_o - V_x}{\left(\frac{1}{j\omega C_2}\right) \parallel R_2} = \frac{V_x}{R_3} \quad 2$$

$$V_x = \frac{V_s}{1 + R_1 \omega C_1 j}$$

$$V_o = \left(1 + \frac{R_2}{R_3(R_2 j\omega C_2 + 1)}\right) V_x$$

$$\frac{V_o}{V_s} = \frac{V_o}{V_x} \cdot \frac{V_x}{V_s} = \frac{1 + \frac{R_2}{R_3(R_2 j\omega C_2 + 1)}}{1 + R_1 \omega C_1 j} \quad 2$$

On y ② :

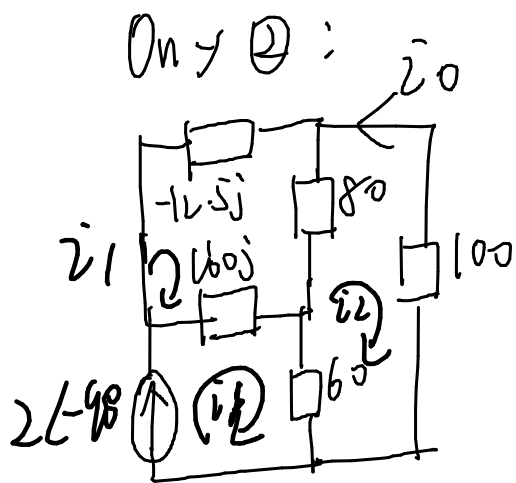

$$\begin{cases} v_1 \cdot (-12.5j) + (v_1 - v_2) 80 + (v_1 + 2j) \cdot 160j = 0 \\ (v_2 - v_1) 80 + (v_2 \cdot 100) + (v_2 + 2j) 60 = 0 \end{cases}$$

$$v_0 = -v_2$$

$$(80 + 147.5j)v_1 + (-80)v_2 = 320$$

$$-80v_1 + 240v_2 = -120j$$

$$-2v_1 + 6v_2 = -3j$$

$$v_1 = 3v_2 + \frac{3}{2}j$$

$$(240 + 442.5j)v_2 - 221.25 + 120j - 80v_2 = 320$$