

EE 111 Homework 9

Due date: Jun. 5<sup>th</sup>, 2019  
Turn in your homework in class

Rule:

- Work on your own. Discussion is permissible, but similar submissions will be judged as plagiarism.
- Please show all intermediate steps: a correct solution without an explanation will get zero credit.
- Please submit on time. No late submission will be accepted.
- Please prepare your submission in English only. No Chinese submission will be accepted.

1. Determine the Laplace transforms of these functions:

(a)  $f(t) = 5e^{-5t}u(t-5)$

(b)  $g(t) = 5 \cos(2t-1)u(t)$

(c)  $h(t) = \sin(2t)u(t-\tau)$

(d)  $p(t) = \begin{cases} 5t & 0 < t < 1 \\ -5t & 1 < t < 2 \\ 0 & \text{otherwise} \end{cases}$

a)  $f(t) = 5 \cdot e^{-5(t-5)} u(t-5) \cdot e^{-25}$  2'  
 $F(s) = \frac{5 \cdot e^{-5s}}{e^{25}(s+5)}$  2'

$f(t)$  变形 2'  
 $F(t)$  2'


b)  $g(t) = 5 \cos(2t-1)u(t)$  2'  
 $= 5 \cos(2t) \cos(1)u(t) + 5 \sin(2t) \sin(1)u(t)$   
 $G(s) = 5 \cos(1) \cdot \frac{s}{s^2+4} + 5 \sin(1) \cdot \frac{2}{s^2+4}$  2'  
 OR  
 $G(s) = \frac{2.7025}{s^2+4} + \frac{8.415}{s^2+4}$

c)  $\sin 2t = \sin[2(t-\tau) + 2\tau]$   
 $= \sin 2(t-\tau) \cos 2\tau + \cos 2(t-\tau) \sin 2\tau$   
 $f(t) = \cos 2\tau \sin 2(t-\tau)u(t-\tau) + \sin 2\tau \cos 2(t-\tau)u(t-\tau)$  2'  
 $F(s) = \cos 2\tau e^{-\tau s} \frac{2}{s^2+4} + \sin 2\tau e^{-\tau s} \frac{s}{s^2+4}$  2'

d)  $f(t) = 5t[u(t) - u(t-1)] - 5t[u(t-1) - u(t-2)]$   
 $= 5[tu(t) - 2tu(t-1) + tu(t-2)]$  2'  
 $= 5[tu(t) - 2(t-1)u(t-1) - 2u(t-1) + (t-2)u(t-2) + 2u(t-2)]$   
 $F(s) = 5[\frac{1}{s^2} - \frac{2e^{-s}}{s^2} - \frac{2e^{-s}}{s} + \frac{e^{-2s}}{s^2} + \frac{2e^{-2s}}{s}]$  2'  
 $= 5 \cdot \frac{1-2e^{-s}+e^{-2s}}{s^2} + 5 \cdot \frac{2e^{-2s}-2e^{-s}}{s}$

g' (2x4) 2. Determine the Laplace transform of the **period function** in the following Figures

b) tips: sin(t)

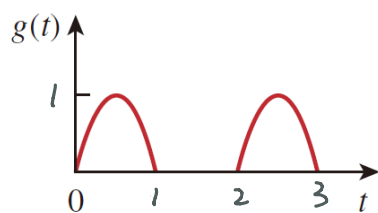


$$g(t) = \begin{cases} \sin \pi t & 0 < t < 1 \\ 0 & 1 < t < 2 \end{cases} \quad 1'$$

$$\begin{aligned} g_1(t) &= \sin(\pi t) \quad 0 < t < 1 \\ &= \sin(\pi t) [u(t) - u(t-1)] \\ &= \sin(\pi t) u(t) - \sin(\pi t) u(t-1) \\ &= \sin(\pi t) u(t) + \sin(\pi(t-1)) u(t-1) \end{aligned} \quad 1'$$

$$G_1(s) = \frac{\pi}{s^2 + \pi^2} (1 + e^{-s})$$
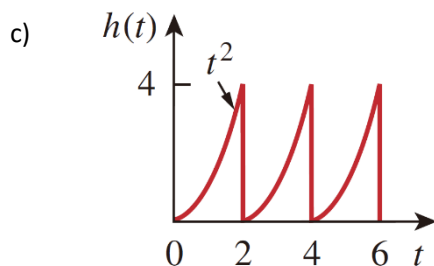
$$G(s) = \frac{G_1(s)}{1 - e^{-2s}} = \frac{\pi(1 + e^{-s})}{(s^2 + \pi^2) \cdot (1 - e^{-2s})} \quad 2'$$



$$\begin{aligned} h_1(t) &= t^2 [u(t) - u(t-2)] \\ &= t^2 u(t) - t^2 u(t-2) \\ &= t^2 u(t) - (t-2)^2 u(t-2) - 4(t-2) u(t-2) - 4u(t-2) \end{aligned} \quad 1'$$

$$\therefore H_1(s) = \frac{2}{s^3} (1 - e^{-2s}) - \frac{4}{s^2} e^{-2s} - \frac{4}{s} e^{-2s} \quad 1'$$

$$H(s) = \frac{H_1(s)}{(1 - e^{-Ts})}, \quad T=2$$

$$H(s) = \frac{2(1 - e^{-2s}) - 4s e^{-2s} (1 + s)}{s^3 (1 - e^{-2s})} \quad 2'$$

12' (3x4')

3. Find the inverse Laplace transform of:

(a)  $H(s) = \frac{s+8}{s(s+4)}$

(b)  $G(s) = \frac{4-e^{-2s}}{s^2+5s+4}$

(c)  $D(s) = \frac{10s}{(s^2+1)(s^2+4)}$

a)  $H(s) = \frac{s+6}{s(s+4)} = \frac{A}{s} + \frac{B}{s+4}$

$\Rightarrow A=2, B=-1$  1'

$\therefore H(s) = \frac{2}{s} - \frac{1}{s+4}$  1'

$h(t) = (2 - e^{-4t})u(t)$  2'

b) Let  $H(s) = \frac{1}{(s+1)(s+4)} = \frac{A}{s+1} + \frac{B}{s+4}$

$\Rightarrow A = \frac{1}{3}, B = -\frac{1}{3}$  1'

$H(s) = \frac{1}{3(s+1)} - \frac{1}{3(s+4)}$

$h(t) = \frac{1}{3} [e^{-t} - e^{-4t}]$  1'

$G(s) = 4H(s) - e^{-2s}H(s)$

$\therefore g(t) = 4h(t)u(t) - h(t-2)u(t-2)$   
 $= \frac{4}{3} [e^{-t} - e^{-4t}]u(t) - \frac{1}{3} [e^{-(t-2)} - e^{-4(t-2)}]u(t-2)$  2'

c)  $D(s) = \frac{10s}{(s^2+1)(s^2+4)} = \frac{As+B}{s^2+1} + \frac{Cs+D}{s^2+4}$

$10s = (s^2+4)(As+B) + (s^2+1)(Cs+D)$

$\Rightarrow A = \frac{10}{3}, B = 0, C = -\frac{10}{3}, D = 0$  1'

$\therefore D(s) = \frac{10s/3}{s^2+1} - \frac{10s/3}{s^2+4}$  1'

$d(t) = \left( \frac{10}{3} \cos t - \frac{10}{3} \cos 2t \right) u(t)$  2'

求系数 1'  
 $F(s)$  拆解 1'  
 求  $f(t)$  2'

4. (10pt) There is no energy stored in the circuit shown in Fig.4 at the time the switch is opened.

- (a) Derive the integrodifferential equations that govern the behavior of the node voltages  $v_1$  and  $v_2$ .  
 (b) Show that

$$V_2(s) = \frac{sI_g(s)}{C[s^2 + (R/L)s + (1/LC)]}.$$

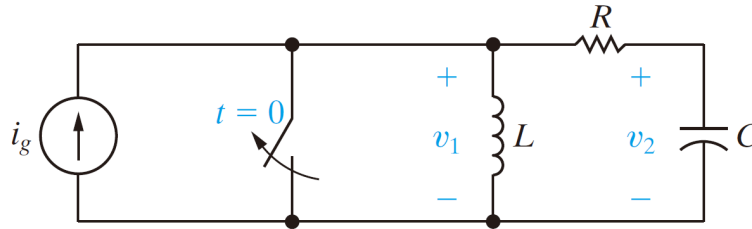


Fig. 4

**Solution:**

- (a)

$$\frac{1}{L} \int_0^t v_1 d\tau + \frac{v_1 - v_2}{R} = i_g u(t) \quad (3')$$

$$C \frac{dv_2}{dt} + \frac{v_2}{R} - \frac{v_1}{R} = 0 \quad (3')$$

- (b)

$$\frac{V_1}{sL} + \frac{V_1 - V_2}{R} = I_g \quad (2')$$

$$\frac{V_2 - V_1}{R} + sCV_2 = 0 \quad (2')$$

Solving,

$$V_2(s) = \frac{sI_g(s)}{C[s^2 + (R/L)s + (1/LC)]}$$

5. (12pt) ( $C=1.5625\text{mF}$ ) The switch in the circuit shown in Fig.5 has been in position x for a long time. At  $t = 0$ , the switch moves instantaneously to position y.

- (a) Construct an  $s$ -domain circuit for  $t > 0$ .  
 (b) Find  $I_o(s)$ .  
 (c) Find  $i_o(t)$ .


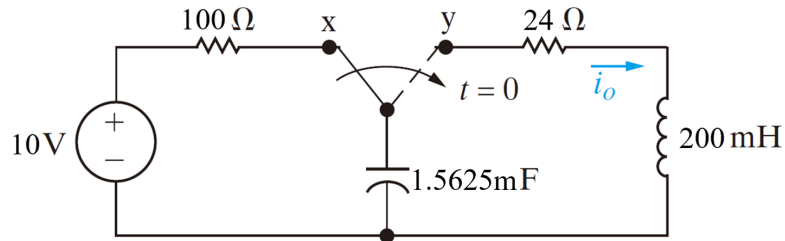


Fig. 5

**Solution:**

(a)

(4')

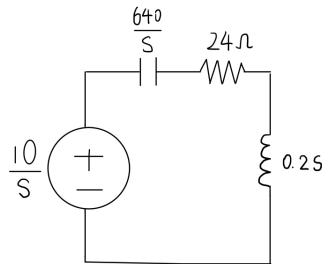

(b)

$$\frac{640}{s}I_o + 24I_o + 0.2sI_o - \frac{10}{s} = 0 \quad (2')$$

$$\Rightarrow I_o(s) = \frac{\frac{10}{s}}{\frac{640}{s} + 24 + 0.2s} = \frac{50}{s^2 + 120s + 3200} \quad (2')$$

(c)

$$I_o(s) = \frac{50}{(s+40)(s+80)} = \frac{K_1}{s+40} + \frac{K_2}{s+80}$$

$$K_1 = \frac{50}{s+80} \Big|_{s=-40} = 1.25 \quad (1')$$

$$K_2 = \frac{50}{s+40} \Big|_{s=-80} = -1.25 \quad (1')$$

$$I_o(s) = \frac{1.25}{s+40} - \frac{1.25}{s+80}$$

$$i_o(t) = (1.25e^{-40t} - 1.25e^{-80t})u(t)A \quad (2')$$

5. (12pt) ( $C=1.565\text{mF}$ ) The switch in the circuit shown in Fig.5 has been in position x for a long time. At  $t = 0$ , the switch moves instantaneously to position y.

- (a) Construct an  $s$ -domain circuit for  $t > 0$ .  
 (b) Find  $I_o(s)$ .  
 (c) Find  $i_o(t)$ .


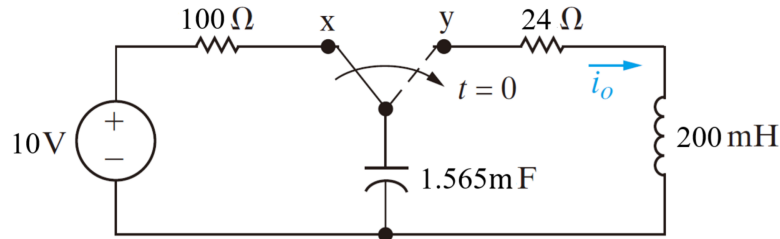


Fig. 5

**Solution:**

(a)

(4')

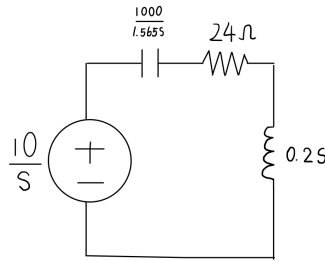

(b)

$$\frac{1000}{1.565s} I_o + 24 I_o + 0.2s I_o - \frac{10}{s} = 0 \quad (2')$$

$$\Rightarrow I_o(s) = \frac{\frac{10}{s}}{\frac{1000}{1.565s} + 24 + 0.2s} = \frac{50}{s^2 + 120s + 3194.888} \quad (2')$$

(c)

$$I_o(s) = \frac{50}{(s + 39.873)(s + 80.127)} = \frac{K_1}{s + 39.873} + \frac{K_2}{s + 80.127}$$

$$K_1 = \frac{50}{s + 80.127} \Big|_{s=-39.873} = 1.242 \quad (1')$$

$$K_2 = \frac{50}{s + 39.873} \Big|_{s=-80.127} = -1.242 \quad (1')$$

$$I_o(s) = \frac{1.242}{s + 39.873} - \frac{1.242}{s + 80.127}$$

$$i_o(t) = (1.242e^{-39.873t} - 1.242e^{-80.127t})u(t) \text{ A} \quad (2')$$

6. (16pt) There is no energy stored in the circuit in Fig.6 at the time  $t(0^-)$ , and  $v_g(t) = 325u(t)$  V.

- (a) Find  $V_o(s)$  and  $I_o(s)$ .  
 (b) Find  $v_o(t)$  and  $i_o(t)$ .  
 (c) Do the solutions for  $v_o(t)$  and  $i_o(t)$  make sense in terms of known circuit behavior? Explain.


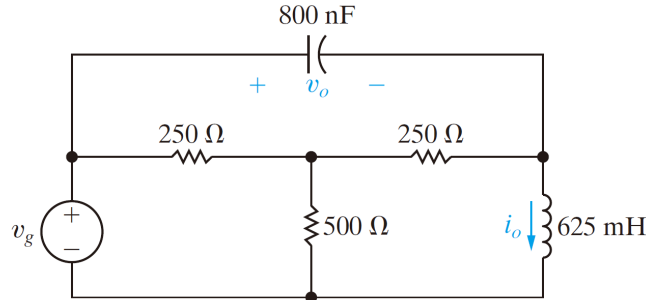


Fig. 6

**Solution:**

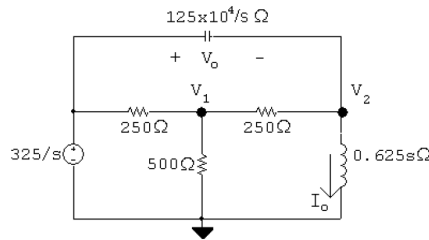

(a)

$$\frac{V_1 - 325/s}{250} + \frac{V_1}{500} + \frac{V_1 - V_2}{250} = 0 \quad (1')$$

$$\frac{V_2}{0.625s} + \frac{V_2 - V_1}{250} + \frac{(V_2 - 325/s)s}{1250000} = 0 \quad (1')$$

Simplify,

$$5V_1 - 2V_2 = \frac{650}{s}$$

$$-5000sV_1 + (s^2 + 5000s + 2000000)V_2 = 325s$$

Then we have

$$V_2 = \frac{325}{s + 1000} \quad (2')$$

$$V_o(s) = \frac{325}{s} - \frac{325}{s + 1000} \quad (2')$$


$$I_o(s) = \frac{V_2}{0.625s} = \frac{0.52}{s} - \frac{0.52}{s + 1000} \quad (2')$$

(b)

$$v_o(t) = (325 - 325e^{-1000t})u(t) \text{ V} \quad (2')$$
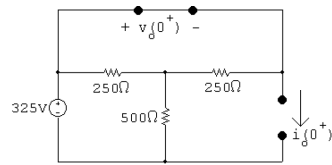
$$i_o(t) = (0.52 - 0.5e^{-1000t})u(t) \text{ A} \quad (2')$$






(c) At  $t = 0^+$  the circuit is

$$v_o(0^+) = 0 \quad i_o(0^+) = 0 \quad \text{Checks} \quad (2')$$

At  $t = \infty$  the circuit is

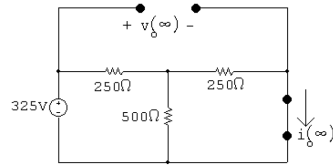

$$v_o(\infty) = 325V \quad i_o(\infty) = \frac{325}{250 + (500 \parallel 250)} \cdot \frac{500}{750} = 0.52A \quad \text{Checks} \quad (2')$$

7. (12pt) ( $C=3.33\text{mF}$ ) The op amp in the circuit shown in Fig.7 is ideal. There is no energy stored in the capacitors at the instant the circuit is energized.

- (a) Find  $v_o(t)$  if  $v_{g1}(t) = 40u(t)$  V and  $v_{g2}(t) = 16u(t)$  V.  
 (b) How many milliseconds after the two voltage sources are turned on does the op amp saturate?

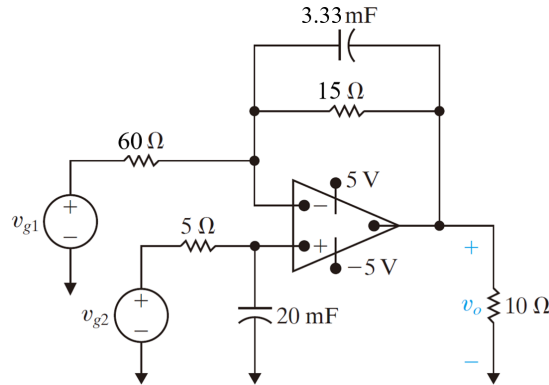


Fig. 7

**Solution:**

(a)

$$\frac{V_p - 16/s}{5} + \frac{V_p}{50/s} = 0 \Rightarrow V_p = \frac{160}{s(s+10)} \quad (2')$$

$$\frac{V_p - 40/s}{60} + \frac{V_p - V_o}{15} + \frac{V_p - V_o}{300/s} = 0 \quad (2')$$

$$V_o = \frac{-40s + 2000}{s(s+10)(s+20)} \quad (2')$$

$$= \frac{10}{s} - \frac{24}{s+10} + \frac{14}{s+20}$$

$$v_o(t) = (10 - 24e^{-10t} + 14e^{-20t})u(t) \text{ V} \quad (2')$$

(b)

$$10 - 24e^{-10t} + 14e^{-20t} = 5 \quad (2')$$

$$e^{-10t} = 0 \quad \text{or} \quad 0.2427$$

$$t = 141.60 \text{ ms} \quad (2')$$

7. (12pt) ( $C=30\text{mF}$ ) The op amp in the circuit shown in Fig.7 is ideal. There is no energy stored in the capacitors at the instant the circuit is energized.

- (a) Find  $v_o(t)$  if  $v_{g1}(t) = 40u(t)$  V and  $v_{g2}(t) = 16u(t)$  V.  
 (b) How many milliseconds after the two voltage sources are turned on does the op amp saturate?

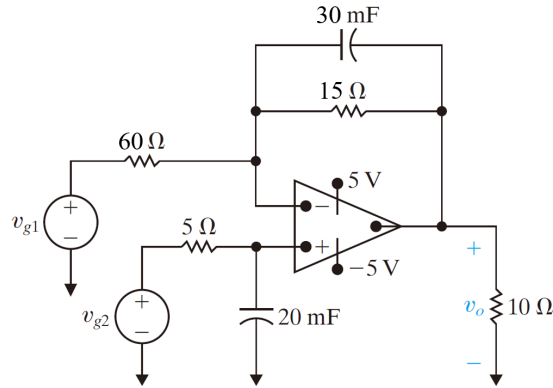


Fig. 8

**Solution:**

(a)

$$\frac{V_p - 16/s}{5} + \frac{V_p}{50/s} = 0 \Rightarrow V_p = \frac{160}{s(s+10)} \quad (2')$$

$$\frac{V_p - 40/s}{60} + \frac{V_p - V_o}{15} + \frac{V_p - V_o}{100/3s} = 0 \quad (2')$$

$$\begin{aligned} V_o &= \frac{1240s + 2000}{s(s+10)(9s+20)} \\ &= \frac{10}{s} - \frac{104}{7(s+10)} + \frac{34}{7(s+\frac{20}{9})} \end{aligned} \quad (2')$$

$$v_o(t) = (10 - 14.857e^{-10t} + 4.87e^{-2.22t})u(t)V \quad (2')$$

(b)

$$10 - \frac{104}{7}e^{-10t} + \frac{34}{7}e^{-\frac{20}{9}t} = 5 \quad (2')$$

$$t = 45.92ms \quad (2')$$

8. (14pt) The switch in the circuit seen in Fig.8 has been in position a for a long time. At  $t = 0$ , it moves instantaneously to position b. Find  $i_o(t)$  for  $t \geq 0$ .


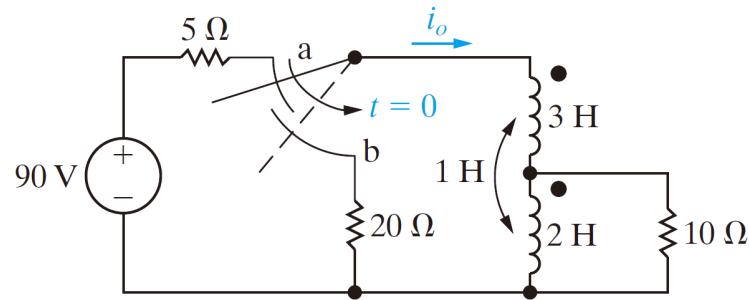


Fig. 9

**Solution:**

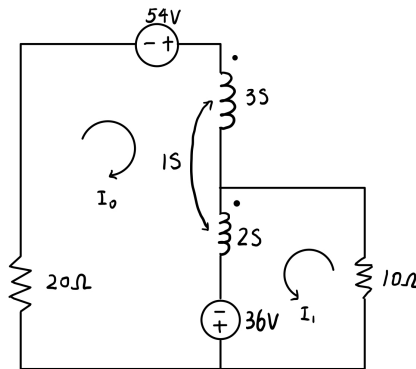

$$\begin{cases} -54 + 3sI_o + s(I_o + I_1) - 18 + 2s(I_o + I_1) + sI_o - 18 - 36 + 20I_o = 0 \\ 2s(I_1 + I_o) + sI_o - 18 - 36 + 10I_o = 0 \end{cases} \quad (4')$$

Solving,

$$I_o = \frac{90s + 1260}{5s^2 + 110s + 200} = \frac{18s + 252}{(s + 2)(s + 20)} = \frac{K_1}{s + 2} + \frac{K_2}{s + 20} \quad (4')$$

$$K_1 = \left. \frac{18s + 252}{s + 20} \right|_{s=-2} = 12 \quad (2')$$

$$K_2 = \left. \frac{18s + 252}{s + 2} \right|_{s=-20} = 6 \quad (2')$$

$$\Rightarrow I_o = \frac{12}{s + 2} + \frac{6}{s + 20}$$

$$i_o(t) = (12e^{-2t} + 6e^{-20t})u(t)A \quad (2')$$