



# AC Steady-State Analysis

## Discussion7



# Quick Review

- Sinusoids with Phasors
- Impedance and combinations
- KCL/KVL in frequency domain
- Miscellaneous



# Sum of Sinusoidal Functions

If

$$v = v_1 + v_2 + \cdots + v_n$$

where  $v_i$  are sinusoidal voltages of the same frequency,  
then

$$\mathbf{V} = \mathbf{V}_1 + \mathbf{V}_2 + \cdots + \mathbf{V}_n$$

$$v = v_1 + v_2 + \cdots + v_n$$

$$V_m \cos(\omega t + \theta) = V_{m1} \cos(\omega t + \theta_1) + V_{m2} \cos(\omega t + \theta_2) + \cdots + V_{mn} \cos(\omega t + \theta_n)$$

$$\text{Re}(V_m e^{j\theta} e^{j\omega t}) = \text{Re}(V_{m1} e^{j\theta_1} e^{j\omega t}) + \cdots + \text{Re}(V_{mn} e^{j\theta_n} e^{j\omega t})$$

$$\mathbf{V}_k = V_{mk} e^{j\theta_k}$$

$$\text{Re}(\mathbf{V} e^{j\omega t}) = \text{Re}((\mathbf{V}_1 + \cdots + \mathbf{V}_n) e^{j\omega t})$$

$$\mathbf{V} = \mathbf{V}_1 + \mathbf{V}_2 + \cdots + \mathbf{V}_n$$



## Example

If  $y_1 = 20\cos(\omega t - 30^\circ)$  and  $y_2 = 40\cos(\omega t + 60^\circ)$ , express  $y = y_1 + y_2$  as a single sinusoidal function.

1. Use trigonometric identities
2. Use the phasor concept

$$\begin{aligned}y &= (20 \cos 30 + 40 \cos 60) \cos \omega t \\&\quad + (20 \sin 30 - 40 \sin 60) \sin \omega t \\&= 37.32 \cos \omega t - 24.64 \sin \omega t. \\y &= 44.72 \cos (\omega t + 33.43^\circ)\end{aligned}$$

$$\begin{aligned}\mathbf{Y} &= \mathbf{Y}_1 + \mathbf{Y}_2 \\&= 20\angle -30^\circ + 40\angle 60^\circ \\&= (17.32 - j10) + (20 + j34.64) \\&= 37.32 + j24.64 \\&= 44.72\angle 33.43^\circ.\end{aligned}$$



# Kirchhoff's Laws in the Frequency Domain

- Let  $v_1, v_2, \dots, v_n$  be the voltages around a closed loop.  
Then according to KCL

$$v_1 + v_2 + \dots + v_n = 0$$

$$\mathbf{V}_1 + \mathbf{V}_2 + \dots + \mathbf{V}_n = 0$$

Similarly, KCL holds for phasors:

$$i_1 + i_2 + \dots + i_n = 0$$

$$\mathbf{I}_1 + \mathbf{I}_2 + \dots + \mathbf{I}_n = 0,$$



# AC Phasor Analysis General Procedure

## Step 1: Adopt cosine reference

$$\begin{aligned} v_s(t) &= 12 \sin(\omega t - 45^\circ) \\ &= 12 \cos(\omega t - 45^\circ - 90^\circ) = 12 \cos(\omega t - 135^\circ) \text{ V.} \\ V_s &= 12e^{-j135^\circ} \text{ V.} \end{aligned}$$

## Step 2: Transform circuit to phasor domain

## Step 3: Cast KCL and/or KVL equations in phasor domain


$$Z_R \mathbf{I} + Z_C \mathbf{I} = \mathbf{V}_s,$$

which is equivalent to

$$\left( R + \frac{1}{j\omega C} \right) \mathbf{I} = 12e^{-j135^\circ}.$$

### Step 1


Adopt Cosine Reference  
(Time Domain)

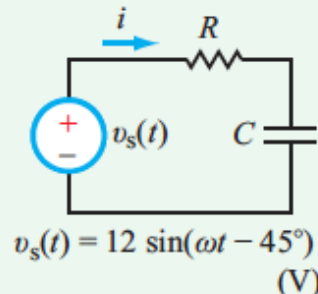
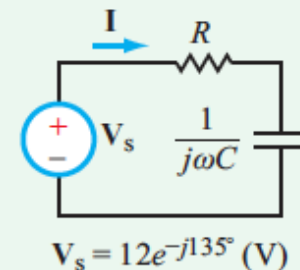
### Step 2

Transfer to Phasor Domain

$$\begin{aligned} i &\rightarrow \mathbf{I} \\ v &\rightarrow \mathbf{V} \\ R &\rightarrow Z_R = R \\ L &\rightarrow Z_L = j\omega L \\ C &\rightarrow Z_C = 1/j\omega C \end{aligned}$$



### Step 3

Cast Equations in  
Phasor Form

$$\mathbf{I} \left( R + \frac{1}{j\omega C} \right) = \mathbf{V}_s$$

### Step 4

Solve for Unknown Variable  
(Phasor Domain)

$$\mathbf{I} = \frac{\mathbf{V}_s}{R + \frac{1}{j\omega C}}$$

### Step 5

Transform Solution  
Back to Time Domain

$$\begin{aligned} i(t) &= \Re[\mathbf{I}e^{j\omega t}] \\ &= 6 \cos(\omega t - 105^\circ) \\ &\quad \text{(mA)} \end{aligned}$$



# AC Phasor Analysis General Procedure

## Step 4: Solve for unknown variable

$$\mathbf{I} = \frac{12e^{-j135^\circ}}{R + \frac{1}{j\omega C}} = \frac{j12\omega C e^{-j135^\circ}}{1 + j\omega RC}.$$

Using the specified values, namely  $R = \sqrt{3} \text{ k}\Omega$ ,  $C = 1 \text{ }\mu\text{F}$ , and  $\omega = 10^3 \text{ rad/s}$ ,

$$\mathbf{I} = \frac{j12 \times 10^3 \times 10^{-6} e^{-j135^\circ}}{1 + j10^3 \times \sqrt{3} \times 10^3 \times 10^{-6}} = \frac{j12e^{-j135^\circ}}{1 + j\sqrt{3}} \text{ mA.}$$

$$\mathbf{I} = \frac{12e^{-j135^\circ} \cdot e^{j90^\circ}}{2e^{j60^\circ}} = 6e^{j(-135^\circ+90^\circ-60^\circ)} = 6e^{-j105^\circ} \text{ mA.}$$


## Step 5: Transform solution back to time domain

To return to the time domain, we apply the fundamental relation between a sinusoidal function and its phasor counterpart, namely

$$i(t) = \Re[\mathbf{I}e^{j\omega t}] = \Re[6e^{-j105^\circ} e^{j\omega t}] = 6 \cos(\omega t - 105^\circ) \text{ mA.}$$

### Step 1


Adopt Cosine Reference  
(Time Domain)

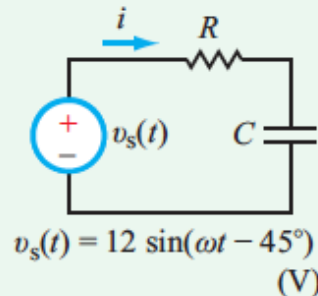
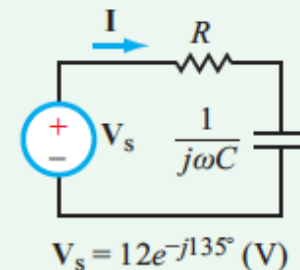
### Step 2

Transfer to Phasor Domain

$$\begin{aligned} i &\rightarrow \mathbf{I} \\ v &\rightarrow \mathbf{V} \\ R &\rightarrow \mathbf{Z}_R = R \\ L &\rightarrow \mathbf{Z}_L = j\omega L \\ C &\rightarrow \mathbf{Z}_C = 1/j\omega C \end{aligned}$$



### Step 3

Cast Equations in  
Phasor Form

$$\mathbf{I} \left( R + \frac{1}{j\omega C} \right) = \mathbf{V}_s$$



### Step 4

Solve for Unknown Variable  
(Phasor Domain)

$$\mathbf{I} = \frac{\mathbf{V}_s}{R + \frac{1}{j\omega C}}$$



### Step 5

Transform Solution  
Back to Time Domain

$$\begin{aligned} i(t) &= \Re[\mathbf{I}e^{j\omega t}] \\ &= 6 \cos(\omega t - 105^\circ) \text{ (mA)} \end{aligned}$$

# Example: RL Circuit

$$v_s(t) = 15 \sin(4 \times 10^4 t - 30^\circ) \text{ V.}$$

Also,  $R = 3 \Omega$  and  $L = 0.1 \text{ mH}$ . Obtain an expression for the voltage across the inductor.

## Solution:

**Step 1:** Convert  $v_s(t)$  to the cosine reference


$$v_s(t) = 15 \sin(4 \times 10^4 t - 30^\circ) = 15 \cos(4 \times 10^4 t - 120^\circ) \text{ V,}$$

$$\mathbf{V}_s = 15e^{-j120^\circ} \text{ V.}$$


**Step 2:** Transform circuit to the phasor domain

**Step 3:** Cast KVL in phasor domain
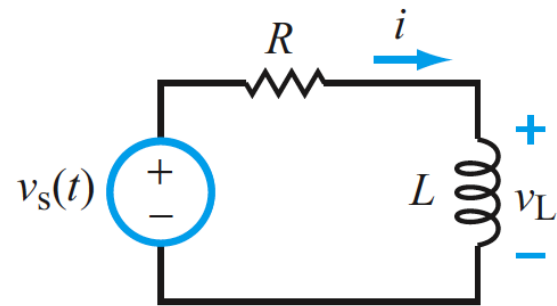
$$R\mathbf{I} + j\omega L\mathbf{I} = \mathbf{V}_s.$$



(a) Time domain

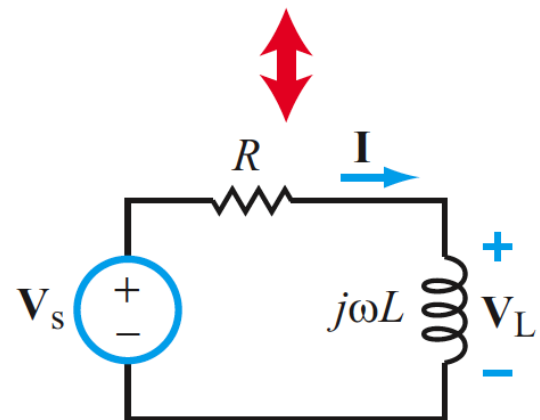

(b) Phasor domain





**Step 4:** Solve for unknown variable

$$\begin{aligned}\mathbf{I} &= \frac{\mathbf{V}_s}{R + j\omega L} = \frac{15e^{-j120^\circ}}{3 + j4 \times 10^4 \times 10^{-4}} \\ &= \frac{15e^{-j120^\circ}}{3 + j4} = \frac{15e^{-j120^\circ}}{5e^{j53.1^\circ}} = 3e^{-j173.1^\circ} \text{ A.}\end{aligned}$$


The phasor voltage across the inductor is related to  $\mathbf{I}$  by

$$\begin{aligned}\mathbf{V}_L &= j\omega L \mathbf{I} \\ &= j4 \times 10^4 \times 10^{-4} \times 3e^{-j173.1^\circ} \\ &= j12e^{-j173.1^\circ} \\ &= 12e^{-j173.1^\circ} \cdot e^{j90^\circ} = 12e^{-j83.1^\circ} \text{ V,}\end{aligned}$$


where we replaced  $j$  with  $e^{j90^\circ}$ .

**Step 5:** Transform solution to the time domain
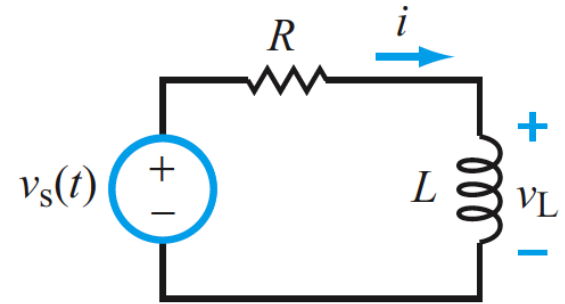
$$\begin{aligned}v_L(t) &= \Re[\mathbf{V}_L e^{j\omega t}] \\ &= \Re[12e^{-j83.1^\circ} e^{j4 \times 10^4 t}] \\ &= 12 \cos(4 \times 10^4 t - 83.1^\circ) \text{ V.}\end{aligned}$$




(a) Time domain

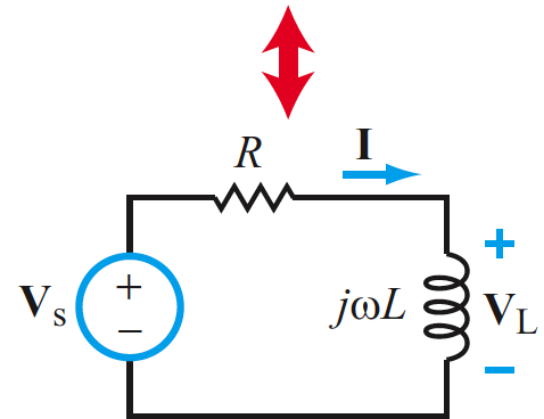

(b) Phasor domain



## Exercise1

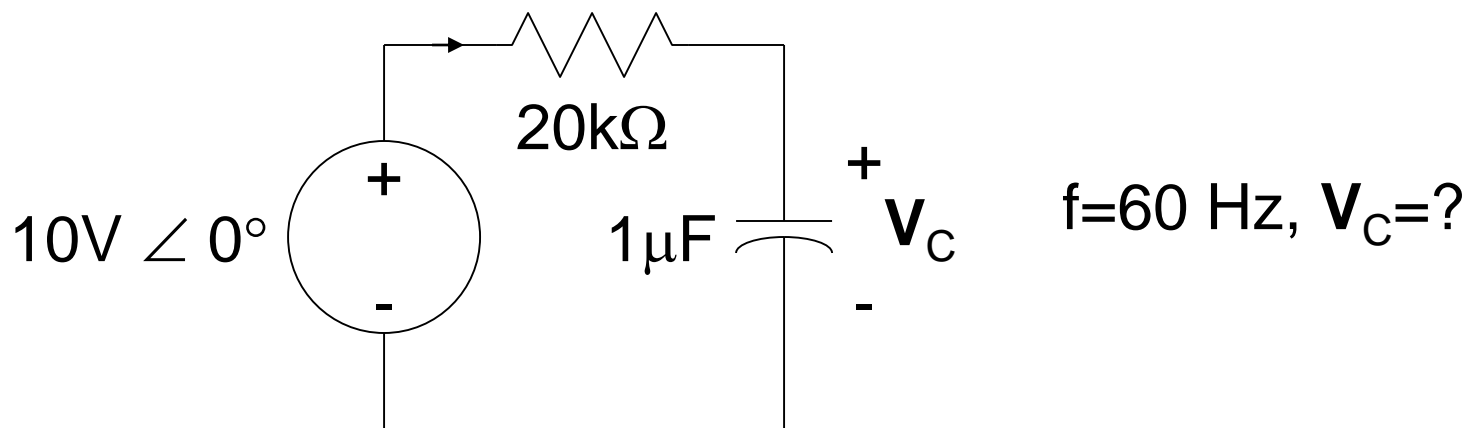


1.  $f=60\text{ Hz}$ ,  $V_C=?$
2.  $\omega = 10$ , find  $V_C$

First compute impedances for resistor and capacitor:

$$\mathbf{Z}_R = R = 20\text{k}\Omega = 20\text{k}\Omega \angle 0^\circ$$
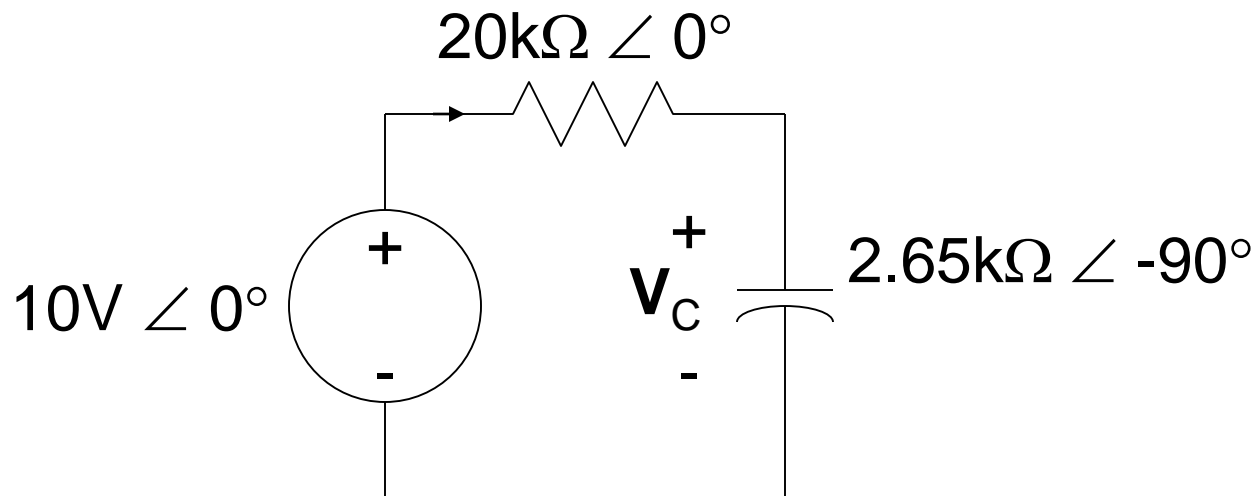
$$\mathbf{Z}_C = 1/j(2\pi f \times 1\mu\text{F}) = 2.65\text{k}\Omega \angle -90^\circ$$




Now use the voltage divider to find  $V_C$ :

$$V_C = 10V \angle 0^\circ \left( \frac{2.65k\Omega \angle -90^\circ}{2.65k\Omega \angle -90^\circ + 20k\Omega \angle 0^\circ} \right)$$


$$V_C = 1.31V \angle -82.4^\circ$$




## Exercise2

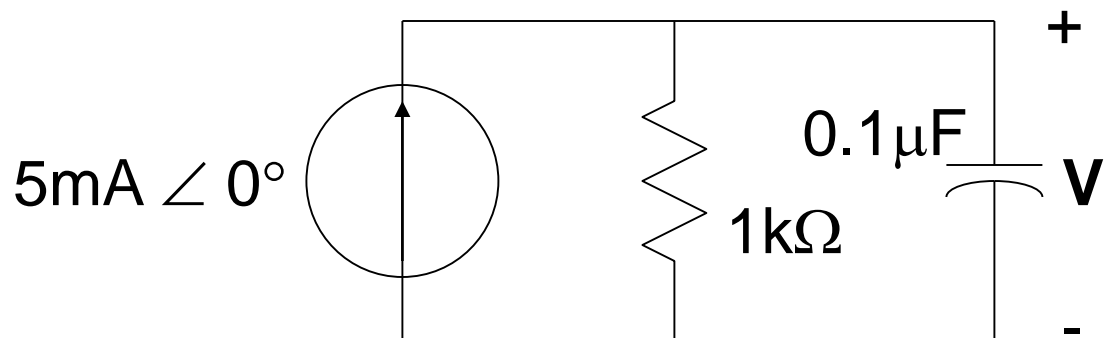

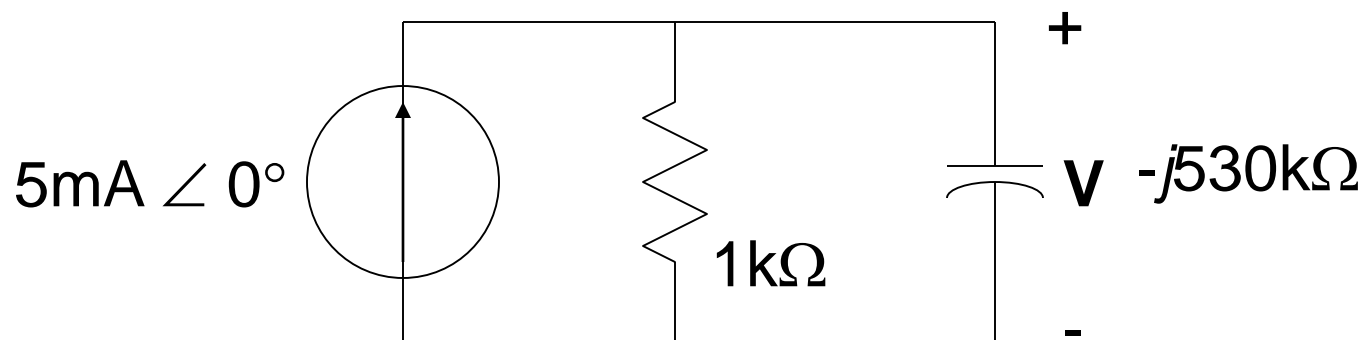Find  $v(t)$  for  $\omega = 2\pi \times 3000$



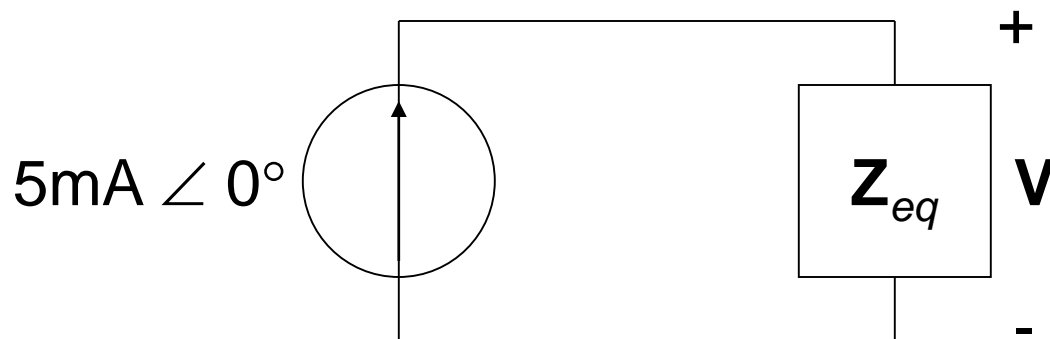

$$\mathbf{Z}_{eq} = \frac{1000 \times (-j530)}{1000 - j530} = \frac{10^3 \angle 0^\circ \times 530 \angle -90^\circ}{1132 \angle -27.9^\circ}$$

$$\mathbf{Z}_{eq} = 468.2\Omega \angle -62.1^\circ$$


$$\mathbf{V} = \mathbf{I}\mathbf{Z}_{eq} = 5\text{mA} \angle 0^\circ \times 468.2\Omega \angle -62.1^\circ$$

$$\mathbf{V} = 2.34\text{V} \angle -62.1^\circ$$


$$v(t) = 2.34 \cos(2\pi 3000t - 62.1^\circ) \text{V}$$




## Change the Frequency

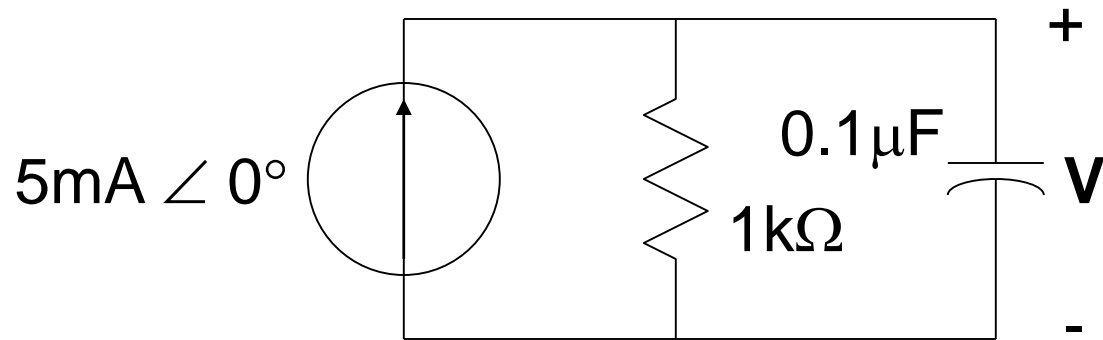

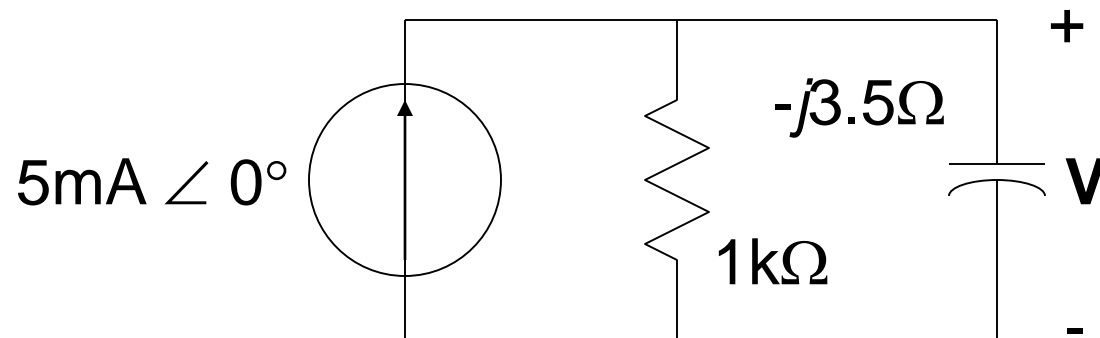Find  $v(t)$  for  $\omega = 2\pi \cdot 455000$



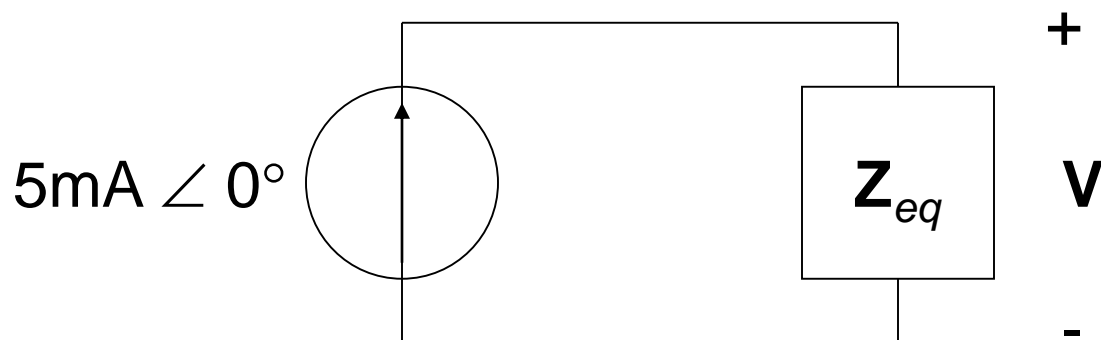

$$\mathbf{Z}_{eq} = \frac{1000 \times (-j3.5)}{1000 - j3.5} = \frac{10^3 \angle 0^\circ \times 3.5 \angle -90^\circ}{1000 \angle -0.2^\circ}$$

$$\mathbf{Z}_{eq} = 3.5 \angle -89.8^\circ \Omega$$


$$\mathbf{V} = \mathbf{I}\mathbf{Z}_{eq} = 5 \angle 0^\circ \text{mA} \times 3.5 \angle -89.8^\circ \Omega \quad \mathbf{V} = 17.5 \angle -89.8^\circ \text{mV}$$

$$v(t) = 17.5 \cos(2\pi 455000t - 89.8^\circ) \text{mV}$$


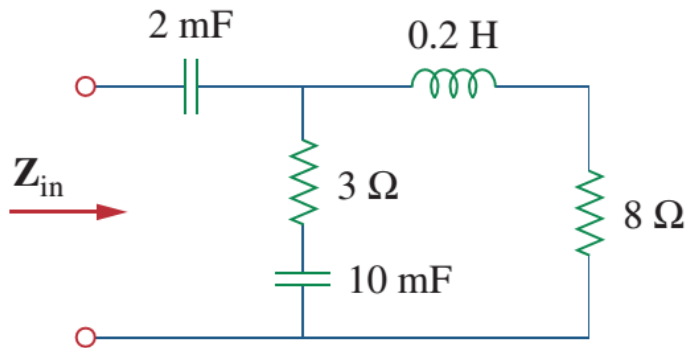
## Exercise3

- Find the input impedance of the circuit below.  $\omega = 50\text{rad/s}$ .



$$\mathbf{Z}_1 = \frac{1}{j\omega C} = \frac{1}{j50 \times 2 \times 10^{-3}} = -j10 \Omega$$

$$\mathbf{Z}_2 = 3 + \frac{1}{j\omega C} = 3 + \frac{1}{j50 \times 10 \times 10^{-3}} = (3 - j2) \Omega$$

$$\mathbf{Z}_3 = 8 + j\omega L = 8 + j50 \times 0.2 = (8 + j10) \Omega$$



$$\begin{aligned}\mathbf{Z}_{\text{in}} &= \mathbf{Z}_1 + \mathbf{Z}_2 \parallel \mathbf{Z}_3 = -j10 + \frac{(3 - j2)(8 + j10)}{11 + j8} \\ &= -j10 + \frac{(44 + j14)(11 - j8)}{11^2 + 8^2} = -j10 + 3.22 - j1.07 \Omega\end{aligned}$$




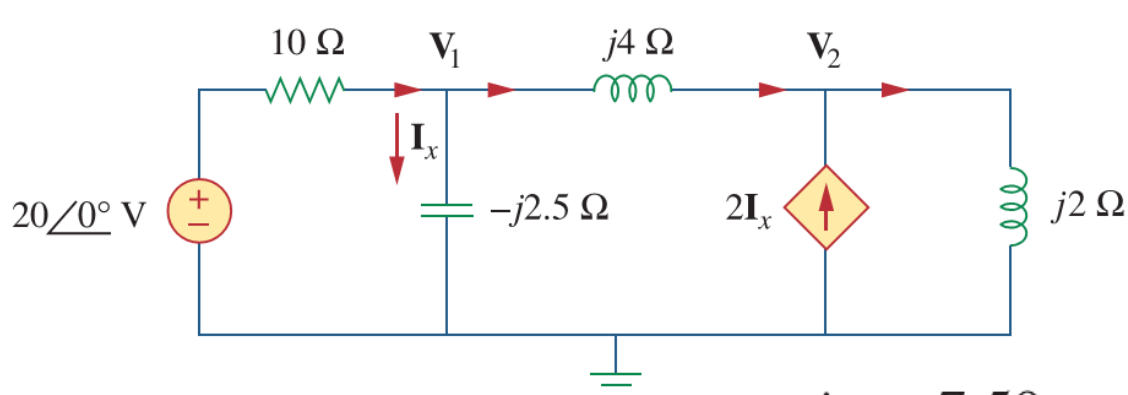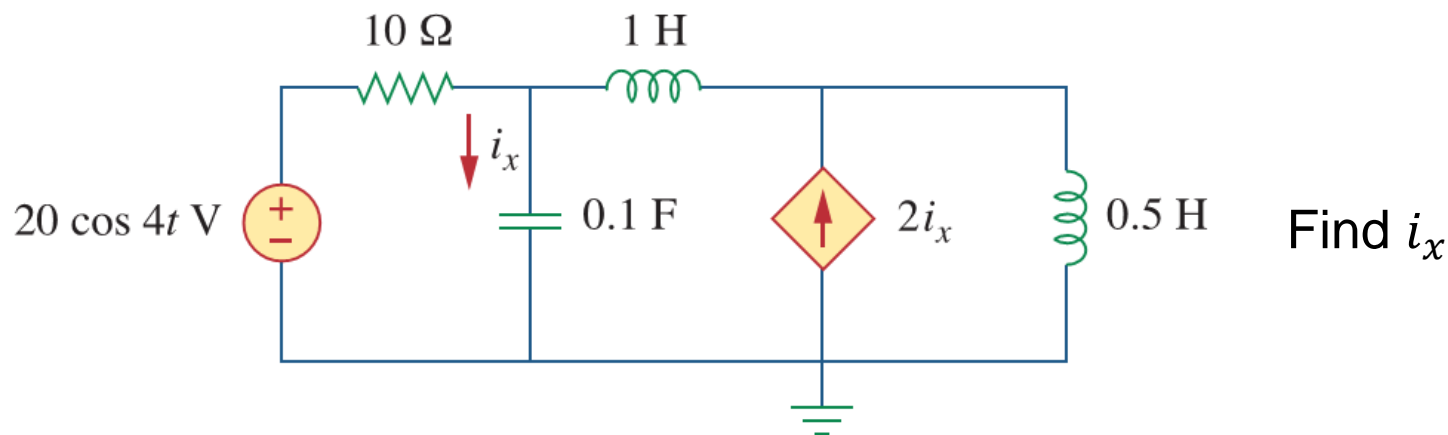
# Nodal Analysis

- Note that AC sources appear as DC sources with their values expressed as their amplitude.




$$\frac{20 - V_1}{10} = \frac{V_1}{-j2.5} + \frac{V_1 - V_2}{j4}$$

$$2I_x + \frac{V_1 - V_2}{j4} = \frac{V_2}{j2}$$

$$i_x = 7.59 \cos(4t + 108.4^\circ) \text{ A}$$



# Thevenin Equivalent

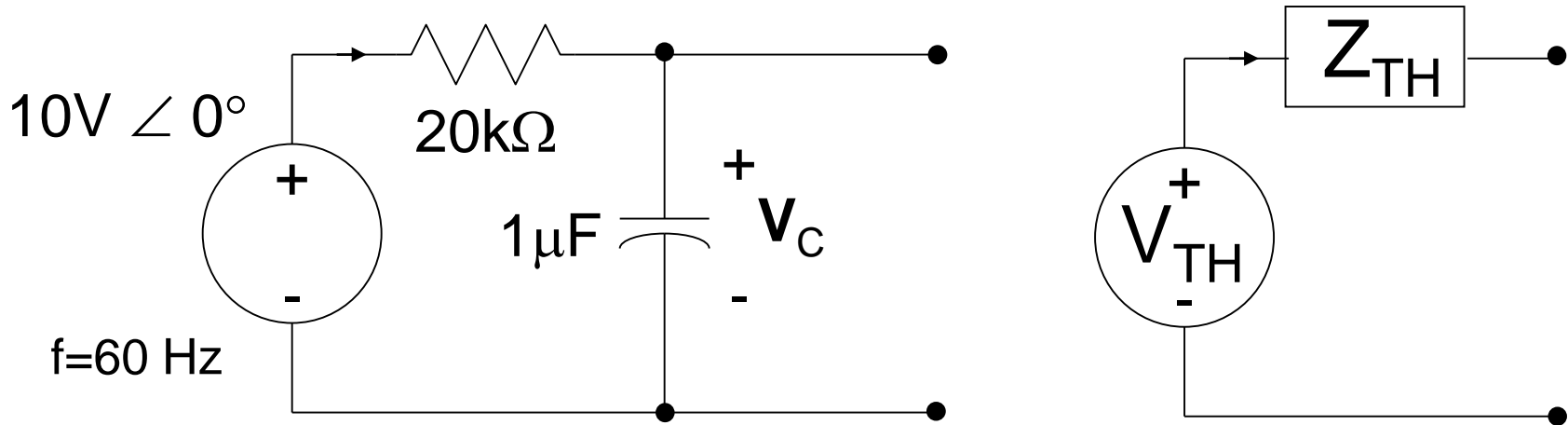

$$\mathbf{Z}_R = R = 20\text{k}\Omega = 20\text{k}\Omega \angle 0^\circ$$

$$\mathbf{Z}_C = 1/j(2\pi f \times 1\mu\text{F}) = 2.65\text{k}\Omega \angle -90^\circ$$

$$\mathbf{V}_{TH} = \mathbf{V}_{OC} = 10\text{V} \angle 0^\circ \left( \frac{2.65\text{k}\Omega \angle -90^\circ}{2.65\text{k}\Omega \angle -90^\circ + 20\text{k}\Omega \angle 0^\circ} \right) = 1.31 \angle -82.4$$

$$\mathbf{Z}_{TH} = \mathbf{Z}_R \parallel \mathbf{Z}_C = \left( \frac{20\text{k}\Omega \angle 0^\circ \cdot 2.65\text{k}\Omega \angle -90^\circ}{2.65\text{k}\Omega \angle -90^\circ + 20\text{k}\Omega \angle 0^\circ} \right) = 2.62 \angle -82.4$$



## Something need to notice

- A sinusiod function can be equivalently transformed to a phasor  $v(t) = V_m \cos(\omega t + \phi) \Leftrightarrow \mathbf{V} = V_m \angle \phi$
- Get familiar with the relations and caculation for complex numbers and phasors
- When we describe the impedance, we need to specify at what frequency we are describing the impedance.




# Outline


- **Most analytical techniques we used before can be applied to frequency-domain circuits !!**
- Nodal/Mesh analysis
- Superposition
- Source transformation/Thevenin/Norton
- Applications
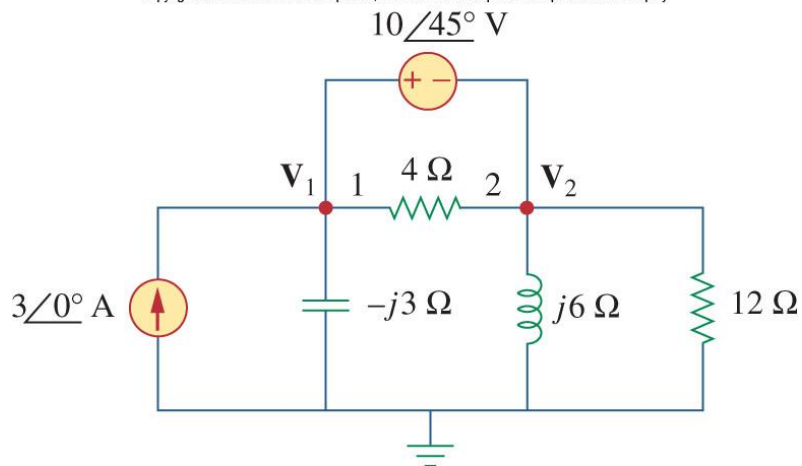
# Nodal Analysis - Supernode

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display



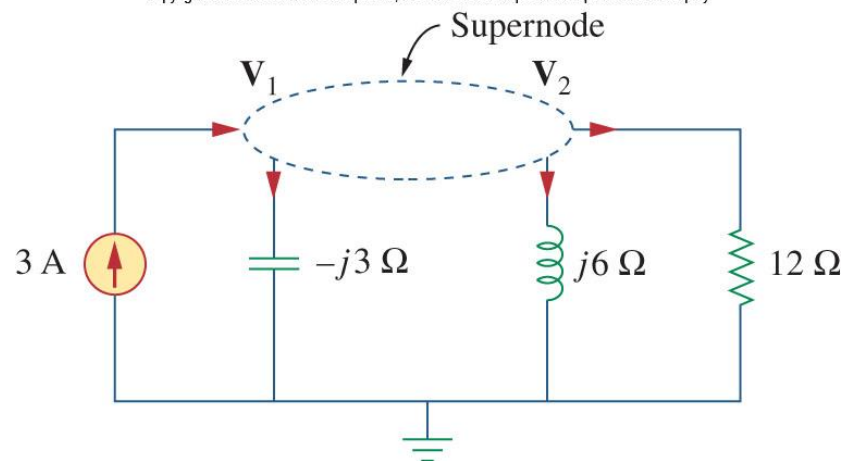Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display



### Example 7-12: Nodal Analysis

Apply the nodal-analysis method to determine  $i_L(t)$  in the circuit of Fig. 7-25(a). The sources are given by:

$$v_{s1}(t) = 12 \cos 10^3 t \text{ V},$$

$$v_{s2}(t) = 6 \sin 10^3 t \text{ V}.$$

**Solution:** We first will demonstrate how to solve this problem using the standard nodal-analysis method, and then we will solve it again by applying the by-inspection method.

#### Nodal-Analysis Method

Our first step is to transform the given circuit to the phasor domain. Accordingly,

$$\mathbf{Z}_C = \frac{1}{j\omega C} = \frac{-j}{10^3 \times 0.25 \times 10^{-3}} = -j4 \Omega,$$

$$\mathbf{Z}_L = j\omega L = j10^3 \times 10^{-3} = j1 \Omega,$$

$$\mathbf{V}_{s1} = 12 \text{ V},$$

and

$$\mathbf{V}_{s2} = -j6 \text{ V},$$

$$\mathbf{I}_1 = \frac{\mathbf{V}_1 - \mathbf{V}_3}{R_3} = \frac{\mathbf{V}_1 - \mathbf{V}_3}{2},$$


$$\mathbf{I}_2 = \frac{\mathbf{V}_1 - \mathbf{V}_2 + \mathbf{V}_{s1}}{R_2} = \frac{\mathbf{V}_1 - \mathbf{V}_2 + 12}{2},$$

$$\mathbf{I}_3 = \frac{\mathbf{V}_1}{R_1 + \mathbf{Z}_C} = \frac{\mathbf{V}_1}{3 - j4}.$$


Inserting the expressions for  $\mathbf{I}_1$  to  $\mathbf{I}_3$  in Eq. (7.109) and then rearranging the terms leads to

$$\left( \frac{1}{2} + \frac{1}{2} + \frac{1}{3 - j4} \right) \mathbf{V}_1 - \frac{1}{2} \mathbf{V}_2 - \frac{1}{2} \mathbf{V}_3 = -6.$$

Electric Ci

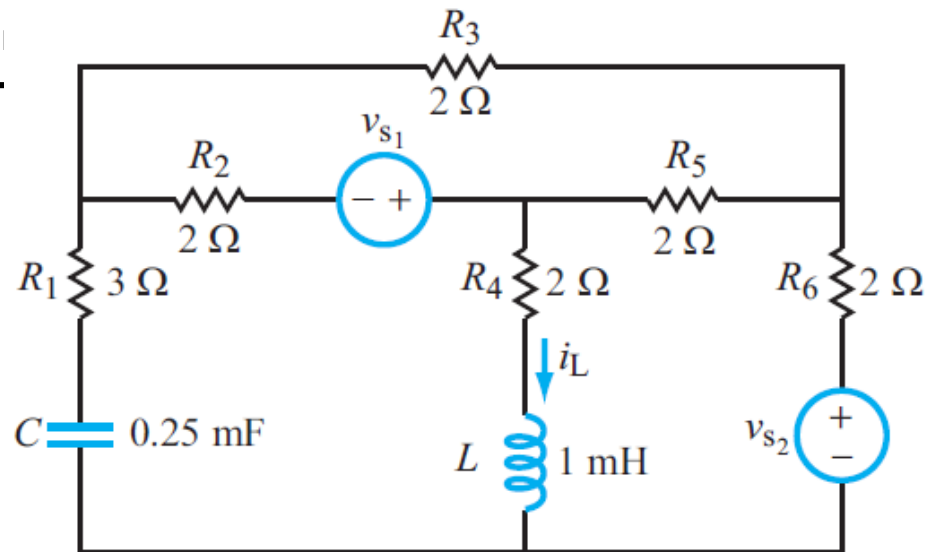

Lecture 7

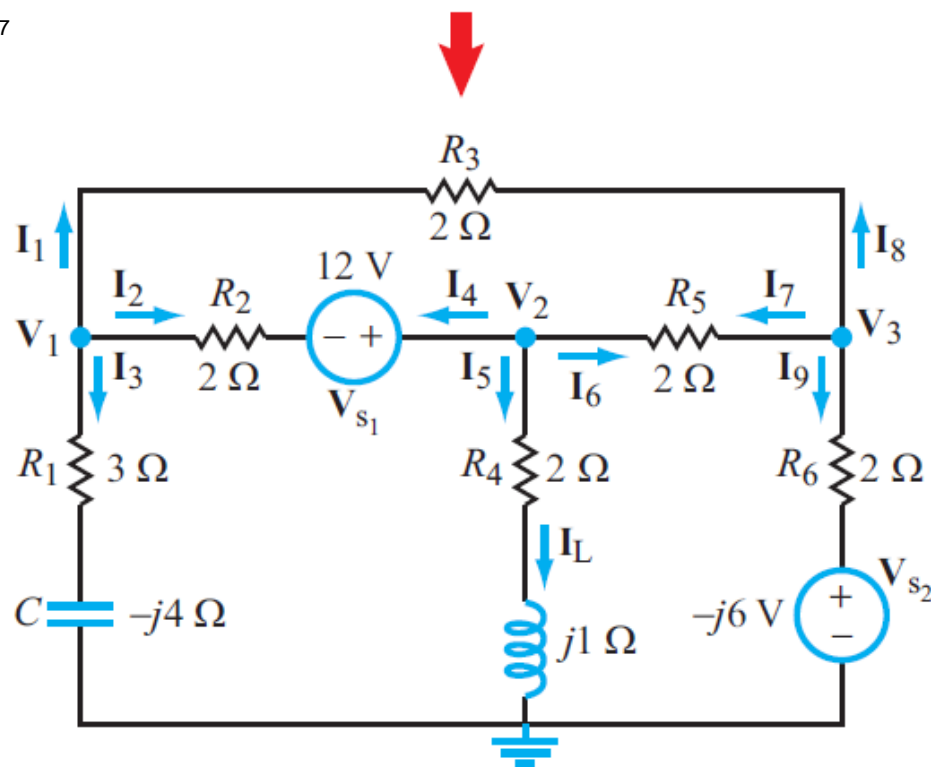

Node 1

Cont.

## Example 7-12: Nodal Analysis (cont.)



School of Information Science and Technology

$$(2.24 + j0.32)V_1 - V_2 - V_3 = -12 \quad (\text{node 1}).$$

Similarly, at node 2,

$$\frac{V_2 - V_1 - 12}{2} + \frac{V_2}{2 + j1} + \frac{V_2 - V_3}{2} = 0,$$

which can be simplified to

$$-V_1 + (2.8 - j0.4)V_2 - V_3 = 12 \quad (\text{node 2}),$$

and at node 3,

$$\frac{V_3 - V_2}{2} + \frac{V_3 - V_1}{2} + \frac{V_3 + j6}{2} = 0,$$

or

$$-V_1 - V_2 + 3V_3 = -j6 \quad (\text{node 3}).$$

Equations (7.112) to (7.114) now are ready to be cast in matrix form:

$$\begin{bmatrix} (2.24 + j0.32) & -1 & -1 \\ -1 & (2.8 - j0.4) & -1 \\ -1 & -1 & 3 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \\ V_3 \end{bmatrix} = \begin{bmatrix} -12 \\ 12 \\ -j6 \end{bmatrix}.$$

Matrix inversion, either manually or by MATLAB<sup>®</sup> provides the solution:


$$V_1 = -(4.72 + j0.88) \text{ V},$$

$$V_2 = (2.46 - j0.89) \text{ V},$$


$$V_3 = -(0.76 + j2.59) \text{ V}.$$

Circuits (Fall 2016)

Pingqiang Zhou

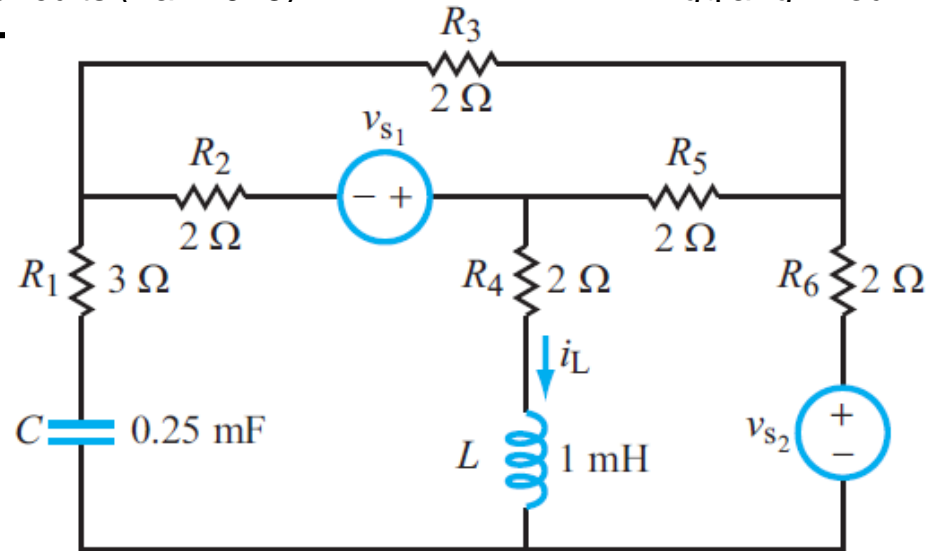

Lecture 7

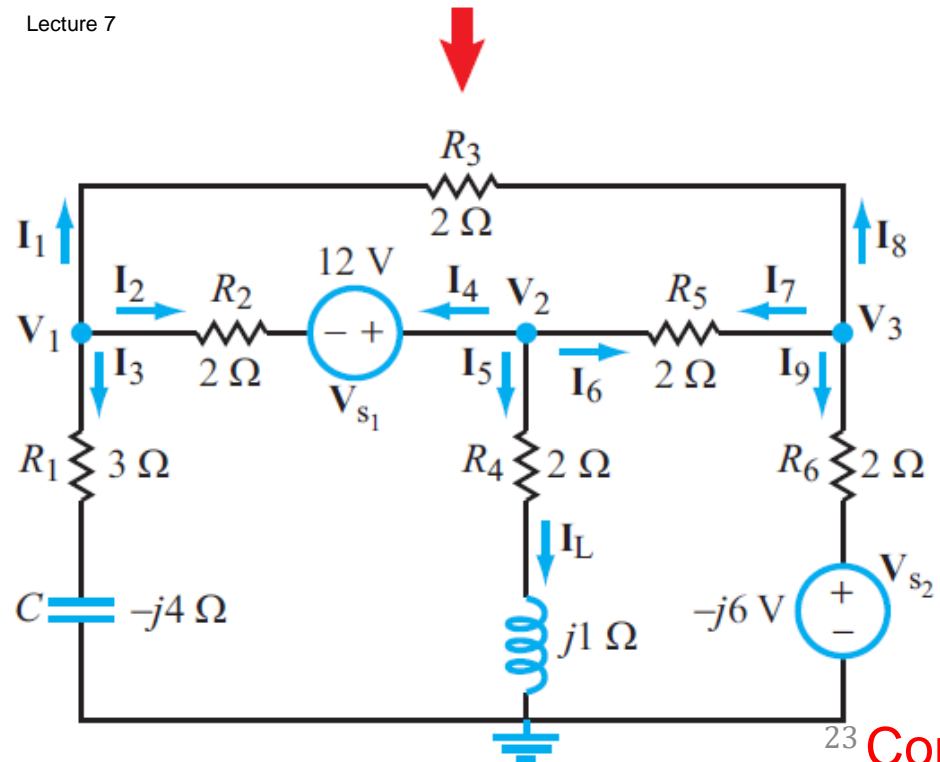



$$\mathbf{V}_3 = -(0.76 + j2.59) \text{ V.}$$

Hence,

$$\begin{aligned} \mathbf{I}_L &= \frac{\mathbf{V}_2}{2 + j1} = \frac{2.46 - j0.89}{2 + j1} \\ &= 0.81 - j0.85 = 1.17e^{-j46.5^\circ} \end{aligned}$$

and its corresponding time-domain counterpart is

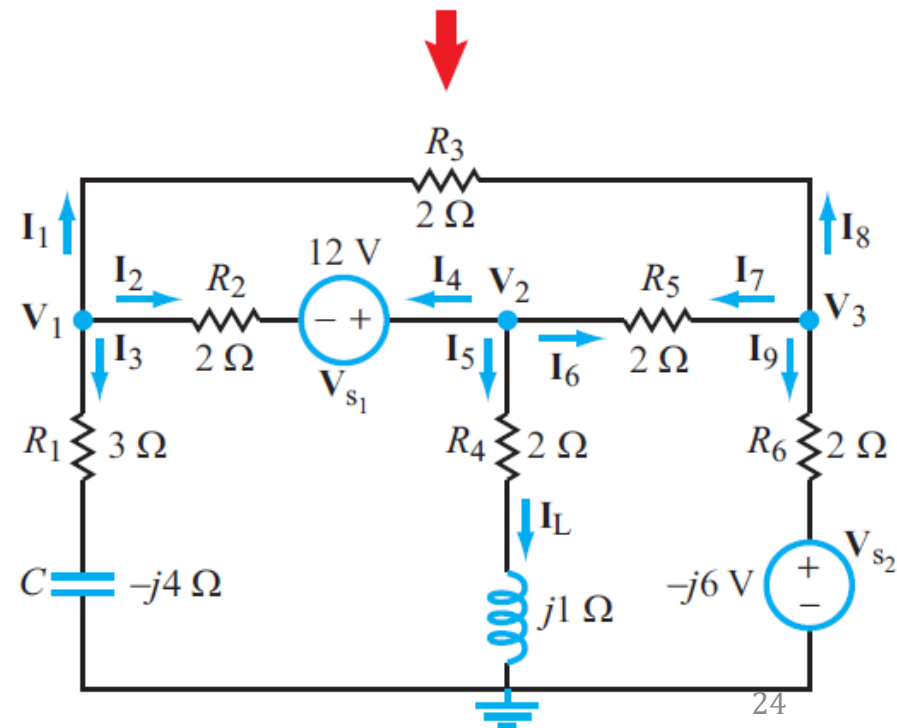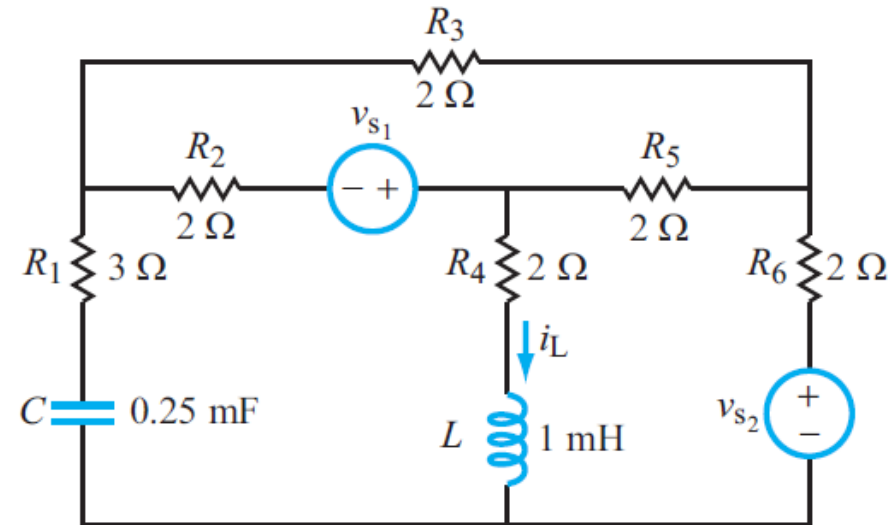
$$\begin{aligned} i_L(t) &= \Re\{\mathbf{I}_L e^{j1000t}\} \\ &= \Re\{1.17e^{-j46.4^\circ} e^{j1000t}\} \\ &= 1.17 \cos(1000t - 46.5^\circ) \text{ A.} \end{aligned}$$






# Mesh Analysis

- Just as in KCL, the KVL analysis also applies to phasor and frequency domain circuits. In KVL, supermesh analysis is also valid.

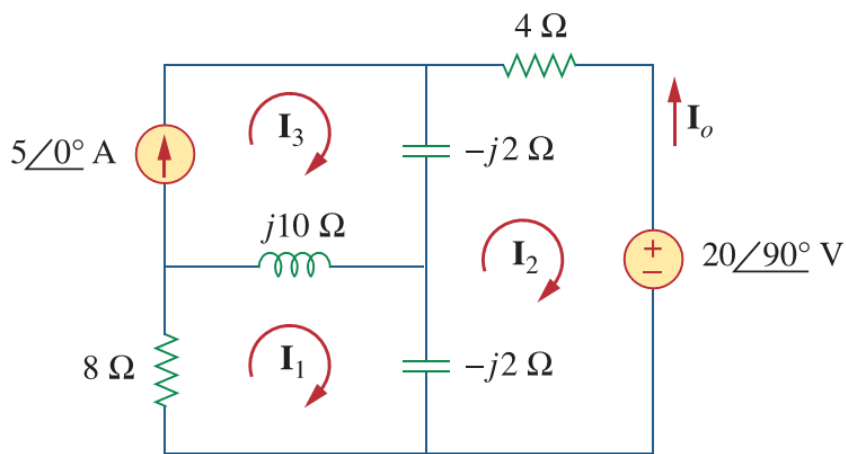

**Figure 10.7**  
For Example 10.3.

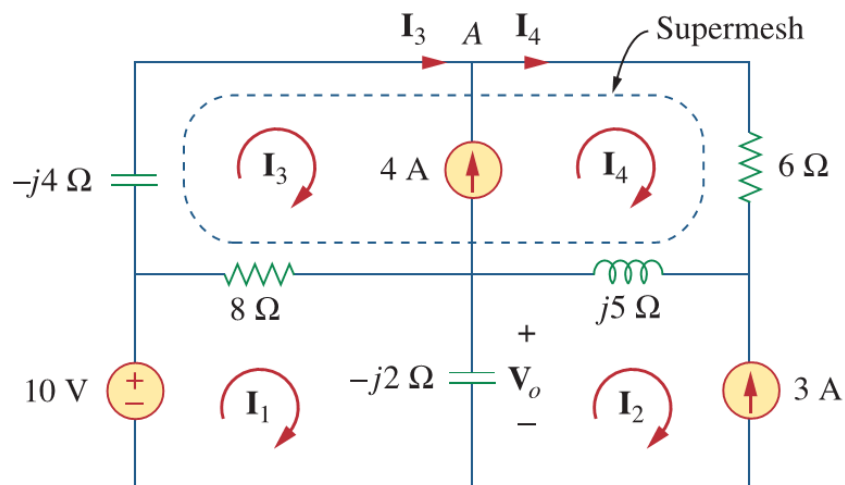

**Figure 10.10**  
Analysis of the circuit in Fig. 10.9.



# Example 7-14: Mesh Analysis by Inspection

$$\begin{bmatrix} \mathbf{Z}_{11} & \mathbf{Z}_{12} & \mathbf{Z}_{13} \\ \mathbf{Z}_{21} & \mathbf{Z}_{22} & \mathbf{Z}_{23} \\ \mathbf{Z}_{31} & \mathbf{Z}_{32} & \mathbf{Z}_{33} \end{bmatrix} \begin{bmatrix} \mathbf{I}_1 \\ \mathbf{I}_2 \\ \mathbf{I}_3 \end{bmatrix} = \begin{bmatrix} \mathbf{V}_{t1} \\ \mathbf{V}_{t2} \\ \mathbf{V}_{t3} \end{bmatrix}$$

$\mathbf{Z}_{kk}$  = sum of all impedances in loop  $k$

$\mathbf{Z}_{k\ell}$  =  $\mathbf{Z}_{\ell k}$  = **negative** of impedance(s) shared by loop  $k$  and  $\ell$ , with  $k \neq \ell$

$\mathbf{I}_k$  = phasor current of loop  $k$

$\mathbf{V}_{tk}$  = total of phasor voltage sources contained in loop  $k$ , with the polarity defined as positive if  $\mathbf{I}_k$  flows from  $(-)$  to  $(+)$  through the source.

In view of these definitions, the matrix equation for the circuit in Fig. 7-28 is given by

$$\begin{bmatrix} (7 - j3) & -(2 + j1) & -2 \\ -(2 + j1) & (6 + j1) & -2 \\ -2 & -2 & 6 \end{bmatrix} \begin{bmatrix} \mathbf{I}_1 \\ \mathbf{I}_2 \\ \mathbf{I}_3 \end{bmatrix} = \begin{bmatrix} 12 \\ j6 \\ -12 \end{bmatrix}.$$


Matrix inversion leads to

$$\mathbf{I}_1 = (0.43 + j0.86) \text{ A},$$

$$\mathbf{I}_2 = (-0.38 + j1.71) \text{ A},$$

and
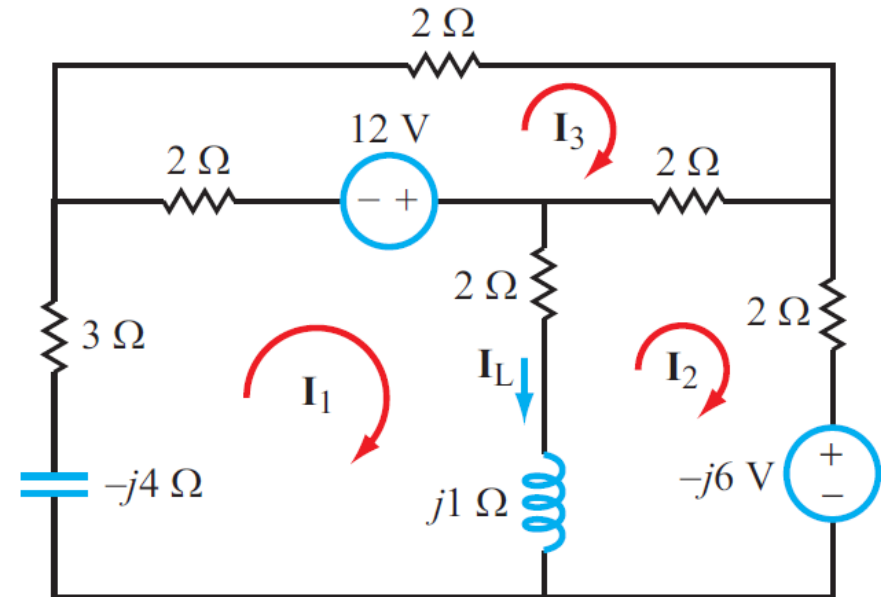
$$\mathbf{I}_3 = (-1.98 + j0.86) \text{ A}.$$



$$\begin{aligned} \mathbf{I}_L &= \mathbf{I}_1 - \mathbf{I}_2 = (0.43 + j0.86) - (-0.38 + j1.71) \\ &= 0.81 - j0.85 = 1.17e^{-j46.4^\circ} \text{ A}, \end{aligned}$$

and its time-domain counterpart is

$$\begin{aligned} i_L(t) &= \Re\{\mathbf{I}_L e^{j\omega t}\} = \Re[1.17e^{-j46.4^\circ} e^{j1000t}] \\ &= 1.17 \cos(1000t - 46.4^\circ) \text{ A}. \end{aligned}$$




# Outline

- ~~Nodal/Mesh analysis~~
- Superposition
- Source transformation/Thevenin/Norton
- Applications





# Superposition


- Since AC circuits are linear, it is also possible to apply the principle of superposition.

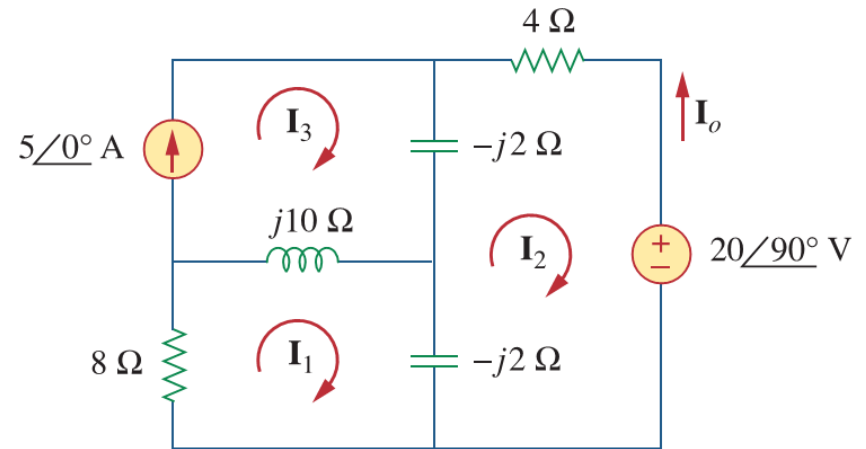

**Figure 10.7**

For Example 10.3.

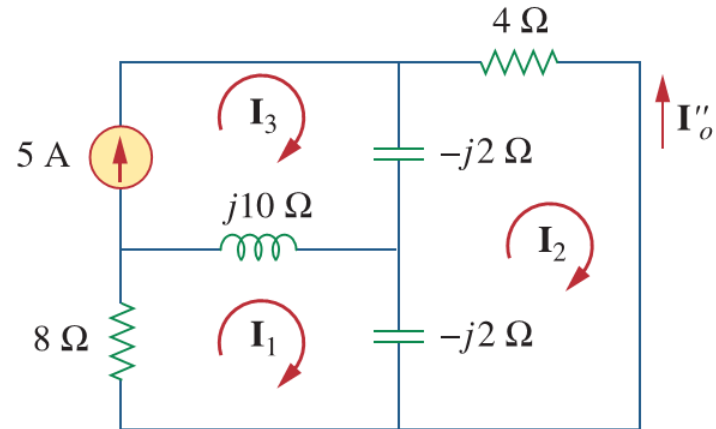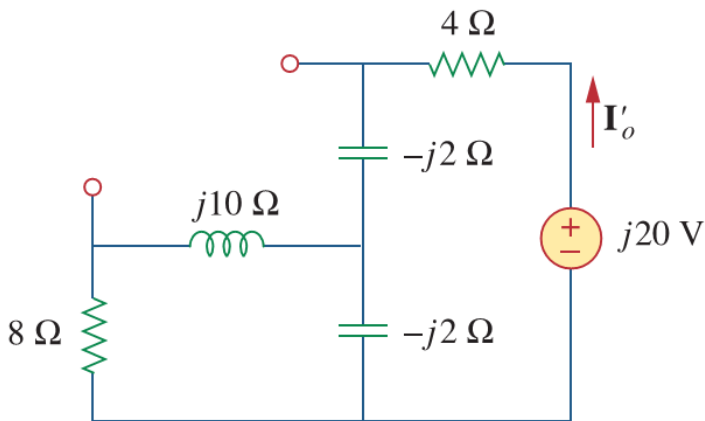

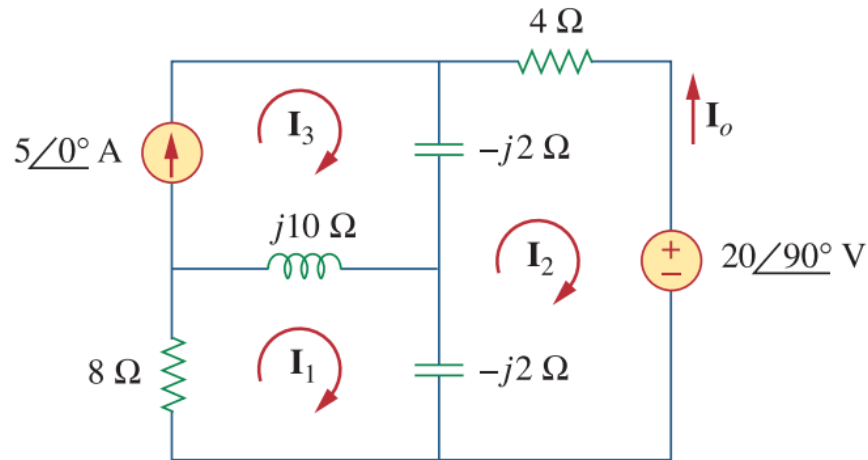

where  $\mathbf{I}'_o$  and  $\mathbf{I}''_o$  are due to the voltage and current sources, respectively. To find  $\mathbf{I}'_o$ , consider the circuit in Fig. 10.12(a). If we let  $\mathbf{Z}$  be the parallel combination of  $-j2$  and  $8 + j10$ , then

$$\mathbf{Z} = \frac{-j2(8 + j10)}{-2j + 8 + j10} = 0.25 - j2.25$$

and current  $\mathbf{I}'_o$  is

$$\mathbf{I}'_o = \frac{j20}{4 - j2 + \mathbf{Z}} = \frac{j20}{4.25 - j4.25}$$

or

$$\mathbf{I}'_o = -2.353 + j2.353 \quad (10.5.2)$$

To get  $\mathbf{I}''_o$ , consider the circuit in Fig. 10.12(b). For mesh 1,

$$(8 + j8)\mathbf{I}_1 - j10\mathbf{I}_3 + j2\mathbf{I}_2 = 0 \quad (10.5.3)$$

For mesh 2,

$$(4 - j4)\mathbf{I}_2 + j2\mathbf{I}_1 + j2\mathbf{I}_3 = 0 \quad (10.5.4)$$

For mesh 3,

$$\mathbf{I}_3 = 5 \quad (10.5.5)$$

From Eqs. (10.5.4) and (10.5.5),

$$(4 - j4)\mathbf{I}_2 + j2\mathbf{I}_1 + j10 = 0$$

Expressing  $\mathbf{I}_1$  in terms of  $\mathbf{I}_2$  gives

$$\mathbf{I}_1 = (2 + j2)\mathbf{I}_2 - 5 \quad (10.5.6)$$

Substituting Eqs. (10.5.5) and (10.5.6) into Eq. (10.5.3), we get

$$(8 + j8)[(2 + j2)\mathbf{I}_2 - 5] - j50 + j2\mathbf{I}_2 = 0$$

or

$$\mathbf{I}_2 = \frac{90 - j40}{34} = 2.647 - j1.176$$

Current  $\mathbf{I}''_o$  is obtained as


$$\mathbf{I}''_o = -\mathbf{I}_2 = -2.647 + j1.176 \quad (10.5.7)$$

From Eqs. (10.5.2) and (10.5.7), we write

$$\mathbf{I}_o = \mathbf{I}'_o + \mathbf{I}''_o = -5 + j3.529 = 6.12 \angle 144.78^\circ \text{ A}$$
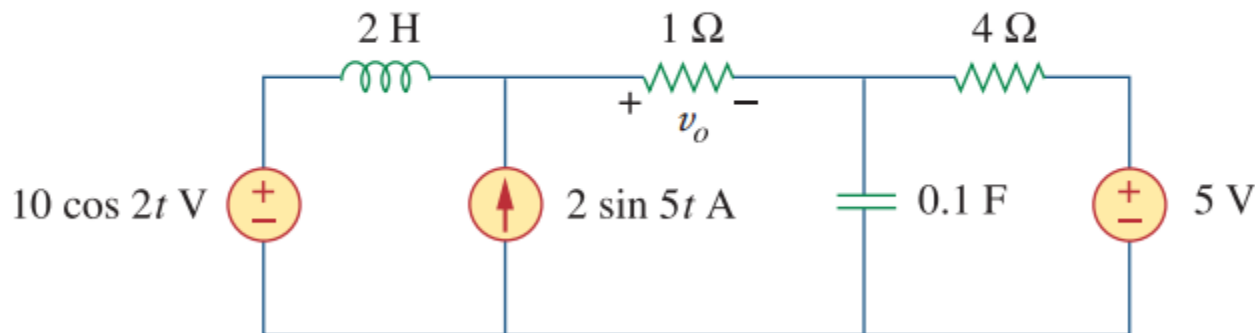
## Superposition II


Find  $v_o$  of the circuit of Fig. 10.13 using the superposition theorem.




- What happens if the sources are at different frequencies?
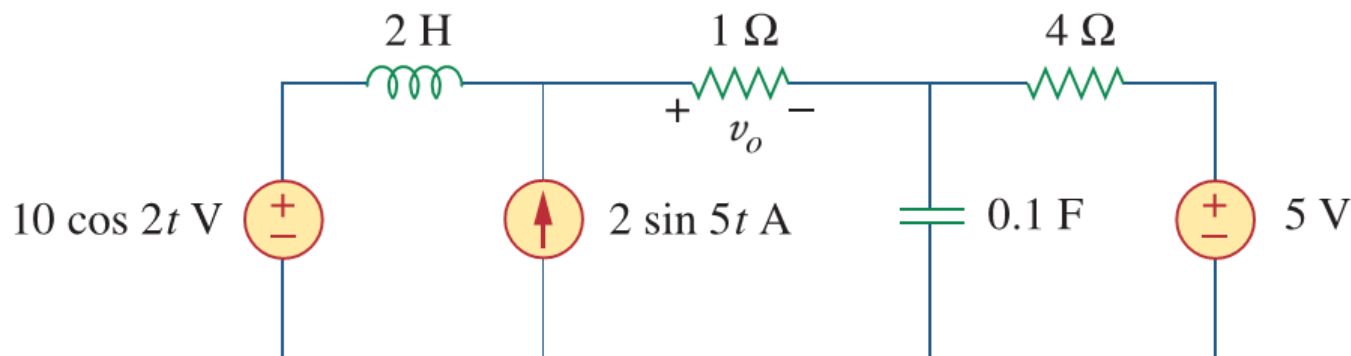
# Superposition II


- Particularly important when the circuit has sources operating at different frequencies.
  - The complication is that each source must have its own frequency domain equivalent circuit, because each element has a different impedance at different frequencies.
  - Also, the resulting voltages and current must be converted back to time domain before being added. This is because there is an exponential factor  $e^{j\omega t}$  implicit in sinusoidal analysis.



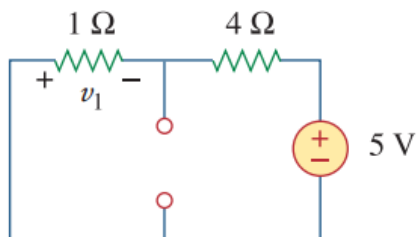

(a)

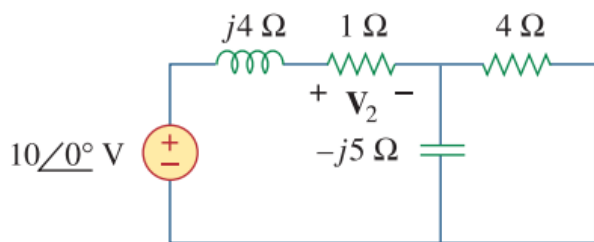
$$-v_1 = \frac{1}{1+4}(5) = 1 \text{ V}$$



(b)

$$\mathbf{V}_2 = \frac{1}{1+j4+\mathbf{Z}}(10\angle 0^\circ) = \frac{10}{3.439+j2.049} = 2.498\angle -30.79^\circ$$

$$v_2 = 2.498 \cos(2t - 30.79^\circ)$$

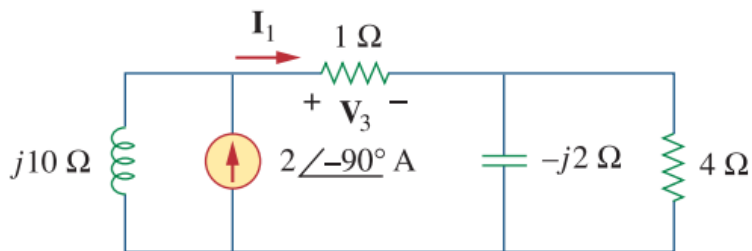

(c)

$$\mathbf{I}_1 = \frac{j10}{j10+1+\mathbf{Z}_1}(2\angle -90^\circ) \text{ A}$$

$$\mathbf{V}_3 = \mathbf{I}_1 \times 1 = \frac{j10}{1.8+j8.4}(-j2) = 2.328\angle -80^\circ \text{ V}$$

$$v_3 = 2.33 \cos(5t - 80^\circ) = 2.33 \sin(5t + 10^\circ) \text{ V}$$






# Outline

- ~~Nodal/Mesh analysis~~
- ~~Superposition~~
- Source transformation/Thevenin/Norton
- Applications
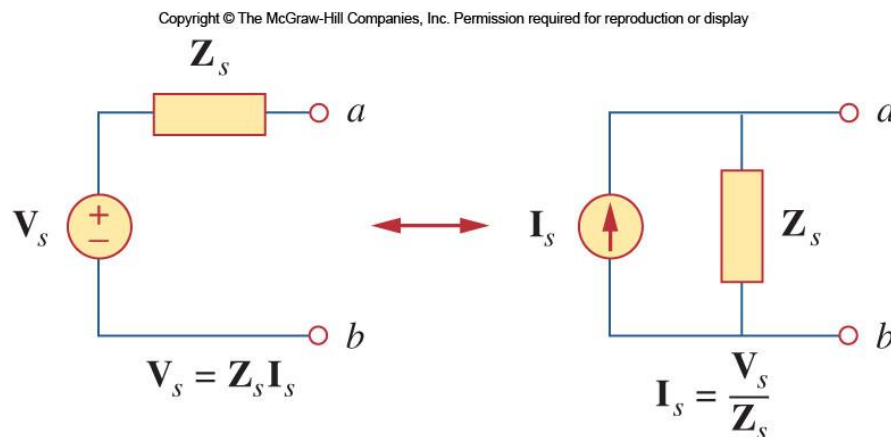
# Source Transformation


- Source transformation in frequency domain involves transforming a voltage source in series with an impedance to a current source in parallel with an impedance.
- Or vice versa:

$$V_s = Z_s I_s \Leftrightarrow I_s = \frac{V_s}{Z_s}$$


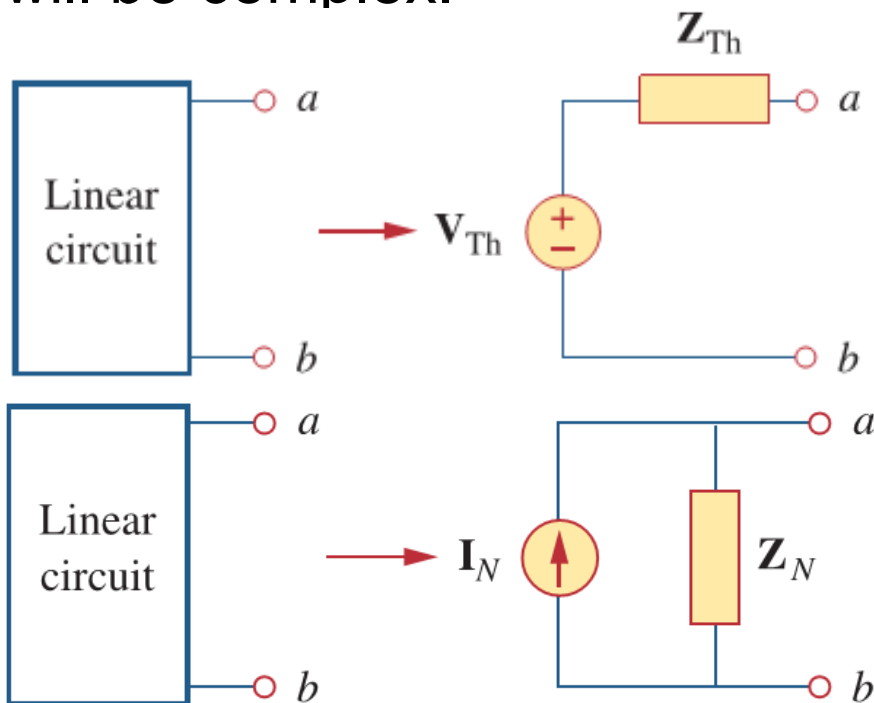
# Thevenin and Norton Equivalency




- Both Thevenin and Norton's theorems are applied to AC circuits the same way as DC.
- The only difference is the fact that the calculated values will be complex.



$$V_{Th} = Z_N I_N, \quad Z_{Th} = Z_N$$









## Example

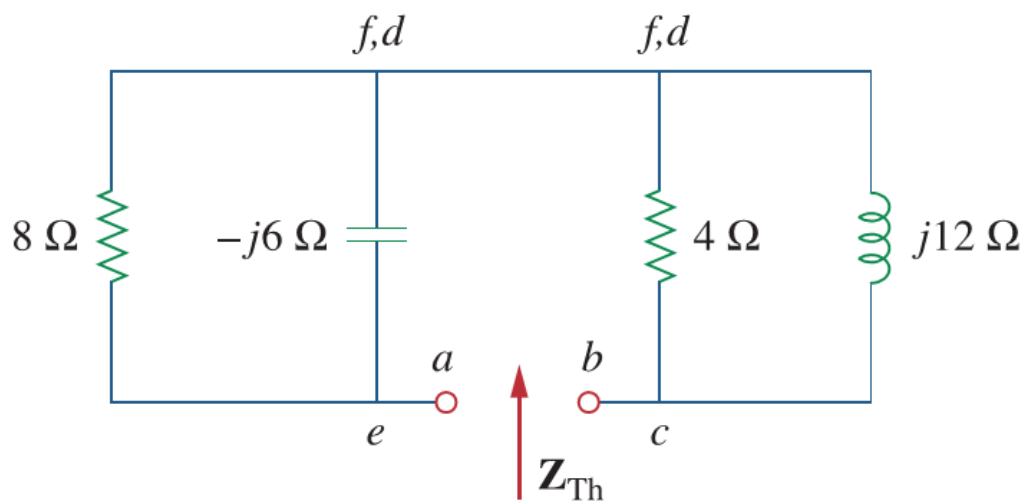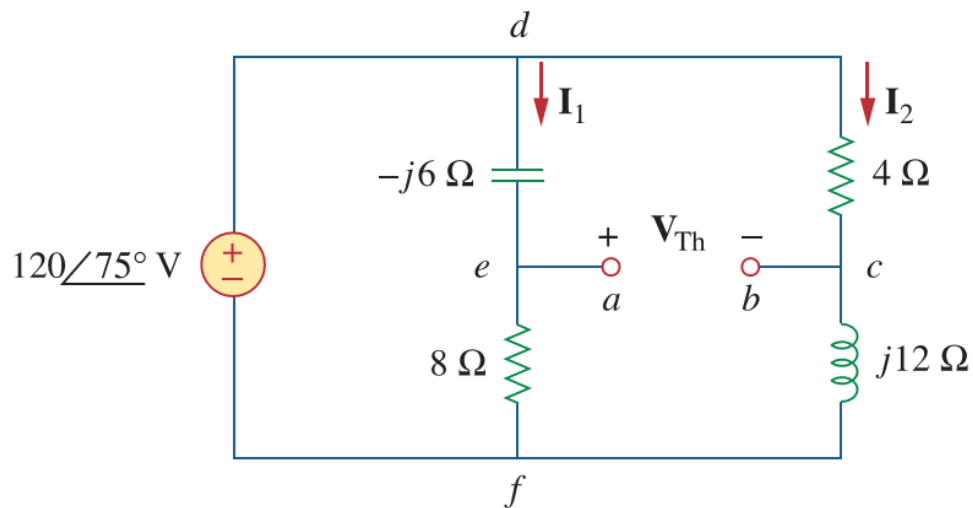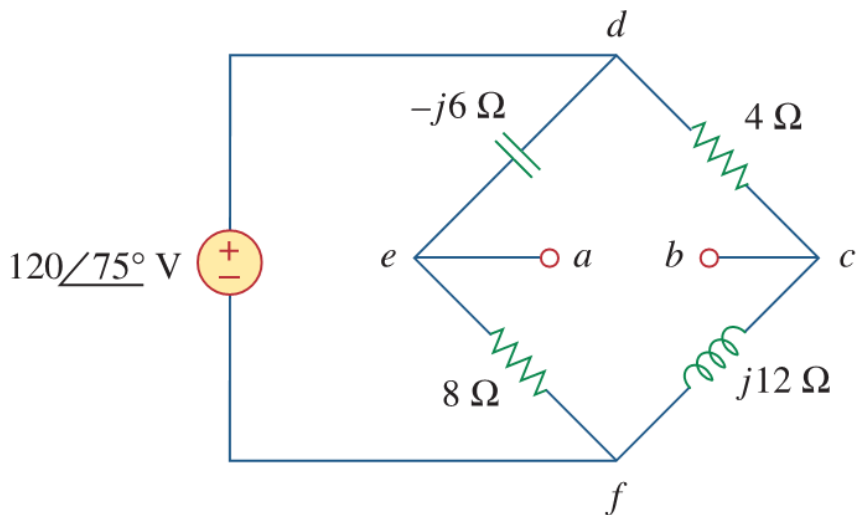



## Example 7-9: Thévenin Circuit

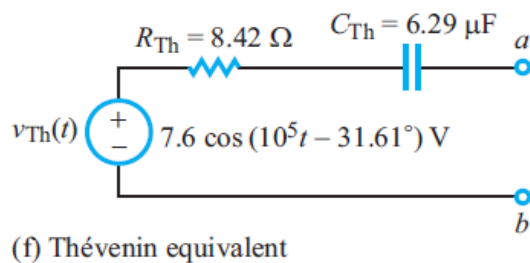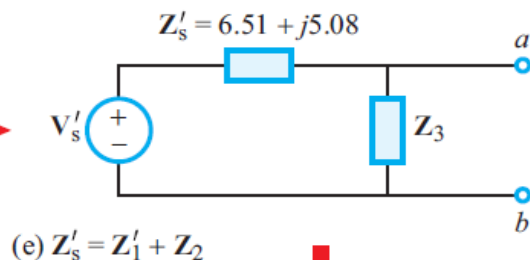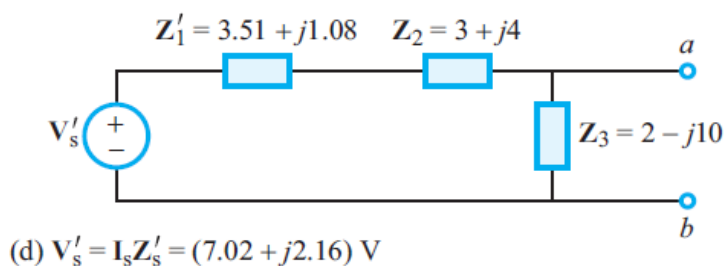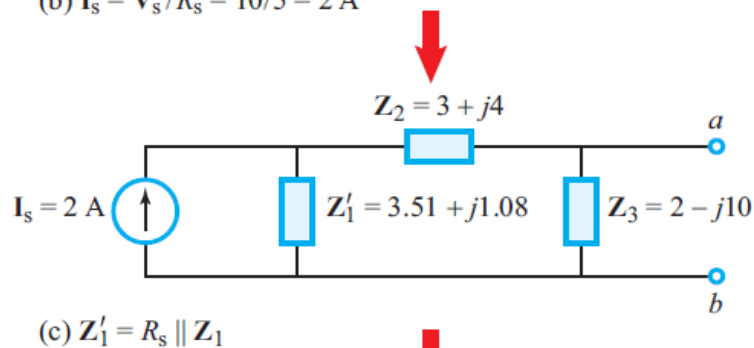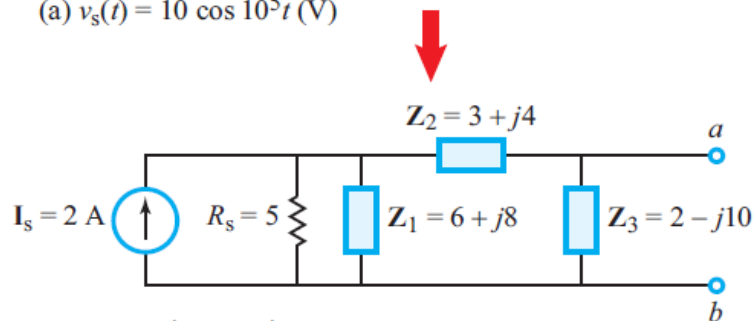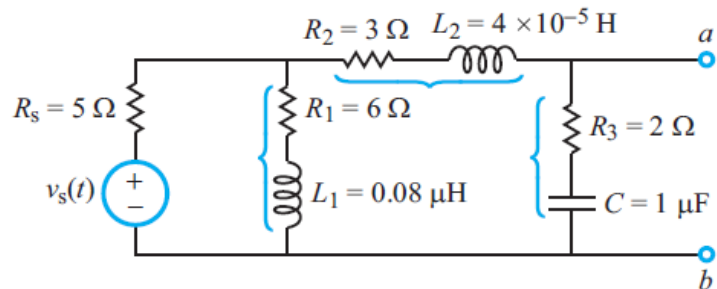

$$Z_{Th} = Z'_s \parallel Z_3$$

$$= \frac{(6.51 + j5.08)(2 - j10)}{(6.51 + j5.08) + (2 - j10)} = (8.42 - j1.59) \Omega$$

$$R_{Th} = 8.42 \Omega, \quad C_{Th} = \frac{1}{1.59\omega} = 6.29 \mu F$$




# Outline

- ~~Nodal/Mesh analysis~~
- ~~Superposition~~
- ~~Source transformation/Thevenin/Norton~~
- Applications



## Application: AC Bridges

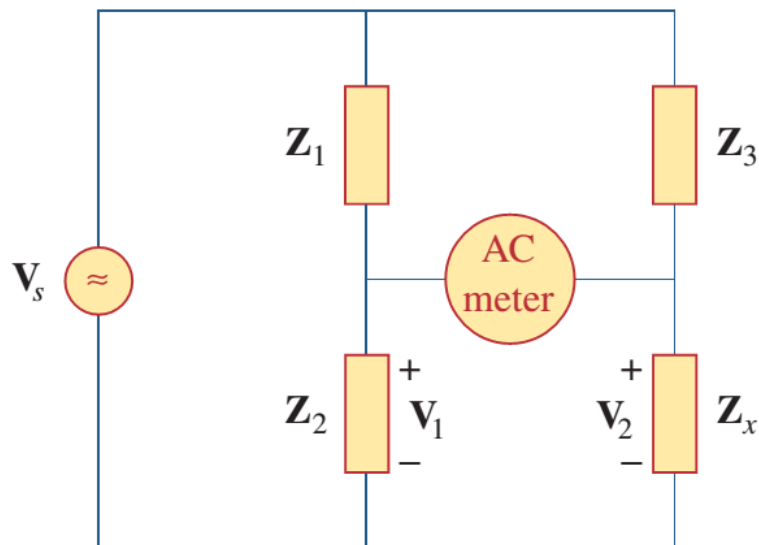

$$V_1 = \frac{Z_2}{Z_1 + Z_2} V_s = V_2 = \frac{Z_x}{Z_3 + Z_x} V_s$$



$$Z_x = \frac{Z_3}{Z_1} Z_2$$



# AC Op Amp Circuits

**Question 1:** Are op amps used in ac circuits?

**Answer 1:** Yes.

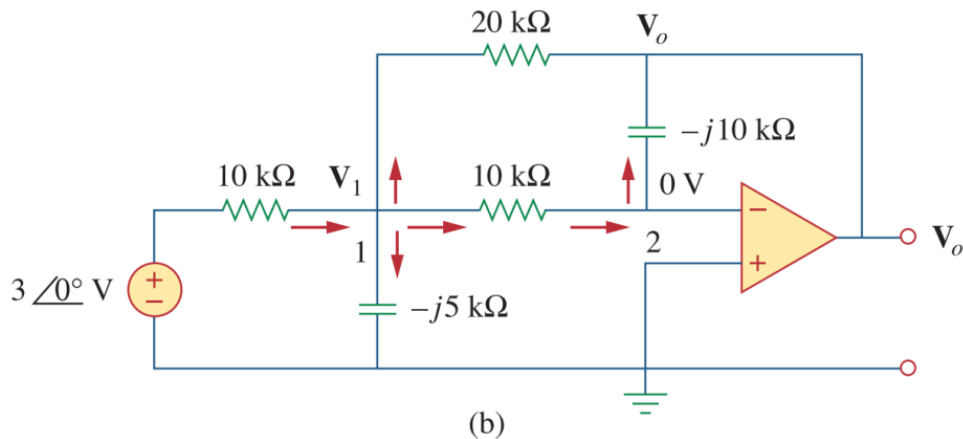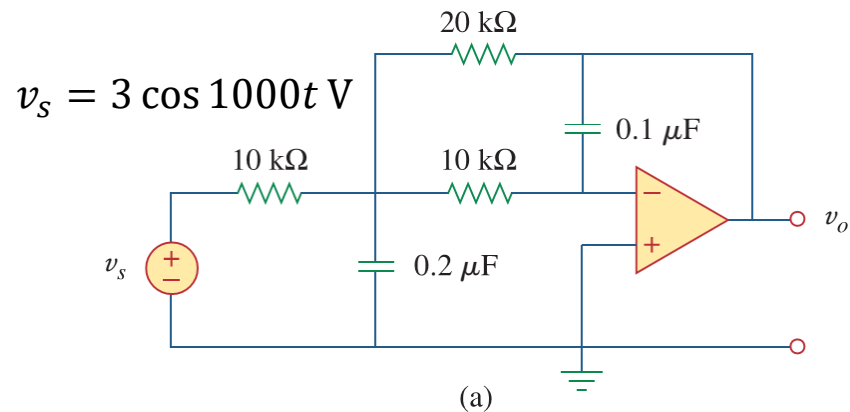





**Solution:**

We first transform the circuit to the frequency domain, as shown in Fig. 10.31(b), where  $\mathbf{V}_s = 3\angle 0^\circ$ ,  $\omega = 1000$  rad/s. Applying KCL at node 1, we obtain

$$\frac{3\angle 0^\circ - \mathbf{V}_1}{10} = \frac{\mathbf{V}_1}{-j5} + \frac{\mathbf{V}_1 - 0}{10} + \frac{\mathbf{V}_1 - \mathbf{V}_o}{20}$$

or

$$6 = (5 + j4)\mathbf{V}_1 - \mathbf{V}_o \quad (10.11.1)$$

At node 2, KCL gives

$$\frac{\mathbf{V}_1 - 0}{10} = \frac{0 - \mathbf{V}_o}{-j10}$$

which leads to

$$\mathbf{V}_1 = -j\mathbf{V}_o \quad (10.11.2)$$

Substituting Eq. (10.11.2) into Eq. (10.11.1) yields

$$6 = -j(5 + j4)\mathbf{V}_o - \mathbf{V}_o = (3 - j5)\mathbf{V}_o$$

$$\mathbf{V}_o = \frac{6}{3 - j5} = 1.029\angle 59.04^\circ$$

Hence,




$$v_o(t) = 1.029 \cos(1000t + 59.04^\circ) \text{ V}$$



**Question 2:** Is the ideal op-amp model applicable to ac circuits?


**Answer 2:** The ideal op-amp model is based on the assumption that the open-loop gain  $A$  is very large ( $> 10^4$ ), which is true at dc and low frequencies, but not necessarily so at high frequencies. The range of frequencies over which  $A$  is large depends on the specific op-amp design. As we shall see later on

# AC Op-Amp

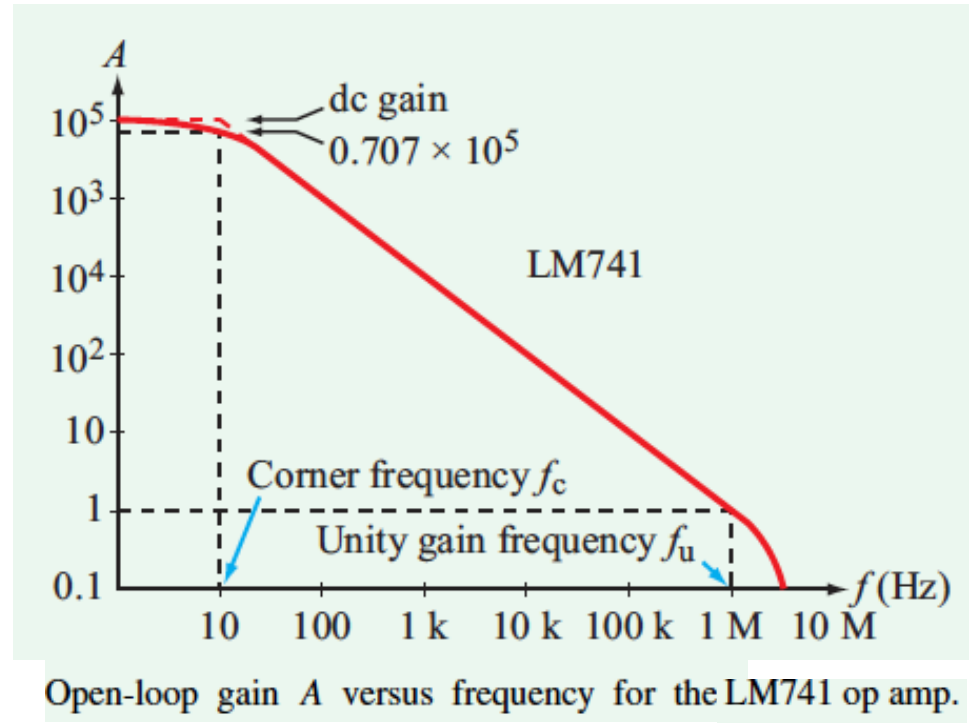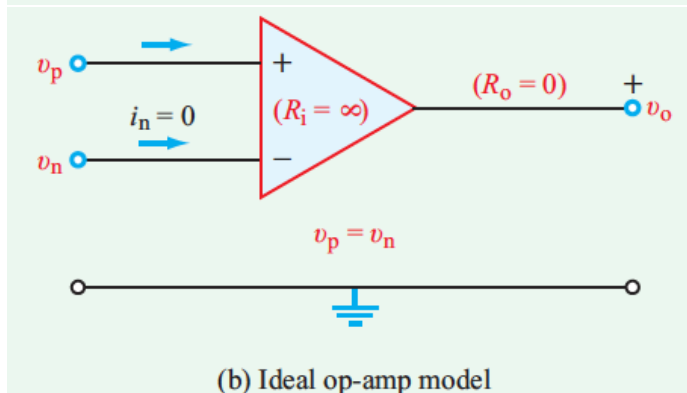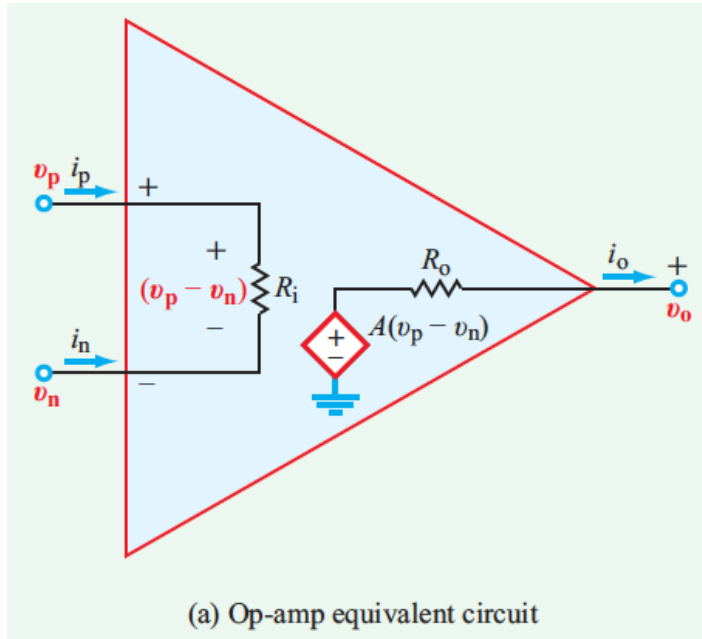


See more at  
<http://www.matni.com/Arabic/Elec-Info/LM741%20DETAILS/741.html>

# Example

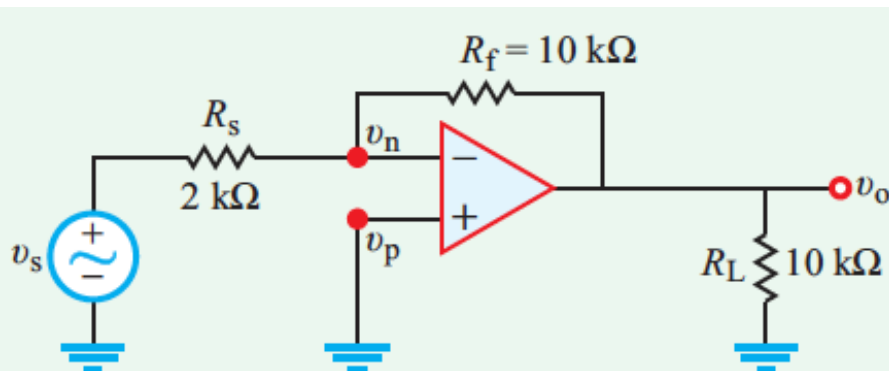

(a) Inverting amplifier circuit

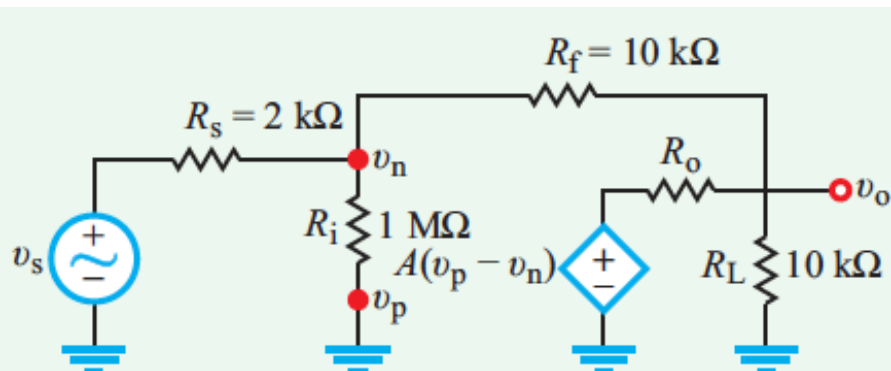


(b) Equivalent circuit model

$$\frac{v_n - v_s}{R_s} + \frac{v_n}{R_i} + \frac{v_n - v_o}{R_f} = 0,$$

$$\frac{v_o - v_n}{R_f} + \frac{v_o - A(v_p - v_n)}{R_o} + \frac{v_o}{R_L} = 0.$$

$$G = \frac{v_o}{v_s} = \frac{R_f}{R_s}$$
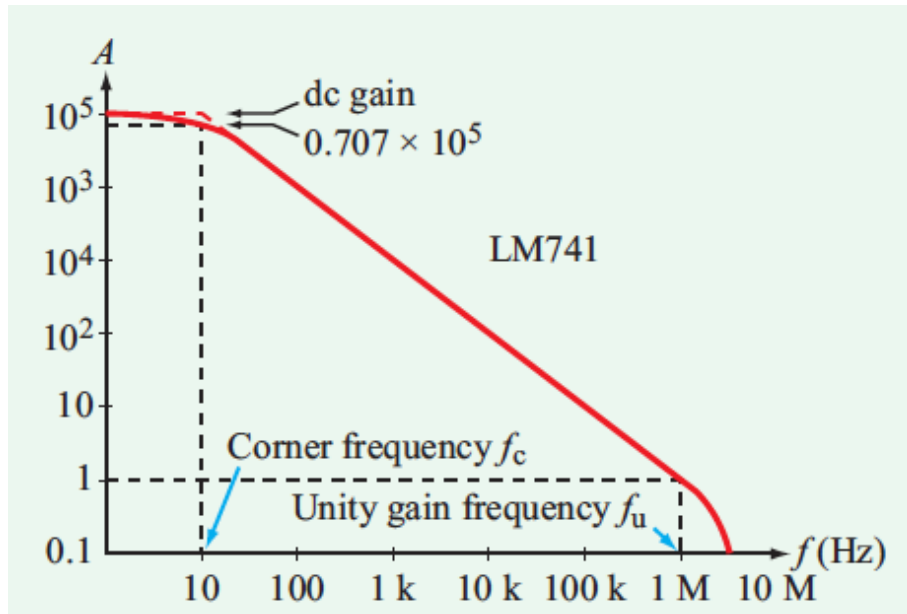
$$\left[ \frac{R_s R_i (R_o - A R_f)}{(R_L R_o + R_f R_L + R_f R_o)(R_i R_f + R_s R_f + R_s R_i) - R_s R_i (R_o - A R_f)} \right]$$



Open-loop gain  $A$  versus frequency for the LM741 op amp.

$f$ (Hz)	$A$	$G$	Error
0 (dc)	$10^5$	-4.997	0.06%
100	$10^4$	-4.970	0.6%
1 k	$10^3$	-4.714	5.7%
10 k	$10^2$	-3.111	37.8%
100 k	10	-0.707	85.9%
1 M	1	-0.081	98.4%

The error is defined as  $G_{\text{ideal}} = -5$

$$\% \text{ error} = \left( \frac{G_{\text{ideal}} - G}{G_{\text{ideal}}} \right) \times 100.$$

**Audio:** dc to 1 kHz: Minor distortion      **Video:** Up to 1 MHz: Serious distortion

**Conclusion:** The LM741 model is not suitable for video signals; it is necessary to use an Op-amp model with a higher corner frequency.