

Homework 10

Due date: Jun. 13th, 2018
Turn in your homework in class

Rules:

- Work on your own. Discussion is permissible, but extremely similar submissions will be judged as plagiarism.
- Please show all intermediate steps: a correct solution without an explanation will get zero credit.
- Please submit on time. No late submission will be accepted.
- Please prepare your submission in English only. No Chinese submission will be accepted.

1. (20%) Find the Laplace transform of each of the following functions:

(a). $f(t) = 20e^{-500(t-10)}u(t-10)$.

(b). $f(t) = (5t + 20)[u(t + 4) - u(t + 2)] - 5t[u(t + 2) - u(t - 2)] - 10u(t - 2)$.

2. (20%) Find $f(t)$ for each of the following functions:

(a). $F(s) = \frac{6(s+10)}{(s+5)(s+8)}$

(b). $F(s) = \frac{320}{s^2(s+8)}$

(c). $F(s) = \frac{8(s+1)^2}{(s^2+10s+34)(s^2+8s+20)}$

(d). $F(s) = \frac{25(s+4)^2}{s^2(s+5)^2}$

3. (20%) Find V_0 (s domain) and v_0 (time domain) in the circuit shown in Fig.1 if the initial energy is zero and the switch is closed at $t = 0$.

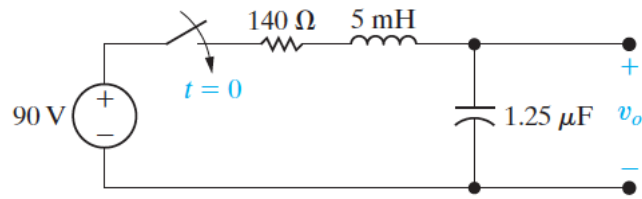


Fig.1

4. The switch in the circuit in Fig.2 has been closed for a long time. At $t = 0$ the switch is opened.
- (a). Find i_o for $t \geq 0$.
- (b). Find v_o for $t \geq 0$.

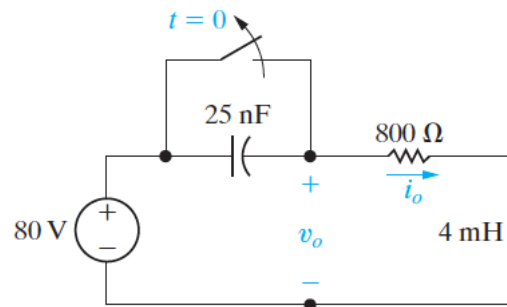


Fig.2

5. The switch in the circuit in Fig.3 has been closed for a long time before opening at $t = 0$. Find v_o for $t \geq 0$.

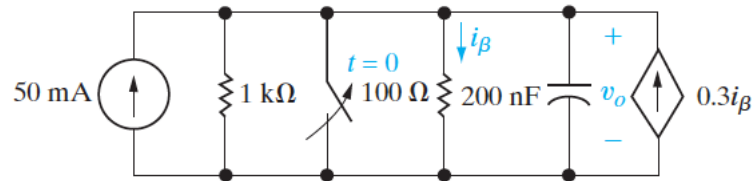


Fig.3