

Student Name: _____ Student Number: _____

EE 111 Electric Circuits Midterm-Fall 2021

Nov 11 2021, 8:15 AM – 9:55 AM

6 problems in total (1 A4 crib sheet allowed)

Answer the Questions in English and on Answer Sheets only

Copy and Re-draw the circuits on Answer Sheets for all problems

Two-decimal policy applies for the final answer

1. (16 points) For the circuit shown in Fig.1, use mesh-current method to find i_b .

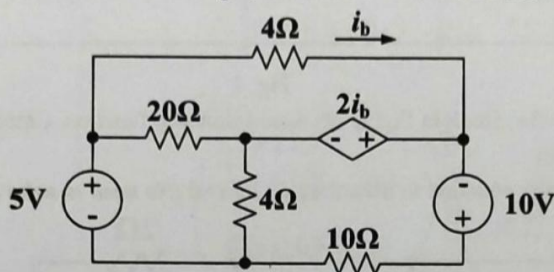


Fig. 1

2. (16 points) The variable dc current source i_{dc} in Fig.2 can be adjusted. Find the value of i_{dc} so that the power absorbed by the 4A current source is zero. (Hint: determine if there is any current through the 40-Ω resistor, and then you may use nodal analysis method)

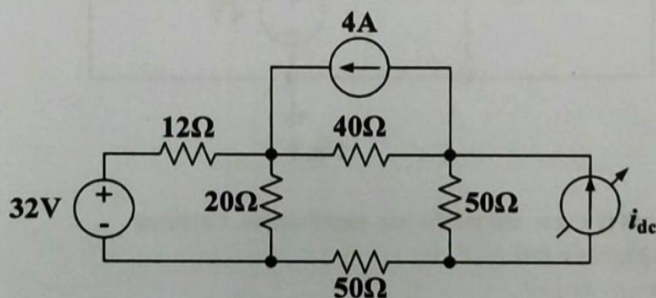


Fig. 2

3. (16 points) Find the Thevenin equivalent OR Norton equivalent with respect to the terminal a and b for the circuit in Fig.3.

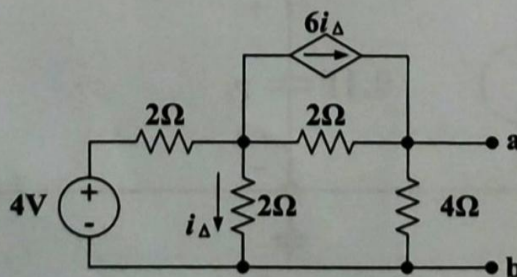


Fig. 3

4. (16 points) There is no energy stored in the capacitor when Switch 1 closes at $t = 0$. Twenty milliseconds (20ms) later, Switch 2 is closed, as shown in Fig.4. Find $v_o(t)$ for $t > 0$ and sketch it in one graph.

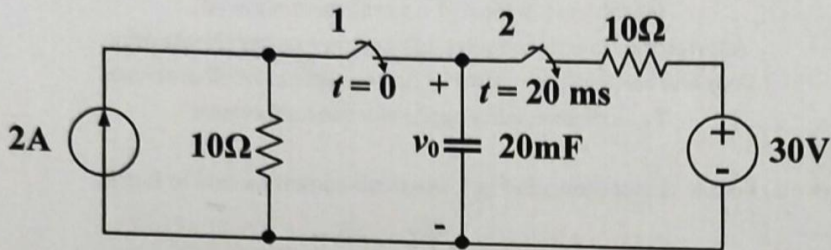


Fig. 4

5. (16 points) For the circuit in Fig.5, $u(t)$ means unit step function. Calculate
 (a) $i_L(0^+)$, $di_L(0^+)/dt$
 (b) Find the 2nd-order equation to describe $i_L(t)$ for $t > 0$ (No need to solve it)

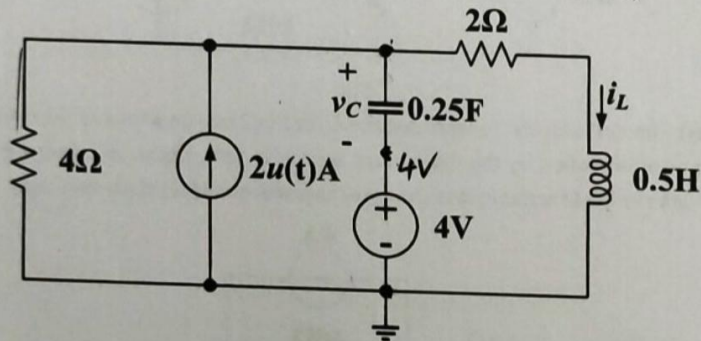


Fig. 5

6. For the circuit in Fig.6, $u(t)$ means unit step function. Calculate
 (15 points) (a) $i_L(t)$ for $t > 0$
 (5 points) (b) $v_c(t)$ for $t > 0$


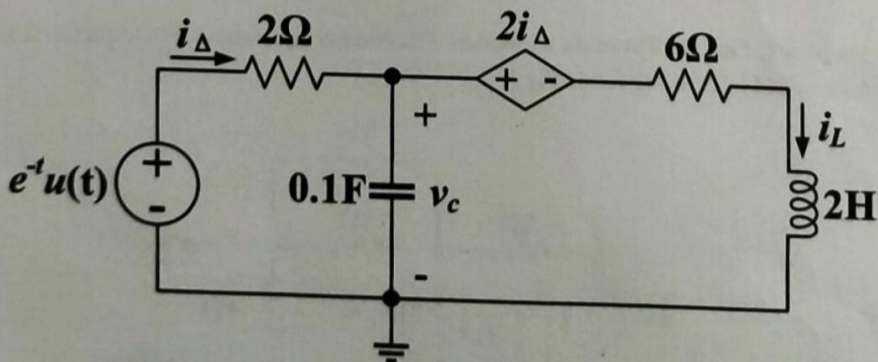


Fig. 6

Student Name: _____ Student Number: _____

16'

Solution of Problem 1

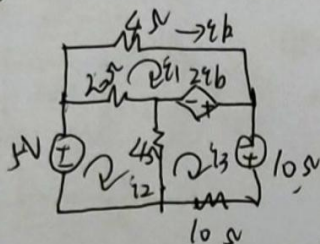

$$i_b = i_1$$

$$20(i_b - i_2) + 4i_b + 2i_b = 0 \quad 3'$$

$$20(i_2 - i_b) + 4(i_2 - i_3) - 5 = 0 \quad 3'$$

$$10i_3 + 4(i_3 - i_2) - 2i_b - 10 = 0 \quad 3'$$

$$\Rightarrow i_b = 0.86 \text{ (A)} \quad 3'$$


$$\begin{pmatrix} i_2 = 1.12 \text{ (A)} \\ i_3 = 1.16 \text{ (A)} \end{pmatrix} \leftarrow \begin{matrix} 3' \\ 7.129 \end{matrix}$$

16'

Student Name: _____

Student Number: _____

Solution of Problem 2

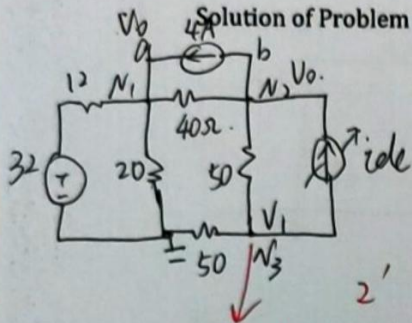

如果这个接地

$$\text{所以 } i_{dc} = 6.5 \text{ A}$$

Because the power absorbed by 4A is 0W.
the voltage on the terminals a and b is 0V.

Suppose the voltage on terminal a is V_0 , N_3 is V_1 .


Apply KCL to Nodes 1 and 2 and 3.

$$\begin{cases} \frac{32 - V_0}{12} + 4A = \frac{V_0 - 0}{20\Omega} & 3' \\ -4A + i_{dc} = \frac{V_0 - V_1}{40\Omega} & 3' \\ -i_{dc} + \frac{V_0 - V_1}{50\Omega} = \frac{V_1}{50\Omega} & 3' \end{cases} \Rightarrow \begin{cases} V_0 = 50V \\ V_1 = -200V \\ i_{dc} = 9A \end{cases} \quad 3'$$

Student Name: _____

Student Number: _____

Solution of Problem 3

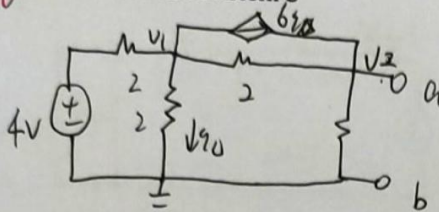

Apply KCL

$$\begin{cases} \frac{V_1 - 4}{2} + i_D + \frac{V_1 - V_2}{2} + 6i_D = 0 & (1) \\ \frac{V_1}{2} = i_D & (2) \\ \frac{V_2 - V_1}{2} - 6i_D + \frac{V_2}{4} = 0 & (3) \end{cases}$$

$$\Rightarrow V_1 = \frac{12}{13} (V) = 0.92 (V)$$

$$V_2 = \frac{56}{13} (V) = 4.31 (V)$$

$$V_{OC} = V_2 = 4.31 (V)$$

$$\Rightarrow V_C = \frac{4}{9} (V)$$



$$i_D = \frac{2}{9} (A)$$

$$i_{SC} = \frac{14}{9} (A) \approx 1.56 (A)$$

(if you draw Norton equivalent, you need to write it as a decimal.)

$$R_{Th} = \frac{V_{OC}}{i_{SC}} = \frac{\frac{56}{13}}{\frac{14}{9}} = \frac{36}{13} \approx 2.77 (\Omega)$$



Thevenin equivalent

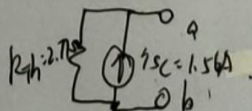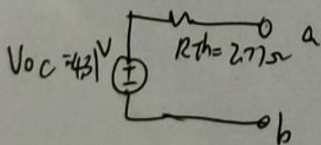

Student Name: _____


Student Number: _____

16' Solution of Problem 4

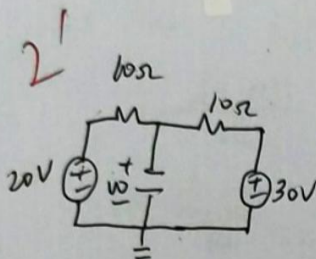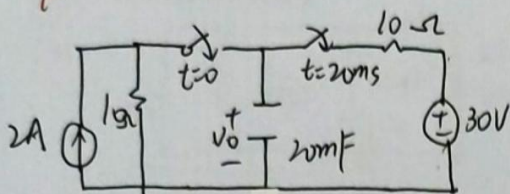

$$t=0s: V_C(0^+) = V_C(0^-) = 0V \quad 1'$$
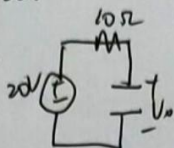
$$20 = V_0(t) + 10 \cdot C \frac{dV_0(t)}{dt}$$



$$\frac{dV_0(t)}{dt} + 5V_0(t) = 100 \quad 2'$$

$$V_0(t) = 20 + e^{-5t} (0 - 20) = 20 - 20e^{-5t} (V) \quad 3'$$

$$t = 20ms \quad V_0(0.02) = 20 - 20e^{-0.1} (V)$$

$$t = 20ms: KCL: \frac{20 - V_0(t)}{10} + \frac{30 - V_0(t)}{10} = C \frac{dV_0(t)}{dt} \quad 1'$$

$$\frac{dV_0(t)}{dt} + 10V_0(t) = 250 \quad 2' \quad V_S = 25(V) \quad 1'$$


$$V_0(t) = e^{-10(t-0.02)} (V_0(0.02) - V_S) + V_S$$

$$= e^{-10t+0.2} (20 - 20e^{-0.1} - 25) + 25$$

$$= 25 - e^{-10t+0.2} (20e^{-0.1} + 5) (V) \quad 2'$$


$$= 25 - 23.1e^{-10(t-0.02)} (V) \quad t > 20ms$$
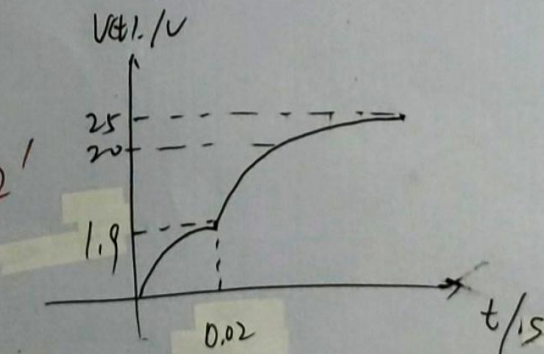
$$V_0(t) = \begin{cases} 20 - 20e^{-5t} (V) & 0 < t < 20ms \\ 25 - 23.1e^{-10(t-0.02)} (V) & t > 20ms \end{cases}$$



Student Name: _____ Student Number: _____

Solution of Problem 5

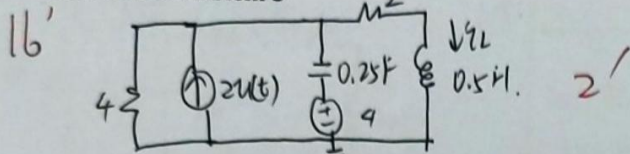

1a) $t=0$: $i_L(0^+) = i_L(0^-) = 0$ $v_C(0^+) = v_C(0^-) = 4 - 4(V)$

$L \frac{di_L(0^+)}{dt} + 2i_L(0^+) = 4 + v_C(0^+)$ $3'$

$0.5 \frac{di_L(0^+)}{dt} = 4 \Rightarrow \frac{di_L(0^+)}{dt} = 8(A/s)$ $2'$

for $t > 0$

1b) $v_1(t) = v_C(t) + 4$ $2'$

$C \frac{dv_1(t)}{dt} + i_L(t) + \frac{v_1(t)}{4} = 0$ $2'$

$L \frac{di_L(t)}{dt} + 2i_L(t) = v_1(t)$ $2'$


$\Rightarrow 0.125 \frac{d^2 i_L(t)}{dt^2} + 0.625 \frac{di_L(t)}{dt} + 1.5 i_L(t) = 2$ $2'$

Student Name: _____

Student Number: _____

20'

Solution of Problem 6

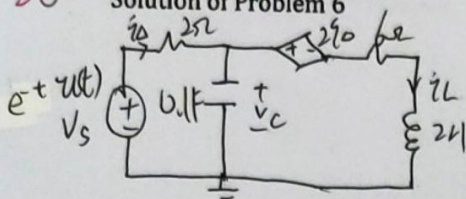

(1) $\frac{V_s - V_C}{2} = i_L$ (1) $V_s = e^{-t} u(t)$ (2)
 $i_L = i_C + i_L$ (3)
 $i_L = C \frac{dV_C}{dt} = 0.1 \frac{dV_C}{dt}$ (3)
 $i_L = \frac{V_C - 25i_L - V_L}{6}$ (4)
 $V_L = L \frac{di_L}{dt} = 2 \frac{di_L}{dt}$ (5)

Analysis total 4'

Substitute (1) (2) (3) into (4)

$\Rightarrow V_C = 3i_L + \frac{1}{2}V_s + \frac{dV_C}{dt} \cdot 0.1$ (1')

$\frac{dV_C}{dt} = 3 \frac{di_L}{dt} - \frac{1}{2}V_s + \frac{d^2V_C}{dt^2}$

Substitute (1) (2) (3) into (5) $\frac{V_s}{2} - \frac{1}{2}(3i_L + \frac{1}{2}V_s + \frac{dV_C}{dt}) = 0.1(\frac{d^2V_C}{dt^2} - \frac{1}{2}V_s + \frac{d^2V_C}{dt^2}) + i_L$
 $\frac{d^2i_L}{dt^2} + 8 \frac{di_L}{dt} + 25 i_L = 3e^{-t} u(t)$ (1')


$i_{Lh} = e^{-4t}(A_1 \cos 3t + A_2 \sin 3t) (A)$ Homogenous Solution.

Particular solution: $i_L = A_3 e^{-t} (A)$ Substitute into equation:

$A_3 e^{-t} - 8 A_3 e^{-t} + 25 A_3 e^{-t} = 3e^{-t} \quad A_3 = \frac{1}{6}$ (1')

$i_L(t) = \frac{1}{6} e^{-t} + e^{-4t}(A_1 \cos 3t + A_2 \sin 3t) (A)$

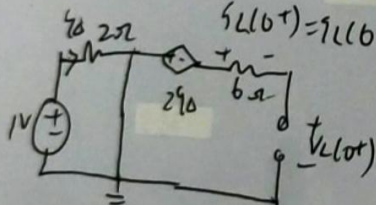$i_L(0^+) = i_L(0^-) = 0 (A)$ $V_L(0^+)$ is determined by the following circuit.



$\begin{cases} i_L = 0.5 (A) & V_L(0^+) = -2i_L = -1 (V) \\ 0 = \frac{1}{6} + A_1 \\ -1 = 2(-\frac{1}{6} + (-4) \cdot (A_1 + 3A_2)) \end{cases} \Rightarrow \begin{cases} A_1 = -\frac{1}{6} \\ A_2 = -\frac{1}{3} \end{cases}$ (1')

$i_L(t) = \frac{1}{6} e^{-t} + e^{-4t}(-\frac{1}{6} \cos 3t - \frac{1}{3} \sin 3t) (A)$ (2')

(2) $V_C = 3i_L + \frac{1}{2}V_s + \frac{dV_C}{dt} = \frac{1}{2}e^{-t} + e^{-4t}(-\frac{1}{2} \cos 3t - \sin 3t) + \frac{1}{2}e^{-t} - \frac{1}{6}e^{-t} + e^{-4t}(\frac{1}{3} \cos 3t + \frac{4}{3} \sin 3t + \frac{1}{2} \sin 3t - \cos 3t)$
 $= \frac{5}{6} e^{-t} + e^{-4t}(-\frac{1}{6} \cos 3t + \frac{5}{6} \sin 3t) (V)$
 $= 0.83 e^{-t} + e^{-4t}(-0.83 \cos 3t + 0.83 \sin 3t) (V)$ (3')