

## Homework 1

Due date:

Mar.12th, 2018

Turn in your homework in class

Rules:

- Work on your own. Discussion is permissible, but extremely similar submissions will be judged as plagiarism.
- Please show all intermediate steps: a correct solution without an explanation will get zero credit.
- Please submit on time. No late submission will be accepted.
- Please prepare your submission in English only. No Chinese submission will be accepted.

1. Determine the current flowing through an element if the charge flow is given by (a)(b). Also, find the charge flowing through an element if the current is given by (c)(d).

(a)  $q(t) = 1.7t(1 - e^{-1.2t}) \text{ nC}$

(b)  $q(t) = 0.2t\sin(120\pi t) + \cos(2e^{-\sin t}) \text{ mC}$

(c)  $i(t) = 4e^{-t} - 3e^{-2t} \text{ mA}, q(0) = 0.2 \text{ C}$

(d)  $i(t) = 12e^{-3t} \cos(40\pi t) \text{ nA}, q(0) = 2.28 \text{ pC}$

2. Find the current  $i_1$  and  $i_2$  shown in Figure 1.

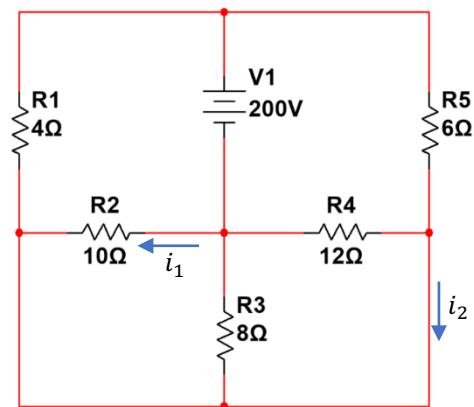


Figure 1

3. Find the power absorbed by each of the elements from  $p_1$  to  $p_5$  with the following circuit shown in Figure 2.

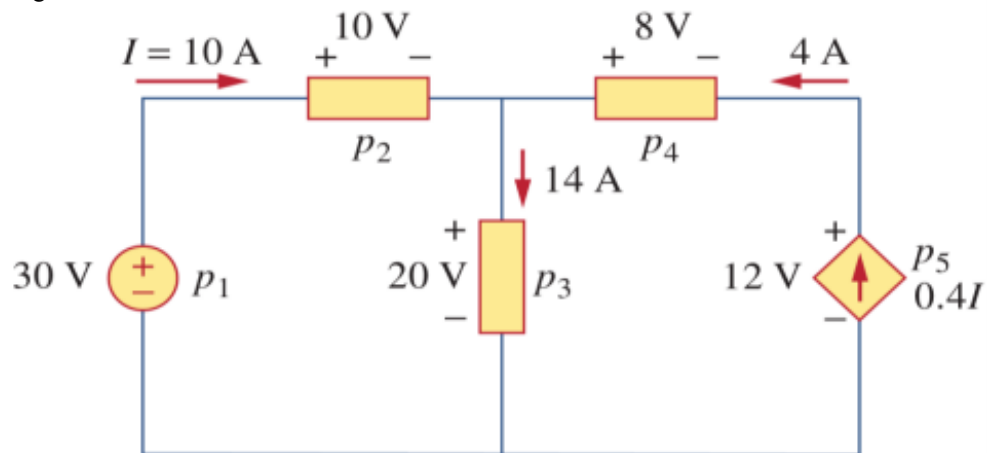


Figure 2

4. Find  $i_1$ ,  $i_6$ ,  $v$  and power on the voltage source of 8V with the circuit shown in the Figure 3.

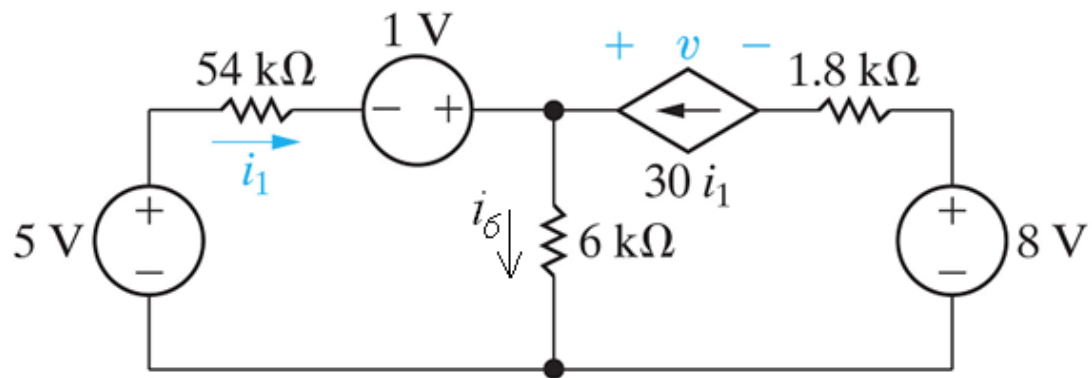


Figure 3

5. Use nodal analysis to find  $V_o$  in the circuit of Figure 4.

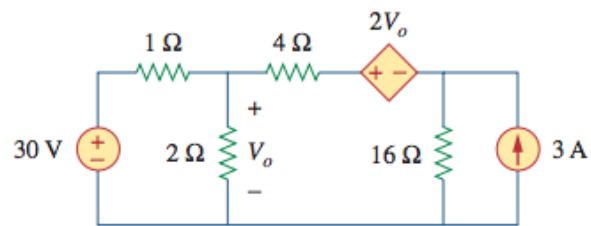


Figure 4

6. Apply mesh analysis to find  $I_x$  in the circuit of Figure 5.

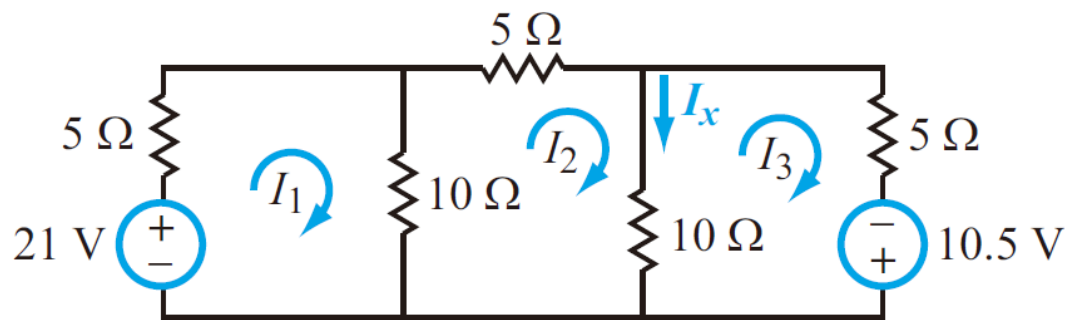


Figure 5

7. Determine  $A$  if  $V_{\text{out}}/V_S = 9$  in the circuit of Figure 6.

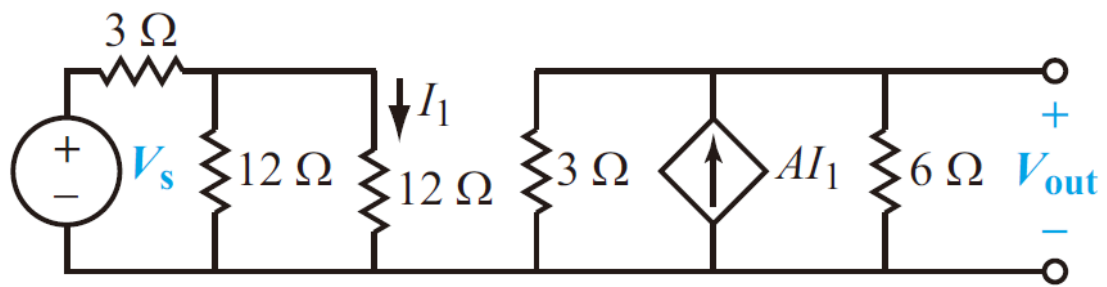


Figure 6