


EE 111 Homework 4

Due date: Apr. 17th, 2019
Turn in your homework in class


Rule:

- Work on your own. Discussion is permissible, but similar submissions will be judged as plagiarism.
- Please show all intermediate steps: a correct solution without an explanation will get zero credit.
- Please submit on time. No late submission will be accepted.
- Please prepare your submission in English only. No Chinese submission will be accepted.

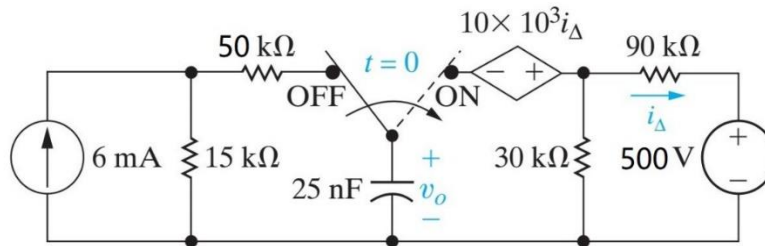
1. The switch in the circuit shown in the figure has been in the OFF position for a long time. At $t=0$, the switch moves instantaneously to the ON position. Find $v_o(t)$ for $t \geq 0$.



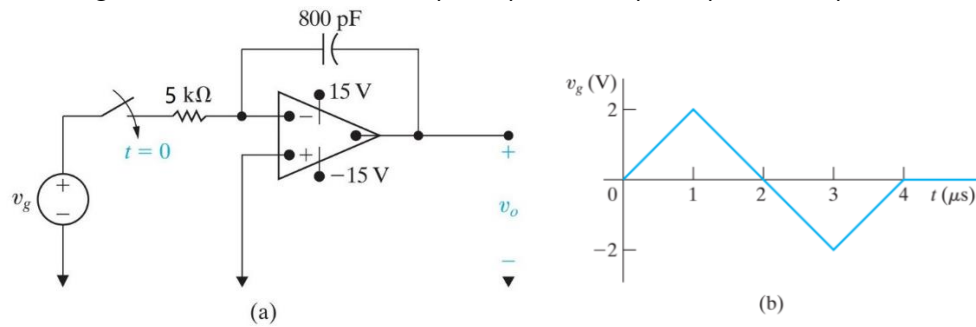
2. The voltage source in the circuit in the figure(a) is generating the triangular waveform shown in the figure(b). Assume the energy stored in the capacitor is zero at $t=0$ and the op amp is ideal. Derive the numerical expressions for $v_o(t)$ for the following time intervals: $0 \leq t \leq 1 \mu\text{s}$; $1 \mu\text{s} \leq t \leq 3 \mu\text{s}$; $3 \mu\text{s} \leq t \leq 4 \mu\text{s}$.



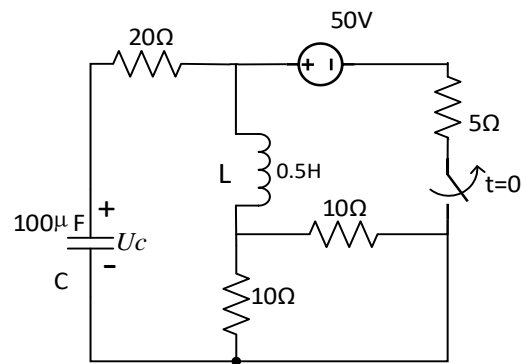3. At $t = 0$, the switch is opened. Determine $U_C(t)$ in the circuit for $t \geq 0$.



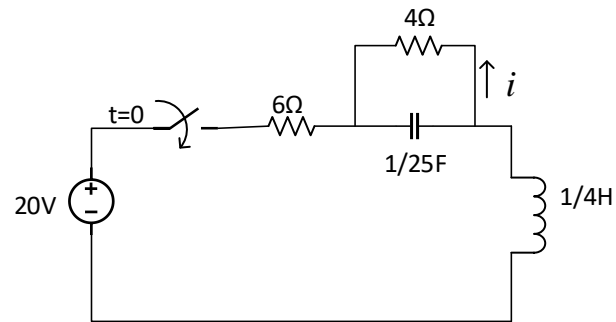
4. When $t < 0$, no energy is stored in the capacitor nor the inductor in the circuit below, Find $i(t)$ for $t \geq 0$.




5. In the circuit below, let $i_L(0)=2\text{A}$, $u_C(0)=0$, please determine

a) i_L ;


b) i_R

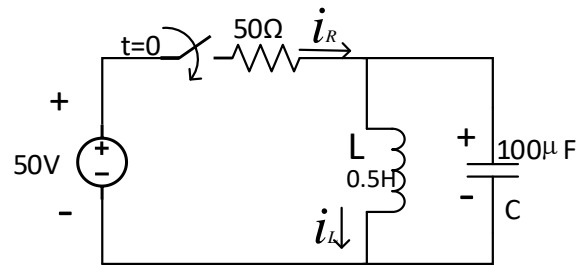

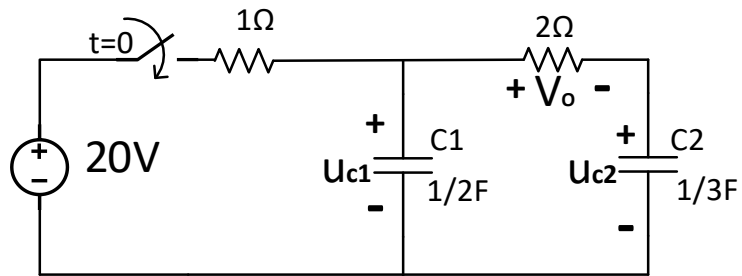
6. The initial capacitor C_1 voltage is 20V and the initial capacitor C_2 voltage is 29 V. For $t > 0$, obtain $V_o(t)$ in the circuit of below.



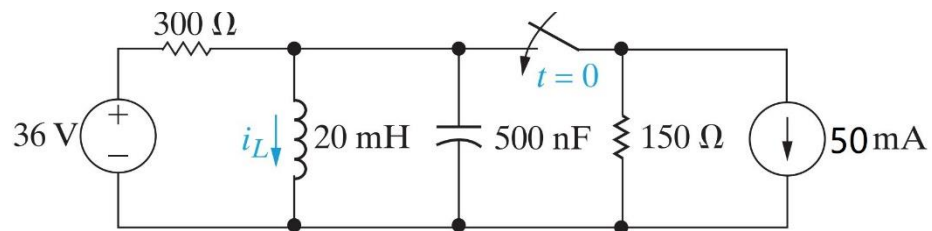
7. The switch in the circuit has been open a long time before closing at $t=0$. Find $i_L(t)$ for $t \geq 0$.



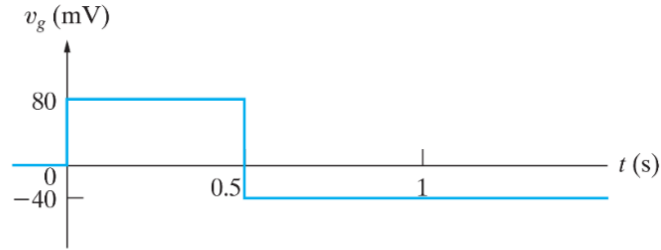8. The voltage signal of Fig.(a) is applied to the cascaded integrating amplifiers shown in Fig.(b). There is no energy stored in the capacitors at the instant the signal is applied.
- Derive the numerical expressions for $v_o(t)$ and $v_{o1}(t)$ for the time intervals $0 \leq t \leq 0.5$ s and $0.5 \text{ s} \leq t \leq 2$ s.
 - Determine which operational amplifier firstly enters its saturation mode from linear mode and find the moment t_{sat} the transition occurs.



(a)

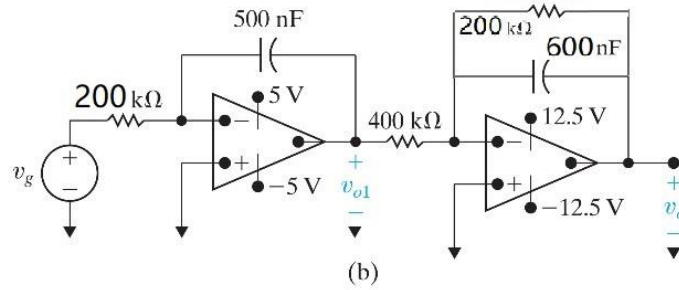

(b)