

Homework 7

Due date:

May 14th, 2018

Turn in your homework in class

Rules:

- Please try to work on your own. Discussion is permissible, but identical submissions are unacceptable!
- Please show all intermediate steps: a correct solution without an explanation will get zero credit.
- Please submit on time. No late submission will be accepted.
- Please prepare your submission in English only. No Chinese submission will be accepted.

1. (9%) Simplify the following expressions and give the answer with rectangular form and polar form.

(a)
$$\frac{(5+j8)+(-2+j11)*j5}{(6+3j)*(-2-8j)-(3+6j)/(4-j8)}$$

(b)
$$\frac{(5\angle 60^\circ - 96\angle -105^\circ)*(-20+j8)}{(8-j9)*(10\angle 45^\circ)}$$

(c)
$$\left(\frac{-45-j18}{8-j6}\right)^2 / \sqrt{(15+j9)/(14+j6)}$$

2. (7%) Simplify the following expressions by using phasors:

(a) $i_1(t) = 40 \cos(\omega t - 48^\circ) + 89 \cos(\omega t + 87^\circ) A$

(b) $i_2(t) = 88 \sin(\omega t + 65^\circ) - 756 \cos(\omega t + 44^\circ) A$

(c) $i_3(t) = 218 \cos(8t) - 950 \sin(8t) mA$

(d) $v_1(t) = 64 \sin(8t - 95^\circ) + 24 \sin(8t + 23^\circ) V$

(e) $v_2(t) = 50 \sin(100t - 65^\circ) + 45 \cos(100t + 20^\circ) + 30 \sin(100t - 80^\circ) mV$

(f) $v_3(t) = 4 \cos(55t + 66^\circ) + 4 \cos(55t - 66^\circ) V$

(g) $v_4(t) = 25 \sin(35t) - 50 \cos(35t) \mu V$

3. (8%) Find steady state solution of $v(t)$ or $i(t)$ in the following integro differential equations using the phasor approach:


(a) $v(t) + \int 54v(t)dt = 25 \cos(6t)$.

(b) $2 \frac{dv(t)}{dt} + 8v(t) + 3 \int v(t)dt = 50 \sin(8t - 30^\circ)$.

(c) $8i(t) + \frac{7di(t)}{dt} = 560 \cos(6t + 75^\circ)$.

(d) $50 \int i(t)dt + 2i(t) + \frac{di(t)}{dt} = 6 \cos(3t - 66^\circ)$.

4. (8%) The voltage applied to the circuit shown in Figure 4 at $t=0$ is $50 \cos(90t + 36^\circ) \text{ V}$. The circuit resistance is 60Ω and the initial current in the 25mH inductor is zero.
- Find $i(t)$ for $t \geq 0$.
 - Write the expressions for the transient and steady-state components of $i(t)$.
 - What are the maximum amplitude, frequency(in radians per second), and phase angle of the steady-state current?
 - By how many degrees are the voltage and the steady-state current out of phase?

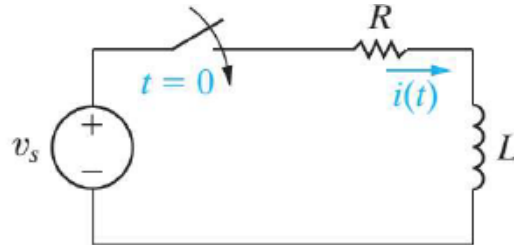**Figure 4**

5. (10%) Determine the equivalent impedance:

(a) Z_1 at $\omega=300\text{rad/s}$ in Figure 5-a.

(b) Z_2 at 1000Hz in Figure 5-b.

(c) Z_3 at 800Hz in Figure 5-c.

(d) Z_4 in Figure 5-d.

(e) Z_5 at $\omega = 10^4\text{rad/s}$ in Figure 5-e.

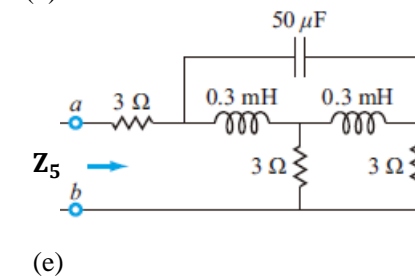
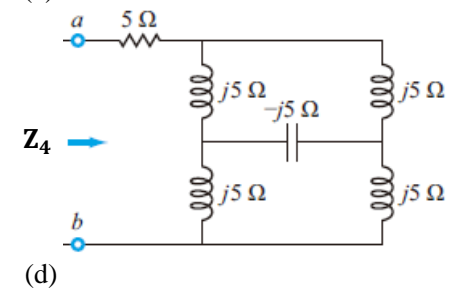
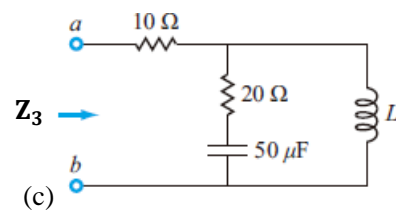
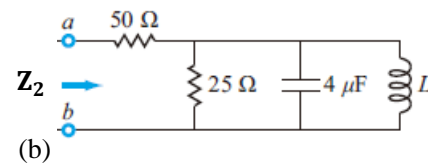
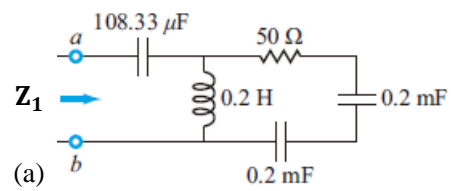


Figure 5

6. (9%) Determine $i_x(t)$ by using mesh method in the circuit of Figure 6, given that $v_s(t) = 6\cos 5 \times 10^5 t$ V.

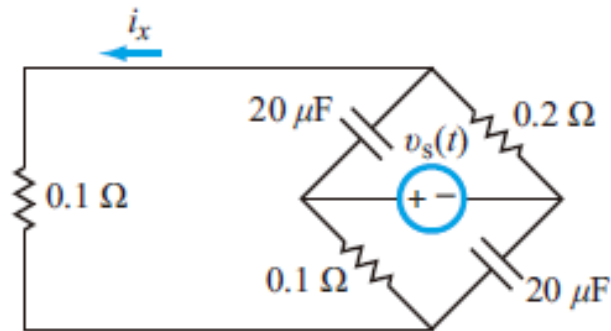


Figure 6

7. (9%) Find the value of ω at which $v_s(t)$ and $i_s(t)$ in the circuit of Figure 7 are in-phase (in-phase means that there is no imaginary part in the total Z_{eq}).

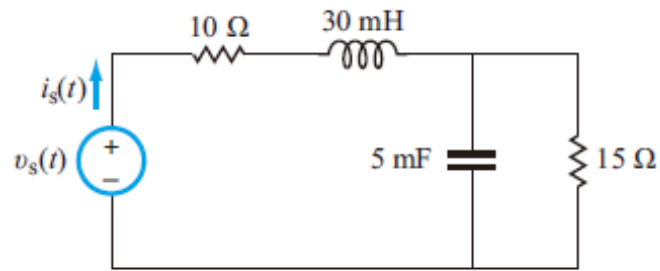


Figure 7

8. (9%) The input signal in the op-amp circuit of Figure 8 is given by

$$v_{in}(t) = 0.5\cos 2000t \text{ V.}$$

Obtain an expression for $v_{out}(t)$ and then evaluate it for $R_1 = 2k\Omega$, $R_2 = 10k\Omega$, and $C = 0.1 \mu\text{F}$.

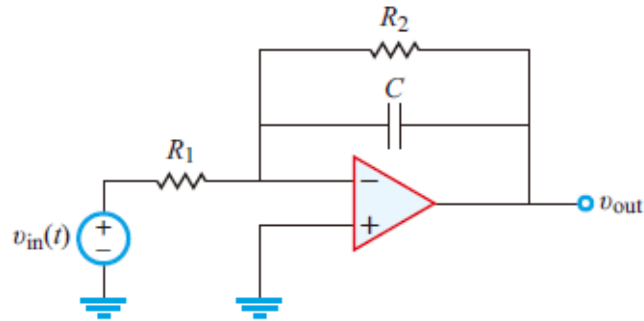


Figure 8

9. (9%) The circuit in Figure 9 is in the phasor domain. Determine and plot its Thevenin equivalent circuit at terminals (a,b) .

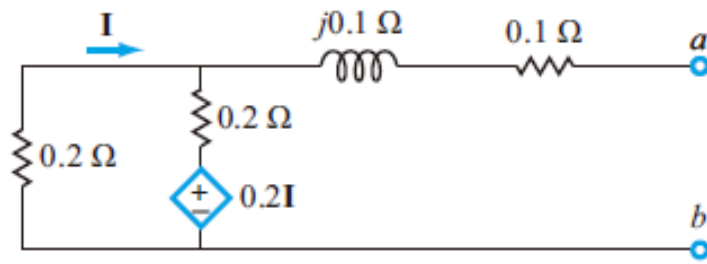


Figure 9

10. (12%) Find v_o in the circuit of Figure 10 using superposition.

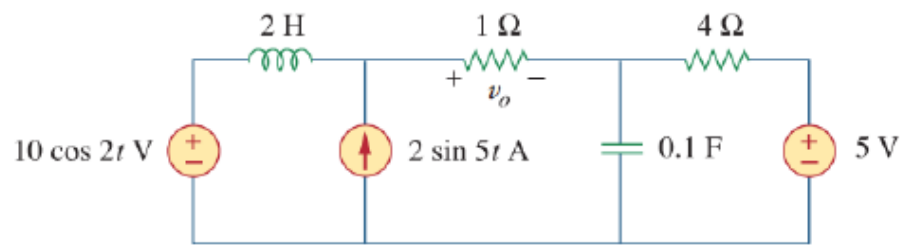


Figure 10

11. (10%) The input circuit shown in Figure 11 contains two sources, given by

$$i_s(t) = 2 \cos 10^3 t \text{ A}$$

$$v_s(t) = 8 \sin 10^3 t \text{ V}$$

This input circuit is to be connected to a load circuit that provides optimum performance when the impedance Z of the input circuit is purely real. The circuit includes a “matching” element whose *type* and *magnitude* should be chosen to realize that condition. What should those attributes (type and magnitude) be?

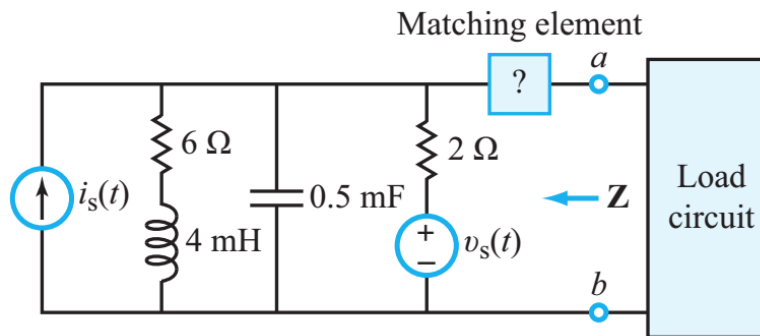


Figure 11