

Problem 1 (7 points)

For each of the 7 devices in the circuit of Fig. 1, determine whether the device is a supplier or a recipient of power and how much power it is supplying or receiving.

Note: Use the passive sign convention.

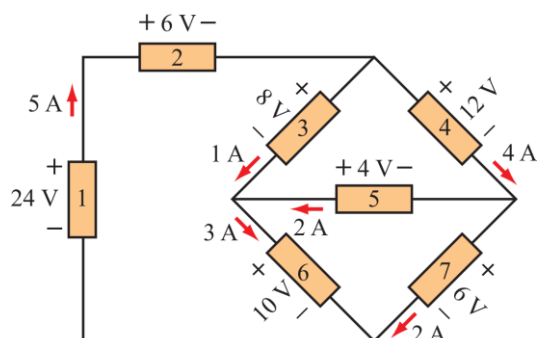


Fig. 1 for Problem 1.

Solution:

| | Voltage (V) | Current (A) | Power (W) | Power Supplier (S) or Recipient (R)? |
|----------|-------------|-------------|-----------|--------------------------------------|
| Device 1 | 24 | -5 | -120 | S |
| Device 2 | 6 | 5 | -30 | R |
| Device 3 | 8 | 1 | 8 | R |
| Device 4 | 12 | 4 | 48 | R |
| Device 5 | 4 | -2 | -8 | S |
| Device 6 | 10 | 3 | 30 | R |
| Device 7 | 6 | 2 | 12 | R |



Problem 2 (12 points)Find I in the circuit of Fig. 2.

Fig. 2 for Problem 2.

Solution:



Problem 3 (12 points)Find current I_x in the circuit of Fig.3.

Fig. 3 for Problem 3.

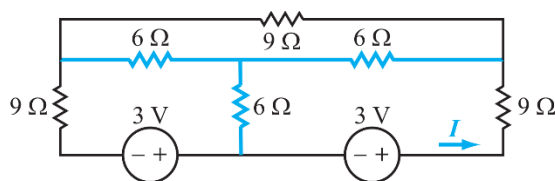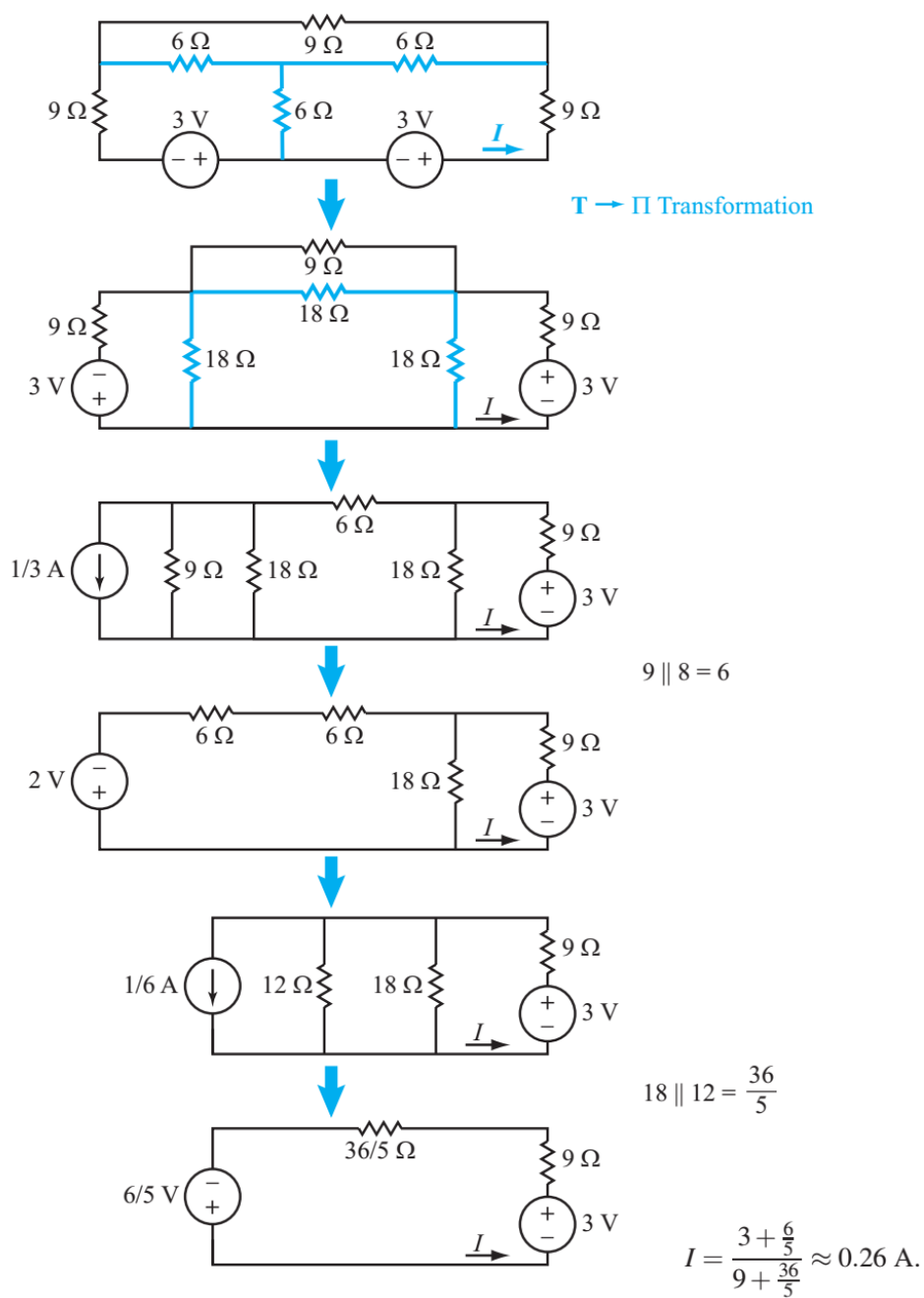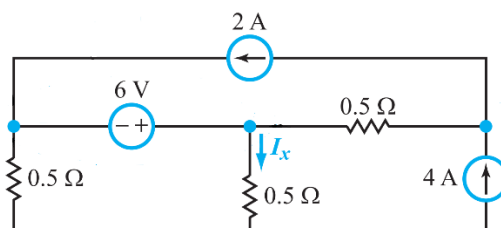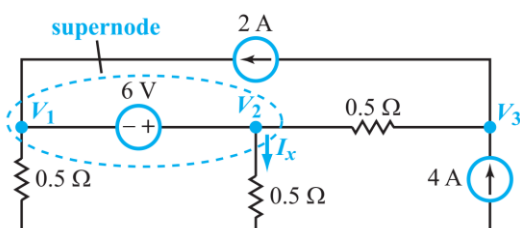

Solution: The presence of a voltage source between designated nodes 1 and 2 makes the combination of nodes 1 and 2 a supernode. Hence,

$$\frac{V_1}{0.5} - 2 + \frac{V_2}{0.5} + \frac{V_2 - V_3}{0.5} = 0. \quad (1)$$

For node 3,

$$\frac{V_3 - V_2}{0.5} - 4 + 2 = 0, \quad (2)$$

and the auxiliary equation is

$$V_2 - V_1 = 6. \quad (3)$$

Combining the three equations leads to:

$$V_1 = -2 \text{ V}, \quad V_2 = 4 \text{ V}, \quad V_3 = 5 \text{ V}.$$

Hence,

$$I_x = \frac{V_2}{0.5} = \frac{4}{0.5} = 8 \text{ A}.$$

Problem 5 (15 points)

For the circuit in Fig. 5,

- Find the Thevenin equivalent circuit at terminals (a, b) as seen by the load resistor R_L .
- Choose R_L so that the current flowing through it is 0.16mA. **0.2K**
- Choose R_L so that the power delivered to it is maximum. How much power will that be?


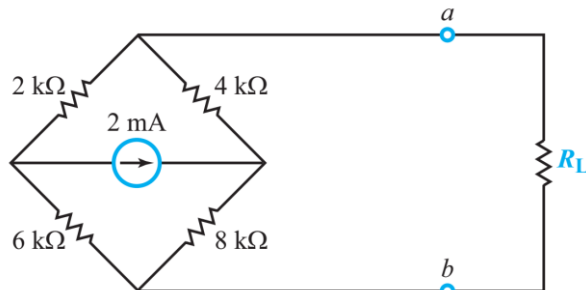


Fig. 5 for Problem 5.

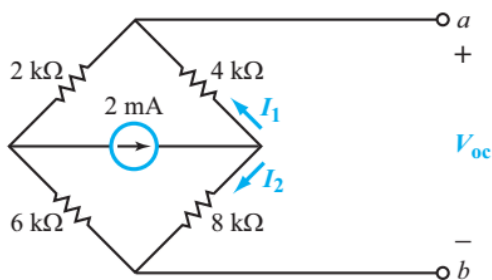Solution: We need to find the Thévenin equivalent circuit at terminals (a, b), as if R_L were not present.



The current source will divide among I_1 and I_2 such that

$$(4 + 2)I_1 = (8 + 6)I_2$$


Also, $I_1 + I_2 = 2 \text{ mA}$.

The solution yields:

$$I_1 = 1.4 \text{ mA}, \quad I_2 = 0.6 \text{ mA}.$$

$$\begin{aligned} V_{oc} &= (-4I_1 + 8I_2) \times 10^3 \\ &= -4 \times 1.4 + 8 \times 0.6 = -0.8 \text{ V}. \end{aligned}$$

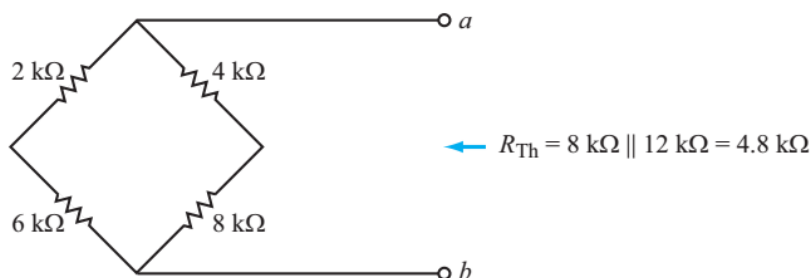To find R_{Th} , we suppress the current source and simplify the circuit:



b) $R_L = 200\Omega$

c) $R_L = 4.8k\Omega$, max power = $\frac{(0.4V)^2}{4.8k\Omega} = 33\mu W$.

Problem 6 (12 points)

In the circuit shown in Fig. 6, find the gain $G = \frac{v_o}{v_s}$.

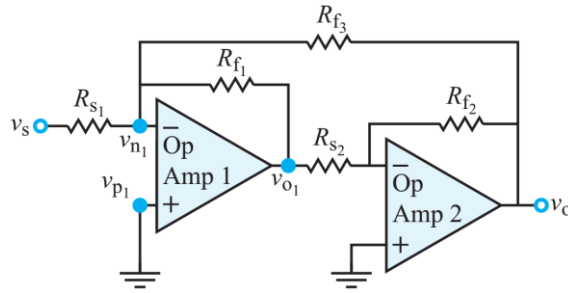


Fig. 6 for Problem 6.

Solution: For the second op amp,

$$v_o = \left(-\frac{R_{f_2}}{R_{s_2}} \right) v_{o_1} \quad (1)$$

For the first op amp,

$$\frac{v_{n_1} - v_s}{R_{s_1}} + \frac{v_{n_1} - v_{o_1}}{R_{f_1}} + \frac{v_{n_1} - v_o}{R_{f_3}} = 0$$

Also,

$$v_{n_1} = v_{p_1} = 0.$$

Hence,

$$-\frac{v_s}{R_{s_1}} - \frac{v_{o_1}}{R_{f_1}} - \frac{v_o}{R_{f_3}} = 0 \quad (2)$$

Simultaneous solution of (1) and (2) leads to

$$v_o = \frac{v_s}{R_{s_1}} \left[\frac{R_{f_1} R_{f_2} R_{f_3}}{R_{f_3} R_{s_2} - R_{f_1} R_{f_2}} \right].$$

Problem 7 (10 points)

The ideal operational amplifier circuit shown in Fig. 7 is driven by a input ramp signal

$$v_I(t) = \begin{cases} 0 \text{ V}, & t < 0 \\ 1000t \text{ V}, & t \geq 0 \end{cases}$$

Assume that the capacitor voltage is zero for $t < 0$. What are the value of output voltage $v_O(t)$ at $t = 1\text{ms}$?

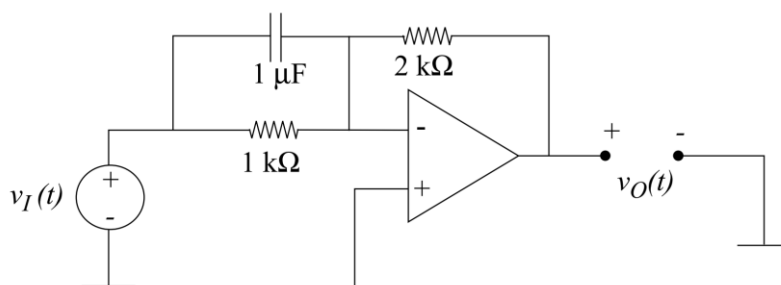


Fig. 7 for Problem 7.

Solution:

KCL at node v^- :

$$\frac{v_I(t) - 0}{1000} + C \frac{dv_I(t)}{dt} + \frac{v_O(t) - 0}{2000} = 0, \text{ since } v^- = v^+ = 0$$

$$\text{Therefore, } v_I(t) = 1000t, \frac{dv_I(t)}{dt} = 1000, \text{ so}$$

$$v_O(t) = -2000 \cdot t - 2 \text{ [volts]}$$

$$v_O(t = 1\text{ms}) = -4\text{Volts}$$

Problem 8 (20 points)


Design an op-amp circuit that can perform the operation

$$i_o = (30i_1 - 8i_2 + 0.6) \text{ A}$$

Where i_1 and i_2 are two input current sources.

Solution: Below is just one possible solution.

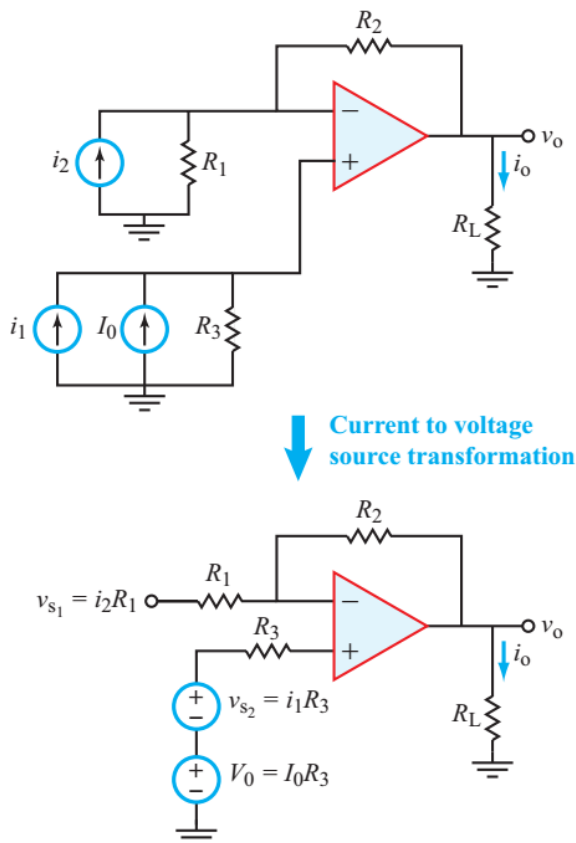Remember to include the internal resistance of current sources when you calculate the gain!!!



$$\begin{aligned} v_o &= \left(-\frac{R_2}{R_1}\right) v_{s1} + \left(\frac{R_2 + R_1}{R_1}\right) [v_{s2} + V_0] \\ &= \left(-\frac{R_2}{R_1}\right) i_2 R_1 + \left(\frac{R_2 + R_1}{R_1}\right) [i_1 R_3 + I_0 R_3] \end{aligned}$$

Choose $R_1 = 2 \text{ k}\Omega$, $R_2 = 8 \text{ k}\Omega$. Hence,

$$v_o = -8 \times 10^3 i_2 + 5[i_1 R_3 + I_0 R_3]$$

Choose $R_3 = 6 \text{ k}\Omega$, so that the coefficient of i_1 is 30×10^3 .

Choose $I_0 = 0.02 \text{ A} = 20 \text{ mA}$, so that $5I_0 R_3 = 0.6 \times 10^3$.

Hence,

$$v_o = -8 \times 10^3 i_2 + 30 \times 10^3 i_1 + 0.6 \times 10^3 \quad (\text{V})$$

$$i_o = \frac{v_o}{R_L}$$

Choose $R_L = 1 \text{ k}\Omega$,

$$i_o = (30i_1 - 8i_2 + 0.6) \text{ A.}$$