

Homework 7

Due date:

May 14th, 2018

Turn in your homework in class

Rules:

- Please try to work on your own. Discussion is permissible, but identical submissions are unacceptable!
- Please show all intermediate steps: a correct solution without an explanation will get zero credit.
- Please submit on time. No late submission will be accepted.
- Please prepare your submission in English only. No Chinese submission will be accepted.

1. (9%) Simplify the following expressions and give the answer with rectangular form, polar form and exponential form.

$$(a) \frac{(5+j8)+(-2+j11)*j5}{(6+3j)*(-2-8j)-(3+6j)/(4-j8)}$$

$$(b) \frac{(5\angle 60^\circ - 96\angle -105^\circ)*(-20+j8)}{(8-j9)*(10\angle 45^\circ)}$$

$$(c) \left(\frac{-45-j18}{8-j6}\right)^2 / \sqrt{(15+j9)/(14+j6)}$$

Solutions: [每个 1.5 分=1.5%*3*2=9%]

$$(a) \frac{209}{435} - j\frac{217}{435} \text{ or } 0.48 - j0.50 \quad 0.693 \angle -46.076^\circ \text{ or } 0.693e^{j(-46.076^\circ)} \text{ or } 0.693e^{j(-0.256\pi)}$$

$$(b) -10.13 - j14.92 \quad 18.04 \angle -124.17^\circ \text{ or } 18.04e^{j(-124.17^\circ)} \text{ or } 18.04e^{j(-0.69\pi)}$$

$$(c) -6.99 + j11.53 \quad 13.49 \angle 121.23^\circ \text{ or } 13.49e^{j(121.23^\circ)} \text{ or } 13.49e^{j(0.67\pi)}$$

2. (7%) Simplify the following expressions by using phasors:

- (a) $i_1(t) = 40 \cos(\omega t - 48^\circ) + 89 \cos(\omega t + 87^\circ) \text{ A}$
- (b) $i_2(t) = 88 \sin(\omega t + 65^\circ) - 756 \cos(\omega t + 44^\circ) \text{ A}$
- (c) $i_3(t) = 218 \cos(8t) - 950 \sin(8t) \text{ mA}$
- (d) $v_1(t) = 64 \sin(8t - 95^\circ) + 24 \sin(8t + 23^\circ) \text{ V}$
- (e) $v_2(t) = 50 \sin(100t - 65^\circ) + 45 \cos(100t + 20^\circ) + 30 \sin(100t - 80^\circ) \text{ mV}$
- (f) $v_3(t) = 4 \cos(55t + 66^\circ) + 4 \cos(55t - 66^\circ) \text{ V}$
- (g) $v_4(t) = 25 \sin(35t) - 50 \cos(35t) \mu\text{V}$

Solution:

(a) $i_1(t) = 40 \cos(\omega t - 48^\circ) + 89 \cos(\omega t + 87^\circ) \text{ A}$
 $I_1 = 40 \angle -48^\circ + 89 \angle 87^\circ = 66.98 \angle 62.06^\circ \text{ A } 0.5'$
 $\Rightarrow i_1(t) = 66.98 \cos(\omega t + 62.06^\circ) \text{ A } 0.5'$

(b) $i_2(t) = 88 \sin(\omega t + 65^\circ) - 756 \cos(\omega t + 44^\circ) \text{ A}$
 $I_2 = 88 \angle 135^\circ - 756 \angle 44^\circ = 791.81 \angle -141.96^\circ \text{ A } 0.5'$
 $\Rightarrow i_2(t) = 791.81 \cos(\omega t - 141.96^\circ) \text{ A } 0.5'$

(c) $i_3(t) = 218 \cos 8t - 950 \sin 8t \text{ mA}$
 $I_3 = 218 \angle 0^\circ - 950 \angle 90^\circ = 974.69 \angle -77.08^\circ \text{ mA } 0.5'$
 $\Rightarrow i_3(t) = 974.69 \cos(8t - 77.08^\circ) \text{ mA } 0.5'$

(d) $v_1(t) = 64 \sin(8t - 95^\circ) + 24 \sin(8t + 23^\circ) \text{ V}$
 $V_1 = 64 \angle -5^\circ + 24 \angle 113^\circ = 56.83 \angle 16.89^\circ \text{ V } 0.5'$
 $\Rightarrow v_1(t) = 56.83 \sin(8t + 16.89^\circ) \text{ V } 0.5'$

(e) $v_2(t) = 50 \sin(100t - 65^\circ) + 45 \cos(100t + 20^\circ) + 30 \sin(100t - 80^\circ) \text{ mV}$
 $V_2 = 50 \angle 25^\circ + 45 \angle 20^\circ + 30 \angle 10^\circ = 124.36 \angle 19.61^\circ \text{ mV } 0.5'$
 $\Rightarrow v_2(t) = 124.36 \cos(100t + 19.61^\circ) \text{ mV } 0.5'$

(f) $v_3(t) = 4 \cos(55t + 66^\circ) + 4 \cos(55t - 66^\circ) \text{ V}$
 $V_3 = 4 \angle 66^\circ + 4 \angle -66^\circ = 3.25 \text{ V } 0.5'$
 $\Rightarrow v_3(t) = 3.25 \text{ V } 0.5'$

(g) $v_4(t) = 25 \sin(35t) - 50 \cos(35t) \mu\text{V}$
 $V_4 = 25 \angle -90^\circ - 50 \angle 0^\circ = 25\sqrt{5} \angle -153.43^\circ (= 55.90 \angle -153.43^\circ) \mu\text{V } 0.5'$
 $\Rightarrow v_4(t) = 25\sqrt{5} \cos(35t - 153.43^\circ) \mu\text{V} (= 55.90 \cos(35t - 153.43^\circ) \mu\text{V}) 0.5'$
 红色划线处单位少一个就减 0.5', 扣完即止.

3. (8%) Find steady state solution of $v(t)$ or $i(t)$ in the following integro differential equations using the phasor approach:

(a) $v(t) + \int 54v(t)dt = 25 \cos(6t)$.

(b) $2 \frac{dv(t)}{dt} + 8v(t) + 3 \int v(t)dt = 50 \sin(8t - 30^\circ)$.

(c) $8i(t) + \frac{7di(t)}{dt} = 560 \cos(6t + 75^\circ)$.

(d) $50 \int i(t)dt + 2i(t) + \frac{di(t)}{dt} = 6 \cos(3t - 66^\circ)$.

Solution:

(a) $V + \frac{V}{j\omega} = 25 \angle 0^\circ, \omega = 6$ 1'

$V = 24.66 \angle 9.46^\circ$ V 0.5'

$v(t) = 24.66 \cos(6t + 9.46^\circ)$ V 0.5'

(b) $2j\omega V + 8V + 3 \frac{V}{j\omega} = 50 \angle 60^\circ, \omega = 8$ 1'

$V = 2.85 \angle -2.89^\circ$ V 0.5'

$v(t) = 2.85 \cos(8t - 2.89^\circ)$ V 0.5'

(c) $8I + 7j\omega I = 560 \angle 75^\circ, \omega = 6$ 1'

$I = 13.10 \angle -4.22^\circ$ A 0.5'

$i(t) = 13.10 \cos(6t - 4.22^\circ)$ A 0.5'

(d) $50 \frac{I}{j\omega} + 2I + j\omega I = 6 \angle -66^\circ, \omega = 3$ 1'

$I = 0.43 \angle 15.67^\circ$ A 0.5'

$i(t) = 0.43 \cos(3t + 15.67^\circ)$ A 0.5'

红色划线处单位少一个就减 0.5', 扣完即止.

4. (8%) The voltage applied to the circuit shown in Figure 4 at $t=0$ is $50 \cos(90t + 36^\circ) \text{ V}$. The circuit resistance is 60Ω and the initial current in the 25mH inductor is zero.
- Find $i(t)$ for $t \geq 0$.
 - Write the expressions for the transient and steady-state components of $i(t)$.
 - What are the maximum amplitude, frequency (in radians per second), and phase angle of the steady-state current?
 - By how many degrees are the voltage and the steady-state current out of phase?

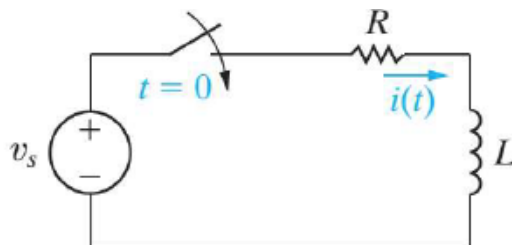


Figure 4

Solution:

- (a) The numerical values of the terms are

$$V_m = 50 \quad 0.5' \quad R/L = 2400 \quad 0.5' \quad \omega L = 2.25 \quad 0.5'$$

$$\sqrt{R^2 + \omega^2 L^2} = 60.042 \quad 0.5'$$

$$\phi = 36^\circ \quad 0.5' \quad \theta = \tan^{-1} 2.25/60, \quad \theta = 2.1476^\circ \quad 0.5'$$

Substitute these values into Equation:

$$i = [-0.692e^{-2400t} + 0.833 \cos(90t - 33.85^\circ)] \text{ A}, \quad t \geq 0 \quad 1'$$

- (b) Transient component: $-0.692e^{-2400t} \text{ A}$ $1'$

$$\text{Steady-state component: } 0.833 \cos(90t - 33.85^\circ) \text{ A} \quad 1'$$

- (c) maximum amplitude: 0.833A , frequency: 90 rad/s , phase angle: -33.85° $1'$

- (d) The current lags the voltage by 33.85° or the voltage leads the current by 33.85° $1'$

5. (10%) Determine the equivalent impedance:
- Z_1 at $\omega=300\text{rad/s}$ in Figure 5-a.
 - Z_2 at 1000Hz with $L=5\text{mH}$ in Figure 5-b.
 - Z_3 at 800Hz with $L=2\text{mH}$ in Figure 5-c.
 - Z_4 in Figure 5-d.
 - Z_5 at $\omega=10^4\text{rad/s}$ in Figure 5-e.

Solutions: [每个 2' : 5*2'=10%]

答案每少一个单位则减 1', 扣完为止

(a)

$$Z_1 = -j3.611 \times 10^{-7} \Omega \times (j60 \Omega // (50 \Omega - j6.67 \times 10^{-7} \Omega))$$

$$= 8.88 \times 10^{-6} - j1.07 \times 10^{-5} \Omega = 1.387 \times 10^{-5} \angle -50.19^\circ \Omega$$

$f=1\text{kHz} \rightarrow \omega=2\pi f=2\pi \text{krad/s}$

(b)

$$Z_2 = 50 \Omega + (25 \Omega // j6.37 \times 10^{-4} \Omega // j10 \pi \Omega)$$

$$= 50 - j6.37 \times 10^{-4} \Omega = 50 \angle -7.3 \times 10^{-4} \Omega$$

(c)

$$Z_3 = 10 \Omega + (j3.2 \pi \Omega // (20 \Omega - j9.9 \times 10^{-2} \Omega))$$

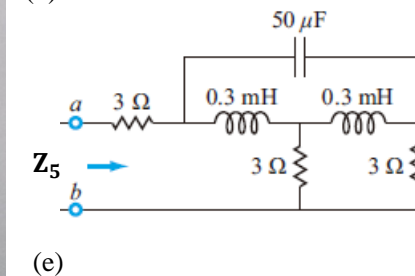
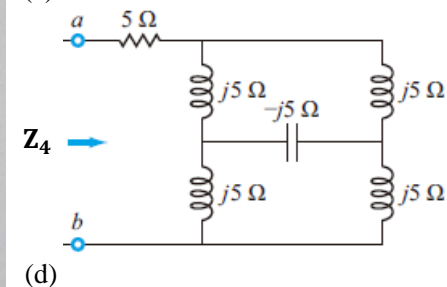
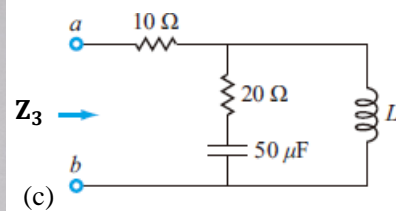
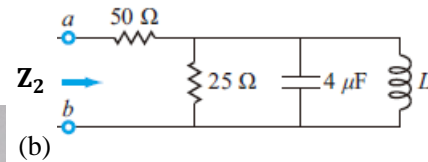
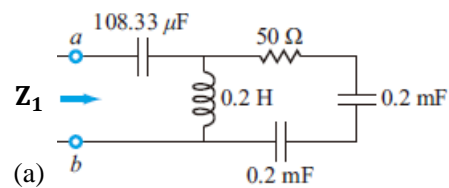
$$= 14.03 + j8.03 \Omega = 16.17 \angle 29.76^\circ \Omega$$


Figure 5

(d)

$$Z_a = \frac{Z_1 Z_2 + Z_2 Z_3 + Z_1 Z_3}{Z_1}$$

$$= \frac{(j5)(-j5) + (-j5)(j5) + (j5)^2}{j5} = -j5 \Omega$$

$$Z_b = \frac{Z_1 Z_2 + Z_2 Z_3 + Z_1 Z_3}{Z_2} = j5 \Omega$$


$$Z_c = Z_a = -j5 \Omega$$

$$Z = 5 + j5 // 2(j5 // -j5)$$

$$= 5 + j5 // 2 \left(\frac{25}{j5 - j5} \right)$$

$$= 5 + j5 // \infty$$

$$= (5 + j5) = 5\sqrt{2} e^{j45^\circ}$$

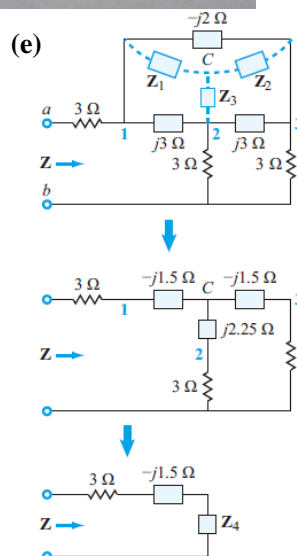

$$Z_L = j\omega L = j10^4 \times 0.3 \times 10^{-3} = j3 \Omega$$

$$Z_C = \frac{-j}{\omega C} = \frac{-j}{10^4 \times 50 \times 10^{-6}} = -j2 \Omega$$

$$Z_1 = \frac{j3 \times (-j2)}{j3 + j3 - j2} = \frac{6}{j4} = -j1.5 \Omega$$

$$Z_2 = Z_1 = -j1.5 \Omega$$

$$Z_3 = \frac{(j3)^2}{j4} = \frac{-9}{j4} = j2.25 \Omega$$

$$Z_4 = (3 + j2.25) // (3 - j1.5) = (2.077 + j0.115) \Omega$$

$$Z = (3 - j1.5) + (1.99 + j0.62) = (5.077 - j1.385) \Omega$$

6. (9%) Determine $i_x(t)$ by using mesh method in the circuit of Figure 6, given that $v_s(t) = 6\cos 5 \times 10^5 t$ V.


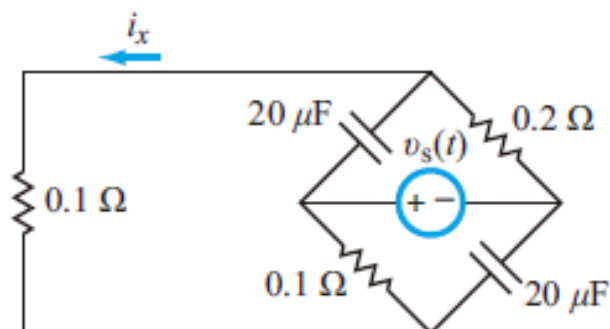


Figure 6

Solution:

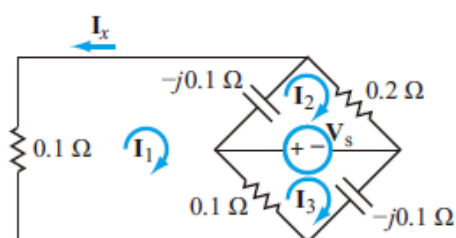

At $\omega = 5 \times 10^5$ rad/s,

$$Z_C = \frac{-j}{\omega C} = \frac{-j}{5 \times 10^5 \times 20 \times 10^{-6}} = -j0.1 \Omega$$

$$V_s = 6\angle 0^\circ \text{ V}$$

Application of the mesh current by inspection method gives:

$$\begin{bmatrix} (0.1 + 0.1 - j0.1) & j0.1 & -0.1 \\ j0.1 & (0.2 - j0.1) & 0 \\ -0.1 & 0 & (0.1 - j0.1) \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} 0 \\ 6 \\ -6 \end{bmatrix}$$

Solution of matrix equation gives

方程组每个式子 1', 共 3'

$$I_1 = (6.79 - j23.77) \text{ A}$$

$$I_2 = (15.85 - j4.53) \text{ A}$$

$$I_3 = -(14.72 + j38.49) \text{ A}$$

解出三个答案, 每个 1', 共 3'

$$I_x = -I_1 = (6.79 - j23.77) \text{ A} = 24.72e^{-j74.06^\circ} \text{ A} \quad 1'$$

$$i_x(t) = 24.72 \cos(5 \times 10^5 t - 74.06^\circ) \text{ A.} \quad 2'$$

如果最后的单位(A)少了, 扣 1', 扣完即止

7. (9%) Find the value of ω at which $v_s(t)$ and $i_s(t)$ in the circuit of Figure 7 are in-phase (in-phase means that there is no imaginary part in the total Z_{eq}).

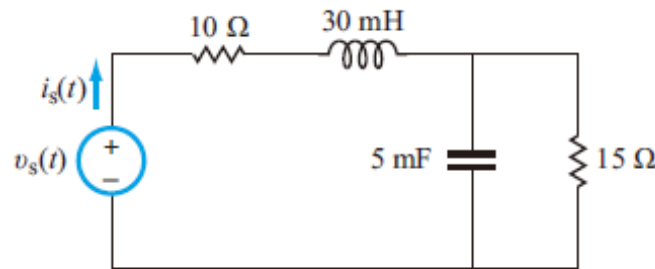


Figure 7

Solution: Transforming the circuit to the phasor domain leads to the circuit in Fig. P7.75(a).

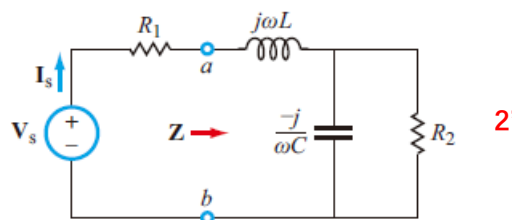


Fig. P7.75(a)

For I_s to be in-phase with V_s , it is necessary that the impedance of the circuit to the right of terminals (a, b) be purely real.

$$\begin{aligned}
 Z &= j\omega L + R_2 \parallel \left(\frac{-j}{\omega C} \right) \\
 &= j\omega L - \frac{jR_2/\omega C}{R_2 - \frac{j}{\omega C}} \\
 &= \left(j\omega L \left(R_2 - \frac{j}{\omega C} \right) - j \frac{R_2}{\omega C} \right) \times \left[\frac{1}{R_2 - \frac{j}{\omega C}} \right] \\
 &= \left[\frac{L}{C} + j \left(\omega L R_2 - \frac{R_2}{\omega C} \right) \right] \left[\frac{\omega C}{R_2 \omega C - j} \right] \\
 &= \left[\frac{L}{C} + j \left(\frac{\omega^2 L C R_2 - R_2}{\omega C} \right) \right] \left[\frac{\omega C (R_2 \omega C + j)}{R_2^2 \omega^2 C^2 + 1} \right] \\
 &= \frac{\omega L + j(\omega^2 L C R_2 - R_2)}{\omega C} \times \frac{\omega C (R_2 \omega C + j)}{R_2^2 \omega^2 C^2 + 1} \\
 &= [\omega^2 L C R_2 - (\omega^2 L C R_2 - R_2)] + \frac{j[\omega L + R_2 \omega C (\omega^2 L C R_2 - R_2)]}{R_2^2 \omega^2 C^2 + 1}. \quad 3'
 \end{aligned}$$

Equating the imaginary component to zero gives

$$\omega L + R_2 \omega C (\omega^2 L C R_2 - R_2) = 0 \quad 1'$$

$$L + R_2^2 L C^2 \omega^2 - R_2^2 C = 0$$

$$\omega = \sqrt{\frac{R_2^2 C - L}{R_2^2 C^2 L}} \quad 2'$$

$$\begin{aligned}
 &= \left[\frac{(15)^2 \times 5 \times 10^{-3} - 30 \times 10^{-3}}{(15)^2 \times (5 \times 10^{-3})^2 \times 30 \times 10^{-3}} \right]^{1/2} = 80.55 \text{ rad/s.} \quad 1' \\
 &\quad \text{少单位则减 1', 扣完为止}
 \end{aligned}$$

8. (9%) The input signal in the op-amp circuit of Figure 8 is given by

$$v_{in}(t) = 0.5\cos 2000t \text{ V.}$$

Obtain an expression for $v_{out}(t)$ and then evaluate it for $R_1 = 2\text{ k}\Omega$, $R_2 = 10\text{ k}\Omega$, and $C = 0.1\text{ }\mu\text{F}$.


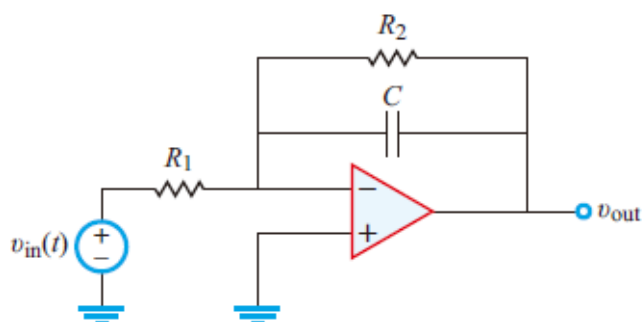


Figure 8

Solution:

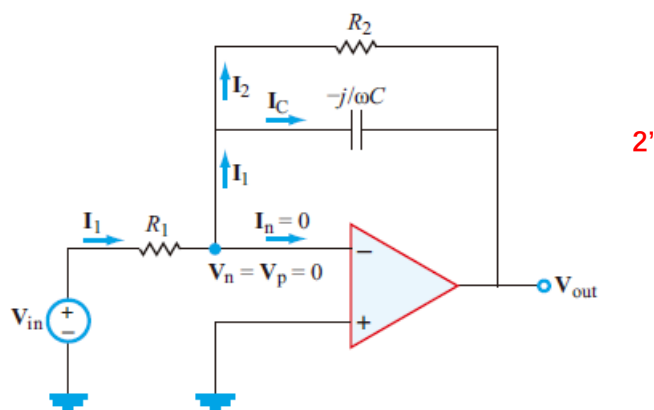

$$V_{in} = 0.5\angle 0^\circ \text{ V.}$$

Since $V_n = 0$,

$$I_1 = \frac{V_{in}}{R_1}.$$

Also,

$$\begin{aligned} I_1 &= I_2 + I_C \\ &= \frac{V_n - V_{out}}{R_2} + \frac{V_n - V_{out}}{-j/\omega C} \quad 2' \\ &= -V_{out} \left(\frac{1}{R_2} + j\omega C \right). \end{aligned}$$

Hence,

$$\begin{aligned} V_{out} &= -\left(\frac{R_2}{R_1} \right) \left(\frac{1}{1 + j\omega R_2 C} \right) V_{in} \\ &= -\left(\frac{R_2}{R_1} \right) \frac{1 - j\omega R_2 C}{1 + \omega^2 R_2^2 C^2} V_{in}. \quad 3' \end{aligned}$$

For $V_{in} = 0.5 \text{ V}$, $R_1 = 2 \text{ k}\Omega$, $R_2 = 10 \text{ k}\Omega$, $\omega = 2000 \text{ rad/s}$, and $C = 0.1 \text{ }\mu\text{F}$,

$$\begin{aligned} V_{out} &= -0.5(1 - j2) \\ &= 0.5\sqrt{5} e^{j180^\circ} \cdot e^{-j63.4^\circ} \\ &= 1.12 e^{j116.6^\circ} \text{ V.} \quad 1' \end{aligned}$$

$$v_{out}(t) = 1.12 \cos(2000t + 116.6^\circ) \text{ (V).} \quad 1'$$

9. (9%) The circuit in Figure 9 is in the phasor domain. Determine and plot its Thevenin equivalent circuit at terminals (a,b) .


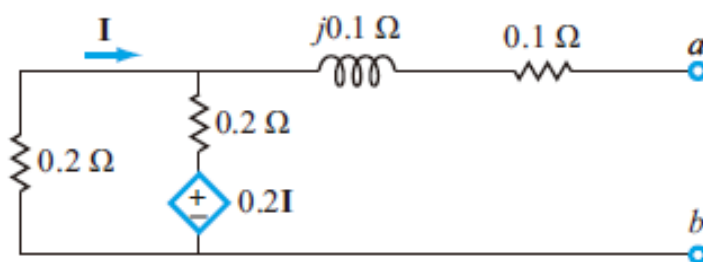


Figure 9

Solution: Since the circuit has no independent sources,

$$V_{Th} = 0. \quad 1'$$

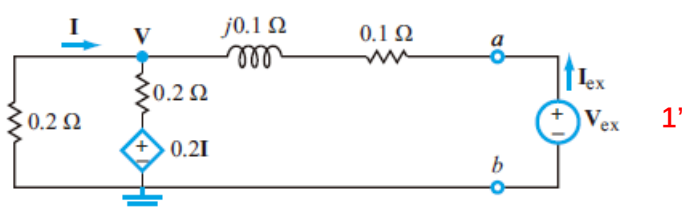

To determine Z_{Th} , we add an external source V_{ex} and compute I_{ex} .

At node V:

$$\frac{V}{0.2} + \frac{V - 0.2I}{0.2} + \frac{V - V_{ex}}{0.1 + j0.1} = 0. \quad 2'$$

Also,

$$I = -\frac{V}{0.2}.$$

Solution leads to

$$\begin{aligned} V &= \left[\frac{25 - j15}{85} \right] V_{ex} = [0.294 - j0.176] V_{ex}. \quad 1' \\ I_{ex} &= \frac{V_{ex} - V}{0.1(1 + j)} \\ &= \frac{10}{1 + j} [1 - 0.294 + j0.176] V_{ex} = (4.41 - j2.65) V_{ex}. \quad 1' \\ Z_{Th} &= \frac{V_{ex}}{I_{ex}} = \frac{1}{4.41 - j2.65} = (0.17 + j0.10) \Omega. \quad 1' \end{aligned}$$

共 3'

$$Z_{TH} = (0.17 + j0.10) \Omega$$



2'

10. (12%) Find v_o in the circuit of Figure 10 using superposition.



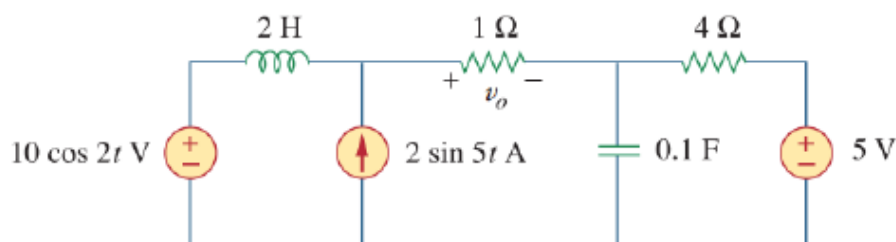


Figure 10

Solution:

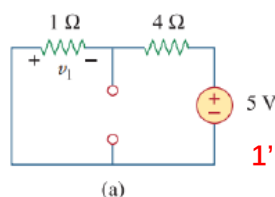

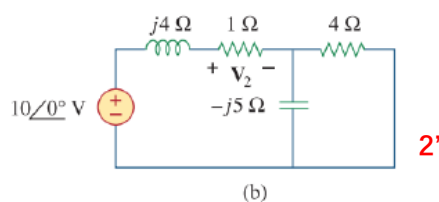
$$-v_1 = \frac{1}{1+4}(5) = 1 \text{ V} \quad 2'$$



$$V_2 = \frac{1}{1+j4+Z}(10 \angle 0^\circ) = \frac{10}{3.439+j2.049} = 2.498 \angle -30.79^\circ$$
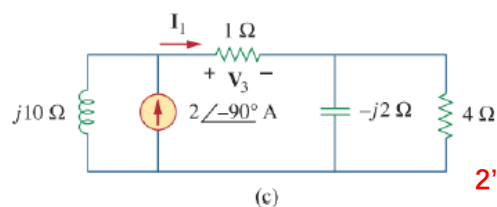
$$v_2 = 2.498 \cos(2t - 30.79^\circ) \quad 2'$$



$$I_1 = \frac{j10}{j10+1+Z_1}(2 \angle -90^\circ) \text{ A}$$

$$V_3 = I_1 \times 1 = \frac{j10}{1.8+j8.4}(-j2) = 2.328 \angle -80^\circ \text{ V}$$

$$v_3 = 2.33 \cos(5t - 80^\circ) = 2.33 \sin(5t + 10^\circ) \text{ V} \quad 2'$$

$$v = v_1 + v_2 + v_3 = -1 + 2.498 \cos(2t - 30.79^\circ) + 2.33 \sin(5t + 10^\circ) \text{ V} \quad 1'$$

少单位则减 1', 扣完为止

11. (10%) The input circuit shown in Figure 11 contains two sources, given by

$$i_s(t) = 2 \cos 10^3 t \text{ A}$$

$$v_s(t) = 8 \sin 10^3 t \text{ V}$$

This input circuit is to be connected to a load circuit that provides optimum performance when the impedance Z of the input circuit is purely real. The circuit includes a “matching” element whose *type* and *magnitude* should be chosen to realize that condition. What should those attributes (type and magnitude) be?


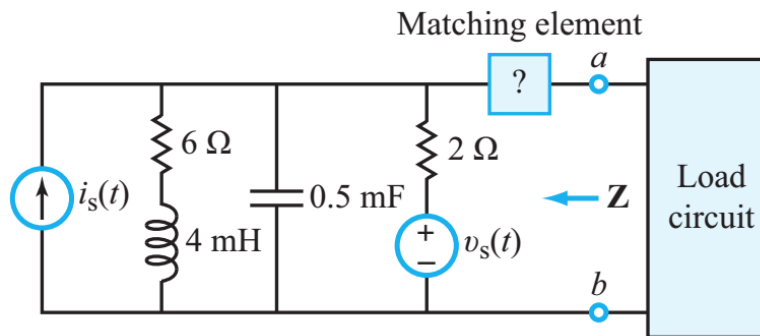


Figure 11

Solution:

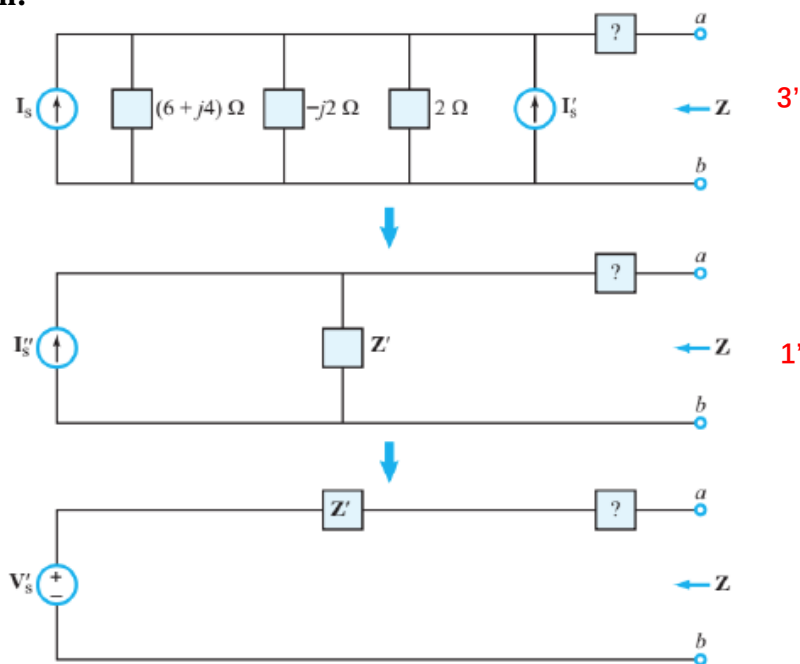

The matching element Z_x has to cancel the imaginary part of Z' . Hence

$$Z_x = +j0.76 \Omega. \quad 1'$$

So it has to be an inductor L such that

$$\omega L = 0.76,$$

or

$$L = \frac{0.76}{10^3} = 0.76 \text{ mH}. \quad 1'$$

$$I'_s = \frac{V_s}{2} = \frac{-j8}{2} = -j4 \text{ A} \quad 1'$$

$$I''_s = I_s + I'_s = (2 - j4) \text{ A} \quad 1'$$

$$Z' = (6 + j4) \parallel (-j2) \parallel 2 = (1.1 - j0.76) \Omega \quad 1'$$

$$V_{Th} = V'_s = I''_s Z' = (2 - j4)(1.1 - j0.76) = -(0.84 + j5.92) \text{ V}.$$

少单位则减 1', 扣完为止