

## Homework 2

Due date:

Mar.17<sup>th</sup>, 2021


Turn in your homework in class

Rules:

- Please work on your own. Discussion is permissible, but extremely similar submissions will be judged as plagiarism!
- Please show all intermediate steps: a correct solution without an explanation will get zero credit.
- Please submit on time. No late submission will be accepted.
- Please prepare your submission in English only. No Chinese submission will be accepted.

1. [12%] The circuit is shown in **Fig 1**.


- Use superposition theorem to find  $i'$ ,  $V'$  and the power absorbed by the dependent source.
- Calculate the power absorbed by the independent sources.

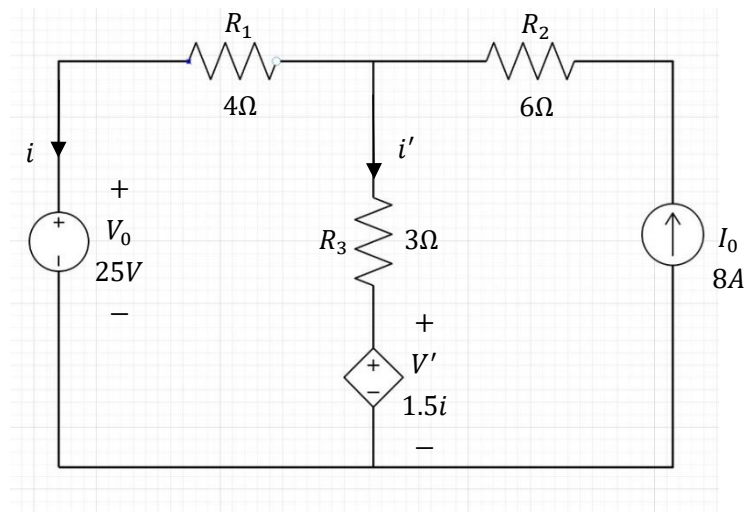


**Fig 1.**

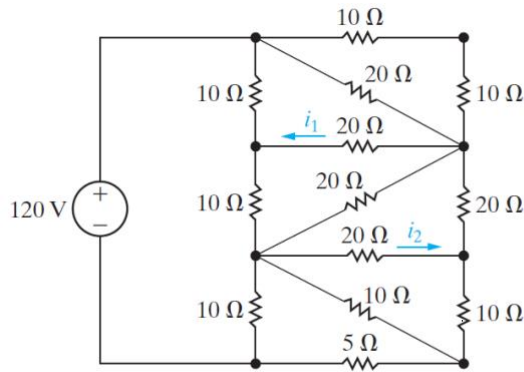2. [13%] The circuits are shown in **Fig 2.1** and **Fig 2.2**.

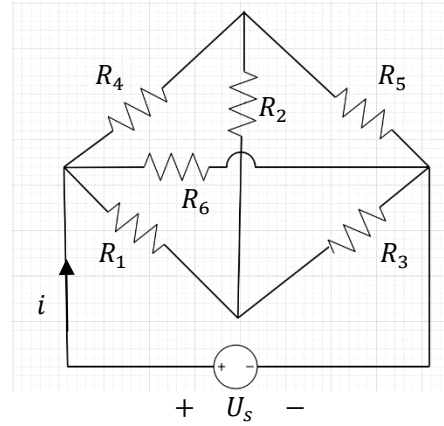- a) Find  $i_1$  and  $i_2$  in the circuit shown in **Fig 2.1**.
- b) In **Fig 2.2**,  $R_1 = 5\Omega$ ,  $R_2 = 3\Omega$ ,  $R_3 = 4\Omega$ ,  $R_4 = 7\Omega$ ,  $R_5 = 8\Omega$ ,  $R_6 = 9\Omega$ ,  $U_s = 1V$ , Find  $i$  in the circuit shown in **Fig 2.2** (Hint: You can use  $Y - \Delta$  transformation to simply the circuit.)

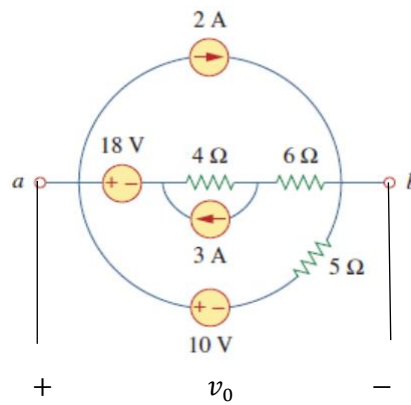


**Fig 2.1.**

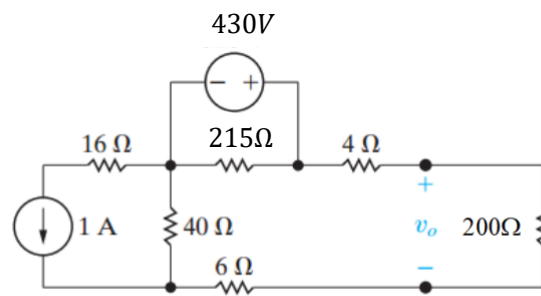


**Fig 2.2.**

3. [11%] The circuit is shown in **Fig 3**.
- a) Using superposition theorem to find  $v_0$
  - b) Using source transformation to find  $v_0$
  - c) Find the Thevenin and Norton equivalent circuit at terminals a and b.

**Fig 3.**

4. [10%] The circuit is shown in **Fig 4**.
- Use source transformation to find  $v_o$  in the circuit in **Fig 4**.
  - Find the power extracted from the 430V source.
  - Find the power extracted from the 1A current source.
  - Verify that the total power delivered equals the total power dissipated.

**Fig 4.**

5. [10%] The circuit is shown in Fig 5.

- Find the Norton equivalent circuit at terminals a, b.
- If we replace the dependent source in the red frame (the voltage of the dependent source is  $250i_x$ ) with an independent source  $V_1 = 5V$ . We connect a load resistance  $R_L$  between terminal a and b. Find  $R_L$  for maximum power deliverable to  $R_L$ .
- Under b) condition, determine the maximum power on  $R_L$ .

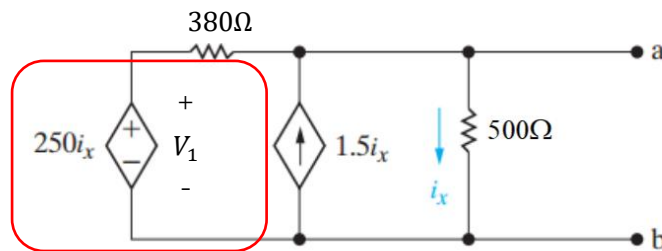


Fig 5.

6. [6%] For the circuit in Fig. 6, find  $k$  from the given voltage transfer function of  $V_o/V_s = -3.1875$ . Assume that all Op Amps are ideal and work in their linear regions.

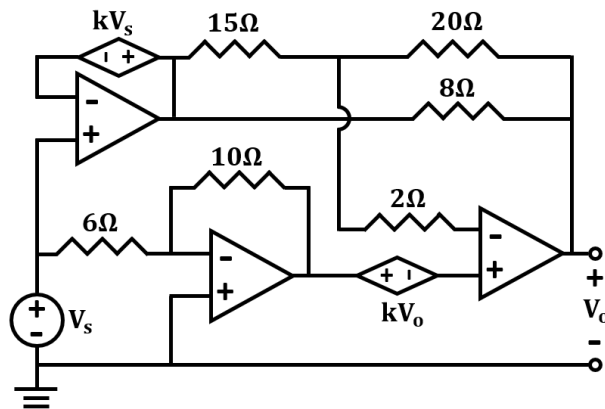


Fig 6.

7. [6%] Consider the circuit in the following Fig. 7 that  $v_A = 0.7\text{V}$  and  $v_B = 1.2\text{V}$ . Find the output voltage  $v_o$  assuming that all Op Amps are ideal and work in their linear regions.

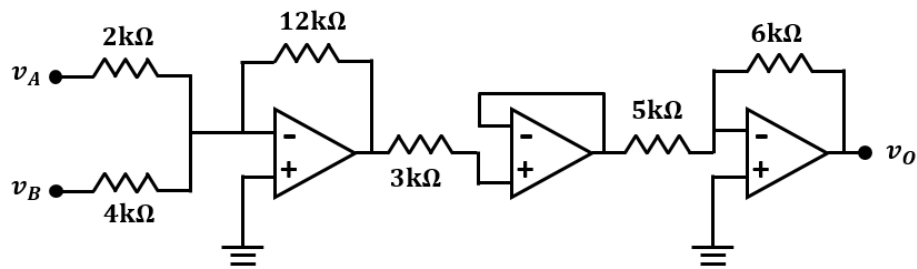


Fig 7.

8. [10%] The circuit in the Fig. 8 is some kind of a differential amplifier.  $V_{CC} = 4V$ . Assume that the Op Amp is ideal.
- a) Derive an expression for the output voltage  $v_o$  in terms of  $v_1$ ,  $v_2$ ,  $R_1$ ,  $R_2$ ,  $R_3$  and  $R_4$ .
  - b) If we connect a load resistor  $R_L$  between the output (node  $v_o$ ) and the ground, would the result of the previous expression change for  $v_o$ ? Why?
  - c) Let  $v_2 = 2v_1$ ,  $R_1 = 3k\Omega$ ,  $R_2 = 15k\Omega$ , and  $R_3 = 6k\Omega$ . Find  $R_4$  so that  $v_o = 0$ .
  - d) Let  $v_1 = 3V$  and  $v_2 = 1V$ . Using the values given in c) part including the computed value for  $R_4$ , find  $v_o$ .

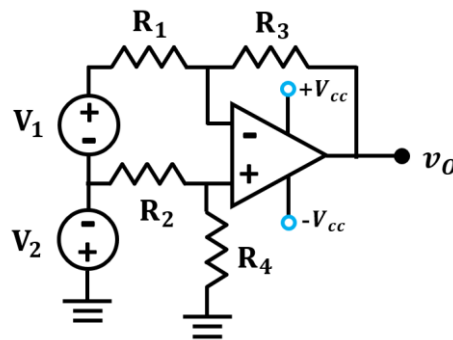


Fig 8.



9. [12%] For the circuit of the Figure below, if we want to have a maximum power of **60mW** transfer into the resistor load  $R_o$ , what resistance values should  $R_L$  and  $R_o$  be? Assume that the Op Amp is ideal.

(Hint: you can first calculate the Thevenin equivalent circuit at terminal  $v_o$  and the ground (neglecting  $R_o$ ). Afterwards, use maximum power transfer theory to find proper  $R_L$  and  $R_o$ .)

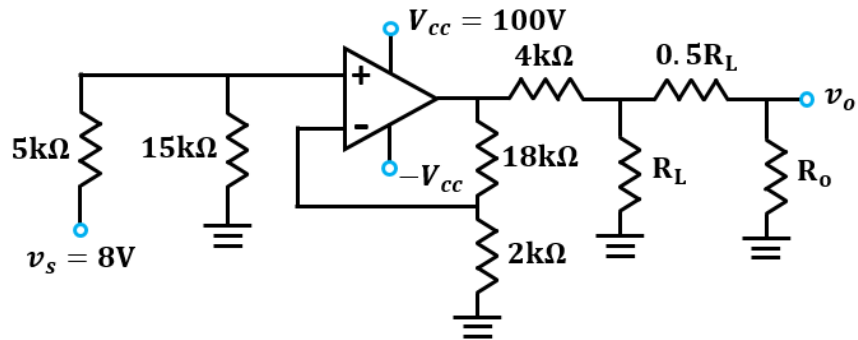
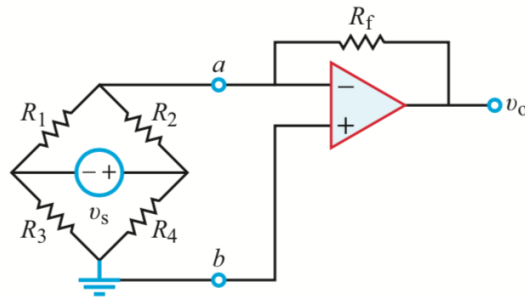


Fig 9.

10. [10%] In the circuit of Figure below, a bridge circuit (circuit on the left part of the terminal (a, b) ) is connected at the input side of an inverting Op Amp circuit. Assume that the Op Amp is ideal and work in the linear region.
- Obtain the Thevenin equivalent at terminal (a, b) for the left side circuit in terms of  $v_s$ ,  $R_1$ ,  $R_2$ ,  $R_3$  and  $R_4$ .
  - Use the result in (a) and  $R_f$  to obtain an expression for  $G = v_o/v_s$ .
  - Evaluate  $G$  for  $R_1 = R_4 = 100\Omega$ ,  $R_2 = R_3 = 101\Omega$ , and  $R_f = 100k\Omega$ .

**Fig 10.**