

Homework 4

Due date: Apr. 9th, 2018
Turn in your homework in class

Rules:

- Work on your own. Discussion is permissible, but extremely similar submissions will be judged as plagiarism.
- Please show all intermediate steps: a correct solution without an explanation will get zero credit.
- Please submit on time. No late submission will be accepted.
- Please prepare your submission in English only. No Chinese submission will be accepted.

1. The current in a $150\mu\text{H}$ inductor is known to be:

$$i_L = 25te^{-500t} \text{ A for } t \geq 0$$

- (a) Find the voltage across the inductor for $t > 0$.
(b) Find the power (in microwatts) at the terminals of the inductor when $t = 5\text{ms}$.

$$[\text{a}] \quad v = L \frac{di}{dt}$$

$$= (150 \times 10^{-6})(25)[e^{-500t} - 500te^{-500t}] = 3.75e^{-500t}(1 - 500t) \text{ mV}$$

$$[\text{b}] \quad i(5\text{ms}) = 25(0.005)(e^{-2.5}) = 10.26 \text{ mA}$$

$$v(5\text{ms}) = 0.00375(e^{-2.5})(1 - 2.5) = -461.73 \mu\text{V}$$

$$p(5\text{ms}) = vi = (10.26 \times 10^{-3})(-461.73 \times 10^{-6}) = -4.74 \mu\text{W}$$

2. Assume that the initial energy stored in the inductors of Fig. 1 is zero. Find the equivalent inductance with respect to the terminals a, b.

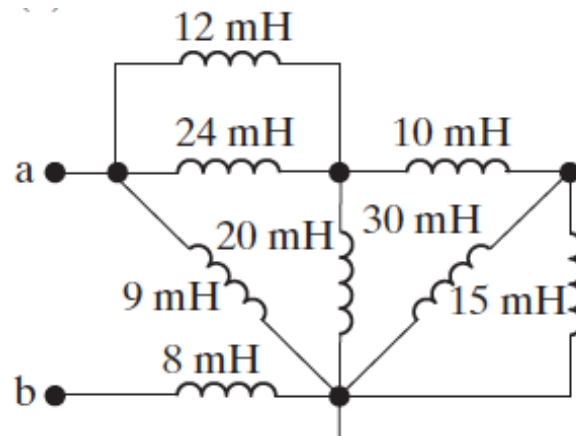


Fig. 1

$$[\mathbf{a}] \quad 15 \parallel 30 = 10 \text{ mH}$$

$$10 + 10 = 20 \text{ mH}$$

$$20 \parallel 20 = 10 \text{ mH}$$

$$12 \parallel 24 = 8 \text{ mH}$$

$$10 + 8 = 18 \text{ mH}$$

$$18 \parallel 9 = 6 \text{ mH}$$

$$L_{ab} = 6 + 8 = 14 \text{ mH}$$

3. The capacitance and associated voltage for each capacitor is given in Fig. 2. Find the equivalent capacitance and the associated voltage with respect to the terminals a, b for the circuit shown in Fig. 2.


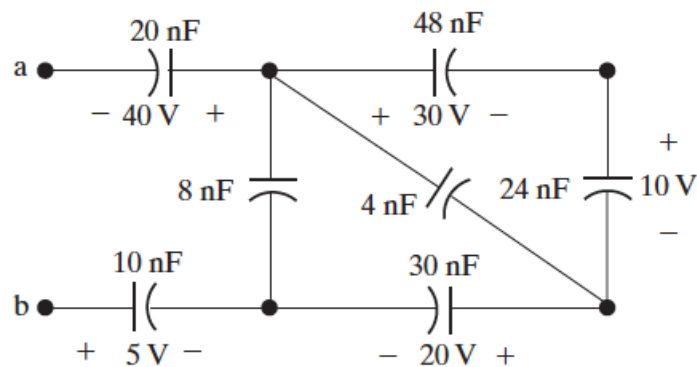


Fig. 2


$$[a] \quad \frac{1}{C_1} = \frac{1}{48} + \frac{1}{24} = \frac{1}{16}; \quad C_1 = 16 \text{ nF}$$

$$C_2 = 4 + 16 = 20 \text{ nF}$$

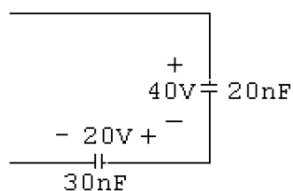


$$\frac{1}{C_3} = \frac{1}{20} + \frac{1}{30} = \frac{1}{12}; \quad C_3 = 12 \text{ nF}$$

$$C_4 = 12 + 8 = 20 \text{ nF}$$

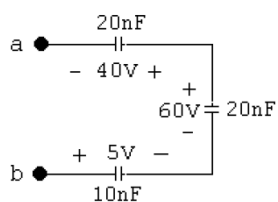

$$\frac{1}{C_5} = \frac{1}{20} + \frac{1}{20} + \frac{1}{10} = \frac{1}{5}; \quad C_5 = 5 \text{ nF}$$

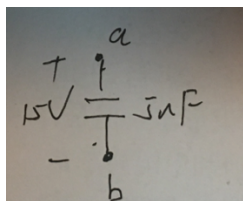Equivalent capacitance is 5 nF with an initial voltage drop of +15 V.



4. The switch in the circuit in Fig. 3 has been open for a long time. At $t = 0$ the switch is closed.
- (a) Determine $i_o(0)$ and $i_o(\infty)$.
- (b) Determine $i_o(t)$ for $t \geq 0$.

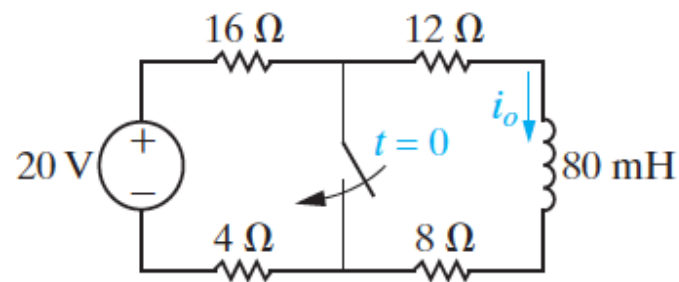


Fig. 3

$$[\mathbf{a}] \quad i_o(0) = \frac{20}{16 + 12 + 4 + 8} = \frac{20}{40} = 0.5 \text{ A}$$

$$i_o(\infty) = 0 \text{ A}$$

$$[\mathbf{b}] \quad i_o = 0.5e^{-t/\tau}; \quad \tau = \frac{L}{R} = \frac{80 \times 10^{-3}}{12 + 8} = 4 \text{ ms}$$

$$i_o = 0.5e^{-250t} \text{ A}, \quad t \geq 0$$

5. The switch shown in Fig. 4 has been open for a long time before closing at $t = 0$. Write the expression for the capacitor voltage, $v(t)$, for $t \geq 0$.


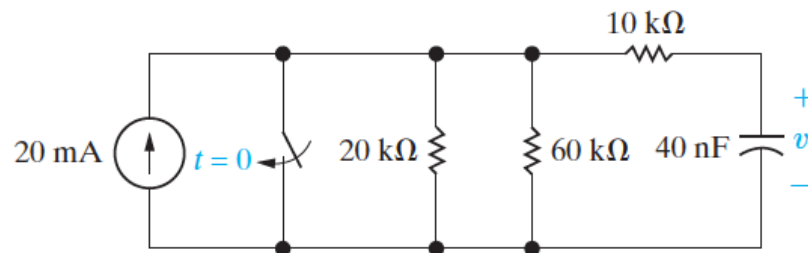



Fig. 4

For $t < 0$:

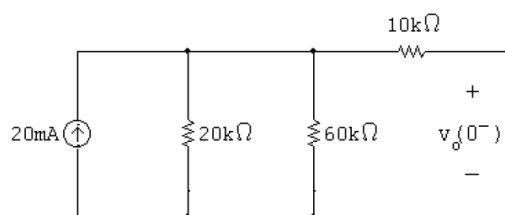

$$V_o = (20,000 \parallel 60,000)(20 \times 10^{-3}) = 300 \text{ V}$$

For $t \geq 0$:

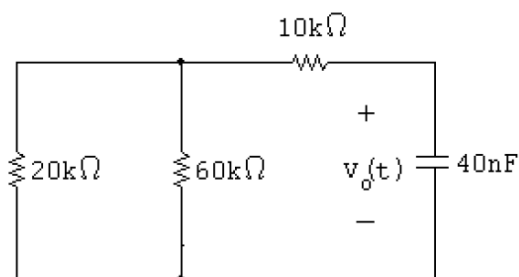

$$R_{eq} = 10,000 + (20,000 \parallel 60,000) = 25 \text{ k}\Omega$$

$$\tau = R_{eq}C = (25,000)(40 \times 10^{-9}) = 1 \text{ ms}$$

$$v(t) = V_o e^{-t/\tau} = 300 e^{-1000t} \text{ V} \quad t \geq 0$$