



Lecture 2

Kirchhoff's Laws & Circuit Analysis




Outline

- Kirchhoff's Laws
 - KCL
 - KVL
- Circuit Analysis
 - Nodal Analysis
 - Mesh Analysis



七桥问题

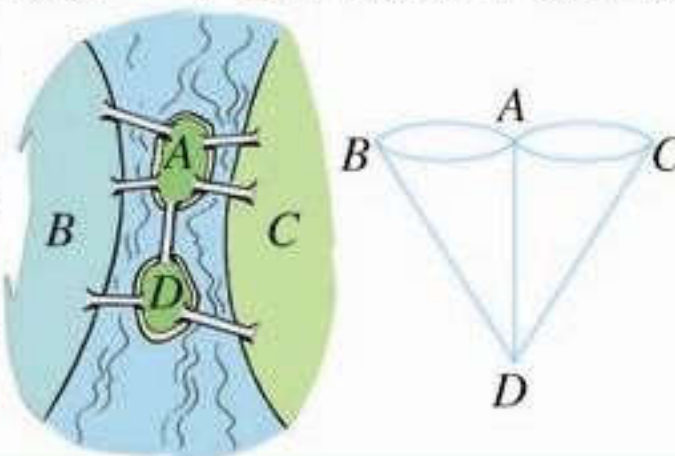
18 世纪东普鲁士的哥尼斯堡城，有一条河穿过，河上有两个小岛，有七座桥把两个岛与河岸联系起来（如下图）。有人提出一个问题：一个步行者怎样才能不重复、不遗漏地一次走完七座桥，最后回到出发点。后来大数学家欧拉把它转化成一个几何问题（如右图）——一笔画问题。





Terminology: Nodes, Branches and Loops

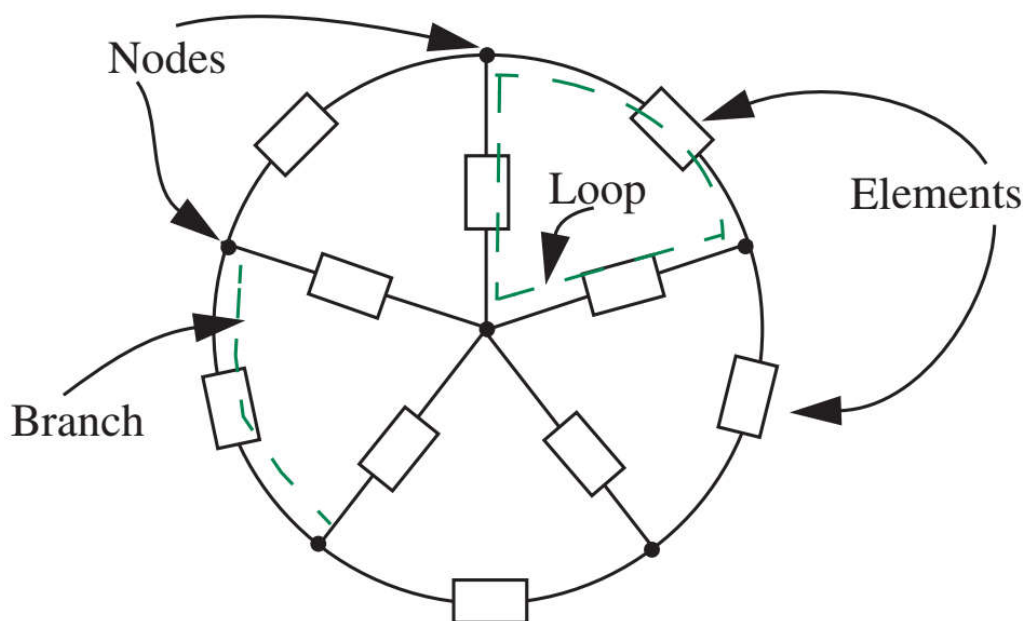- **Node**: A point where two or more circuit elements are connected.
- **Branch**: A path that connects two nodes.
- **Loop**: Any closed path in a circuit.






Kirchhoff's Laws

- Kirchhoff's Current Law (KCL):
 - The algebraic sum of all the **currents** entering any **node** in a circuit equals zero.
 - Why?

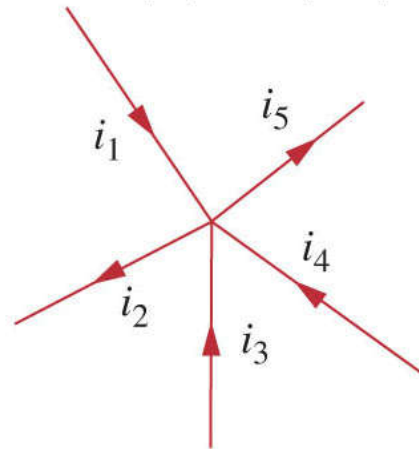Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display




Gustav Robert Kirchhoff
1824-1887



A Major Implication of KCL

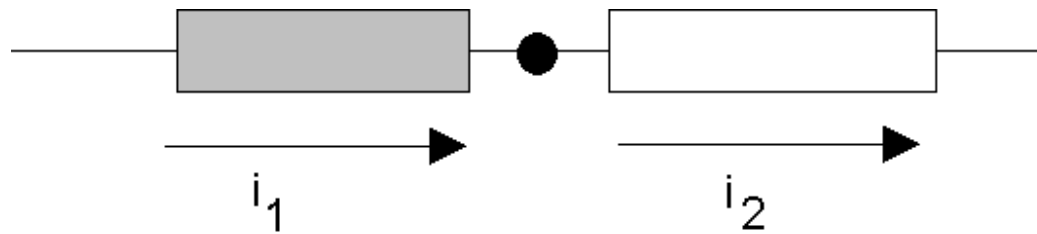- KCL tells us that **all of the elements that are connected *in series* carry the same current.**




Current entering node = Current leaving node



Generalization of KCL



- The sum of currents entering/leaving a **closed surface** is zero.
 - Circuit branches can be inside this surface, *i.e.* the surface can enclose more than one node!

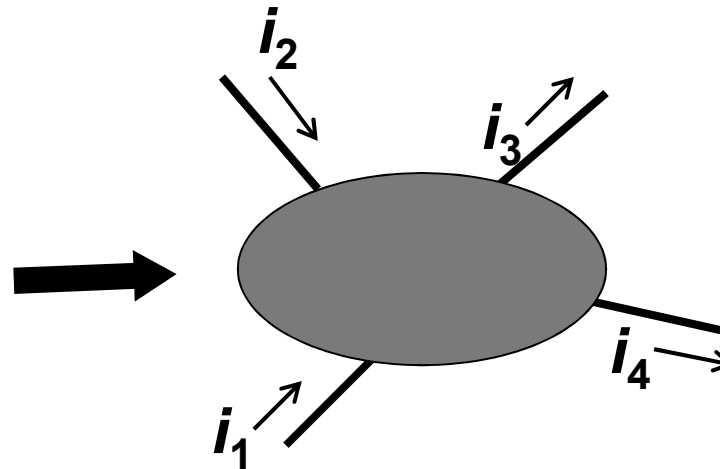This could be a big chunk of a circuit, *e.g.* a “black box”






Generalized KCL Examples

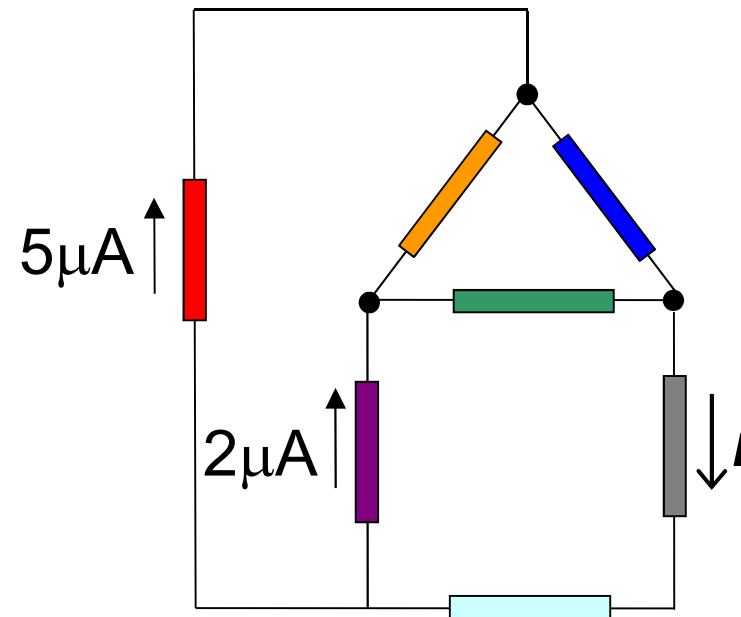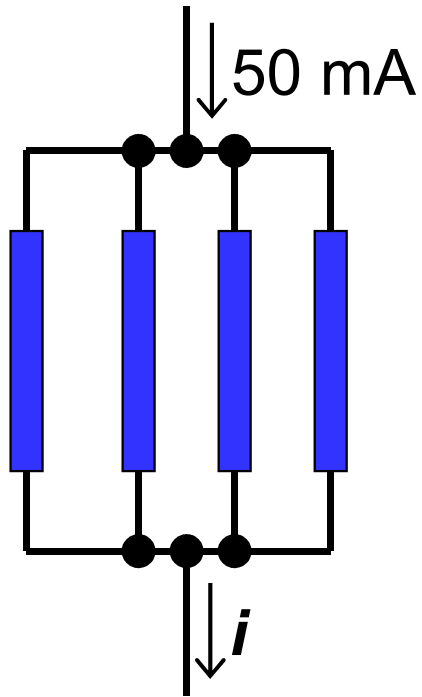




When will KCL be Invalid?

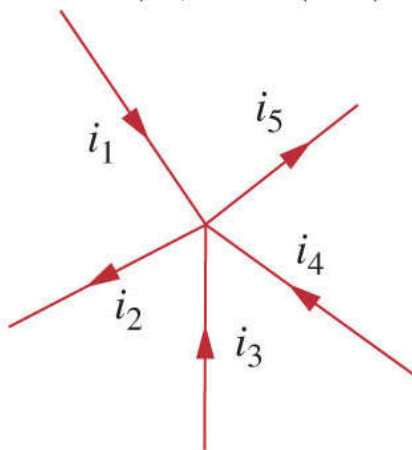Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display





Notation: Node and Branch Voltages

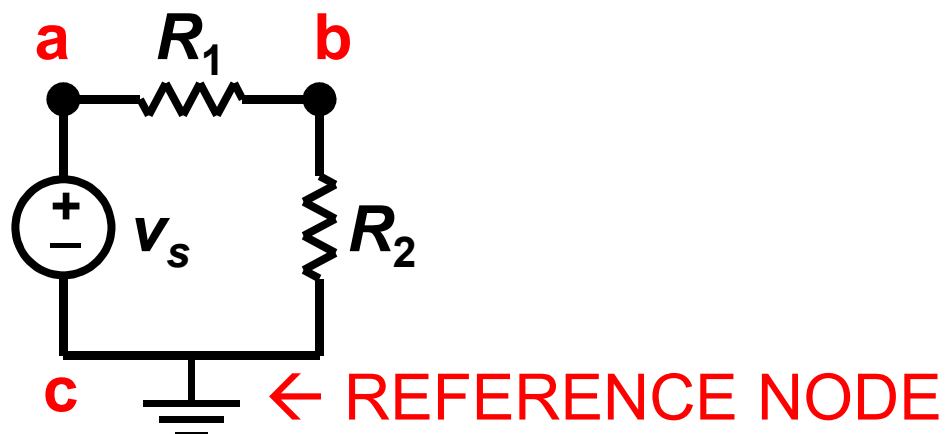


- Use one node as the reference (the “common” or “ground” node) – label it with a symbol.
- The voltage drop from node x to the reference node is called the **node voltage** v_x .
- The voltage across a circuit element is defined as the difference between the node voltages at its terminals.



Kirchhoff's Voltage Law (KVL)

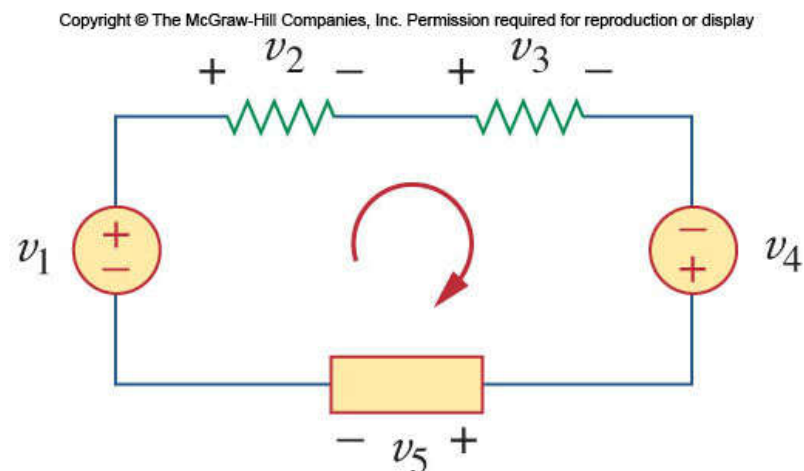
- The algebraic sum of all the **voltages** around any **loop** in a circuit equals zero.
- **Why?**





KVL Example

Three closed paths:

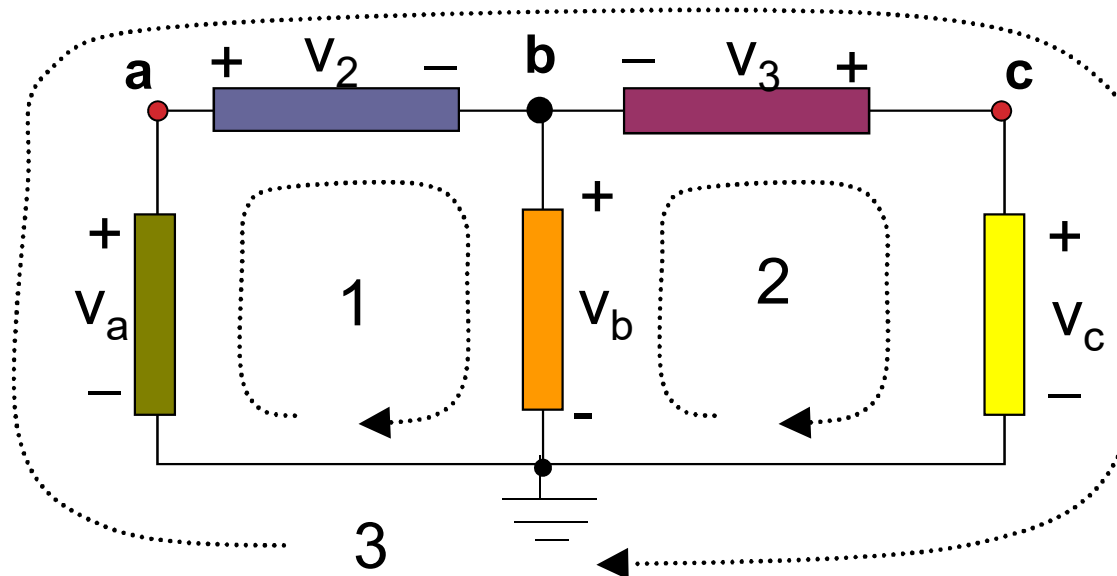

Path 1:


Path 2:

Path 3:




A Major Implication of KVL

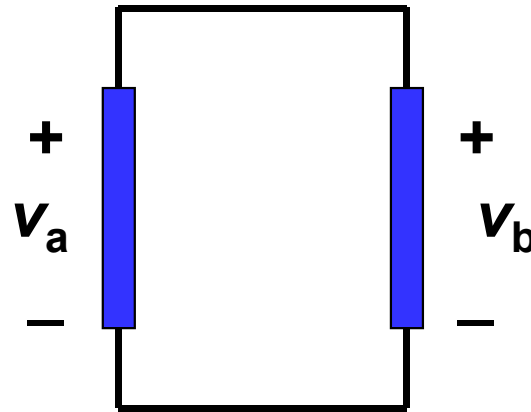- KVL tells us that **any set of elements which are connected at both ends carry the same voltage.**
- We say these elements are connected **in parallel.**






Series Resistors

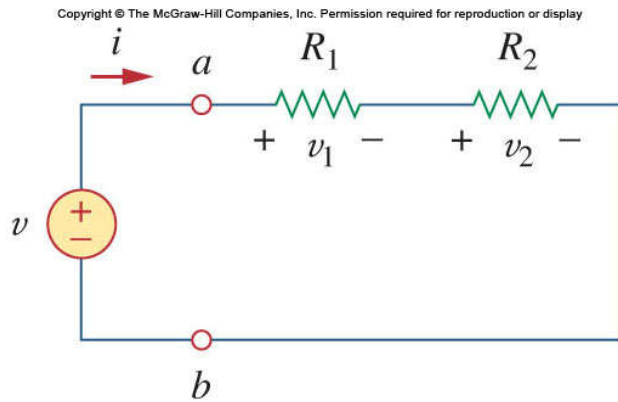


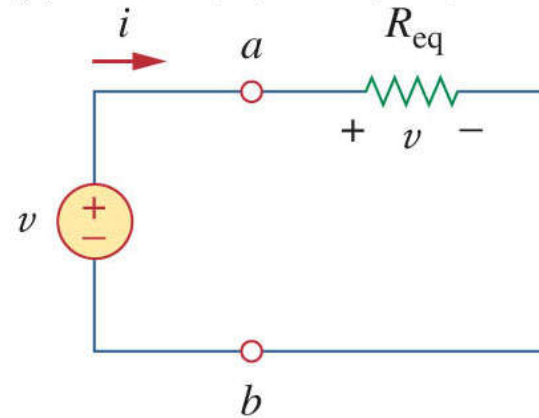Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display





Voltage Division


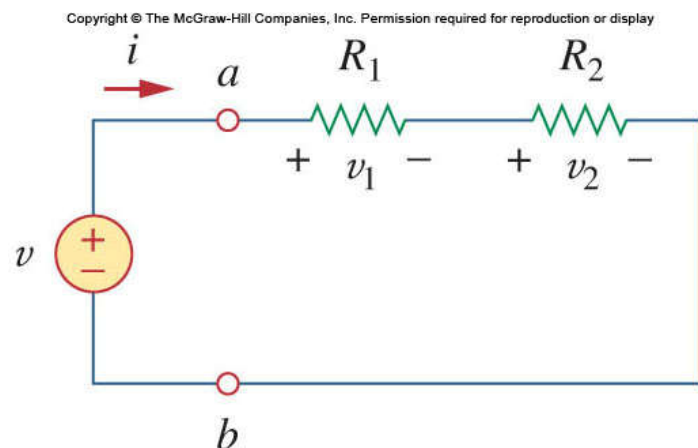


Three-terminal rheostat





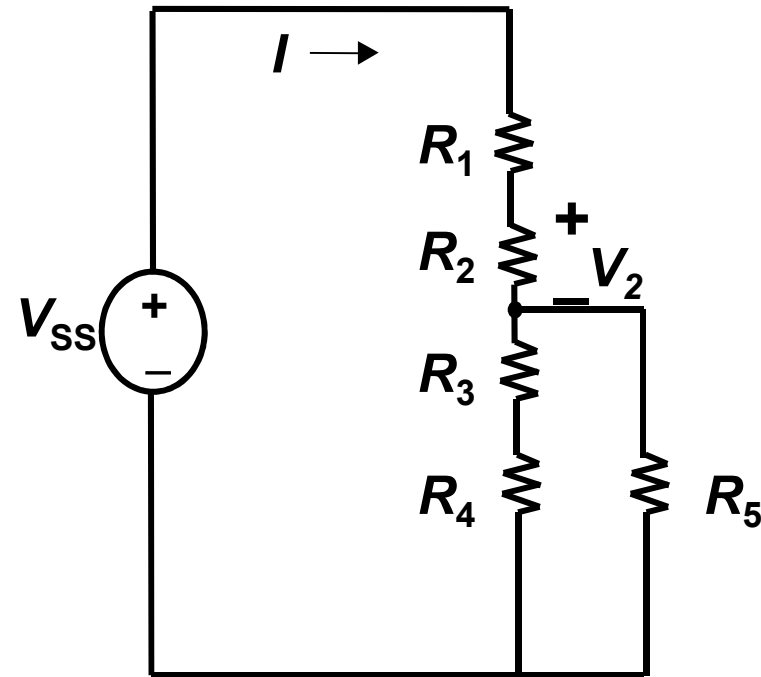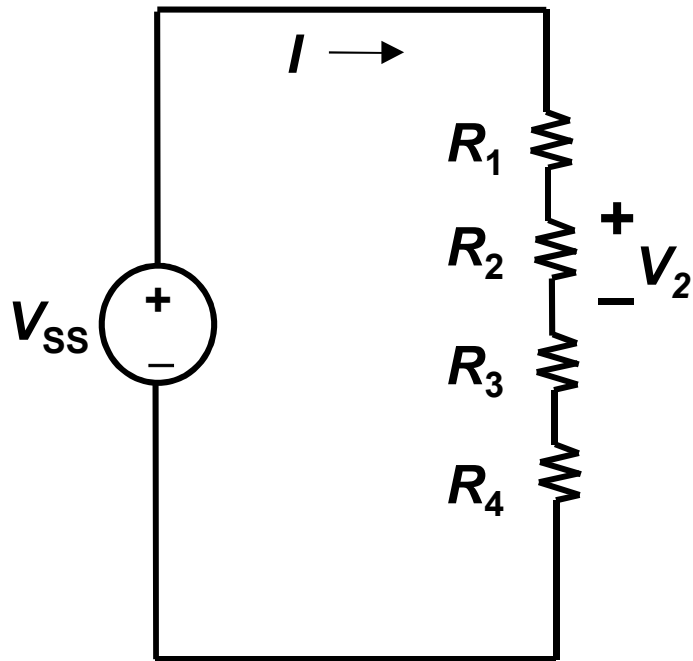
When can the Voltage Divider Formula be Used?






Parallel Resistors

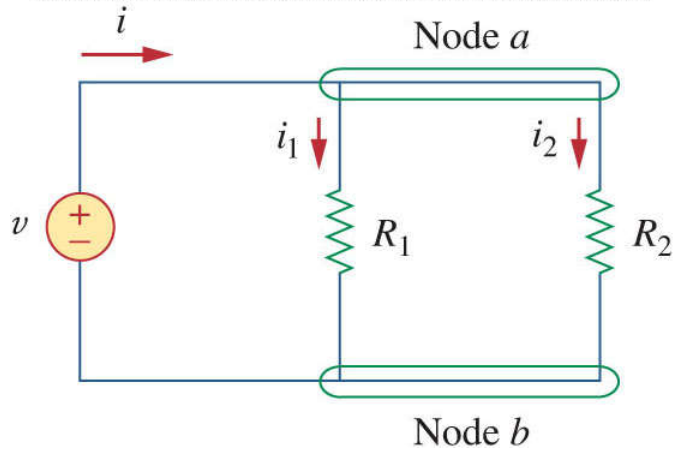Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display




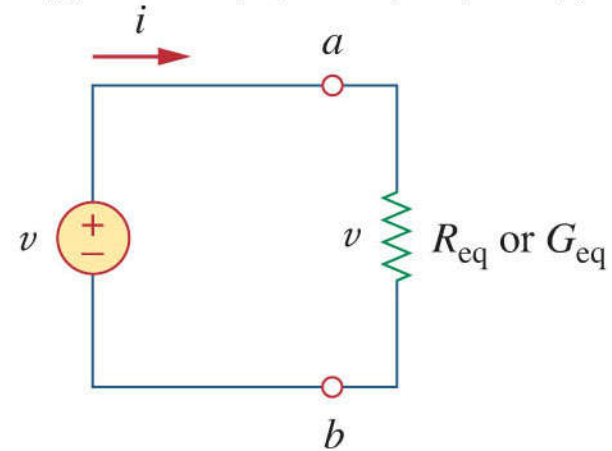Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display






Current Division

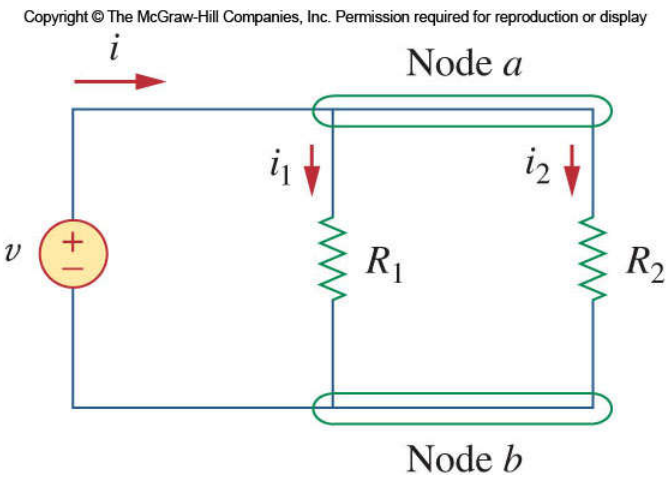



Exercise

- Find the voltage across each resistor

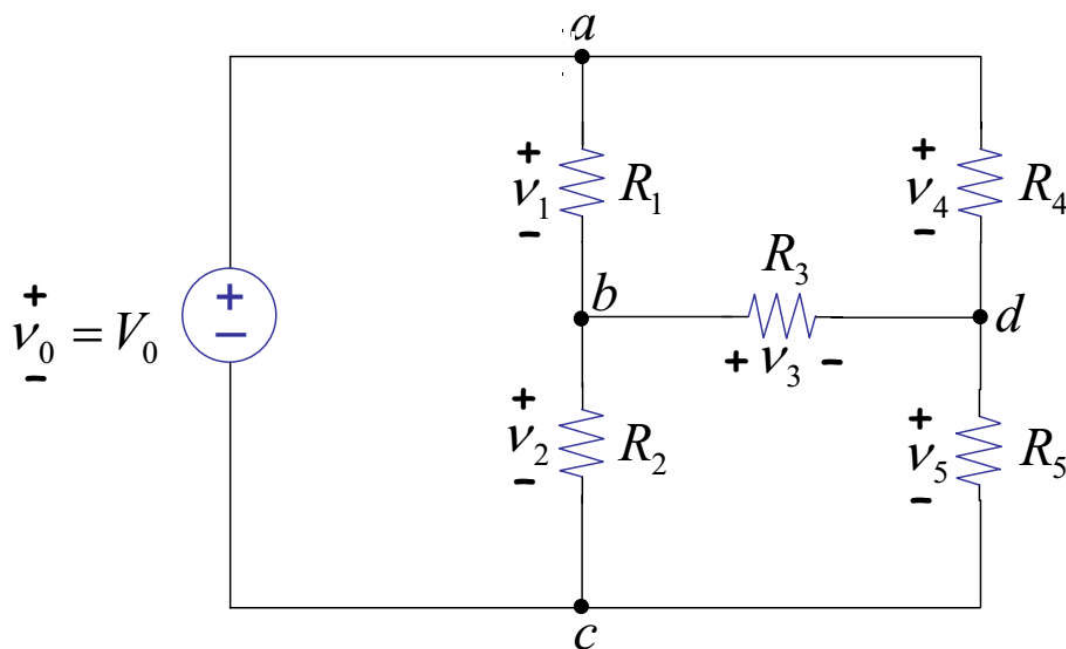




Summary

- KCL and KVL


$$\sum_{n=1}^N i_n = 0$$

$$\sum_{m=1}^M v_m = 0$$

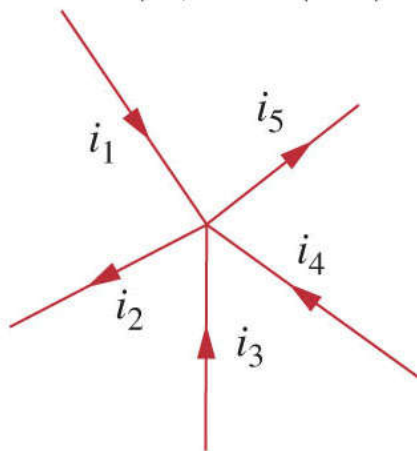Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display



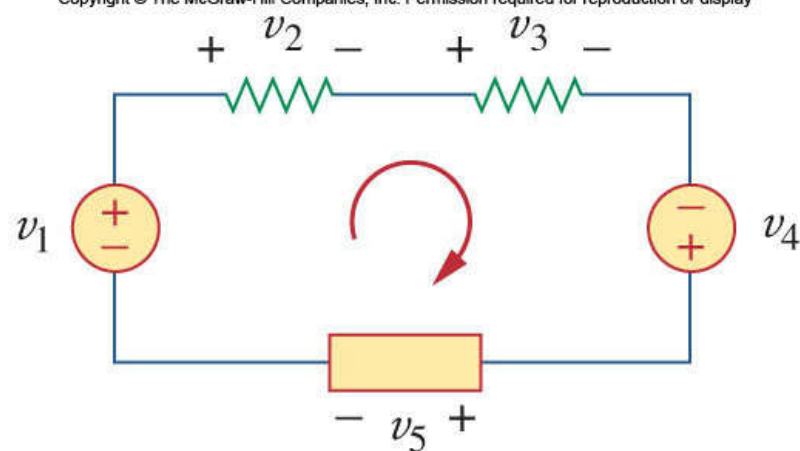
Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display








What you have learned

- KCL
- KVL
- Element relationships

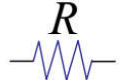For R, $V = IR$ 

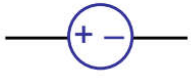For voltage source, $V = V_0$ 

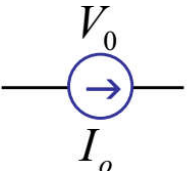For current source, $I = I_0$ 

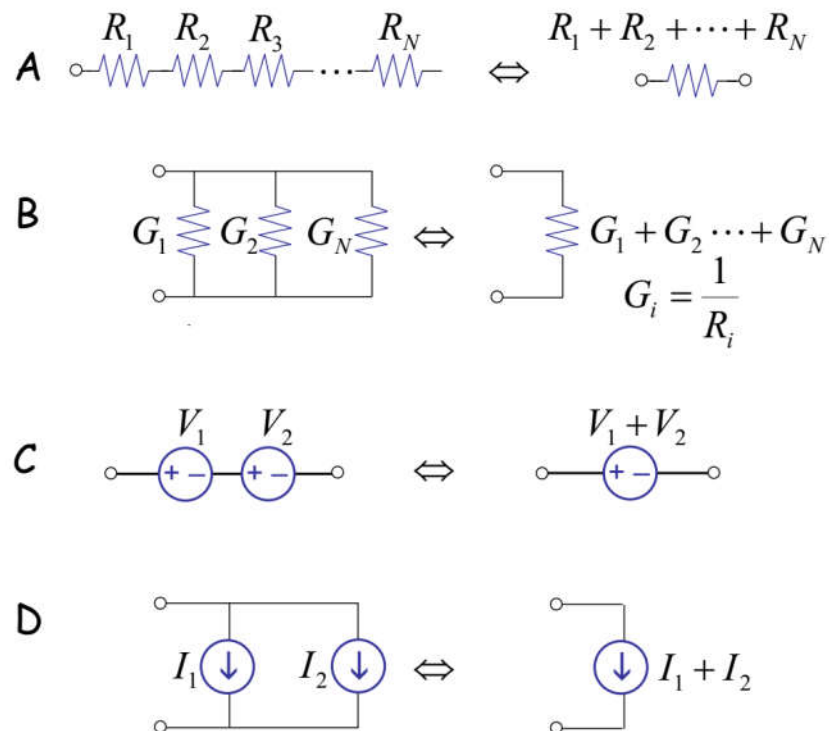



Circuit Analysis


- Two techniques will be presented in this lecture:
 - Nodal analysis, which is based on KCL
 - Used in SPICE, the internal engine of circuit simulators.
 - Mesh analysis, which is based on KVL
- The analysis will result in a set of simultaneous equations which may be solved by Cramer's rule or computationally (using MATLAB for example)

<http://bwracs.eecs.berkeley.edu/Courses/IcBook/SPICE/>

<http://www.ni.com/white-paper/5413/zhs/>



Example

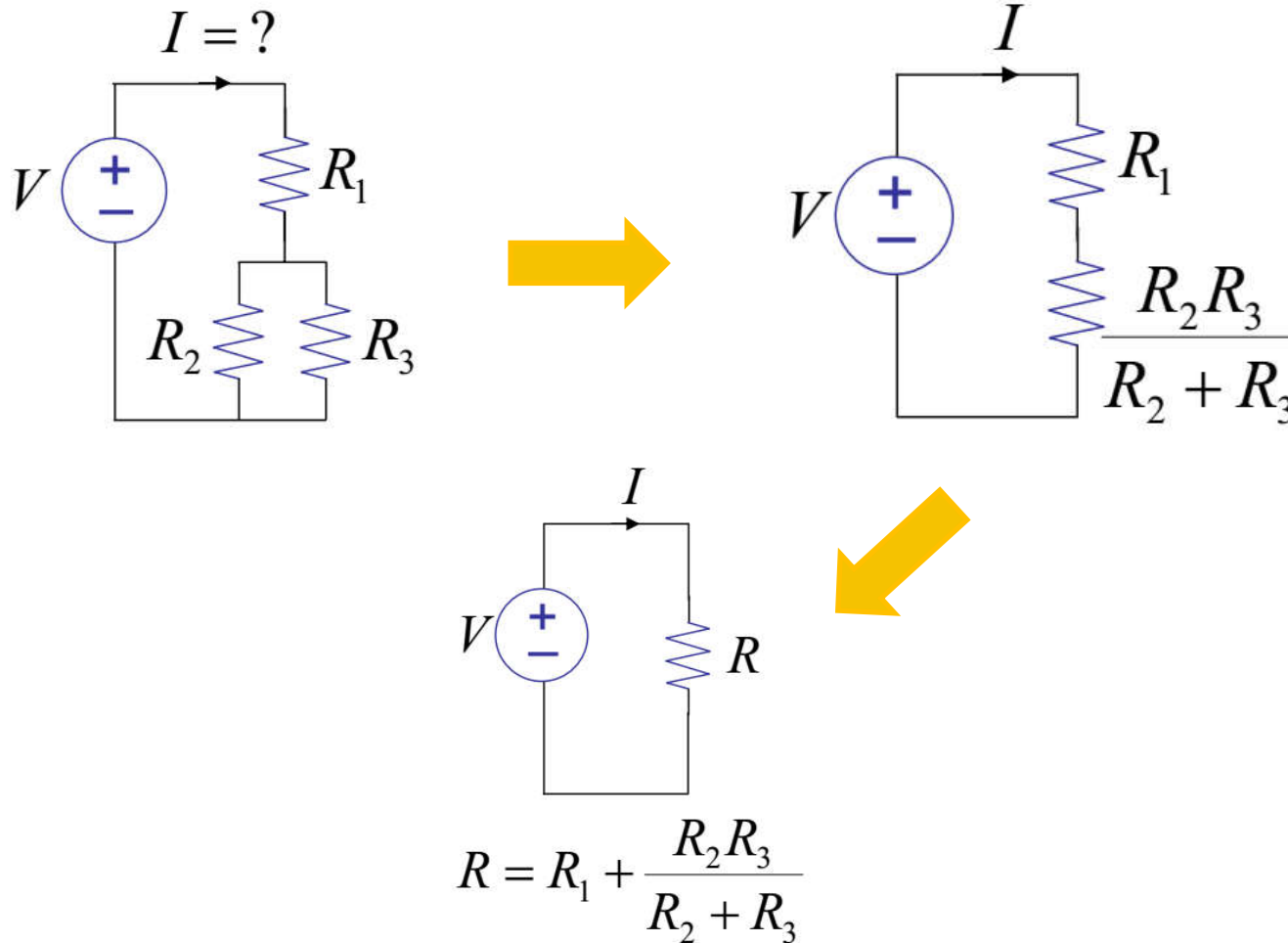







Nodal Analysis – Three Steps

- Given a circuit with n nodes, the nodal analysis is accomplished via three steps:
 1. Select a node as the reference (i.e., ground) node. Define the node voltages (**except reference node and the ones set by the voltage sources**). Voltages are relative to the reference node.
 2. Apply KCL at nodes with unknown voltage, expressing current in terms of the node voltages (using the I - V relationships of branch elements).
Special cases: floating voltage sources.
 3. Solve the resulting simultaneous equations to obtain the unknown node voltages.



Nodal Analysis Example #1

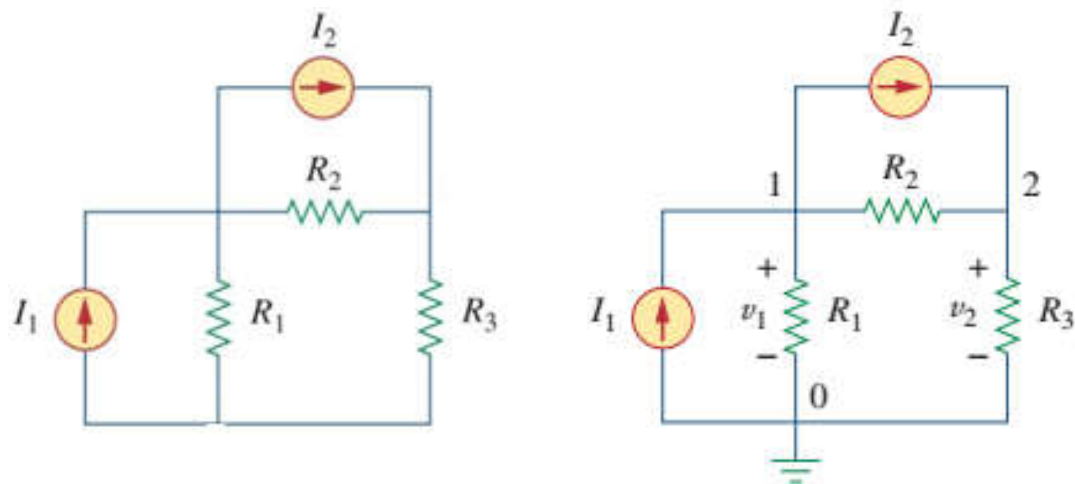

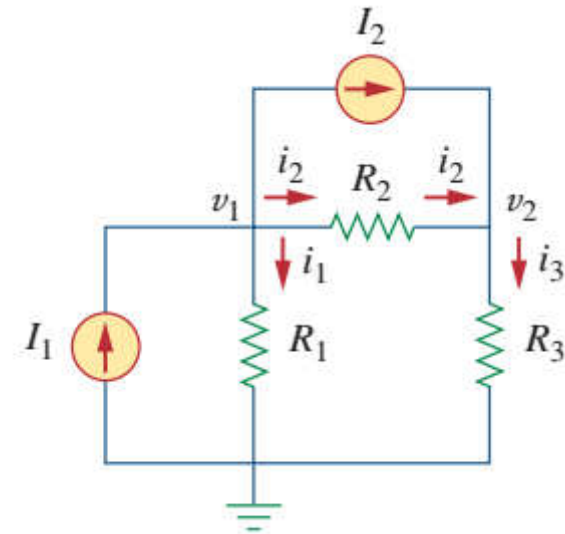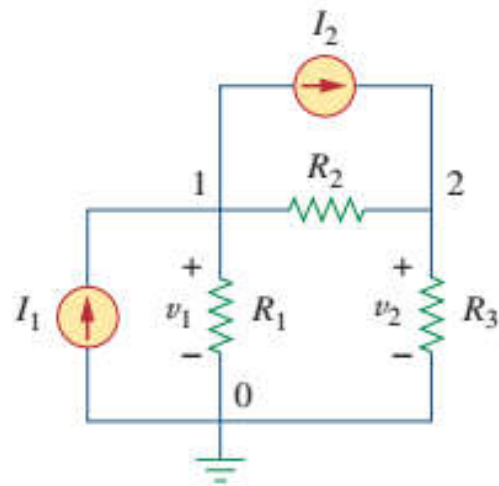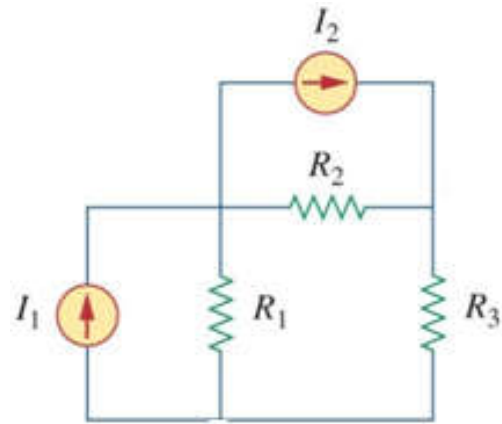



Cramer's Rule:
(optional)


$$\begin{cases} a_{11}x_1 + a_{12}x_2 = b_1 \\ a_{21}x_1 + a_{22}x_2 = b_2 \end{cases}$$

方程组有唯一解 $\Leftrightarrow \begin{vmatrix} a_{11} & a_{12} \\ a_{21} & a_{22} \end{vmatrix} \neq 0$

$$x_1 = \frac{\begin{vmatrix} b_1 & a_{12} \\ b_2 & a_{22} \end{vmatrix}}{\begin{vmatrix} a_{11} & a_{12} \\ a_{21} & a_{22} \end{vmatrix}}, \quad x_2 = \frac{\begin{vmatrix} a_{11} & b_1 \\ a_{21} & b_2 \end{vmatrix}}{\begin{vmatrix} a_{11} & a_{12} \\ a_{21} & a_{22} \end{vmatrix}}$$





Nodal Analysis: Example #2

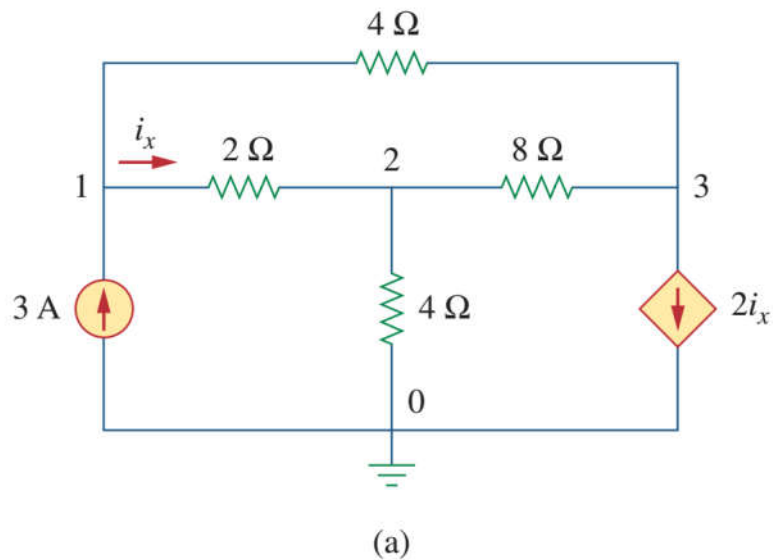



Nodal Analysis: Example #2

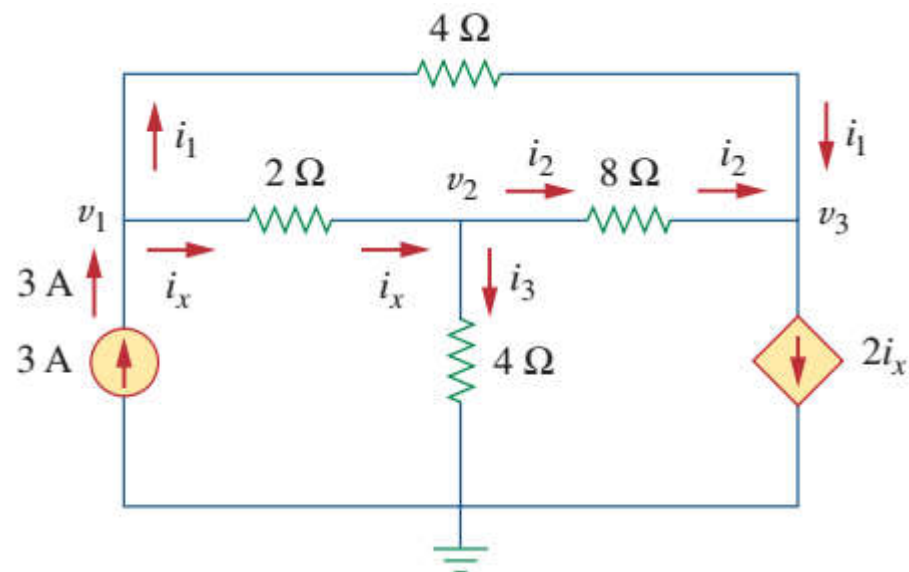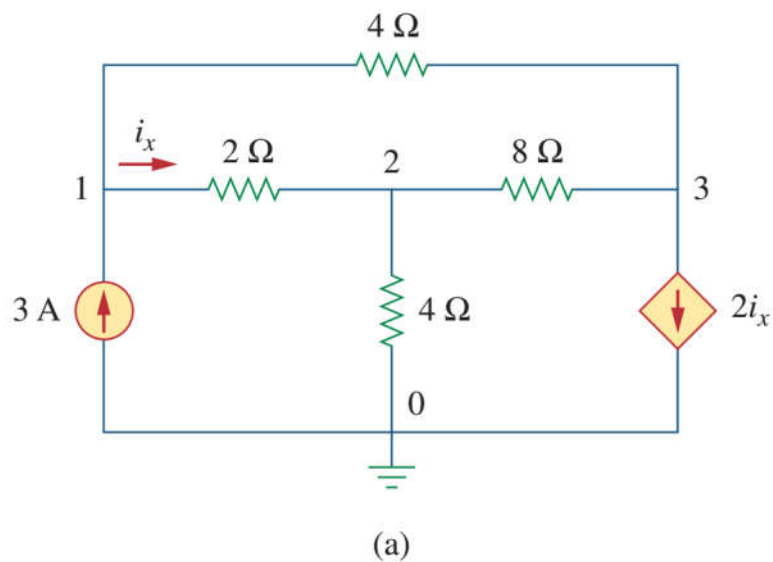





Nodal Analysis with Voltage Sources

Challenges:

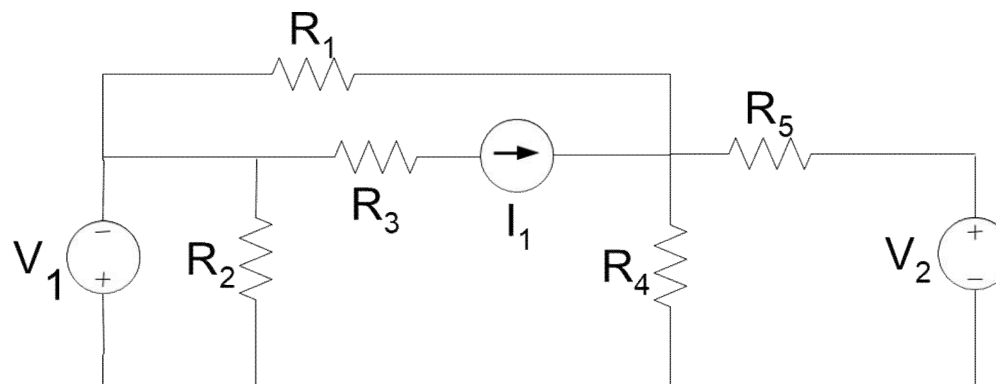- Determine node number
- Deal with different types of sources




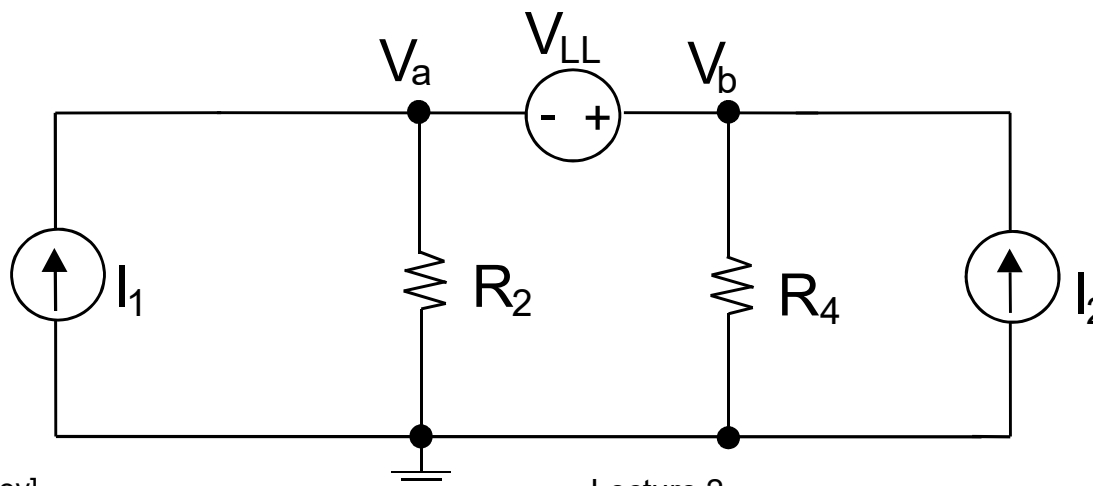A “floating” voltage source is one for which **neither** side is connected to the reference node, e.g. V_{LL} in the circuit below:






Nodal Analysis: Supernode

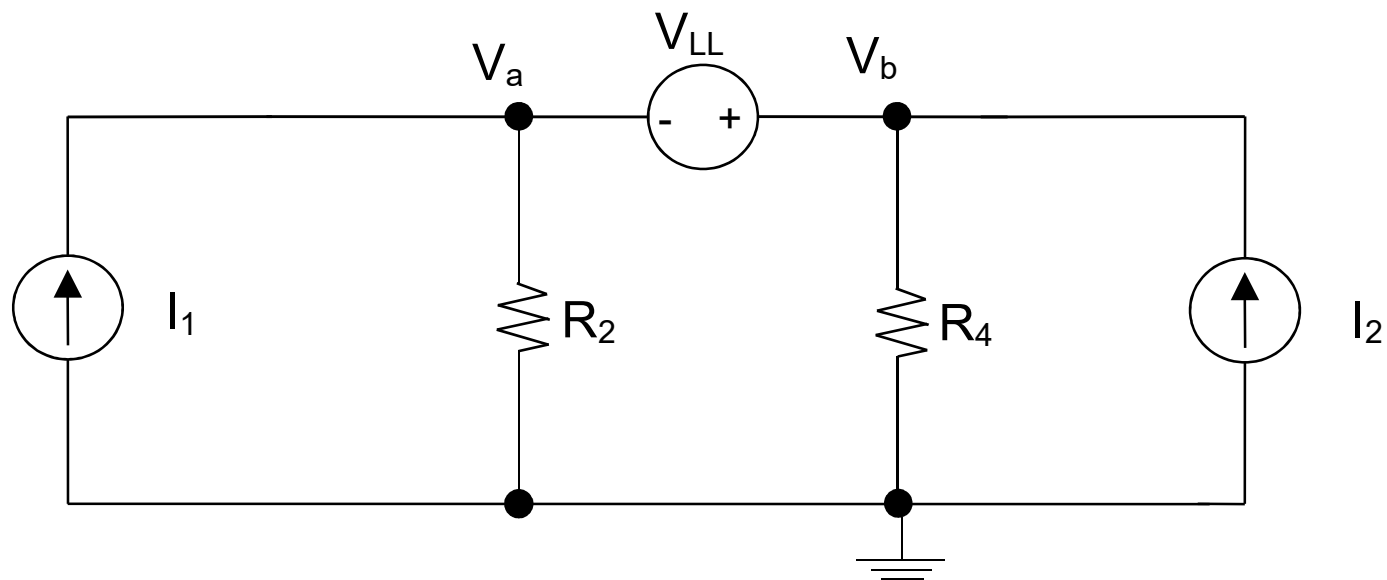



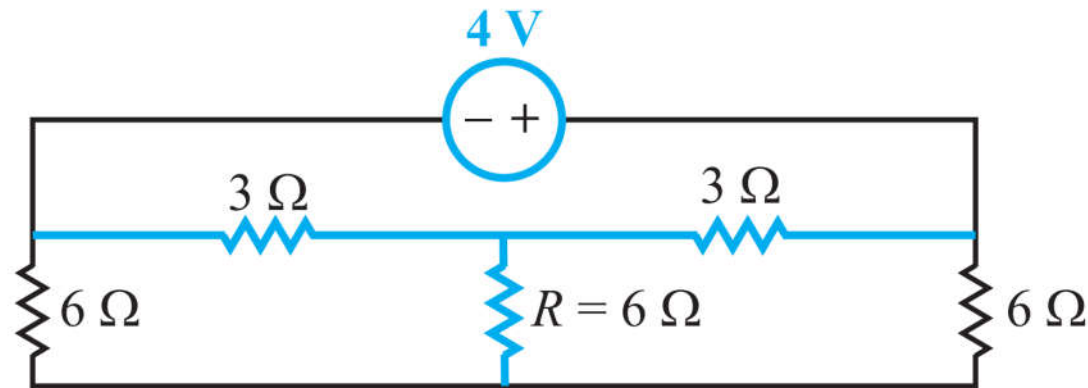Exercise


- Find the power supplied by the voltage source.





Mesh Analysis

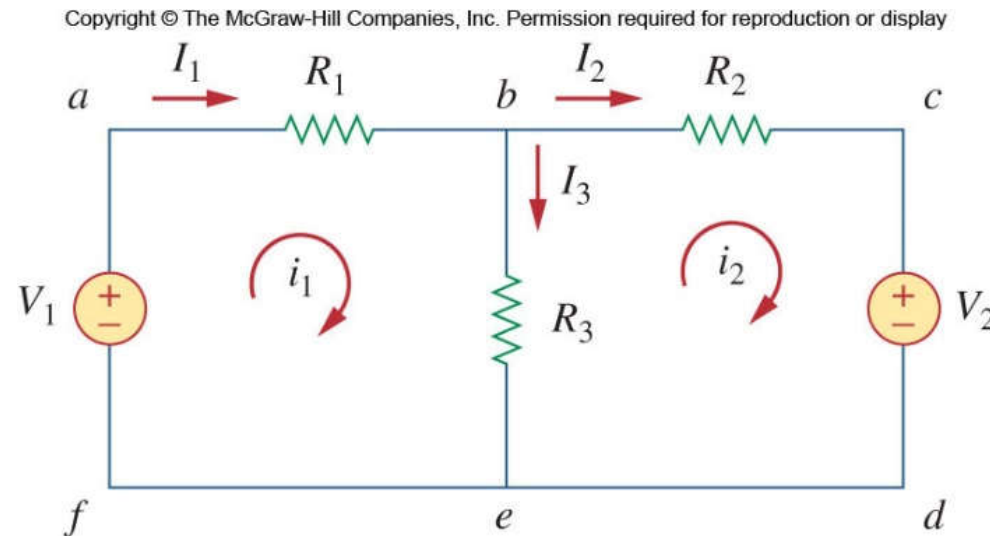- Another general procedure for analyzing circuits is to use the mesh currents as the circuit variables.




- Mesh analysis uses KVL to find unknown currents.



Loop, Independent Loop, Mesh

- A loop is a closed path with no node passed more than once.
- A loop is independent if it contains at least one branch which is not a part of any other independent loop.
- A mesh is a loop that does not contain any other loop within it.

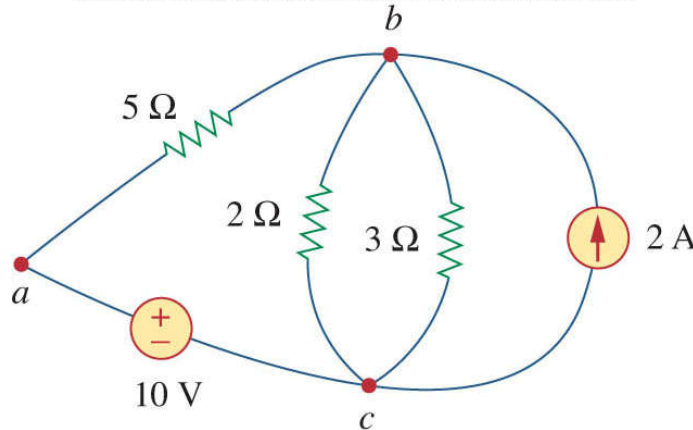Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display



- b – number of branches
- n – number of nodes
- l_{ind} – number of ind. loops



Mesh = Independent loop?

$$l_{ind} = b - (n - 1)$$



Planar vs Nonplanar

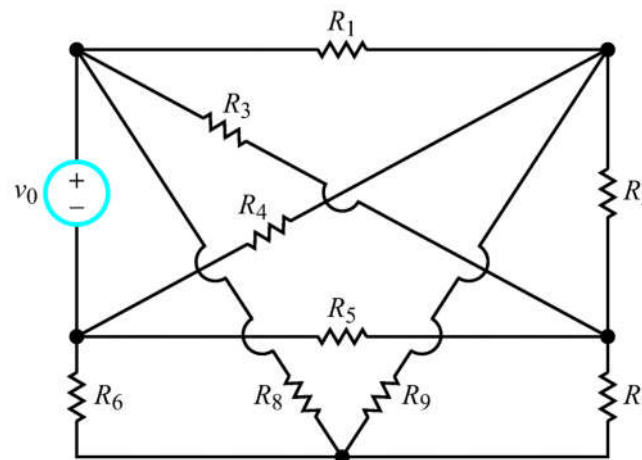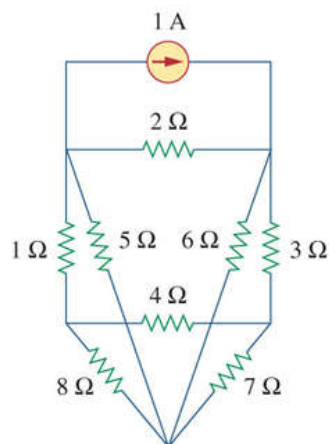
- Mesh analysis is limited in one aspect: It can only apply to circuits that is planar.
 - A planar circuit can be drawn such that there are no crossing branches.





Mesh Analysis Steps

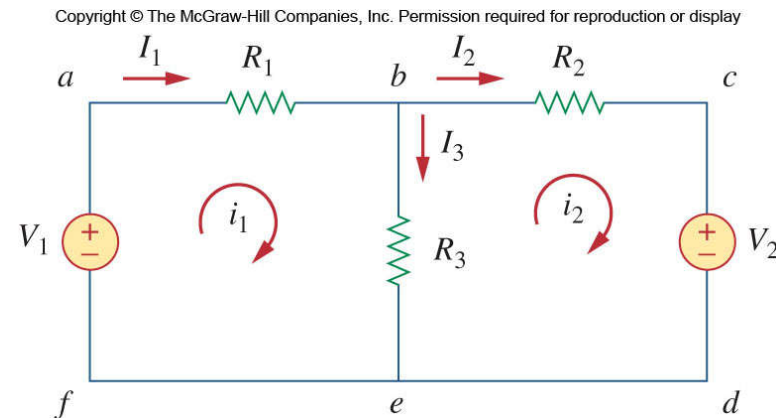
- Mesh analysis follows these steps:
 1. Assign mesh currents i_1, i_2, \dots, i_n to the n meshes
 2. Apply KVL to each of the n mesh currents.
 3. Solve the resulting n simultaneous equations to get the mesh currents.







Mesh Analysis with Current Sources

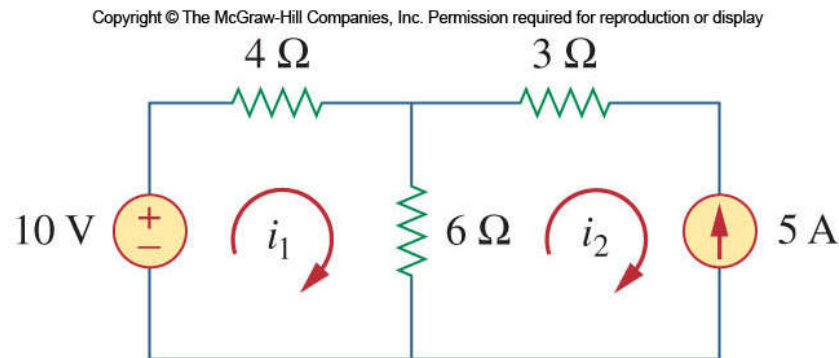- The presence of a current source makes the mesh analysis simpler in that it reduces the number of equations.
 - If the current source is located on only one mesh, the current for that mesh is defined by the source. For example:







Supermesh

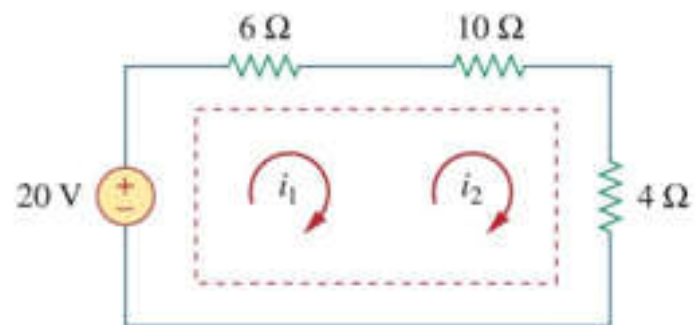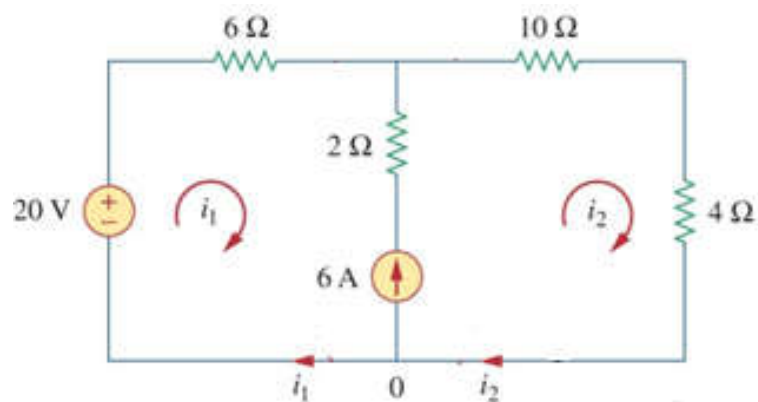



Summary

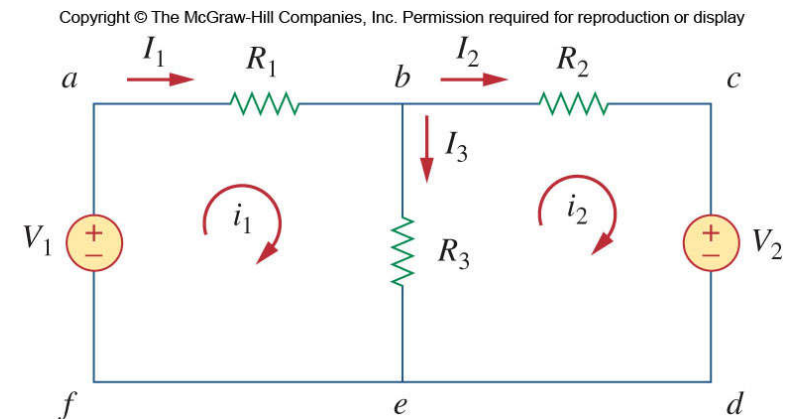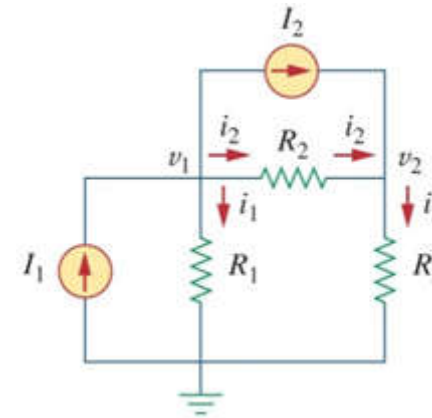
- Node Analysis
 - Node voltage is the unknown
 - Solve by KCL
 - Special case: Floating voltage source
- Mesh Analysis
 - Loop current is the unknown
 - Solve by KVL
 - Special case: Current source







Application: DC Transistor Circuit

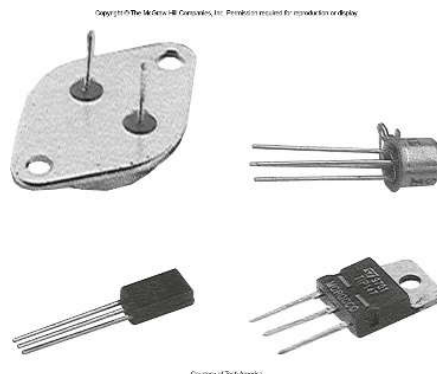- In general, there are two types of transistors commonly used: Field Effect (FET) and Bipolar Junction (BJT). Here we will use the approaches learned in this lecture to analyze a BJT circuit.



- A BJT is a three terminal device, where
 - The input current into one terminal (the base) affects the current flowing out of a second terminal (the collector).
 - The third terminal (the emitter) is the common terminal for both currents.

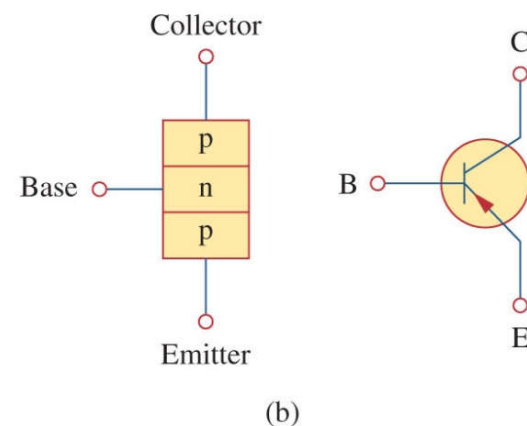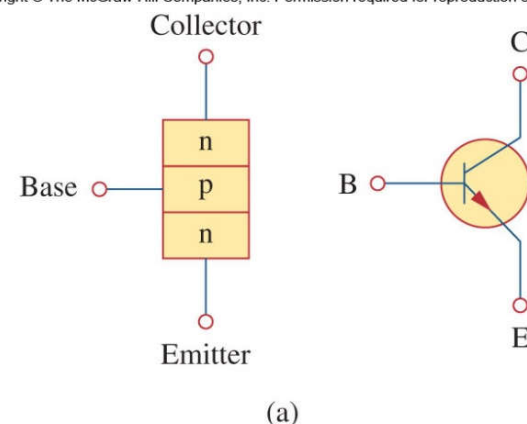Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display






KCL and KVL for a BJT

- The currents from each terminal can be related to each other as follows:
- The base and collector current can be related to each other by the parameter β , which can range from 50-1000

$$I_C = \beta I_B$$

- Applying KVL to the BJT gives:

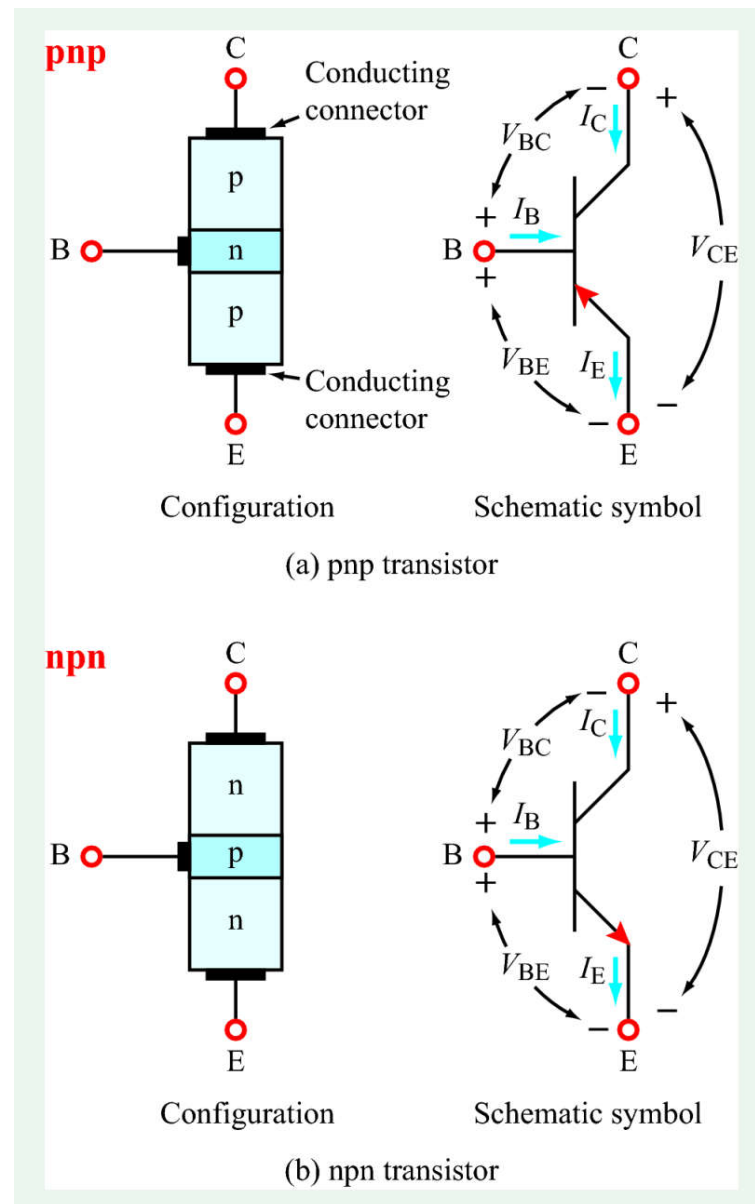




Analysis of a BJT Circuit

- A transistor has a few operating modes depending on the applied voltages/currents. In this problem, we will be interested in the operation in “active mode”
 - the mode used for amplifying signals.

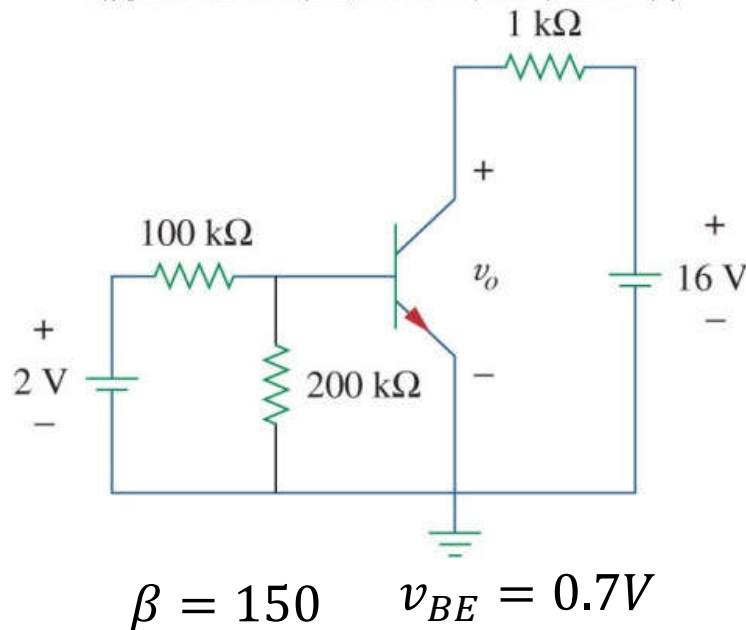Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display






Mesh Analysis?

$$\beta = 150 \quad v_{BE} = 0.7V$$

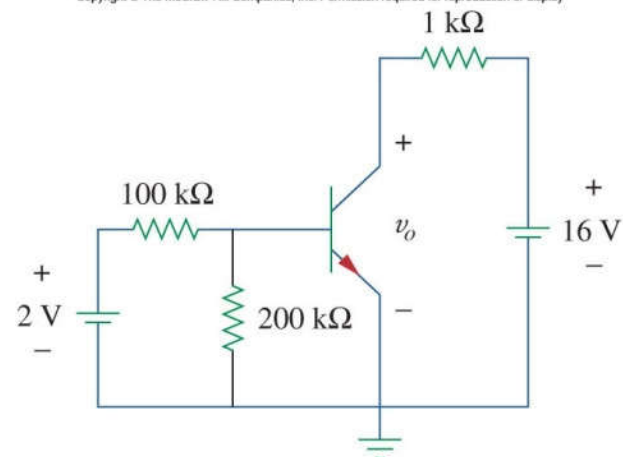
Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display





DC model of a BJT

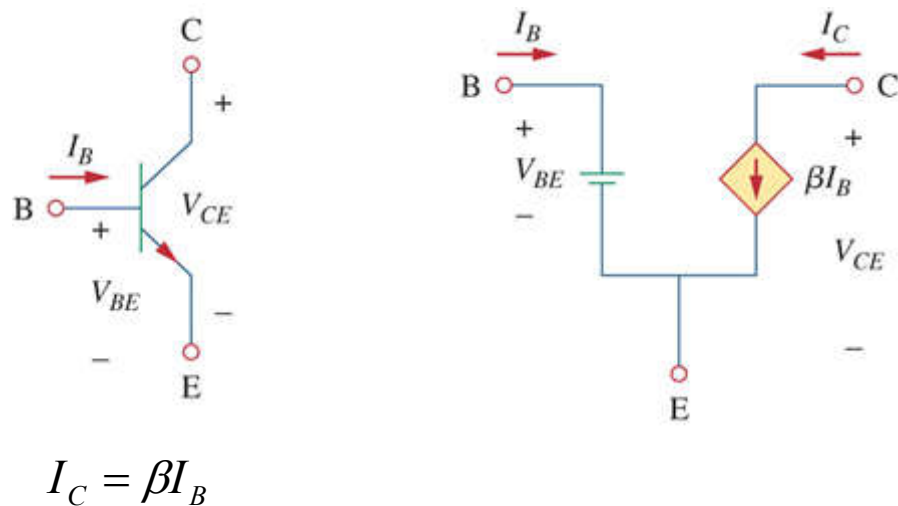- The figure below shows the equivalent DC model for a BJT in active mode




Note that nodal analysis can be applied after using this model.




Setting up a BJT circuit

$$\beta = 150$$

$$v_{BE} = 0.7V$$

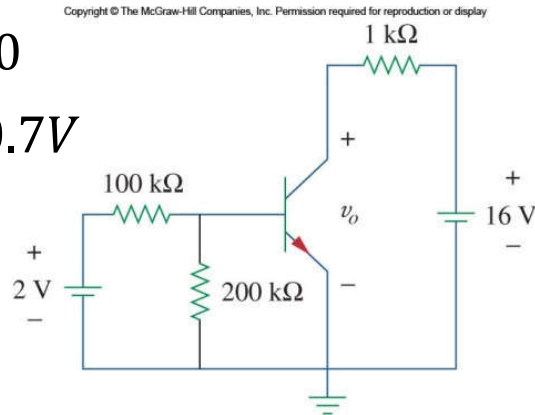

Original circuit

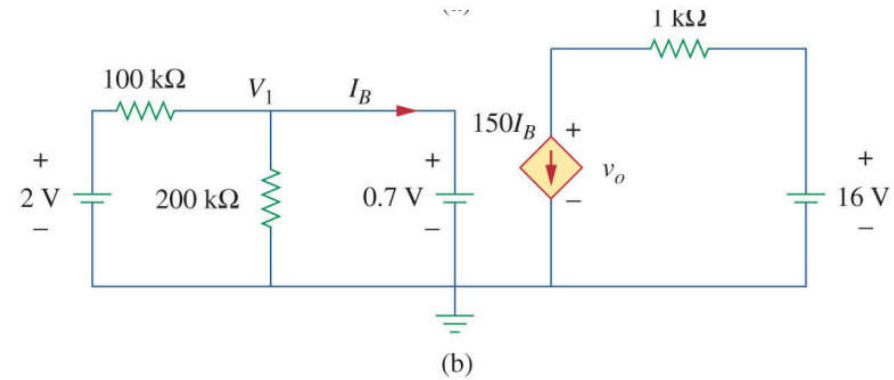

Circuit for nodal analysis