



# Lecture 10

## - Three-Phase Circuits/Transformers




# Outline--Three-Phase Circuits

- Balanced Three-Phase System
  - Balanced sources
  - Balanced loads
- Circuit analysis
  - Phase voltage/current
  - Line voltage/current




## Three-Phase System (in USA)

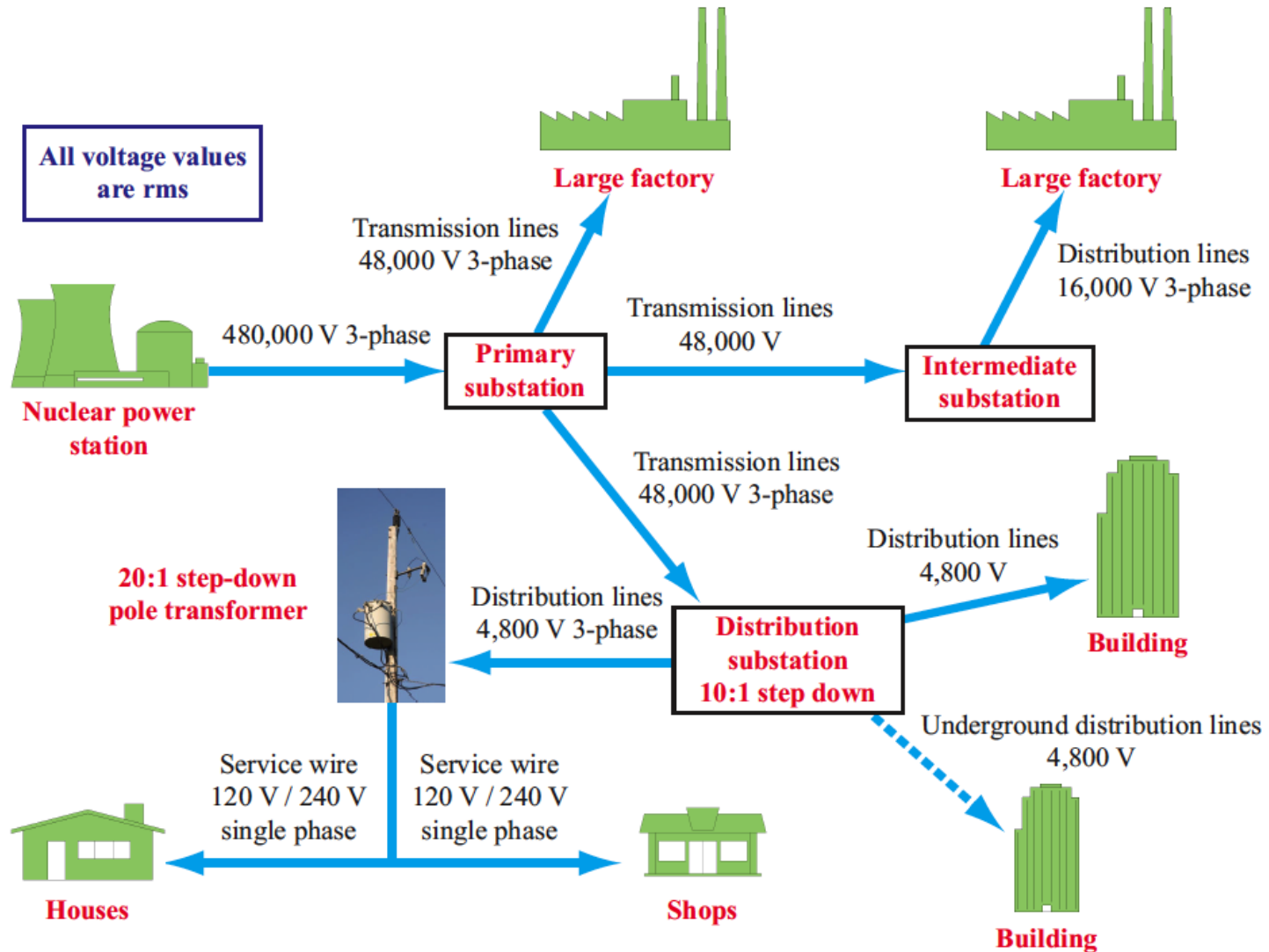




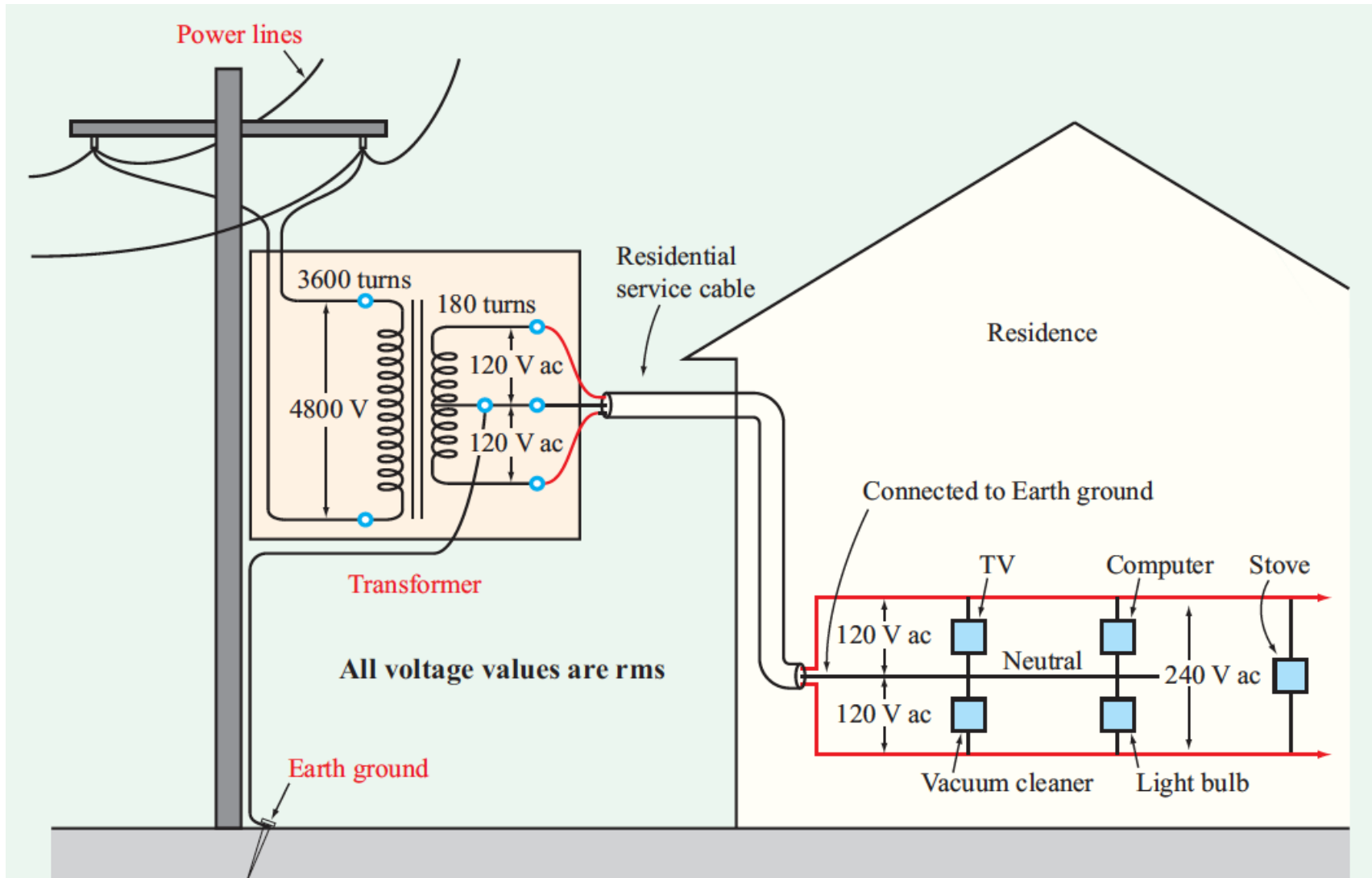
# A 4800-V rms single-phase connected to residential user through a 20 : 1 step-down transformer





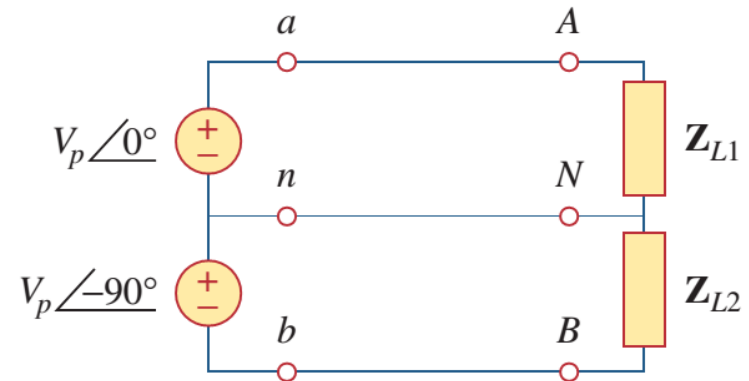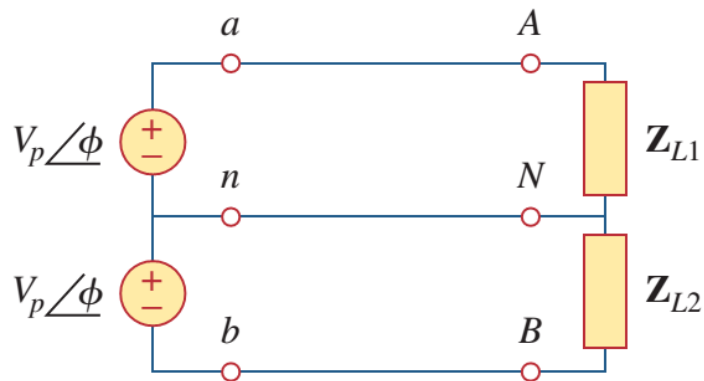
# Single Phase vs. Polyphase

- Households have single-phase power supply
  - This typically in a three wire form, where two 120V sources with the same phase are connected in series.
  - This allows for appliances to use either 120 or 240V
- Circuits that operate at the same frequency but with multiple sources at different phases are called polyphase.








# Three-phase four-wire system in China

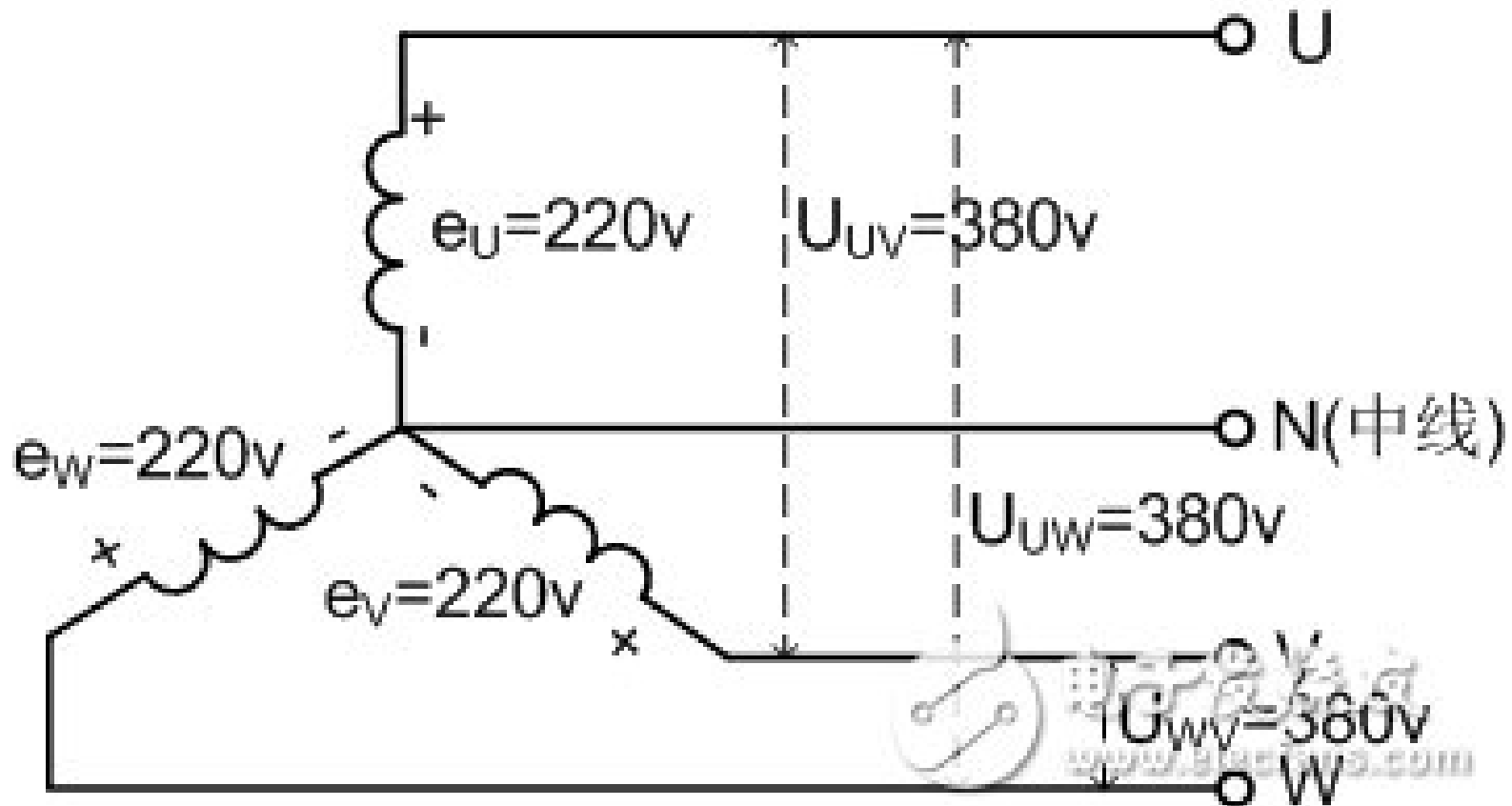

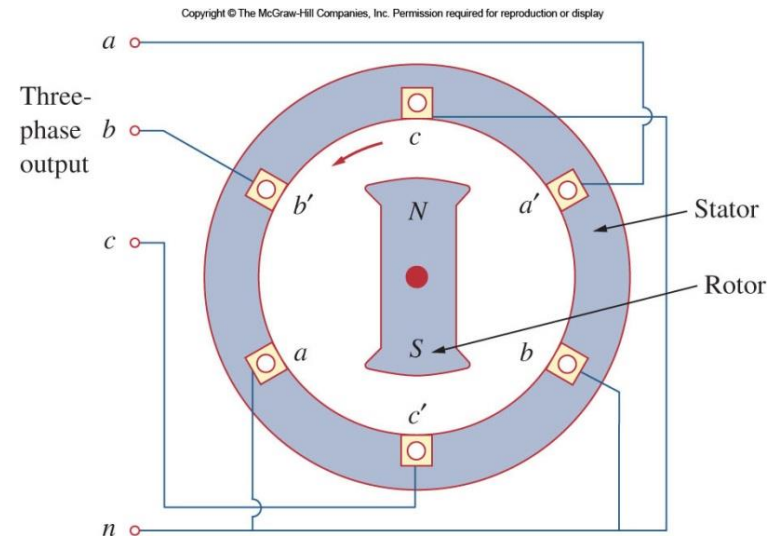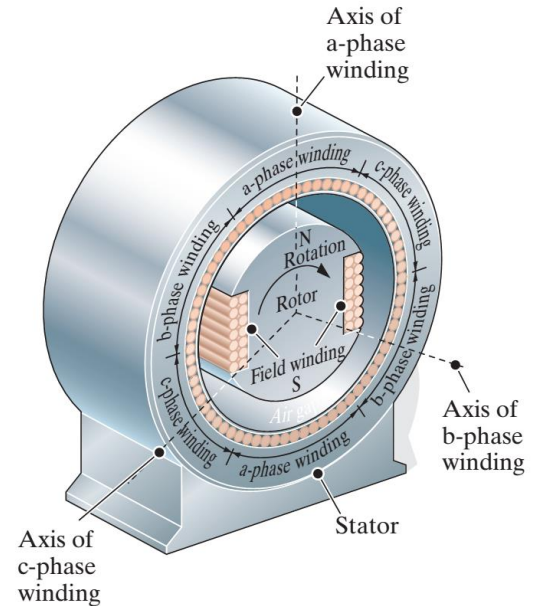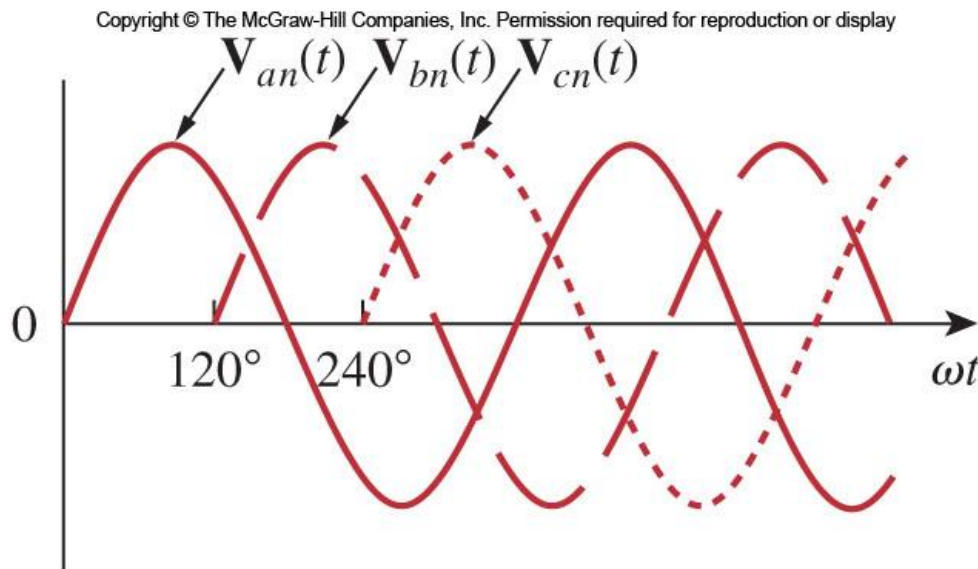
# Three-Phase Sources

- Three phase voltages are typically produced by a three-phase AC generator.
- The output voltages look like below.


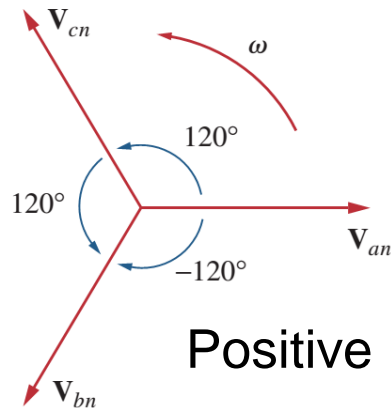
# Balanced Three-Phase Sources

- Balanced phase voltage are equal in magnitude and are out of phase with each other by 120deg
- It's easy to know  $V_{an} + V_{bn} + V_{cn} = 0$
- Two sequences for the phases:




Positive

$$V_{an} = V_p \angle 0^\circ$$

$$V_{bn} = V_p \angle -120^\circ$$
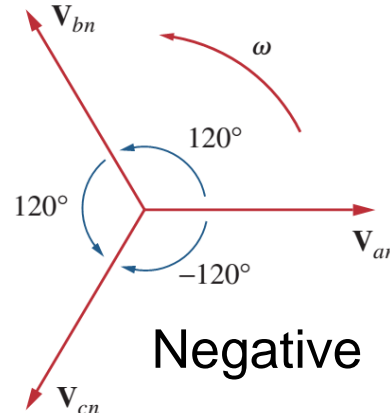
$$V_{cn} = V_p \angle -240^\circ = V_p \angle +120^\circ$$




Negative

$$V_{an} = V_p \angle 0^\circ$$

$$V_{cn} = V_p \angle -120^\circ$$

$$V_{bn} = V_p \angle -240^\circ = V_p \angle +120^\circ$$

Lecture 10

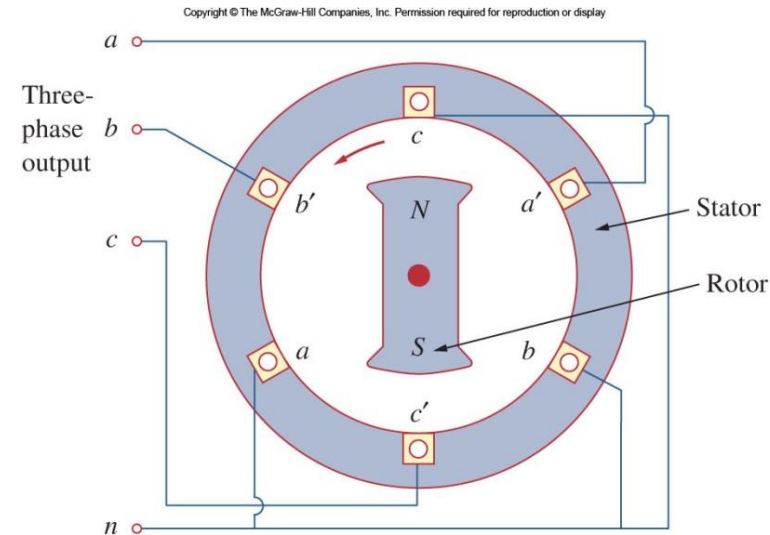



$$|V_{an}| = |V_{bn}| = |V_{cn}|$$





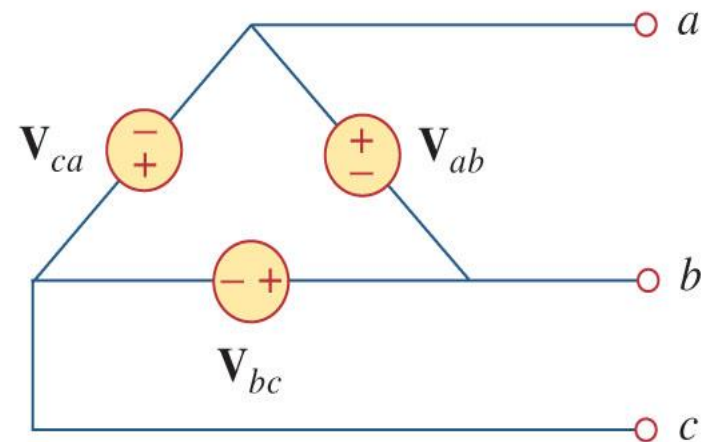
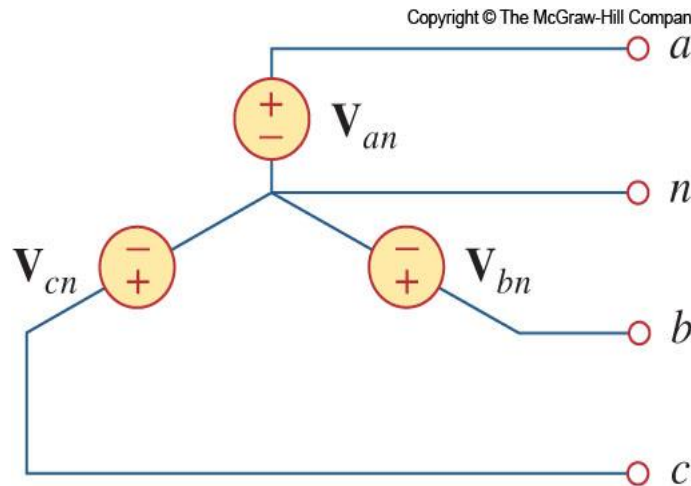
# Connecting the Sources

- Three phase voltage sources can be connected by either three or four wire configurations.
  - Three-wire configuration accomplished by Delta connected source.
  - Four-wire system accomplished using a Y(Wye) connected source.


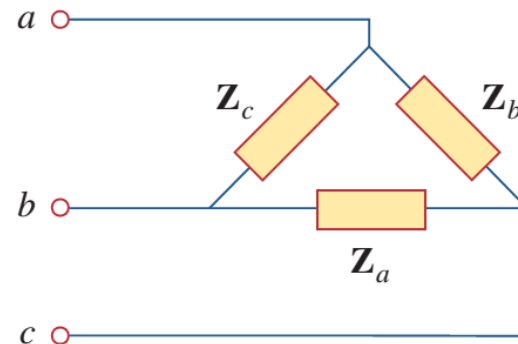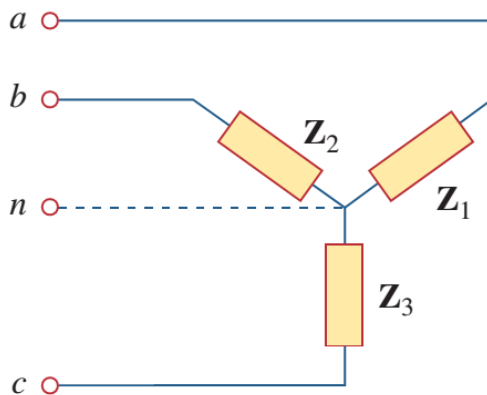
# Balanced Loads


- A balanced load is one that has the same impedance presented to all three voltage sources.
  - *Phase impedance are equal in magnitude and in phase*
- They may also be connected in either Delta or wye
  - For a balanced wye connected load:  $Z_1 = Z_2 = Z_3 = Z_Y$
  - For a balanced delta connected load:  $Z_a = Z_b = Z_c = Z_\Delta$



- The load impedance per phase for the two load configurations can be interchanged.



# Source-Load configurations

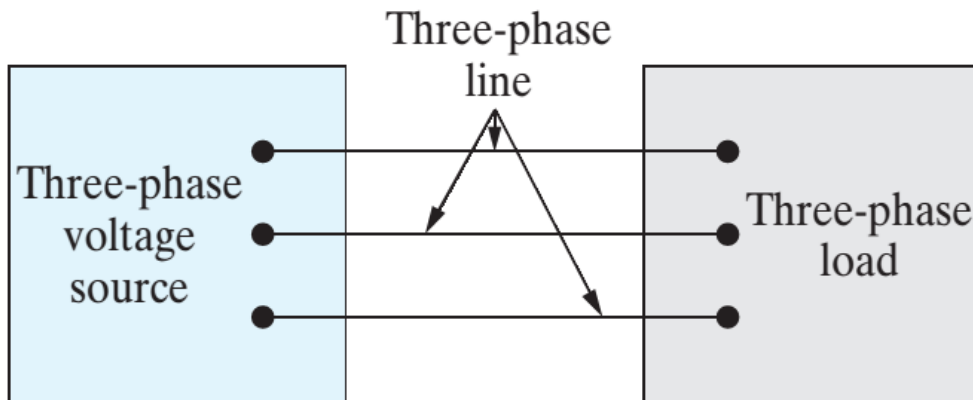


Source	Load
Y	Y
Y	$\Delta$
$\Delta$	Y
$\Delta$	$\Delta$



# Source-Load Configurations

Y-Y

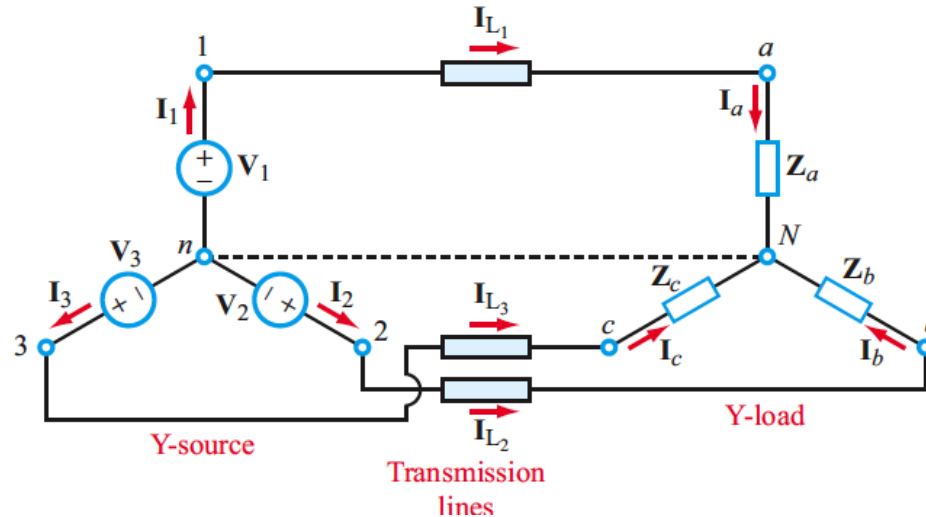


Load Phase Currents

$I_a, I_b, I_c$   
(same as line currents  
 $I_{L1}, I_{L2}, \text{ and } I_{L3}$ )

Load Phase Voltages

$V_{aN}, V_{bN}, V_{cN}$

Y-Delta

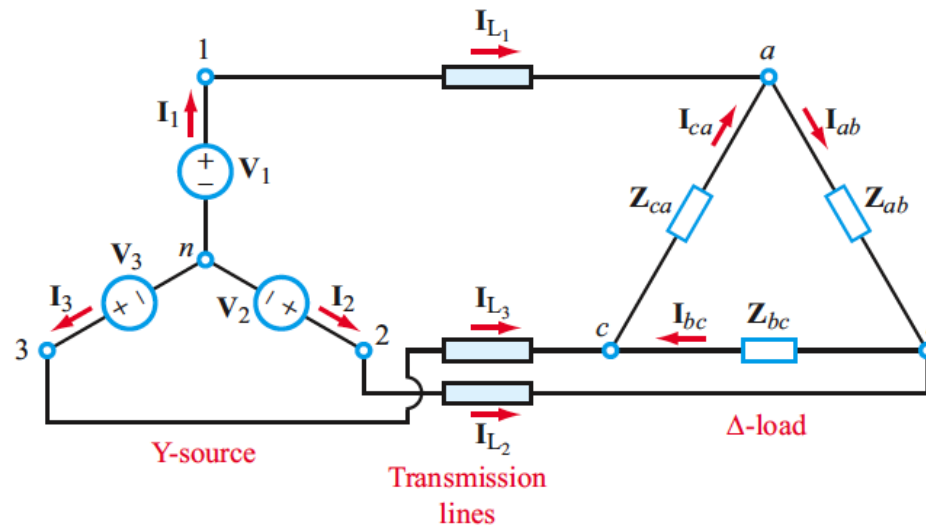

Load Phase Currents

$I_{ab}, I_{bc}, I_{ca}$


Load Phase Voltages

$V_{ab}, V_{bc}, V_{ca}$



# Source-Load Configurations

Delta-Y

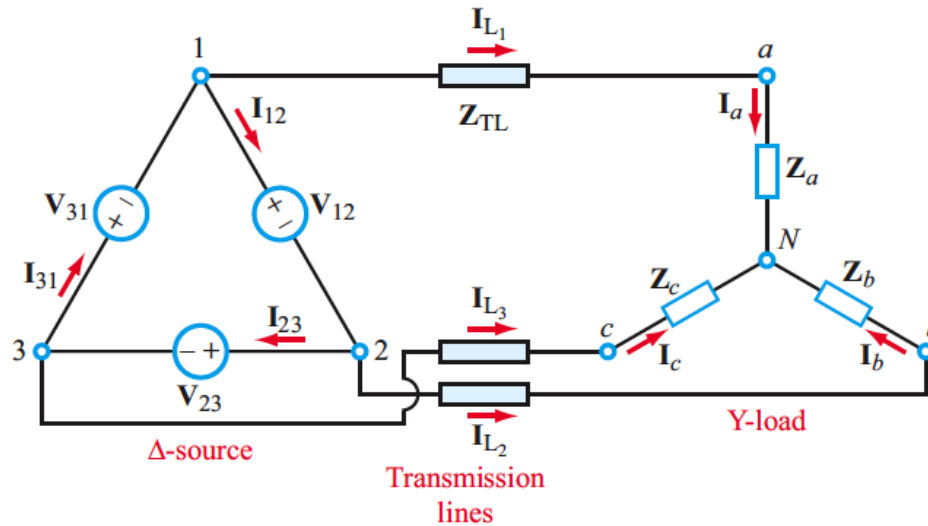


Load Phase Currents

$I_a, I_b, I_c$   
(same as line currents  
 $I_{L1}, I_{L2},$  and  $I_{L3}$ )

Load Phase Voltages

$V_{aN}, V_{bN}, V_{cN}$

Delta-Delta

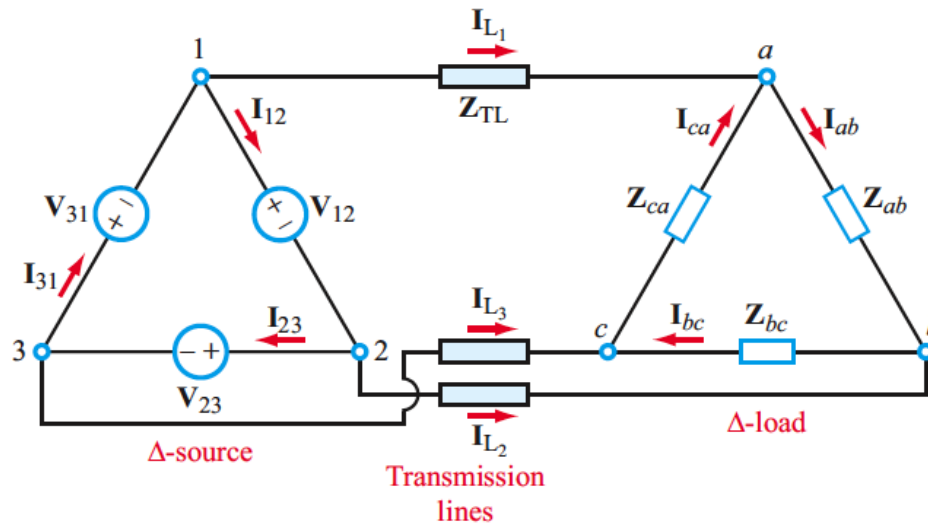

Load Phase Currents

$I_{ab}, I_{bc}, I_{ca}$

Load Phase Voltages

$V_{ab}, V_{bc}, V_{ca}$   
(same as source voltages  
if  $Z_{TL}$  is negligible)


# Balanced Y-Y connection

- Any three-phase system **can be reduced to an equivalent Y-Y system.**
- The load impedances  $Z_Y$  will be assumed to be balanced.
  - This can be the source  $Z_s$ , line  $Z_l$  and load  $Z_L$  together.

$$Z_Y = Z_s + Z_\ell + Z_L$$

- How about  $Z_n$  ?

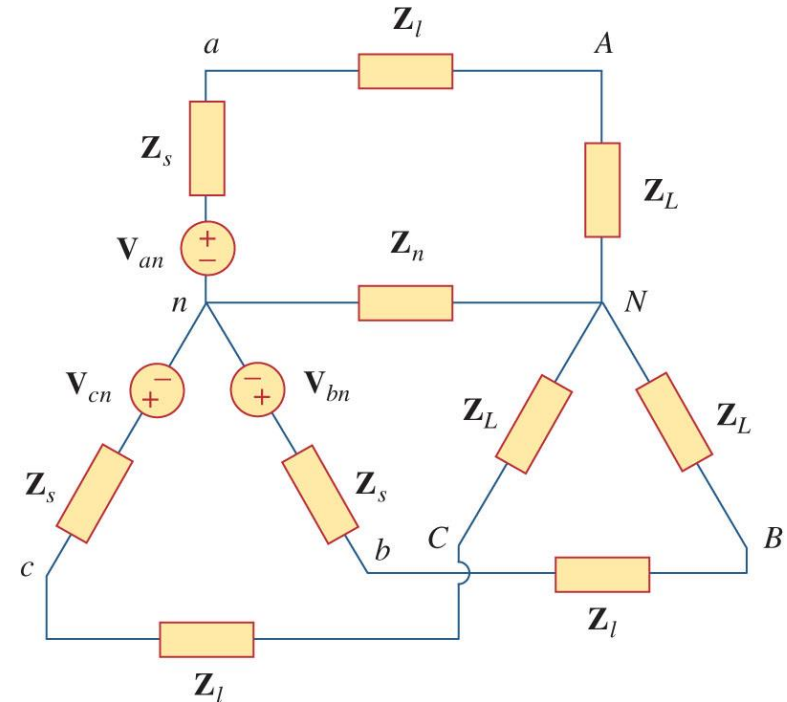Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display







# Line-to-Line Voltage

- Use the positive sequence:

$$V_{an} = V_p \angle 0^\circ$$

$$V_{bn} = V_p \angle -120^\circ \quad V_{cn} = V_p \angle +120^\circ$$

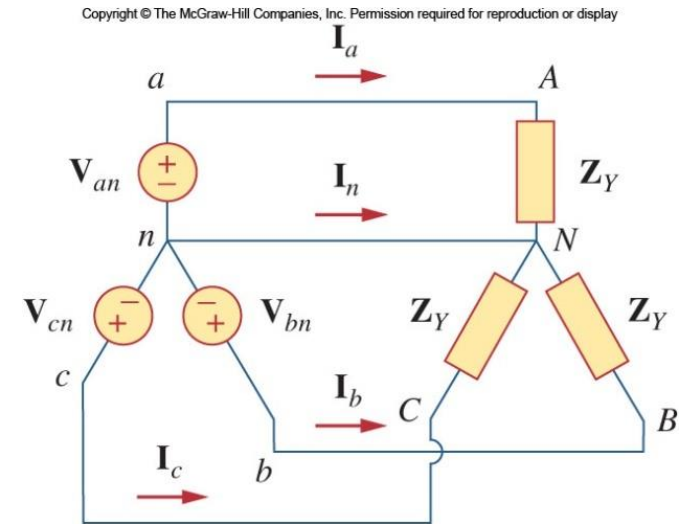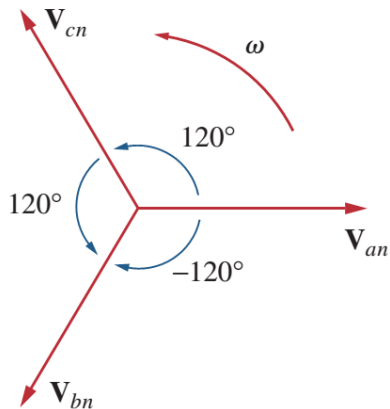
The line to line (or line in short) voltages:




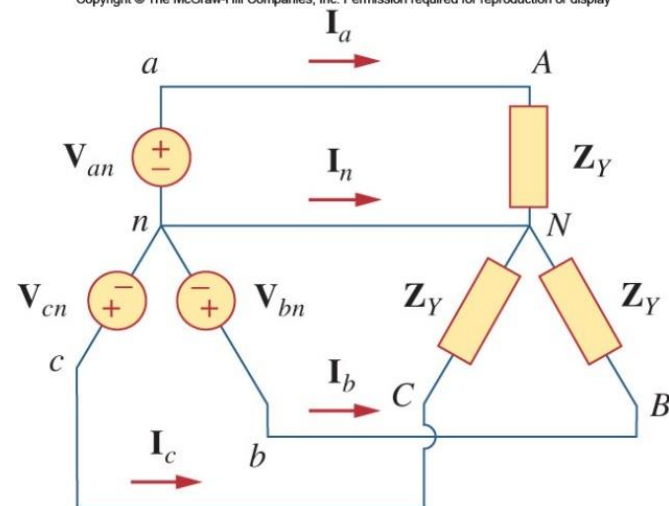
# Line Currents

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display









## Example

- Calculate the line currents.

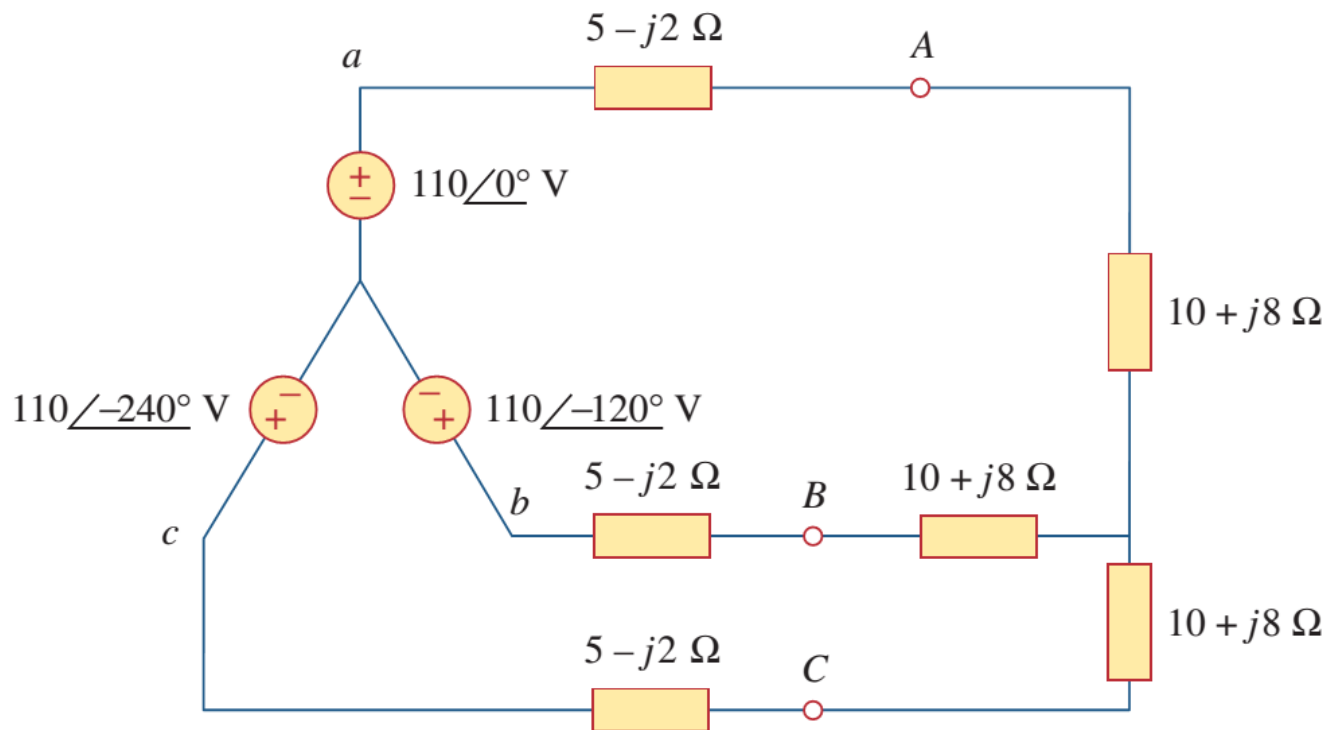



# Wye- $\Delta$

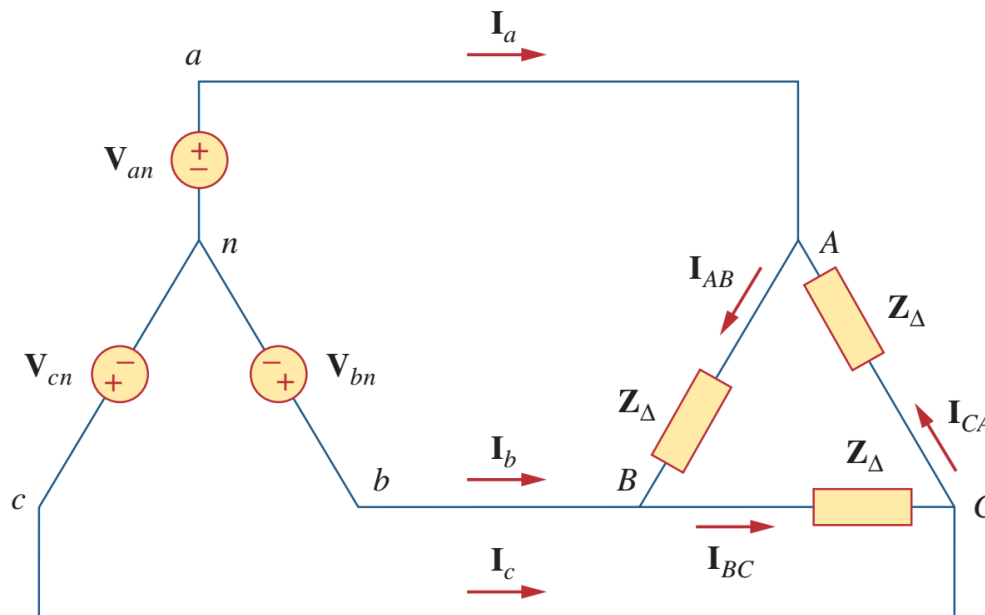


$$\begin{aligned} \mathbf{V}_{an} &= V_p \angle 0^\circ \\ \mathbf{V}_{bn} &= V_p \angle -120^\circ, \quad \mathbf{V}_{cn} = V_p \angle +120^\circ \end{aligned}$$

$$\begin{aligned} \mathbf{V}_{ab} &= \sqrt{3}V_p \angle 30^\circ = \mathbf{V}_{AB}, \quad \mathbf{V}_{bc} = \sqrt{3}V_p \angle -90^\circ = \mathbf{V}_{BC} \\ \mathbf{V}_{ca} &= \sqrt{3}V_p \angle -150^\circ = \mathbf{V}_{CA} \end{aligned}$$

$$\mathbf{I}_{AB} = \frac{\mathbf{V}_{AB}}{\mathbf{Z}_\Delta}, \quad \mathbf{I}_{BC} = \frac{\mathbf{V}_{BC}}{\mathbf{Z}_\Delta}, \quad \mathbf{I}_{CA} = \frac{\mathbf{V}_{CA}}{\mathbf{Z}_\Delta}$$




# Wye- $\Delta$

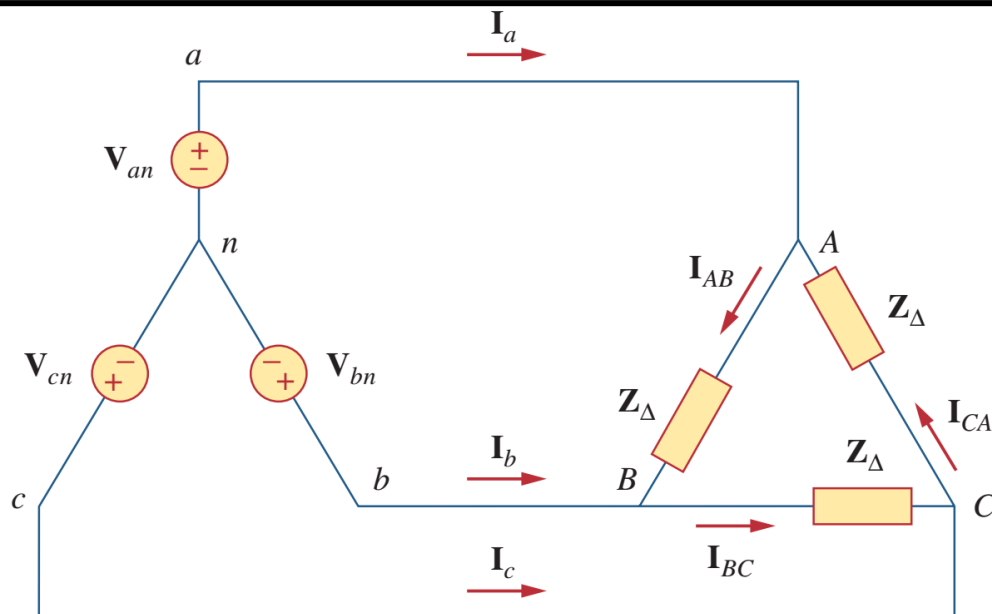

$$\mathbf{I}_a = \mathbf{I}_{AB} - \mathbf{I}_{CA}, \quad \mathbf{I}_b = \mathbf{I}_{BC} - \mathbf{I}_{AB}, \quad \mathbf{I}_c = \mathbf{I}_{CA} - \mathbf{I}_{BC}$$


Since  $\mathbf{I}_{CA} = \mathbf{I}_{AB} \angle -240^\circ$ ,
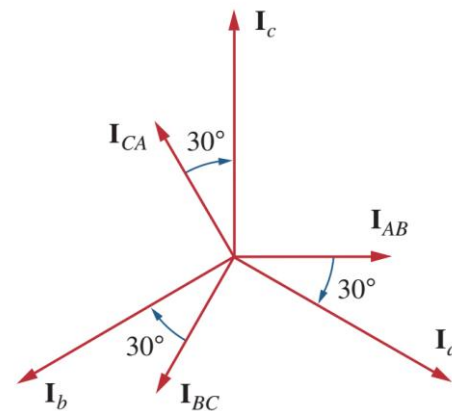
$$\begin{aligned} \mathbf{I}_a &= \mathbf{I}_{AB} - \mathbf{I}_{CA} = \mathbf{I}_{AB}(1 - 1 \angle -240^\circ) \\ &= \mathbf{I}_{AB}(1 + 0.5 - j0.866) = \mathbf{I}_{AB}\sqrt{3} \angle -30^\circ \end{aligned}$$






•  $\Delta$ - $\Delta$

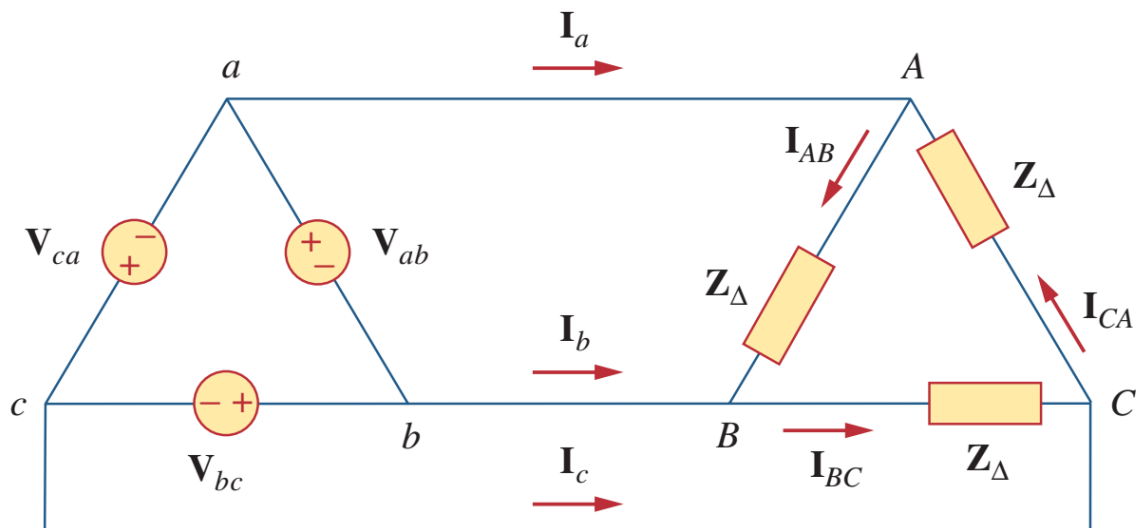

$\Delta$ -Wye

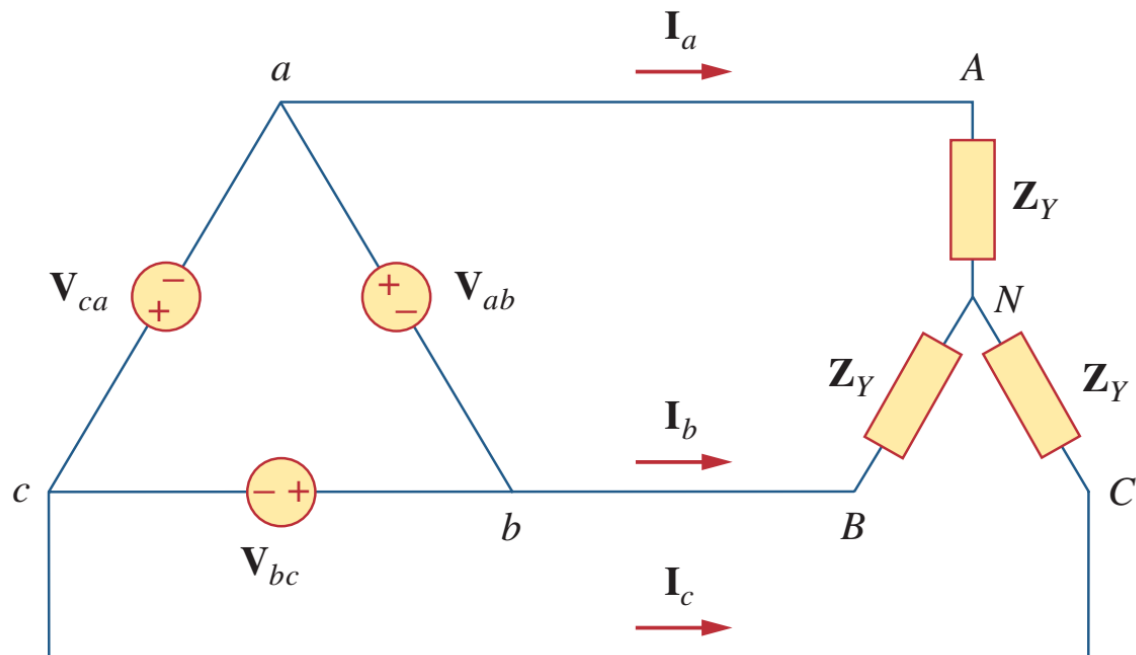




Y-Y	$\mathbf{V}_{an} = V_p \angle 0^\circ$ $\mathbf{V}_{bn} = V_p \angle -120^\circ$ $\mathbf{V}_{cn} = V_p \angle +120^\circ$ <p>Same as line currents</p>	$\mathbf{V}_{ab} = \sqrt{3}V_p \angle 30^\circ$ $\mathbf{V}_{bc} = \mathbf{V}_{ab} \angle -120^\circ$ $\mathbf{V}_{ca} = \mathbf{V}_{ab} \angle +120^\circ$ $\mathbf{I}_a = \mathbf{V}_{an} / \mathbf{Z}_Y$ $\mathbf{I}_b = \mathbf{I}_a \angle -120^\circ$ $\mathbf{I}_c = \mathbf{I}_a \angle +120^\circ$
Y-Δ	$\mathbf{V}_{an} = V_p \angle 0^\circ$ $\mathbf{V}_{bn} = V_p \angle -120^\circ$ $\mathbf{V}_{cn} = V_p \angle +120^\circ$ $\mathbf{I}_{AB} = \mathbf{V}_{AB} / \mathbf{Z}_\Delta$ $\mathbf{I}_{BC} = \mathbf{V}_{BC} / \mathbf{Z}_\Delta$ $\mathbf{I}_{CA} = \mathbf{V}_{CA} / \mathbf{Z}_\Delta$	$\mathbf{V}_{ab} = \mathbf{V}_{AB} = \sqrt{3}V_p \angle 30^\circ$ $\mathbf{V}_{bc} = \mathbf{V}_{BC} = \mathbf{V}_{ab} \angle -120^\circ$ $\mathbf{V}_{ca} = \mathbf{V}_{CA} = \mathbf{V}_{ab} \angle +120^\circ$ $\mathbf{I}_a = \mathbf{I}_{AB} \sqrt{3} \angle -30^\circ$ $\mathbf{I}_b = \mathbf{I}_a \angle -120^\circ$ $\mathbf{I}_c = \mathbf{I}_a \angle +120^\circ$
Δ-Δ	$\mathbf{V}_{ab} = V_p \angle 0^\circ$ $\mathbf{V}_{bc} = V_p \angle -120^\circ$ $\mathbf{V}_{ca} = V_p \angle +120^\circ$ $\mathbf{I}_{AB} = \mathbf{V}_{ab} / \mathbf{Z}_\Delta$ $\mathbf{I}_{BC} = \mathbf{V}_{bc} / \mathbf{Z}_\Delta$ $\mathbf{I}_{CA} = \mathbf{V}_{ca} / \mathbf{Z}_\Delta$	<p>Same as phase voltages</p> $\mathbf{I}_a = \mathbf{I}_{AB} \sqrt{3} \angle -30^\circ$ $\mathbf{I}_b = \mathbf{I}_a \angle -120^\circ$ $\mathbf{I}_c = \mathbf{I}_a \angle +120^\circ$
Δ-Y	$\mathbf{V}_{ab} = V_p \angle 0^\circ$ $\mathbf{V}_{bc} = V_p \angle -120^\circ$ $\mathbf{V}_{ca} = V_p \angle +120^\circ$ <p>Same as line currents</p>	<p>Same as phase voltages</p> $\mathbf{I}_a = \frac{V_p \angle -30^\circ}{\sqrt{3}\mathbf{Z}_Y}$ $\mathbf{I}_b = \mathbf{I}_a \angle -120^\circ$ $\mathbf{I}_c = \mathbf{I}_a \angle +120^\circ$




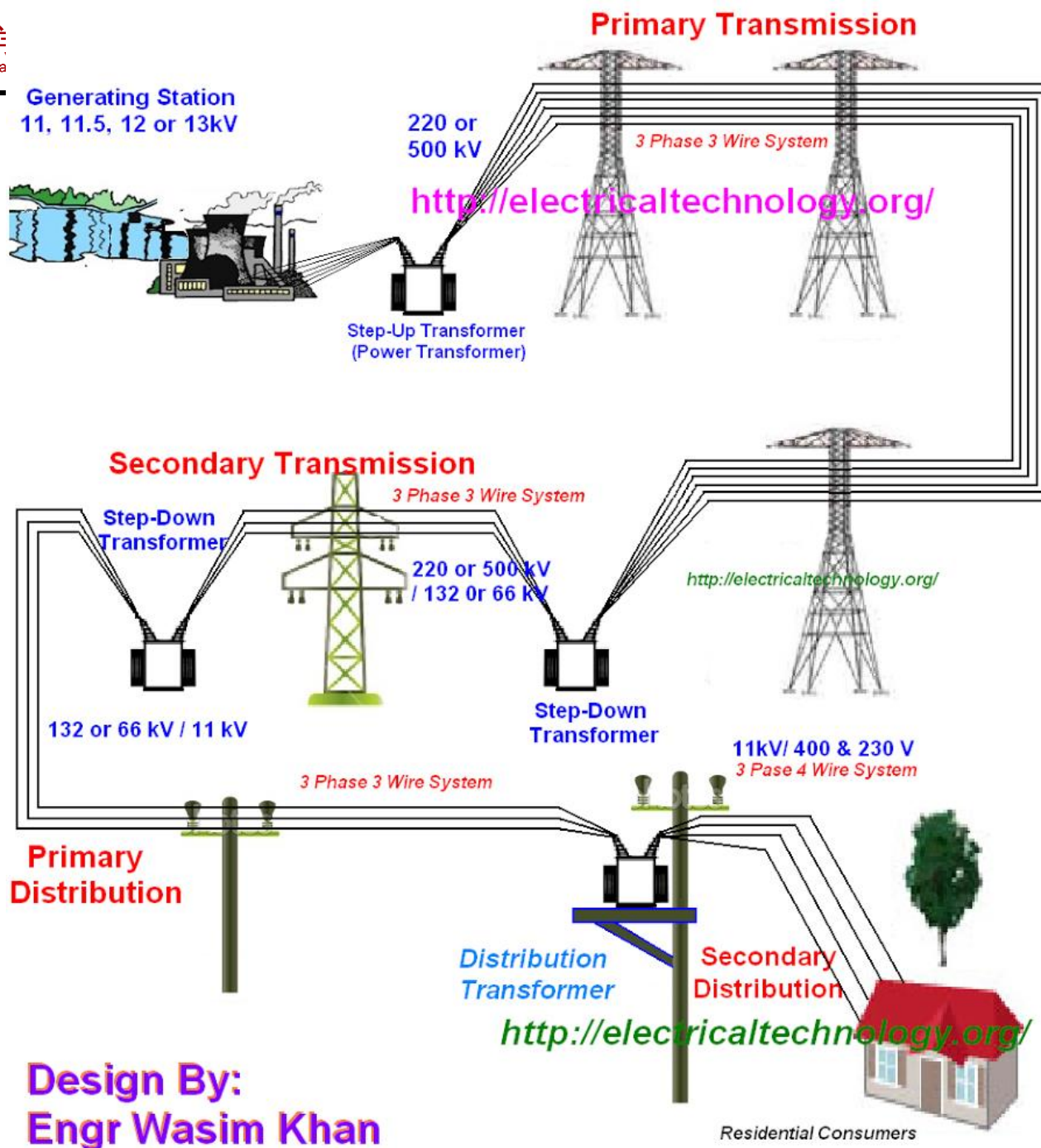
# Outline-Transformers

- Mutual inductance (review)
- Transformers


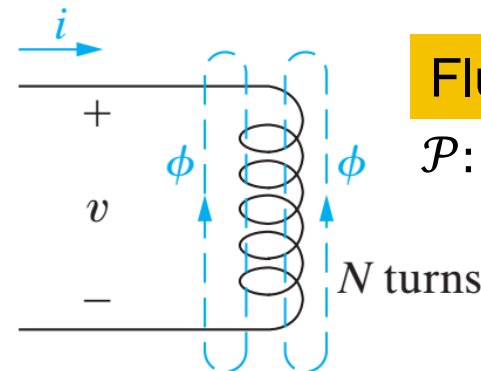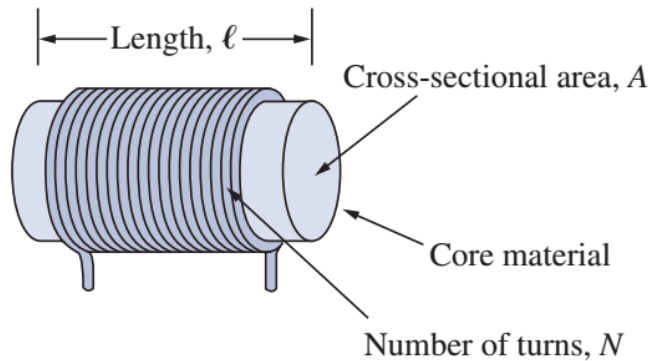
## Review: Self Inductance

- Self inductance: reaction of the inductor to the change in current through itself.



$$\text{Flux } \phi = \mathcal{P}Ni$$


$\mathcal{P}$ : permeance

$$v = N \frac{d\phi}{dt} = L \frac{di}{dt}, L = N \frac{d\phi}{di}$$


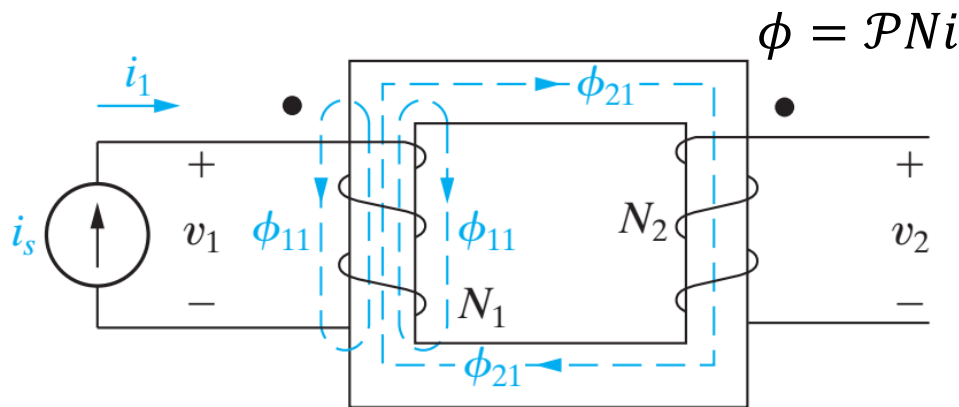
# Mutual Inductance

- Mutual inductance: reaction of the inductor to change in current through another inductor.



$$\phi_1 = \phi_{11} + \phi_{21}$$

$$\phi_{11} = \mathcal{P}_{11}N_1i_1, \quad \phi_{21} = \mathcal{P}_{21}N_1i_1,$$

$$\phi_1 = \mathcal{P}_1N_1i_1$$


$$\begin{aligned} v_1 &= \frac{d(N_1\phi_1)}{dt} = N_1 \frac{d}{dt}(\phi_{11} + \phi_{21}) \\ &= N_1^2(\mathcal{P}_{11} + \mathcal{P}_{21}) \frac{di_1}{dt} = N_1^2\mathcal{P}_1 \frac{di_1}{dt} \end{aligned}$$

$$\phi = \mathcal{P}Ni$$

$$\begin{aligned} v_2 &= \frac{d(N_2\phi_{21})}{dt} = N_2 \frac{d}{dt}(\mathcal{P}_{21}N_1i_1) \\ &= N_2N_1\mathcal{P}_{21} \frac{di_1}{dt} \\ &= M_{21} \frac{di_1}{dt} \end{aligned}$$



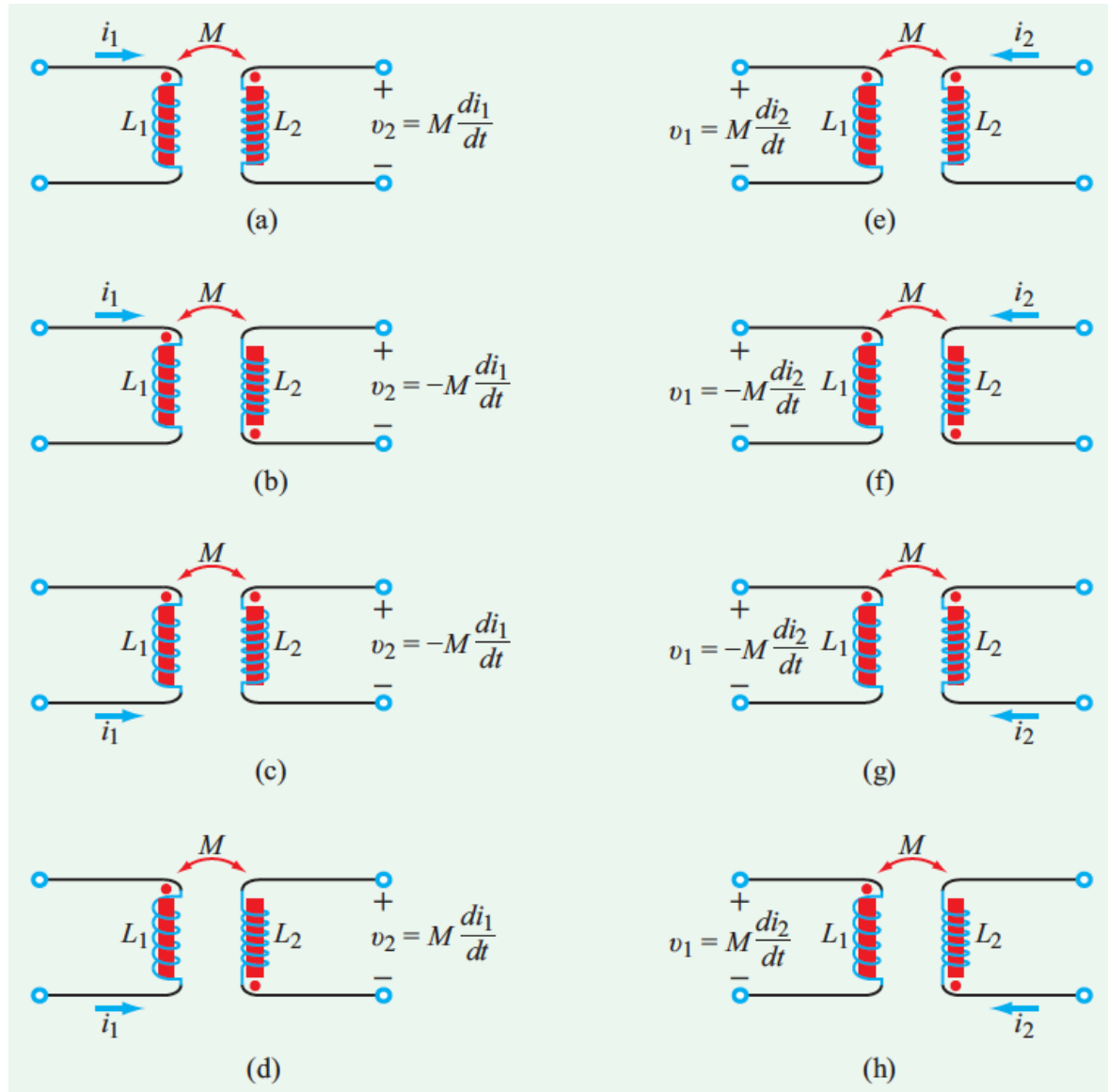
# Dot Convention: Defines Directions of Windings


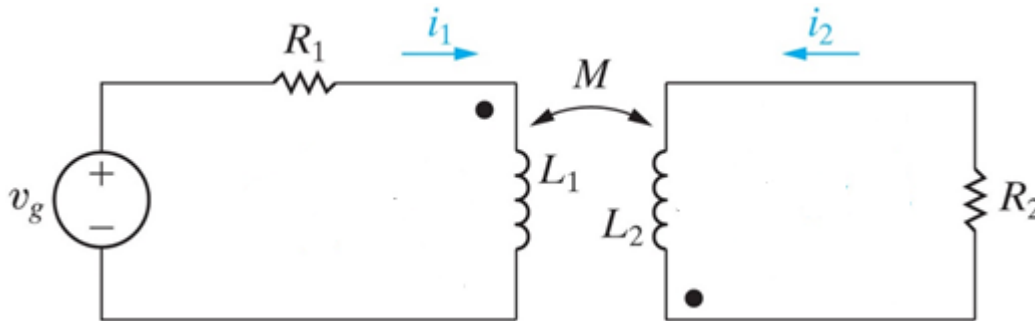
# Mutual Inductance: General Case


- Two circuits lined by a magnetic field
  - $L_1, L_2$ : self-inductances
  - $M$ : mutual inductance
  - Dots: indicating polarity of mutually induced voltages.




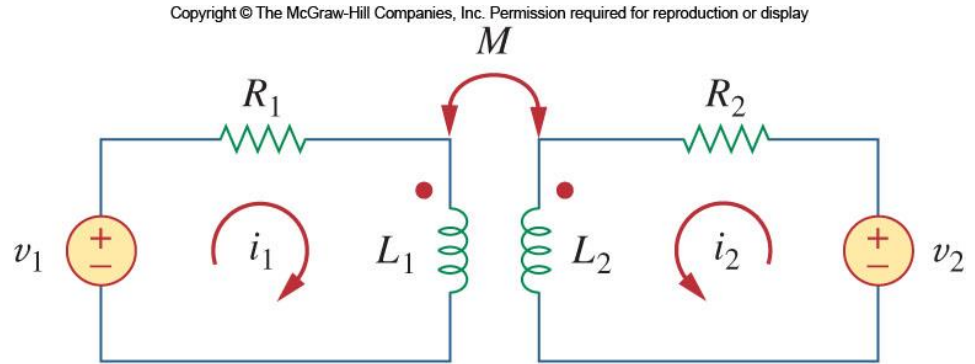
## Exercise

- Relate  $v_1, v_2$  with  $i_1$  and  $i_2$ .
  - In time domain
  - In phasor domain




# Energy in a Coupled Circuit


- The energy stored in an inductor is
- For coupled inductors, the total energy stored is

$$w = \frac{1}{2} L_1 i_1^2 + \frac{1}{2} L_2 i_2^2 \pm M i_1 i_2$$

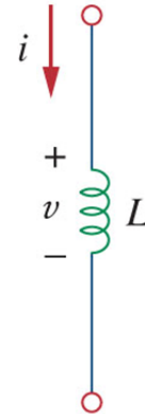- The positive sign is selected when the currents both enter or leave the dotted terminals.



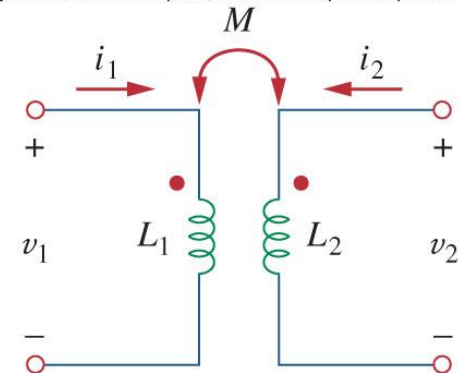Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display



# Coupling Coefficient $k$


- The system cannot have negative energy

$$\frac{1}{2}L_1i_1^2 + \frac{1}{2}L_2i_2^2 - Mi_1i_2 \geq 0 \quad \Rightarrow \quad M \leq \sqrt{L_1L_2}$$

- Define a parameter describes how closely  $M$  approaches upper limit.


$$k = \frac{M}{\sqrt{L_1L_2}}$$

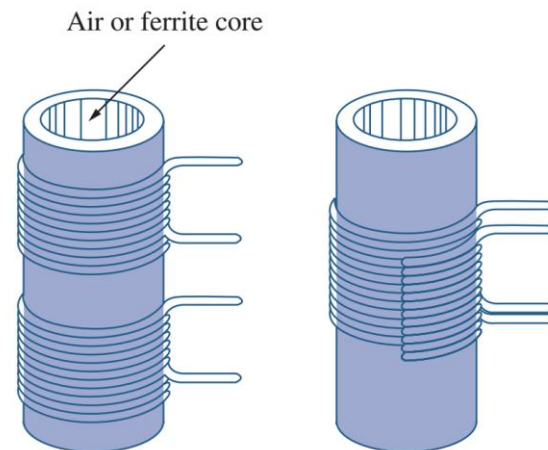- Coupling coefficient,  $0 \leq k \leq 1$ .
- determined by the physical configuration of the coils.


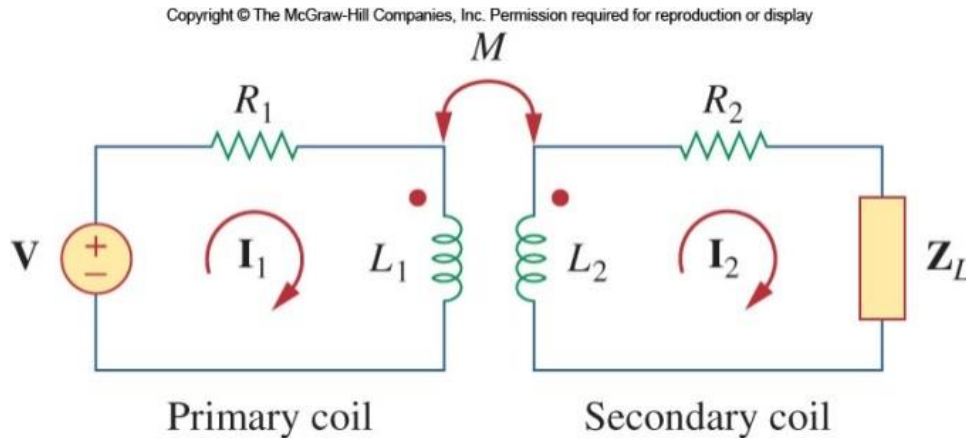
# Linear Transformers


- A transformer is a magnetic device that takes advantage of mutual inductance.
  - Called linear if the coils are wound on a magnetically linear material, i.e. permeability  $\mu$  is constant.


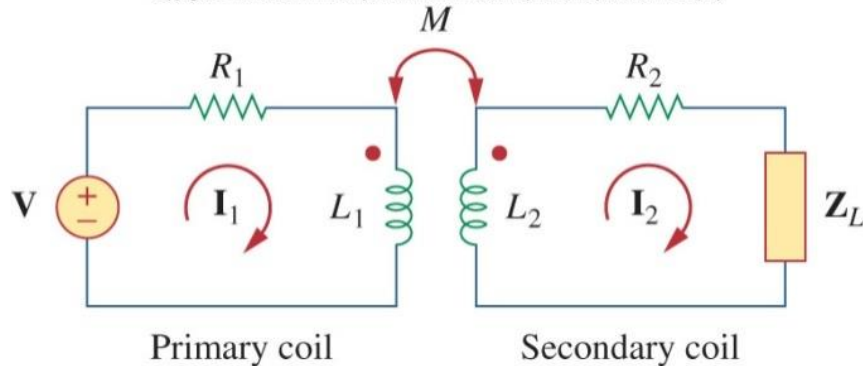
# Transformer Impedance

- An important parameter to know for a transformer is how the input impedance  $Z_{in}$  is seen from the source.
  - $Z_{in}$  is important because it governs the behavior of the primary circuit.

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display




$$Z_{in} = \frac{V}{I_1} = R_1 + j\omega L_1 + \frac{\omega^2 M^2}{R_2 + j\omega L_2 + Z_L}$$

Reflected impedance from secondary to primary



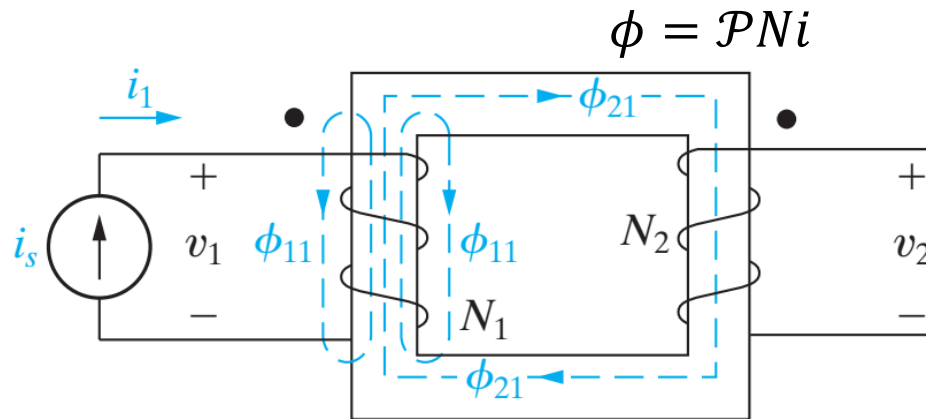
# Ideal Transformers

- The ideal transformer has:
  - Coils with very large reactance  
( $L_1, L_2, M \rightarrow \infty$ )
  - Coupling coefficient  $k=1$ .
  - Primary and secondary coils are lossless,  $R_1 = R_2 = 0$ .



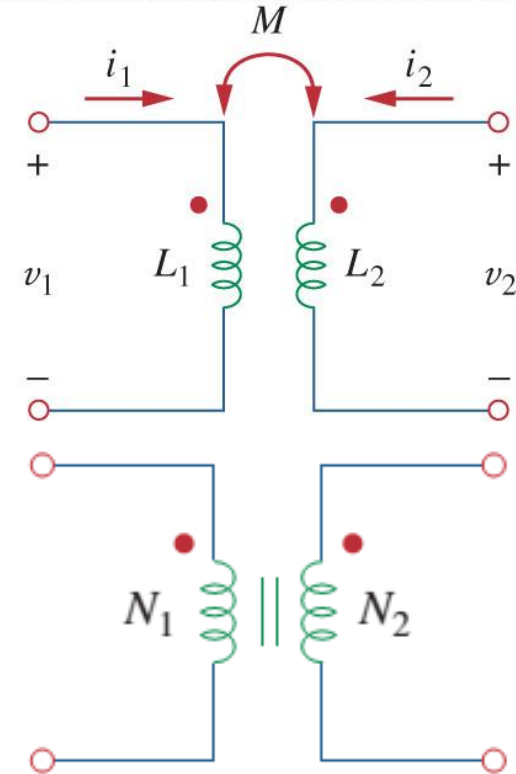
Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display



$$\frac{V_2}{V_1} = \frac{N_2}{N_1} = n$$
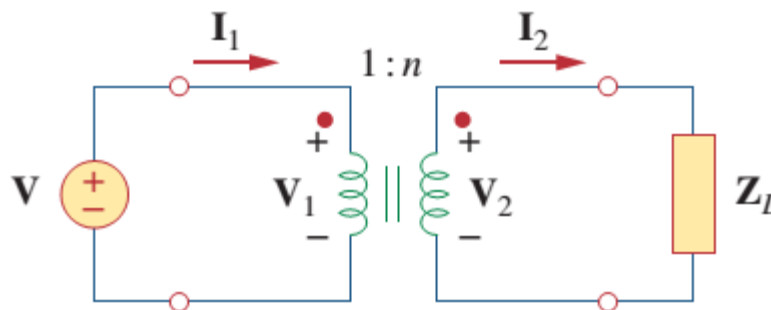
## Ideal Transformers II

$$\frac{V_2}{V_1} = \frac{N_2}{N_1} = n$$



- The current is related as:
- Reflected impedance

$$Z_{in} = \frac{V_1}{I_1} =$$

# Ideal Autotransformer

- Autotransformer uses one winding for primary & secondary
  - It does not offer isolation!

