

## Homework 3


Due time: 18:30 on Oct. 28<sup>th</sup>, 2021

Turn in your homework in class or to tutorial classroom (1B110)

Rules:

- Work on your own. Discussion is permissible, but extremely similar submissions will be judged as plagiarism.
- Please show all intermediate steps: a correct solution without an explanation will get zero credit.
- Please submit on time. No late submission will be accepted.
- Please prepare your submission in English only. No Chinese submission will be accepted.
- If needed, round the number to the nearest hundredths, i.e., rounding it to 2 decimal places.

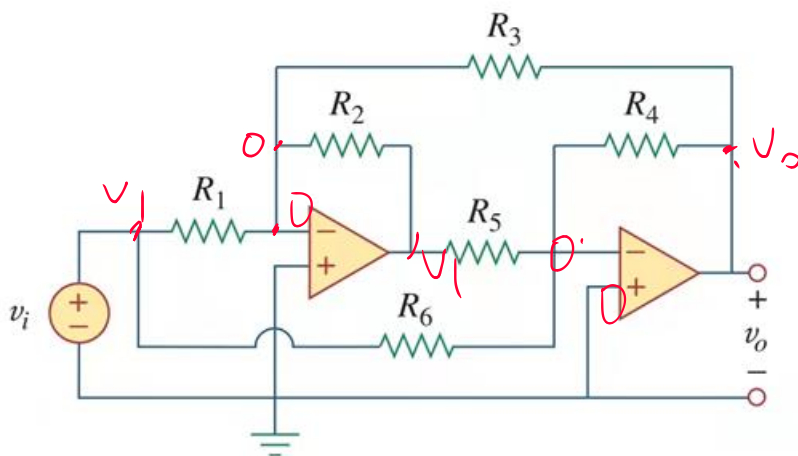1. For the circuit below, assume the operational amplifiers are both working in their linear mode, determine the gain  $v_o/v_i$  of the circuit using resistance  $R_1$  to  $R_6$ .



$$\left\{ \begin{array}{l} \frac{-v_i}{R_1} = \frac{v_1}{R_2} + \frac{v_o}{R_3} \\ \frac{v_i}{R_6} + \frac{v_1}{R_5} + \frac{v_o}{R_4} = 0 \end{array} \right. \Rightarrow v_1 = -\left(\frac{R_2}{R_1}v_i + \frac{R_2}{R_3}v_o\right)$$


$$\frac{v_i}{R_6} + \frac{v_o}{R_4} - \frac{R_2}{R_1 R_5} v_i - \frac{R_2}{R_3 R_5} v_o = 0$$

$$\left(\frac{1}{R_6} - \frac{R_2}{R_1 R_5}\right) v_i = \left(\frac{R_2}{R_3 R_5} - \frac{1}{R_4}\right) v_o$$

$$\frac{v_o}{v_i} = \frac{\frac{1}{R_6} - \frac{R_2}{R_1 R_5}}{\frac{R_2}{R_3 R_5} - \frac{1}{R_4}} = \frac{R_1 R_3 R_4 R_5 - R_2 R_3 R_4 R_6}{R_1 R_2 R_4 R_6 - R_1 R_3 R_5 R_6}$$

2. For the circuit below, assume the operational amplifiers are both working in their linear mode,

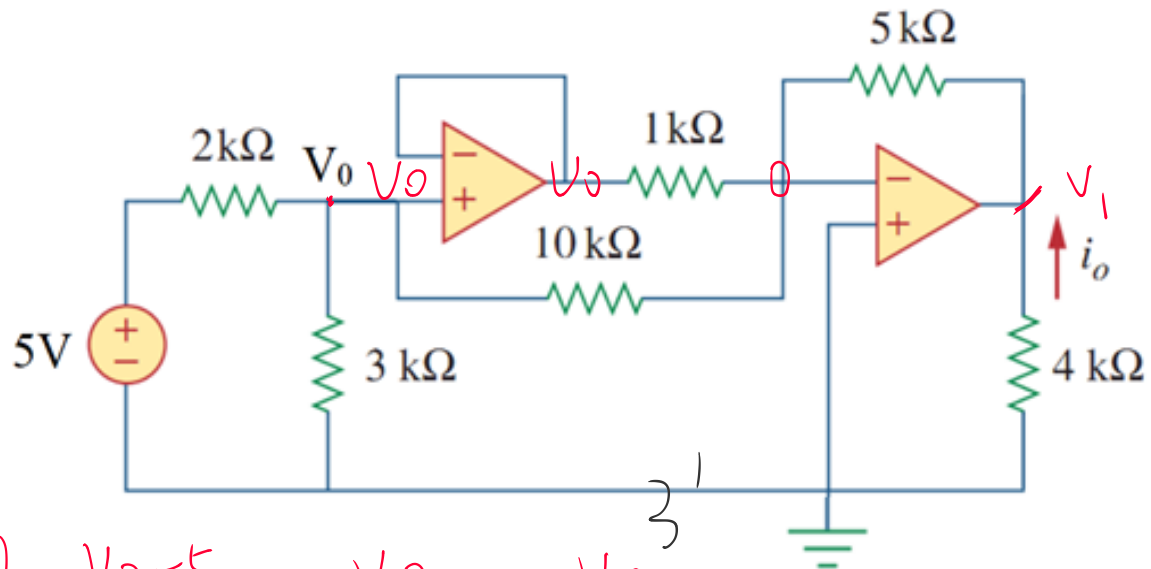- (1) Calculate  $V_0$  in the op amp circuit.
- (2) Calculate  $i_o$  in the op amp circuit.




$$(1) \frac{V_0 - 5}{2000} + \frac{V_0}{3000} + \frac{V_0}{10000} = 0 \Rightarrow V_0 = \frac{75}{28} \text{ (V)} = 2.68 \text{ (V)}$$

$$(2) \frac{-V_0}{1000} - \frac{V_0}{10000} - \frac{V_1}{5000} = 0 \Rightarrow V_1 = -\frac{825}{56} \text{ (V)}$$


$$i_o = \frac{-V_1}{4000} = \frac{825}{224000} = 3.68 \times 10^{-3} \text{ (A)}$$

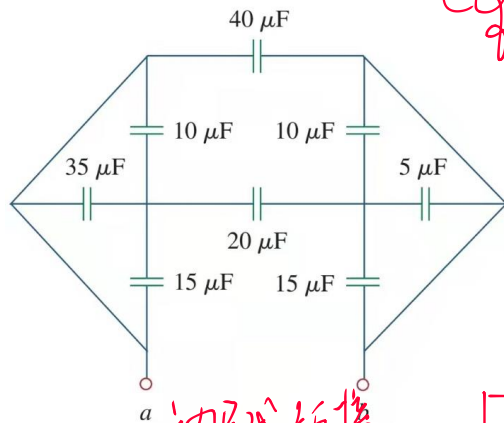3. Find equivalent capacitance  $C_{ab}$  and inductance  $L_{ab}$  for the following two networks:



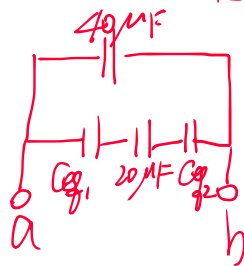
(1)  $C_{eq1} = 35 \mu F // 15 \mu F // 10 \mu F$   
 $= 35 + 15 + 10 = 60 \mu F$  3'

$C_{eq2} = 15 \mu F // 10 \mu F // 5 \mu F$   
 $= 15 + 10 + 5 = 30 \mu F$  3'



$C_{ab} = \frac{1}{\frac{1}{C_{eq1}} + \frac{1}{20} + \frac{1}{C_{eq2}}} + 40 = 50 \mu F$


2'

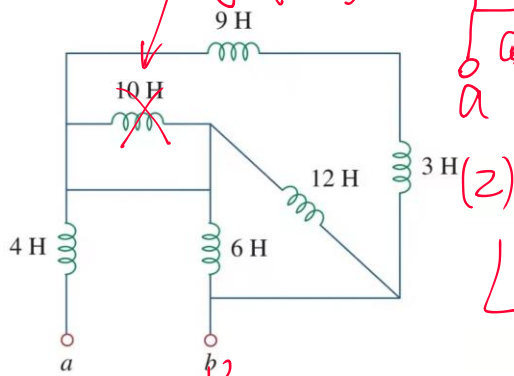

(2)

$L_{eq} = 6 // 12 // (9 + 3) + 4 = 7 \text{ H}$

3'

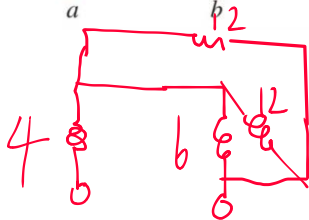


4. For the circuit below

$$v(t) = 5e^{-50t} \text{ V}, \quad t > 0$$

$$i(t) = 150e^{-50t} \text{ mA}, \quad t > 0$$

(1) Find R and C in the circuit.

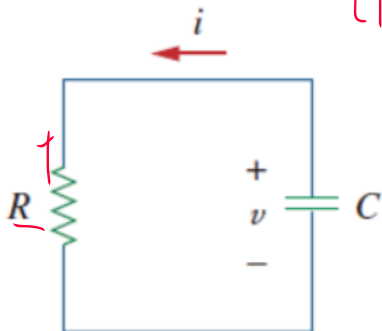(2) Calculate the energy dissipated on R during the time slot of  $0 < t < 0.1 \text{ s}$



1) natural response:  $v(t) = V_0 e^{-\frac{t}{\tau}} \Rightarrow \tau = \frac{1}{50} \text{ (s)}$   $V_0 = 5 \text{ (V)}$

$$i(t) = \frac{v(t)}{R} = \frac{V_0 e^{-\frac{t}{\tau}}}{R} \Rightarrow R = \frac{V_0}{i_0} = \frac{5}{0.15} \text{ (}\Omega\text{)}$$

$$-\frac{1}{\tau} = -\frac{1}{RC} \Rightarrow C = 6 \times 10^{-4} \text{ (F)}$$

(2)  $W_{\text{diss}} = \int_0^{0.1} v(t) i(t) dt$

$$= \int_0^{0.1} 5e^{-50t} \cdot 0.15e^{-50t} dt$$

$$= \int_0^{0.1} 0.75 e^{-100t} dt$$

$$= -7.5 \times 10^{-3} e^{-100t} \Big|_0^{0.1}$$

$$= -7.5 (e^{-10} - 1) \times 10^{-3}$$


$$= 7.5 \times 10^{-3} \text{ (J)}$$

5. For the circuit below:

There is no energy stored in the capacitor in the circuit before  $t = 0$ s.

When  $t = 0$ s, Switch 1 is closed. When  $t = 20\mu\text{s}$ , Switch 2 is closed.

Find  $V_0(t)$  for  $t \geq 0$ .

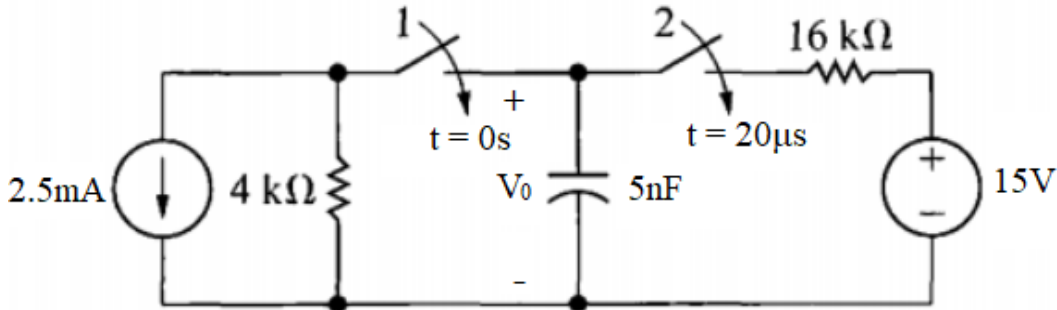

$$\tau = RC = 4 \times 10^3 \times 5 \times 10^{-9} = 2 \times 10^{-5} \text{ (s)} \quad 2'$$


$$\text{at } t=0\text{s}, V_0(0^-) = V_0(0^+) = 0 \text{ (V)} \quad 2'$$

$$V_0(\infty) = -2.5 \times 10^{-3} \times 4 \times 10^3 = -10 \text{ (V)} \quad 2'$$

$$V_0(t) = V_0(\infty) + [V_0(0) - V_0(\infty)] e^{-\frac{t}{\tau}} \quad 2'$$

$$\text{for } t > 20\mu\text{s}: = -10 + 10 e^{-\frac{t}{2 \times 10^{-5}}} \text{ (V)} \quad 2'$$
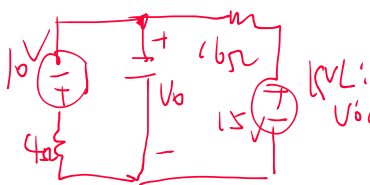
$$\text{at } t = 20\mu\text{s} \Rightarrow V_0'(0) = -10 + 10 e^{-1} \text{ (V)} = -6.32 \text{ (V)} \quad 2'$$



$$V_0'(\infty) = \frac{25 \times 4 \times 10^3}{(16+4) \times 10^3} = -5 \text{ (V)} \quad 2'$$

$$\tau' = R'C = (4 \parallel 16) \times 10^3 \times 5 \times 10^{-9} = 1.6 \times 10^{-5} \text{ (s)} \quad 2'$$

$$V_0'(t) = -5 + [10 e^{-1} + 5] e^{-\frac{t-2 \times 10^{-5}}{\tau'}}$$

$$= -5 + (-5 + 10 e^{-1}) e^{-\frac{t-2 \times 10^{-5}}{1.6 \times 10^{-5}}} \text{ (V)}$$

$$= -5 - 1.32 e^{-\frac{t-2 \times 10^{-5}}{1.6 \times 10^{-5}}} \text{ (V)} \quad 2'$$


$$\Rightarrow V_0(t) = \begin{cases} -10 + 10 e^{-\frac{t}{2 \times 10^{-5}}} \\ -5 - 1.32 e^{-\frac{t-2 \times 10^{-5}}{1.6 \times 10^{-5}}} \end{cases} \quad 2'$$

注意單位  
 $\checkmark \quad 0 \leq t < 20\mu\text{s}$   
 $\checkmark \quad t \geq 20\mu\text{s}$

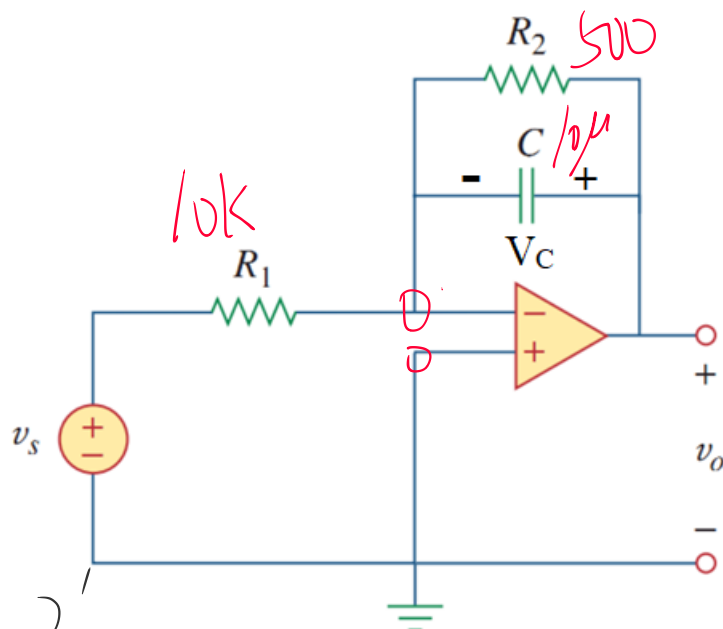6. For the circuit below. assume the operational amplifier is always working in its linear mode,  $V_C(0^-) = 5V$ ,  $R_1 = 10k\Omega$ ,  $R_2 = 500\Omega$ ,  $C = 10\mu F$

$$V_S(t) = \begin{cases} 0, & t \leq 0 \\ e^{-200t}, & t > 0 \end{cases}$$

Find output voltage of the Op Amp  $V_O(t)$  for  $t > 0$ .



$$V_O = V_C$$

$$\frac{-V_S}{R_1} = \frac{V_O}{R_2} + C \frac{dV_C}{dt}$$

$$-10^{-4} e^{-200t} = 2 \times 10^{-3} V_O + 10^{-5} \frac{dV_O}{dt}$$

$$-10 e^{-200t} = 200 V_O + \frac{dV_O}{dt}$$

$$V_O = e^{-200t} \left( \int_0^t -10 e^{-200t} \cdot e^{200t} dt + C \right) = (-10t + C) e^{-200t}$$

$$\text{Since } V_O(0) = V_C(0) = V_C(0^-) = 5V$$

$$\Rightarrow C = 5$$



$$\Rightarrow V_O(t) = (-10t + 5) e^{-200t} \quad (t > 0)$$

7. For the circuit below:

The switch in the circuit has been in *position a* for a long time.

At  $t = 0$  s, it moves instantaneously to *position b*, where it remains for 5 s before moving instantaneously to *position c*.

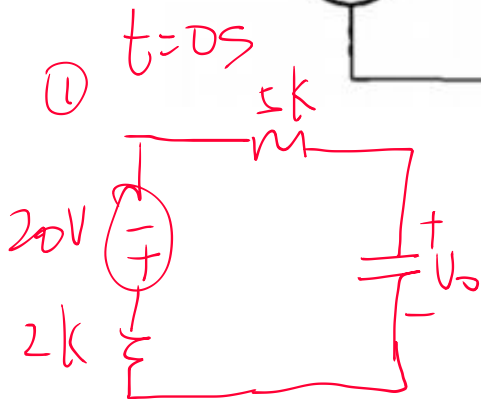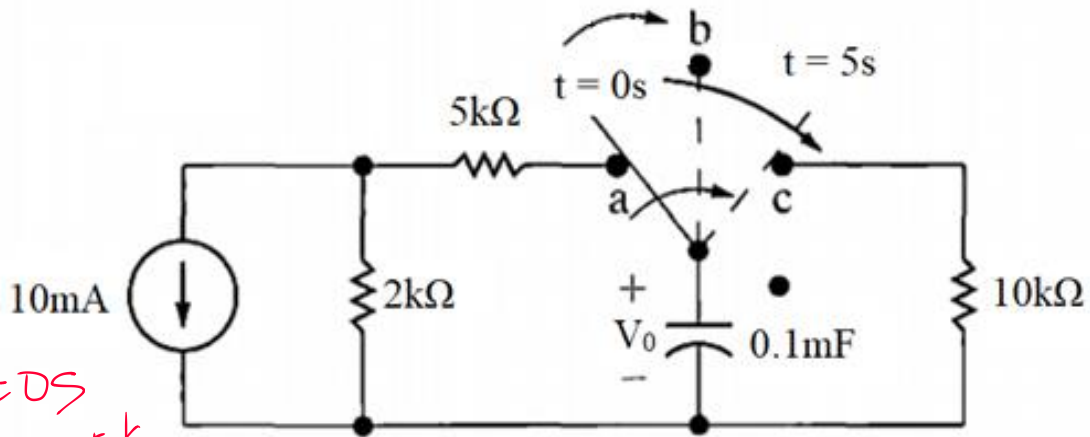Find the expressions for  $V_0(t)$  for  $t \geq 0$ .



$$V_0(0) = \frac{2 \times 10^{-3} \times 10 \times 10^{-3}}{2} = -20(V)$$

②  $0 < t < 5s$  : the circuit is closed, thus  $V_0(t)$  remains  $-20V$

③  $5s \leq t$   $V_0(t) = V_0(5s) = -20(V)$  Since no source  $V_0(t) = 0(V)$

$$i_0(t) = C \frac{dV_0(t)}{dt} \quad \tau = RC = 1(s)$$

$$V_0 = \frac{1}{0.1mF} \times 10k\Omega$$

$$\Rightarrow V_0(t) = -20e^{-(t-5)}(V) \quad t \geq 5s$$

$$\Rightarrow V_0(t) = \begin{cases} -20V & 0 \leq t < 5s \\ -20e^{-(t-5)}V & t \geq 5s \end{cases}$$