

RULES:

- Please try to work on your own. Discussion is permissible, but identical submissions are unacceptable! See “上海科技大学学生学术诚信规范与管理办法”, <http://sist.shanghaitech.edu.cn/cn/NewsDetail.asp?id=782>
- Please show all intermediate steps: a correct solution without an explanation will get zero credit.
- Please submit on time. NO late submission will be accepted.
- Please prepare your submission in English only. No Chinese submission will be accepted.

1. [6%] Three capacitors $C_1=5\mu\text{F}$, $C_2=10\mu\text{F}$, and $C_3=10\mu\text{F}$, are connected in parallel across a 150-V source. Determine:
- the total capacitance,
 - the charge on each capacitor,
 - the total energy stored in the parallel combination.

2. [8%] Consider the circuit in Fig. 1. Find:
- L_{eq} , $i_1(t)$ if $i_s=3e^{-t}\text{mA}$,
 - $v_o(t)$,
 - the energy stored in the 20-mH inductor at $t=1\text{s}$.

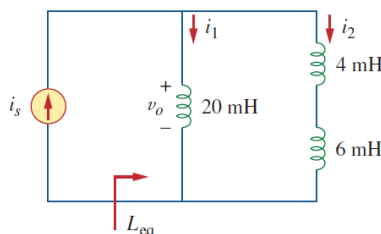


Fig. 1

3. [6%] A 4-mF capacitor has the terminal voltage

$$v = \begin{cases} 50\text{V}, & t \leq 0 \\ Ae^{-100t} + Be^{-600t}\text{V}, & t \geq 0 \end{cases}$$

If the capacitor has an initial current of 2 A, find:

- the constants A and B,
- the energy stored in the capacitor at $t = 0$,
- the capacitor current for $t > 0$.

4. [8%] A 100-mH inductor is connected in parallel with a 2-k Ω resistor. The current through the inductor is $i(t) = 50e^{-400t}$ mA.
- Find the voltage v_L across the inductor.
 - Find the voltage v_R across the resistor.
 - Does $v_L(t) + v_R(t) = 0$?
 - Calculate the energy in the inductor at $t=0$.

5. [8%] A noninverting current amplifier is portrayed in Fig.2. Calculate the gain i_o/i_s . Take $R_1 = 8k\Omega$ and $R_2 = 1k\Omega$.

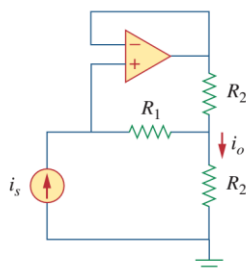


Fig.2

6. [8%] A voltage-to-current converter is shown in Fig.3, where $i_L = Av_i$. if $R_1R_2 = R_3R_4$. Find the constant term A.

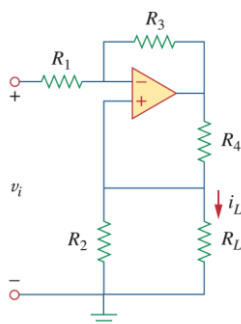


Fig.3

7. [10%] The switch in the circuit has been in position *a* for a long time and $v_2 = 0V$. At $t = 0$, the switch is thrown to position *b*. Calculate
- i, v_1 , and v_2 for $t \geq 0^+$.
 - the energy stored in the capacitor at $t = 0$.
 - the energy trapped in the circuit if the switch remains in position *b* indefinitely.
 - the total energy dissipated in the $25k\Omega$ resistor if the switch remains in position *b* indefinitely.

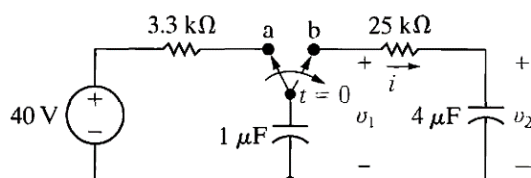


Fig.4

8. [8%] The switch in the circuit has been in position 1 for a long time. At $t = 0$ the switch moves instantaneously to position 2. Find the value of R so that 10% of the initial energy stored in the 10 mH inductor is dissipated in R in $10\mu\text{s}$.

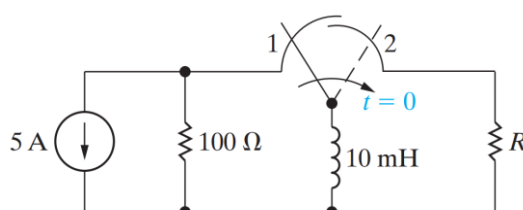


Fig.5

9. [10%] (a) Use component values from Appendix H (in the text book) to create a first-order RL circuit (see Fig. 6) with a time constant of $8\mu\text{s}$. Use a single inductor and a network of resistors, if necessary. Draw your circuit.

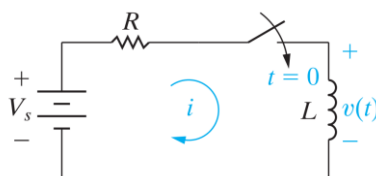


Fig. 6

- (b) Suppose the inductor you chose in part (a) has no initial stored energy. At $t=0$, a switch connects a voltage source with a value of 25V in series with the inductor and equivalent resistance. Write an expression for the current through the inductor for t greater or equal to 0 .
- (c) Using your result from part (b), calculate the time at which the current through the inductor reaches 75% of its final value.

10. [10%] The switch in the circuit shown in Fig.6. has been in the OFF position for a long time. At $t=0$, the switch moves instantaneously to the ON position. Find $V_0(t)$ for t greater or equal to 0 .

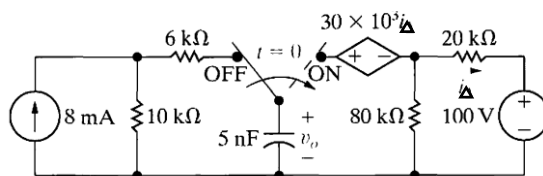


Fig.6

11. [10%] a) Show that the two magnetically coupled coils in the figure below can be replaced by a single coil having an inductance of

$$L_{ab} = \frac{L_1 L_2 - M^2}{L_1 + L_2 - 2M}$$

(Hint: Let i_1 and i_2 be clockwise mesh currents in the left and right windows of the figure below. Sum the voltages around the two meshes. In mesh 1 let V_{ab} be the unspecified applied voltage. Solve for di_1/dt as a function of V_{ab} .)

- b) Show that if the magnetic polarity of coil 2 is reversed, then

$$L_{ab} = \frac{L_1 L_2 - M^2}{L_1 + L_2 + 2M}$$

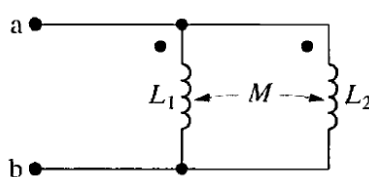


Fig.7

12. [10%] In the circuit below, switch 1 has been in position a and switch 2 has been closed for a long time. At $t = 0$, switch 1 moves instantaneously to position b. Eight hundred microseconds later, switch 2 opens, remains open for 300 μs , and then recloses. Find V_0 1.5 ms after switch 1 makes contact with terminal b.

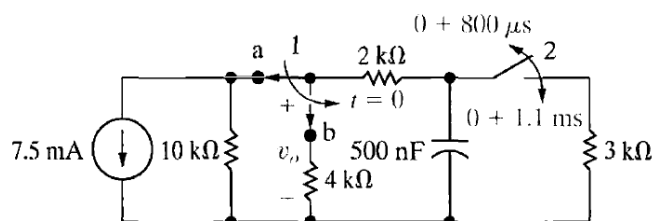


Fig.8