




Lecture 6


- Second-Order Circuits

Second-Order Circuits

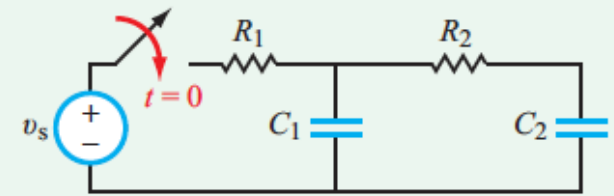
- Two energy storage elements
- Analysis: Determine voltage or current as a function of time
- A second order circuit is characterized by a second order differential equation.
- Initial/final values of voltage/current, *and their derivatives* are needed




(a) 2 capacitors

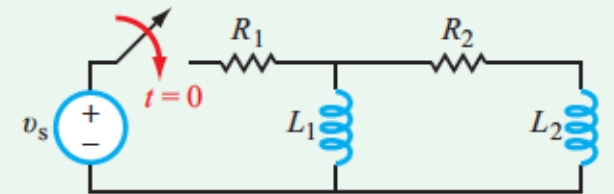

(b) 2 inductors

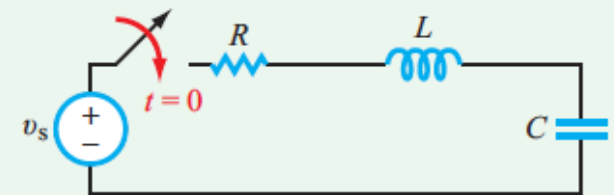


(c) Series RLC

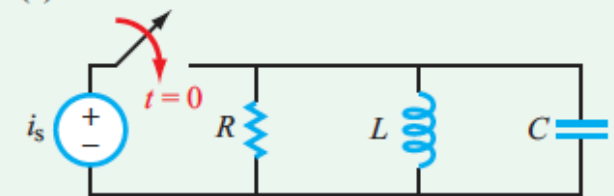

(d) Parallel RLC

Source-Free Series RLC

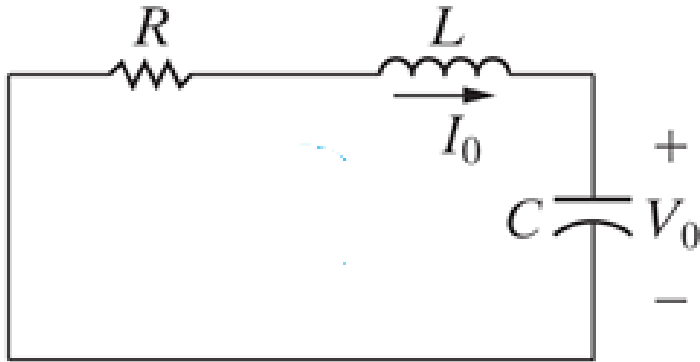


$$\frac{d^2 v}{dt^2} + \frac{R}{L} \frac{dv}{dt} + \frac{1}{LC} v = 0$$

$$s^2 + \frac{R}{L}s + \frac{1}{LC} = 0$$

$$s = -\frac{R}{2L} \pm \sqrt{\left(\frac{R}{2L}\right)^2 - \frac{1}{LC}}$$



Initial and Final Conditions

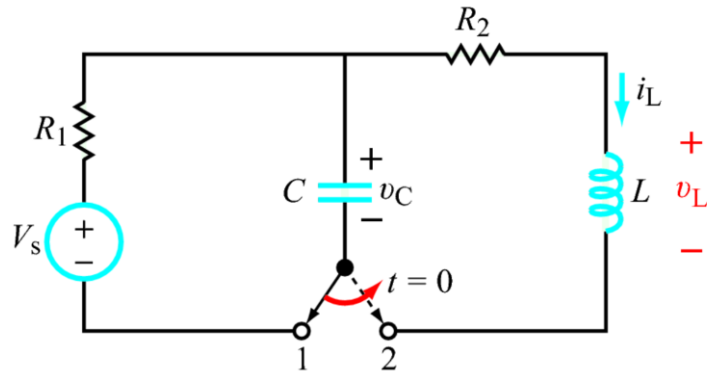




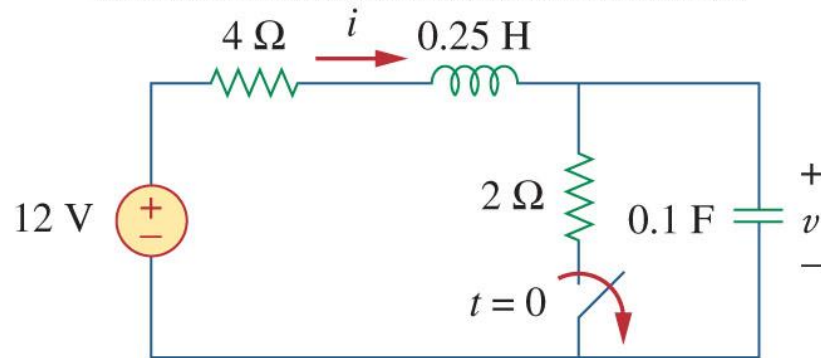
Example

- The switch has been closed for a long time. It is open at $t = 0$. Find
 - $i(0^+)$, $v(0^+)$
 - $di(0^+)/dt$, $dv(0^+)/dt$
 - $i(\infty)$, $v(\infty)$


Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display



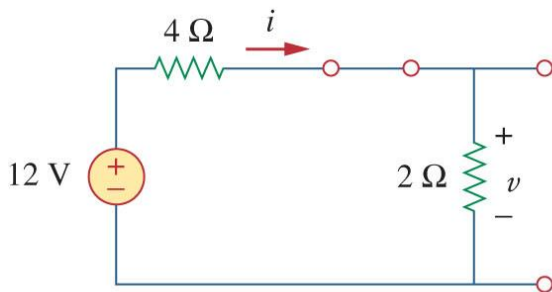
Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display



(a)

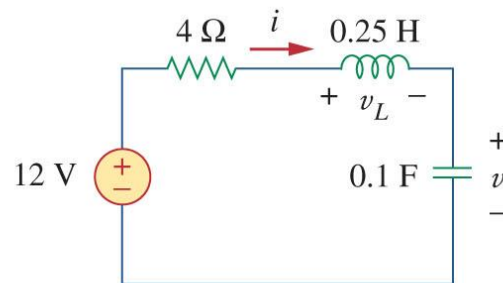

(b)

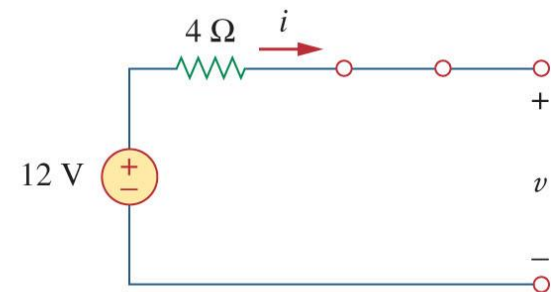

(c)




Exercise

- Assume the circuit has reached steady state at $t = 0^-$.


Find

- $i(0^+)$, $v(0^+)$
- $di(0^+)/dt$, $dv(0^+)/dt$
- $i(\infty)$, $v(\infty)$

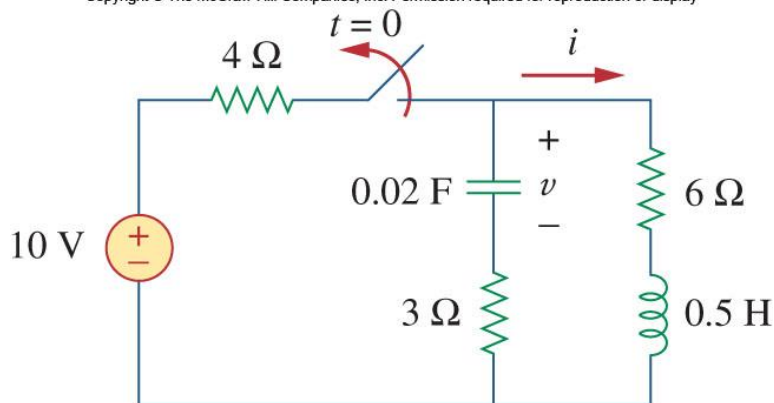Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display



Source-Free Series RLC

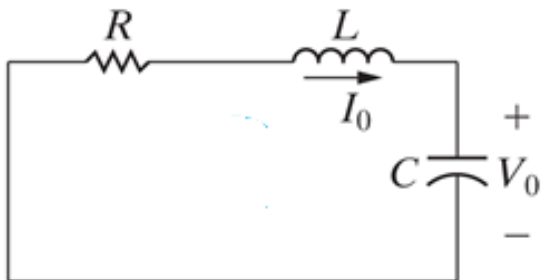


$$\frac{d^2 v}{dt^2} + \frac{R}{L} \frac{dv}{dt} + \frac{1}{LC} v = 0$$

$$s^2 + \frac{R}{L} s + \frac{1}{LC} = 0$$

$$s = -\frac{R}{2L} \pm \sqrt{\left(\frac{R}{2L}\right)^2 - \frac{1}{LC}}$$



Case 1: Overdamped ($\alpha > \omega_0$)

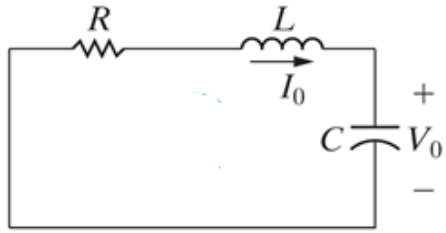

$$\frac{d^2 v}{dt^2} + \frac{R}{L} \frac{dv}{dt} + \frac{1}{LC} v = 0$$


$$s = -\frac{R}{2L} \pm \sqrt{\left(\frac{R}{2L}\right)^2 - \frac{1}{LC}}$$


$$\alpha = \frac{R}{2L} \quad \omega_0 = \frac{1}{\sqrt{LC}}$$



An example


$$V_c = 2e^{-t} + 3e^{-t/2}$$

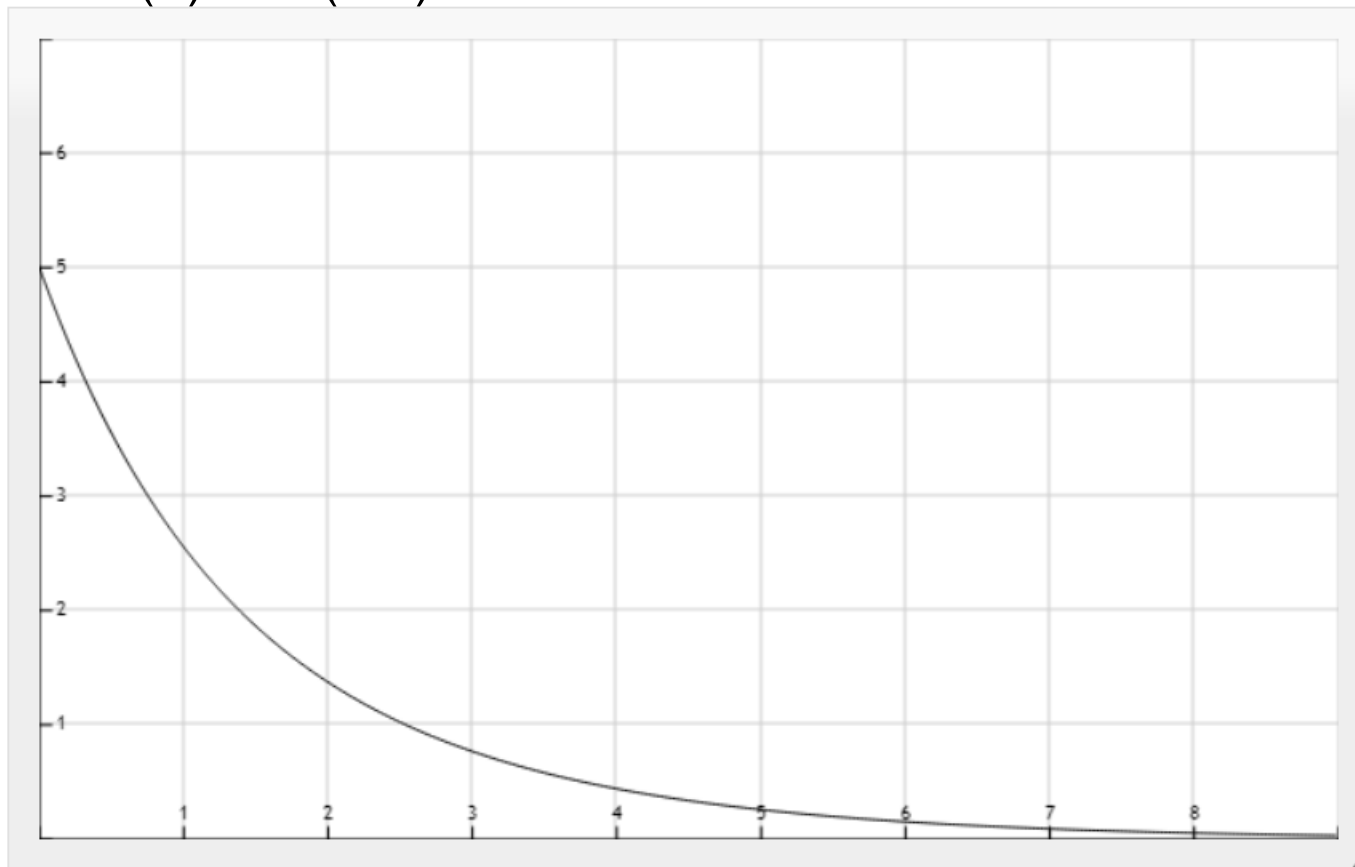

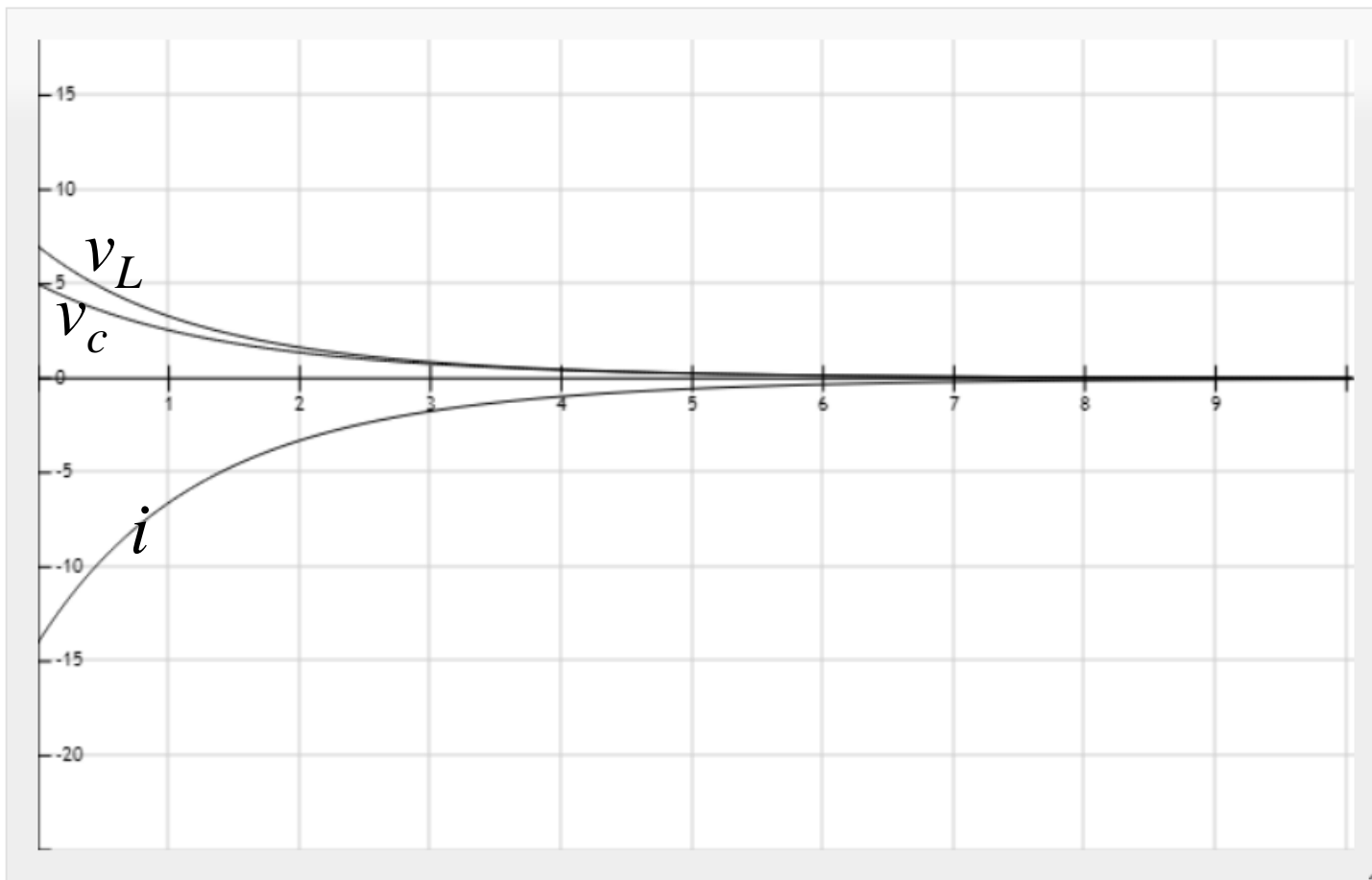





Another example

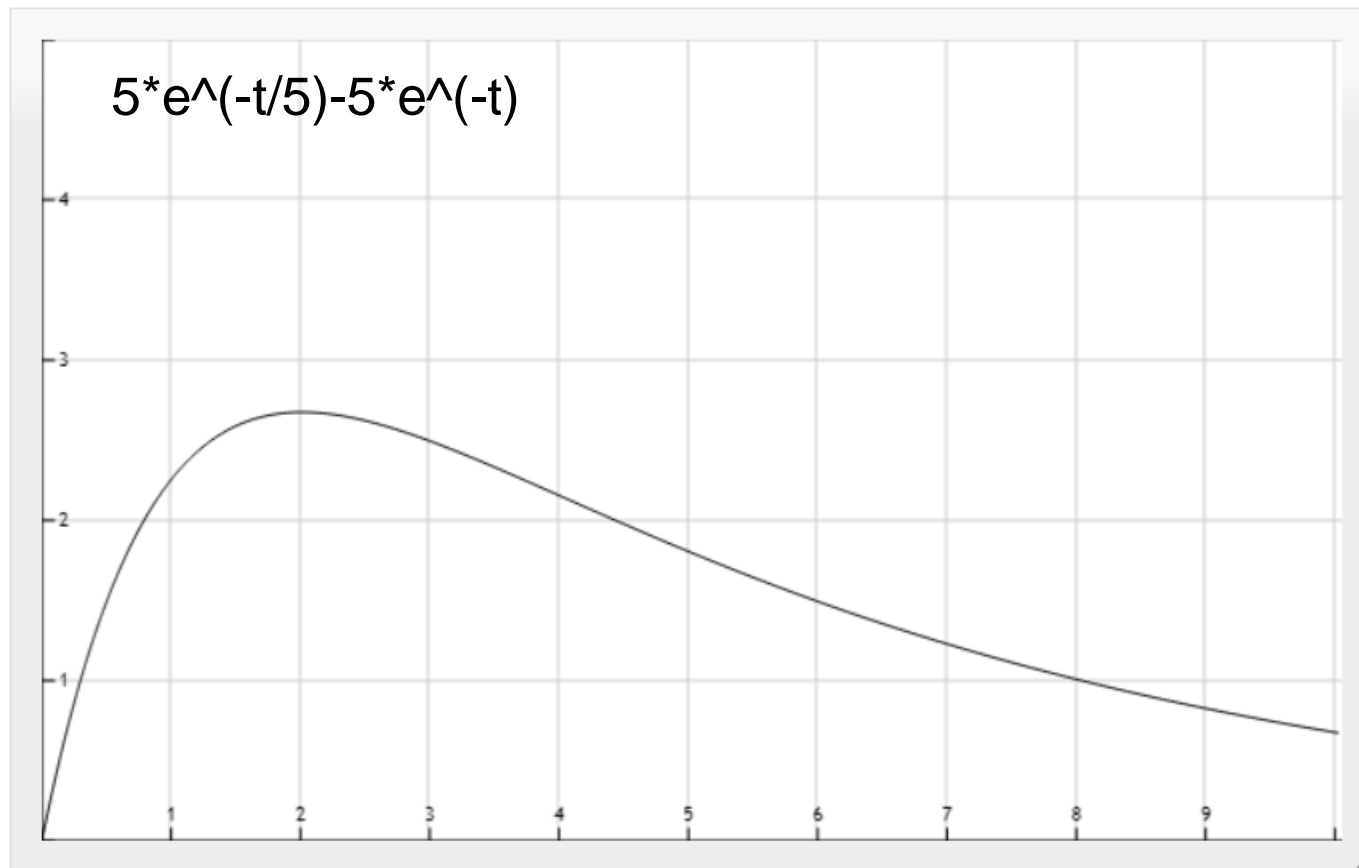




Zoomed-in
 V_L for $t > 4$

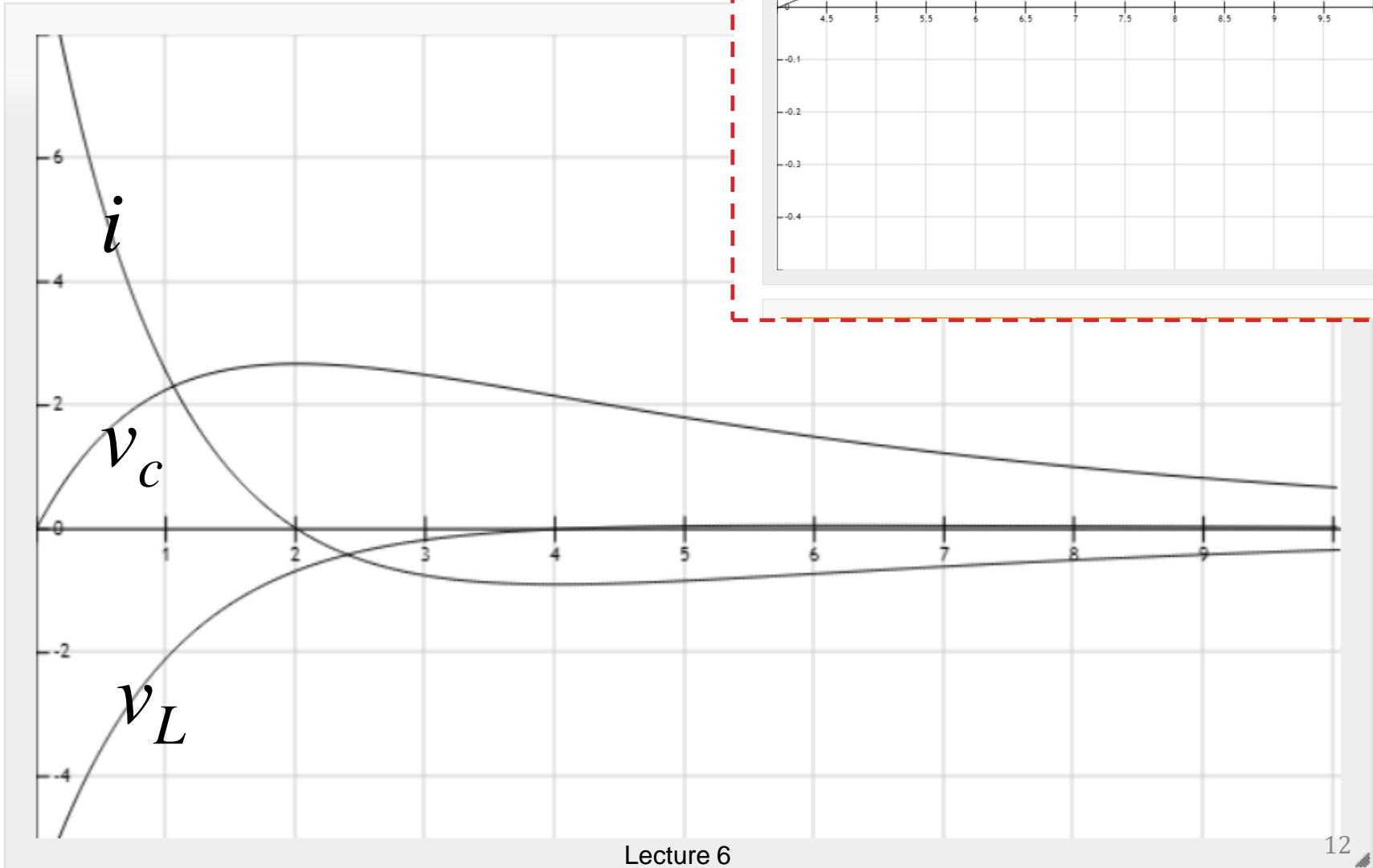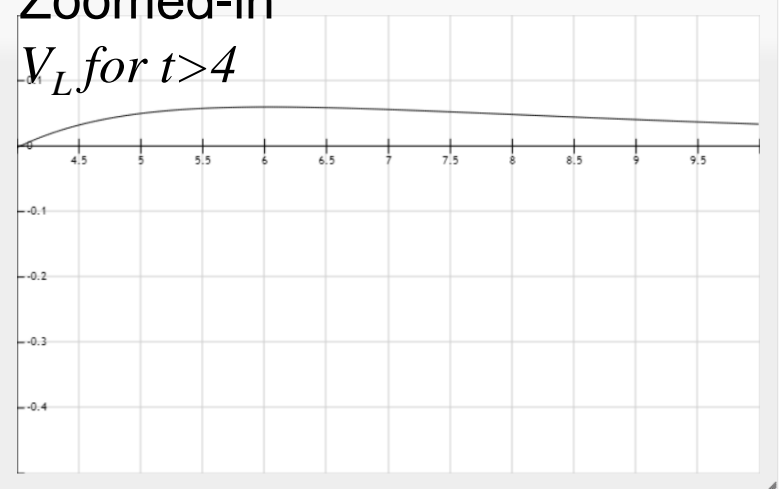

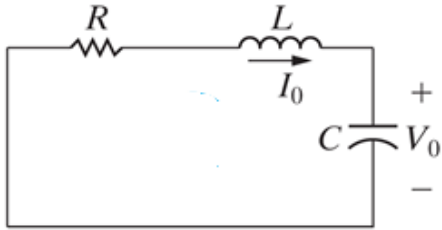Case 2: Critically Damped ($\alpha = \omega_0$)



$$\frac{d^2 v}{dt^2} + \frac{R}{L} \frac{dv}{dt} + \frac{1}{LC} v = 0 \quad s = -\frac{R}{2L} \pm \sqrt{\left(\frac{R}{2L}\right)^2 - \frac{1}{LC}}$$

$$\alpha = \frac{R}{2L} \quad \omega_0 = \frac{1}{\sqrt{LC}} \quad s_1 = -\alpha + \sqrt{\alpha^2 - \omega_0^2} \quad s_2 = -\alpha - \sqrt{\alpha^2 - \omega_0^2}$$

$$s_1 = s_2 = -\alpha = -\frac{R}{2L} \quad v(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t}$$




Case 2: Critically Damped ($\alpha=\omega_0$)


$$v(t) = (A_1 t + A_2)e^{-\alpha t}$$



Case 2: Critically Damped ($\alpha = \omega_0$)

$$v(t) = (A_1 t + A_2)e^{-\alpha t}$$

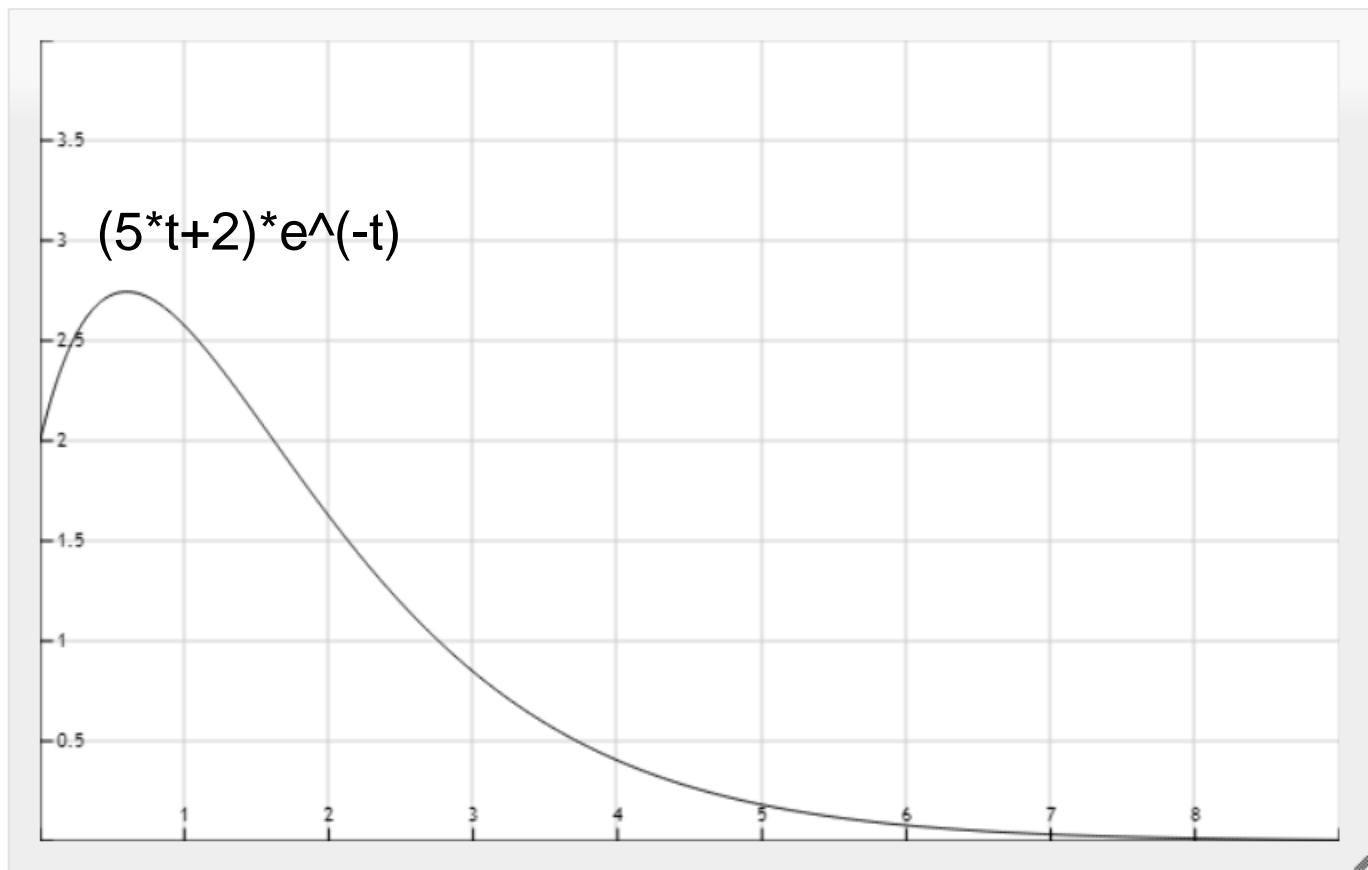

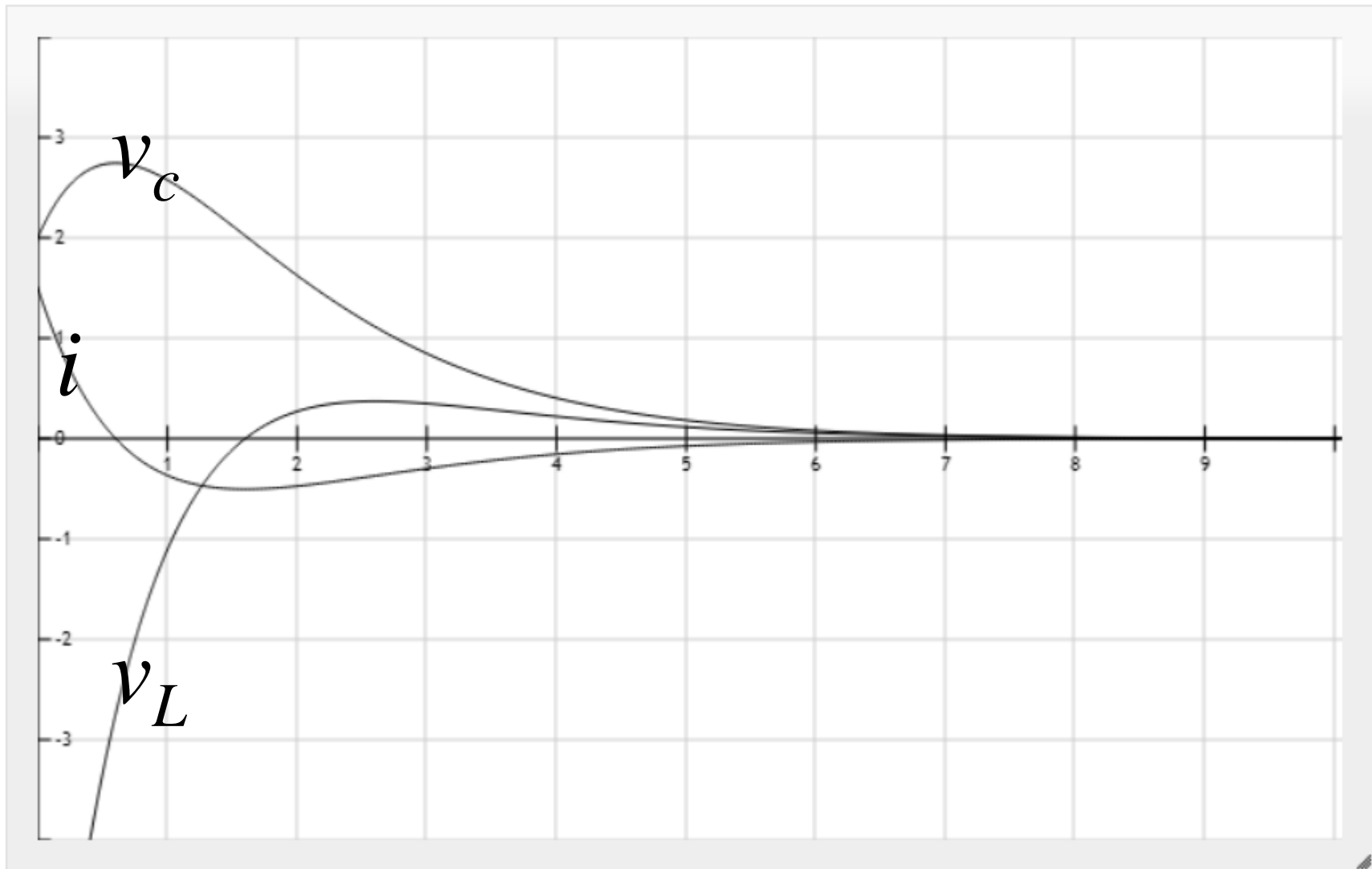



Case 3: Underdamped ($\alpha < \omega_0$)

$$s = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2}$$

$$s_1 = -\alpha + \sqrt{\alpha^2 - \omega_0^2} = -\alpha + \sqrt{-(\omega_0^2 - \alpha^2)} = -\alpha + j\omega_d$$

$$s_2 = -\alpha - \sqrt{\alpha^2 - \omega_0^2} = -\alpha - \sqrt{-(\omega_0^2 - \alpha^2)} = -\alpha - j\omega_d$$

where $j = \sqrt{-1}$ and $\omega_d = \sqrt{\omega_0^2 - \alpha^2}$.

- ω_0 is often called the resonant frequency;
- ω_d is called the damping frequency.


The natural response

$$v(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t}$$


becomes

$$v(t) = e^{-\alpha t} (B_1 \cos \omega_d t + B_2 \sin \omega_d t)$$
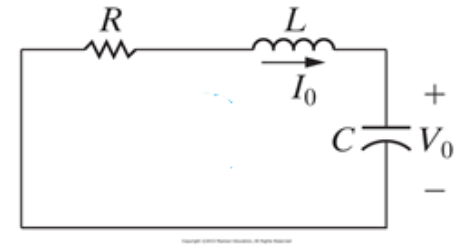
$$v(t) = e^{-\alpha t} (B_1 \cos \omega_d t + B_2 \sin \omega_d t)$$




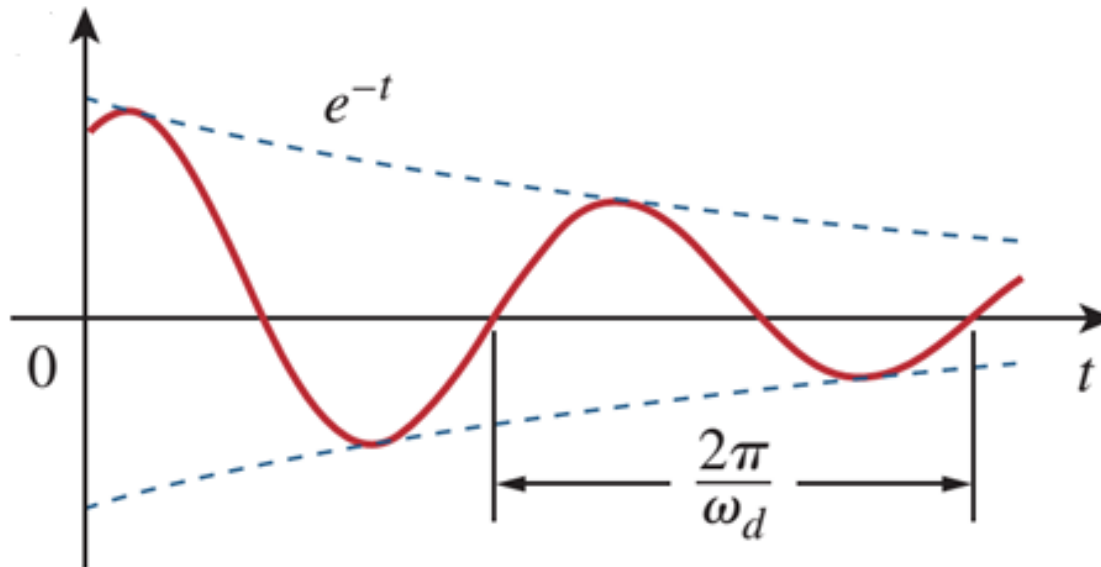
- Exponential $e^{-\alpha t}$ * Sine/Cosine term
 - Exponentially damped, time constant = $1/\alpha$
 - Oscillatory, period $T = \frac{2\pi}{\omega_d}$






T=?

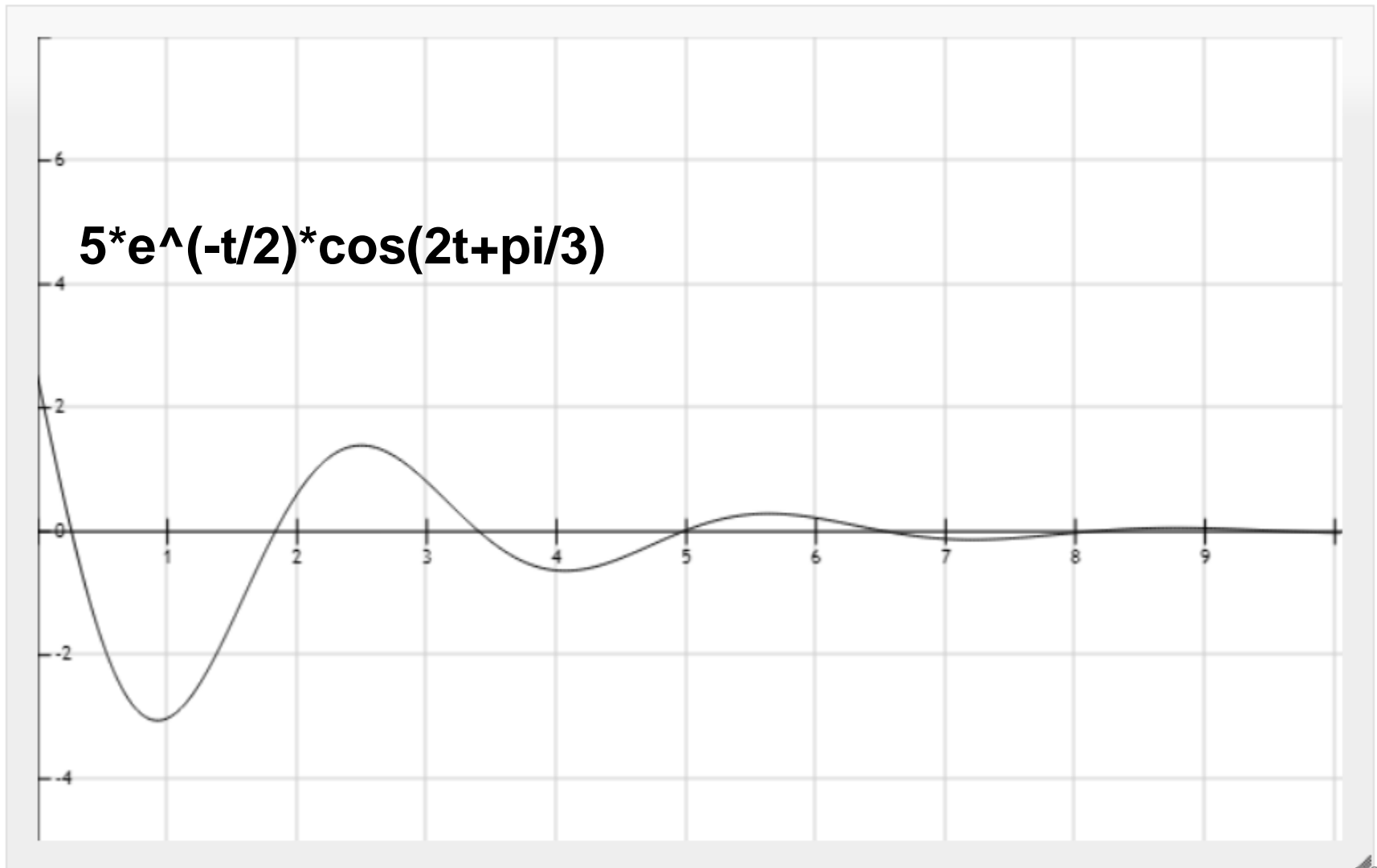

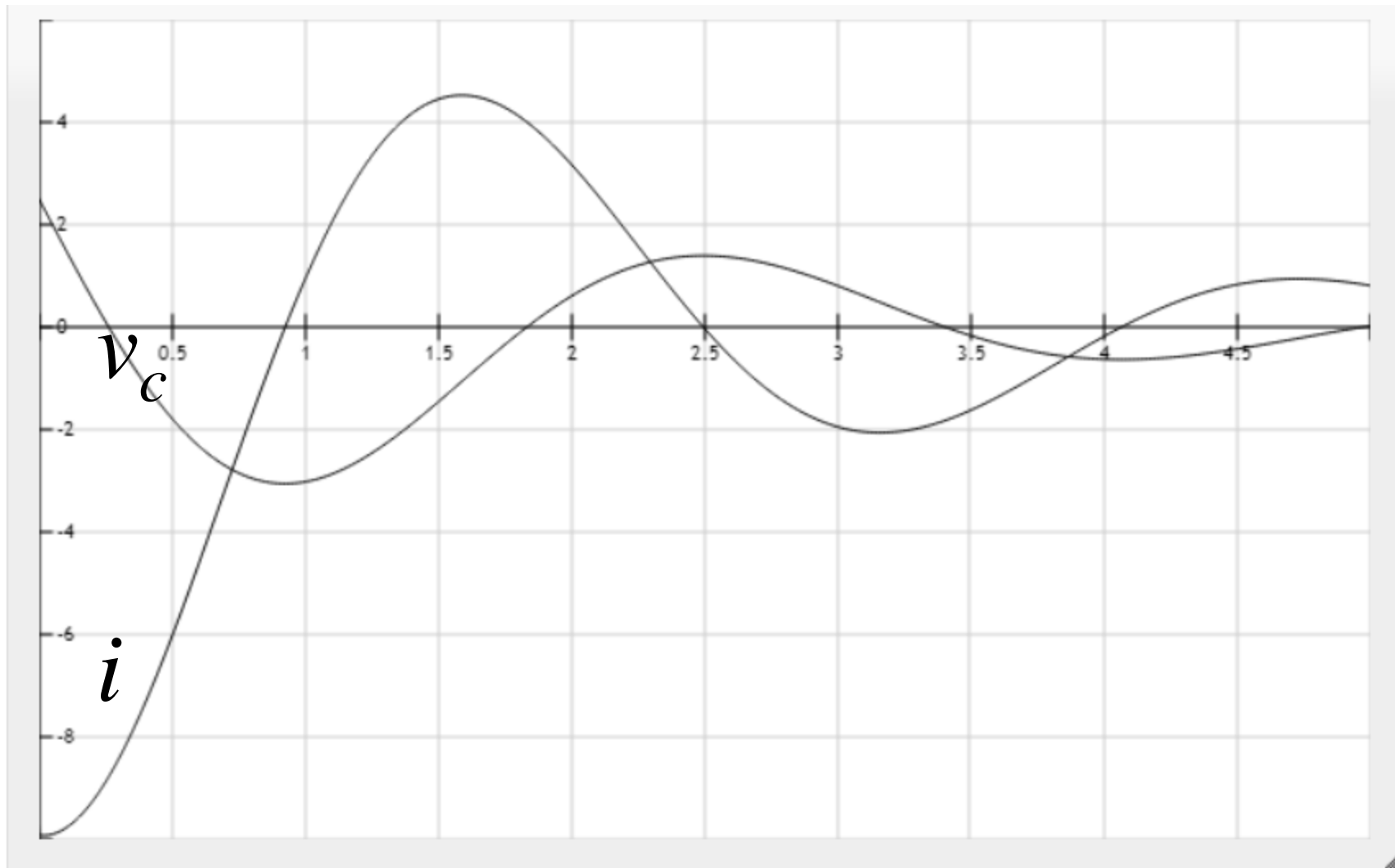

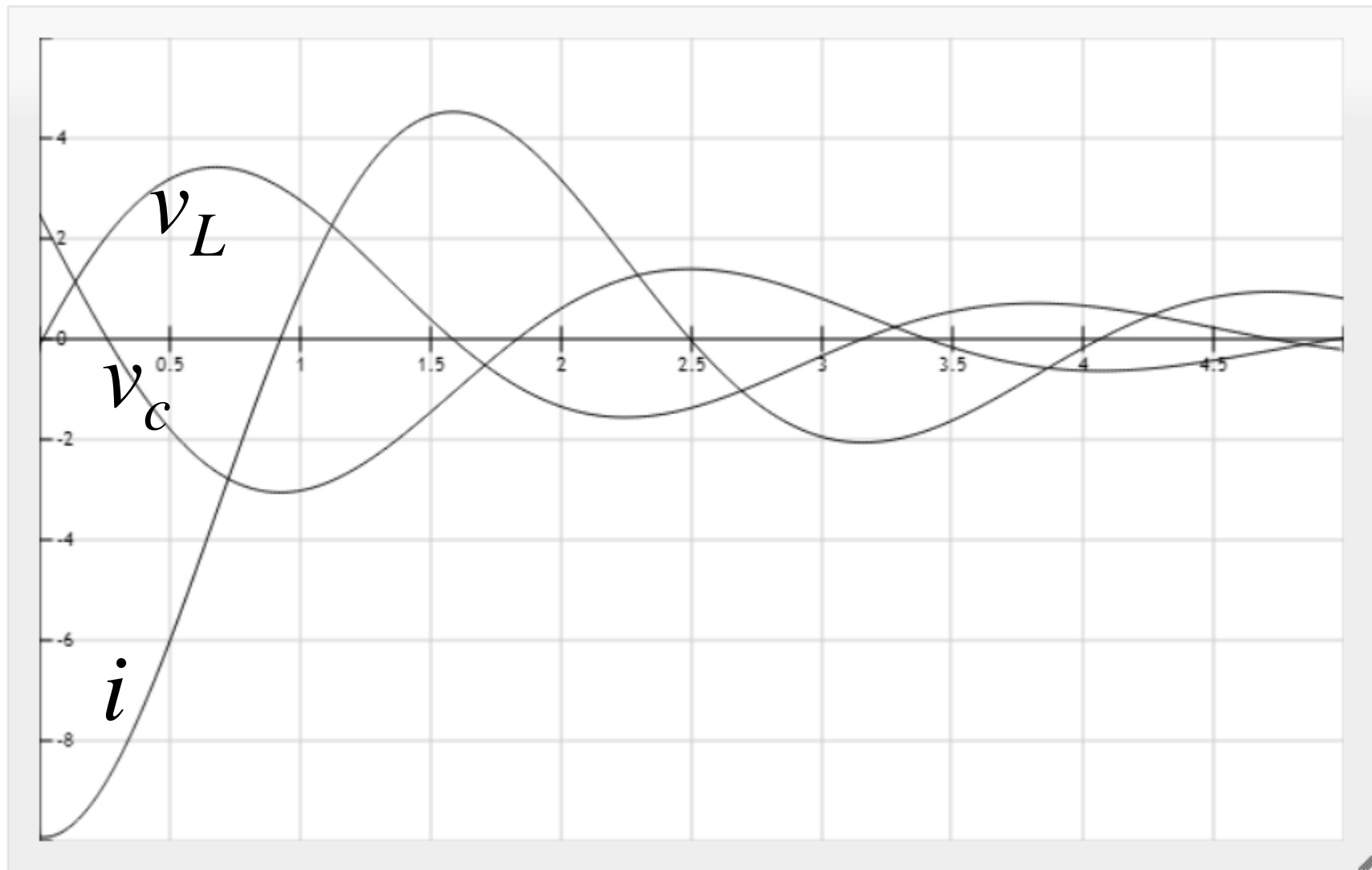

Properties of Series RLC Network

- Behavior captured by damping
 - Gradual loss of the initial stored energy
 - α determines the rate of damping

- $\alpha > \omega_0$ (i.e., $R > 2\sqrt{\frac{L}{C}}$), overdamped


$$v(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t}$$

- $\alpha = \omega_0$ (i.e., $R = 2\sqrt{\frac{L}{C}}$), critically damped

$$v(t) = (A_1 t + A_2) e^{-\alpha t}$$

- $\alpha < \omega_0$ (i.e., $R < 2\sqrt{\frac{L}{C}}$), underdamped
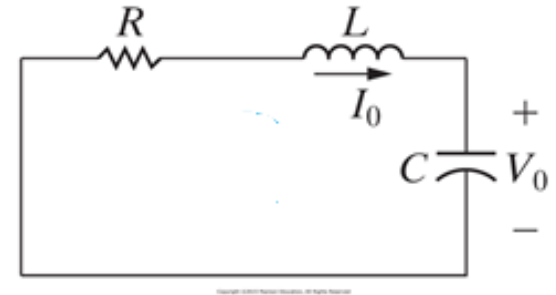
$$v(t) = e^{-\alpha t} (B_1 \cos \omega_d t + B_2 \sin \omega_d t)$$






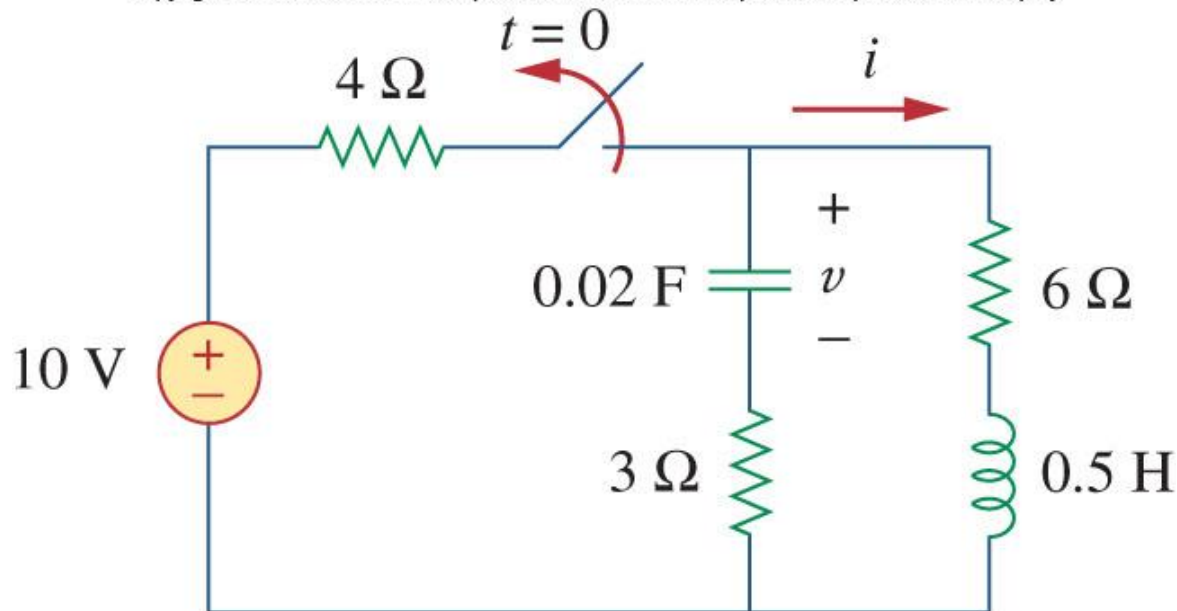Example

- Find $v(t)$ & $i(t)$ in the circuit below. Assume the circuit has reached steady state at $t = 0^-$.


Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display



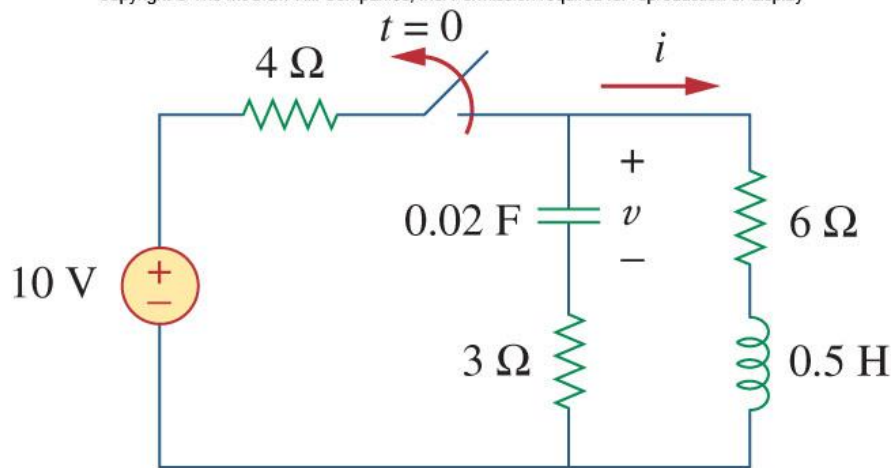Example



- Find $v(t)$ & $i(t)$ in the circuit below. Assume the circuit has reached steady state at $t = 0^-$.

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display



$$\alpha = \frac{R}{2L} = 9 \quad \omega_0 = \frac{1}{\sqrt{LC}} = 10$$

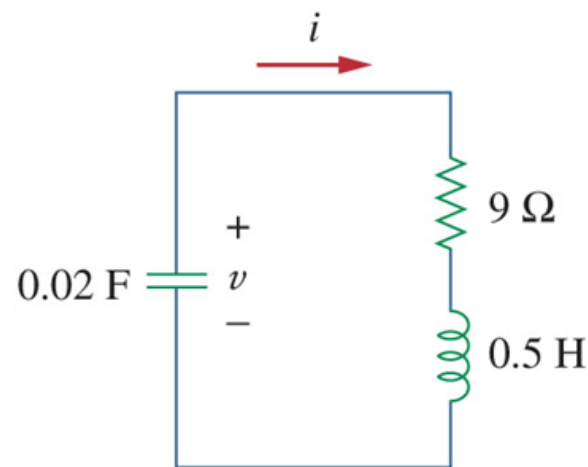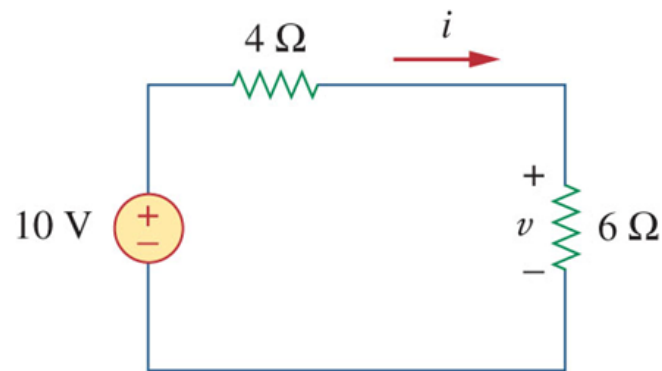
$$s_{1,2} = -\alpha \mp \sqrt{\alpha^2 - \omega_0^2} = -9 \mp j4.359$$





Source-Free Parallel RLC Network

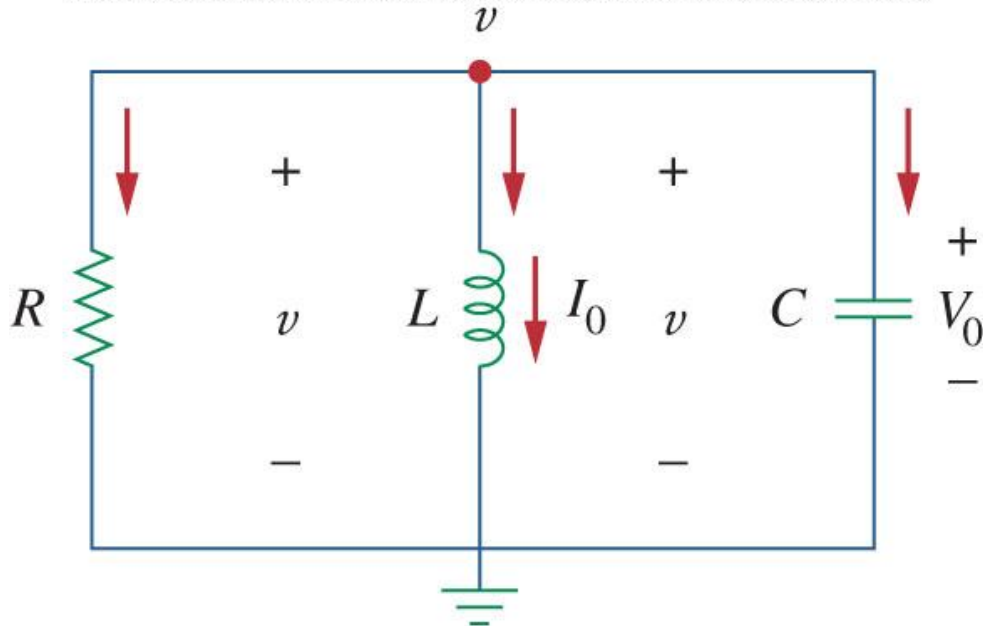Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display



Source-Free Parallel RLC Network

$$\frac{d^2v}{dt^2} + \frac{1}{RC} \frac{dv}{dt} + \frac{1}{LC} v = 0$$

- The characteristic equation is:


$$s^2 + \frac{1}{RC} s + \frac{1}{LC} = 0$$

From this, we can find the roots of the characteristic equation to be:

$$s_{1,2} = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2}$$

$$\alpha = \frac{1}{2RC} \quad \omega_0 = \frac{1}{\sqrt{LC}}$$

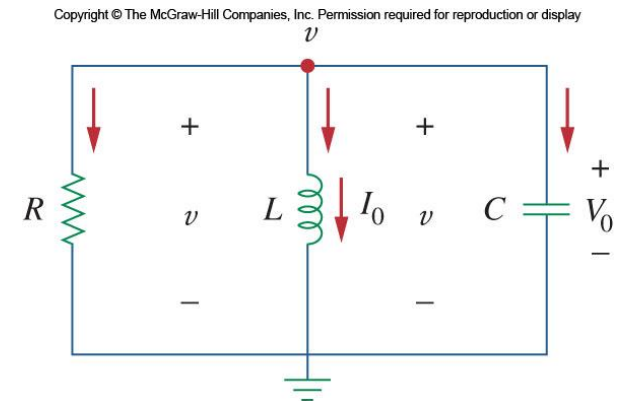As in last time, there are three scenarios to consider.



Three Damping Cases

$$\frac{d^2v}{dt^2} + \frac{1}{RC} \frac{dv}{dt} + \frac{1}{LC} v = 0$$

$$s_{1,2} = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2}$$

$$\alpha = \frac{1}{2RC} \quad \omega_0 = \frac{1}{\sqrt{LC}}$$

- For the overdamped case, the roots are real and negative,

$$v(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t}$$

- For critically damped, the roots are real and equal

$$v(t) = (A_2 + A_1 t) e^{-\alpha t}$$

- In the underdamped case, the roots are complex

$$v(t) = e^{-\alpha t} (A_1 \cos \omega_d t + A_2 \sin \omega_d t)$$


Series vs. Parallel (Source-Free RLC Network)

• Series

$$v(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t}$$

$$v(t) = (A_1 t + A_2) e^{-\alpha t}$$
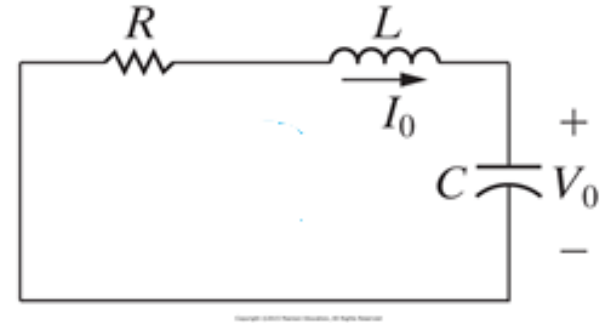
$$v(t) = e^{-\alpha t} (B_1 \cos \omega_d t + B_2 \sin \omega_d t)$$




• Parallel


$$v(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t}$$

$$v(t) = (A_2 + A_1 t) e^{-\alpha t}$$
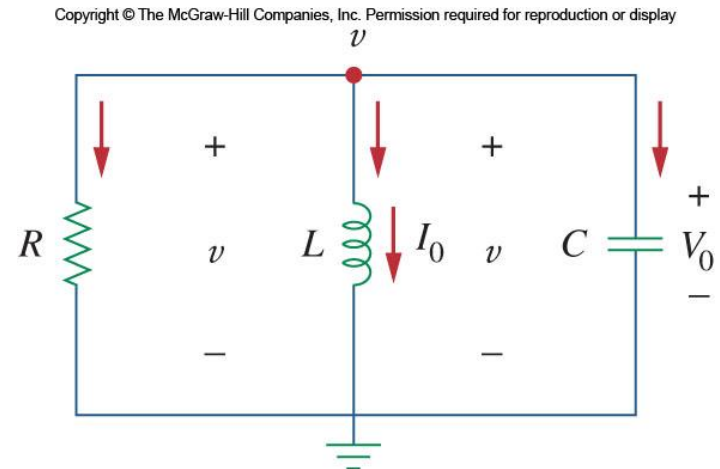
$$v(t) = e^{-\alpha t} (A_1 \cos \omega_d t + A_2 \sin \omega_d t)$$



Step Response of a Series RLC Circuit

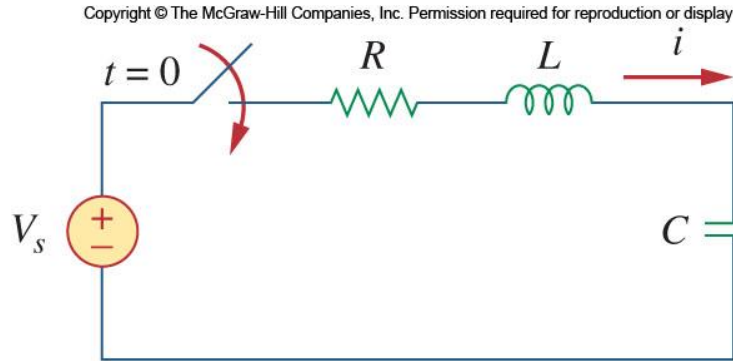

$$\frac{d^2v}{dt^2} + \frac{R}{L} \frac{dv}{dt} + \frac{v}{LC} = \frac{V_s}{LC}$$

- The solution

$$v(t) = v_t(t) + v_{ss}(t)$$

- The complete solutions for the three conditions of damping are:

$$v(t) = V_s + (A_1 e^{s_1 t} + A_2 e^{s_2 t}) \quad (\text{Overdamped})$$

$$v(t) = V_s + (A_1 + A_2 t) e^{-\alpha t} \quad (\text{Critically Damped})$$

$$v(t) = V_s + (A_1 \cos \omega_d t + A_2 \sin \omega_d t) e^{-\alpha t} \quad (\text{Underdamped})$$

Example

- Find $v(t)$ and $i(t)$ for $t > 0$.

Consider three cases:

- $R = 5\Omega$
- $R = 4\Omega$
- $R = 1\Omega$

When $R = 5\Omega$,


- For $t < 0$, switch closed, capacitor open, inductor shorted.


$$i(0) = 4A = C \frac{dv(0)}{dt}, \quad v(0) = 4V, \quad \frac{dv(0)}{dt} = 16$$

- For $t > 0$, switch open, a series RLC network

$$\alpha = \frac{R}{2L} = 2.5, \quad \omega_0 = \frac{1}{\sqrt{LC}} = 2, \quad s_{1,2} = -1, -4 \quad \text{Overdamped.}$$
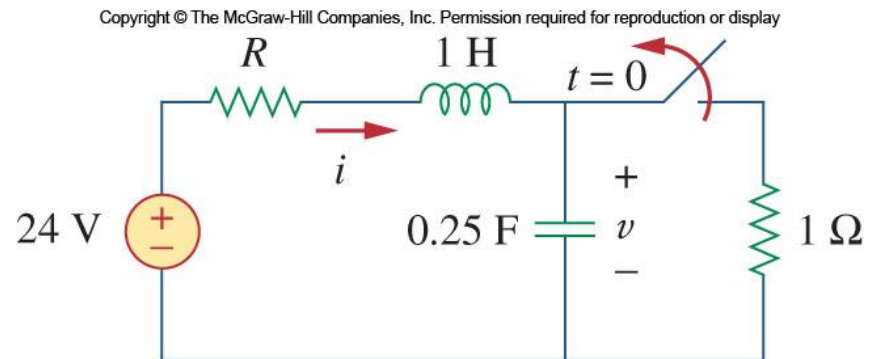
$$v(t) = v_{ss} + (A_1 e^{-t} + A_2 e^{-4t})$$



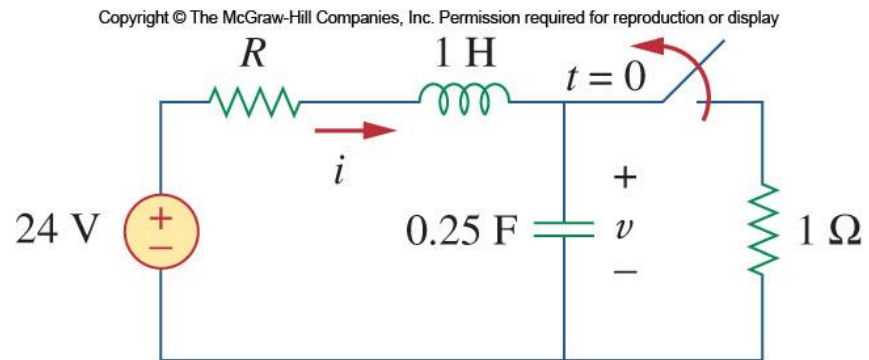

When $R = 4\Omega$,


- For $t < 0$, switch closed, capacitor open, inductor shorted.

$$i(0) = 4.8A = C \frac{dv(0)}{dt}, \quad v(0) = 4.8V, \quad \frac{dv(0)}{dt} = 19.2$$

- For $t > 0$, switch open, a series RLC network

$$\alpha = \frac{R}{2L} = 2, \quad \omega_0 = \frac{1}{\sqrt{LC}} = 2, \quad s_{1,2} = -2 \quad \text{Critically damped}$$

$$v(t) = v_{ss} + (A_1 + A_2 t)e^{-2t}$$

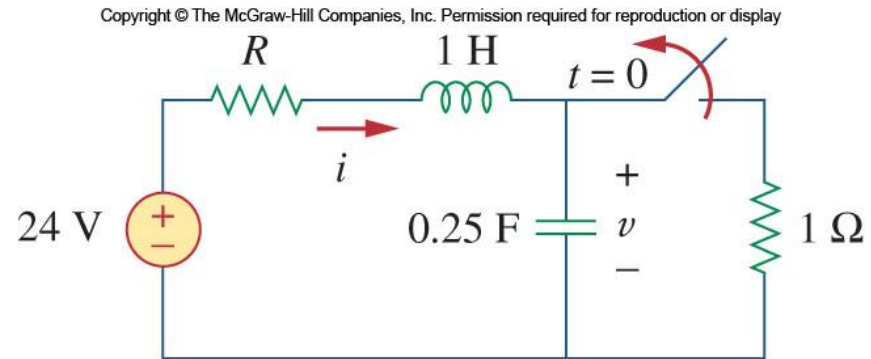

When $R = 1\Omega$,

- For $t < 0$, switch closed, capacitor open, inductor shorted.

$$i(0) = 12A = C \frac{dv(0)}{dt}, \quad v(0) = 12V, \quad \frac{dv(0)}{dt} = 48$$


- For $t > 0$, switch open, a series RLC network

$$\alpha = \frac{R}{2L} = 0.5, \quad \omega_0 = \frac{1}{\sqrt{LC}} = 2, \quad s_{1,2} = -0.5 \pm j1.936 \quad \text{Underdamped}$$

$$v(t) = v_{ss} + (A_1 \cos 1.936t + A_2 \sin 1.936t)e^{-0.5t}$$




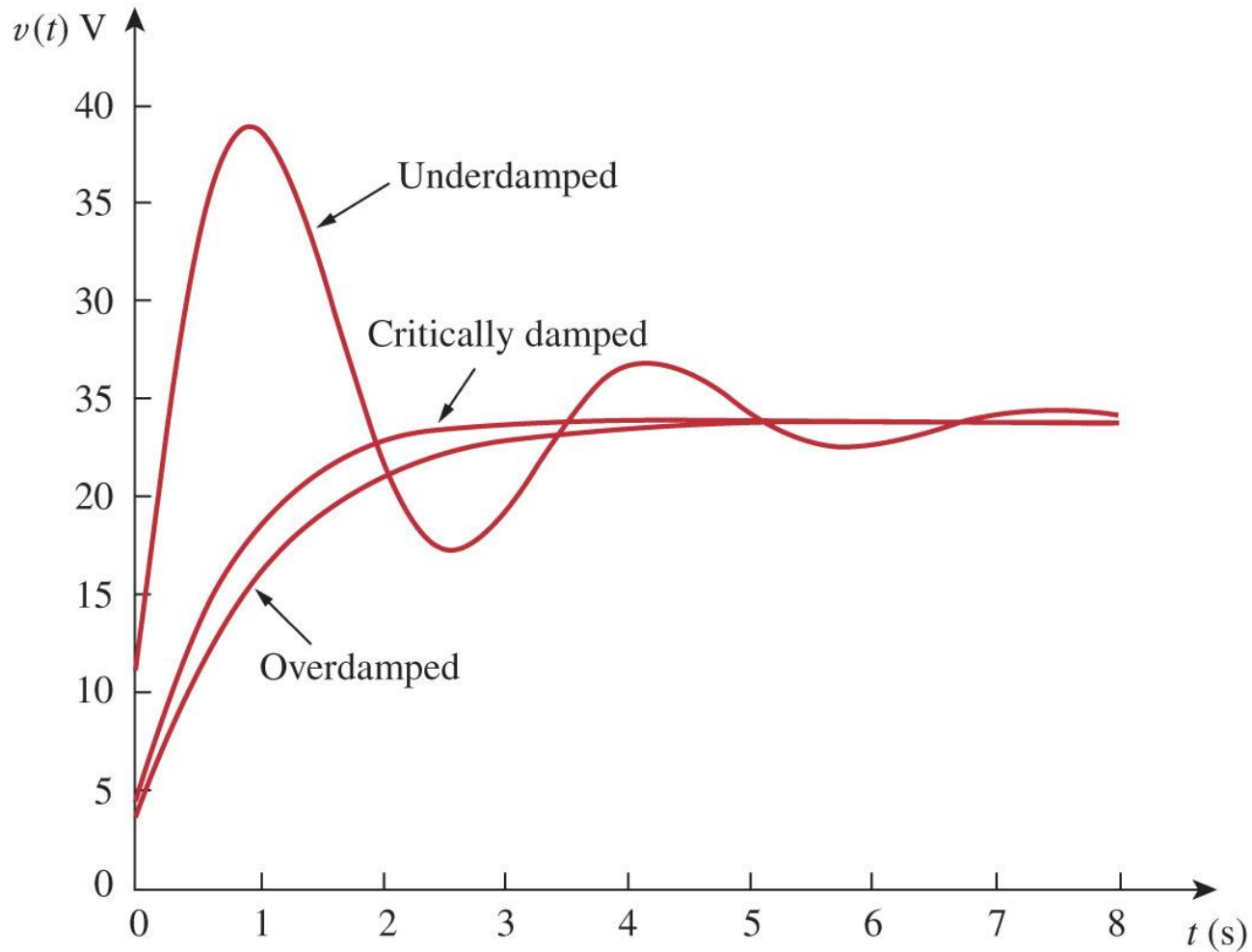Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display



Step Response of a Parallel RLC Circuit

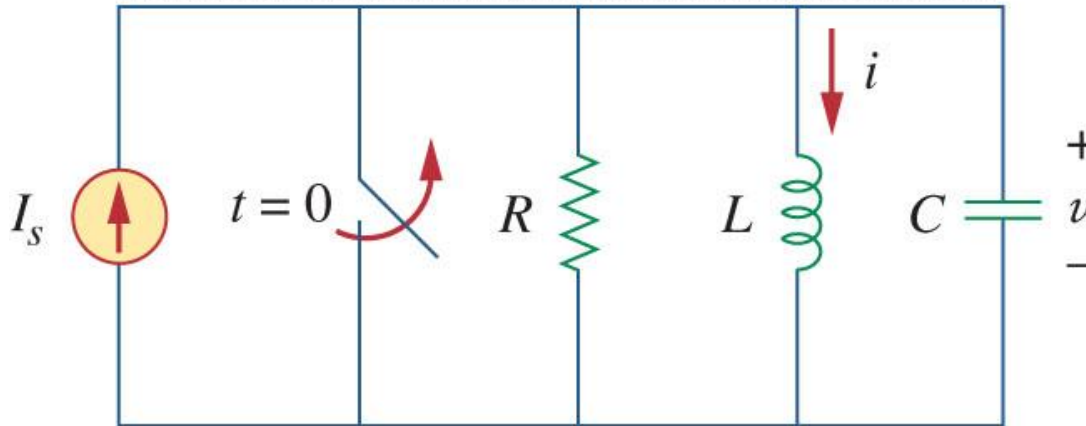Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display



Apply KCL,

$$\frac{v}{R} + i + C \frac{dv}{dt} = I_s$$

But

$$v = L \frac{di}{dt}$$

So we get

$$\frac{d^2 i}{dt^2} + \frac{1}{RC} \frac{di}{dt} + \frac{i}{LC} = \frac{I_s}{LC}$$



Step Response of a Parallel RLC Circuit

$$\frac{d^2 i}{dt^2} + \frac{1}{RC} \frac{di}{dt} + \frac{i}{LC} = \frac{I_s}{LC}$$

- As in the series RLC case, the response is a combination of **transient and steady state responses**:

$$i(t) = I_s + A_1 e^{s_1 t} + A_2 e^{s_2 t} \quad (\text{Overdamped})$$


$$i(t) = I_s + (A_1 + A_2 t) e^{-\alpha t} \quad (\text{Critically Damped})$$

$$i(t) = I_s + (A_1 \cos \omega_d t + A_2 \sin \omega_d t) e^{-\alpha t} \quad (\text{Underdamped})$$

Here the variables A_1 and A_2 are obtained from the initial conditions, $i(0)$ and $di(0)/dt$.

Example

- Find $i(t)$ and $i_R(t)$ for $t > 0$.

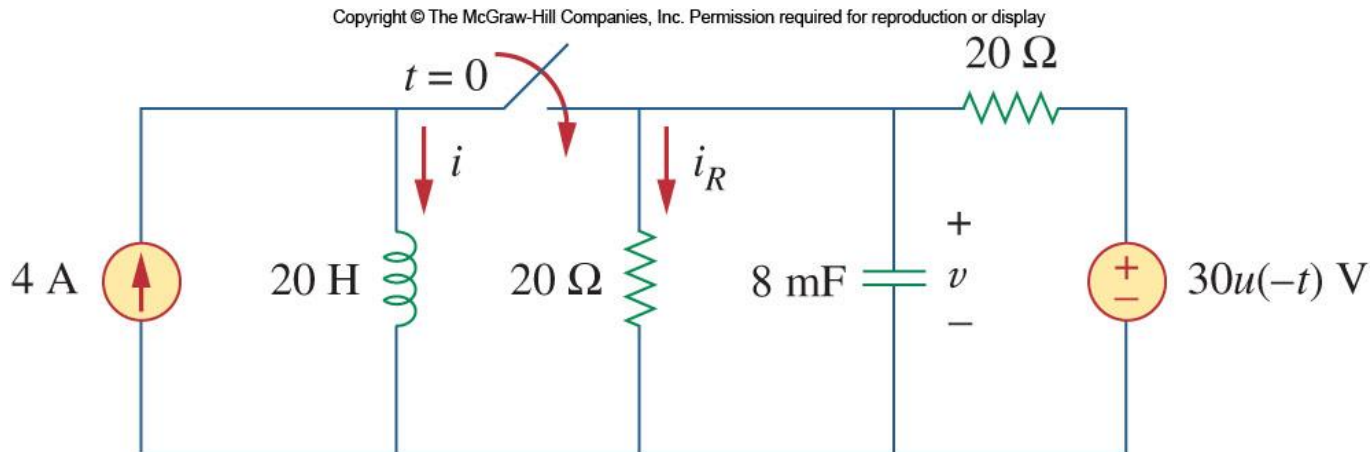



Initial values ($t < 0$): $i(0) = 4A$, $v(0) = \frac{20}{20+20} \times 30V = 15V = L \frac{di(0)}{dt}$

For $t > 0$, $\alpha = \frac{1}{2RC} = \frac{1}{2 \times 10 \times 8 \times 10^{-3}} = 6.25$, $\omega_0 = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{20 \times 8 \times 10^{-3}}} = 2.5$

$$s_{1,2} = -6.25 \pm 5.7282$$
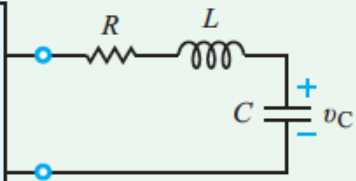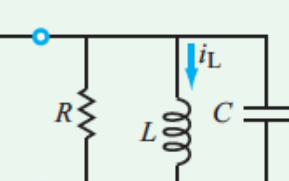
$$i(t) = I_s + A_1 e^{s_1 t} + A_2 e^{s_2 t}$$



<p style="text-align: center;">Series RLC</p> <div style="border: 1px solid black; padding: 5px; width: fit-content;"> <p>Input: dc circuit with switch action @ $t = 0$</p> </div> 	<p style="text-align: center;">Parallel RLC</p> <div style="border: 1px solid black; padding: 5px; width: fit-content;"> <p>Input: dc circuit with switch action @ $t = 0$</p> </div> 
<p style="text-align: center;">Total Response</p>	<p style="text-align: center;">Total Response</p>
<p>Overdamped ($\alpha > \omega_0$)</p> $v_C(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t} + v_C(\infty)$ $A_1 = \frac{\frac{1}{C} i_C(0) - s_2 [v_C(0) - v_C(\infty)]}{s_1 - s_2}$ $A_2 = \left[\frac{\frac{1}{C} i_C(0) - s_1 [v_C(0) - v_C(\infty)]}{s_2 - s_1} \right]$	<p>Overdamped ($\alpha > \omega_0$)</p> $i_L(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t} + i_L(\infty)$ $A_1 = \frac{\frac{1}{L} v_L(0) - s_2 [i_L(0) - i_L(\infty)]}{s_1 - s_2}$ $A_2 = \left[\frac{\frac{1}{L} v_L(0) - s_1 [i_L(0) - i_L(\infty)]}{s_2 - s_1} \right]$
<p>Critically Damped ($\alpha = \omega_0$)</p> $v_C(t) = (B_1 + B_2 t) e^{-\alpha t} + v_C(\infty)$ $B_1 = v_C(0) - v_C(\infty)$ $B_2 = \frac{1}{C} i_C(0) + \alpha [v_C(0) - v_C(\infty)]$	<p>Critically Damped ($\alpha = \omega_0$)</p> $i_L(t) = (B_1 + B_2 t) e^{-\alpha t} + i_L(\infty)$ $B_1 = i_L(0) - i_L(\infty)$ $B_2 = \frac{1}{L} v_L(0) + \alpha [i_L(0) - i_L(\infty)]$
<p>Underdamped ($\alpha < \omega_0$)</p> $v_C(t) = e^{-\alpha t} (D_1 \cos \omega_d t + D_2 \sin \omega_d t) + v_C(\infty)$ $D_1 = v_C(0) - v_C(\infty)$ $D_2 = \frac{\frac{1}{C} i_C(0) + \alpha [v_C(0) - v_C(\infty)]}{\omega_d}$	<p>Underdamped ($\alpha < \omega_0$)</p> $i_L(t) = e^{-\alpha t} (D_1 \cos \omega_d t + D_2 \sin \omega_d t) + i_L(\infty)$ $D_1 = i_L(0) - i_L(\infty)$ $D_2 = \frac{\frac{1}{L} v_L(0) + \alpha [i_L(0) - i_L(\infty)]}{\omega_d}$
<p style="text-align: center;">Auxiliary Relations</p> <div style="display: flex; justify-content: space-around;"> <div style="text-align: left;"> $\alpha = \begin{cases} \frac{R}{2L} & \text{Series RLC} \\ \frac{1}{2RC} & \text{Parallel RLC} \end{cases}$ $s_1 = -\alpha + \sqrt{\alpha^2 - \omega_0^2}$ </div> <div style="text-align: left;"> $\omega_0 = \frac{1}{\sqrt{LC}}$ $\omega_d = \sqrt{\omega_0^2 - \alpha^2}$ $s_2 = -\alpha - \sqrt{\alpha^2 - \omega_0^2}$ </div> </div>	



General Second-Order Circuits

- The principles of the approach to solve the series and parallel forms of RLC circuits can **be applied** to general second-order circuits, by taking the following six steps:
 1. First determine the initial conditions, $x(0)$ and $dx(0)/dt$.
 2. **Applying KVL and KCL**, to find the general second-order differential equation to describe $x(t)$.
 3. **Depending on the roots of C.E. , the form of the general solution (3 cases) of homogeneous equation can be determined.**
 4. We obtain the **particular solution** by observation/calculation, **specially** for a DC/step response

$$x_{p.s.}(t) = x(\infty)$$

5. The total response = general solution + particular solution.

$$X(t) = x_{p.s.}(t) + x_{g.s.}(t)$$

6. Using the initial conditions to determine the constants of $X(t)$.



General solution for second-order circuits for $t \geq 0$.

$x(t)$ = unknown variable (voltage or current)

Differential equation: $x'' + ax' + bx = c$

Initial conditions: $x(0)$ and $x'(0)$

Final condition: $x(\infty) = \frac{c}{b}$

$$\alpha = \frac{a}{2} \quad \omega_0 = \sqrt{b}$$

Overdamped Response $\alpha > \omega_0$

$$x(t) = [A_1 e^{s_1 t} + A_2 e^{s_2 t} + x(\infty)]$$

$$s_1 = -\alpha + \sqrt{\alpha^2 - \omega_0^2} \quad s_2 = -\alpha - \sqrt{\alpha^2 - \omega_0^2}$$

$$A_1 = \frac{x'(0) - s_2[x(0) - x(\infty)]}{s_1 - s_2} \quad A_2 = -\left[\frac{x'(0) - s_1[x(0) - x(\infty)]}{s_1 - s_2} \right]$$

Critically Damped $\alpha = \omega_0$

$$x(t) = [(B_1 + B_2 t)e^{-\alpha t} + x(\infty)]$$

$$B_1 = x(0) - x(\infty) \quad B_2 = x'(0) + \alpha[x(0) - x(\infty)]$$

Underdamped $\alpha < \omega_0$

$$x(t) = [D_1 \cos \omega_d t + D_2 \sin \omega_d t] e^{-\alpha t} + x(\infty)$$

$$D_1 = x(0) - x(\infty) \quad D_2 = \frac{x'(0) + \alpha[x(0) - x(\infty)]}{\omega_d}$$

$$\omega_d = \sqrt{\omega_0^2 - \alpha^2}$$



$x(t)$ = unknown variable (voltage or current)

Differential equation:

$$x'' + ax' + bx = c$$

Initial conditions:

$$x(0) \text{ and } x'(0)$$

Final condition:

$$x(\infty) = \frac{c}{h}$$

[Important]

1. This table works well when c is a constant, as $x(\infty)$ is actually a particular solution (特解) of the equation.
2. When c is a function of time (t), such as $c = 5t$; $c = t^2 + 3$; you should also be able to solve the equation (Requirement of the course).





General RLC Circuits

- Find the complete response v for $t > 0$ in the circuit.

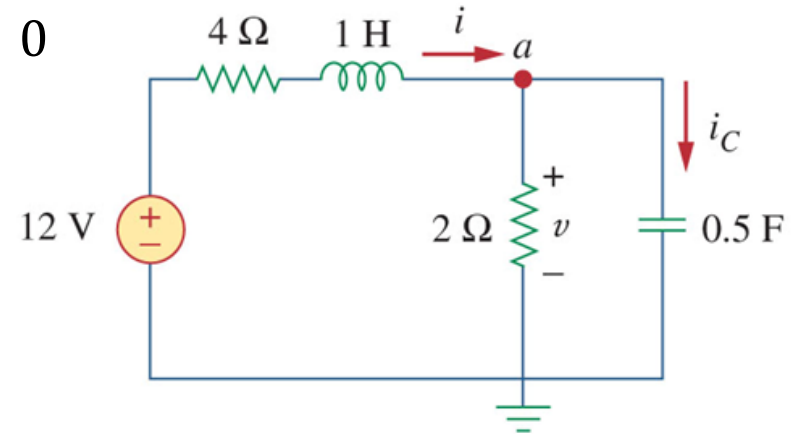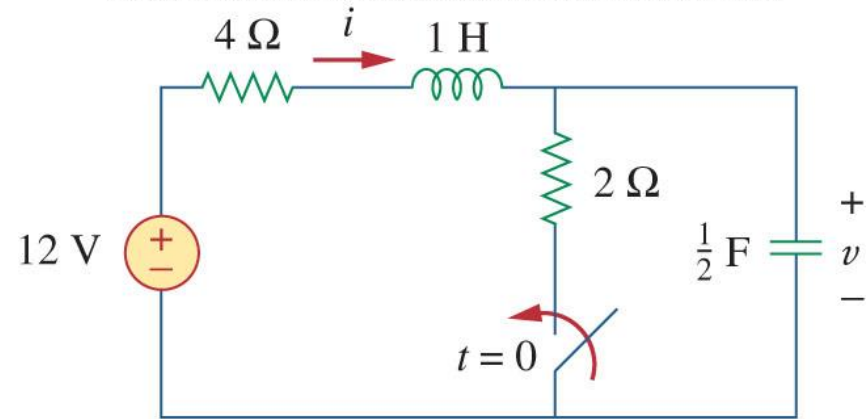1. Initial conditions

$$v(0^+) = v(0^-) = 12V, i(0^+) = i(0^-) = 0$$


$$\frac{dv(0^+)}{dt} = \frac{i_C(0^+)}{C} = \frac{-12/2}{0.5} = -12 V/s$$





General RLC Circuits

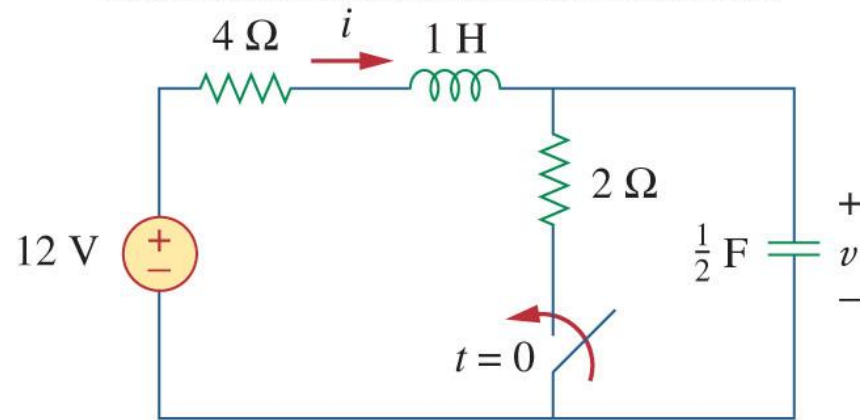- Find the complete response v for $t > 0$ in the circuit.



- Initial conditions

$$v(0^+) = v(0^-) = 12V, i(0^+) = i(0^-) = 0$$

$$\frac{dv(0^+)}{dt} = \frac{i_C(0^+)}{C} = \frac{-12/2}{0.5} = -12 V/s$$

- KCL at node a : $i = \frac{v}{2} + 0.5 \frac{dv}{dt}$

$$\text{KVL on left mesh: } 4i + 1 \frac{di}{dt} + v = 12$$

$$\Rightarrow \frac{d^2v}{dt^2} + 5 \frac{dv}{dt} + 6v = 24 \Rightarrow \text{General Solution } v_t(t) = A_1 e^{-2t} + A_2 e^{-3t}$$

- Particular Solution : Steady-state response $v_{ss}(t) = 4V$

$$\text{4. Put together : } v(t) = 4 + A_1 e^{-2t} - A_2 e^{-3t}$$


$$\text{5. Using initial conditions to determine } A_1, A_2$$



Self-test-General RLC Circuit

- Find the complete response v for $0 < t < 1$ in the circuit.

$$V=12t$$

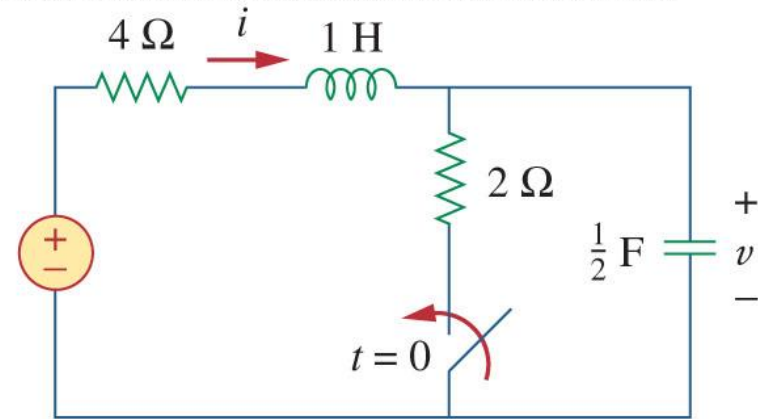

Example of 2nd-order op-amp circuits $C_2 = 100\mu F$

- Find v_o for $t > 0$ when $v_s = 10u(t)mV$.

KCL at node 1:

$$\frac{v_s - v_1}{R_1} = C_2 \frac{dv_2}{dt} + \frac{v_1 - v_o}{R_2}$$


KCL at node 2:

$$C_1 \frac{dv_o}{dt} = \frac{v_1 - v_o}{R_2}$$

and we have $v_1 - v_2 = v_o$


$$\Rightarrow \frac{d^2 v_o}{dt^2} + \left(\frac{1}{R_1 C_2} + \frac{1}{R_2 C_2} \right) \frac{dv_o}{dt} + \frac{v_o}{R_1 R_2 C_1 C_2} = \frac{v_s}{R_1 R_2 C_1 C_2}$$

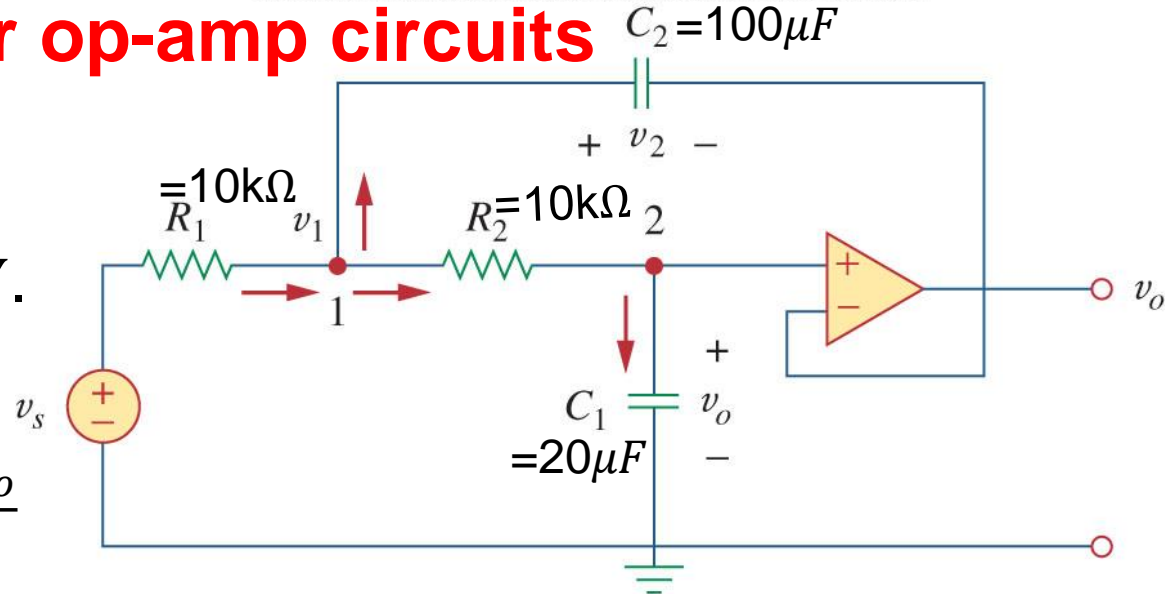Initial conditions: $v_o(0^+) = 0, C_1 \frac{dv_o(0^+)}{dt} = \frac{v_1(0^+) - v_o(0^+)}{R_2} = \frac{v_2(0^+)}{R_2} = 0$






Example---求 $V_{su}(t)$ 状态下 I_L

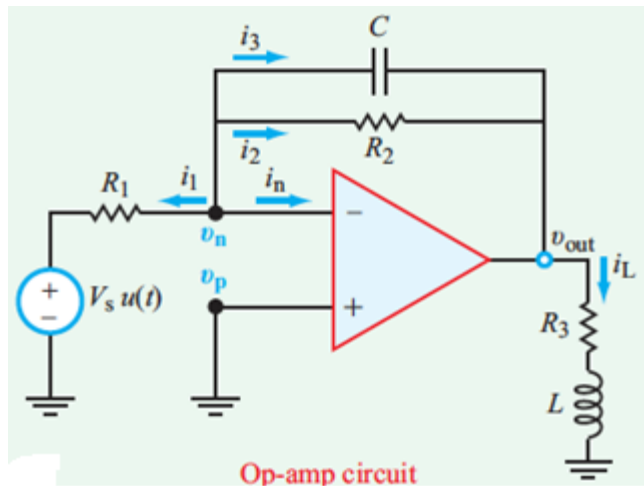



Example

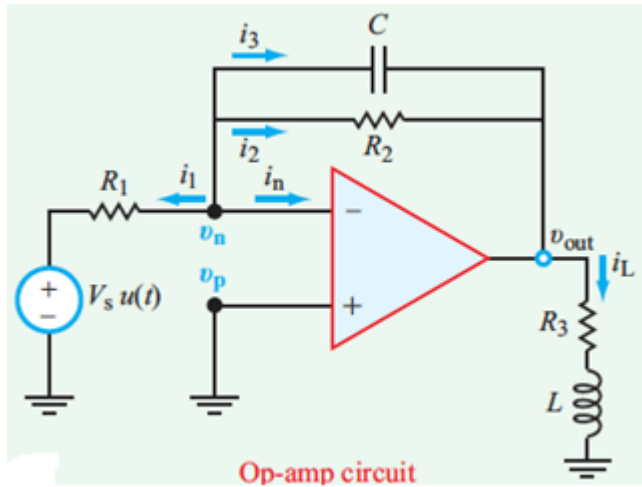

$$i_L(0) = i_L(0^-) = 0, \quad i_L'(0) = \frac{1}{L} v_L(0) = 0.$$

$$\frac{R_3}{R_2} i_L + \left(\frac{L}{R_2} + R_3 C \right) \frac{di_L}{dt} + LC \frac{d^2 i_L}{dt^2} = -\frac{V_s}{R_1}$$