







Lecture 5

- RC/RL First-Order Circuits







Temporal Behavior of Circuit Responses

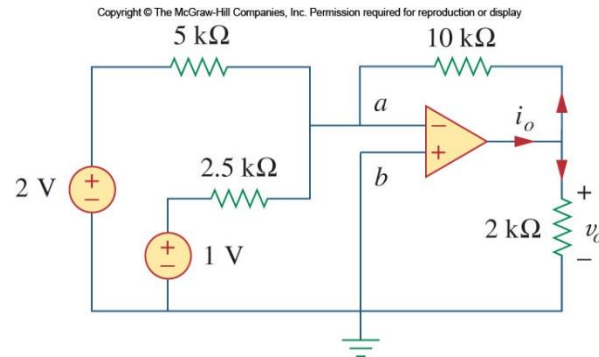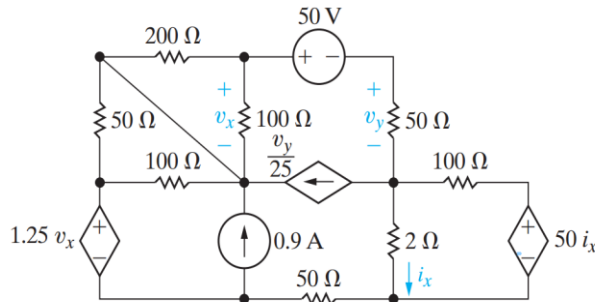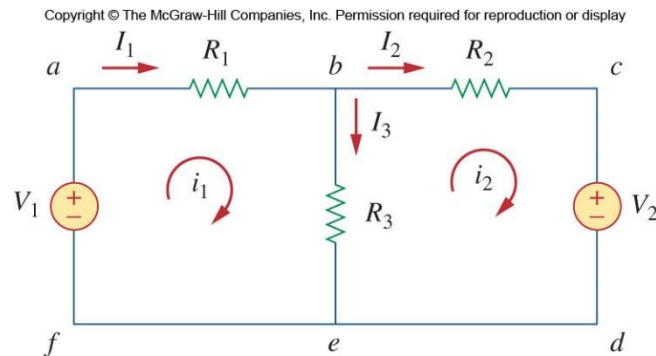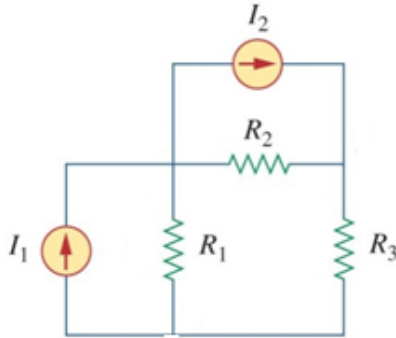- Till now we discussed static analysis of a circuit
 - Responses at a given time depend only on inputs at that time.
 - Circuit responds to input changes infinitely fast.



Temporal Behavior of Circuit Responses

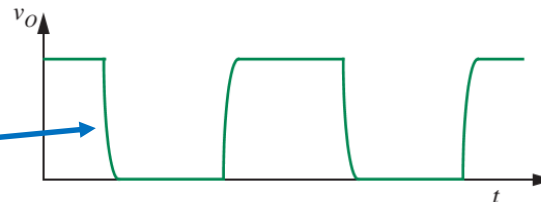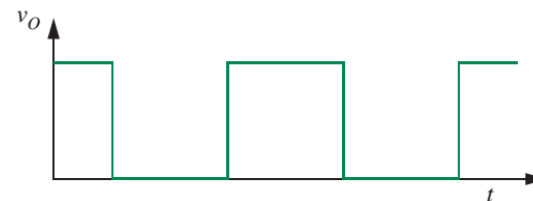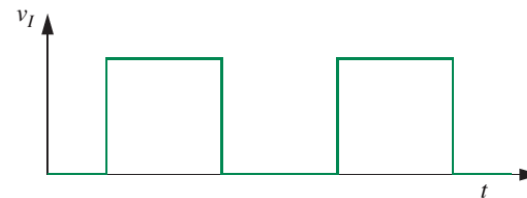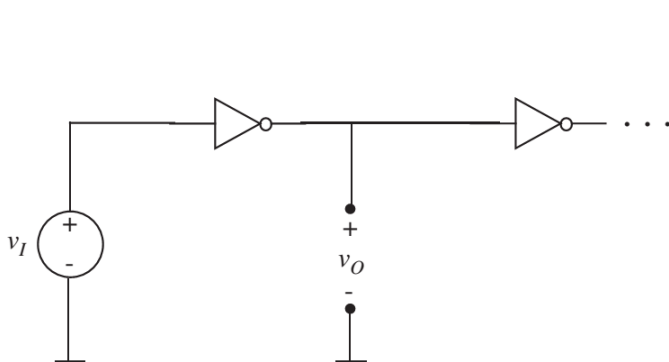- From now on we start to discuss dynamic circuit
 - **Time-varying** sources and responses



We have to introduce capacitors and inductors to explain such temporal behavior.




Outline


- Capacitors and inductors
- Natural response of RC/RL circuits
- Step response of RC/RL circuits

Capacitors

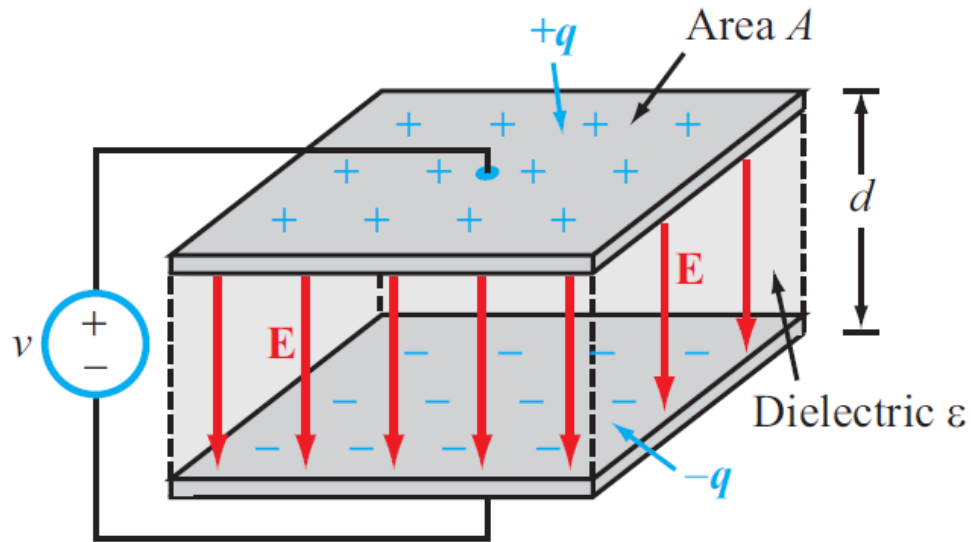Storage element that stores energy in electric field



Parallel plate capacitor

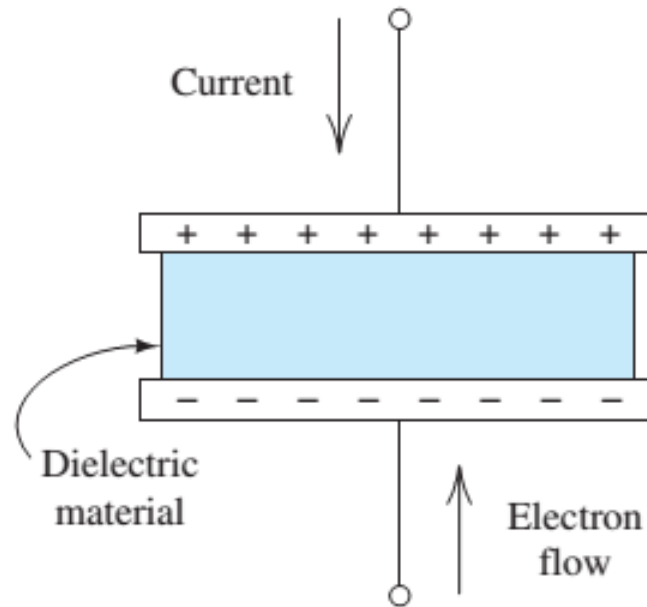



(a) As current flows through a capacitor, charges of opposite signs collect on the respective plates

Does DC voltage generate current flow through a capacitor?

Does AC voltage generate current flow through a capacitor?




V-I Relationship of Capacitors

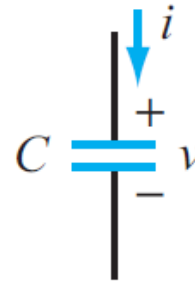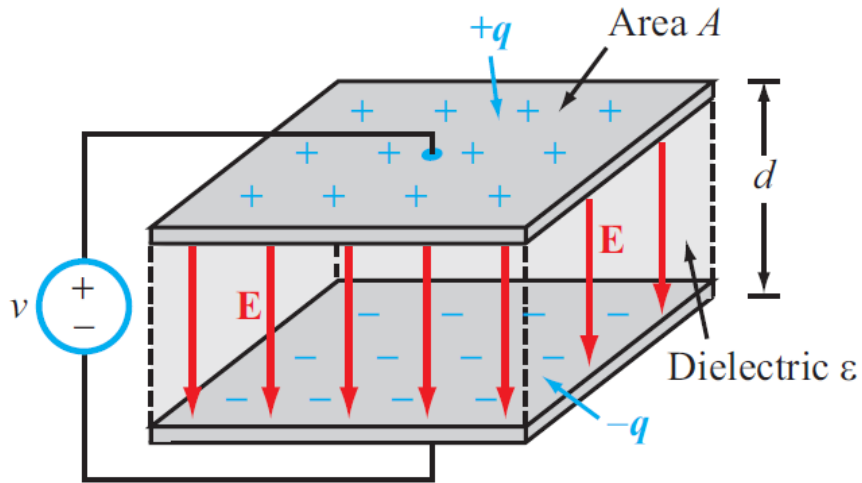




Example

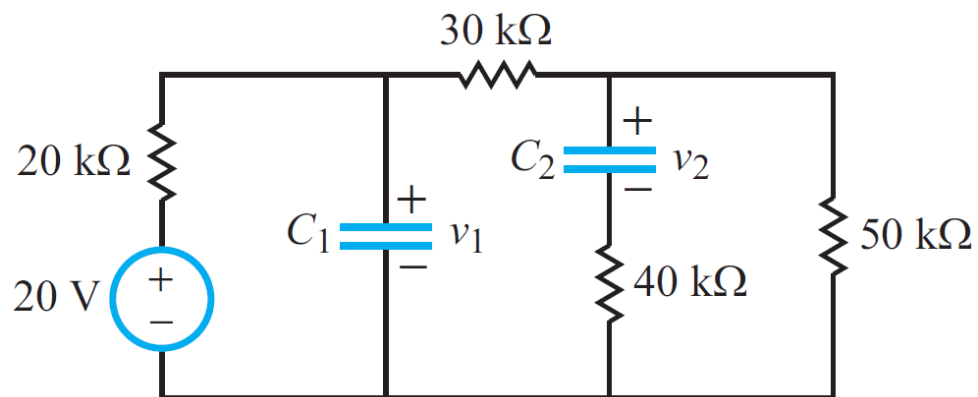



Stored Energy





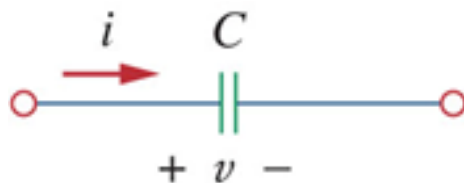


$$i = C \frac{dv}{dt}$$



- The instantaneous power delivered to the capacitor is
- The energy stored in a capacitor is:



Capacitor Response

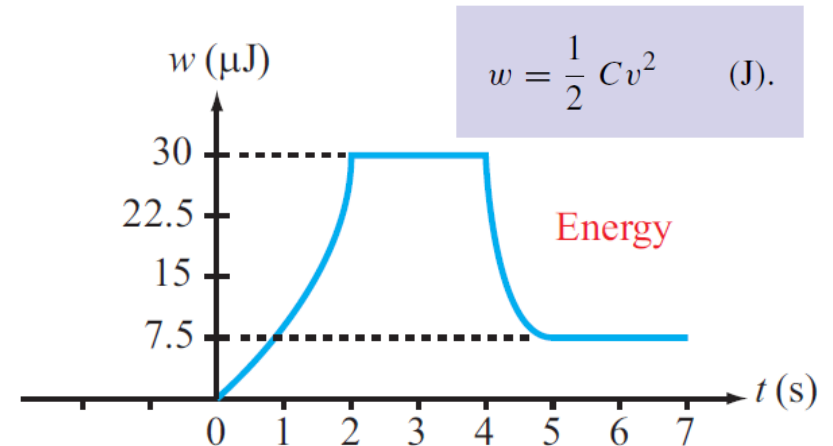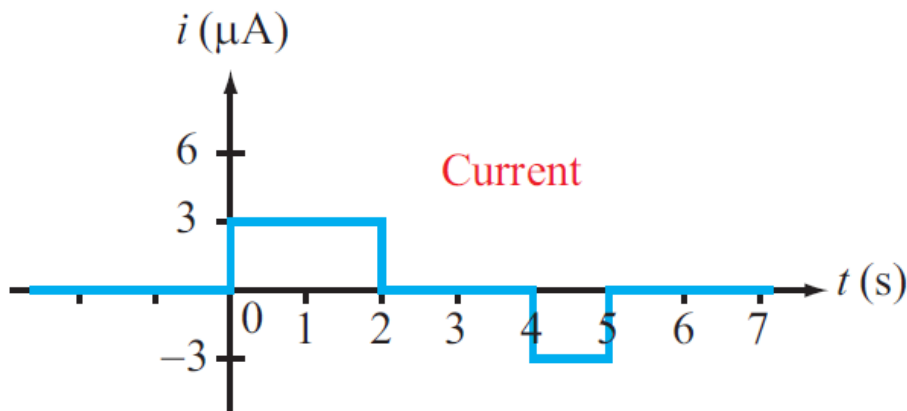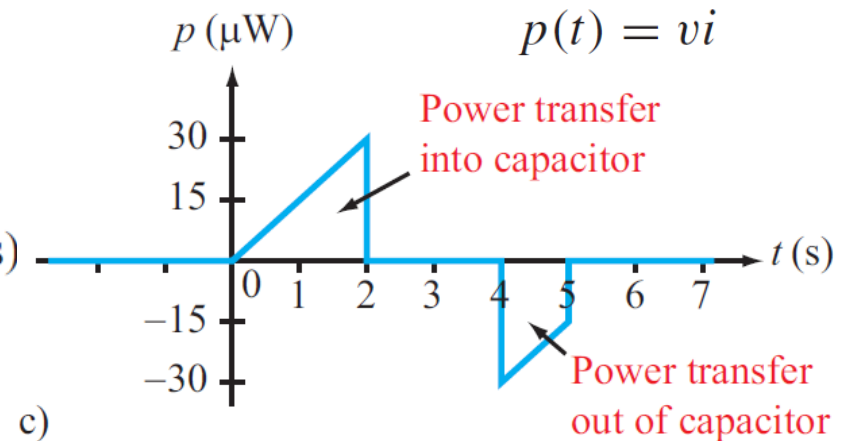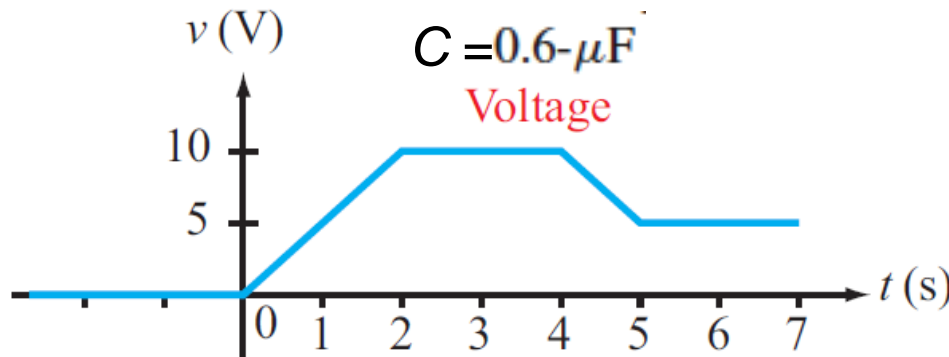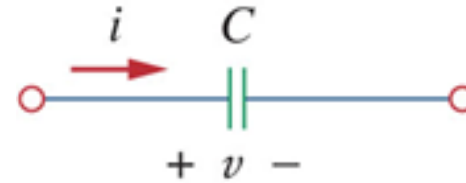


Important Property of Capacitors

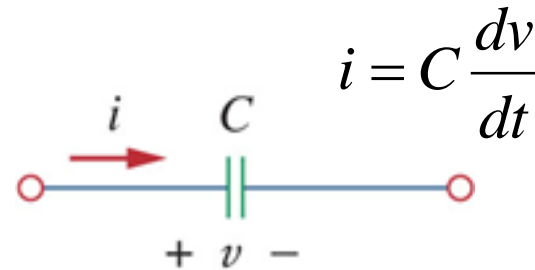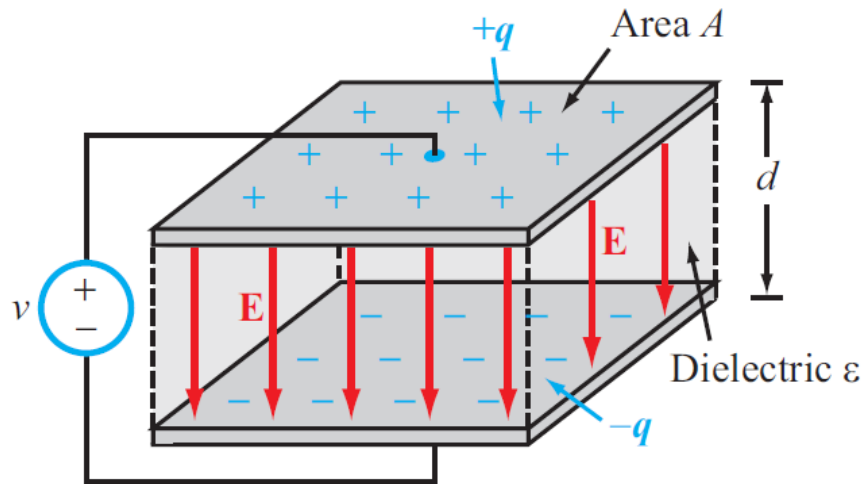


$$i = C \frac{dv}{dt}$$

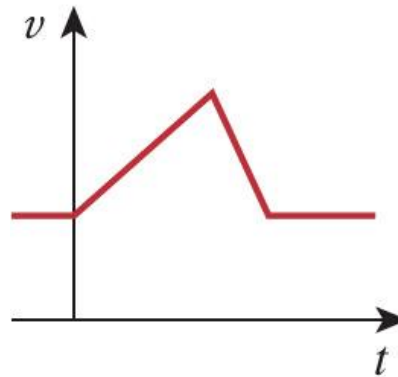Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display



(a)


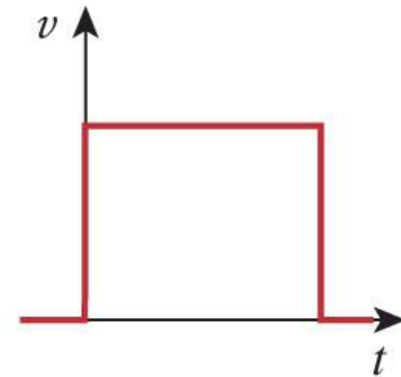


(b)





Capacitors in Series

Combining In-Series Capacitors

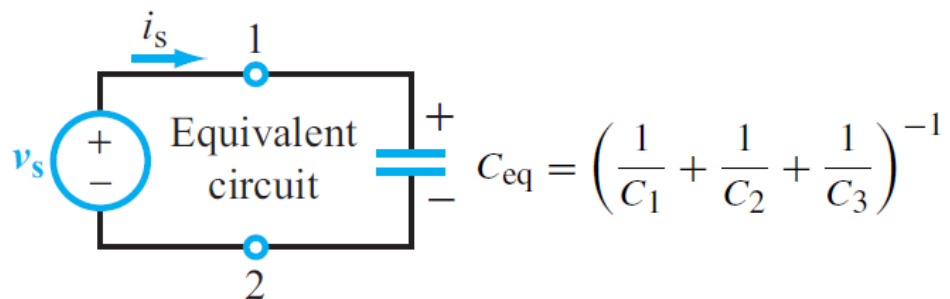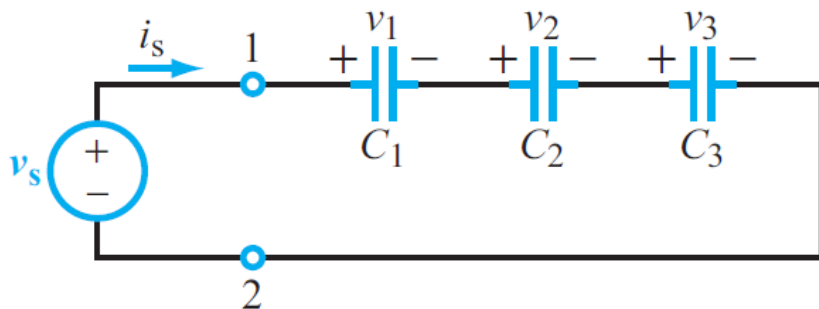




Capacitors in Parallel

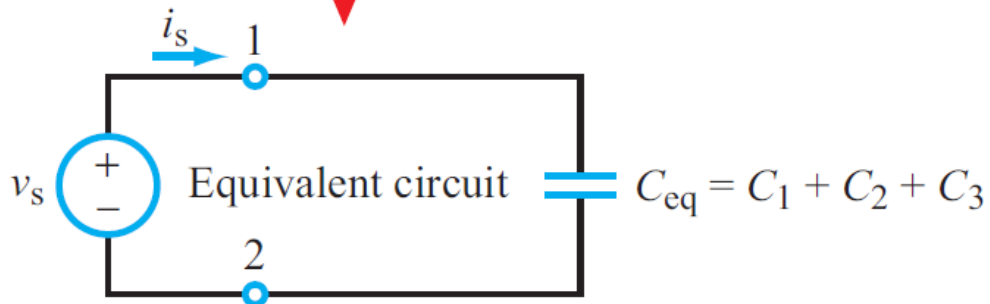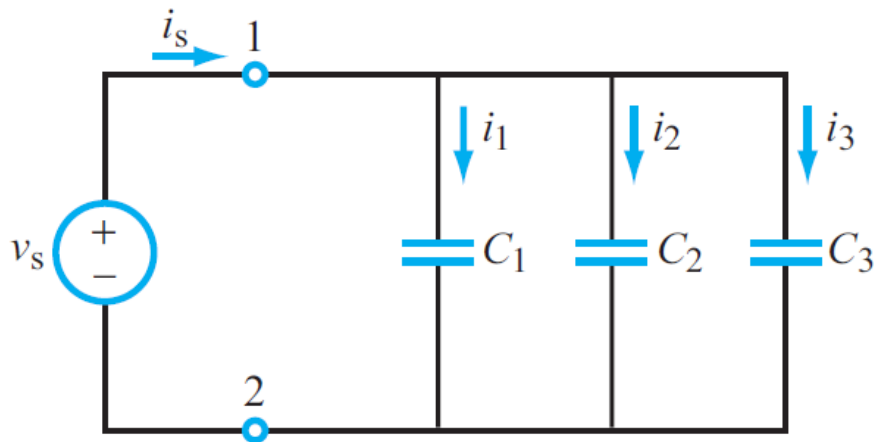



Voltage Division

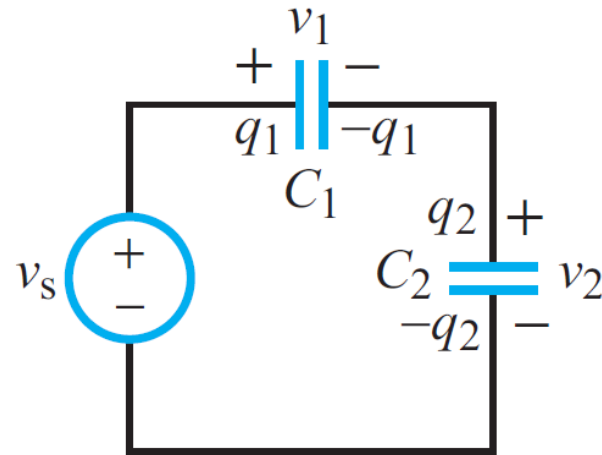


$$v_1 = \left(\frac{C_2}{C_1 + C_2} \right) v_s$$


$$v_2 = \left(\frac{C_1}{C_1 + C_2} \right) v_s$$

Inductors

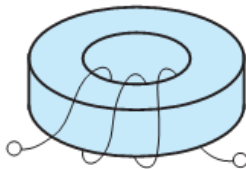
- A storage element that stores energy in magnetic field.
 - They have applications in power supplies, transformers, radios, TVs, radars, and electric motors.
- Any conductor has inductance, but the effect is typically enhanced by coiling the wire up.



(a) Toroidal inductor

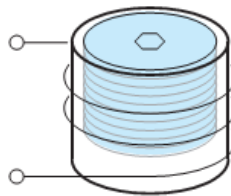

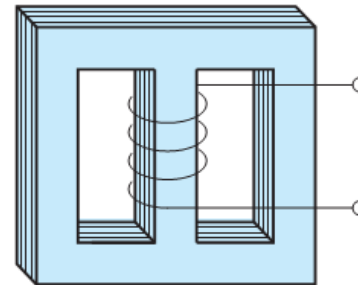(b) Coil with an iron-oxide slug that can be screwed in or out to adjust the inductance





(c) Inductor with a laminated iron core

$$L = \frac{N^2 \mu S}{l}$$



V-I Relationship of Inductors

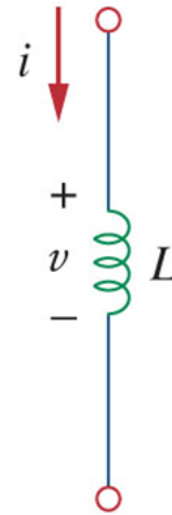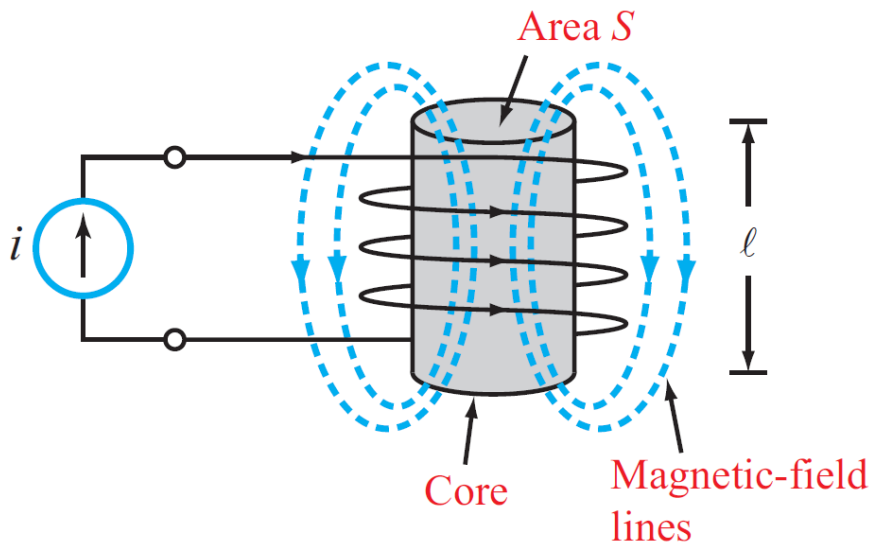


$$v = L \frac{di}{dt}$$



Energy Stored in an Inductor

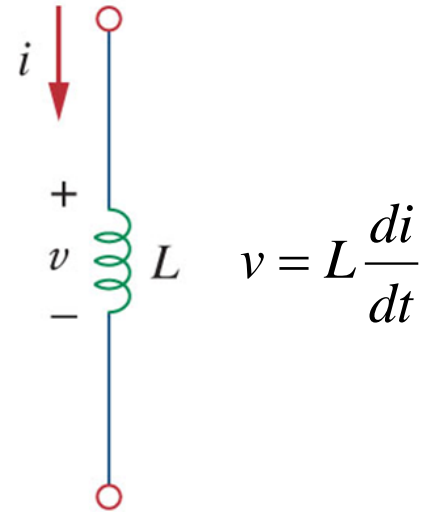
- The power delivered to the inductor is:
- The energy stored is:






Inductor Response
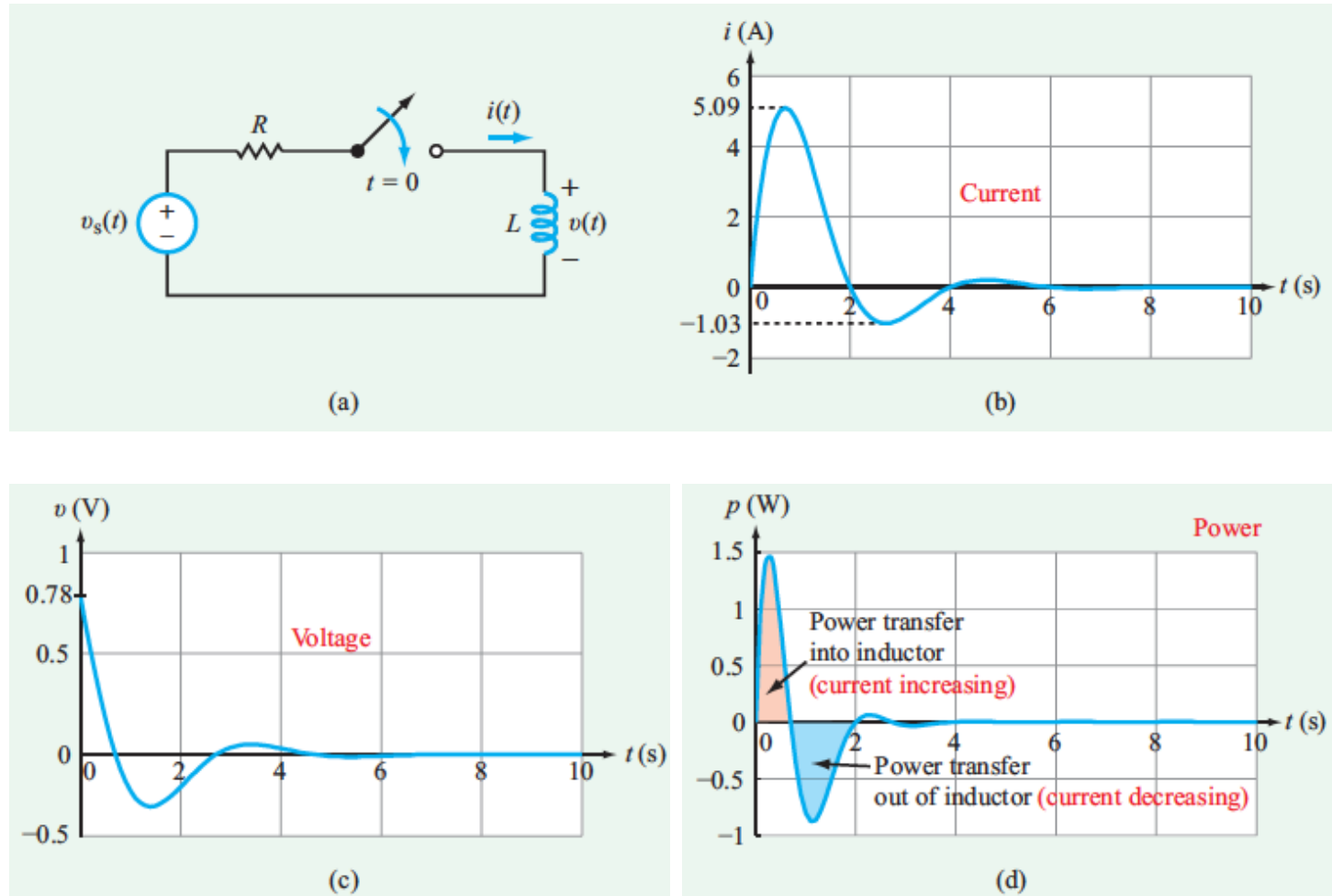
$$i(t) = 10e^{-0.8t} \sin(\pi t/2) \text{ A}, \quad (\text{for } t \geq 0)$$







Important Property of Inductors

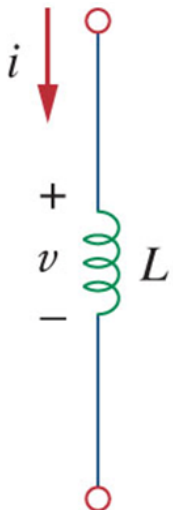



$$v = L \frac{di}{dt}$$

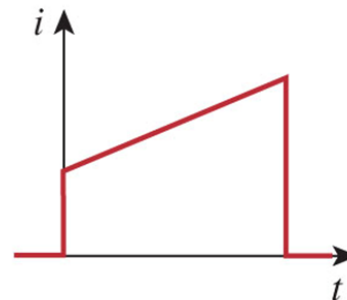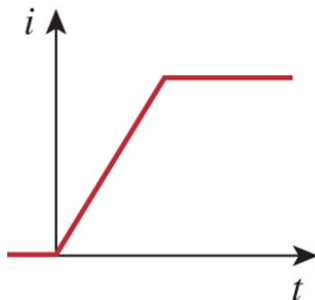Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display







Inductors in Series

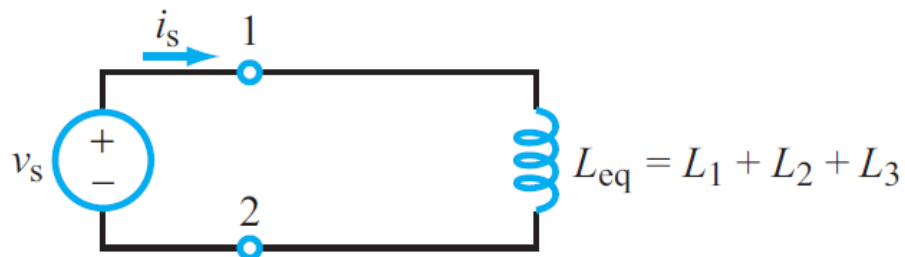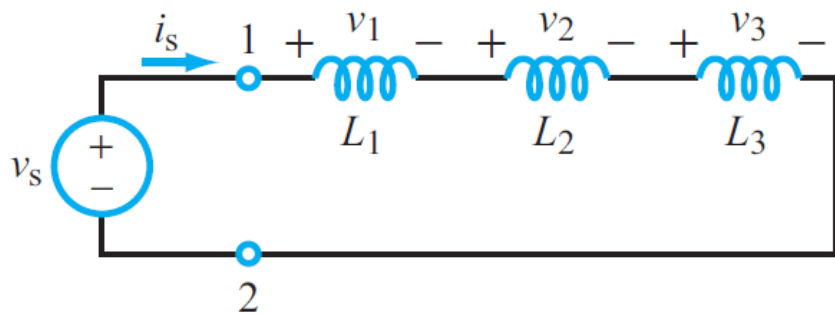





Inductors in Parallel

Combining In-Parallel Inductors

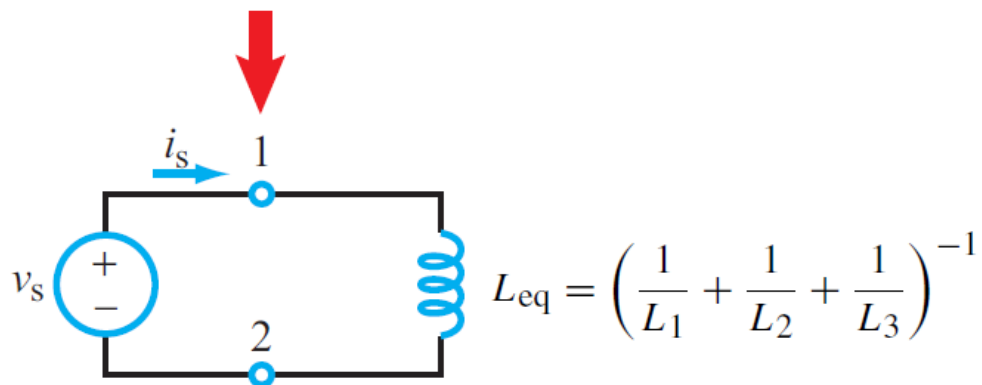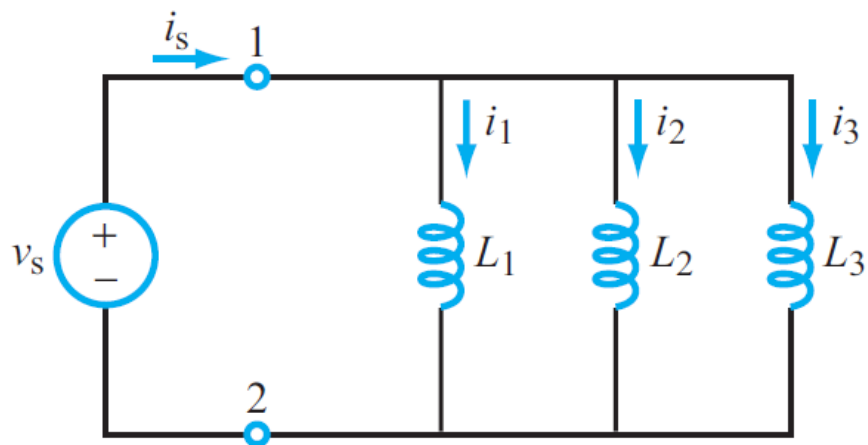



Example

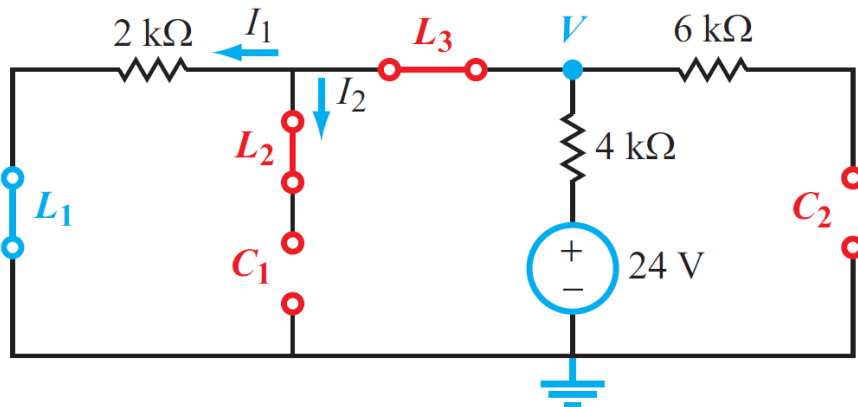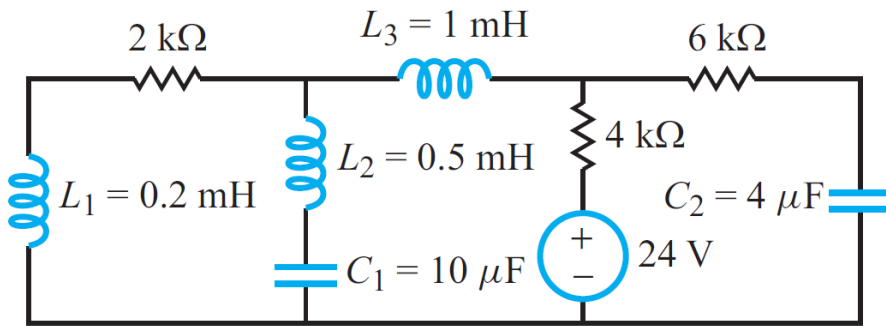



Summary of Capacitors and Inductors

Table 5-4: Basic properties of R , L , and C .

Property	R	L	C
i - v relation	$i = \frac{v}{R}$	$i = \frac{1}{L} \int_{t_0}^t v dt' + i(t_0)$	$i = C \frac{dv}{dt}$
v - i relation	$v = iR$	$v = L \frac{di}{dt}$	$v = \frac{1}{C} \int_{t_0}^t i dt' + v(t_0)$
p (power transfer in)	$p = i^2 R$	$p = Li \frac{di}{dt}$	$p = Cv \frac{dv}{dt}$
w (stored energy)	0	$w = \frac{1}{2} Li^2$	$w = \frac{1}{2} Cv^2$
Series combination	$R_{eq} = R_1 + R_2$	$L_{eq} = L_1 + L_2$	$\frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2}$
Parallel combination	$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2}$	$\frac{1}{L_{eq}} = \frac{1}{L_1} + \frac{1}{L_2}$	$C_{eq} = C_1 + C_2$
dc behavior	no change	short circuit	open circuit
Can v change instantaneously?	yes	yes	no
Can i change instantaneously?	yes	no	yes





Outline

- Capacitors and inductors
- Natural response of RC/RL circuits
- Step response of RC/RL circuits

RC and RL Circuits

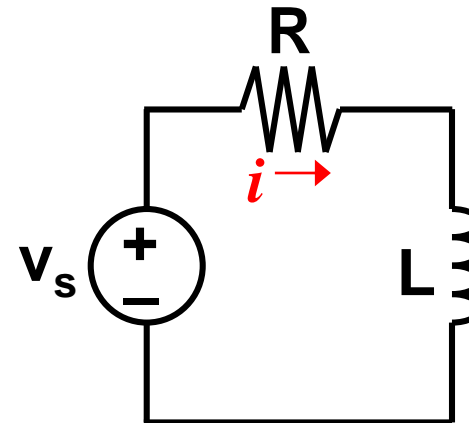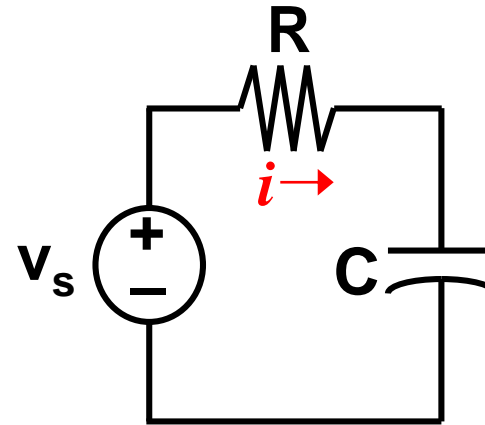
- A circuit that contains only sources, resistors and a capacitor is called an **RC circuit**.
- A circuit that contains only sources, resistors and an inductor is called an **RL circuit**.






RC and RL Circuits

RC Circuit

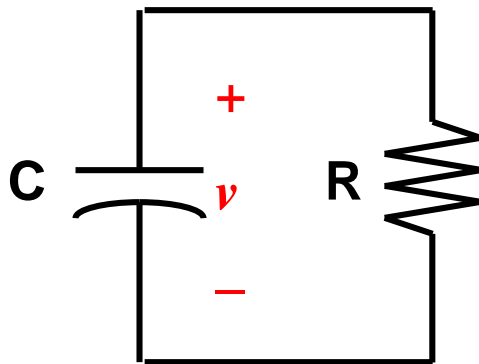

- Capacitor voltage cannot change instantaneously
- In steady state, a capacitor behaves like an open circuit


RL Circuit

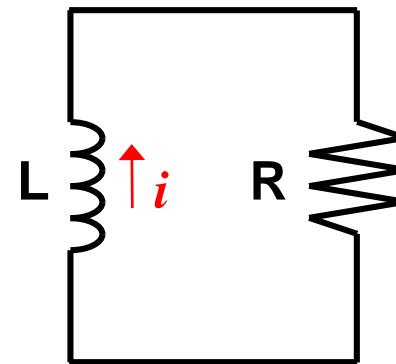


- Inductor current cannot change instantaneously
- In steady state, an inductor behaves like a short circuit.

Natural Response of a Charged Capacitor

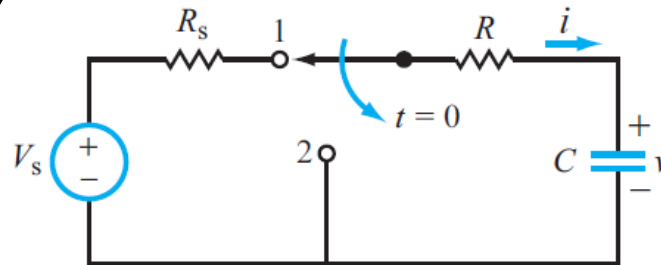
Behavior (*i.e.*, current and voltage) when stored energy in the inductor or capacitor is released to the resistive part of the network (containing no independent sources).



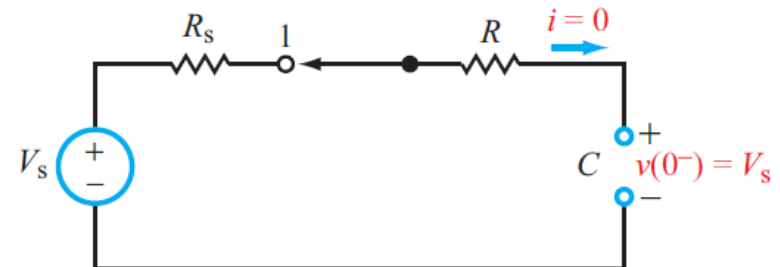(a) $t = 0^-$ is the instant just before the switch is moved from terminal 1 to terminal 2;




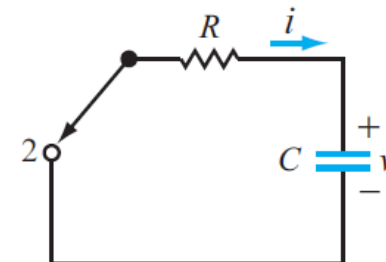(b) $t = 0$ is the instant just after it was moved, $t = 0$ is synonymous with $t = 0^+$.






Natural Response of a Charged Capacitor


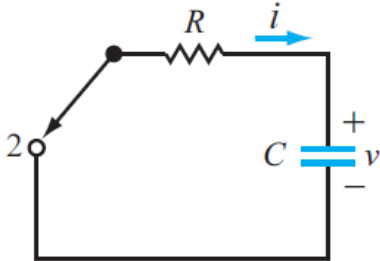




Natural Response of RC

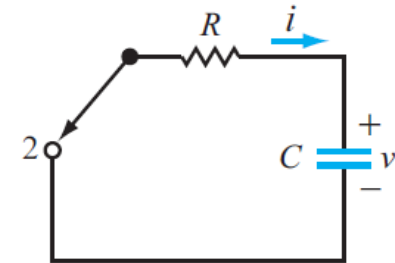


Time constant: $\tau = RC$

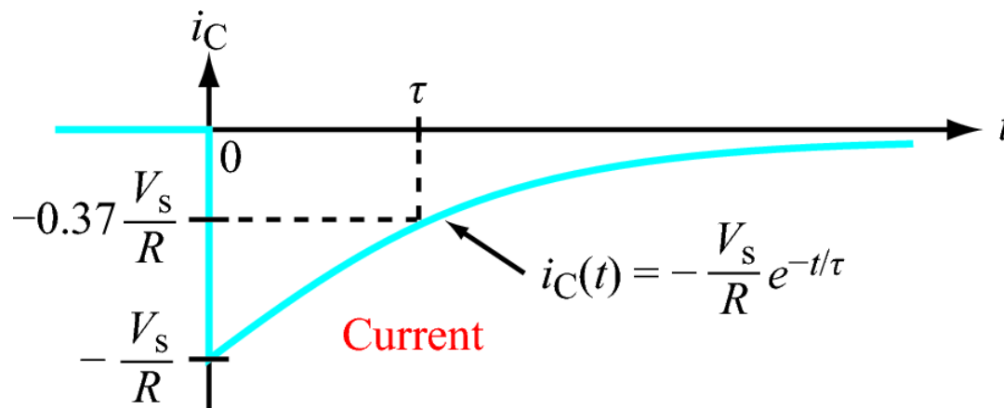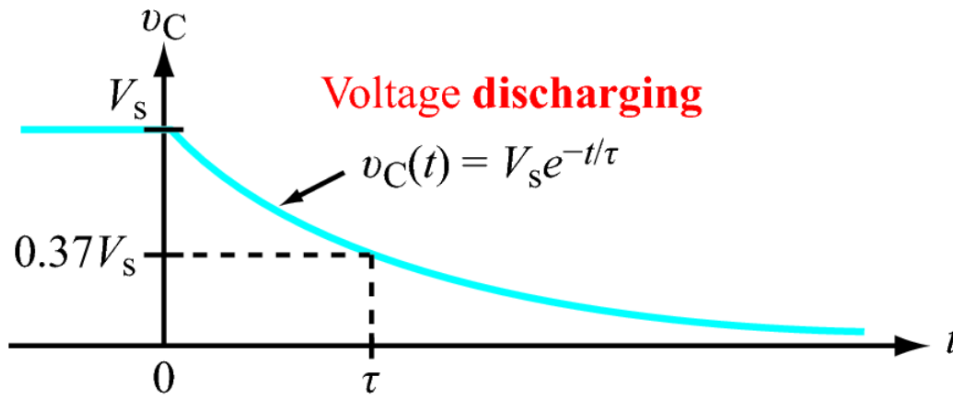

Time Constant $\tau (= RC)$

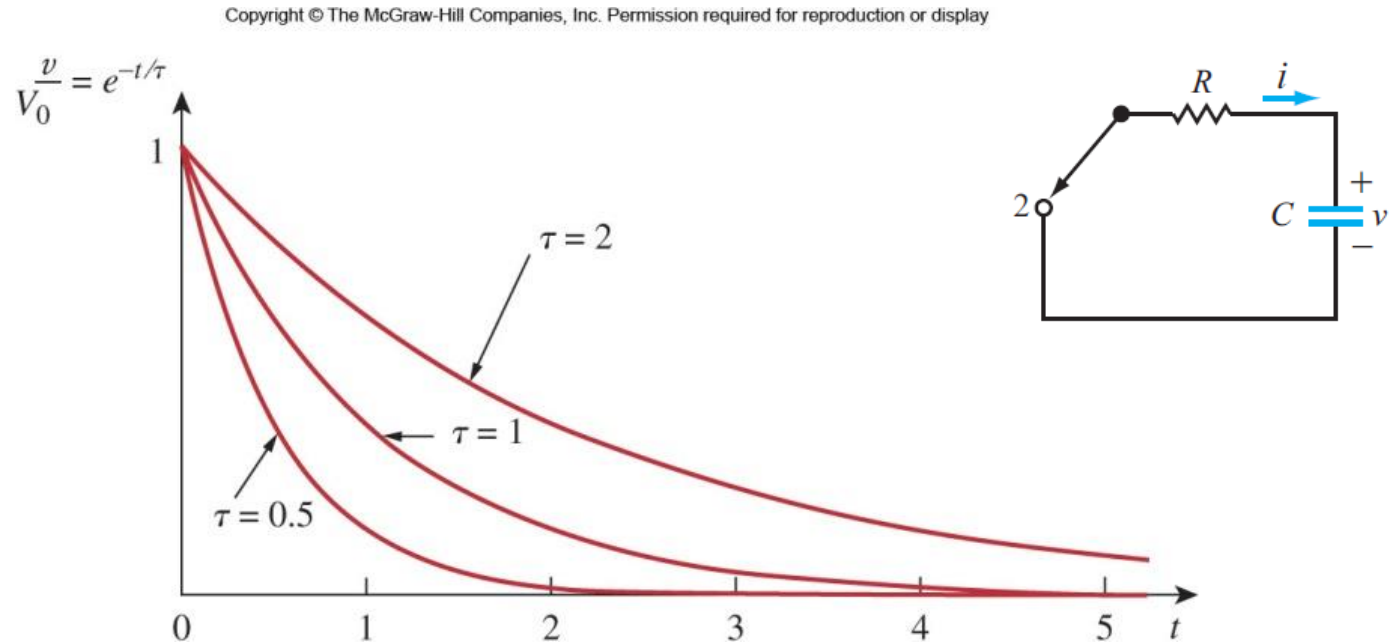- A circuit with a small time constant has a fast response and vice versa.






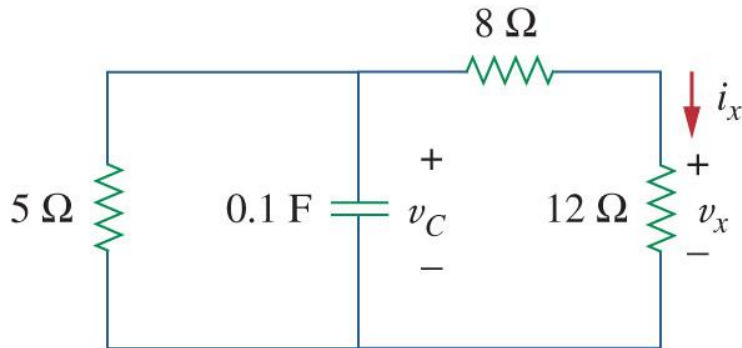Example




- In the circuit below, let $v_C(0) = 15\text{V}$. Find v_C , v_x , and i_x for $t > 0$.

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display






Natural Response of the RL Circuit

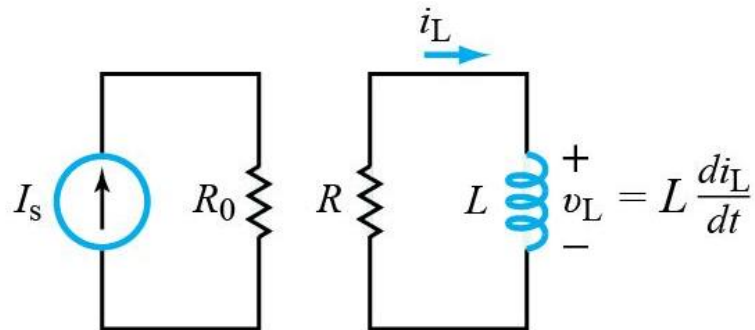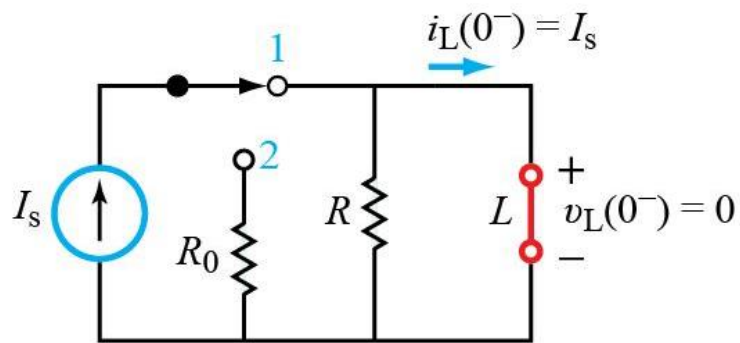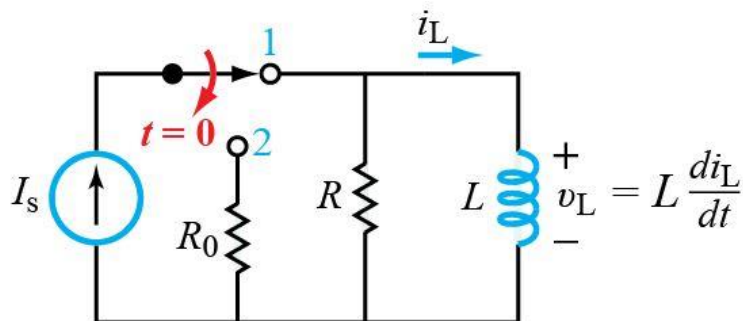




Natural Response of the RL Circuit

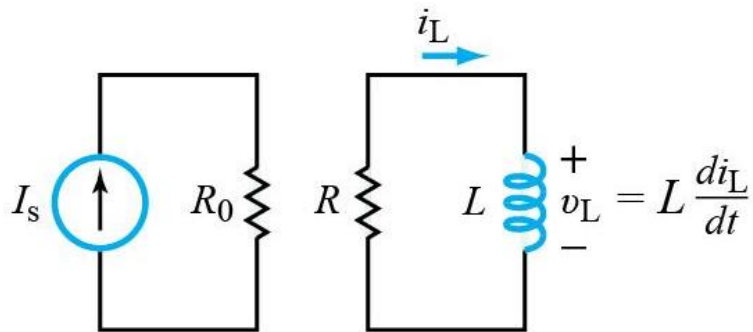



Natural Response of the RL Circuit

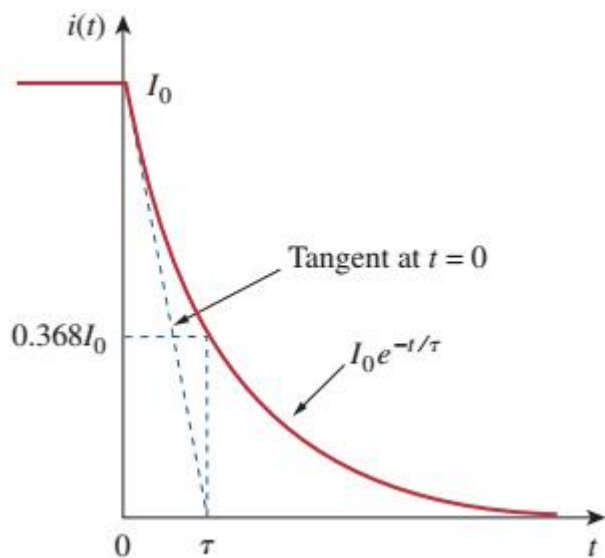




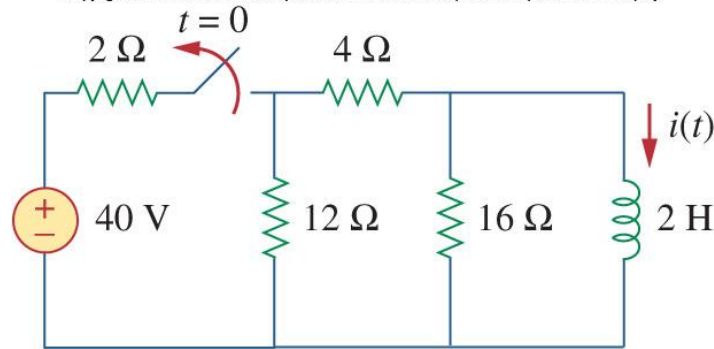
Example

- The switch in the circuit below has been closed for a long time. At $t = 0$, the switch is opened. Calculate $i(t)$ for $t > 0$.


Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display



When $t < 0$

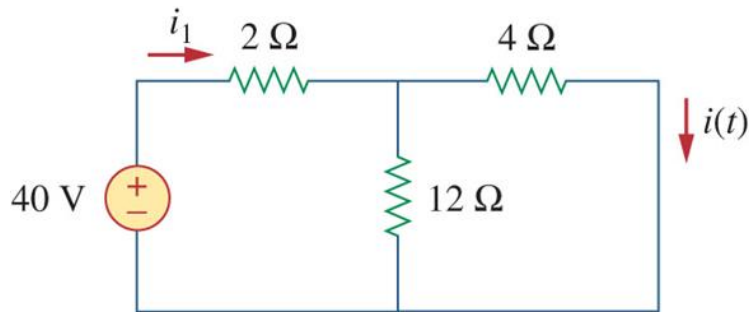


When $t > 0$

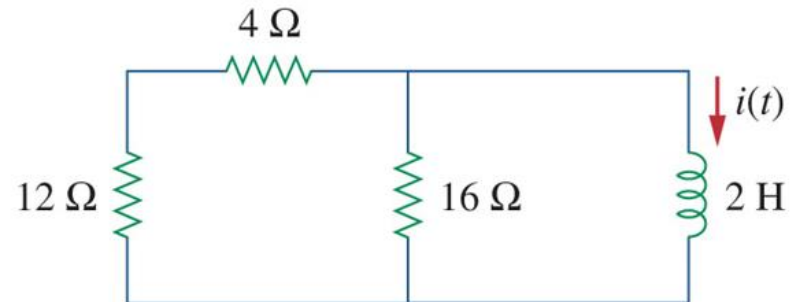

Natural Response Summary

RC Circuit

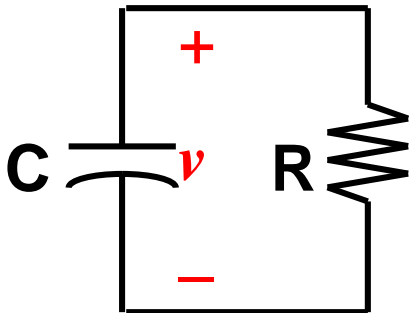


- **Capacitor voltage** cannot change instantaneously

$$v(0^-) = v(0^+)$$

$$v(t) = v(0)e^{-t/\tau}$$

- time constant $\tau = RC$

RL Circuit

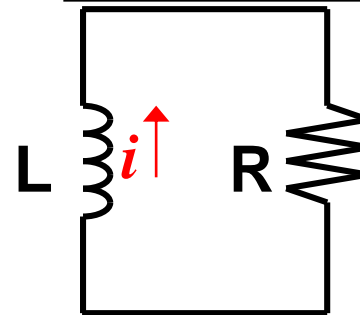

- **Inductor current** cannot change instantaneously

$$i(0^-) = i(0^+)$$

$$i(t) = i(0)e^{-t/\tau}$$

- time constant $\tau = \frac{L}{R}$




Outline

- Capacitors and inductors
- Natural response of RC/RL circuits
- Step response of RC/RL circuits

Step Response of RC Circuit

- When a DC source is suddenly applied to a RC circuit, the circuit response is known as the step response.

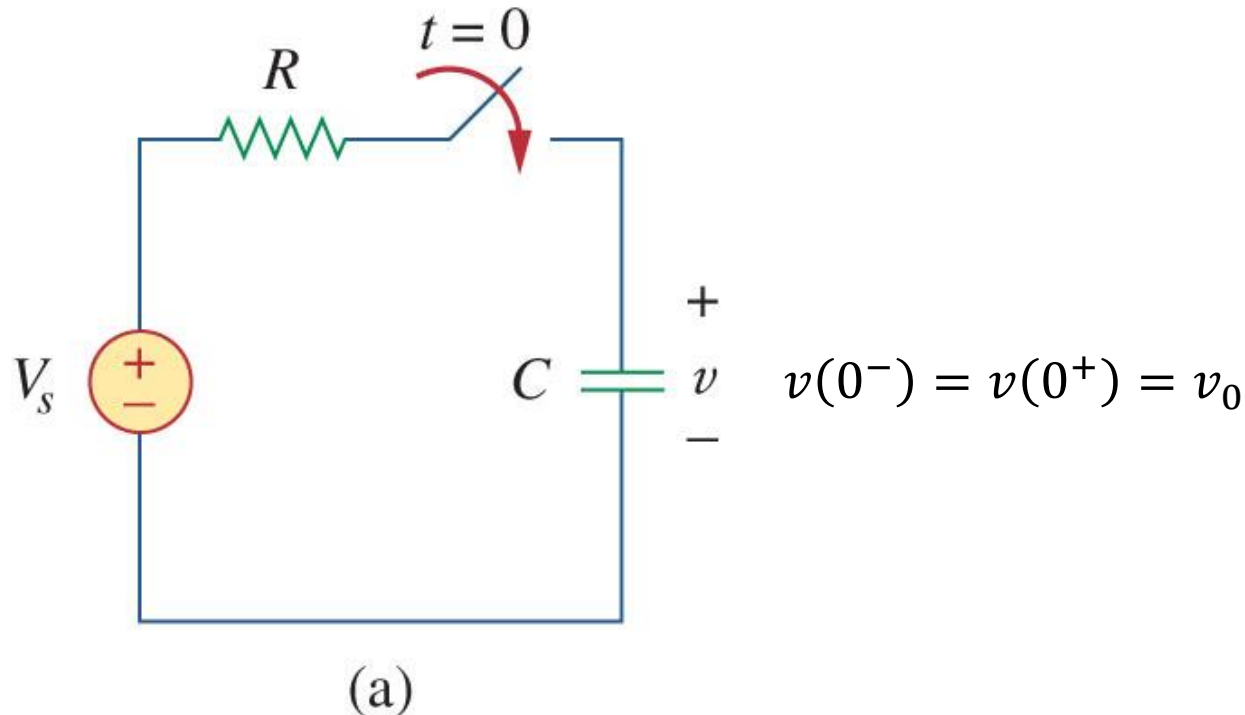
Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display





Step Response of the RC Circuit

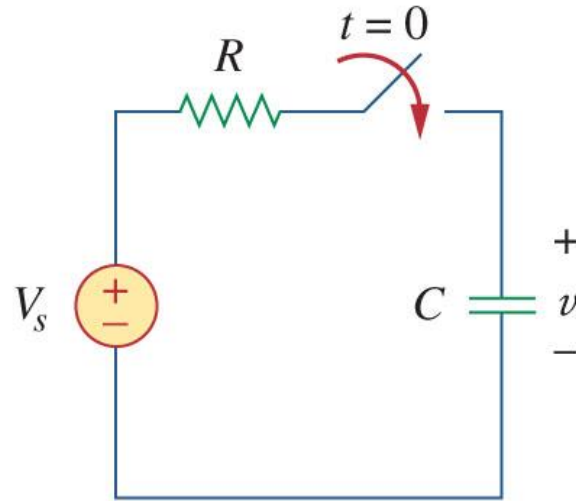Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display




$$v(0^-) = v(0^+) = v_0$$





Step Response of the RC Circuit

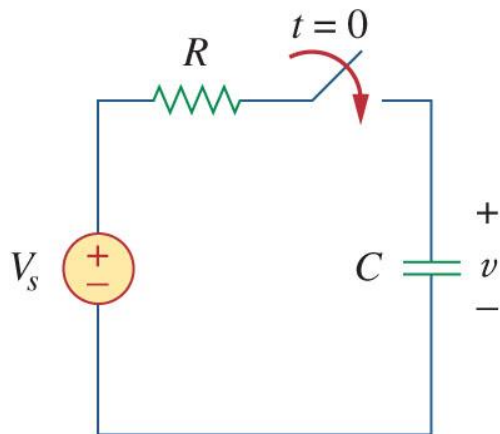
Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display



$$v(0^-) = v(0^+) = v_0$$

$$v(t) = \begin{cases} V_0, & t < 0 \\ V_s + (V_0 - V_s)e^{-t/\tau} & t > 0 \end{cases}$$

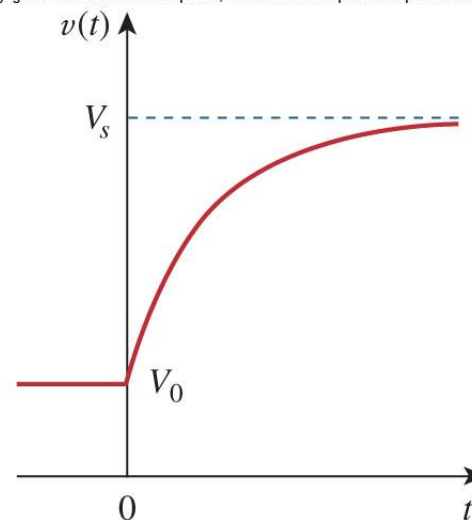Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display




- This is known as the complete response, or total response.



Forced Response

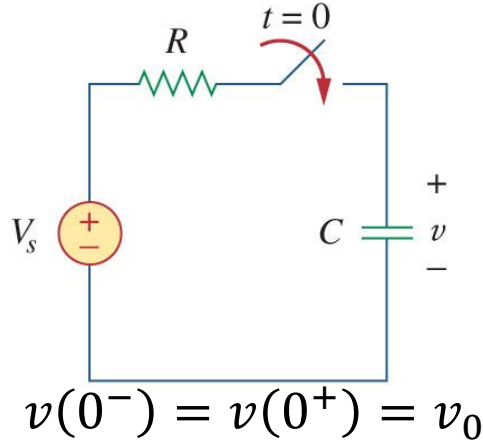Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display




- The complete response

$$v(t) = \begin{cases} V_0, & t < 0 \\ V_s + (V_0 - V_s)e^{-t/\tau} & t > 0 \end{cases}$$

can be written as:

$$v = v_n + v_f$$

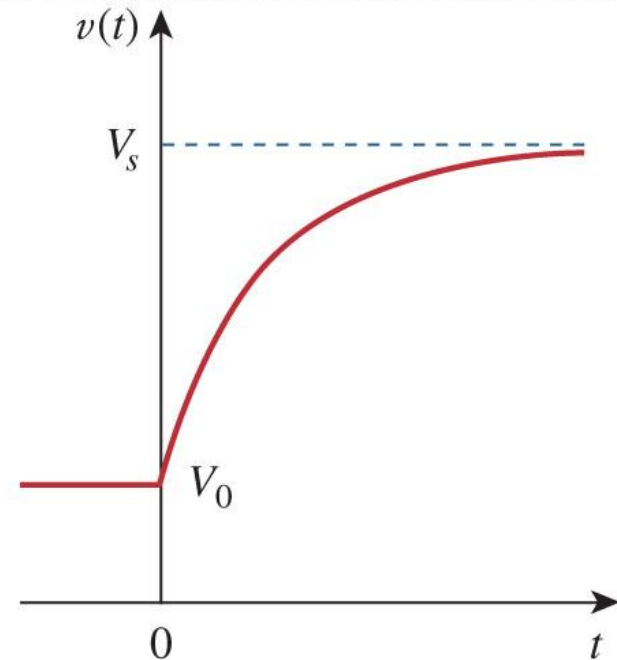Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display





$$\text{Complete response} = \underset{\text{stored energy}}{\text{natural response}} + \underset{\text{independent source}}{\text{forced response}}$$

or

$$v = v_n + v_f$$

where


$$v_n = V_o e^{-t/\tau}$$

and

$$v_f = V_s(1 - e^{-t/\tau})$$

Another Perspective
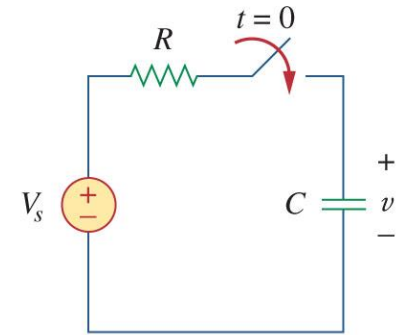
$$v(t) = \begin{cases} V_0, & t < 0 \\ V_s + (V_0 - V_s)e^{-t/\tau} & t > 0 \end{cases}$$




- Another way to look at the response is to break it up into the transient response and the steady state response:

$$v(t) = \underbrace{v(\infty)}_{\text{steady } v_{ss}} + \underbrace{[v(0) - v(\infty)]e^{-t/\tau}}_{\text{transient } v_t}$$



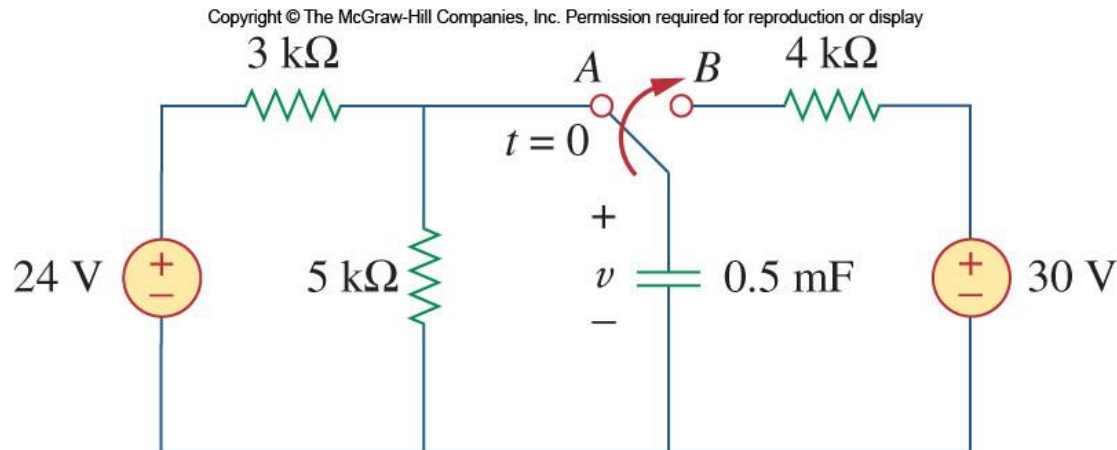Example


- The switch has been in position A for a long time. At $t = 0$, the switch moves to B. Find $v(t)$.





Step Response of the RL Circuit

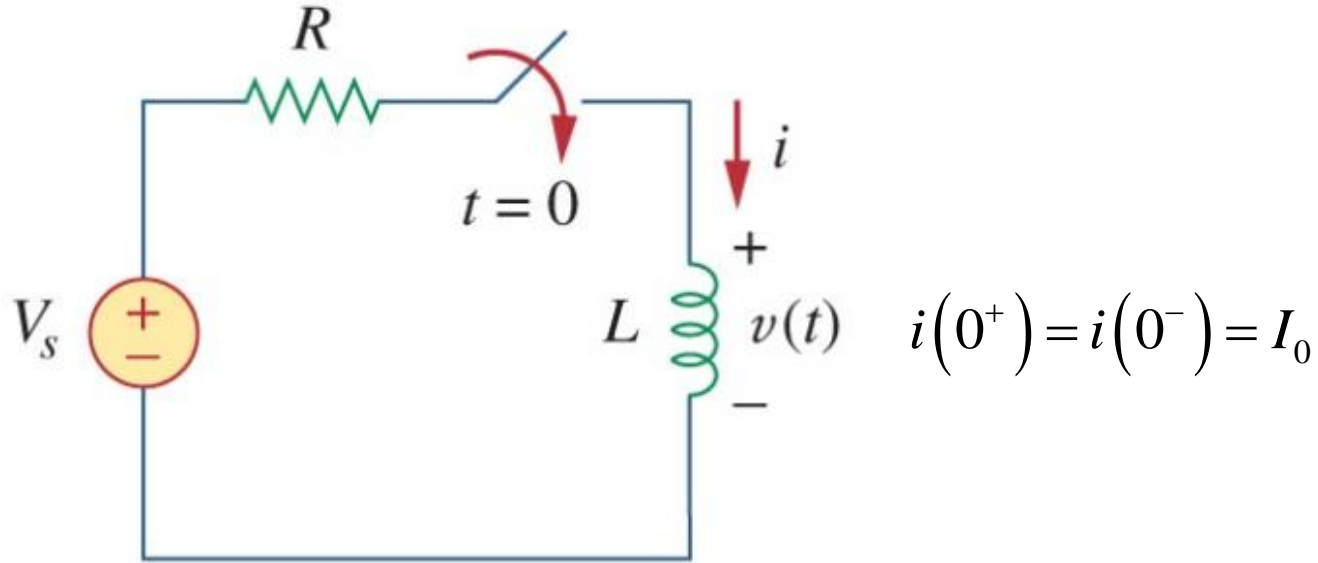Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display



Step Response of the RL Circuit



- We will use the transient and steady state response approach.
- We know that the transient response will be an exponential:

$$i_t = Ae^{-t/\tau}$$

- After a sufficiently long time, the current will reach the steady state:

$$i_{ss} = \frac{V_s}{R}$$

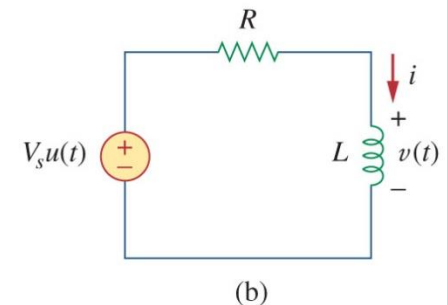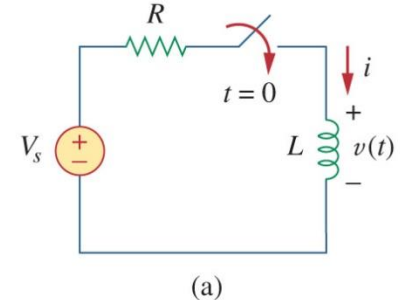
Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display



Step Response of RL Circuit

- This yields an overall response of:

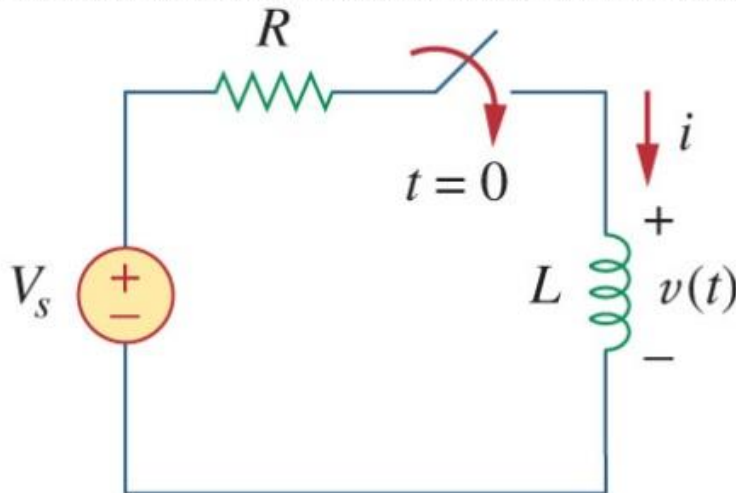Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display



$$i = Ae^{-t/\tau} + \frac{V_s}{R}$$

$$i(0^+) = i(0^-) = I_0 \quad A = I_0 - \frac{V_s}{R}$$

$$i(t) = \frac{V_s}{R} + \left(I_0 - \frac{V_s}{R} \right) e^{-t/\tau}$$



Response of a Circuit

- **Circuit (dynamic) response**

- the reaction of a certain voltage or current in the circuit to change, such as the adding of a new source, the elimination of a source, in the circuit configuration.

- **Transient response**

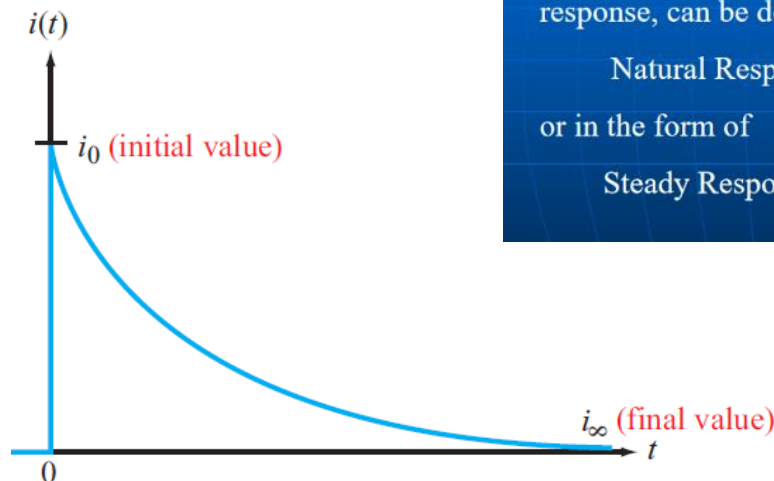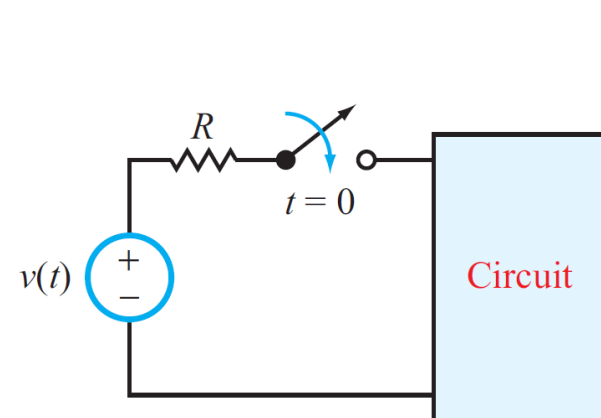- Behavior when voltage or current source are **suddenly** applied to or removed from the circuit due to switching.
- Temporary behavior



The solution of a linear circuit, called dynamic response, can be decomposed into

Natural Response + Forced Response

or in the form of


Steady Response + Transient Response



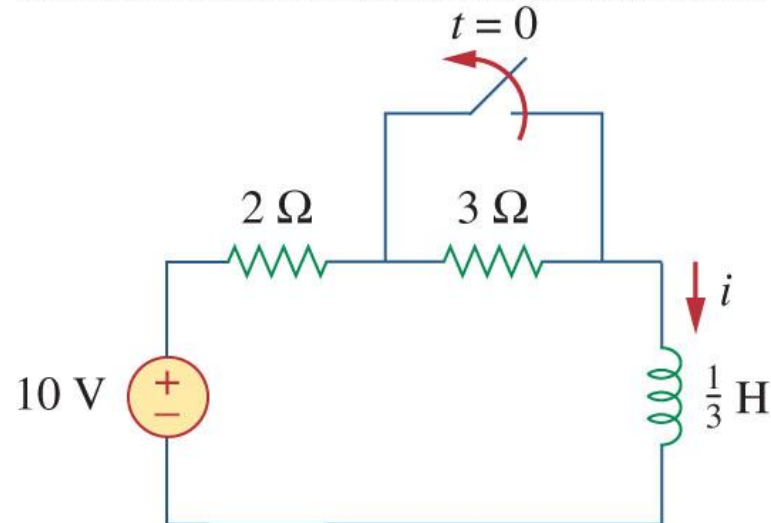Example

- Find $i(t)$ in the circuit for $t > 0$. Assume that the switch has been closed for a long time.

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display





General Procedure for Finding RC/RL Response

1. Identify the variable of interest

- For RL circuits, it is usually the inductor current $i_L(t)$.
- For RC circuits, it is usually the capacitor voltage $v_c(t)$.

2. Determine the initial value (at $t = t_0^-$ and t_0^+) of the variable

- Recall that $i_L(t)$ and $v_c(t)$ are continuous variables:

$$i_L(t_0^+) = i_L(t_0^-) \quad \text{and} \quad v_c(t_0^+) = v_c(t_0^-)$$

- Assuming that the circuit reached steady state before t_0 : use the fact that **an inductor behaves like a short circuit in steady state** or that **a capacitor behaves like an open circuit in steady state**.



Procedure (cont'd)

3. Calculate the final value of the variable (as $t \rightarrow \infty$)

- Again, make use of the fact that **an inductor behaves like a short circuit in steady state ($t \rightarrow \infty$)** or that **a capacitor behaves like an open circuit in steady state ($t \rightarrow \infty$)**.


4. Calculate the time constant for the circuit

- **$\tau = CR$ for an RC circuit** where **R** is the Thévenin equivalent resistance “seen” by the capacitor.
- **$\tau = L/R$ for an RL circuit**, where **R** is the Thévenin equivalent resistance “seen” by the inductor.



Sequential switch

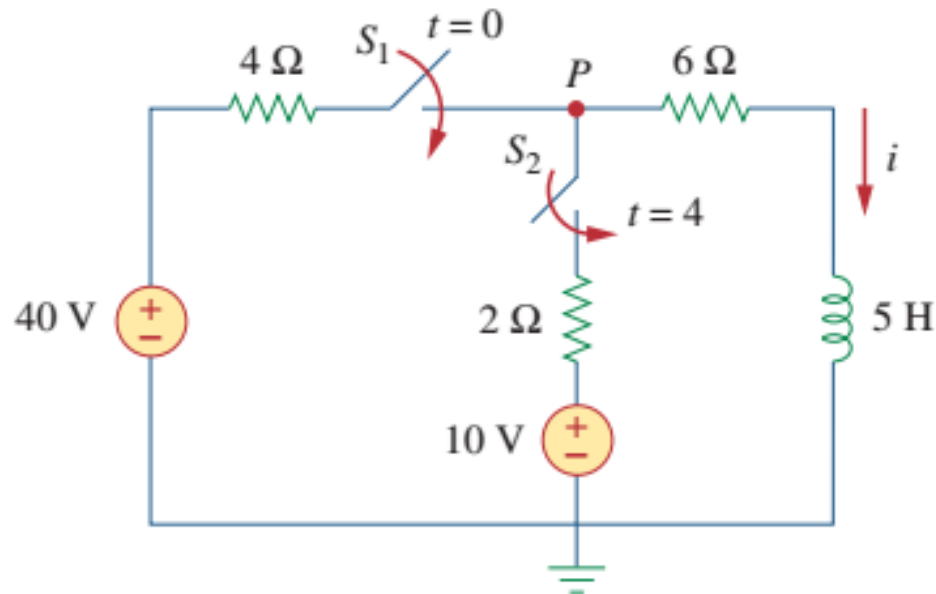At $t = 0$, switch 1 in Fig. 7.53 is closed, and switch 2 is closed 4 s later. Find $i(t)$ for $t > 0$. Calculate i for $t = 2$ s and $t = 5$ s.




We need to consider the three time intervals $t \leq 0$, $0 \leq t \leq 4$, and $t \geq 4$ separately. For $t < 0$, switches S_1 and S_2 are open so that $i = 0$. Since the inductor current cannot change instantly,

$$i(0^-) = i(0) = i(0^+) = 0$$






First order op-amp circuit

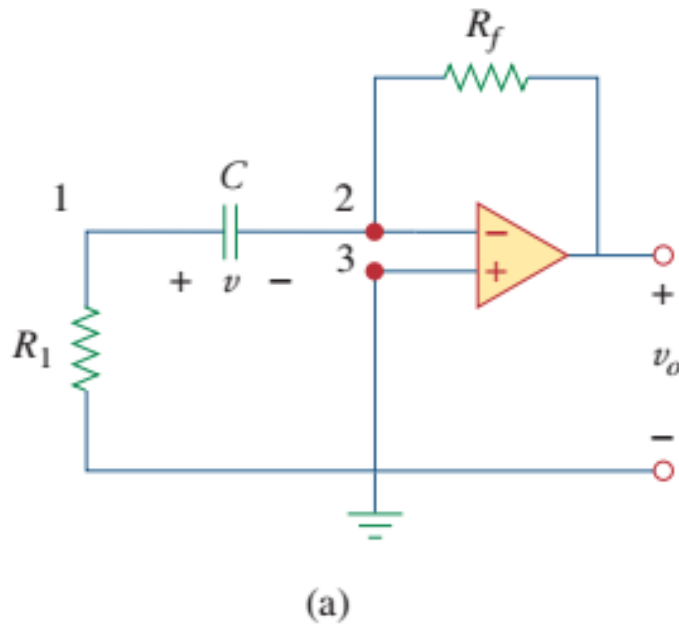For the op amp circuit in Fig. 7.55(a), find v_o for $t > 0$, given that $v(0) = 3 \text{ V}$. Let $R_f = 80 \text{ k}\Omega$, $R_1 = 20 \text{ k}\Omega$, and $C = 5 \mu\text{F}$.





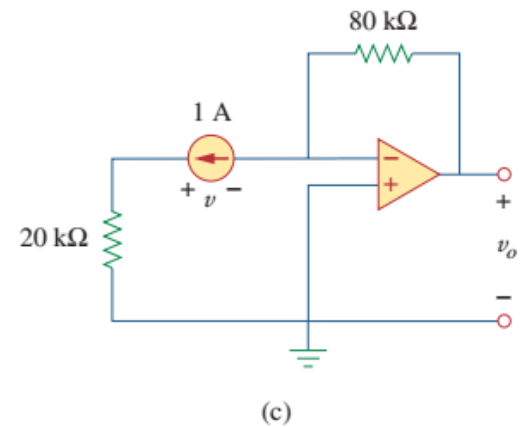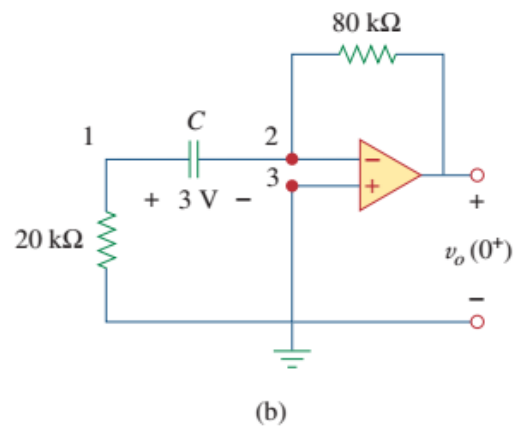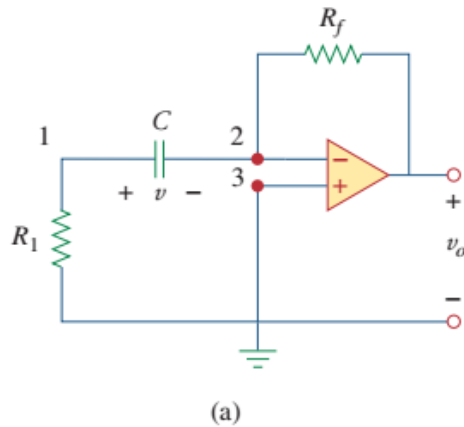For the op amp circuit in Fig. 7.55(a), find v_o for $t > 0$, given that $v(0) = 3 \text{ V}$. Let $R_f = 80 \text{ k}\Omega$, $R_1 = 20 \text{ k}\Omega$, and $C = 5 \mu\text{F}$.





**Calculate $v(t)$ for $0 < t < 2\text{s}$
given $v(0) = 2\text{V}$, $R = 5\Omega$, $C = 0.4\text{F}$**

$$V_s = e^{-t}?$$

$$V_s = e^{-t/2}?$$

