
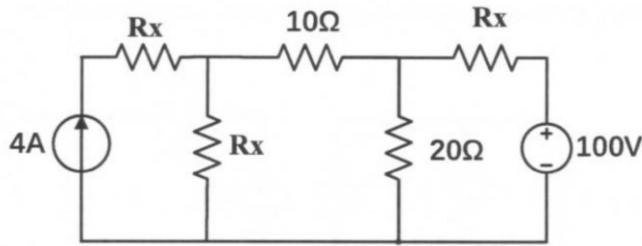


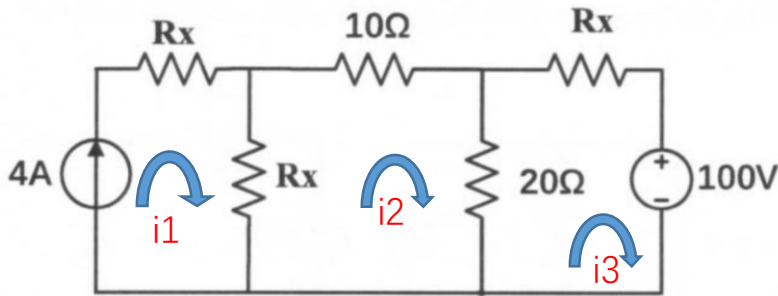1. For the circuit below, determine the value of R_x such that NO current flows through the $10\ \Omega$ resistor in the circuit. (12pt)



Mesh analysis:



Mesh1 : $i_1 = 4A$ ①(2')

Mesh2 : $R_x(i_2 - i_1) + 10i_2 + 20(i_2 - i_3) = 0$ ②(2')


Mesh3 : $20(i_3 - i_2) + R_x i_3 + 100 = 0$ ③(2')

Additional equation(No current flows the $10\ \Omega$ resistor) : $i_2 = 0A$ ④(2')

We can get: $R_x^2 + 20R_x - 500 = 0$

and the value of R_x is : $R_x = 10(\sqrt{6} - 1) = 14.49\ \Omega$ (4')

Nodal analysis:

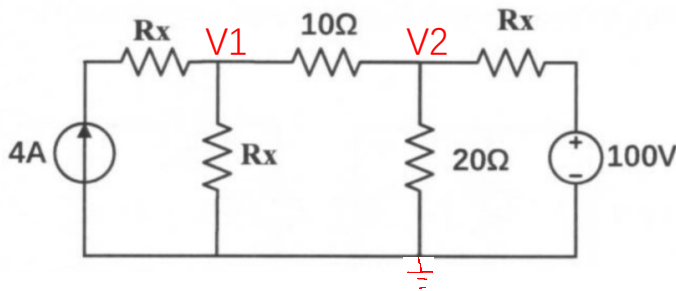


Node 1 : $-4 + \frac{V_1}{R_x} + \frac{V_1 - V_2}{10} = 0$ ①(3')

Node 2 : $\frac{V_2 - V_1}{10} + \frac{V_2}{20} + \frac{V_2 - 100}{R_x} = 0$ ②(3')

Additional equation(No current flows the $10\ \Omega$ resistor) : $V_1 = V_2$ ③(2')

We can get: $R_x^2 + 20R_x - 500 = 0$

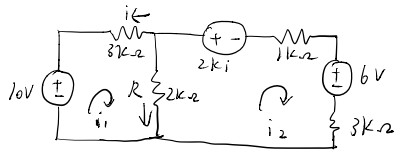and the value of R_x is : $R_x = 10(\sqrt{6} - 1) = 14.49\ \Omega$ (4')




mesh

$$\begin{cases} \text{mesh 1: } -10 + 3k i_1 + 2k(i_1 - i_2) = 0 & \dots 2 \text{ 为方程共6分, 按实际情况给分} \\ \text{mesh 2: } 6k i_2 - 2k i_1 + 2ki + 6 = 0 & \dots 2 \\ i = -i_1 & \dots 2 \end{cases}$$

$$\Rightarrow \begin{cases} i_1 = \frac{24}{11000} \text{ A} & \dots 2 \\ i_2 = \frac{1}{2200} \text{ A} & \dots 2 \end{cases}$$

$$i_R = i_1 - i_2 \approx 0.0017 \text{ A} = 1.7 \text{ mA} \quad \dots 2$$

nodal

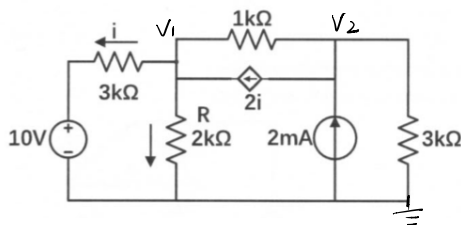


$$\begin{cases} \text{nodal 1: } \frac{V_1 - 10}{3k} + \frac{V_1}{2k} + \frac{V_1 - V_2}{1k} = 2i & \dots 2 \\ \text{nodal 2: } \frac{V_2 - V_1}{1k} + \frac{V_2}{3k} + 2i = 0.002 & \dots 2 \\ i = \frac{V_1 - 10}{3k} & \dots 2 \end{cases}$$

为方程共6分, 按实际情况给分


$$\begin{cases} V_1 = \frac{38}{11} \text{ V} & \dots 3 \\ V_2 = \frac{81}{11} \text{ V} & \dots 1 \end{cases}$$

$$i_R = \frac{V_1}{2k} = \frac{19}{11} \text{ mA} \approx 1.73 \text{ mA} \quad \dots 2$$

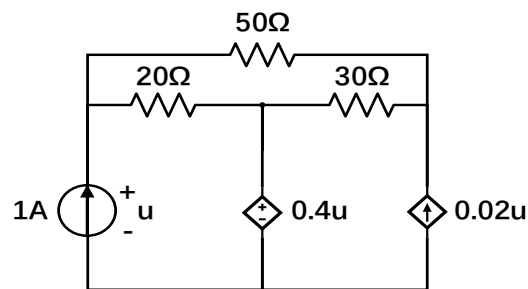3. Use Mesh Analysis method to calculate the power supplied by the 1A current source. (12')



Mesh analysis:

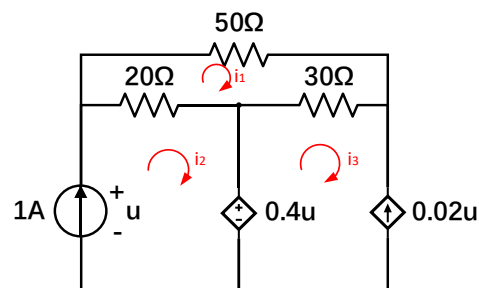

Mesh 1: $50i_1 + 30(i_1 - i_3) + 20(i_1 - i_2) = 0$ ①(2')

Mesh2: $20(i_2 - i_3) + 0.4u - u = 0$ ②(2')

Mesh3: $i_3 = -0.02u$ ③(2')

Additional equation: $i_2 = 1$ ④(1')

We can get: $u = \frac{100}{3} = 33.33v$ (2')

and the power is $P = -ui_2 = -\frac{100}{3} = -33.33W$ (2')

It represents the 1A current source is supplying power of 33.33W.....(1')



Hint: if students used the nodal analysis method, they would not get grades.

4. Linear Property & Superposition (12pt)

(1) For the two independent sources below, if keeping the independent voltage source only (turn off the independent current source), find V_o and the power absorbed by the 2Ω resistor.

(2) For the two independent sources below, if keeping the independent current source only (turn off the independent voltage source), find V_o and the power absorbed by the 2Ω resistor.

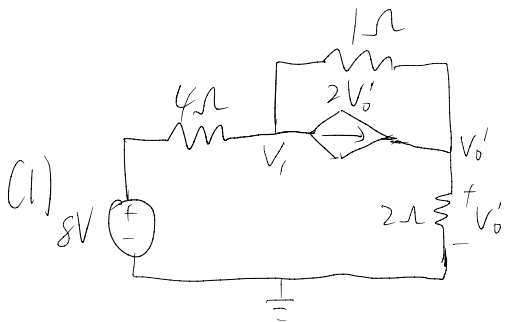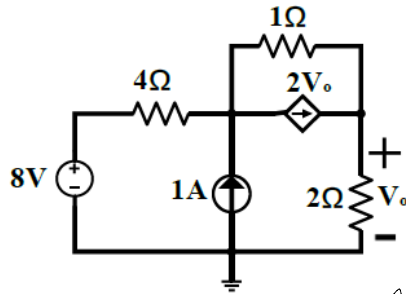(3) From the results in (1) and (2), find the power absorbed by the 2Ω resistor in the following figure.




$$\begin{cases} \frac{V_1 - 8V}{4\Omega} + 2V_o' + \frac{V_1 - V_o'}{1\Omega} = 0 \sim 1' \\ \frac{V_o' - V_1}{1\Omega} - 2V_o' + \frac{V_o'}{2\Omega} = 0 \sim 1' \end{cases}$$

$$V_o' = \frac{16}{3}V = 5.33V \quad (5.33V \pm 0.01V \text{ 都给分}) \sim 1'$$

$$P_1 = \frac{V_o'^2}{2\Omega} = \frac{128}{9}W = 14.22W \sim 1'$$

$$(14.22W \pm 0.05W \text{ 都给分})$$

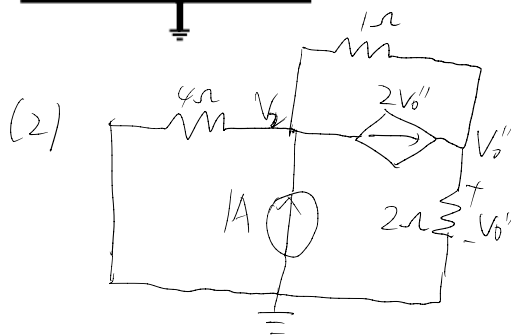

$$\begin{cases} \frac{V_2}{4\Omega} - 1A + 2V_o'' + \frac{V_2 - V_o''}{1\Omega} = 0 \sim 1' \\ \frac{V_o'' - V_2}{1\Omega} - 2V_o'' + \frac{V_o''}{2\Omega} = 0 \sim 1' \end{cases}$$

$$V_o'' = \frac{8}{3}V = 2.67V \quad (2.67V \pm 0.01V \text{ 都给分}) \sim 1'$$

$$P_2 = \frac{V_o''^2}{2\Omega} = \frac{32}{9}W = 3.56W \sim 1'$$

$$(3.56W \pm 0.05W \text{ 都给分})$$

★ (1)中 V_o' , P_1 (2)中 V_o'' , P_2

(3)中 P 五个答案分数均

都给, 但单位少1个扣1分


整个大题因单位扣的分 ≤ 2 分

$$(3) V_o = V_o' + V_o'' = 8V \quad (8V \pm 0.05V \text{ 都给分}) \sim 2'$$

$$P = \frac{V_o^2}{2\Omega} = 32W \sim 2'$$

$$(32W \pm 1W \text{ 都给分})$$
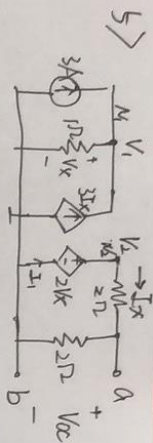
$$★ \text{ 全错无解: } P = P_1 + P_2 = 17.78W$$



Solution: 1° Find V_{oc} .

For N_1 : $3 + \frac{0-V_1}{1} + 3I_x = 0$

For N_2 : $I_1 + \frac{0-V_2}{4} = 0$... 2'


And, $V_2 = 2V_x$

$V_x = V_1$

$I_x = \frac{V_2 - 0}{4}$

$\Rightarrow \begin{cases} V_1 = -6V \\ V_2 = -12V \end{cases}$

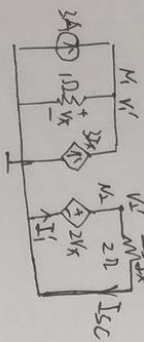$V_{oc} = \frac{2}{2+2} \times V_2 = -6V$... 3'



2° Find I_{sc} .

For N_1 : $3 + \frac{0-V_1'}{1} + 3I_x = 0$


For N_2 : $I_1' + \frac{0-V_2'}{2} = 0$... 2'

And, $V_2' = 2V_x$

$V_x = V_1'$

$I_x = \frac{V_2' - 0}{2}$
 $\Rightarrow \begin{cases} V_1' = -\frac{3}{2}V \\ V_2' = -3V \end{cases}$

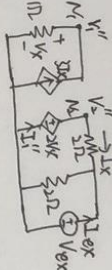$I_{sc} = \frac{V_2'}{2} = -\frac{3}{2}A$... 3'



3° Find R_{eq} .

For N_1 : $\frac{0-V_1''}{1} + 3I_x = 0$

For N_2 : $I_1'' + \frac{V_{ox} - V_2''}{2} = 0$... 2'

And, $V_2'' = 2V_x$

$V_x = V_1''$

$I_x = \frac{V_2'' - V_{ox}}{2}$

$\Rightarrow \begin{cases} V_1'' = \frac{3}{4}V_{ox} \\ V_2'' = \frac{3}{2}V_{ox} \end{cases}$

$I_{ox} = \frac{V_{ox} - V_2''}{2} + \frac{V_{ox} - 0}{2} = \frac{1}{4}V_{ox}$


$R_{eq} = \frac{V_{ox}}{I_{ox}} = 4\Omega$... 3'

1°, 2°, 3° 任意两个部分组合为10分题组。其中,每个部分均网孔/节点方程2分,并给正确结果5分。另外,3°可取 V_{ox} 的特定值计算,评分标准相同。

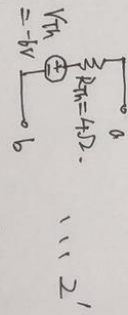(1) Thevenin equivalent circuit.

$V_{Th} = V_{oc} = -6V$


$R_{Th} = R_{eq} = \frac{V_{oc}}{I_{sc}} = 4\Omega$



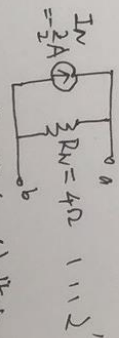(2) Norton equivalent circuit

$I_N = I_{sc} = -\frac{3}{2}A$


$R_N = R_{eq} = \frac{V_{oc}}{I_{sc}} = 4\Omega$



等效电路为每个2分。其中,电流源反向标记,电压、电流取正值。

6. Max power transfer. 14分

1) ① 开路求 V_{th} — 10分

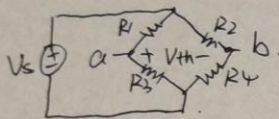

$$V_{th} = \left(\frac{R_3}{R_1+R_3} - \frac{R_4}{R_2+R_4} \right) V_s \quad -4分$$

$$i_{sc} = \frac{V_s - V}{R_1} + \frac{0 - V}{R_3} \quad -1分$$

$$= \frac{1}{R_1} V_s - \frac{\left(\frac{1}{R_1} + \frac{1}{R_3} \right) \left(\frac{1}{R_1} + \frac{1}{R_2} \right)}{\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_4}} \cdot V_s$$

$$R_{th} = \frac{V_{th}}{i_{sc}}$$

$$= \frac{R_2 R_1 R_2 R_3 + R_1 R_3 R_4 + R_2 R_3 R_4 + R_1 R_2 R_4}{(R_1 + R_3)(R_2 + R_4)}$$

$$= \frac{R_2 R_4 (R_1 + R_3) + R_1 R_3 (R_2 + R_4)}{(R_1 + R_3)(R_2 + R_4)}$$

$$= \frac{R_2 R_4}{R_2 + R_4} + \frac{R_1 R_3}{R_1 + R_3} \quad -1分$$

② R_L 与 R_{th} 关系
When power delivered to R_L is max


$$R_L = R_{th} \quad -2分$$

$$(2) P_{max} = \frac{\left(\frac{1}{2} V_{th} \right)^2}{R_L} \quad -2分$$


$$= \frac{1}{4} V_s^2 \cdot \frac{(R_2 R_3 - R_1 R_4)^2}{R_2 R_4 (R_1 + R_3)^2 (R_2 + R_4) + R_1 R_3 (R_1 + R_3) (R_2 + R_4)} \quad -2分$$

② 求 R_{th}

法① 直接求等效电阻

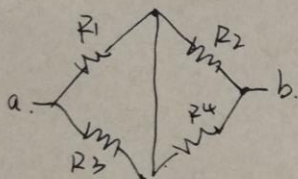


可等效为

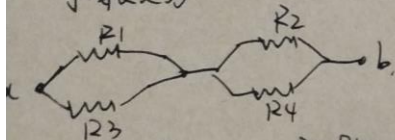

$$R_{th} = \frac{R_1 R_3}{R_1 + R_3} + \frac{R_2 R_4}{R_2 + R_4} \quad -4分$$

法② 短路求 i_{sc}

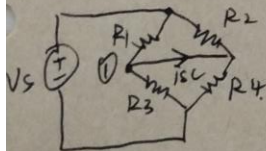


assume at Node ①, voltage is V .

use KCL:

$$\frac{V - V_s}{R_1} + \frac{V - V_s}{R_2} + \frac{V - 0}{R_3} + \frac{V - 0}{R_4} = 0 \quad -1分$$

$$V = \frac{\frac{1}{R_1} + \frac{1}{R_2}}{\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_4}} V_s \quad -1分$$

使用RL公式求未知答案 14分

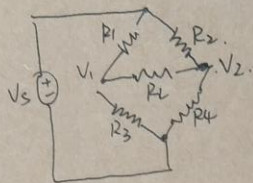

$$\begin{cases} \frac{V_1 - V_S}{R_1} + \frac{V_1 - V_2}{R_2} + \frac{V_1 - 0}{R_3} = 0 \\ \frac{V_2 - V_S}{R_2} + \frac{V_2 - V_1}{R_2} + \frac{V_2 - 0}{R_4} = 0 \end{cases} \quad -2\frac{3}{4}'$$

$$V_1 = \frac{[(\frac{1}{R_2} + \frac{1}{R_4} + \frac{1}{R_L}) \cdot \frac{R_L}{R_1} + \frac{1}{R_2}] \cdot V_S}{(\frac{1}{R_2} + \frac{1}{R_4} + \frac{1}{R_L}) (1 + \frac{R_L}{R_1} + \frac{R_L}{R_3}) - \frac{1}{R_L}} \quad -2'$$

$$V_2 = \frac{[(\frac{1}{R_1} + \frac{1}{R_3} + \frac{1}{R_L}) \cdot \frac{R_L}{R_2} + \frac{1}{R_2}] \cdot V_S}{(\frac{1}{R_1} + \frac{1}{R_3} + \frac{1}{R_L}) (1 + \frac{R_L}{R_2} + \frac{R_L}{R_4}) - \frac{1}{R_L}} \quad -2'$$

$$V_{RL} = V_1 - V_2$$

V_{RL} 为 R_L 的函数.

$$\frac{dV_{RL}}{dR_L} = 0 \rightarrow \text{解出 } R_L \text{ 为何值时}$$

$$P = \frac{(V_{RL})^2}{R_L}$$

$$\frac{dP}{dR_L} = 0 \quad \text{取 } R_L > 0 \text{ 时的值}$$

可解出 R_L 为何值时.

P 最大.

$$R_L = \frac{R_1 \cdot R_3}{R_1 + R_3} + \frac{R_2 \cdot R_4}{R_2 + R_4} \quad -4'$$


代入 P .

$$\text{可得 } P = \frac{1}{4} V_S^2 \cdot \frac{(R_2 R_3 - R_1 R_4)^2}{R_2 R_4 (R_2 + R_4) (R_1 + R_3)^2 + R_1 R_3 (R_1 + R_3) (R_2 + R_4)^2} \quad -4'$$



7. Assume that the ideal operational amplifier is operating in its linear range. (12pt)

(1) Solve for v_b . (2) Solve for v_o . (3) Solve for i_o .

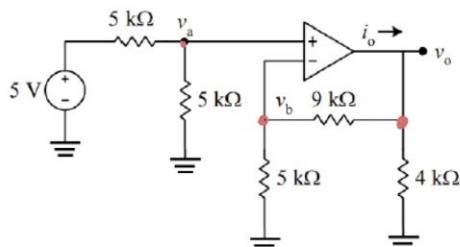

* 关于 3) 问

公式部分 1) 分母为 9, 4 而非 9k, 4k \Rightarrow 给 1 分
2) 分母 4k, 9k 写对, 但方向写反 \Rightarrow 给 1 分
3) 其余错误不得分

答案部分: 写 2.25A 而非 2.25mA, 一律不得分
(属于答案错误而非单位错误)

* 关于 1), 2), 3) 问, 只要式子列对, 答案错仍给过程分

* 前 2 小问求错, 3) 问答案对不给分 (已验证你无法得出该答案)

* 未在对应小问给出对应答案 (写在别处), 此次未扣分

$$4' 1) \frac{v_a - 5}{5k} + \frac{v_a}{5k} = 0 \quad 2'$$

$$\Rightarrow v_a = 2.5V$$

$$v_b = v_a = 2.5V \quad 2'$$

$$4' 2) \frac{v_o - v_b}{9k} = \frac{v_b}{5k} \quad 2'$$


$$5v_o - 5v_b = 9v_b$$

$$v_o = \frac{14}{5} v_b = 7V \quad 2'$$

$$4' 3) \frac{v_o - v_b}{9k} + \frac{v_o}{4k} = i_o \quad 2'$$

$$i_o = 2.25mA \quad 2'$$

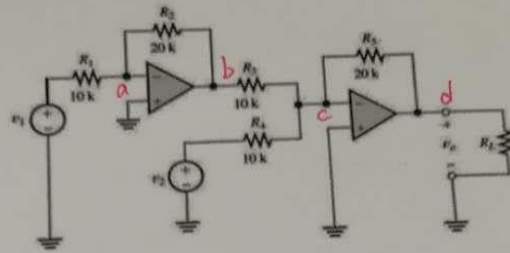8. Assume that the ideal operational amplifiers in following circuit are both operating in linear range. Please calculate the output voltage v_o given $v_1 = 4V$ and $v_2 = 6V$. (12pt)



1)

$$\begin{cases} V_a = 0V \\ V_c = 0V \end{cases} \quad (2')$$

$$\frac{V_1 - V_a}{10k} + \frac{V_b - V_a}{20k} = 0 \quad (4')$$

$$\frac{V_2 - V_c}{10k} + \frac{V_b - V_c}{10k} + \frac{V_d - V_c}{20k} = 0 \quad (4')$$

$$V_d = V_o$$

$$\begin{cases} V_b = -8V \\ V_o = 4V \end{cases} \quad (2')$$

2) $V_b = -\frac{R_2}{R_1} V_1 = -8V \quad (4')$

$$V_d = -\left(\frac{R_5}{R_3} V_b + \frac{R_5}{R_4} V_2\right) \quad (4')$$

$$V_o = V_d = 4V \quad (4')$$