

Homework 6

Due date: Dec.9th, 2021


Turn in your homework in class

Rules:

- Work on your own. Discussion is permissible, but extremely similar submissions will be judged as plagiarism.
- Please show all intermediate steps: a correct solution without an explanation will get zero credit.
- Please submit on time. No late submission will be accepted.
- Please prepare your submission in English only. No Chinese submission will be accepted.
- If needed, round the number to the nearest hundredths, i.e., rounding it to 2 decimal places.

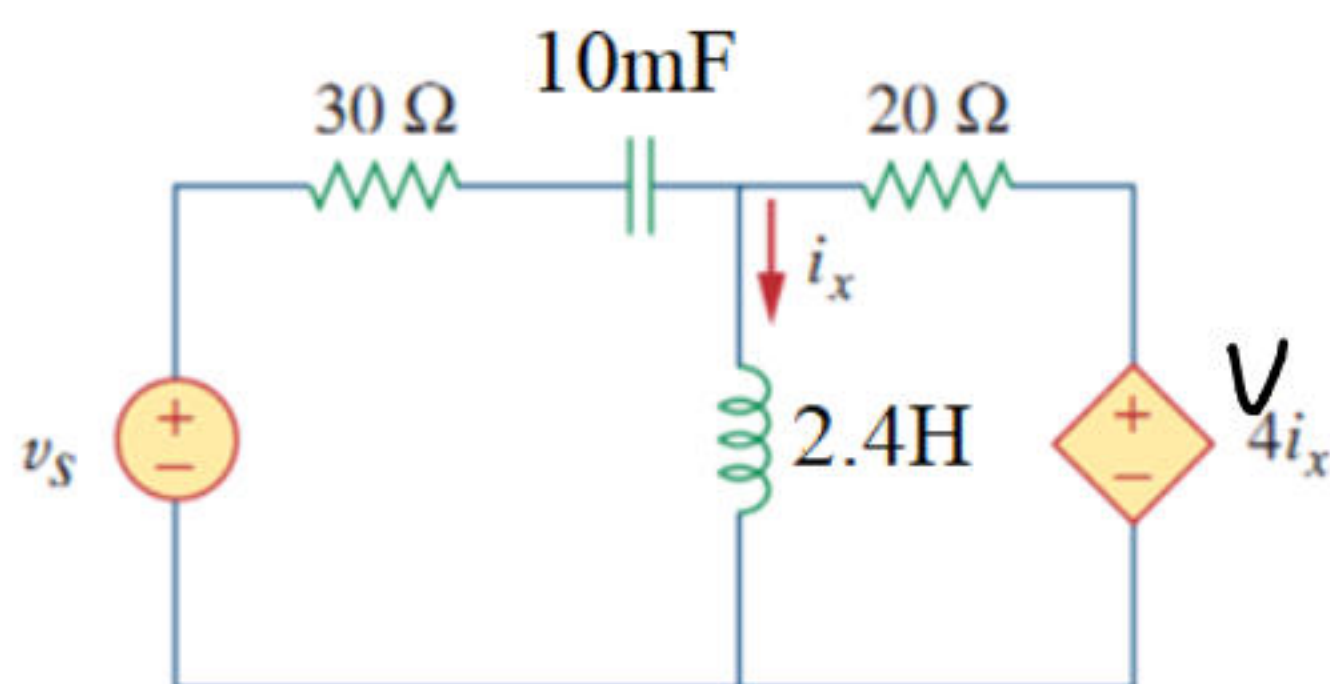1. The circuit below is in steady state and $V_s = 40\sin(5t + 15^\circ)V$ in time domain

- Calculate $i_x(t)$ in S.S.
- Calculate the **apparent power** on the 10mF capacitor.
- Calculate the **complex power** absorbed by the **controlled source**.



$$Z_C = \frac{1}{j\omega C} = -20j \Omega$$

$$Z_L = j\omega L = 12j \Omega$$

$$V_s = 40 \angle -75^\circ V$$

(a)

$$KCL: \frac{V_s - V_X}{30 - 20j} + \frac{4i_X - V_X}{20} = i_X$$

$$V_X = 12j i_X$$

$$\frac{V_s}{30 - 20j} = 12j \cdot \left(\frac{1}{20} + \frac{1}{30 - 20j} \right) + \left| -\frac{1}{5} \right| i_X$$

$$i_X = -0.113 - 1.029j A = 1.034 \angle -96.25^\circ A$$

$$= 1.034 \cos(5t - 96.25^\circ) A$$

$$(b) \quad i_C = \frac{V_s - 12j \cdot i_X}{30 - 20j} = 1.034 \angle -59.38^\circ A$$

$$V_C = i_C \cdot -20j = -17.796 - 10.533j V = 20.68 \angle -149.38^\circ V$$

$$S_{apparent} = \frac{1}{2} V_m I_m = 10.692 VA$$

$$(c) \quad i_{CS} = i_C - i_X = 0.654 \angle 12.185^\circ A$$


$$V_{CS} = 4i_X = 4.136 \angle -96.25^\circ V$$

$$S = \frac{1}{2} V_{CS} \cdot i_{CS}^* = -0.428 - 1.283j VA = 1.352 \angle -108.44^\circ VA$$

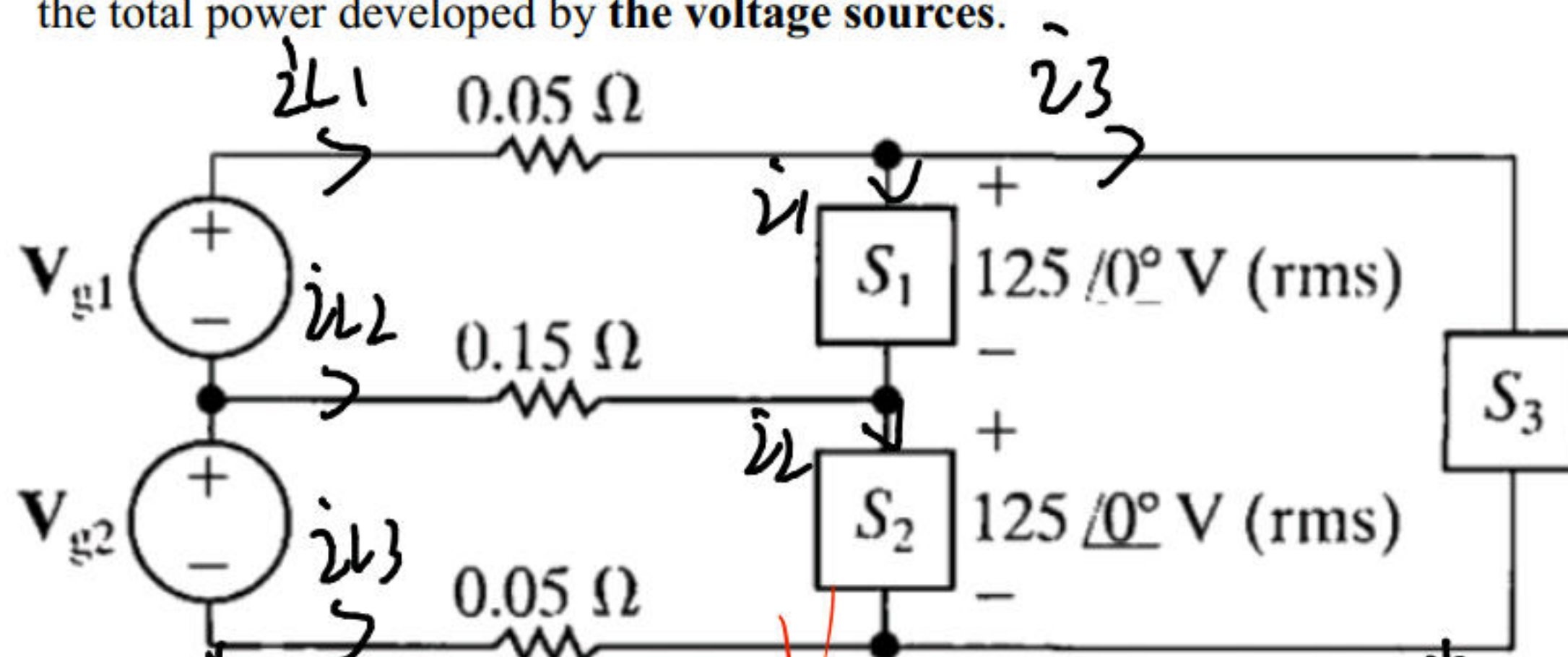2. Consider the following circuit with three elements S_1 , S_2 and S_3 . The voltages on the S_1 and S_2 are given. The complex power absorbed by S_1 , S_2 and S_3 are

$$S_1 = (10 + j2.5) \text{ kVA}, \quad S_2 = (12.5 + j5) \text{ kVA}, \quad S_3 = 4 \text{ kVA}, \text{ respectively}$$

- Find V_{g1} (rms) and V_{g2} (rms).
- Calculate the **complex power** developed by the voltage sources V_{g1} and V_{g2} .
- Prove that the total power dissipated by S_1 , S_2 and S_3 **and the resistors** is equal to the total power developed by **the voltage sources**.



$$a) \quad \bar{i}_1 = \left(\frac{S_1}{V_1} \right)^* = (80 - 20j) \text{ Arms} \quad \bar{i}_2 = \left(\frac{S_2}{V_2} \right)^* = (100 - 40j) \text{ Arms}$$

$$\bar{i}_3 = \left(\frac{S_3}{V_3} \right)^* = 16 \text{ Arms}$$

$$\bar{i}_{L1} = \bar{i}_1 + \bar{i}_3 = (96 - 20j) \text{ Arms}$$

$$\bar{i}_{L2} = \bar{i}_1 + \bar{i}_2 = (20 - 20j) \text{ Arms}$$

$$\bar{i}_{L3} = -\bar{i}_2 - \bar{i}_3 = (-116 + 40j) \text{ Arms}$$

$$\text{KVL: } \begin{cases} V_{g1} = \bar{i}_{L1} \cdot 0.05 + V_1 - \bar{i}_{L2} \cdot 0.15 \\ V_{g2} = \bar{i}_{L2} \cdot 0.15 + V_2 - \bar{i}_{L3} \cdot 0.05 \end{cases} \Rightarrow \begin{cases} V_{g1} = 126.8 + 2j \text{ Vrms} \\ V_{g2} = 133.8 - 5j \text{ Vrms} \end{cases}$$


$$b) \quad S_{g1} = -V_{g1} \cdot \bar{i}_{L1}^* = -12132.8 - 2728j \text{ VA} = 12435.7 \angle -167^\circ \text{ VA}$$

$$S_{g2} = V_{g2} \cdot \bar{i}_{L3}^* = -15720.8 - 4772j \text{ VA} = 16429.1 \angle -163^\circ \text{ VA}$$

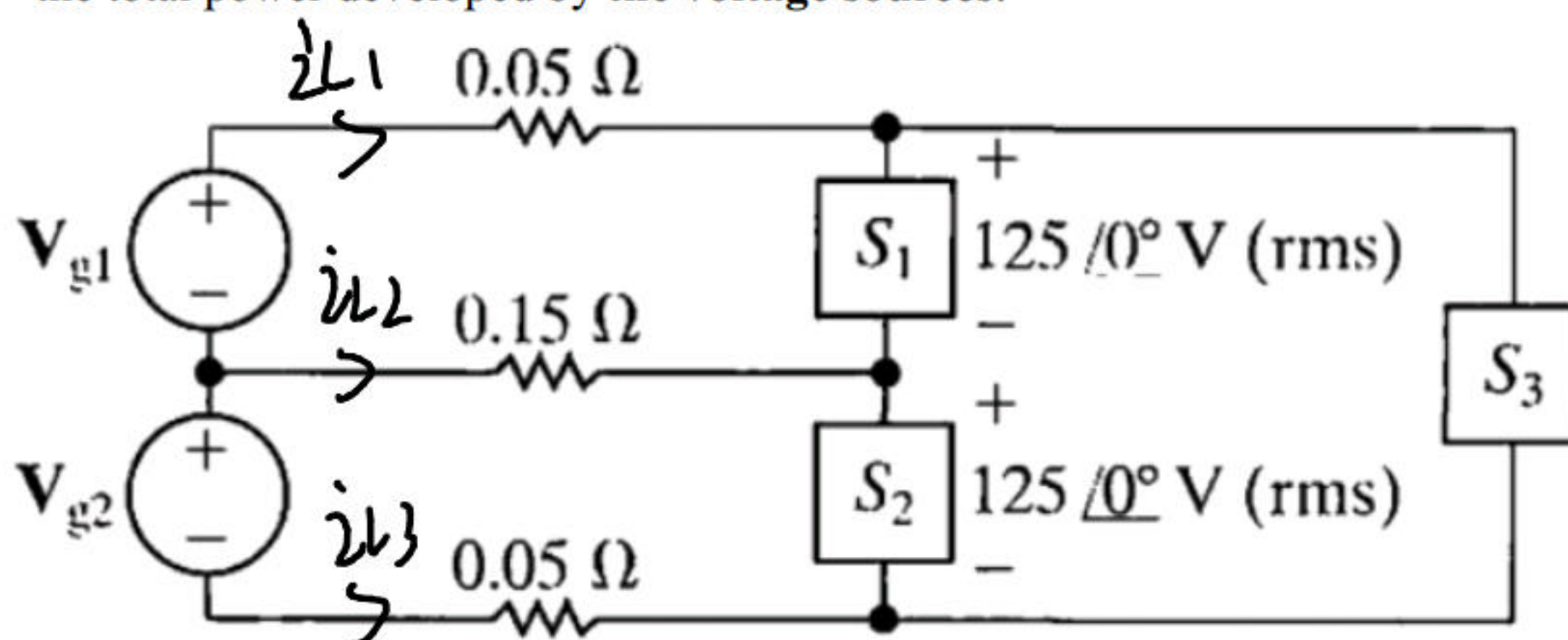2. Consider the following circuit with three elements S_1 , S_2 and S_3 . The voltages on the S_1 and S_2 are given. The complex power absorbed by S_1 , S_2 and S_3 are

$$S_1 = (10 + j2.5) \text{ kVA}, \quad S_2 = (12.5 + j5) \text{ kVA}, \quad S_3 = 4 \text{ kVA}, \text{ respectively}$$

- Find V_{g1} (rms) and V_{g2} (rms).
- Calculate the **complex power** developed by the voltage sources V_{g1} and V_{g2} .
- Prove that the total power dissipated by S_1 , S_2 and S_3 **and the resistors** is equal to the total power developed by **the voltage sources**.



$$c) \quad S_{R1} = \|i_{L1}\|^2 R_1 = 480.8 \text{ VA} \quad 2'$$

$$S_{R2} = \|i_{L2}\|^2 \cdot R_2 = 120 \text{ VA} \quad 2'$$

$$S_{R3} = \|i_{L3}\|^2 \cdot R_3 = 752.8 \text{ VA} \quad 2'$$

$$S_{\text{release}} = -27853.6 - 7500j \text{ VA} = S_{g1} + S_{g2} \quad 2'$$

$$S_{\text{dissipate}} = \sum_{i=1}^3 S_i + \sum_{i=1}^3 S_{Ri} \quad 2'$$


$$= 27853.6 + 7500j \text{ VA}$$

$$S_{\text{release}} + S_{\text{dissipate}} = 0 \quad \text{Q.E.D.} \quad 2'$$

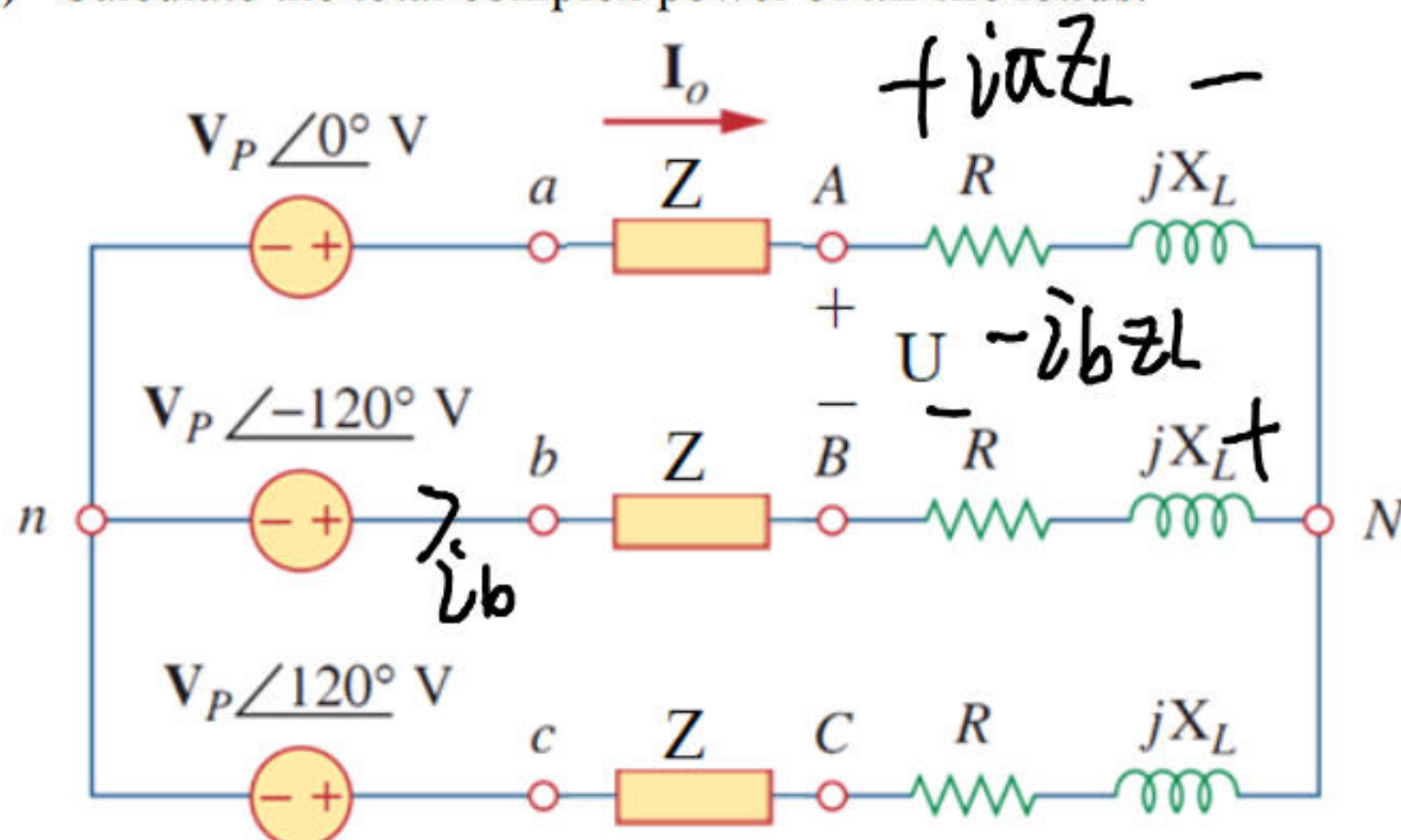
3. Consider the following three-phase circuit. $R=20\Omega$, $X_L=5$, $V_p=50$ (rms).

Line impedance $Z=1+j0.5\Omega$.

- Calculate the **line current** I_o .
- Calculate the **voltage** U shown in the circuit.
- Calculate the total complex power of **all the loads**.



a) For one phase:

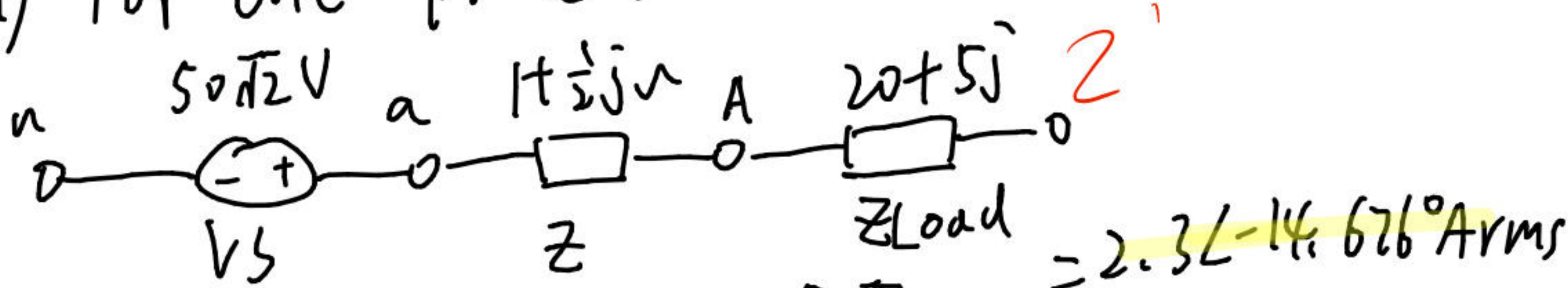

$$I_o = \tilde{I}_a = \frac{V_S}{Z + Z_{load}} = \frac{50\sqrt{2}}{21 + j5.5} = 3.257 \angle -14.676^\circ \text{ A}$$

$$b) \tilde{I}_b = \tilde{I}_a \angle -120^\circ = 3.257 \angle -134.676^\circ \text{ A}$$

$$V = \tilde{I}_a Z_{load} - \tilde{I}_b Z_{load} = 116.298 \angle 29.360^\circ \text{ V} \\ = 82.235 \angle 29.360^\circ \text{ Vrms}$$

c)


$$S = \frac{1}{2} \tilde{I}_a \cdot \tilde{I}_a^* \cdot Z_{load} \cdot 3 = 318.24 + j79.56 \text{ VA}$$

If All Passive Elements

$$S = \frac{1}{2} \tilde{I}_a \cdot \tilde{I}_a^* \cdot (Z_L + Z_{line}) \cdot 3 = 345.42 \angle 14.676^\circ \text{ VA}$$


Both Answers Give full Points

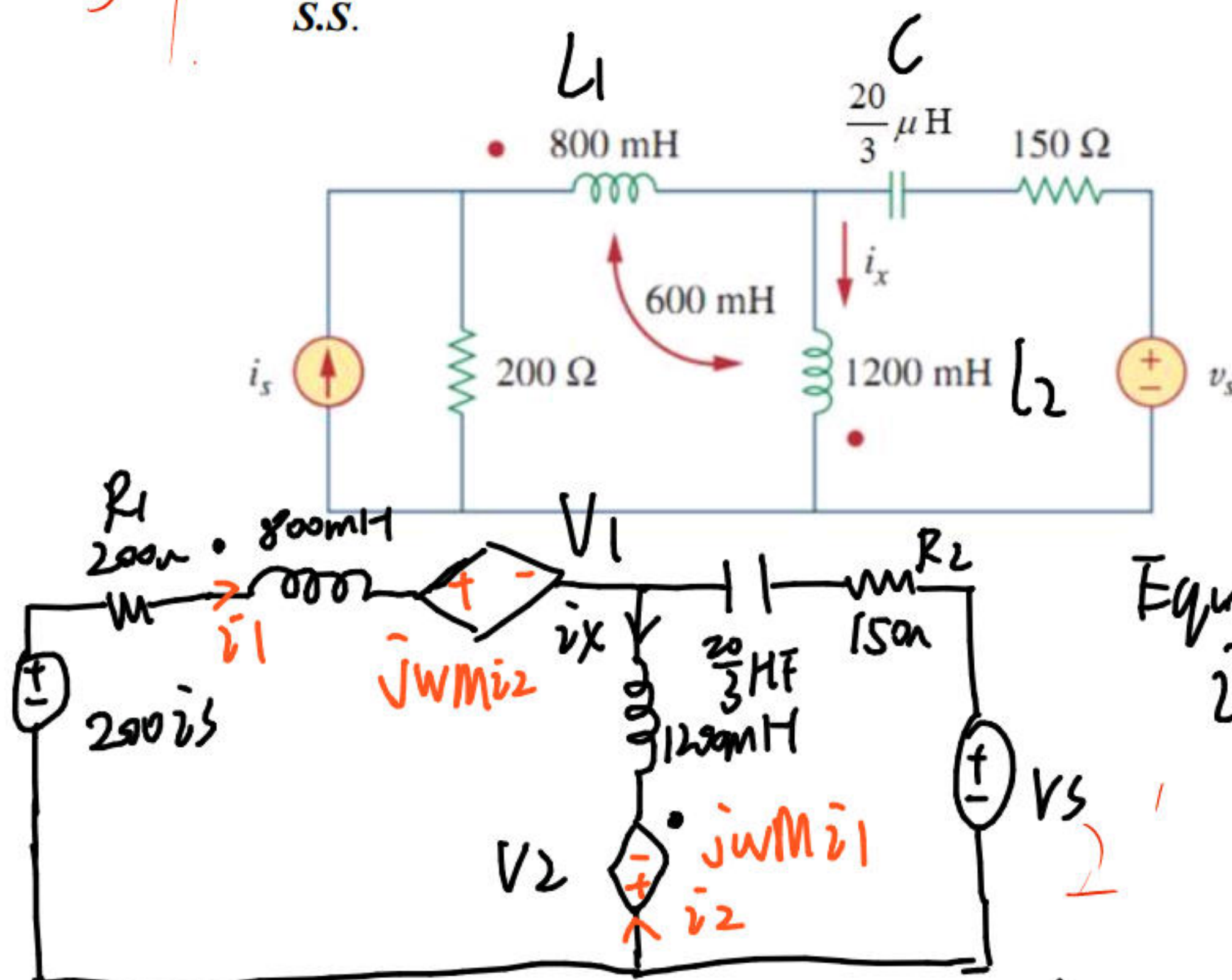4. The following circuit includes a mutual inductance $M=600\text{mH}$, and is in steady state. Given $i_s = 4\sin(600t)\text{A}$, $v_s = 100\cos(300t + 60^\circ)\text{V}$, calculate $i_x(t)$ in S.S.



Equivalent circuit
 $\tilde{v}_2 = -\tilde{v}_x$

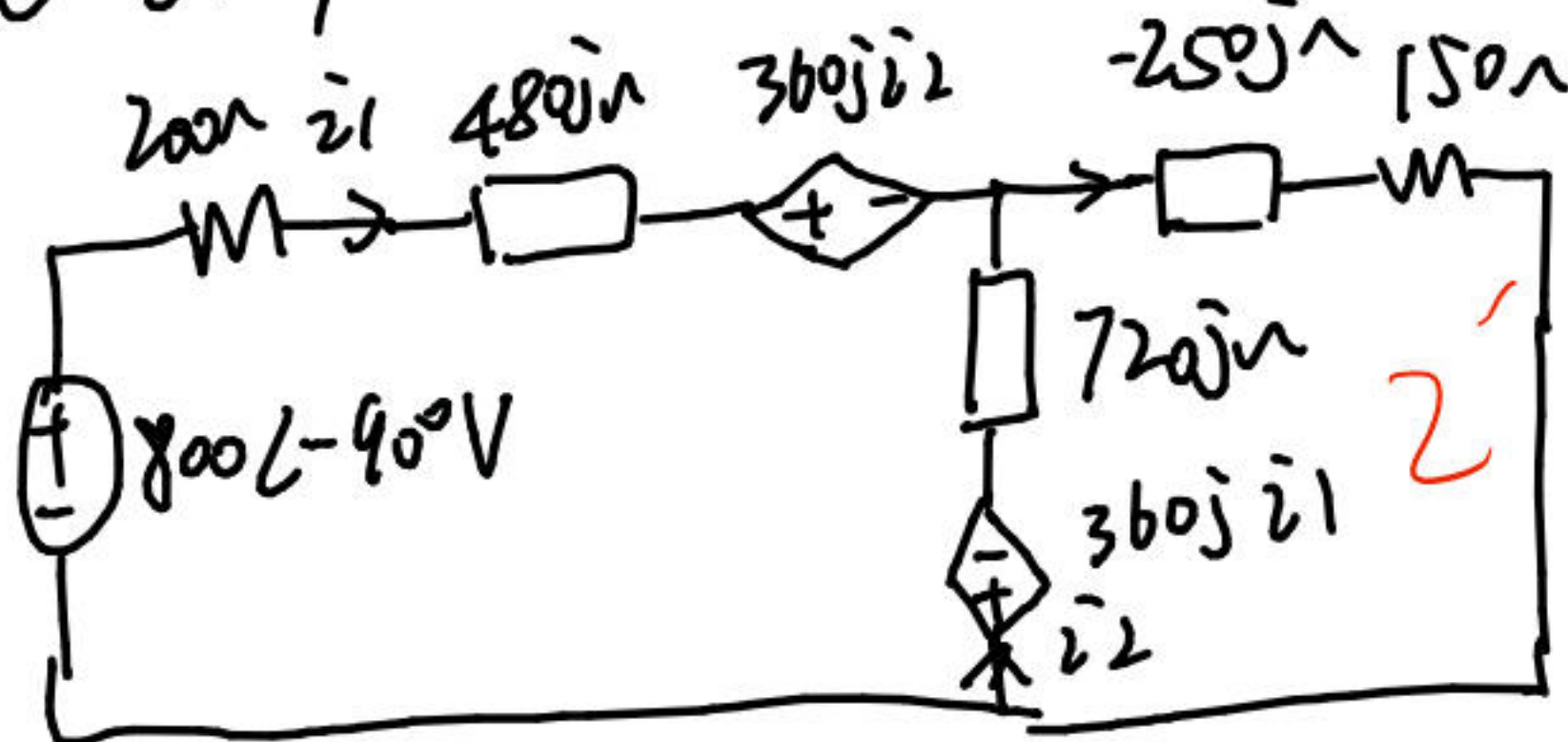① Only v_s is on $\omega = 600\text{ rad/s}$



$$\begin{aligned} Z_{L1} &= j\omega L_1 = 480j\Omega \\ Z_{L2} &= j\omega L_2 = 720j\Omega \\ Z_C &= \frac{1}{j\omega C} = -250j\Omega \\ V_1 &= j\omega M \tilde{i}_2 = 360j \tilde{i}_2 \text{ V} \\ V_2 &= j\omega M \tilde{i}_1 = 360j \tilde{i}_1 \text{ V} \end{aligned}$$


$$\text{KVL: } \begin{cases} R_1 \tilde{i}_s = \tilde{i}_1 \cdot Z_{L1} + V_1 + (\tilde{i}_1 + \tilde{i}_2)(Z_C + R_2) \\ V_2 + \tilde{i}_2 \cdot Z_{L2} + (\tilde{i}_1 + \tilde{i}_2)(Z_C + R_2) = 0 \end{cases}$$

$$800\angle-90^\circ = \tilde{i}_1 \cdot (200 + 480j) + 360j \tilde{i}_2 + (150 - 250j)(\tilde{i}_1 + \tilde{i}_2)$$


$$360j \tilde{i}_1 + \tilde{i}_2 \cdot 720j + (\tilde{i}_1 + \tilde{i}_2) \cdot (150 - 250j) = 0$$

$$\begin{cases} \tilde{i}_2 = 0.833\angle14.572^\circ \text{ A} \\ \tilde{i}_1 = 2.209\angle-129.38^\circ \text{ A} \end{cases}$$

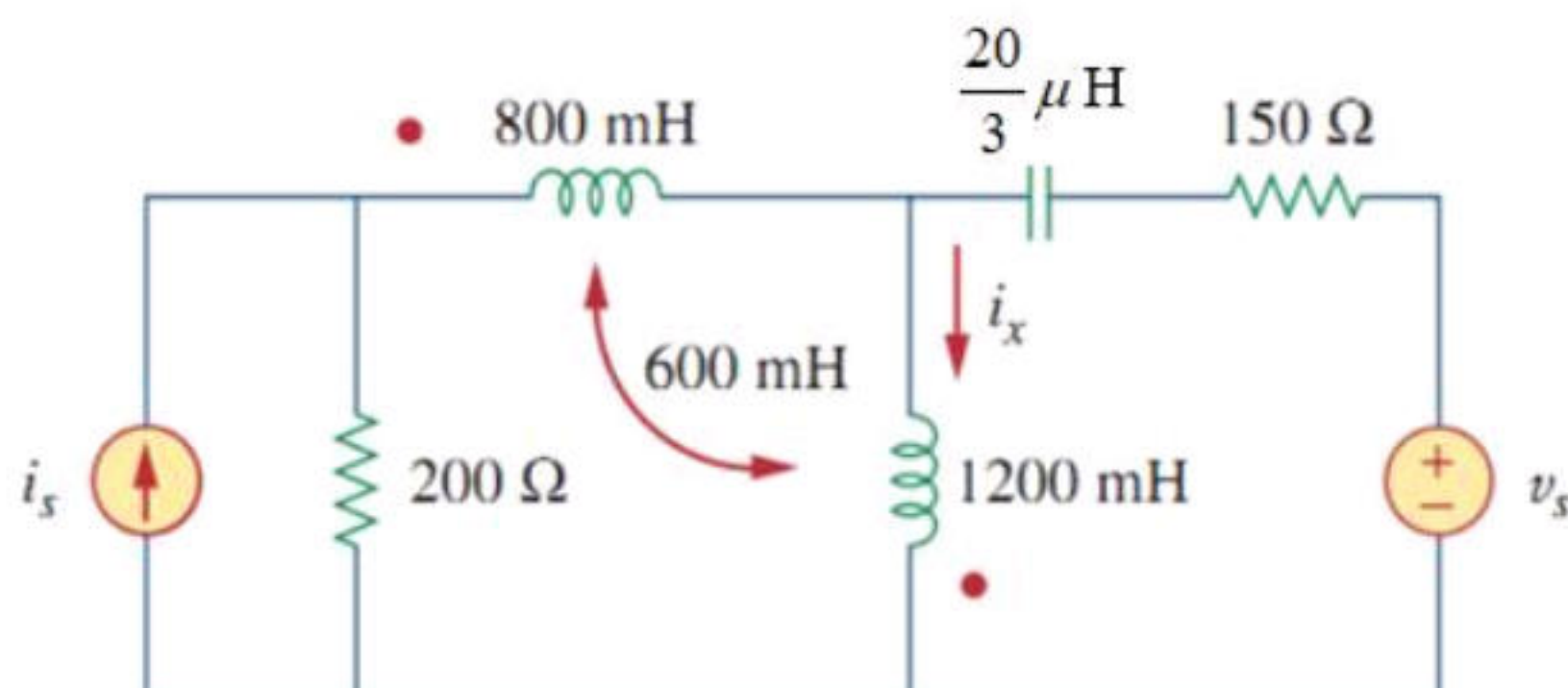4. The following circuit includes a mutual inductance $M=600\text{mH}$, and is in steady state. Given $i_s = 4\sin(600t)\text{A}$, $v_s = 100\cos(300t + 60^\circ)\text{V}$, calculate $i_x(t)$ in S.S.



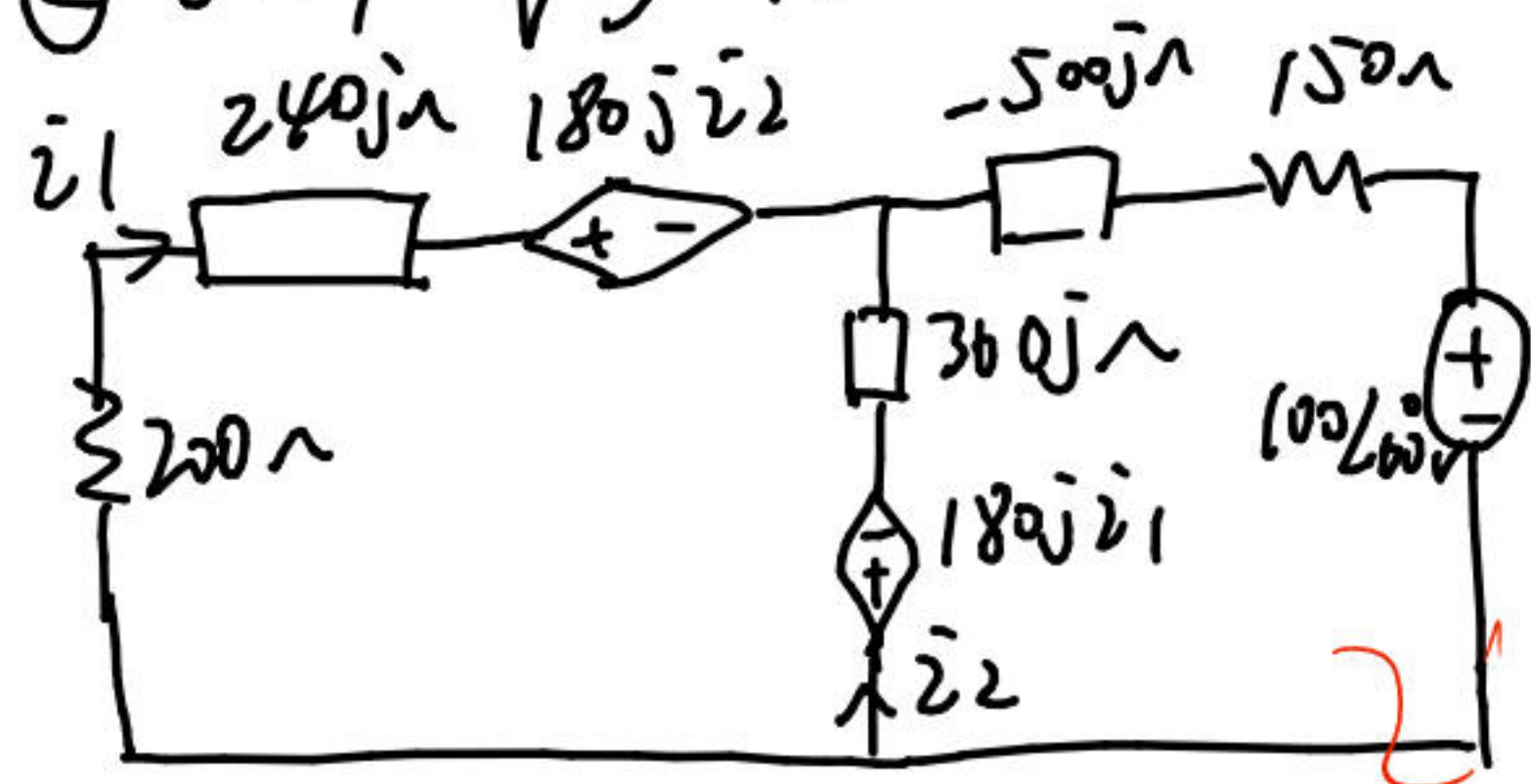② Only V_s is on $\omega = 300\text{ rad/s}$



$$Z_{L1} = 240j\Omega$$

$$Z_{L2} = 30j\Omega$$

$$Z_C = -500j\Omega$$

$$V_1 = 180j i_2$$

$$V_2 = 180j i_1$$

KVL:

$$\begin{cases} i_1 \cdot (R_1 + Z_{L1}) + V_1 + (i_1 + i_2)(Z_C + R_2) + V_s = 0 \\ i_2 \cdot Z_{L2} + V_2 + (i_1 + i_2)(Z_C + R_2) + V_s = 0 \end{cases}$$

$$\begin{cases} i_1 \cdot (200 + 240j) + 180j i_2 + (i_1 + i_2)(-500j + 150) + 100\angle 60^\circ = 0 \\ i_2 \cdot 30j + 180j i_1 + (i_1 + i_2)(-500j + 150) + 100\angle 60^\circ = 0 \end{cases}$$

$$\Rightarrow \begin{cases} i_1 = 0.187\angle -34.76^\circ \text{ A} \\ i_2 = 0.217\angle -108.06^\circ \text{ A} \end{cases}$$

Above all: $i_x(t) = 0.217\cos(300t + 71.94^\circ) + 0.833\cos(600t + 14.52^\circ) \text{ A}$