

Homework 5

Due date: Nov. 25th, 2021

Turn in your homework in class

Rules:

- Work on your own. Discussion is permissible, but extremely similar submissions will be judged as plagiarism.
- Please show all intermediate steps: a correct solution without an explanation will get zero credit.
- Please submit on time. No late submission will be accepted.
- Please prepare your submission in English only. No Chinese submission will be accepted.
- If needed, round the number to the nearest hundredths, i.e., rounding it to 2 decimal places.

1. (a) For the following pairs of sinusoids, determine which one leads and by how much.

(a) $v(t) = 10 \cos(4t - 60^\circ)$ and
 $i(t) = 4 \sin(4t + 50^\circ)$

(b) $v_1(t) = 4 \cos(377t + 10^\circ)$ and
 $v_2(t) = -20 \cos 377t$

(c) $x(t) = 13 \cos 2t + 5 \sin 2t$ and
 $y(t) = 15 \cos(2t - 11.8^\circ)$

- (b) Transform the following sinusoids into phasors:

(a) $-20 \cos(4t + 135^\circ)$ (b) $8 \sin(20t + 30^\circ)$

(c) $20 \cos(2t) + 15 \sin(2t)$


2. For the circuit below:

1) Calculate the equivalent impedance Z_{ab} ;


2) If $V_{ab} = 20 \sin(5t + 105^\circ)$,

i. Calculate current through the $10\ \Omega$ resistor, and indicate the reference direction in the circuit diagram;

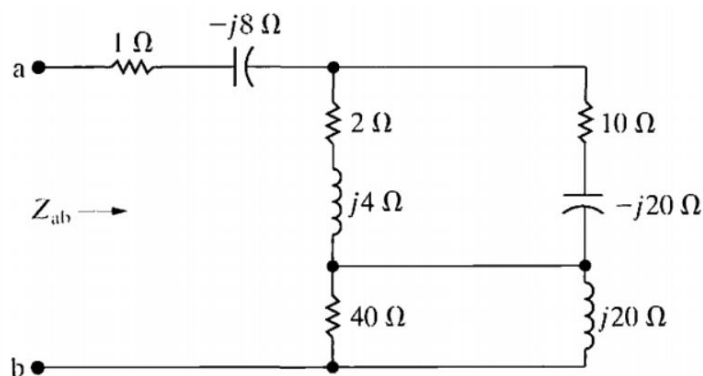ii. Calculate voltage over the $j20\ \Omega$ inductor and indicate the reference direction in the circuit diagram.



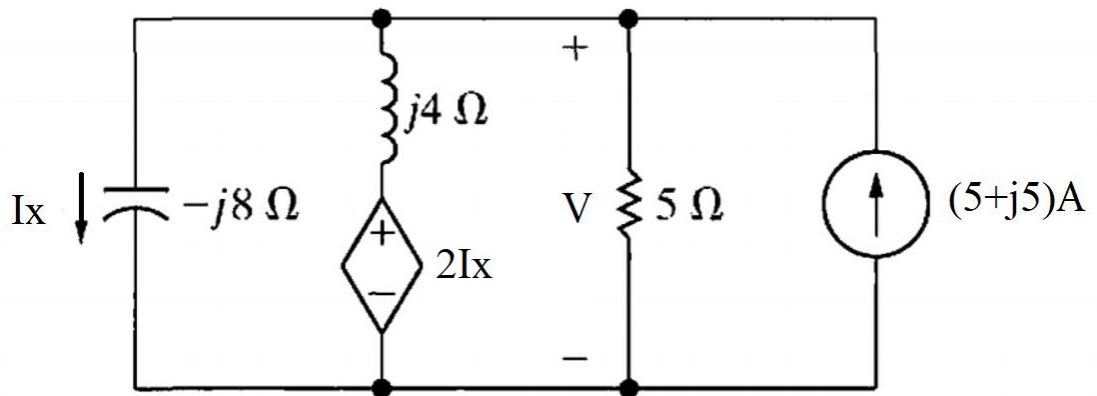3. For the circuit below, given $\omega = 2 \text{ rad/s}$
- 1) Use nodal analysis to find $I_x(t)$, $V(t)$
 - 2) Use mesh analysis to find $I_x(t)$, $V(t)$




4. For the circuit below:


$R=10\Omega$, $L1=10\text{mH}$, $L2=20\text{mH}$, $C=200\text{nF}$,

$V_1(t) = 10\sin(5t + 30^\circ)$, $V_2(t) = 4\cos(5t)$

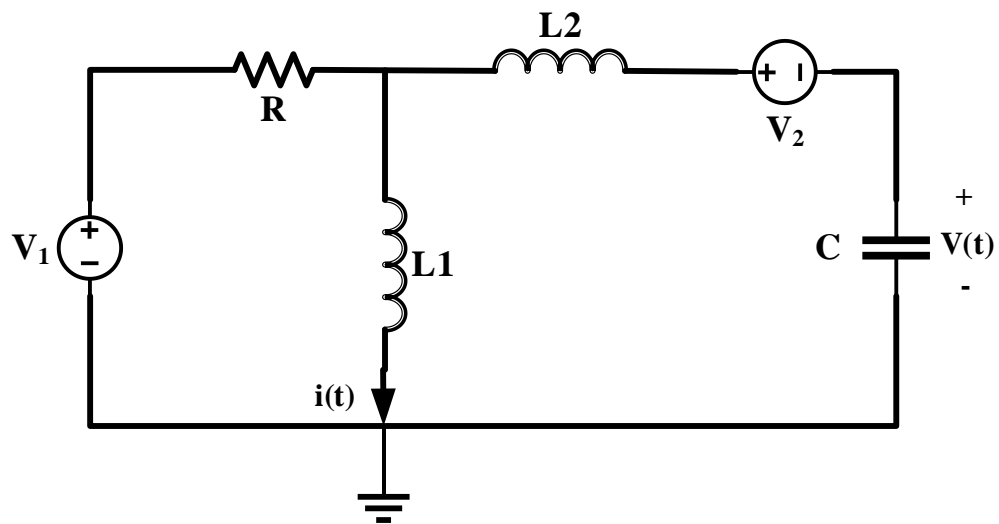
Use superposition theorem to solve the $i(t)$ and $V(t)$



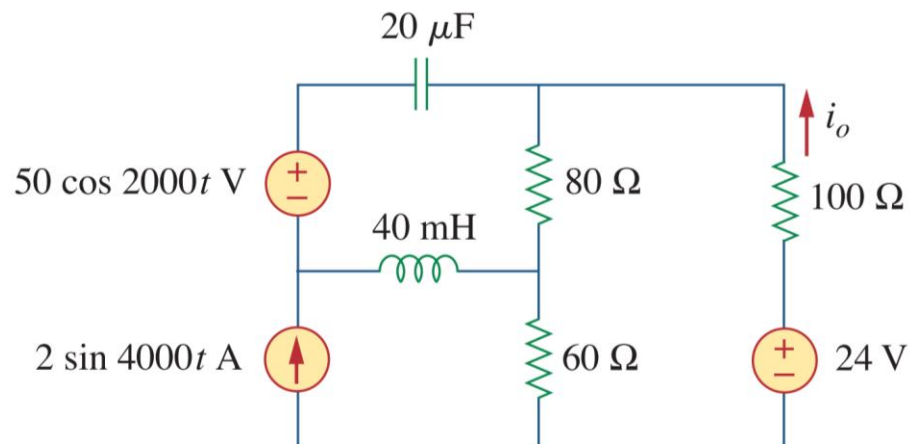5. Find $i_o(t)$ by using superposition method.



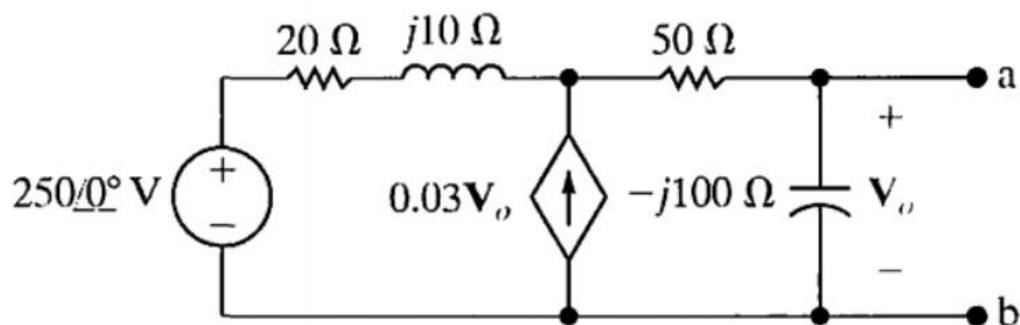6. For the circuit below. The circuit is working in sinusoidal, single frequency ($\omega = 2$ rad/s), and steady state.
- 1) Find the Thevenin AND Norton equivalent circuit at the terminals a and b.
 - 2) Consider an inductor $L=5\text{H}$ is connected to the terminal a and b. Find the current through L $i_L(t)$ and indicate the reference direction in the circuit diagram.



7. For the circuit below. Suppose v_s is a sinusoidal voltage source with the angular frequency ω . Suppose the Op-amp is working in the linear mode. Find the expression for v_o/v_s .

