

Homework 9 Solution

Due date:

Jun. 4th, 2018

Turn in your homework in class

1. Determine the resonant frequency of the circuit shown below.

Given that $R = 1\text{k}\Omega$, $L = 10\text{ mH}$, and $C = 10\text{nF}$.

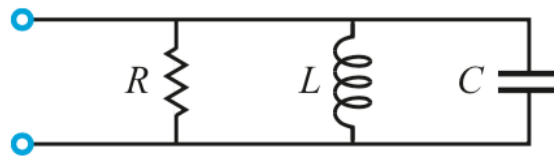


Fig.1

Solution:

$$\begin{aligned}
 \mathbf{Z}_i &= R \parallel (j\omega L) \parallel (-j/\omega C) \\
 &= R \parallel \left(\frac{L/C}{j(\omega L - \frac{1}{\omega C})} \right) \\
 &= R \parallel \left(\frac{-j\omega L}{\omega^2 LC - 1} \right) \\
 &= \left(\frac{-j\omega RL}{\omega^2 LC - 1} \right) \bigg/ \left(R - \frac{j\omega L}{\omega^2 LC - 1} \right) \\
 &= \frac{-j\omega RL}{\omega^2 LC - 1} \cdot \frac{\omega^2 LC - 1}{R(\omega^2 LC - 1) - j\omega L} \\
 &= \frac{-j\omega RL}{\omega^2 LC - 1} \cdot \frac{\omega^2 LC - 1}{R(\omega^2 LC - 1) - j\omega L} \\
 &= \frac{-j\omega RL}{R(\omega^2 LC - 1) - j\omega L} \cdot \frac{R(\omega^2 LC - 1) + j\omega L}{R(\omega^2 LC - 1) + j\omega L} \\
 &= \frac{\omega^2 RL^2 - j\omega R^2 L(\omega^2 LC - 1)}{R^2 L(\omega^2 LC - 1)^2 + \omega^2 L^2} .
 \end{aligned}$$

At resonance, \mathbf{Z}_i is purely real. This occurs when

$$\omega R^2 L(\omega^2 LC - 1) = 0,$$

which is satisfied when

$\omega = 0$ (trivial resonance), or

$$\omega = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{10^{-2} \times 10^{-8}}} = 10^5 \text{ rad/s}.$$

2. For the circuit shown below, determine the transform function $\mathbf{H} = \mathbf{V}_o/\mathbf{V}_i$, and determine the frequency ω at which \mathbf{H} is purely real.

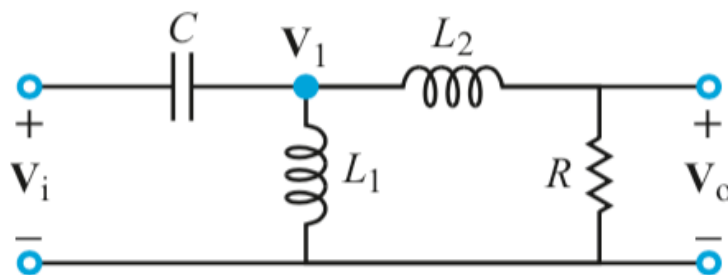


Fig.2

Solution:

(a) KCL at node \mathbf{V}_1 gives:

$$\frac{\mathbf{V}_1 - \mathbf{V}_i}{\mathbf{Z}_C} + \frac{\mathbf{V}_1}{\mathbf{Z}_{L_1}} + \frac{\mathbf{V}_1}{R + \mathbf{Z}_{L_2}} = 0,$$

where $\mathbf{Z}_C = 1/j\omega C$, $\mathbf{Z}_{L_1} = j\omega L_1$, and $\mathbf{Z}_{L_2} = j\omega L_2$.

Also, voltage division gives

$$\mathbf{V}_o = \frac{\mathbf{V}_1 R}{R + j\omega L_2}.$$

Solving for the transfer function gives

$$\mathbf{H} = \frac{\mathbf{V}_o}{\mathbf{V}_i} = \frac{-\omega^2 R L_1 C}{R(1 - \omega^2 L_1 C) + j\omega(L_1 + L_2 - \omega^2 L_1 L_2 C)}.$$

(b) We need to rationalize the expression for \mathbf{H} :

$$\begin{aligned} \mathbf{H} &= \frac{-\omega^2 R L_1 C}{R(1 - \omega^2 L_1 C) + j\omega(L_1 + L_2 - \omega^2 L_1 L_2 C)} \\ &\quad \times \frac{R(1 - \omega^2 L_1 C) - j\omega(L_1 + L_2 - \omega^2 L_1 L_2 C)}{R(1 - \omega^2 L_1 C) - j\omega(L_1 + L_2 - \omega^2 L_1 L_2 C)} \\ &= \frac{-\omega^2 R^2 L_1 C(1 - \omega^2 L_1 C) + j\omega^3 R L_1 C(L_1 + L_2 - \omega^2 L_1 L_2 C)}{R^2(1 - \omega^2 L_1 C)^2 + \omega^2(L_1 + L_2 - \omega^2 L_1 L_2 C)^2}. \end{aligned}$$

The imaginary part of \mathbf{H} is zero if $\omega = 0$ (trivial solution) or if

$$\omega_0 = \sqrt{\frac{L_1 + L_2}{L_1 L_2 C}}.$$

3. Generate Bode magnitude and phase plots for the following voltage transfer functions (with some necessary approximation for straight-line in drawing) (more space for drawing and enough annotation is necessary):

$$(a) \quad H(\omega) = \frac{4 \times 10^4 (60 + j6\omega)}{(4 + j2\omega)(100 + j2\omega)(400 + j4\omega)}$$

$$(b) \quad H(\omega) = \frac{(1 + j0.2\omega)^2 (100 + j2\omega)^2}{(j\omega)^3 (500 + j\omega)}$$

$$(c) \quad H(\omega) = \frac{8 \times 10^{-2} (10 + j10\omega)}{j\omega (16 - \omega^2 + j4\omega)}$$

$$(d) \quad H(\omega) = \frac{4 \times 10^4 \omega^2 (100 - \omega^2 + j50\omega)}{(5 + j5\omega)(200 + j2\omega)^3}$$

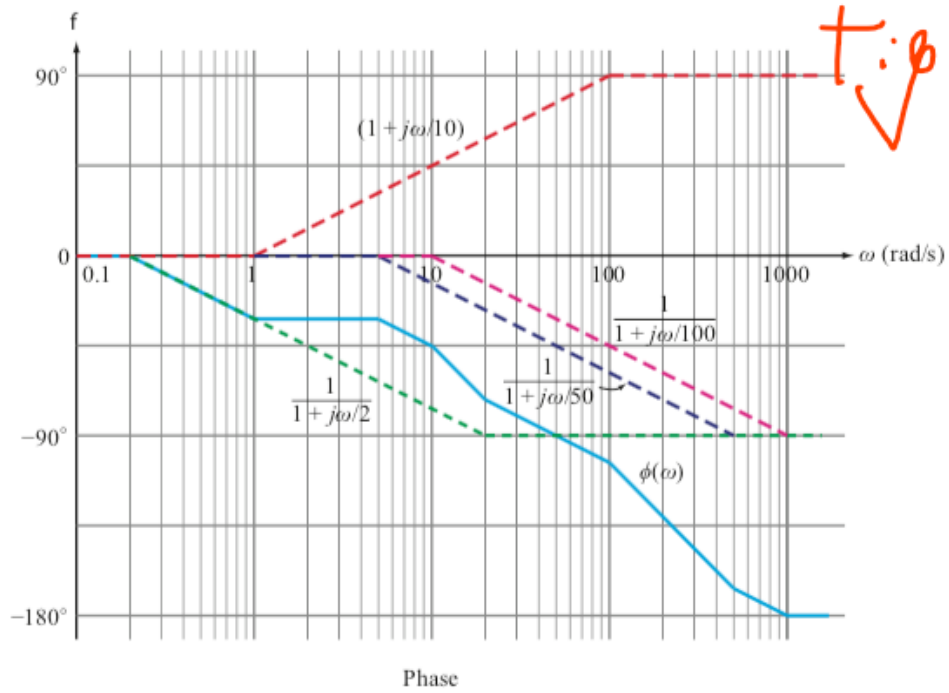
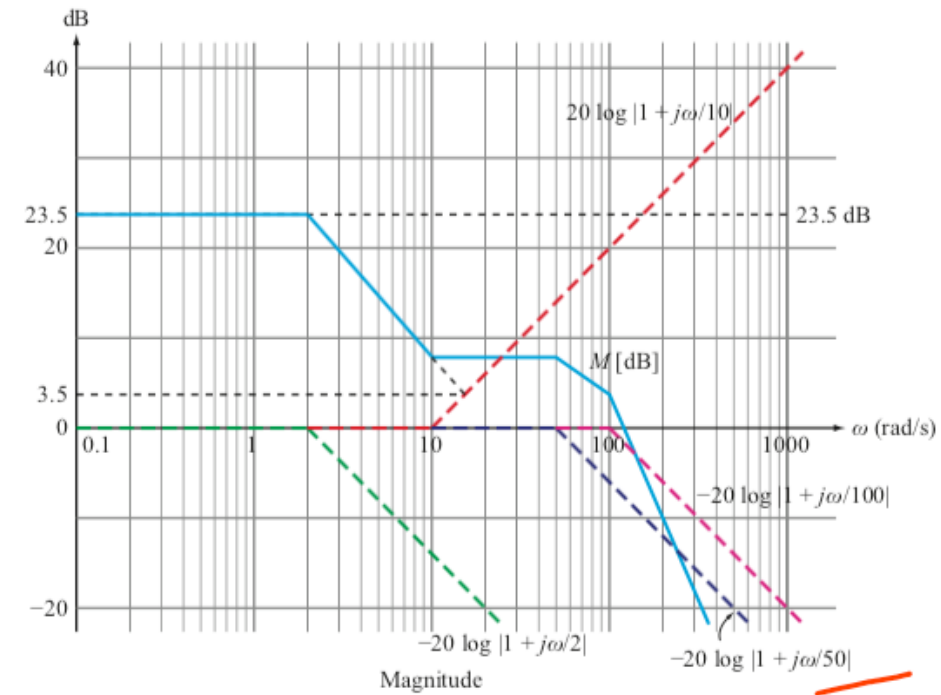


Fig. 1



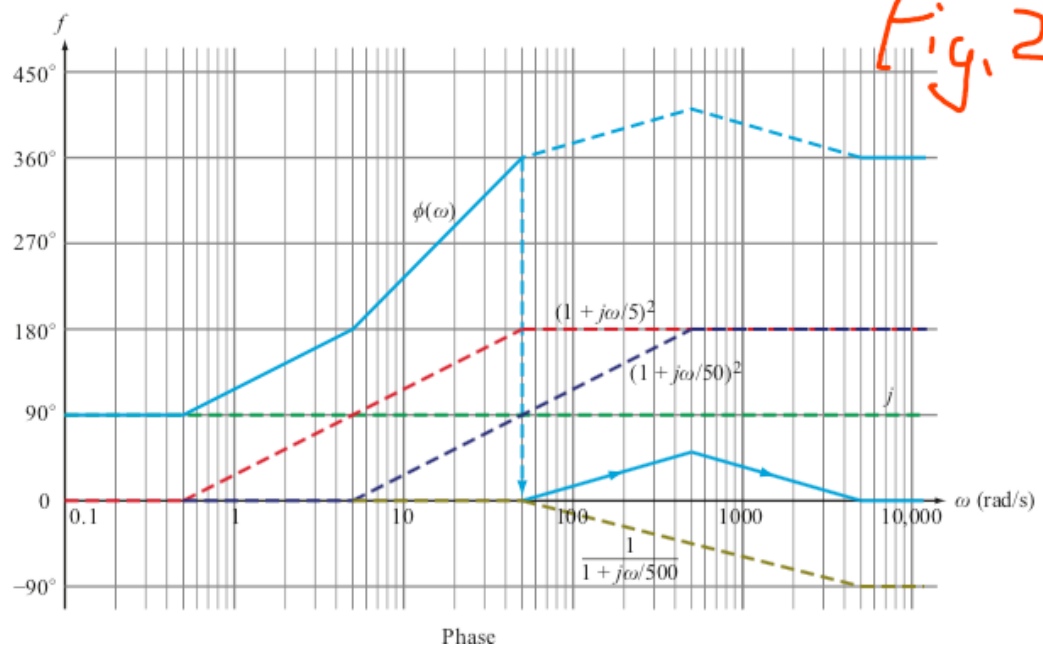
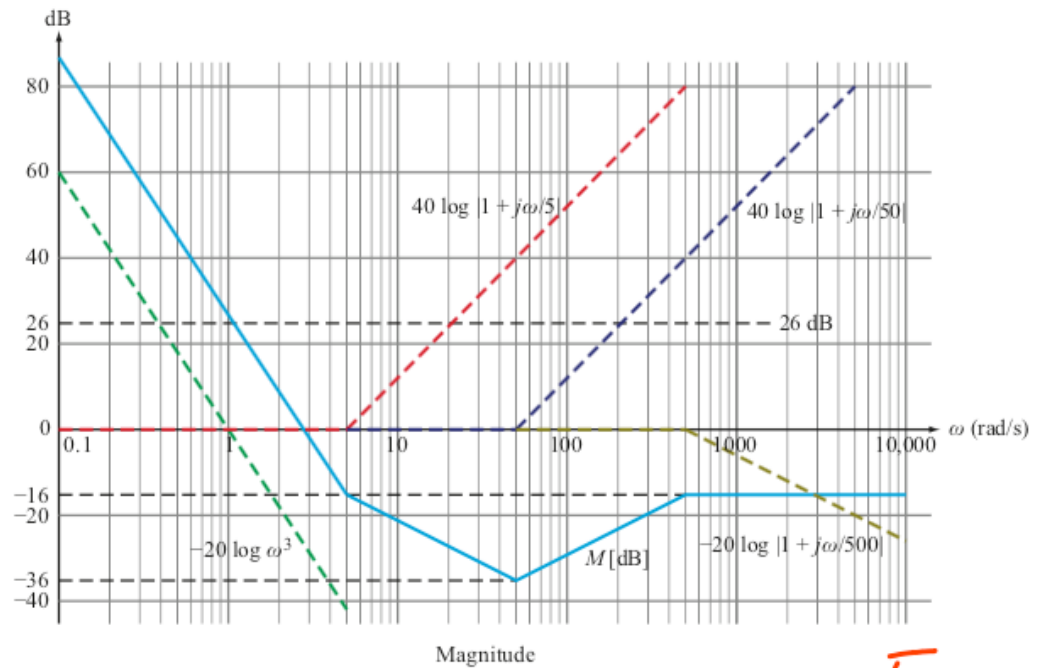


Fig. 2

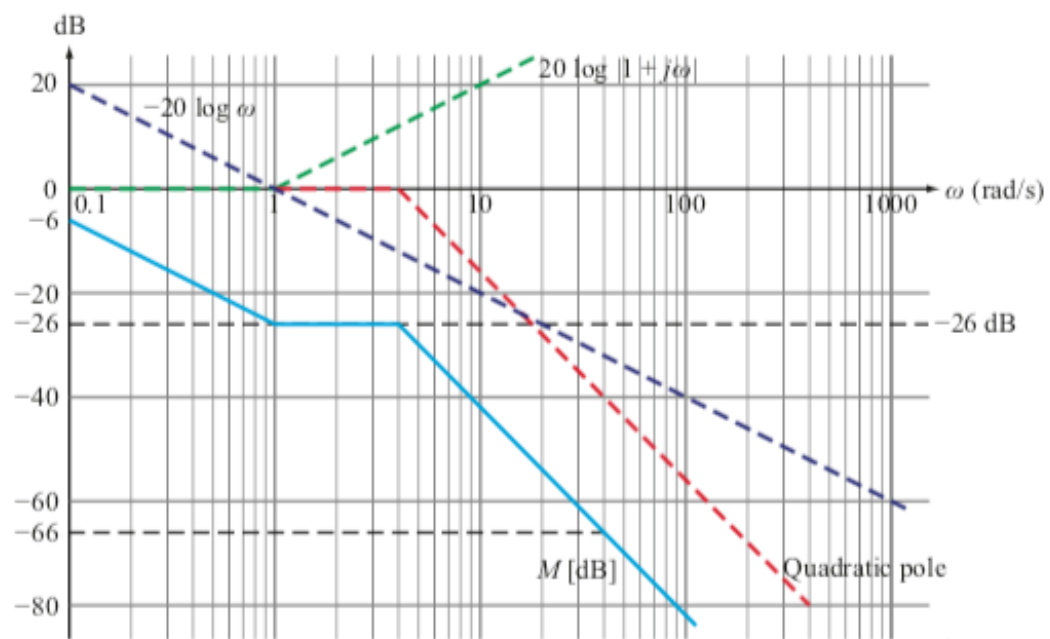


Magnitude

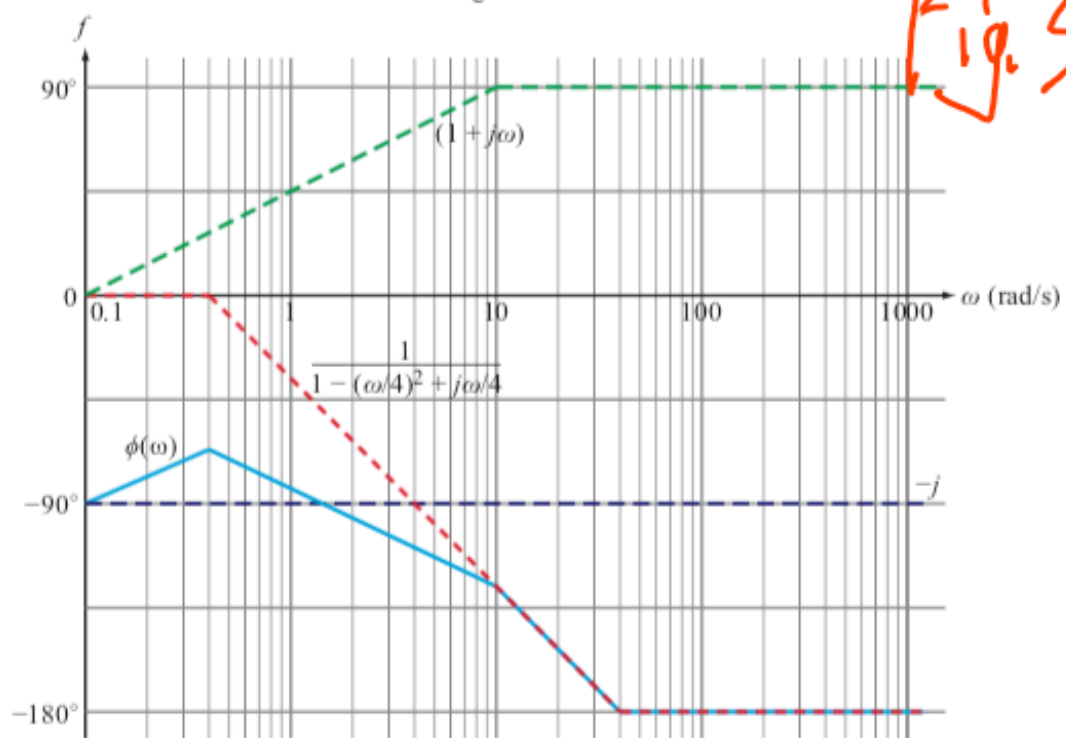

Phase

Fig. 3



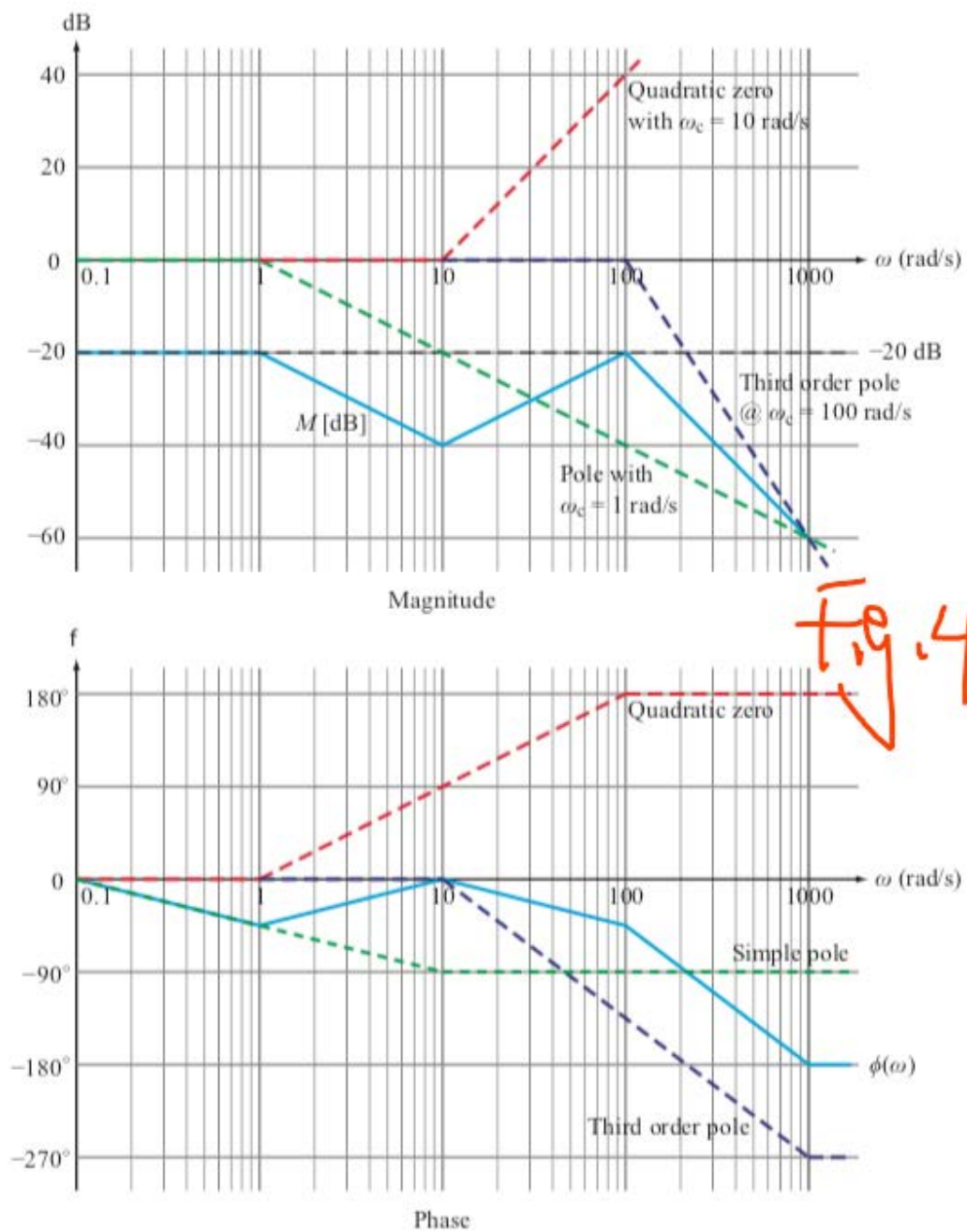


4. Determine the voltage transfer function $\mathbf{H}(\omega)$ corresponding to the Bode magnitude plot shown below and corresponding information provided below:

(a) The phase of $\mathbf{H}(\omega)$ is 90° at $\omega = 0$ in Fig 4.1.

(b) The phase of $\mathbf{H}(\omega)$ is -90° at $\omega = 0$ in Fig 4.2.

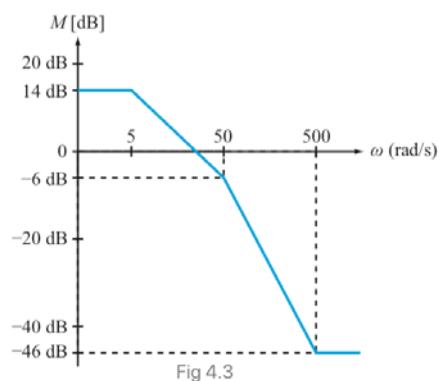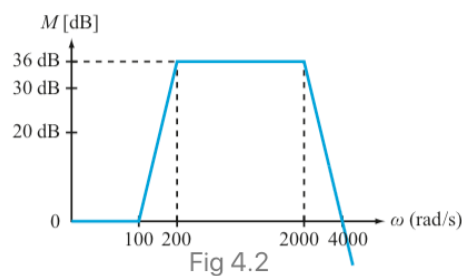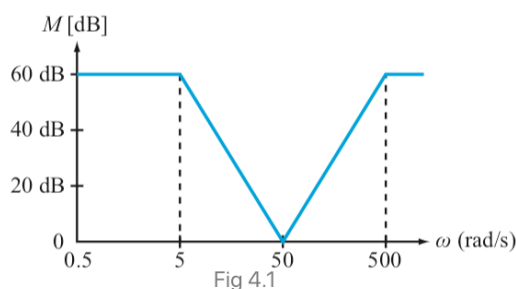(c) The phase of $\mathbf{H}(\omega)$ is 0° at $\omega = 0$ in Fig 4.3.



Solution: $\mathbf{H}(\omega)$ consists of:

(1) A constant term K whose dB value is 60 dB, or

$$K = 10^{60/20} = 1000.$$

(2) A simple pole of order 3 with $\omega_c = 5$ rad/s (slope = -60 dB/decade)

(3) A simple zero of order 6 with $\omega_c = 50$ rad/s (slope reverses from -60 dB/decade to $+60$ dB/decade)

(4) A simple pole of order 3 with $\omega_c = 500$ rad/s (slope changes to 0 dB at $\omega_c = 500$ rad/s).

Hence,

$$\mathbf{H}(\omega) = \frac{(j)^N 1000 (1 + j\omega/50)^6}{(1 + j\omega/5)^3 (1 + j\omega/500)^3} = \frac{j1000(50 + j\omega)^6}{(5 + j\omega)^3 (500 + j\omega)^3}.$$

Given that the phase of $\mathbf{H}(\omega)$ is 90° at $\omega = 0$, it follows that $N = 1$.

Solution: The transfer function consists of:

- (1) A simple zero of order N with $\omega_c = 100$ rad/s
- (2) A simple pole of order N with $\omega_c = 200$ rad/s
- (3) A simple pole of order N with $\omega_c = 2000$ rad/s
- (4) A factor $-j$ (phase at $\omega = 0$ is -90°).

Hence,

$$\mathbf{H}(\omega) = \frac{-j(1 + j\omega/100)^N}{(1 + j\omega/200)^N(1 + j\omega/2000)^N}.$$

To determine N , we note that the first term reaches 36 dB at $\omega = 200$ rad/s. That is, the straight-line approximation

$$20 \log |1 + \omega/100|^N \simeq 20N \log \left. \frac{\omega}{100} \right|_{\omega=200} = 36 \text{ dB},$$

or

$$20N \log 2 = 36 \text{ dB} \quad \implies \quad N = 6.$$

Hence,

$$\begin{aligned} \mathbf{H}(\omega) &= \frac{-j(200)^6(2000)^6(100 + j\omega)^6}{(100)^6(200 + j\omega)^6(2000 + j\omega)^6} \\ &= \frac{-j4.096 \times 10^{21}(100 + j\omega)^6}{(200 + j\omega)^6(2000 + j\omega)^6}. \end{aligned}$$

Solution: The transfer function consists of:

- (1) A constant K whose magnitude in dB is 14 dB.
- (2) A simple pole factor with $\omega_c = 5$ rad/s.
- (3) A simple pole factor with $\omega_c = 50$ rad/s (slope changes from -20 dB/decade to -40 dB/decade at $\omega = 50$ rad/s).
- (4) A simple zero of order 2 at $\omega_c = 500$ rad/s (slope changes to zero).

Hence,

$$K = 10^{14/20} = 5,$$

and

$$\begin{aligned} \mathbf{H}(\omega) &= \frac{5(1 + j\omega/500)^2}{(1 + j\omega/5)(1 + j\omega/50)} \\ &= \frac{(500 + j\omega)^2}{200(5 + j\omega)(50 + j\omega)}. \end{aligned}$$

(10分) 5. Determine the center frequency and bandwidth of the bandpass filters in Fig.5


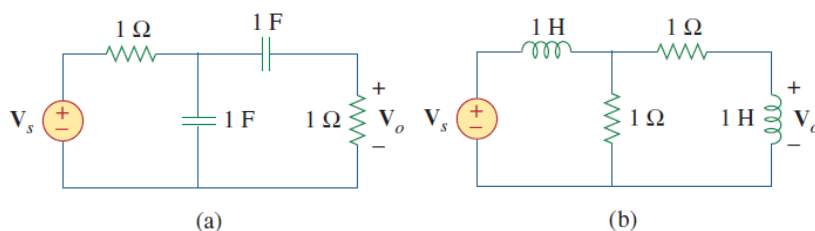


Figure 5

注：由于本周才学Laplace变换，
这道题按 $s=j\omega$ 计算，结果是等价的

Solution

(a) Consider the circuit below.

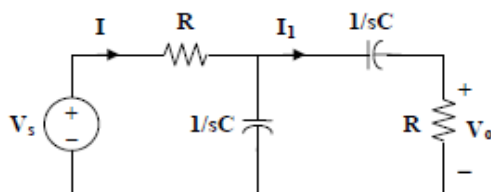

$$Z(s) = R + \frac{1}{sC} \parallel \left(R + \frac{1}{sC} \right) = R + \frac{\frac{1}{sC} \left(R + \frac{1}{sC} \right)}{R + \frac{2}{sC}}$$

$$Z(s) = R + \frac{1 + sRC}{sC(2 + sRC)}$$

$$Z(s) = \frac{1 + 3sRC + s^2 R^2 C^2}{sC(2 + sRC)} \quad 1 \text{分}$$

$$I = \frac{V_s}{Z}$$

$$I_1 = \frac{1/sC}{2/sC + R} I = \frac{V_s}{Z(2 + sRC)}$$

$$V_o = I_1 R = \frac{R V_s}{2 + sRC} \cdot \frac{sC(2 + sRC)}{1 + 3sRC + s^2 R^2 C^2}$$

$$H(s) = \frac{V_o}{V_s} = \frac{sRC}{1 + 3sRC + s^2 R^2 C^2}$$

$$H(s) = \frac{1}{3} \left[\frac{\frac{3}{RC} s}{s^2 + \frac{3}{RC} s + \frac{1}{R^2 C^2}} \right] \quad \text{或} \quad H(\omega) = \frac{R}{3R + j(\omega CR^2 - \frac{1}{\omega C})} \quad 2 \text{分}$$

$$\text{Thus, } \omega_0^2 = \frac{1}{R^2 C^2} \quad \text{or} \quad \omega_0 = \frac{1}{RC} = 1 \text{ rad/s} \quad 1 \text{分}$$

$$B = \frac{3}{RC} = 3 \text{ rad/s} \quad 1 \text{分}$$

每个结果无单位扣1分

(b) Similarly,

$$Z(s) = sL + R \parallel (R + sL) = sL + \frac{R(R + sL)}{2R + sL}$$

$$Z(s) = \frac{R^2 + 3sRL + s^2 L^2}{2R + sL} \quad 1 \text{分}$$

$$I = \frac{V_s}{Z}, \quad I_1 = \frac{R}{2R + sL} I = \frac{R V_s}{Z(2R + sL)}$$

$$V_o = I_1 \cdot sL = \frac{sLR V_s}{2R + sL} \cdot \frac{2R + sL}{R^2 + 3sRL + s^2 L^2}$$

$$H(s) = \frac{V_o}{V_s} = \frac{sRL}{R^2 + 3sRL + s^2 L^2} = \frac{\frac{1}{3} \left(\frac{3R}{L} s \right)}{s^2 + \frac{3R}{L} s + \frac{R^2}{L^2}} \quad 2 \text{分}$$

$$\text{Thus, } \omega_0 = \frac{R}{L} = 1 \text{ rad/s} \quad 1 \text{分} \quad \text{或} \quad H(s) = \frac{R}{3R + j(\omega L - \frac{R^2}{\omega L})}$$

$$B = \frac{3R}{L} = 3 \text{ rad/s} \quad 1 \text{分}$$

11分 6. For the op-amp circuit of Fig. 6:

- Obtain an expression for $H(\omega) = V_o/V_i$ in standard form.
- Generate spectral plots for the magnitude and phase of $H(\omega)$, given that $R_1 = R_2 = 100\Omega$, and $C_1 = 10\mu\text{F}$, $C_2 = 0.4\mu\text{F}$.
- What type of filter is it? What is its maximum gain?


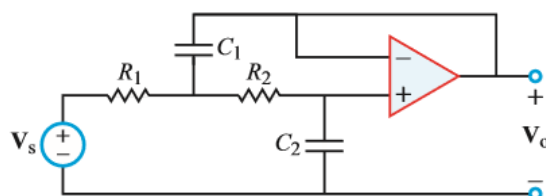


Figure 6

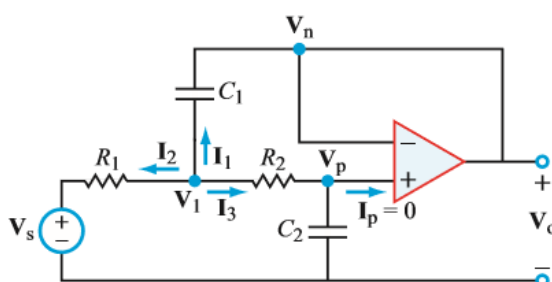

(a) At node V_1 :

$$I_1 + I_2 + I_3 = 0,$$

or equivalently

$$\frac{V_1 - V_o}{1/j\omega C_1} + \frac{V_1 - V_s}{R_1} + \frac{V_1}{R_2 + 1/j\omega C_2} = 0.$$

Also,

$$V_p = V_n = V_o,$$

and by voltage division

$$V_p = \frac{V_1/j\omega C_2}{R_2 + 1/j\omega C_2}. \quad 1\text{分}$$

Simultaneous solution leads to:

$$H(\omega) = \frac{V_o}{V_s} = \frac{1}{1 + j\omega(R_1 + R_2)C_2 + (j\omega\sqrt{R_1 R_2 C_1 C_2})^2}$$


$$= \frac{1}{1 + j2\xi\omega/\omega_c + (j\omega/\omega_c)^2}, \quad 2\text{分, 这一问没有标明数值, 写到这一步或上一步即可}$$

with


$$\omega_c = \frac{1}{\sqrt{R_1 R_2 C_1 C_2}} = \frac{1}{\sqrt{100 \times 100 \times 10^{-5} \times 0.4 \times 10^{-6}}} = 5000 \text{ rad/s},$$

$$\xi = \frac{(R_1 + R_2)C_2\omega_c}{2} = 100 \times 0.4 \times 10^{-6} \times 5000 = 0.2.$$

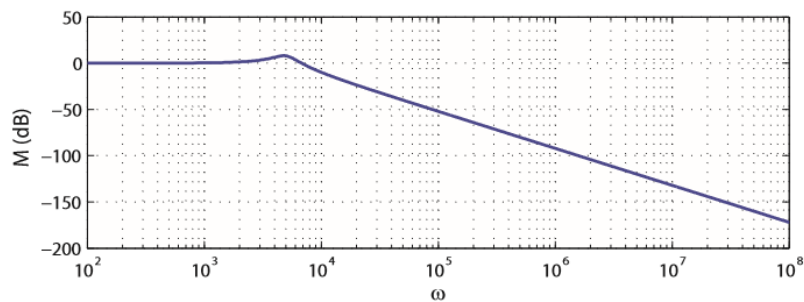(b) Spectral plots of the transfer function are shown in Fig. P9.39(b) and (c).



3分。趋势正确: 1分; 标出坐标轴
单位: 1分; 标出斜率: 1分

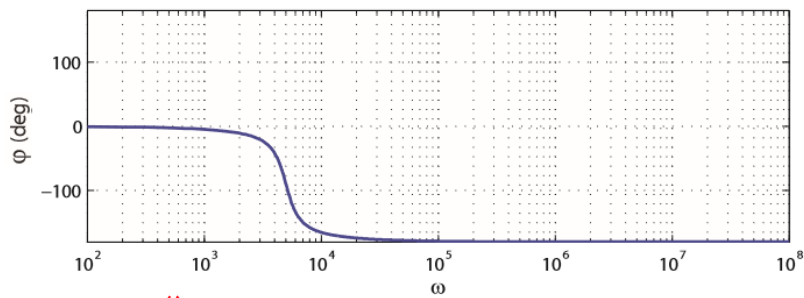

2分。趋势正确: 1分; 标出坐标轴
单位: 1分

1分

(c) This is a low pass filter with a slope of -40 dB/decade at frequencies much greater than $\omega_c = 5000$ rad/s. Maximum gain (at dc) is 0 dB.

1分

- 8分 7. Design the filter in Fig. 7 to meet the following requirements, given $R = 10\text{ k}\Omega$:
- It must attenuate a signal at 2 kHz by 3 dB compared with its value at 10 MHz.
 - It must provide a steady-state output of $v_o(t) = 10 \sin(2\pi \times 10^8 t + 180^\circ) \text{ V}$ for an input $v_s(t) = 10 \sin(2\pi \times 10^8 t) \text{ V}$.

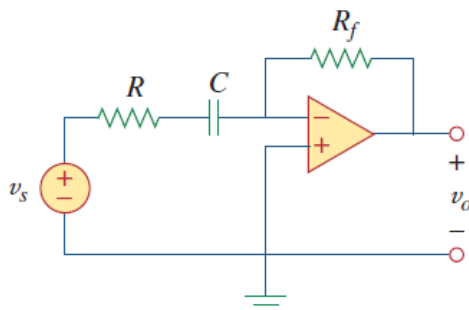


Figure 7

Solution

This is a highpass filter with $f_c = 2 \text{ kHz}$. 3分

$$\omega_c = 2\pi f_c = \frac{1}{RC}$$

$$RC = \frac{1}{2\pi f_c} = \frac{1}{4\pi \times 10^3}$$

10^8 Hz may be regarded as high frequency. Hence the high-frequency gain is

$$\frac{-R_f}{R} = \frac{-10}{4} \quad \text{or} \quad R_f = 2.5R$$

2分, 比值应为-1

If we let $R = 10 \text{ k}\Omega$, then $R_f = 25 \text{ k}\Omega$, and $C = \frac{1}{4000\pi \times 10^4} = 7.96 \text{ nF}$. 1分, $R_f=R=10\text{k}\Omega$ 2分

虽然是设计题，但参数R给定，答案基本固定，如有不同于参考答案的参数设计，酌情给分

11分 8. In the circuit shown below, find current I_o .


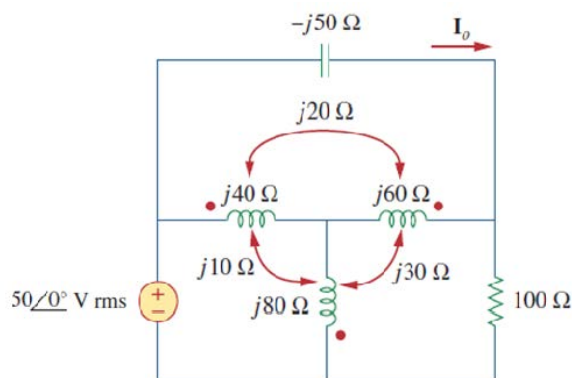


Figure 8

Solution:

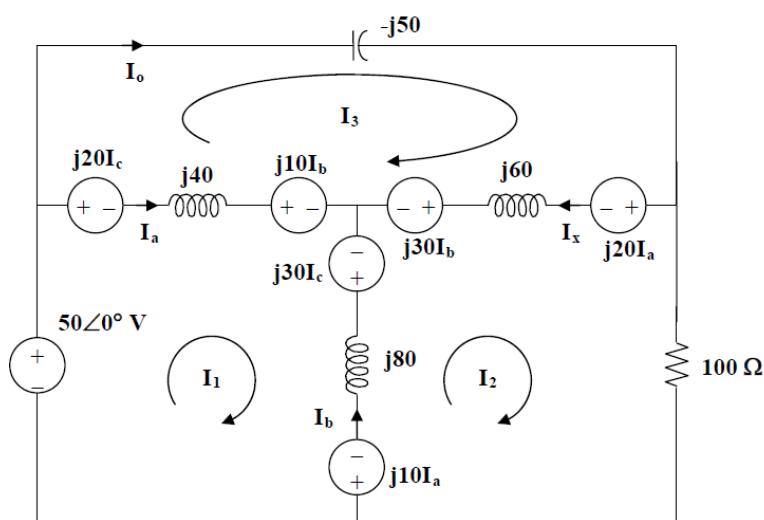

Note the following,

$$I_a = I_1 - I_3$$

$$I_b = I_2 - I_1$$

$$I_c = I_3 - I_2$$

And $I_o = I_3$.

Loop # 1,

$$1. -50 + j20(I_3 - I_2) + j40(I_1 - I_3) + j10(I_2 - I_1) - j30(I_3 - I_2) + j80(I_1 - I_2) - j10(I_1 - I_3) = 0$$

$$2. j100I_1 - j60I_2 - j40I_3 = 50 \quad 3分$$

Multiplying everything by $(1/j10)$ yields :

$$10I_1 - 6I_2 - 4I_3 = -j5$$

Loop # 2,

$$j10(I_1 - I_3) + j80(I_2 - I_1) + j30(I_3 - I_2) - j30(I_2 - I_1) + j60(I_2 - I_3) - j20(I_1 - I_3) + 100I_2 = 0$$

$$-j60I_1 + (100 + j80) I_2 - j20I_3 = 0 \quad (2) \quad \text{3分}$$

Loop # 3,

$$-j50I_3 + j20(I_1 - I_3) + j60(I_3 - I_2) + j30(I_2 - I_1) - j10(I_2 - I_1) + j40(I_3 - I_1) - j20(I_3 - I_2) = 0$$

$$-j40I_1 - j20I_2 + j10I_3 = 0 \quad \text{3分}$$

Multiplying by (1/j10) yields,

$$-4I_1 - 2I_2 + I_3 = 0 \quad (3)$$

Multiplying (2) by (1/j20) yields

$$-3I_1 + (4 - j5) I_2 - I_3 = 0 \quad (4)$$

Multiplying (3) by (1/4) yields

$$-I_1 - 0.5I_2 - 0.25I_3 = 0 \quad (5)$$

Multiplying (4) by (-1/3) yields

$$I_1 - ((4/3) - j(5/3)) I_2 + (1/3) I_3 = -j0.5 \quad (7)$$

Multiplying [(6)+(5)] by 12 yields

$$(-22 + j20) I_2 + 7I_3 = 0 \quad (8)$$

Multiplying [(5)+(7)] by 20 yields

$$-22I_2 - 3I_3 = -j10 \quad (9)$$

(8) leads to

$$I_2 = -7I_3 / (-22 + j20) = 0.2355 \angle 42.3^\circ = (0.17418 + j0.15849) I_3 \quad (10)$$

(9) leads to

$I_3 = (j10 - 22I_2)/3$, substituting (1) into this equation produces,

$$I_3 = j3.333 + (-1.2273 - j1.1623) I_3$$

So $I_3 = I_0 = 1.3040 \angle 63^\circ \text{ amp.}$ 2分，中间过程酌情给分

10分

Electric Circuit, Spring 2018

Homework 9

Due: Jun. 4th

- 10分 9. In the ideal transformer circuit shown below, determine the average power delivered to the load (the $20 - j40\Omega$ resistance).

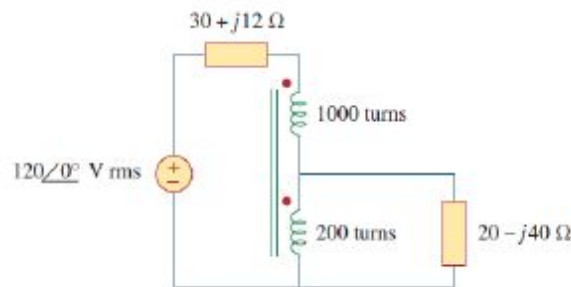


Figure 9

Solution

$$I_1/I_2 = N_2/(N_1 + N_2) = 200/1200 = 1/6, \text{ or } I_1 = I_2/6 \quad \text{2分} \quad (1)$$

$$v_1/v_2 = (N_1 + N_2)/N_1 = 6, \text{ or } v_1 = 6v_2 \quad \text{2分} \quad (2)$$

$$\text{For the primary loop, } 120 = (30 + j12)I_1 + v_1 \quad \text{2分} \quad (3)$$

$$\text{For the secondary loop, } v_2 = (20 - j40)I_2 \quad \text{1分} \quad (4)$$

$$\text{Substituting (1) and (2) into (3),} \quad \text{1分} \quad (4)$$

$$120 = (30 + j12)(I_2/6) + 6v_2$$

and substituting (4) into this yields

~~$$120 = (40 - j38)I_2 \text{ or } I_2 = 1.935 \angle 37.79^\circ \quad \text{1分}$$~~

~~$$p = |I_2|^2(20) = 7.49 \text{ watt} \quad \text{2分, 无单位扣1分}$$~~

$$120 = (125 - j238)I_2 \quad \text{1分}$$

$$3.985W$$

2分, 无单位扣1分

$$I_2 = 0.446 \angle 63^\circ$$