

Homework 1


Due date: Oct. 9th, 2021

Turn in your homework in class


Rules:

- Work on your own. Discussion is permissible, but extremely similar submissions will be judged as plagiarism.
- Please show all intermediate steps: a correct solution without an explanation will get zero credit.
- Please submit on time. No late submission will be accepted.
- Please prepare your submission in English only. No Chinese submission will be accepted.
- If needed, round the number to the nearest hundredths, i.e., rounding it to 2 decimal places.

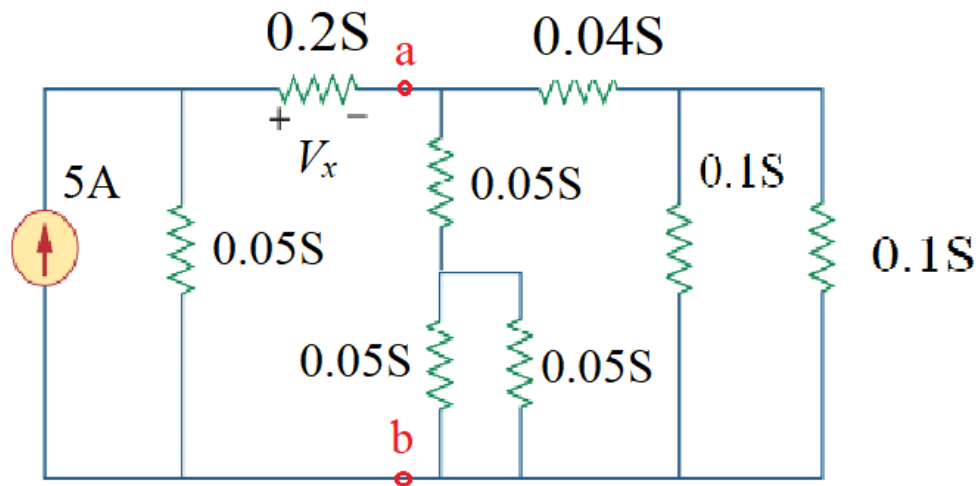
1. In this task you are going to solve circuits with multiple resistors. It will be helpful if you can properly simplify the circuit using correct methods.
- 1.1 For the circuit below, find the equivalent resistance at the right part of the node **a** and **b** and calculate the V_x .



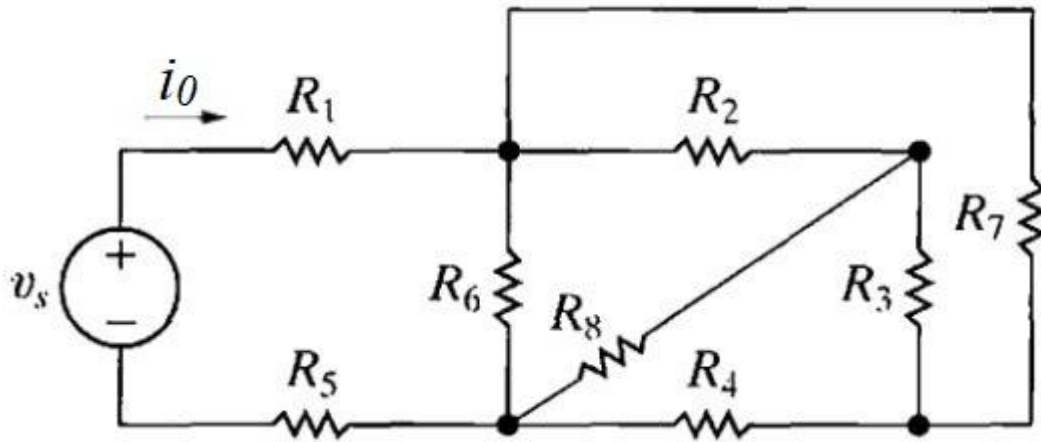
1.2 For the circuit below, where $R_1=3\Omega$, $R_2=20\Omega$, $R_3=10\Omega$, $R_4=R_8=4\Omega$, $R_5=6\Omega$, $R_6=36\Omega$, $R_7=20\Omega$, $V_s=20V$, find i_0 .



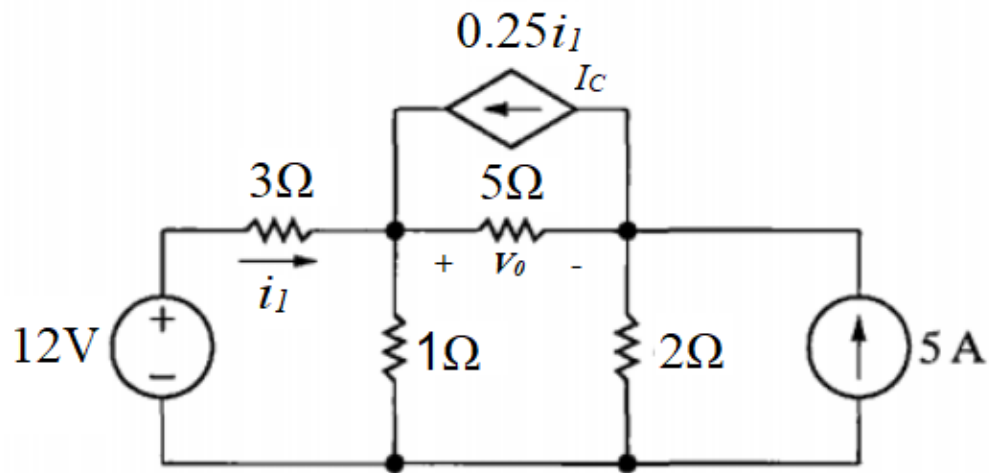
2. For the circuit below.
- 2.1 Apply nodal analysis to find i_1 , V_0 .
- 2.2 Calculate the power on the controlled source I_C .
- 2.3 Determine whether the controlled source I_C dissipates power or releases power.



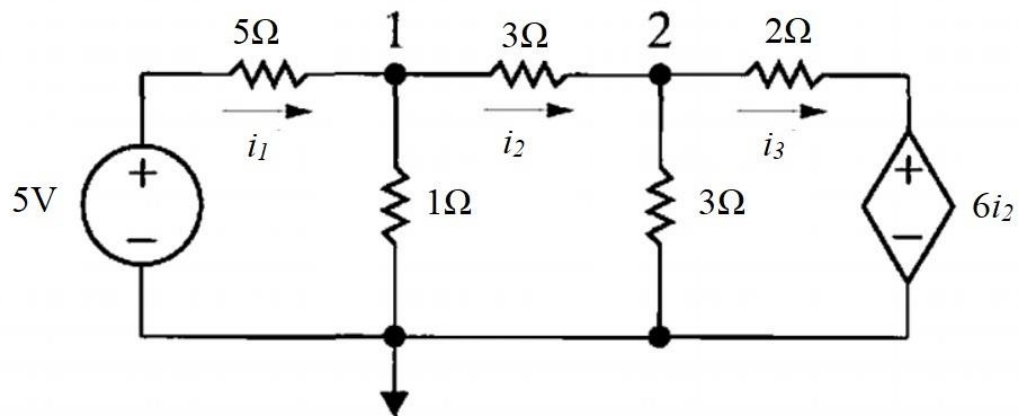3. For the circuit below, apply mesh analysis to find i_1 , i_2 , i_3 .



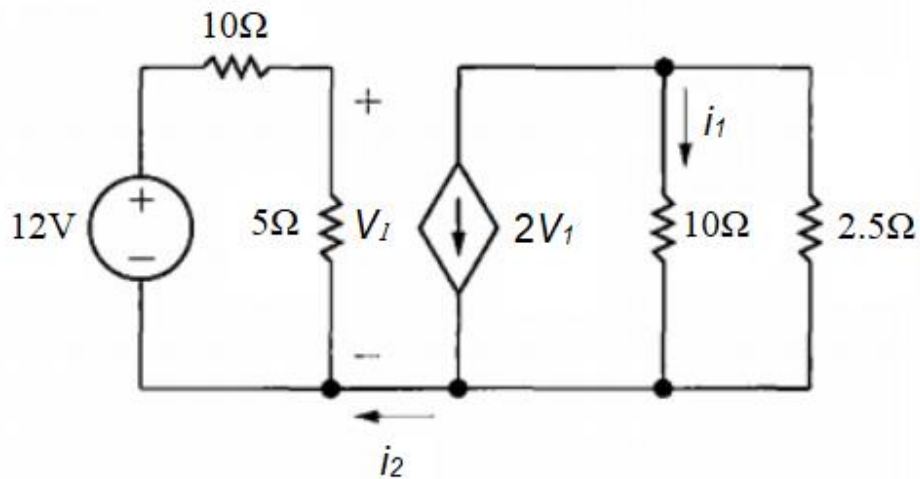4. For the circuit below, apply either nodal or mesh method to find V_1 , i_1 , i_2 .



5. For the circuit below,
- 5.1 apply nodal analysis method to find V_a , V_b .
 - 5.2 apply mesh analysis method to find V_a , V_b .

