

Homework 9

Due date:

Jun 4th, 2018

Turn in your homework in class

Rules:

- Work on your own. Discussion is permissible, but extremely similar submissions will be judged as plagiarism.
- Please show all intermediate steps: a correct solution without an explanation will get zero credit.
- Please submit on time. No late submission will be accepted.
- Please prepare your submission in English only. No Chinese submission will be accepted.

1. Determine the resonant frequency of the circuit shown below.

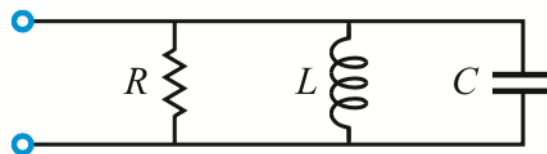
Given that $R = 1\text{k}\Omega$, $L = 10\text{ mH}$, and $C = 10\text{nF}$.

Figure 1

2. For the circuit shown below, determine the transform function $\mathbf{H}(\omega) = \mathbf{V}_o/\mathbf{V}_i$, and determine the frequency ω at which $\mathbf{H}(\omega)$ is purely real.

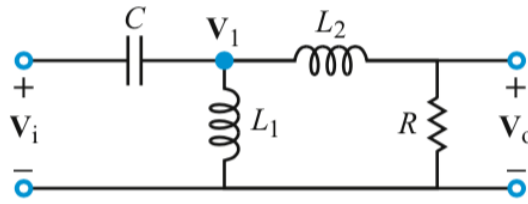


Figure 2

3. Generate Bode magnitude and phase plots for the following voltage transfer functions (with some necessary approximation for straight-line in drawing)
(more space for drawing and enough annotation is necessary):

$$(a) \mathbf{H}(\omega) = \frac{4 \times 10^4 (60 + j6\omega)}{(4 + j2\omega)(100 + j2\omega)(400 + j4\omega)}$$

$$(b) \mathbf{H}(\omega) = \frac{(1 + j0.2\omega)^2 (100 + j2\omega)^2}{(j\omega)^3 (500 + j\omega)}$$

$$(c) \mathbf{H}(\omega) = \frac{8 \times 10^{-2} (10 + j10\omega)}{j\omega (16 - \omega^2 + j4\omega)}$$




$$(d) \mathbf{H}(\omega) = \frac{4 \times 10^4 \omega^2 (100 - \omega^2 + j50\omega)}{(5 + j5\omega)(200 + j2\omega)^3}$$

4. Determine the voltage transfer function $\mathbf{H}(\omega)$ corresponding to the Bode magnitude plot shown below and corresponding information provided below:

(a) The phase of $\mathbf{H}(\omega)$ is 90° at $\omega = 0$ in Fig 4.1.

(b) The phase of $\mathbf{H}(\omega)$ is -90° at $\omega = 0$ in Fig 4.2.

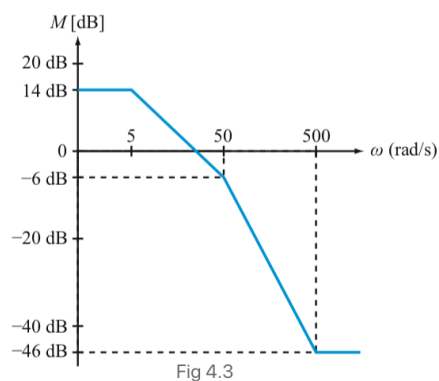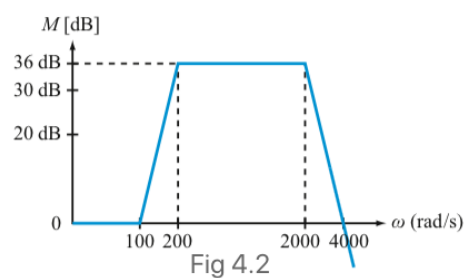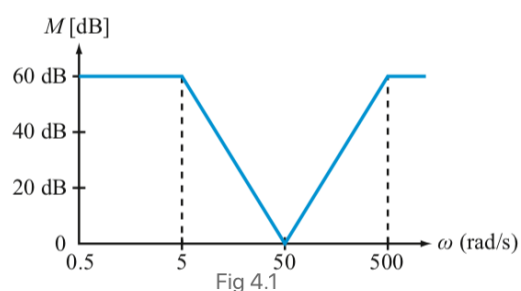(c) The phase of $\mathbf{H}(\omega)$ is 0° at $\omega = 0$ in Fig 4.3.



5. Determine the center frequency and bandwidth of the bandpass filters in Fig.5

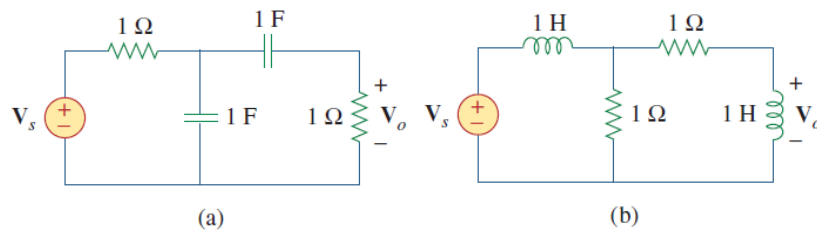


Figure 5

6. For the op-amp circuit of Fig. 6:
- (a) Obtain an expression for $\mathbf{H}(\omega) = \mathbf{V}_o/\mathbf{V}_s$ in standard form.
 - (b) Generate spectral plots for the magnitude and phase of $\mathbf{H}(\omega)$, given that $R_1 = R_2 = 100\Omega$, and $C_1 = 10\mu\text{F}$, $C_2 = 0.4\mu\text{F}$.
 - (c) What type of filter is it? What is its maximum gain?

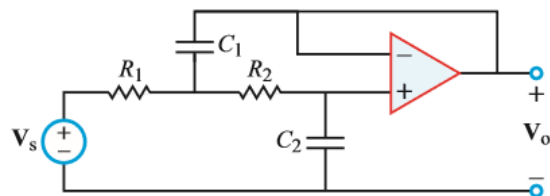
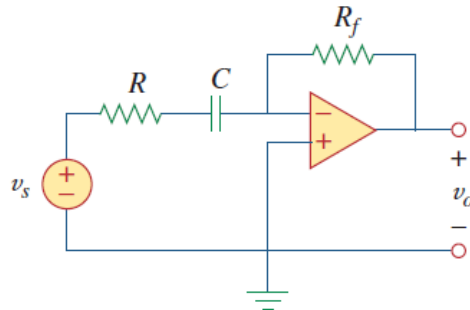


Figure 6

7. Design the filter in Fig. 7 to meet the following requirements, given $R = 10\text{k}\ \Omega$:
- It must attenuate a signal at 2 kHz by 3 dB compared with its value at 10 MHz.
 - It must provide a steady-state output of $v_o(t) = 10 \sin(2\pi \times 10^8 t + 180^\circ)\text{V}$ for an input $v_s(t) = 10 \sin(2\pi \times 10^8 t)\text{V}$.

**Figure 7**

8. In the circuit shown below, find current \mathbf{I}_o .

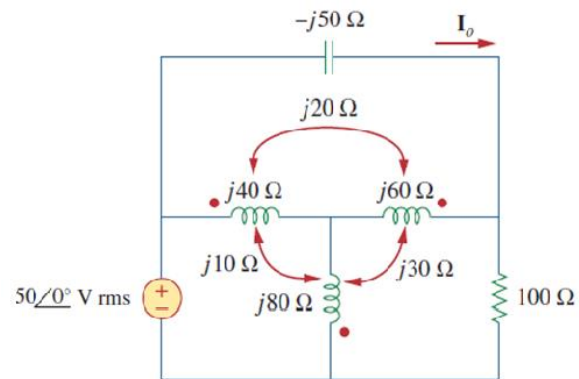


Figure 8

9. In the ideal transformer circuit shown below, determine the average power delivered to the load (the $20 - j40\Omega$ resistance).

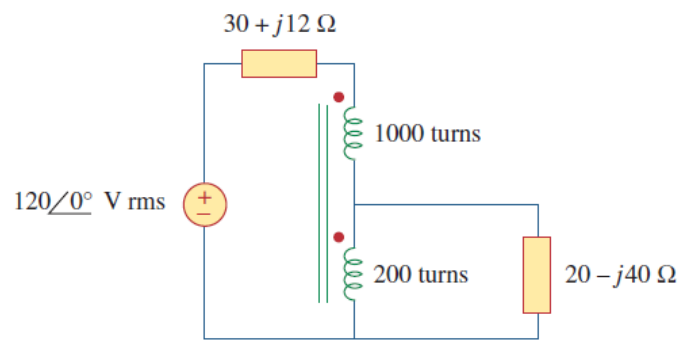


Figure 9