

**Problem 1 (20 points)**

You must show your detailed work to get full credit.

For the Wheatstone bridge circuit shown in Fig.1, solve the following problems:

- (a) Express  $I_a$ , the reading on the ammeter, as a function of all the circuit elements  $R_1$ ,  $R_2$ ,  $R_3$ ,  $R_x$ ,  $R_a$  and  $V_0$ .
- (b) If  $R_1 = 1\Omega$ ,  $R_2 = 2\Omega$ , and  $R_x = 3\Omega$ , to what value should  $R_3$  be adjusted so as to achieve a balanced condition, that is,  $I_a = 0$ ?
- (c) Further, if  $V_0 = 6V$ ,  $R_a = 0.1\Omega$ , and  $R_x$  were then to deviate by a small amount to  $R_x = 3.01\Omega$ , what would be the reading on the ammeter?

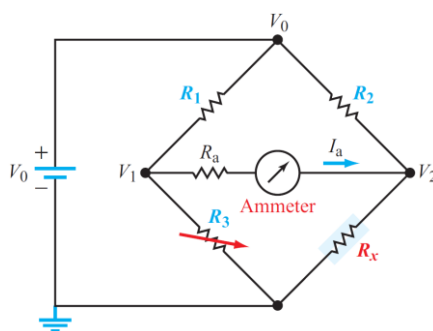


Fig. 1 for Problem 1.

**Problem 2 (15 points)**

You must show your detailed work to get full credit.

The circuit shown in Fig. 2 contains a variable load  $R_L$ .

- (a) Choose  $R_s$  so that  $I_L$  never exceeds 4mA, regardless of the value of  $R_L$ .
- (b) Given that choice, what is the maximum power that  $R_L$  can extract from the circuit?

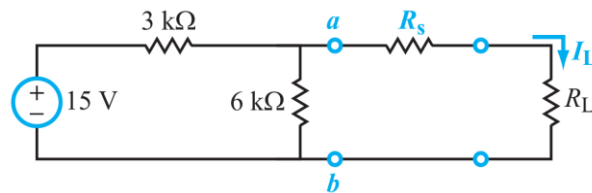


Fig. 2 for Problem 2.

**Problem 3 (20 points)**

You must show your detailed work to get full credit.

For the circuit shown in Fig. 3, assume the op amp is ideal. Given  $v_{in} = A u(t)$ ,  $A = 6V$ ,  $R_1 = 10\text{ k}\Omega$ ,  $R_2 = 5\text{ k}\Omega$ ,  $R_f = 50\text{ k}\Omega$ , and  $C_1 = C_2 = 1\text{ }\mu F$ , determine  $v_{out}(t)$  for  $t \geq 0$ .

Hint: There is no energy stored in the two capacitors at time  $t = 0$ .

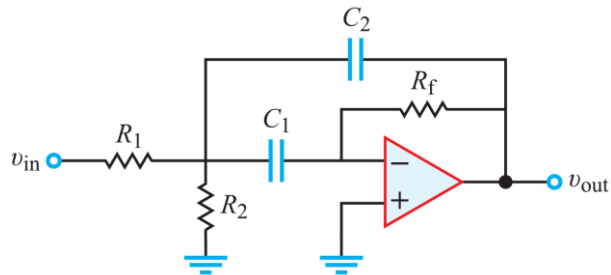


Fig. 3 for Problem 3.

**Problem 4 (15 points)**

You must show your detailed work to get full credit.

Determine the amount of average power delivered to  $R_L$  in the circuit shown in Fig. 4. Assume that the op amp is ideal and  $v_{in}(t) = 0.5 \cos 2000t$  V,  $R_1 = 1 \text{ k}\Omega$ ,  $R_2 = 10 \text{ k}\Omega$ ,  $C = 0.1 \text{ }\mu\text{F}$ ,  $R_L = 1 \text{ k}\Omega$  and  $L = 0.2 \text{ H}$ .

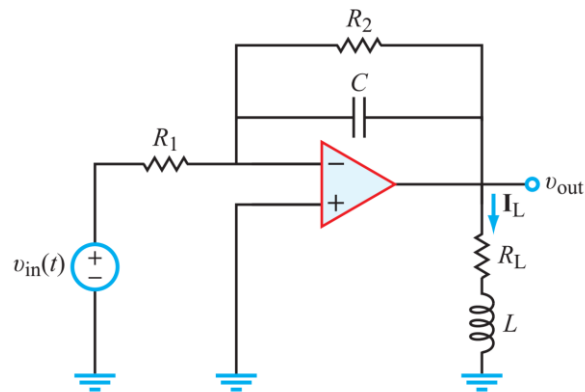


Fig. 4 for Problem 4.

**Problem 5 (15 points)**

You must show your detailed work to get full credit.

For the circuit shown in Fig. 5,

- Find the steady-state expressions for the currents  $i_g$  and  $i_L$  when  $v_g = 168 \cos 800t$  V.
- Find the coefficient of coupling  $k = \frac{M}{\sqrt{L_1 L_2}}$ .
- Find the total energy stored in the magnetically coupled coils at time  $t = 1250\pi$   $\mu$ s.

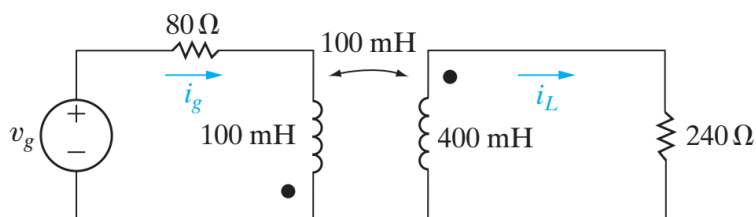


Fig. 5 for Problem 5.

**Problem 6 (15 points)**

You must show your detailed work to get full credit.

For the series RLC circuit of Fig. 6,  $R = 5\ \Omega$ ,  $L = 20\text{ mH}$ ,  $C = 0.5\ \mu\text{F}$ .

- (a) Obtain an expression for the transfer function  $H(\omega) = V_R/V_s$ .
- (b) What are the values of the resonant frequency  $\omega_0$  and quality factor  $Q$ ?
- (c) What are the values of half-power frequencies  $\omega_{c1}$  and  $\omega_{c2}$ ?
- (d) Is it possible to double the magnitude of  $Q$  by changing the values of  $L$  and/or  $C$ , while keeping  $\omega_0$  and  $R$  unchanged? If yes, propose such values, and if no, explain why.

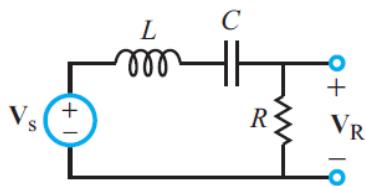


Fig. 6 for Problem 6.